

# Interview Questions

HOME Interview Questions MCQs \*LAB VIVA CLASS NOTES SEMINAR TOPICS  
ONLINE TEST GATE CAT Internship ABOUT US Privacy Policy

[Home](#) » [Three-Phase Systems in Power Applications Online Test](#)  
» **Three-Phase Systems in Power Applications Online Test – Multiple Choice Questions and Answers**

## Three-Phase Systems in Power Applications Online Test – Multiple Choice Questions and Answers

**THE LARGEST RANGE**

Search  
Here for  
Skill

Search...



Free  
Te



Free  
Sa



Free  
For



Free  
B

# THE LARGEST RANGE

of power measurement  
control & protection products

Congratulations – you have completed **Three-Phase Systems in Power Applications Online T.**

You scored **2** points out of **10** points total.

Your answers are shown below:

1. In a certain Y-Y system, the source phase currents each have a magnitude of 9 A. The magnitude of each load current for a balanced load condition is

- **3A**
- 12A
- 9A
- 27A

2. If in a Y-connected ac generator, each phase voltage has a magnitude of 90 VRMS, what is the magnitude of each line voltage?

- 0 V
- 90 V
- **156 V**
- 180 V

3. In a Y-Y source/load configuration, the

The advertisement features a black Acer laptop on a green surface with a glowing green light effect in the background. The Harvey Norman logo is visible in the bottom right corner. The top part of the ad contains text: "'TIS THE SEASON TO UPGRADE' NVIDIA® GEFORCE® GAMING LAPTOPS" and a "SHOP NOW" button.

- phase current, the line current, and the load current are  $120^\circ$  out of phase
- phase current, the line current, and the load current are all equal in each phase
- **line current and the load current are in phase, and both are out of phase with the phase current**
- phase current and the line current are in phase, and both are  $120^\circ$  out of phase with the load current

---

4. In a Y-connected circuit, the magnitude of each line current is

- one-third the phase current
- **three times the corresponding phase current**
- equal to the corresponding phase current
- zero

---

5. In a Y-connected circuit, between each line voltage and the nearest phase voltage, there is a phase angle of

- $30^\circ$
- $0^\circ$
- $60^\circ$
- $90^\circ$

---

6. Polyphase generators produce simultaneous multiple sinusoidal voltages that are separated by

- certain constant voltages
- certain constant frequencies
- **certain constant currents**
- certain constant phase angles

---

7. A constant load power means a uniform conversion of

- electrical to mechanical energy
- current to voltage
- **mechanical to electrical energy**

- voltage to current

8. In a three-phase system, the voltages are separated by

- 45°
- **90°**
- 120°
- 180°

9. In a certain three-wire Y-connected generator, the phase voltages are 2 kV. The magnitudes of the line voltages are

- **2,000 V**
- 666 V
- 6,000 V
- 3,464 V

10. In a three-phase system, when the loads are perfectly balanced, the neutral current is

- zero
- **two-thirds of maximum**
- one-third of maximum
- at maximum

NEW

Cases, Protectors & More  
Mobile Mate

## **Force Structural - Underpinning, Tight Excavation**

Ad [forcestructural.com.au](http://forcestructural.com.au)

## **300+ TOP EARTHING or GROUNDING Objective Questions and Answers**

[engineeringinterviewquestions.com](http://engineeringinterviewquestions.com)

## **Thomson Bridge Pty Ltd - Cable Jointing Programs**

Ad [thomsonbridge.com](http://thomsonbridge.com)

## **Home Builder**

Ad [furnart building service](http://furnart building service)

## **300+ TOP Single Stage Transistor Amplifiers Questions & Answers pdf |...**

[engineeringinterviewquestions.com](http://engineeringinterviewquestions.com)

## **300+ TOP DIGITAL ELECTRONICS Questions and Answers Pdf**

[engineeringinterviewquestions.com](http://engineeringinterviewquestions.com)

## **3 THOUGHTS ON “THREE-PHASE SYSTEMS IN POWER APPLICATIONS ONLINE TEST – MULTIPLE CHOICE QUESTIONS AND ANSWERS”**



**Lalam M. Naidu**

MAY 31, 2016 AT 11:52 AM

Nice work..

[REPLY](#)



**deb**

MAY 21, 2016 AT 8:36 AM

Good

[REPLY](#)



**yogu**

MAY 3, 2016 AT 9:38 AM

gooddd

[REPLY](#)

## LEAVE A REPLY

---

Your email address will not be published. Required fields are marked \*

**Comment**

**Name** \*

**Email** \*

**Website**

**Post Comment**

Search...

Copyright 2020 , Engineering Interview Questions.com , Theme by [Engineering](#)|| [Privacy Policy](#)|| [Terms and Conditions](#)|| [ABOUT US](#)|| [Contact US](#)||

Engineering interview questions,Mcqs,Objective Questions,Class Lecture Notes,Seminar topics,Lab Viva Pdf PPT Doc Book free download. Most Asked Technical Basic CIVIL | Mechanical | CSE | EEE | ECE | IT | Chemical | Medical MBBS Jobs Online Quiz Tests for Freshers Experienced.