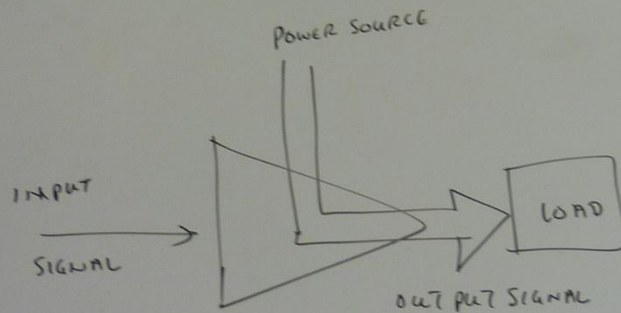


POWER OUTPUT STAGE (PART-1)

FIRST AND INTERMEDIATE STAGE AMPLIFIERS CAN NOT HANDLE THE LARGE POWER. THE OUTPUT STAGE REQUIRES THE POWER AMPLIFIER. THE OUTPUT STAGE MAY BE SERVO MOTOR (OR) INDICATING DEVICES (OR) SPEAKER.

OUTPUT STAGE USUALLY HAS UNITY VOLTAGE GAIN



THE BASIC REQUIREMENTS FOR ANY POWER OUTPUT STAGE ARE


- HIGH EFFICIENCY
- LOW DISTORTION
- LOW OUTPUT IMPEDANCE

OUTPUT STAGE AMPLIFIERS

- (1) CLASS (A)
- (2) CLASS (B)
- (3) CLASS (A+B)

CLASS (A)

- OUTPUT DEVIATION

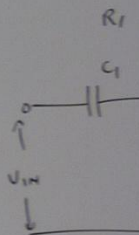


COM
CLA

CLASS (A)

- MAXIMUM
- MAXIMUM
- LOW DISTORTION
- HIGH
- OUTPUT

CLASS (A) AMPLIFIER

— output device conducts for 360°

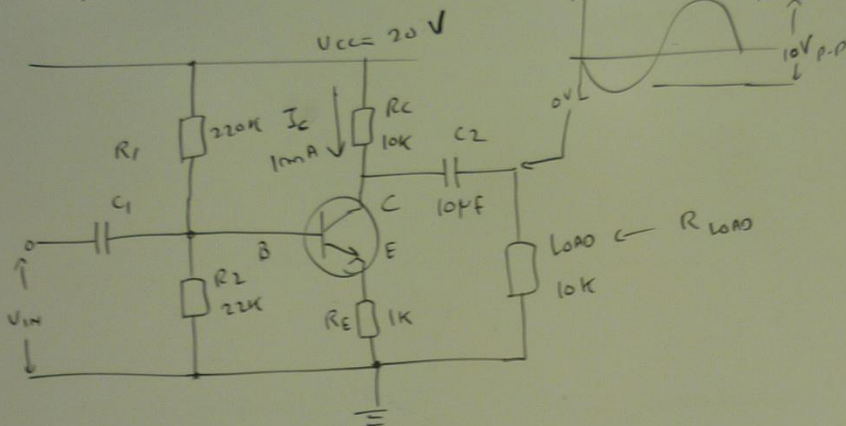

COMMON EMITTER RC COUPLED
CLASS (A) AMPLIFIER

CLASS (A) AMPLIFIER CHARACTERISTICS

- MAXIMUM EFFICIENCY 25% FOR RC COUPLED TYPE
- MAXIMUM EFFICIENCY 50% FOR TRANSFORMER COUPLED TYPE
- LOW DISTORTION THAN CLASS (B)
- HIGH QUIESCENT CURRENT
- OUTPUT DEVICE CONDUCTS FOR 360° OF INPUT SIGNAL

$$P_{IN} = V_{CC} \times I_C$$

$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}}$$


$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

Pb CALCULATE (a) P_{IN} (b) P_{OUT}
(c) V_{O-rms} (d) EFFICIENCY OF
ABOVE CLASS (A) AMPLIFIER

$$P_{IN} = V_{CC} \times I_C = 20 \times 1\text{mA} = 20\text{mW}$$
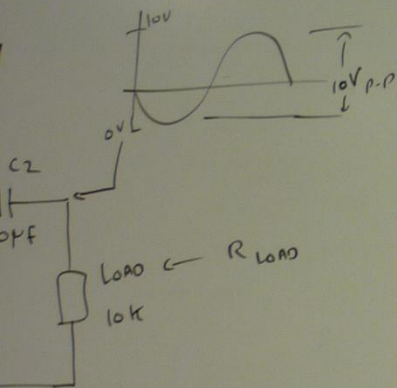
$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142} = 3.53\text{V}$$



$$P_{IN} = V_{CC} \times I_C$$

$$V_{O-rms} = \frac{V_{O-p-p}}{2\sqrt{2}}$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$= \frac{(3.53)^2}{10k} = 1.25 \text{ mW}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$= \frac{1.25}{20} \times 100 = 6.25\%$$

$$\eta = \frac{P_{OUT}}{P_{IN}} =$$

Pb CALCULATE (a) P_{IN} (b) P_{OUT}
(c) V_{O-rms} (d) EFFICIENCY OF
ABOVE CLASS(A) AMPLIFIER

$$P_{IN} = V_{CC} \times I_C = 20 \times 1 \text{ mA} = 20 \text{ mW}$$

$$V_{O-rms} = \frac{V_{O-p-p}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142}$$

$$= 3.53 \text{ V}$$

Pb CALCULATE THE INPUT POWER
REQUIRED FOR AN INDUSTRIAL SOUND
SYSTEM WITH AN EFFICIENCY OF
20% THAT HAS AN OUTPUT POWER
OF 50W.

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$20 = \frac{50}{P_{IN}} \times 100 \rightarrow P_{IN} = \frac{50 \times 100}{20} = 250 \text{ W}$$

1. for RC coupled TYPE

2. for TRANSFORMER
COUPLED TYPE

CLASS(B)

FOR 350 of INPUT SIGNAL

$$P_{IN} = V_{CC} \times I_C$$

$$V_{rms} = \frac{V_{O\ p-p}}{2\sqrt{2}}$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

CALCULATE (a) P_{IN} (b) P_{OUT}
 V_{O-rms} (c) EFFICIENCY OF
 A CLASS (A) AMPLIFIER

$$V_{CC} \times I_C = 20 \times 1\text{mA} = 20\text{mW}$$

$$V_{rms} = \frac{V_{O\ p-p}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142} = 3.53\text{V}$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}} = \frac{(3.53)^2}{10\text{k}} = 1.25\text{mW}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100 = \frac{1.25}{20} \times 100 = 6.25\%$$

Pb CALCULATE THE INPUT POWER
 REQUIRED FOR AN INDUSTRIAL SOUND
 SYSTEM WITH AN EFFICIENCY OF
 20% THAT HAS AN OUTPUT POWER
 OF 50kW.

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$20 = \frac{50}{P_{IN}} \times 100 \rightarrow P_{IN} = \frac{50 \times 100}{20} = 250\text{kW}$$


$$I = \frac{P_{IN}}{V} = \frac{250\text{kW}}{240} = \frac{250 \times 10^3}{240} = 1041.67\text{A}$$

CLASS (A)

POWER OUTPUT STAGE (PART-1)

FIRST AND INTERMEDIATE STAGE AMPLIFIERS CAN NOT HANDLE THE LARGE POWER. THE OUTPUT STAGE REQUIRES THE POWER AMPLIFIER. THE OUTPUT STAGE MAY BE SERVO MOTOR (OR) INDICATING DEVICES (OR) SPEAKER.

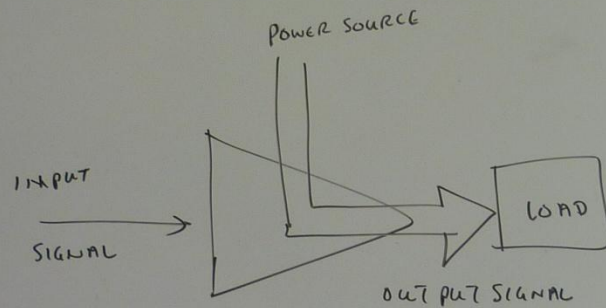OUTPUT STAGE USUALLY HAS UNITY VOLTAGE GAIN



THE BASIC REQUIREMENTS FOR ANY POWER OUTPUT STAGE ARE


- HIGH EFFICIENCY
- LOW DISTORTION
- LOW OUTPUT IMPEDANCE

OUTPUT STAGE AMPLIFIERS

- (1) CLASS (A)
- (2) CLASS (B)
- (3) CLASS (A+B)

CLASS (A) AMPLIFIER

- OUTPUT DEVICE

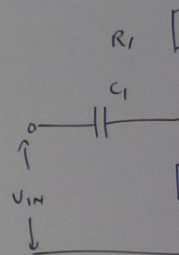


COMMON
CLASS

CLASS (A) AMPLIFIER

- MAXIMUM
- MAXIMUM
- LOW DIST
- HIGH Q
- OUTPUT

CLASS (A) Amplifier

— OUTPUT DEVICE CONDUCTS FOR 360°

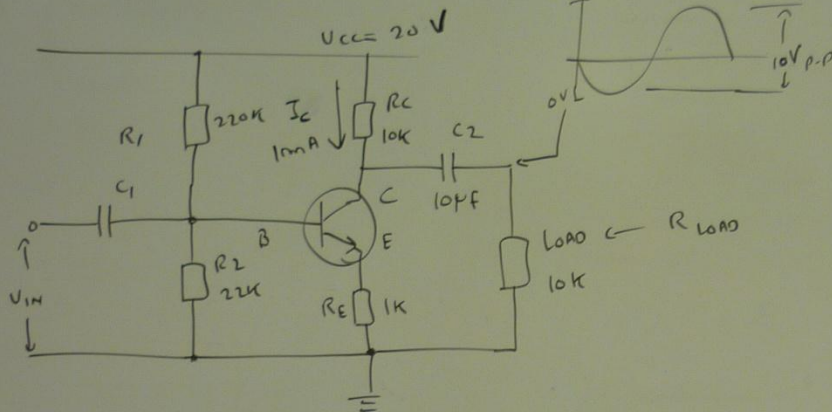

COMMON EMITTER RC COUPLED
CLASS (A) AMPLIFIER

CLASS (A) AMPLIFIER CHARACTERISTICS

- MAXIMUM EFFICIENCY 25% FOR RC COUPLED TYPE
- MAXIMUM EFFICIENCY 50% FOR TRANSFORMER COUPLED TYPE
- LOW DISTORTION THAN CLASS (B)
- HIGH QUIESCENT CURRENT
- OUTPUT DEVICE CONDUCTS FOR 360° OF INPUT SIGNAL

$$P_{IN} = V_{CC} \times I_C$$

$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}}$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

Pb CALCULATE (a) P_{IN} (b) P_{OUT}
(c) V_{O-rms} (d) EFFICIENCY OF
ABOVE CLASS (A) AMPLIFIER

$$P_{IN} = V_{CC} \times I_C = 20 \times 1\text{mA} = 20\text{mW}$$

$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142} = 3.53\text{V}$$

$$P_{OUT} = \frac{V_{O-rms}^2}{R_{LOAD}}$$

$$= \frac{(3.53)^2}{10\text{K}}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$= \frac{12.46}{20} \times 100 = 62.3\%$$

Pb CALCULATE
REQUIRED
SYSTEM WITH
20% THAT
OF SOLW.

$$\% \eta = 20\%$$

$$20 = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$V_{cc} \times I_c$$

$$= \frac{V_{o \text{ p-p}}}{2\sqrt{2}}$$

$$\frac{(V_{o \text{ rms}})^2}{R_{\text{LOAD}}}$$

$$\frac{P_{\text{OUT}}}{P_{\text{IN}}} \times 100$$

Q1. Calculate (a) P_{IN} (b) P_{OUT} (c) Efficiency of CLASS (A) AMPLIFIER

$$I_c = 20 \times 1 \text{ mA} = 20 \text{ mA}$$

$$\frac{V_{o \text{ p-p}}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142}$$

$$= 3.53 \text{ V}$$

$$P_{\text{OUT}} = \frac{(V_{o \text{ rms}})^2}{R_{\text{LOAD}}}$$

$$= \frac{(3.53)^2}{10 \text{ k}} = 1.25 \text{ mW}$$

$$\% \eta = \frac{P_{\text{OUT}}}{P_{\text{IN}}} \times 100$$

$$= \frac{1.25}{20} \times 100 = 6.25\%$$

Q2. Calculate the input power required for an industrial sound system with an efficiency of 20% that has an output power of 50 kW.

$$\% \eta = \frac{P_{\text{OUT}}}{P_{\text{IN}}} \times 100$$

$$20 = \frac{50}{P_{\text{IN}}} \times 100 \rightarrow P_{\text{IN}} = \frac{50 \times 100}{20} = 250 \text{ kW}$$

$$I = \frac{P_{\text{IN}}}{V} = \frac{250 \text{ kW}}{240}$$

$$= \frac{250 \times 10^3}{240}$$

$$= 1041.67 \text{ A}$$

GENERAL FEATURES OF CLASS (B) AMPLIFIER


- MAXIMUM EFFICIENCY - 78.5%
- HIGH DISTORTION (COMPARED TO CLASS (A))
- LOWER POWER DISSIPATION BY THE OUTPUT DEVICES
- TWO OUTPUT DEVICES NEEDED

BOTH CONDUCT FOR 180°.

- VOLTAGE GAIN (A_V) = UNITY

POWER GAIN (A_P) = CURRENT GAINS OF TRANSISTOR

CLASS (B) POWER

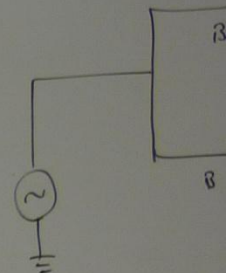

- CLASS (B) AMPLIFIER OF TWO OUTPUT
- Q_1 CONDUCTS FOR THE INPUT SIGNAL
- Q_2 CONDUCTS FOR THE INPUT SIGNAL
- THE OUTPUT SIGNAL IS BOTH TRANSISTORS

Q_1 CONDUCTS FOR 180°

Q_2 OFF

1.25 mW

6.25%

$$I = \frac{P_{IM}}{V} = \frac{250 \text{ kW}}{240} = \frac{250 \times 10^3}{240} = 1041.67 \text{ A}$$

GENERAL FEATURES OF CLASS (B) AMPLIFIER

- MAXIMUM EFFICIENCY - 78.5%
- HIGH DISTORTION (COMPARED TO CLASS (A))
- LOWER POWER DISSIPATION BY THE OUTPUT DEVICES
- TWO OUTPUT DEVICES NEEDED


BOTH CONDUCT FOR 180°

- VOLTAGE GAIN (A_V) = UNITY

POWER GAIN (A_P) = CURRENT GAINS OF TRANSISTOR

$$P_{IM} = \frac{50 \times 100}{20} = 250 \text{ W}$$

CLASS (B) POWER OUTPUT STAGE


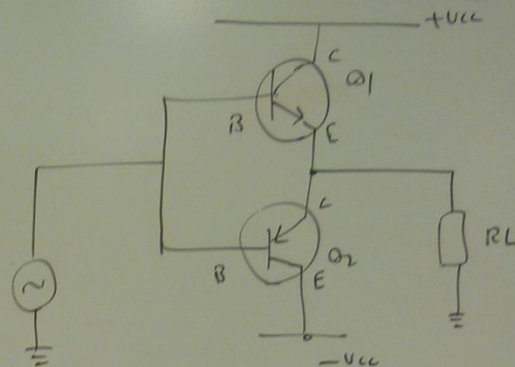


- CLASS (B) AMPLIFIER REQUIRES A MINIMUM OF TWO OUTPUT DEVICES
- Q_1 CONDUCTS FOR THE POSITIVE HALF OF THE INPUT SIGNAL
- Q_2 CONDUCTS FOR THE NEGATIVE HALF.
- THE OUTPUT SIGNAL IS PRODUCED BY BOTH TRANSISTORS.


Q_1 CONDUCTS - Q_2 OFF

Q_1 OFF - Q_2 CONDUCT

DUAL POLARITY POWER SUPPLY

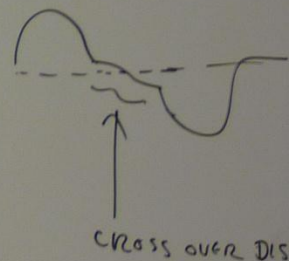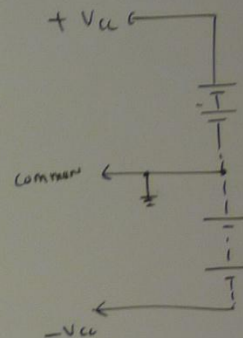

(B) POWER OUTPUT STAGE

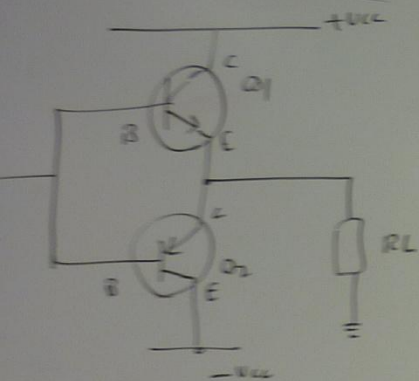

AMPLIFIER REQUIRES A MINIMUM
OUTPUT DEVICES

FOR THE POSITIVE HALF OF
INPUT SIGNAL


CONDUCTS FOR THE NEGATIVE HALF.

OUTPUT SIGNAL IS PRODUCED BY
TRANSISTORS.

CONDUCTS - Q2 off

off - Q2 conducts

DUAL POLARITY POWER SUPPLY

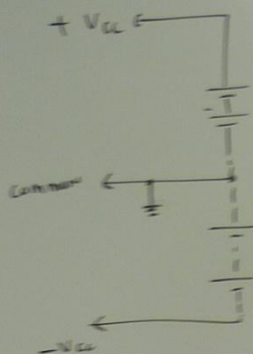

CROSS OVER DISTORTION


POWER OUTPUT EQUATIONS

$$P_{OUT} = \frac{(V_{O-RMS})^2}{R_{LOAD}}$$

$$P_{OUT} = \frac{\left(\frac{V_{O-P-P}}{2\sqrt{2}}\right)^2}{R_{LOAD}}$$

$$P_{OUT} = \frac{(V_{O-P-P})^2}{8 R_{LOAD}}$$

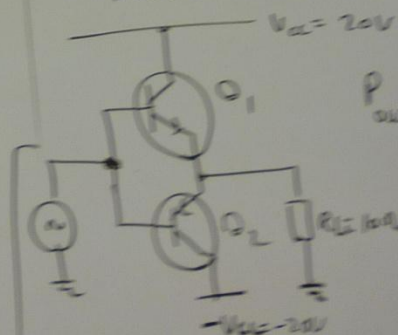P3 CALCULATE THE MAXIMUM OUTPUT
POWER FOR THE GIVEN CIRCUIT



$$P_{OUT} = \frac{(V_{O-P-P})^2}{8 R_L}$$

$$= \frac{(40)^2}{8 \times 10}$$

$$= 20W$$

$$I = \frac{P_{in}}{V} = \frac{250 \text{ kW}}{240} = \frac{250 \times 10^3}{240} = 1041.67 \text{ A}$$

GENERAL FEATURES OF CLASS (B) AMPLIFIER


- MAXIMUM EFFICIENCY - 78.5%
- HIGH DISTORTION (COMPARED TO CLASS (A))
- LOWER POWER DISSIPATION BY THE OUTPUT DEVICES
- TWO OUTPUT DEVICES NEEDED

BOTH CONDUCT FOR 180°

- VOLTAGE GAIN (A_V) = UNITY



POWER GAIN (A_P) = CURRENT GAINS OF TRANSISTOR

CLASS (B) POWER OUTPUT STAGE

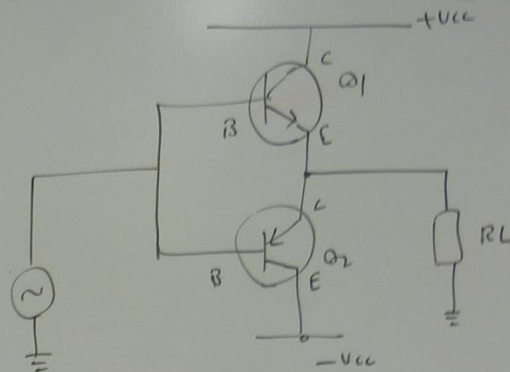

- CLASS (B) AMPLIFIER REQUIRES A MINIMUM OF TWO OUTPUT DEVICES
- Q_1 CONDUCTS FOR THE POSITIVE HALF OF THE INPUT SIGNAL
- Q_2 CONDUCTS FOR THE NEGATIVE HALF.
- THE OUTPUT SIGNAL IS PRODUCED BY BOTH TRANSISTORS.

DUAL POLARITY POWER SUPPLY

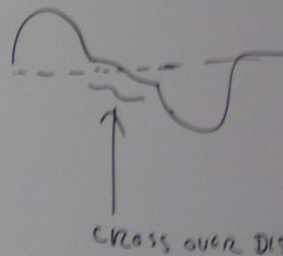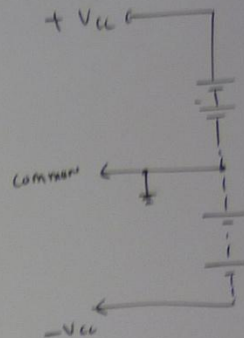


Q_1 CONDUCTS - Q_2 OFF

Q_1 OFF - Q_2 CONDUCT


$$I_{IN} = \frac{50 \times 100}{20} = 250 \text{ mA}$$

(B) POWER OUTPUT STAGE


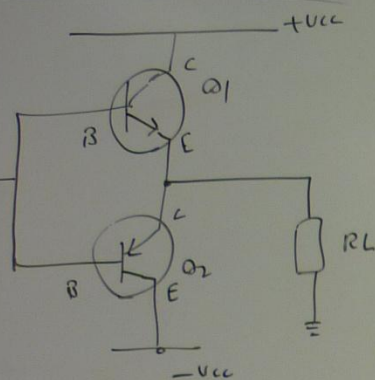


B) AMPLIFIER REQUIRES A MINIMUM OUTPUT DEVICES
 CONDUCTS FOR THE POSITIVE HALF OF INPUT SIGNAL
 CONDUCTS FOR THE NEGATIVE HALF.
 INPUT SIGNAL IS PRODUCED BY TRANSISTORS.

CONDUCTS - Q₂ OFF
 OFF - Q₂ CONDUCT

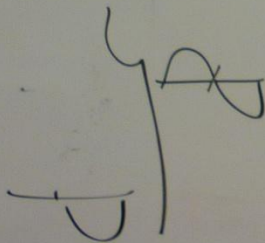

DUAL POLARITY POWER SUPPLY

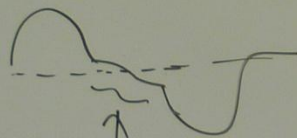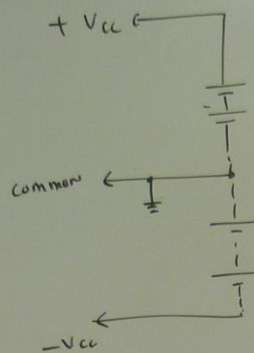

CROSS OVER DISTORTION


POWER OUTPUT EQUATION

$$P_{out} = \frac{(V_{o-rms})^2}{R_{load}}$$

$$P_{out} = \frac{\left(\frac{V_{o-p-p}}{2\sqrt{2}}\right)^2}{R_{load}}$$

$$P_{out} = \frac{(V_{o-p-p})^2}{8 R_{load}}$$

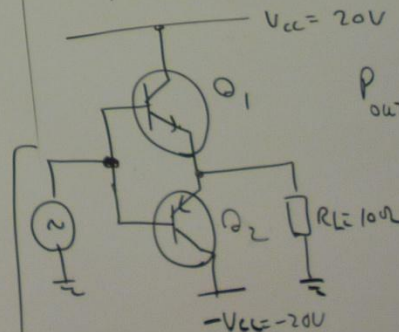PB CALCULATE THE MAXIMUM OUTPUT POWER FOR THE GIVEN CIRCUIT




$$P_{out} = \frac{(V_{o-p-p})^2}{8 R_L}$$

$$= \frac{(40)^2}{8 \times 10}$$

$$= 20W$$

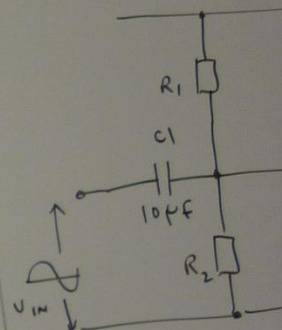PB FOR THE GIVEN
 (a) STATE THE OPT
 (b) CALCULATE THE
 (c) CALCULATE TH
 (d) STATE THE



$$V_c(RMS) = \frac{V}{\sqrt{2}}$$

$$V_c(max) = \sqrt{2} V_c(RMS)$$

$$P_{out} = \frac{(V_o)^2}{R}$$

$$I_c = \frac{V_{cc} - V_c}{R_c}$$


POWER OUTPUT EQUATION

$$P_{OUT} = \frac{(V_{O-RMS})^2}{R_{LOAD}}$$

$$= \frac{\left(\frac{V_{O-P-P}}{2.52}\right)^2}{R_{LOAD}}$$

$$= \frac{(V_{O-P-P})^2}{8 R_{LOAD}}$$

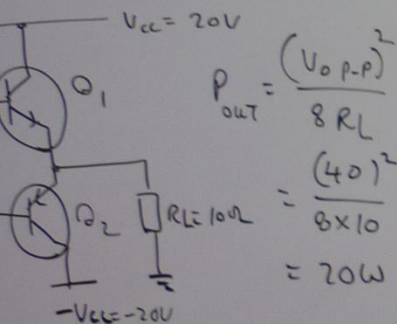CALCULATE THE MAXIMUM OUTPUT POWER FOR THE GIVEN CIRCUIT



$$P_{OUT} = \frac{(V_{O-P-P})^2}{8 R_L}$$

$$= \frac{(40)^2}{8 \times 10}$$

$$= 20W$$


pb FOR THE GIVEN CIRCUIT

(a) STATE THE OPTIMUM VALUE OF COLLECTOR VOLTAGE

(b) CALCULATE THE MAXIMUM OUT PUT POWER

(c) CALCULATE THE POWER BEING DISSIPATED BY Q1 WHEN THE INPUT SIGNAL IS ZERO

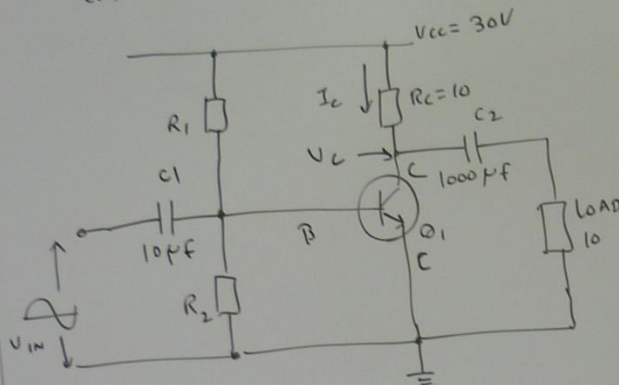(d) STATE THE MAXIMUM EFFICIENCY THE CIRCUIT CAN ACHIEVE.



$$V_{C(RMS)} = \frac{V_{CC}}{2} = \frac{30}{2} = 15V$$

$$V_{C(MAX)} = \sqrt{2} V_{C(RMS)} = \sqrt{2} \times 15 = 21.2V$$


$$P_{OUT} = \frac{(V_{O-RMS})^2}{R_{LOAD}} = \frac{15^2}{10} = 22.5W$$

$$I_C = \frac{V_{CC} - V_C}{R_C} = \frac{30 - 15}{10} = 1.5A$$

$$P_{IN} = V_{CC} \times I_C = 30 \times 1.5 = 45W$$

$$\eta = \frac{P_{OUT}}{P_{IN}} \times 100 = \frac{22.5}{45} = 50\%$$

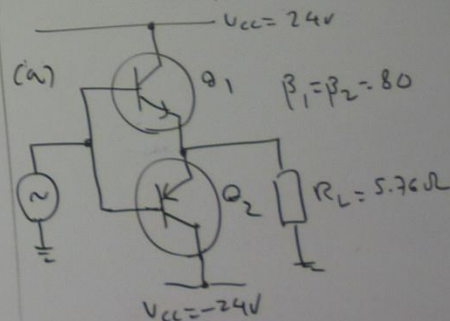pb FOR THE GIVEN CIRCUIT, CALCULATE
(a) THE THEORETICAL MAXIMUM OUTPUT POWER
(b) THE POWER GAIN OF THE CIRCUIT.



$$P_O = \frac{(V_{O-P-P})^2}{8 R_L} = \frac{(2 \times 24)^2}{8 \times 5.76}$$


$$= 50W$$

$$A_P = \beta_1 = \beta_2$$

$$A_P = 80$$

POWER OUTPUT STAGE (PART-2)


CLASS (AB) AMPLIFIER

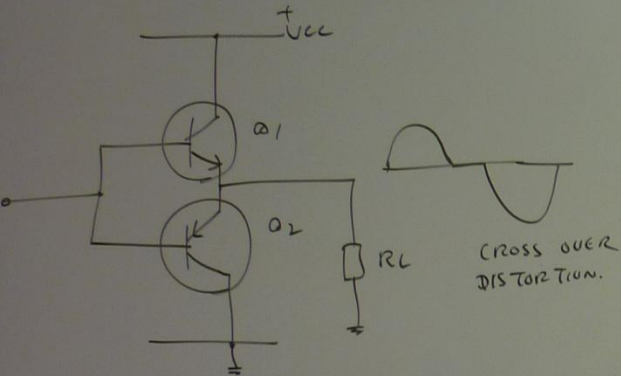

TO ELIMINATE THE CROSS OVER DISTORTION, FORWARD BIAS OF 0.6V NEEDS TO BE APPLIED TO BOTH TRANSISTORS.

CLASS (B) + 0.6V FORWARD BIAS TO ELIMINATE CROSS OVER DISTORTION = CLASS AB AMPLIFIER

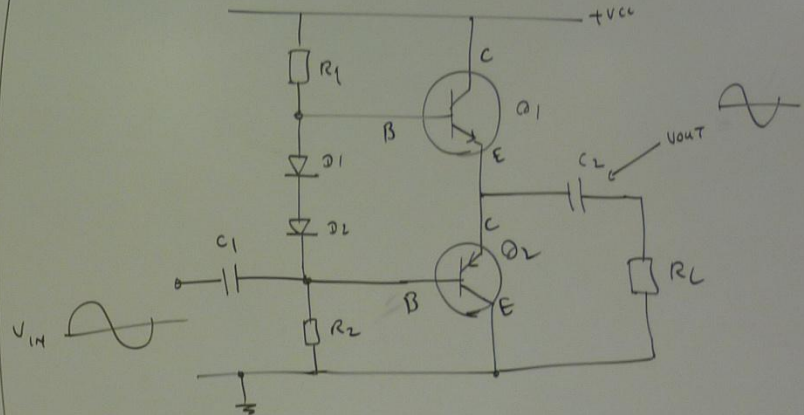
THE BASIC CLASS AB COMPLEMENTARY SYMMETRY AMPLIFIER



CHARACTERISTICS

- maximum efficiency = 78.5%
- EACH TRANSISTOR CONDUCTS FOR EXACTLY 180° OF THE INPUT SIGNAL
- THE CROSS OVER DISTORTION IS ELIMINATED
- THE FORWARD BIAS FOR THE TRANSISTOR IS SUPPLIED BY THE INPUT SIGNAL

DC CONDITION

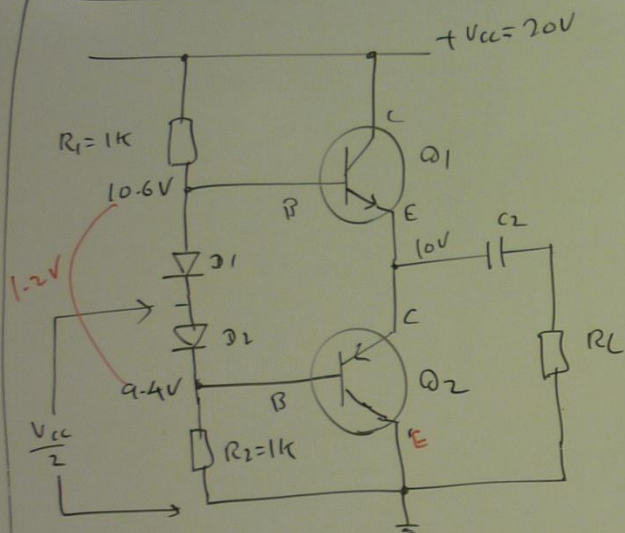

- R_1 must be equal to R_2
- THE DIODES ARE USED TO ENSURE THAT THERE IS A DIFFERENCE OF 1.2V BETWEEN THE VOLTAGES AT THE BASES OF Q_1 AND Q_2
- BOTH TRANSISTOR HAVE A FORWARD BIAS OF 0.6V ACROSS THEIR BASE-EMITTER JUNCTION

LIMITATION


EMITTER VOLTAGE MUST ALWAYS BE LESS 0.6V THAN BASE VOLTAGE.

BOOT STRAPPING

SOME TIME, IT WILL NOT FULLY FILL $V_E - V_B = 0.6V$ WHEN THE SIGNAL SWING IS HIGHER. THE CROSS OVER DISTORTION CAN HAPPEN AGAIN.


TO ELIMINATE THE CROSS OVER DISTORTION AT HIGH SIGNAL SWING, THE BOOTSTRAPPING CIRCUIT IS APPLIED.

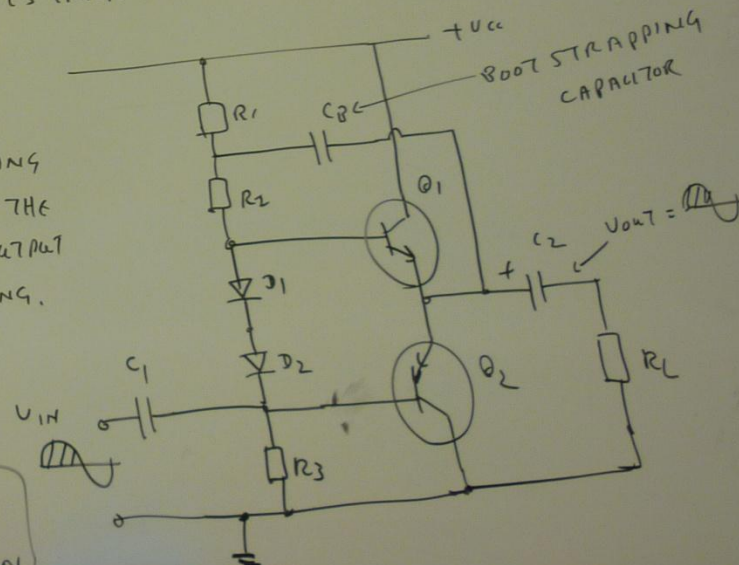APPLYING BOOTSTRAPPING TO OBTAIN THE GREATER OUTPUT SIGNAL SWING.



POWER OUTPUT STAGE (PART-2)


CLASS (AB) AMPLIFIER

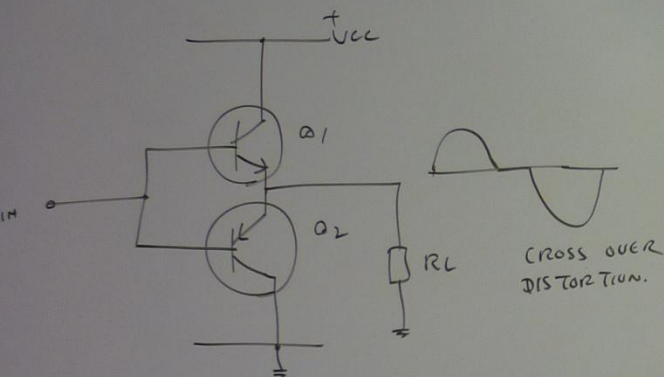

TO ELIMINATE THE CROSS OVER DISTORTION,
FORWARD BIAS OF 0.6V NEEDS TO BE
APPLIED TO BOTH TRANSISTORS.

CLASS (B) + 0.6V FORWARD
BIAS TO ELIMINATE CROSS OVER DISTORTION
= CLASS AB AMPLIFIER

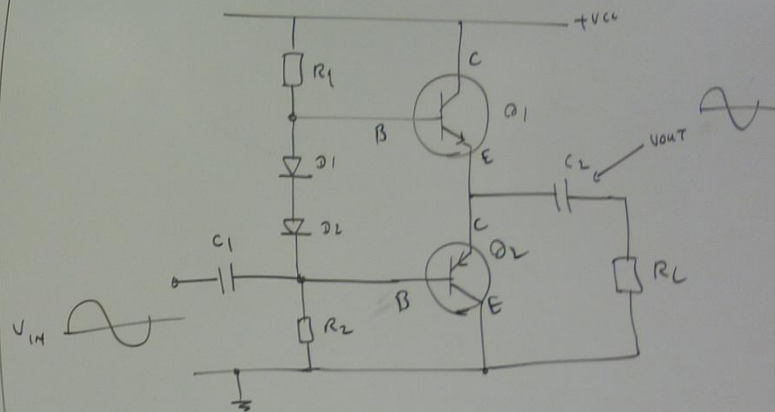THE BASIC CLASS AB COMPLEMENTARY SYMMETRY AMPLIFIER




CHARACTERISTICS

- MAXIMUM EFFICIENCY = 78.5%
- EACH TRANSISTOR CONDUCTS FOR EXACTLY 180° OF THE INPUT SIGNAL
- THE CROSS OVER DISTORTION IS ELIMINATED
- THE FORWARD BIAS FOR THE TRANSISTOR IS SUPPLIED BY THE INPUT SIGNAL

amplifier

DC CONDITION

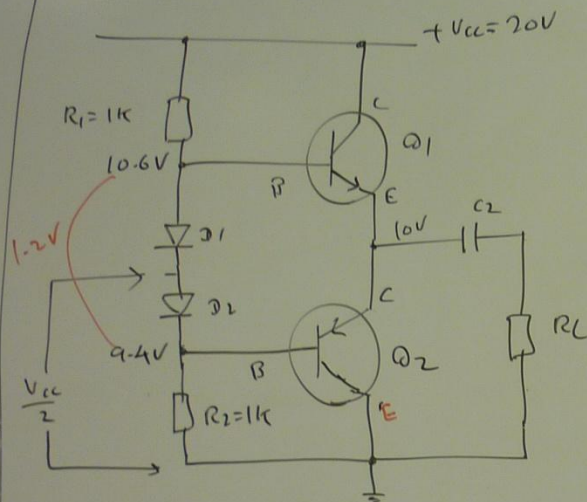

- R_1 must be equal to R_2
- THE DIODES ARE USED TO ENSURE THAT THERE IS A DIFFERENCE OF 1.2V BETWEEN THE VOLTAGES AT THE BASES OF Q_1 AND Q_2
- BOTH TRANSISTOR HAVE A FORWARD BIAS OF 0.6V ACROSS THEIR BASE-EMITTER JUNCTION

LIMITATION


EMITTER VOLTAGE MUST ALWAYS BE LESS 0.6V THAN BASE VOLTAGE.

BOOT STRAPPING

SOME TIME, IT WILL NOT FULL FILL $V_E - V_B = 0.6V$ WHEN THE SIGNAL SWING IS HIGHER. THE CROSS OVER DISTORTION CAN HAPPEN AGAIN.


TO ELIMINATE THE CROSS OVER DISTORTION AT HIGH SIGNAL SWING, THE BOOTSTRAPPING CIRCUIT IS APPLIED.

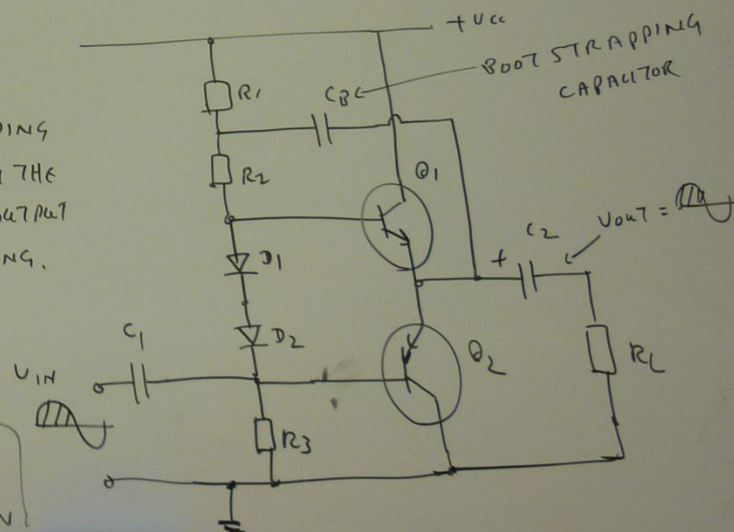APPLYING BOOTSTRAPPING TO OBTAIN THE GREATER OUTPUT SIGNAL SWING.




DARLINGTON OUTPUT TRANSISTORS

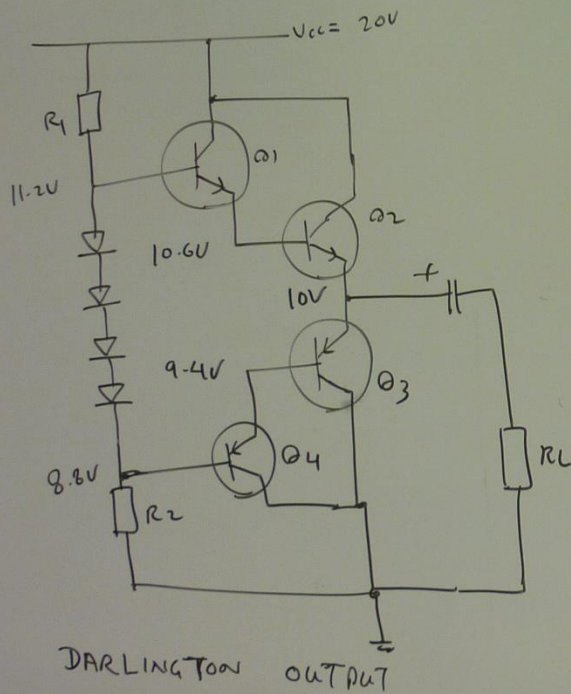TO INCREASE THE CURRENT GAIN OF THE OUTPUT TRANSISTORS, IT IS COMMON TO USE THE DARLINGTON PAIRS.



QUASI COMPLEMENTARY AMPLIFIER

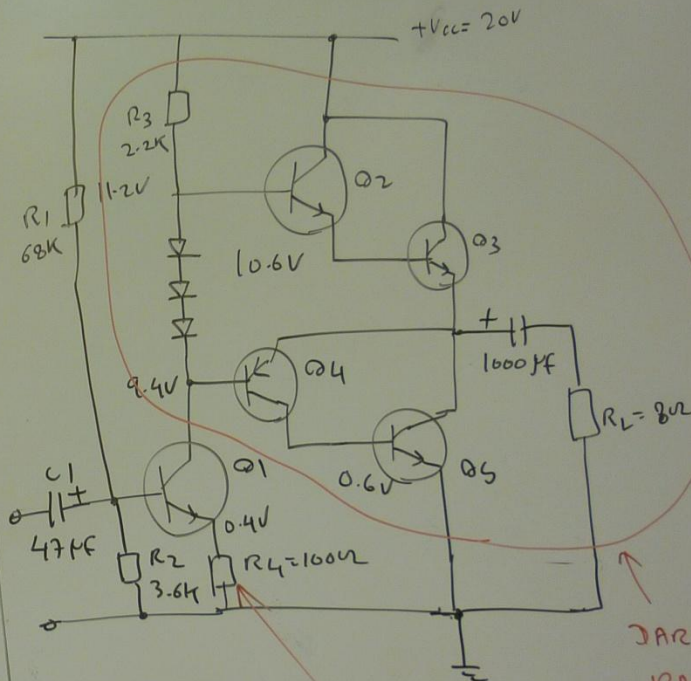


POWER AMPLIFIER WITH AMPLIFIER DRIVER STAGE

DRIVER STAGE

DARLINGTON PAIR
(TO INCREASE CURRENT GAIN)

QUASI COMPLEMENTARY AMPLIFIER

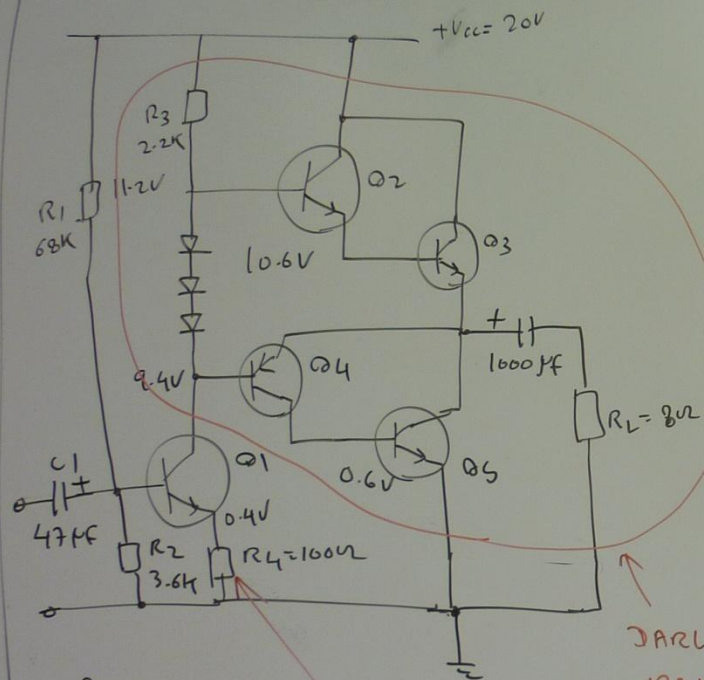

POWER AMPLIFIER WITH AMPLIFIER
DRIVER STAGE

DRIVER STAGE

DARLINGTON
PAIR
(TO INCREASE
CURRENT
GAIN)

POWER OUTPUT CALCULATION =

$$\frac{(V_{o \text{ p-p}})^2}{8 R_L}$$