

CALCULATION OF POWER IN FOUR WIRE STAR CONNECTED UNBALANCED LOADS


FOR 3 ϕ BALANCED LOAD 3ϕ POWER = $\sqrt{3} E I \cos \theta$

FOR 3 ϕ UNBALANCED LOAD, THE ABOVE FORMULA CAN NOT BE USED

$$3\phi \text{ power} = V_{AN} I_A \cos \theta_{IA}^{VAN} + V_{BN} I_B \cos \theta_{IB}^{VBN} + V_{CN} I_C \cos \theta_{IC}^{VCN}$$

ph 3 ϕ 208 V ABC, $Z_A = 10 \angle -60^\circ$, $Z_B = 6 \angle -90^\circ$, $Z_C = 12 \angle 30^\circ$. FIND 3 ϕ POWER
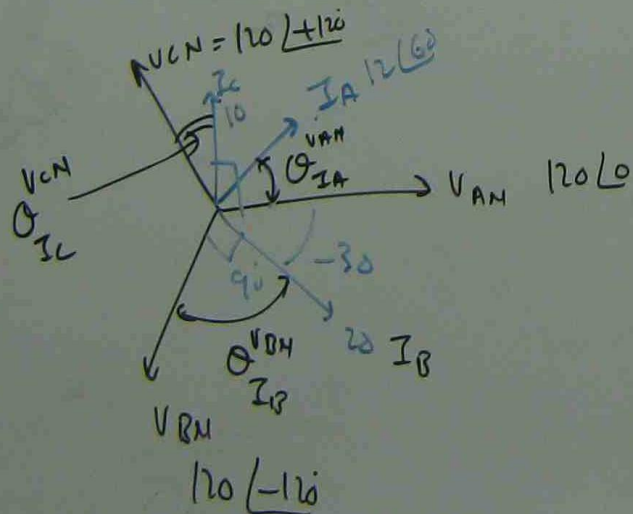
$$V_{AN} = \frac{208}{\sqrt{3}} = 120 \text{ V}$$



$$\bar{I}_A = \frac{V_{AN}}{Z_A} = \frac{120 \angle 0^\circ}{10 \angle -60^\circ} = 12 \angle 60^\circ \text{ A}$$

$$\bar{I}_B = \frac{V_{BN}}{Z_B} = \frac{120 \angle -120^\circ}{6 \angle -90^\circ} = 20 \angle -30^\circ \text{ A}$$

$$\bar{I}_C = \frac{V_{CN}}{Z_C} = \frac{120 \angle 120^\circ}{12 \angle 30^\circ} = 10 \angle 40^\circ \text{ A}$$

$$\theta_{IA}^{VAN} = 60^\circ, \theta_{IB}^{VBN} = 30^\circ$$

$$\theta_{IC}^{VCN} = 30^\circ$$

$$P_A = V_{AN} I_A \cos \theta_{IA}^{VAN} = 120 \times 12 \times \cos 60^\circ = 720 \text{ WATT}$$

$$P_B = V_{BN} I_B \cos \theta_{IB}^{VBN} = 120 \times 20 \times \cos 30^\circ = 0 \text{ WATT}$$

$$P_C = V_{CN} I_C \cos \theta_{IC}^{VCN} = 120 \times 10 \times \cos 30^\circ = 1039 \text{ WATT}$$

$$P_T = P_A + P_B + P_C = 720 + 0 + 1039 = 1759 \text{ WATT}$$

CALCULATION OF POWER IN FOUR WIRE STAR CONNECTED UNBALANCED LOADS


FOR 3 ϕ BALANCED LOAD 3 ϕ POWER = $\sqrt{3} E I \cos \theta$

FOR 3 ϕ UNBALANCED LOAD, THE ABOVE FORMULA CAN NOT BE USED

$$3\phi \text{ power} = V_{AN} I_A \cos \theta_{IA} + V_{BN} I_B \cos \theta_{IB} + V_{CN} I_C \cos \theta_{IC}$$

ph 3 ϕ 208 V ABC, $Z_A = 10 \angle -60^\circ$, $Z_B = 6 \angle -90^\circ$, $Z_C = 12 \angle 30^\circ$. FIND 3 ϕ POWER
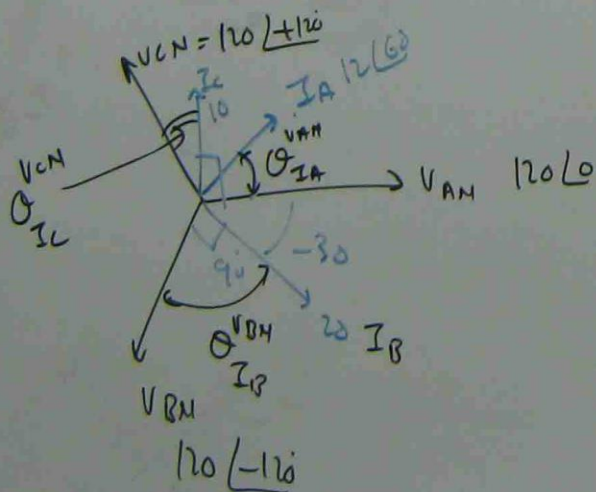
$$V_{AN} = \frac{208}{\sqrt{3}} = 120 \text{ V}$$



$$\bar{I}_A = \frac{V_{AN}}{Z_A} = \frac{120 \angle 0^\circ}{10 \angle -60^\circ} = 12 \angle 60^\circ \text{ A}$$

$$\bar{I}_B = \frac{V_{BN}}{Z_B} = \frac{120 \angle -120^\circ}{6 \angle -90^\circ} = 20 \angle -30^\circ \text{ A}$$

$$\bar{I}_C = \frac{V_{CN}}{Z_C} = \frac{120 \angle 120^\circ}{12 \angle 30^\circ} = 10 \angle 90^\circ \text{ A}$$

$$\theta_{IA}^{VAN} = 60^\circ, \theta_{IB}^{VBN} = 90^\circ$$

$$\theta_{IC}^{VCN} = 30^\circ$$


$$P_A = V_{AN} I_A \cos \theta_{IA} = 120 \times 12 \times \cos 60^\circ = 720 \text{ WATT}$$

$$P_B = V_{BN} I_B \cos \theta_{IB} = 120 \times 20 \times \cos 90^\circ = 0 \text{ WATT}$$

$$P_C = V_{CN} I_C \cos \theta_{IC} = 120 \times 10 \times \cos 30^\circ = 1039 \text{ WATT}$$

$$P_T = P_A + P_B + P_C = 720 + 0 + 1039 = 1759 \text{ WATT}$$

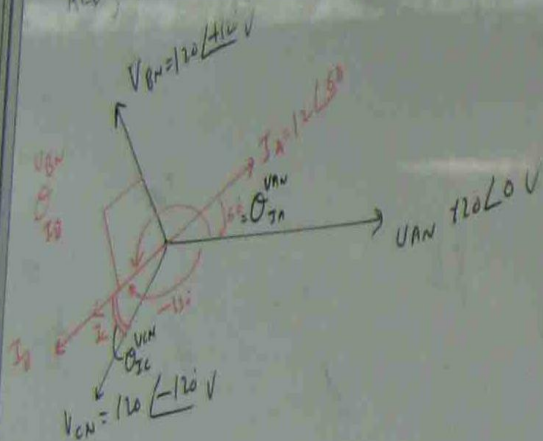Pb IN ABOVE PROBLEM, IF THE PHASE SEQUENCE IS CHANGED TO ACB, FIND TOTAL 3 ϕ POWER



$$\bar{I}_A = \frac{\bar{V}_{AN}}{Z_A} = \frac{120\angle 0^\circ}{10\angle -60^\circ} = 12\angle 60^\circ \text{ A}$$

$$\bar{I}_B = \frac{\bar{V}_{BN}}{Z_B} = \frac{120\angle 120^\circ}{6\angle -90^\circ} = 20\angle 210^\circ \text{ A}$$

$$\bar{I}_C = \frac{\bar{V}_{CN}}{Z_C} = \frac{120\angle -120^\circ}{12\angle 30^\circ} = 10\angle -150^\circ \text{ A}$$

$$\theta_{TA} = 60^\circ$$

$$\theta_{TB} = 90^\circ$$

$$\theta_{TC} = 30^\circ$$

$$P_A = V_{AN} I_A \cos \theta_{TA} = 120 \times 12 \cos 60^\circ = 720 \text{ W}$$

$$P_B = V_{BN} I_B \cos \theta_{TB} = 120 \times 20 \cos 90^\circ = 0$$

$$P_C = V_{CN} I_C \cos \theta_{TC} = 120 \times 10 \cos 30^\circ = 1039 \text{ W}$$

$$P_T = P_A + P_B + P_C$$

$$= 720 + 0 + 1039$$

$$= 1759 \text{ W}$$

BY REVERSING THE PHASE SEQUENCE

(1) LINE CURRENT MAGNITUDE - THE SAME / PHASE ANGLE DIFFERENT

(2) DIFFERENT NEUTRAL CURRENT

(3) THE SAME TOTAL 3 ϕ POWER.

EXERCISE

- ① A 3 ϕ 4 WIRE 415 V SUPPLY IS CONNECTED TO AN UNBALANCED STAR CONNECTED LOAD WHERE

$$Z_A = 32 \angle 30^\circ \Omega, \quad Z_B = 18 \angle -30^\circ \Omega, \quad Z_C = 20 \angle 45^\circ \Omega$$

PHASE SEQUENCE IS ABC. THE REFERENCE VOLTAGE IS V_{AN} .

- CALCULATE (a) LINE CURRENTS $\bar{I}_A, \bar{I}_B, \bar{I}_C$
(b) NEUTRAL CURRENT \bar{I}_N
(c) DRAW PHASOR DIAGRAM

- ② A 3 ϕ 4 WIRE 300 V SUPPLY IS CONNECTED TO AN UNBALANCED LOAD. THE LINE CURRENTS ARE $\bar{I}_A = 15 \angle 30^\circ \text{ A}, \bar{I}_B = 10 \angle -95^\circ \text{ A}, \bar{I}_C = 17 \angle 90^\circ \text{ A}$

THE PHASE ROTATION IS ABC. THE REFERENCE VOLTAGE IS V_{AN} .

CALCULATE (i) THE IMPEDANCES Z_A, Z_B, Z_C

(ii) THE NEUTRAL CURRENT \bar{I}_N .