
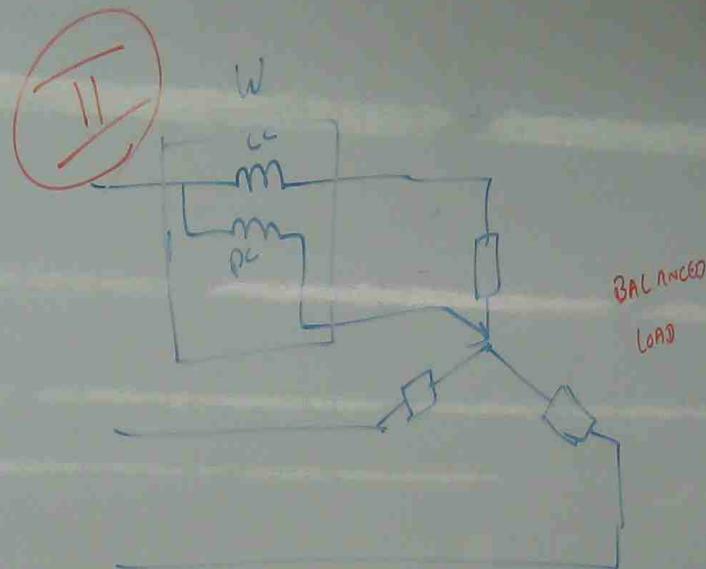


3 ϕ POWER MEASUREMENT

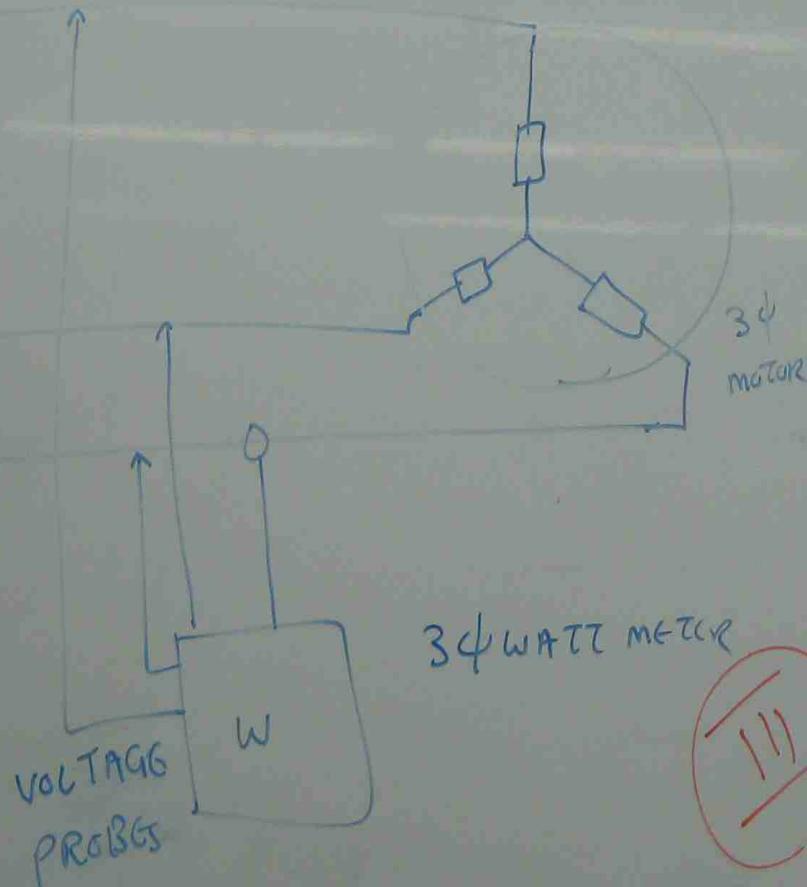


$$3\phi \text{ power} = 3 \times \text{WATT METER READING}$$

FOR 1 ϕ

TWO WATTS METER METHOD FOR 3 ϕ UNBALANCED LOAD

III

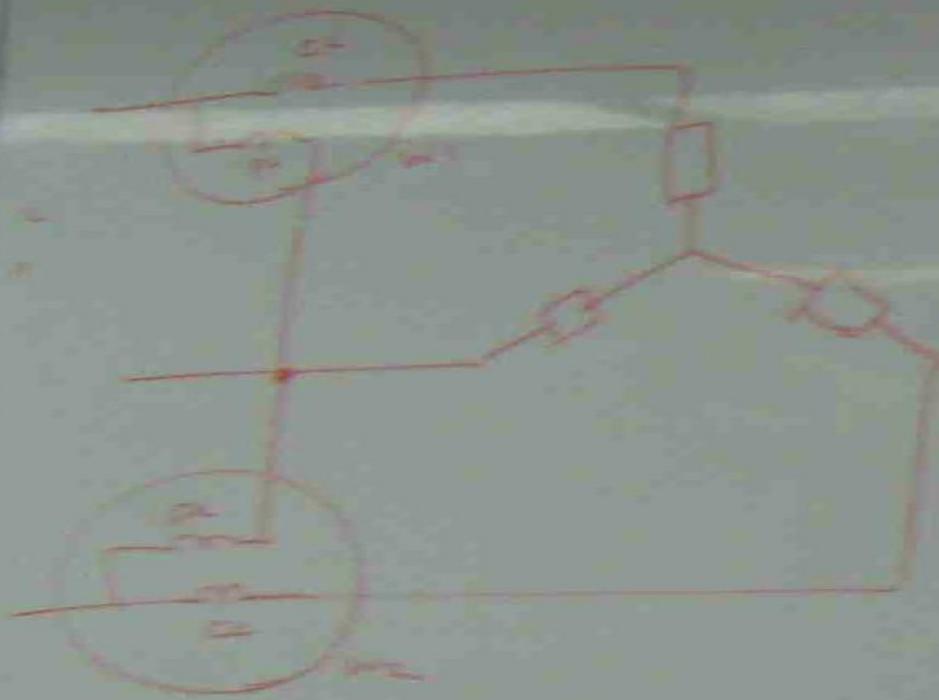


Total power = P_{total}



$$P_{total} = 3 \times \frac{41.5}{\sqrt{2}} \times 7$$

CONNECT THE CIRCUIT

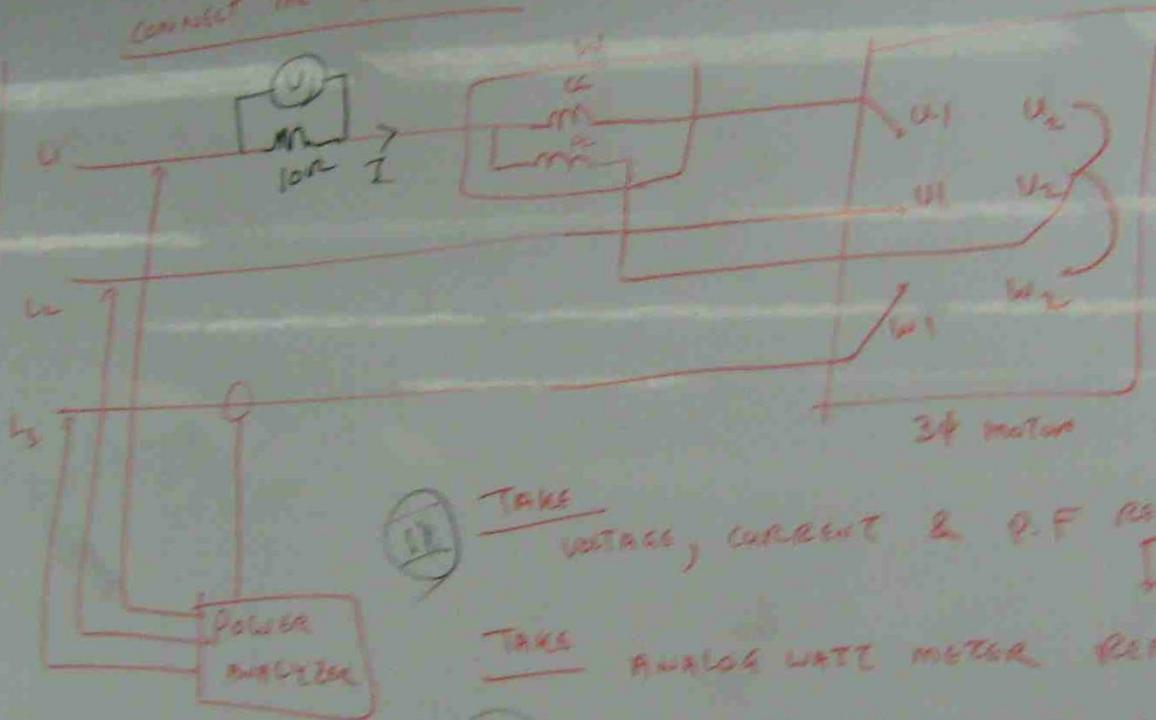

TAKE VOLTAGE, CURRENT & P.F READING OF Power analyzer

$$W = V \times I \times PF$$

TAKE ANALOG WATT METER READING, CONVERTER SCALE FACTOR

Ex: IF 150V, 2A SETTING,

$$I = \frac{V_1}{10A} \text{ Amp}$$

$$3\phi \text{ power} = 3V_2$$

(APPENDAGE)

$$\begin{matrix} 1 \\ 5A \\ 150V \end{matrix} \rightarrow \text{SCALE FACTOR}$$

ACTUAL WATT = READING \times SCALE FACTOR

3φ MOTOR WATT = 3 \times ACTUAL WATT

Customer Service
Centre

TAFE

