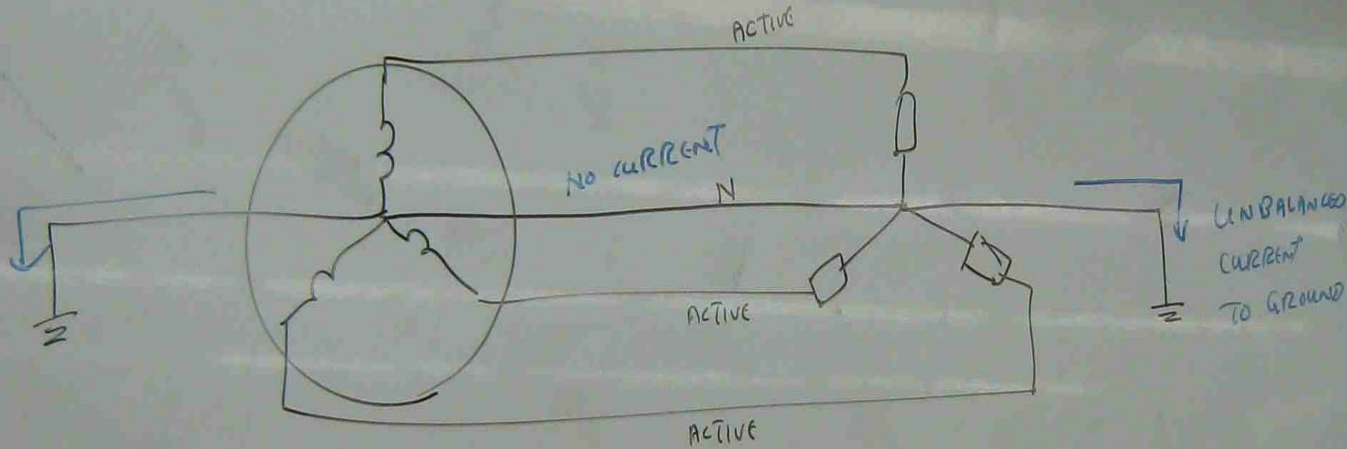




3 ϕ 4 WIRE \times UNBALANCED LOAD



GENERATION

3 ϕ LOAD

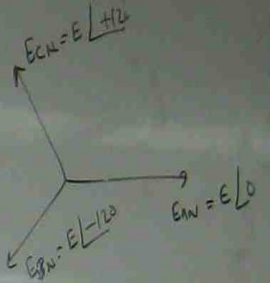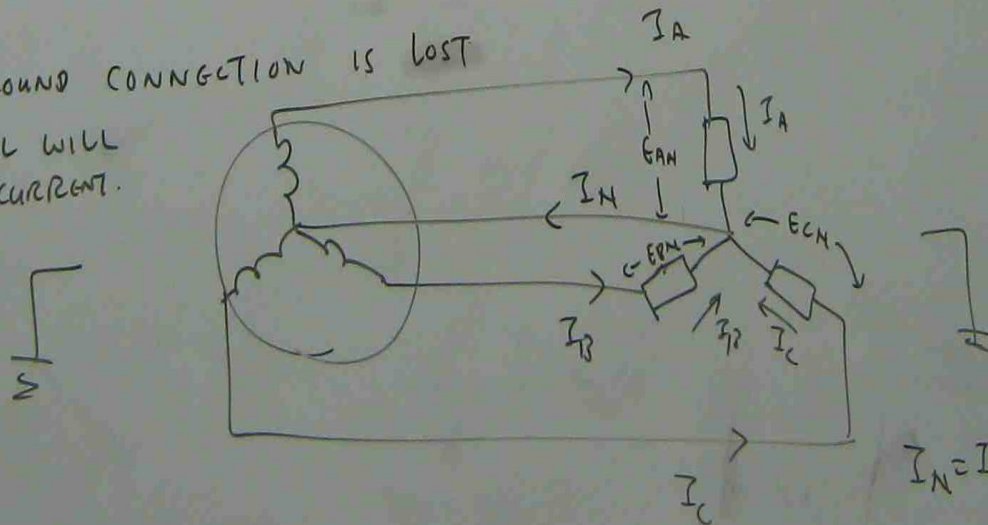IF GROUND CONNECTION IS LOST
NEUTRAL WILL
CARRY CURRENT.



$$E_{AN} = \frac{E_{LINE}}{\sqrt{3}}$$

$$I_A = \frac{E_{AN}}{Z_A} = \frac{E_L \angle 0}{Z_A \angle \phi_A}$$


$$E_{BN} = \frac{E_{LINE}}{\sqrt{3}} =$$

$$I_B = \frac{E_{BN}}{Z_B} = \frac{E_L \angle -120}{Z_B \angle \phi_B}$$

$$E_{CN} = \frac{E_{LINE}}{\sqrt{3}}$$

$$I_C = \frac{E_{CN}}{Z_C} = \frac{E_L \angle +120}{Z_C \angle \phi_C}$$

$$I_N = I_A + I_B + I_C$$

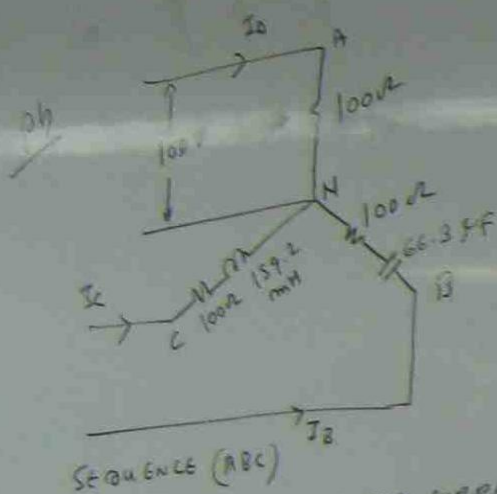

FIND LINE CURRENTS & NEUTRAL CURRENT.

$$Z_A = 100 \Omega$$

$$Z_B = 100 - jX_C \quad X_C = \frac{1}{2\pi fC}$$

$$= 100 - j \frac{1}{2\pi fC}$$

$$= 100 - j \frac{1}{2 \times 3.1416 \times 50 \times 66.3 \times 10^{-6}}$$

$$= 100 - j \frac{10^6}{2 \times 3.1416 \times 50 \times 66.3}$$

$$Z_B = 100 - j48 \Omega = \sqrt{100^2 + 48^2} \angle -\tan^{-1} \frac{48}{100}$$

$$= 111 \angle -26.5^\circ \Omega$$

$$X_L = 2\pi fL$$

$$Z_C = 100 + jX_L$$

$$= 100 + j2\pi fL$$

$$= 100 + j2 \times 3.1416 \times 50 \times 159.2 \times 10^{-3}$$

$$= 100 + j50 = \sqrt{100^2 + 50^2} \angle \tan^{-1} \frac{50}{100}$$

$$E_{CN} = 100 \angle 120^\circ$$

$$= 111.8 \angle 26.5^\circ \Omega$$

$$E_{AN} = 100 \angle 0^\circ$$

$$E_{BN} = 100 \angle -120^\circ$$

$$I_A = \frac{E_{AN}}{Z_A} = \frac{100 \angle 0^\circ}{100} = 1 \angle 0^\circ \text{ A}$$

$$I_B = \frac{E_{BN}}{Z_B} = \frac{100 \angle -120^\circ}{111 \angle -25.6^\circ} = 0.929 \angle -120 - (-25.6)$$

$$= 0.929 \angle -120 + 25.6$$

$$I_B = 0.929 \angle -94.4^\circ \text{ A}$$

$$I_C = \frac{E_{CN}}{Z_C} = \frac{100 \angle 120^\circ}{111.8 \angle 26.5^\circ}$$

$$= 0.894 \angle 120 - 26.5$$

$$I_C = 0.894 \angle 93.5^\circ$$

$$I_N = I_A + I_B + I_C$$

$$= 1 \angle 0^\circ + 0.929 \angle -94.4^\circ + 0.894 \angle 93.5^\circ$$

$$= 1 + 0.929 (\cos(-94.4) + j \sin(-94.4))$$

$$+ 0.894 (\cos 93.5 + j \sin 93.5)$$

$$= 1 - 0.0684 - j0.891 - 0.053 + j0.8922$$

$$= 0.878 + j0.0012$$



$$= \sqrt{0.878^2 + 0.0012^2} \angle \tan^{-1} \frac{0.0012}{0.878}$$

$$I_N = 0.878 \angle 0.978^\circ \text{ A}$$

BREAKING OF NEUTRAL WIRE IN 3 ϕ 4 WIRE SYSTEM

THE SYSTEM BECOMES 3 ϕ 3 WIRE UNBALANCED.

3 ϕ
4 WIRE

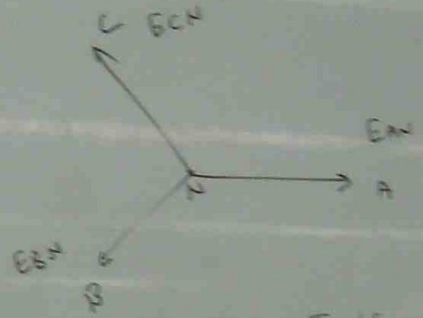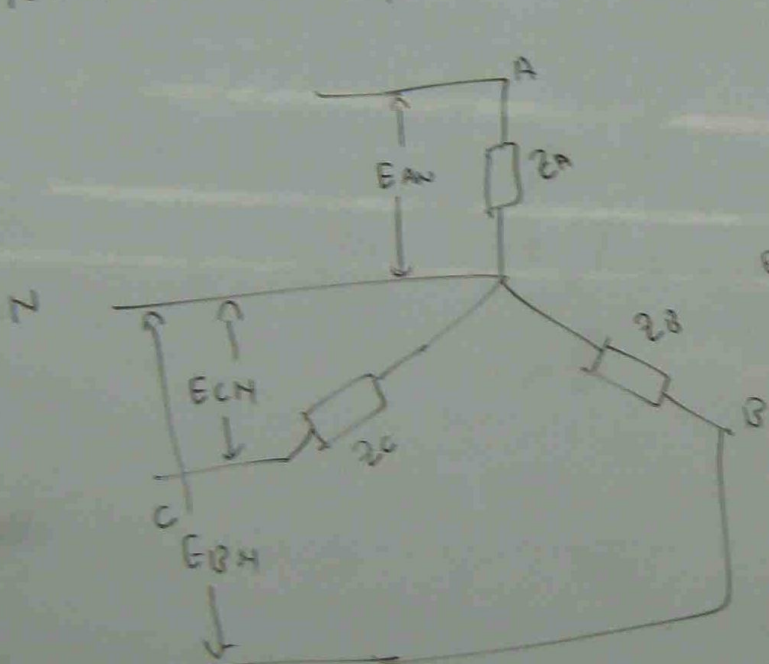

STAR POINT IS
ALSO NEUTRAL
POINT

(3 ϕ 4 WIRE) \leftarrow BALANCE
UNBALANCE

PHASE VOLTAGE
FOLLOWS


$$E_{AN} = \frac{E_{LINE}}{\sqrt{3}}$$

$$E_{BN} = \frac{E_{LINE}}{\sqrt{3}}$$

$$E_{CN} = \frac{E_{LINE}}{\sqrt{3}}$$

WIRE SYSTEM

UNBALANCED

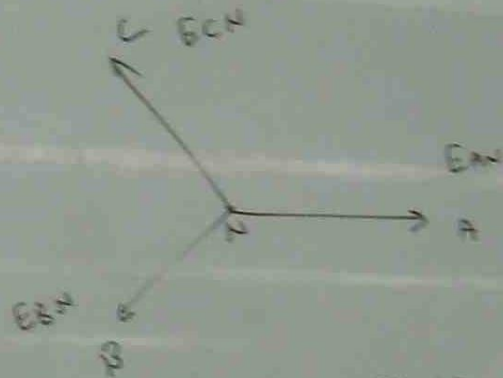


STAR POINT IS
ALSO NEUTRAL
POINT

(3 WIRE) ← BALANCE
UNBALANCE

PHASE VOLTAGE
FOLLOWS

IF NEUTRAL WIRE BROKEN

STAR POINT POSITION CHANGES

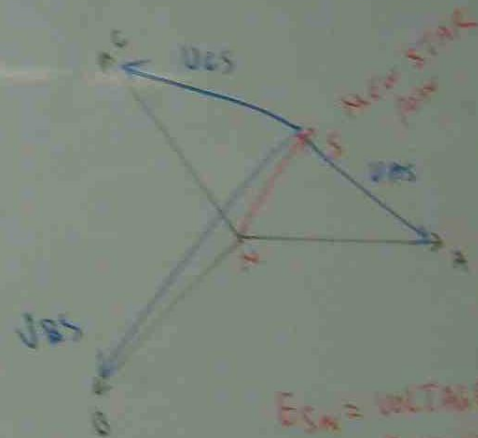

E_{SN} = VOLTAGE
BETWEEN
NEW STAR
POINT

ORIGINAL NEUTRAL
POINT

IN NEW DIAGRAM,

$$E_{BS} > E_{BN}$$

OVER VOLTAGE OCCURS

$$\begin{aligned}
 E_{SN} &= E_{AN} - E_{NS} \\
 E_{SN} &= E_{AN} - E_{BS} \\
 E_{SN} &= E_{CN} - E_{CS}
 \end{aligned}$$


$$E_{AS} = I_A \times Z_A \quad \text{AT UNBALANCED LOAD}$$

$$E_{BS} = I_B \times Z_B \quad \text{AT UNBALANCED LOAD}$$

$$E_{CS} = I_C \times Z_C \quad \text{AT UNBALANCED LOAD}$$

TO CALCULATE I_A, I_B, I_C AT 3 ϕ SWIRE UNBALANCED CONDITION, Δ LOAD IS TO BE CONVERTED TO Δ .


THEN FIND Δ UNBALANCED LINE CURRENTS.

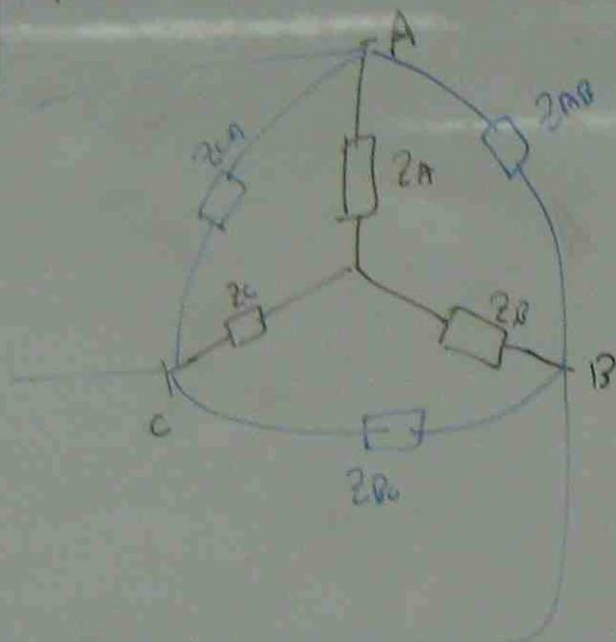


$$Z_{AB} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_C}$$

$$Z_{BC} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_A}$$

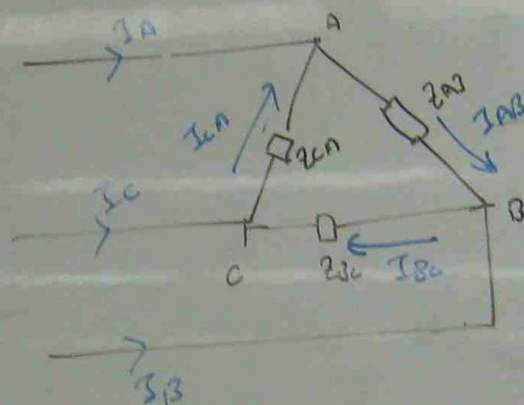$z_{CA} = \frac{z_A z_B + z_B z_C + z_C z_A}{z_B}$



SEQUENCE
 A B C

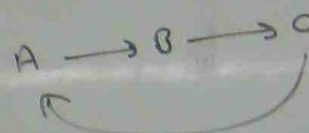

$$I_{AB} = \frac{V_{AB}}{z_{AB}}$$

$$I_{BC} = \frac{V_{BC}}{z_{BC}}$$

$$I_{CA} = \frac{V_{CA}}{z_{CA}}$$

AT (A) $I_A + I_{CA} = I_{AB}$
 $I_A = I_{AB} - I_{CA}$

AT (B) $I_B + I_{AB} = I_{BC}$
 $I_B = I_{BC} - I_{AB}$

AT (C) $I_C + I_{BC} = I_{CA}$
 $I_C = I_{CA} - I_{BC}$

$$E_{AS} = I_A z_A \quad E_{BS} = I_B z_B$$

$$E_{CS} = I_C z_C$$

$$E_{SN} = E_{AN} - E_{AS} \quad \cdot 2$$

(OR)
 $E_{BN} - E_{BS}$
 (OR)
 $E_{CN} - E_{CS}$

ph

A 34 200V system's NEUTRAL WIRE IS BROKEN.

THE FOLLOWING LINE CURRENTS ARE FLOWING

$$Z_A = 50 \angle 0^\circ \Omega, \quad I_A = 1.55 \angle -8.5^\circ \text{ amp.}$$

$$Z_B = 50 \angle 0^\circ \Omega, \quad I_B = 2.47 \angle -176.4^\circ \text{ amp}$$

$$Z_C = 150 \angle 71.6^\circ \Omega, \quad I_C = 1.03 \angle 26.88^\circ \text{ amp.}$$

(i) WHAT ARE THE NEW PHASE VOLTAGE ?

(ii) WHAT IS THE VOLTAGE BETWEEN NEW STAR POINT
 & ORIGINAL POINT

(iii) WHICH PHASE GOT OVER VOLTAGE ?



$$\text{NORMAL PHASE VOLTAGE} = \frac{E\text{-LINE}}{\sqrt{3}} = \frac{200}{1.7321}$$

$$= 115 \text{ V}$$

$$E_{AS} = I_A Z_A = 1.55 \angle -8.5^\circ \times 50 \angle 0^\circ = 1.55 \times 50 \angle -8.5^\circ + 0^\circ \\ = 77.5 \angle -8.5^\circ \checkmark$$

$$E_{BS} = I_B Z_B = 2.47 \angle -176.4^\circ \times 50 \angle 0^\circ \\ = 2.47 \times 50 \angle -176.4^\circ + 0^\circ \\ = 123 \angle -176.4^\circ \checkmark$$

$$E_{CS} = I_C Z_C = 1.03 \angle 26.88^\circ \times 158 \angle 71.6^\circ \\ = 1.03 \times 158 \angle 26.88^\circ + 71.6^\circ \\ = 162.5 \angle 98.7^\circ \checkmark$$

$$E_{SM} = E_{AM} - E_{AS}$$

$$= 115 \angle 0^\circ - 77.5 \angle -8.5^\circ$$

$$= 115 - 77.5 (\cos 8.5^\circ - j \sin 8.5^\circ)$$

\approx

A 3 ϕ 200V system's neutral wire is broken.
The following line currents are flowing

$$Z_A = 50 \angle 0^\circ \Omega, \quad I_A = 1.55 \angle -8.5^\circ \text{ Amp.}$$

$$Z_B = 50 \angle 0^\circ \Omega, \quad I_B = 2.47 \angle -176.4^\circ \text{ Amp}$$

$$Z_C = 158 \angle 71.6^\circ \Omega, \quad I_C = 1.03 \angle 26.88^\circ \text{ Amp.}$$

What are the new phase voltage?

What is the voltage between new star point
& original point

Which phase got over voltage?



$$\begin{aligned} \text{Normal phase voltage} &= \frac{E_{\text{LINE}}}{\sqrt{3}} = \frac{200}{1.732} \\ &= 115 \text{ V} \end{aligned}$$

$$E_{AS} = I_A Z_A = 1.55 \angle -8.5^\circ \times 50 \angle 0^\circ = 1.55 \times 50 \angle -8.5 + 0$$

$$= 77.5 \angle -8.5^\circ \text{ V}$$

$$\begin{aligned} E_{BS} &= I_B Z_B = 2.47 \angle -176.4^\circ \times 50 \angle 0^\circ \\ &= 2.47 \times 50 \angle -176.4 + 0 \\ &= 123.5 \angle -176.4^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} E_{CS} &= I_C Z_C = 1.03 \angle 26.88^\circ \times 158 \angle 71.6^\circ \\ &= 1.03 \times 158 \angle 26.88 + 71.6 \\ &= 162.5 \angle 98.7^\circ \text{ V} \end{aligned}$$

$$E_{SM} = E_{AM} - E_{AS}$$

$$= 115 \angle 0^\circ - 77.5 \angle -8.5^\circ$$

$$= 115 - 77.5 (\cos 8.5 - j \sin 8.5)$$

Ph

A 3 ϕ 200V SYSTEM'S NEUTRAL WIRE IS BROKEN.
THE FOLLOWING LINE CURRENTS ARE FLOWING

$$Z_A = 50 \angle 0^\circ \Omega, \quad I_A = 1.55 \angle -8.5^\circ \text{ Amp.}$$

$$Z_B = 50 \angle 0^\circ \Omega, \quad I_B = 2.47 \angle -176.4^\circ \text{ Amp}$$

$$Z_C = 158 \angle 71.6^\circ \Omega, \quad I_C = 1.03 \angle 26.88^\circ \text{ Amp.}$$

(i) WHAT ARE THE NEW PHASE VOLTAGE?

(ii) WHAT IS THE VOLTAGE BETWEEN NEW STAR POINT
 & ORIGINAL POINT

(iii) WHICH PHASE GOT OVER VOLTAGE?



$$\begin{aligned} \text{NORMAL PHASE VOLTAGE} &= \frac{E_{\text{LINE}}}{\sqrt{3}} = \frac{200}{1.7321} \\ &= 115 \text{ V} \end{aligned}$$

$$E_{AS} = I_A Z_A = 1.55 \angle -8.5^\circ \times 50 \angle 0^\circ = 1.55 \times 50 \angle -8.5 + 0$$

$$= 77.5 \angle -8.5^\circ \text{ V}$$

$$E_{BS} = I_B Z_B = 2.47 \angle -176.4^\circ \times 50 \angle 0^\circ$$

$$= 2.47 \times 50 \angle -176.4 + 0$$

$$= 123.5 \angle -176.4^\circ \text{ V}$$

$$E_{CS} = I_C Z_C = 1.03 \angle 26.88^\circ \times 158 \angle 71.6^\circ$$

$$= 1.03 \times 158 \angle 26.88 + 71.6$$

$$= 162.5 \angle 98.48^\circ \text{ V}$$


$$E_{SX1} = E_{AN} - E_{AS}$$

$$= 115 \angle 0^\circ - 77.5 \angle -8.5^\circ$$

$$= 115 - 77.5 (\cos 8.5 - j \sin 8.5)$$

To calculate I_A, I_B, I_C at 3 wire
UNBALANCED condition, Δ load IS TO BE CONVERTED
TO Δ .


THEN FIND Δ UNBALANCED LINE CURRENTS

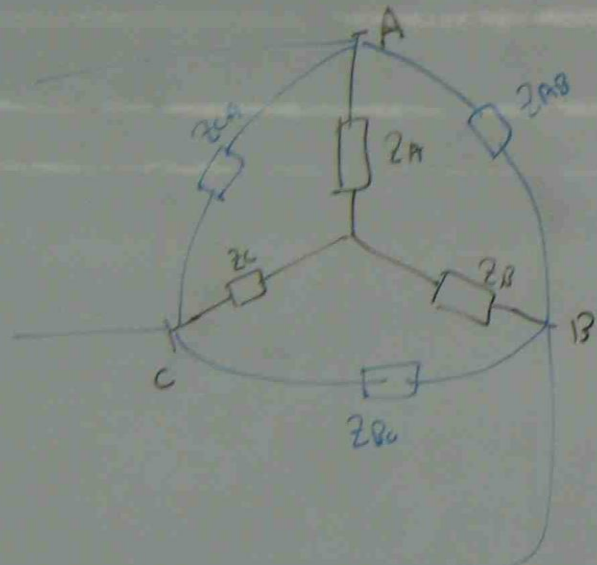

$$Z_{AB} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_C}$$

$$Z_{BC} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_A}$$
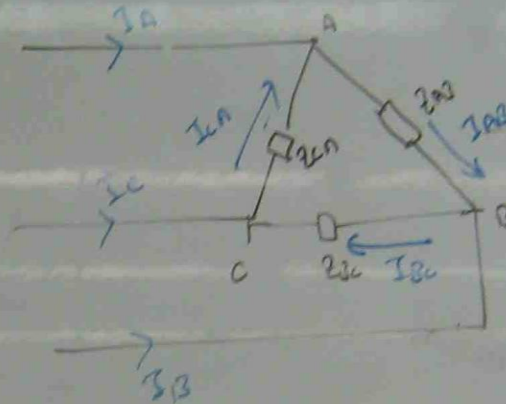
$$Z_{CA} = \frac{Z_A Z_B + Z_B Z_C + Z_C Z_A}{Z_B}$$



AT (A) $I_A + I_{CA} = I_{AB}$
 $I_A = I_{AB} - I_{CA}$

AT (B) $I_B + I_{AB} = I_{BC}$
 $I_B = I_{BC} - I_{AB}$

AT (C) $I_C + I_{BC} = I_{CA}$
 $I_C = I_{CA} - I_{BC}$

$$I_{AB} = \frac{V_{AB}}{Z_{AB}}$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}}$$

$$E_{AS} = I_A Z_A \quad E_{BS} = I_B Z_B$$

$$E_{CS} = I_C Z_C$$

$$E_{SN} = E_{AN} - E_{AS}$$

(OR)

$$E_{BN} = E_{BS} - E_{BS}$$

(OR)

$$E_{CN} = E_{CS} - E_{CS}$$