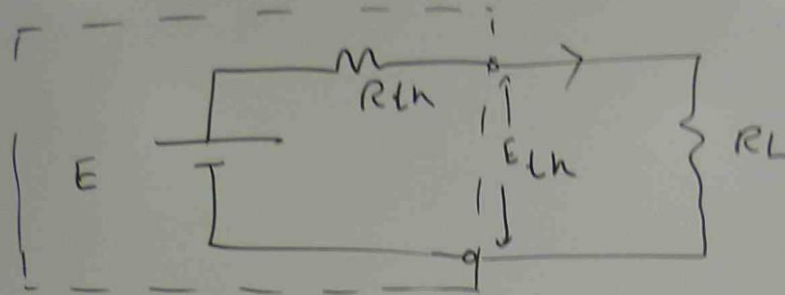


MAXIMUM POWER TRANSFER THEOREM



EQUIVALENT OF
BATTERY


R_L = LOAD RESISTANCE

R_{th} = BATTERY INTERNAL
RESISTANCE
(SOURCE RESISTANCE)

MAXIMUM POWER IS TRANSFERRED WHEN
BATTERY INTERNAL RESISTANCE IS
EQUAL TO LOAD RESISTANCE.

$$R_{th} = R_L \rightarrow P_{max}$$

MAXIMUM POWER TRANSFER THEOREM

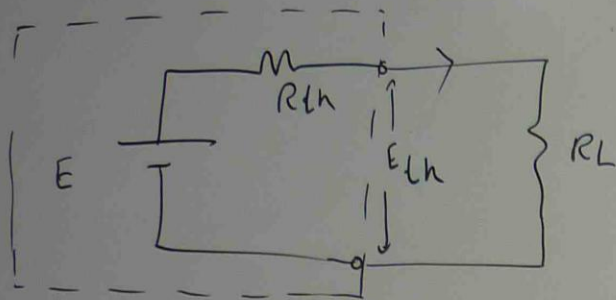

EQUIVALENT OF
BATTERY

R_{th} = BATTERY INTERNAL
RESISTANCE
(SOURCE RESISTANCE)

R_L = LOAD RESISTANCE

MAXIMUM POWER IS TRANSFERRED WHEN
BATTERY INTERNAL RESISTANCE IS
EQUAL TO LOAD RESISTANCE.

$$R_{th} = R_L \rightarrow P_{max}$$


$$\% \text{ EFFICIENCY } (\% \eta) = \frac{\text{LOAD POWER}}{\text{SOURCE POWER}} \times 100$$

$$\text{LOAD MAXIMUM POWER} = \frac{E_{th}^2}{4 R_{th}}$$


LOAD RESISTANCE AT MAXIMUM POWER
TRANSFER

$$R_L = \frac{n R_{th}}{1 - n}$$

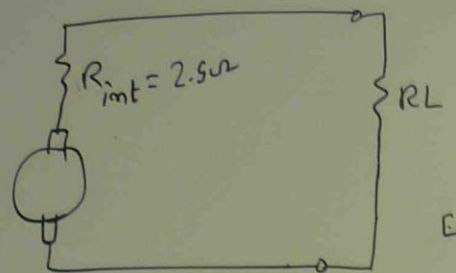
EX A DC GENERATOR, BATTERY AND
LABORATORY SUPPLY ARE CONNECTED TO A
RESISTIVE LOAD R_L IN FIGURE (a) (b)
AND (c) RESPECTIVELY.



(a) DC GENERATOR

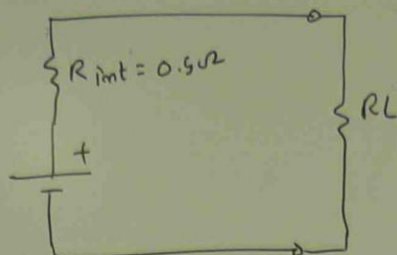

(b) BATTERY

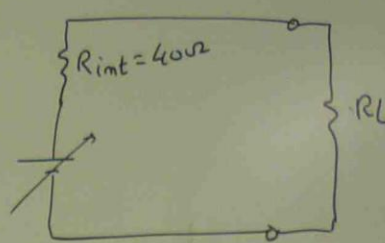

(c) LABORATORY

(a) FOR EACH, DETERMINE THE VALUE OF R_L FOR MAXIMUM POWER TRANSFER TO R_L

(b) DETERMINE R_L FOR 75% EFFICIENCY

(a) DC GENERATOR

$$R_L = R_{th} = 2.5 \Omega$$

(b) BATTERY

$$R_L = R_{th} = 0.5 \Omega$$

(c) LABORATORY

$$R_L = R_{th} = 40 \Omega$$

$$(b) R_L = \frac{n R_{th}}{1 - n}$$


$$75\% \rightarrow n = 0.75$$

$$(a) R_L = \frac{0.75 \times 2.5}{1 - 0.75} = \frac{0.75 \times 2.5}{0.25} = 7.5 \Omega$$

$$(b) R_L = \frac{0.75 \times 0.5}{1 - 0.75} = \frac{0.75 \times 0.5}{0.25} = 1.5 \Omega$$

$$(c) R_L = \frac{0.75 \times 40}{1 - 0.75} = \frac{0.75 \times 40}{0.25} = 120 \Omega$$

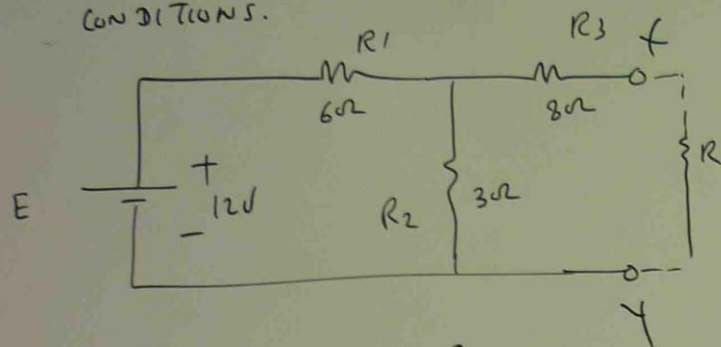EX FOR THE NETWORK OF GIVEN FIGURE, DETERMINE THE VALUE OF R FOR MAXIMUM POWER TO R . AND CALCULATE THE POWER DELIVERED UNDER THESE CONDITIONS.




$E_{th} = ?$
↑
THEVENIN'S
EQUIVALENT
VOLTAGE

$R_{th} = ?$
↑
THEVENIN'S
EQUIVALENT
RESISTANCE.

E_{th}

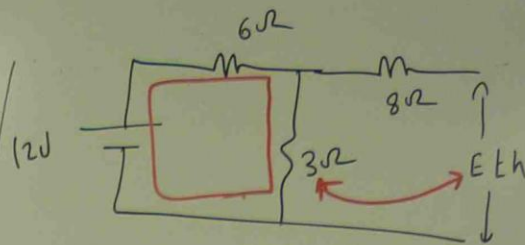- REMOVE LOAD RESISTANCE
- CALCULATE THE VOLTAGE ACROSS TERMINAL



$E_{th} = \text{VOLTAGE ACROSS } 3\Omega$

$$V_{3\Omega} = E \times \frac{3\Omega}{3\Omega + 6\Omega}$$



$$V_{R2} = E \times \frac{R2}{R1 + R2}$$

$$V_{R1} = E \times \frac{R1}{R1 + R2}$$

POTENTIAL DIVIDER
THEOREM

$$V_{3\Omega} = 12 \times \frac{3}{3+6}$$

$$= \frac{36}{9} = 4V$$

$$V_{3\Omega} = E_{th} = 4V$$


$$R_{th} = ?$$

- To find R_{th} , kill the source



- Find the equivalent resistance across terminal

Kill the source


CURRENT SOURCE

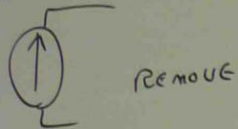


VOLTAGE SOURCE

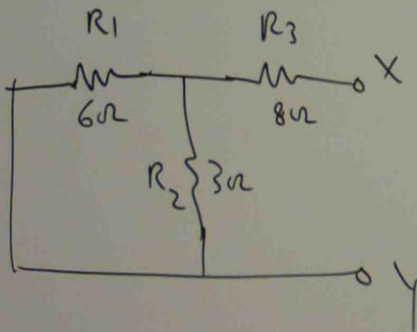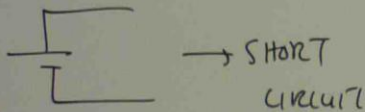
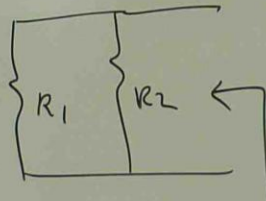
$$R_{xy} = R_{th} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$



$$R_{12} = \frac{R_1 R_2}{R_1 + R_2}$$

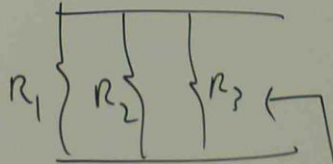

$$R_{123} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$R_{th} = 8 + \frac{6 \times 3}{6 + 3} = 8 + \frac{18}{9} = 10 \Omega$$



$$P_{max} = \frac{E_{th}^2}{4 R_{th}}$$

$$= \frac{4^2}{4 \times 10}$$

$$= \frac{16}{40}$$

$$= 0.4 \text{ WATT}$$

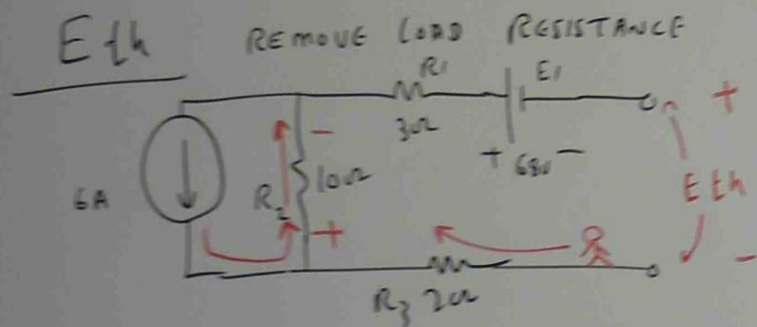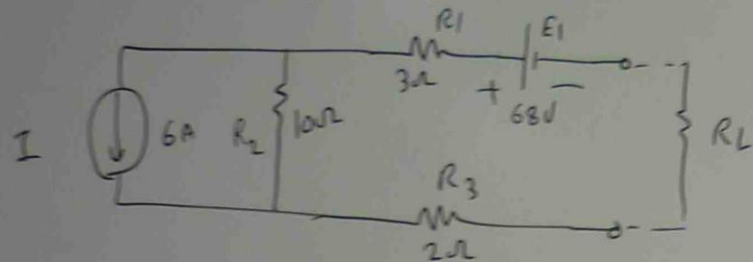
E+ FIND THE VALUE OF R_L IN FIGURE FOR MAXIMUM POWER TO R_L AND DETERMINE THE MAXIMUM POWER



$$(+6 \times 10) + (+68) + E_{th} = 0$$


$$128 + E_1 = 0$$

$$E_1 = -128$$

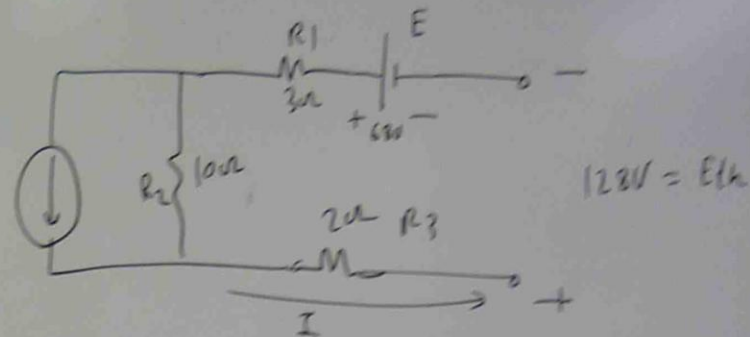

R_{th}

KILL THE SOURCE

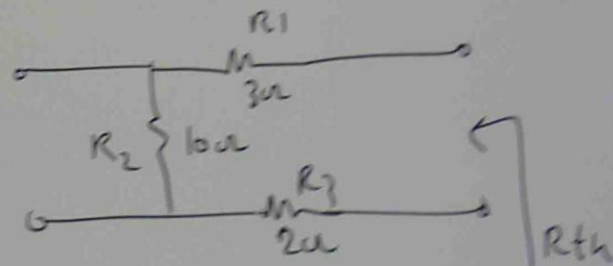

$$R_{th} = R_1 + R_2 + R_3$$

$$= 10 + 3 + 2 = 15\Omega$$

To flow maximum power $R_L = R_{th}$



$$\therefore R_L = 15\Omega$$

$$P_{L \max} = \frac{E_{th}^2}{4 R_{th}}$$

$$= \frac{128^2}{4 \times 15}$$

$$= 237.07 \text{ WATT}$$

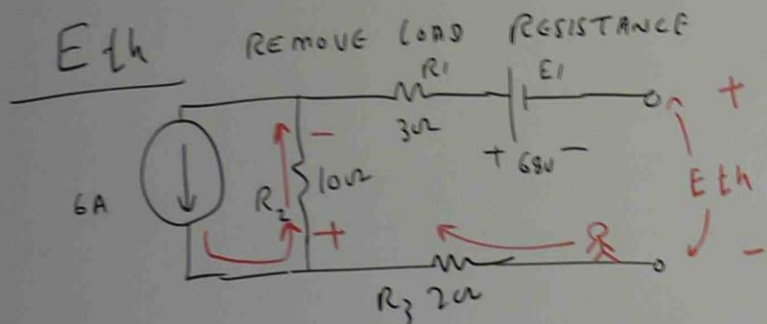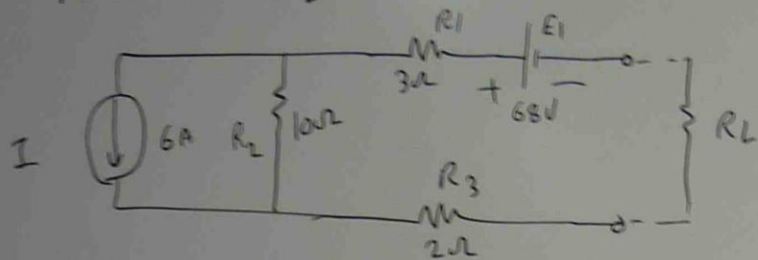
Ex FIND THE VALUE OF R_L IN FIGURE FOR MAXIMUM POWER TO R_L AND DETERMINE THE MAXIMUM POWER



$$(+6 \times 10) + (+68) + E_{th} = 0$$


$$128 + 61 = 0$$

$$E_1 = -128$$

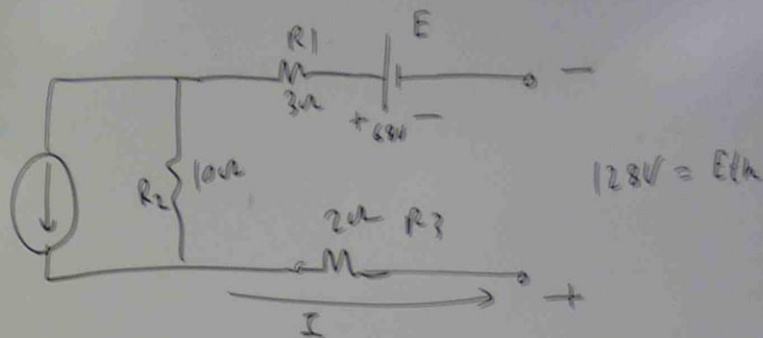

R_{th}

KILL THE SOURCE

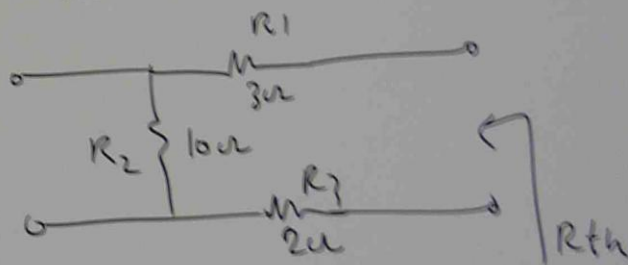

$$R_{th} = R_1 + R_2 + R_3$$

$$= 10 + 3 + 2 = 15\Omega$$

To flow maximum power $R_L = R_{th}$


$$\therefore R_L = 15 \Omega$$

$$P_{L \max} = \frac{E_{th}^2}{4 R_{th}}$$

$$= \frac{128^2}{4 \times 15}$$


$$= 237.07 \text{ WATT}$$

MILLMAN'S THEOREM

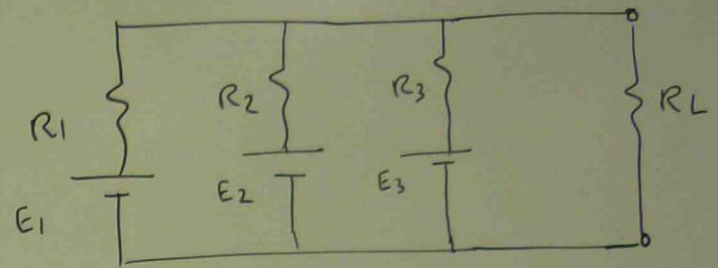


$$E_{eq} = \frac{\frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$
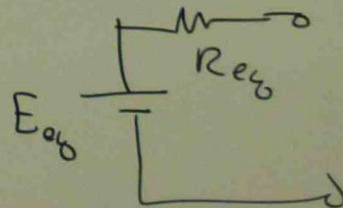
$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$



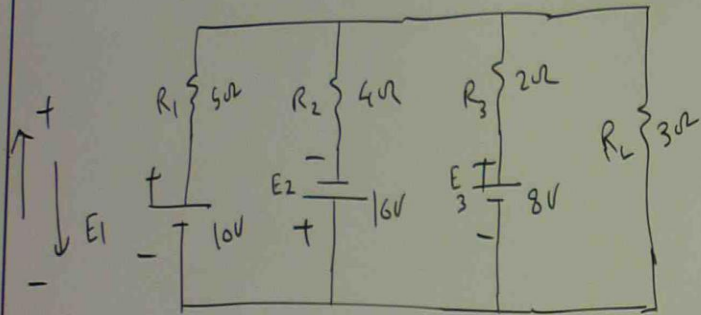Ex USING MILLMAN'S THEOREM, FIND THE CURRENT THROUGH AND VOLTAGE ACROSS THE R_L




$$E_{eq} = \frac{\left(+\frac{E_1}{R_1}\right) + \left(-\frac{E_2}{R_2}\right) + \left(+\frac{E_3}{R_3}\right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$= \frac{\left(\frac{10}{5}\right) + \left(-\frac{16}{4}\right) + \left(\frac{8}{2}\right)}{\frac{1}{5} + \frac{1}{4} + \frac{1}{2}}$$

$$E_{eq} = \frac{2 - 4 + 4}{0.2 + 0.25 + 0.5}$$

$$= \frac{2}{0.95}$$

$$= 2.105 \text{ V}$$

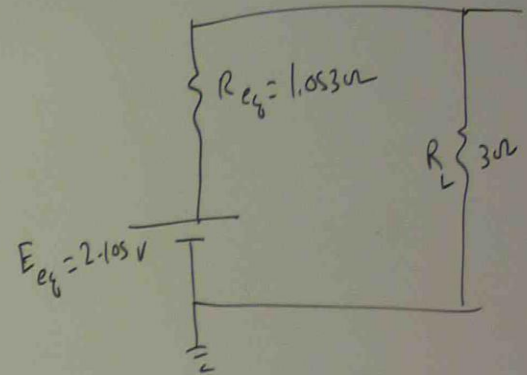

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$= \frac{1}{\frac{1}{5} + \frac{1}{4} + \frac{1}{2}}$$

$$= \frac{1}{0.2 + 0.25 + 0.5}$$

$$= \frac{1}{0.95} = 1.053 \Omega$$

