

G048

CURRENT SOURCE AND VOLTAGE SOURCE

VOLTAGE SOURCE

BATTERY




=




CURRENT SOURCE


TRANSISTOR

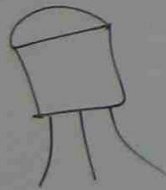


=

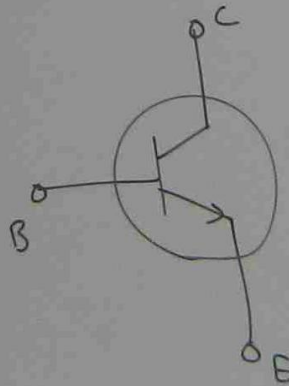

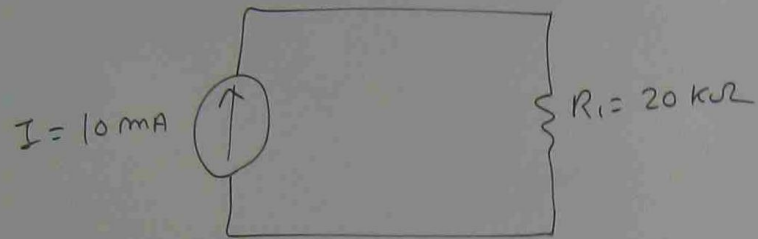Ex FIND THE SOURCE VOLTAGE V_S AND CURRENT I_1 FOR THE GIVEN CIRCUIT.



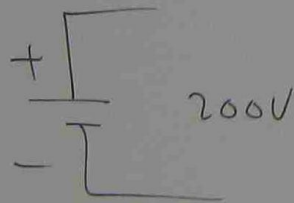
$$\begin{aligned} V_S &= I R_1 \\ &= 10 \text{ mA} \times 20 \text{ k} \\ &= 10 \times 10^{-3} \times 20 \times 10^3 \\ &= 200 \text{ V} \end{aligned}$$



Ex

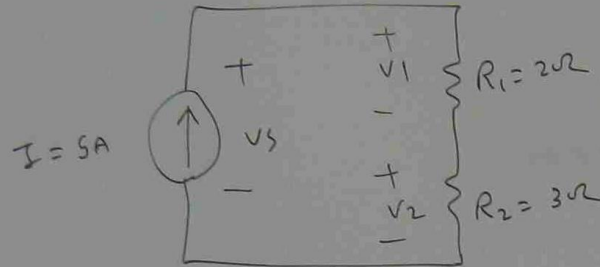CALCULATE THE VOLTAGES V_1 , V_2 AND V_S FOR THE GIVEN CIRCUIT




$$V = I R$$

$$V_1 = I R_1 = 5 \times 2 = 10 \text{ V}$$

$$V_2 = I R_2 = 5 \times 3 = 15 \text{ V}$$

$$V_S = V_1 + V_2 = 10 + 15 = 25 \text{ V}$$


POTENTIAL DIVIDER AND CURRENT DIVIDER

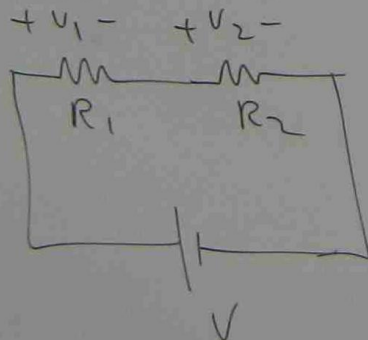

$$V_1 = V \times \frac{R_1}{R_1 + R_2}$$

$$V_2 = V \times \frac{R_2}{R_1 + R_2}$$

POTENTIAL DIVIDER
THEOREM

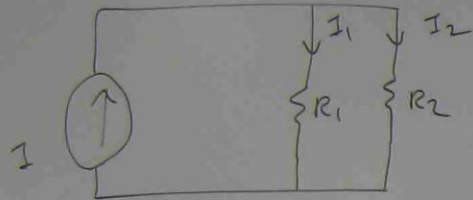


CURRENT
DIVIDER
THEOREM

$$I_1 = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \frac{R_1}{R_1 + R_2}$$

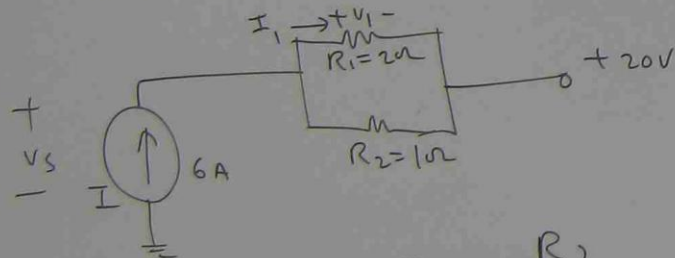Ex DETERMINE THE CURRENT I_1 AND THE VOLTAGE V_S FOR THE GIVEN NETWORK.





$$I_1 = I \times \frac{R_2}{R_1 + R_2}$$

$$= 6 \times \frac{1}{2+1}$$

$$= \frac{6}{3} = 2A$$


$$V_1 = I_1 R_1$$

$$= 2 \times 2 = 4V$$

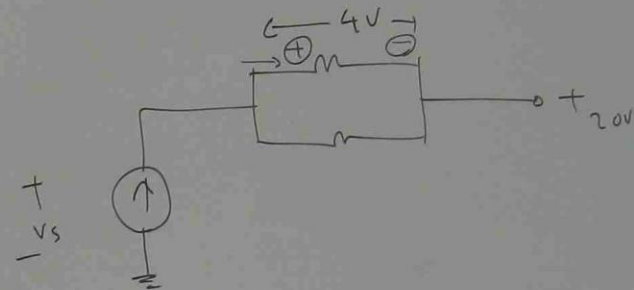
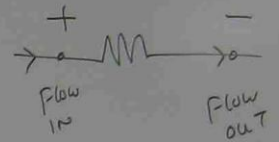


$$V_S = 4 + 20 = 24V$$

SOURCE CONVERSION




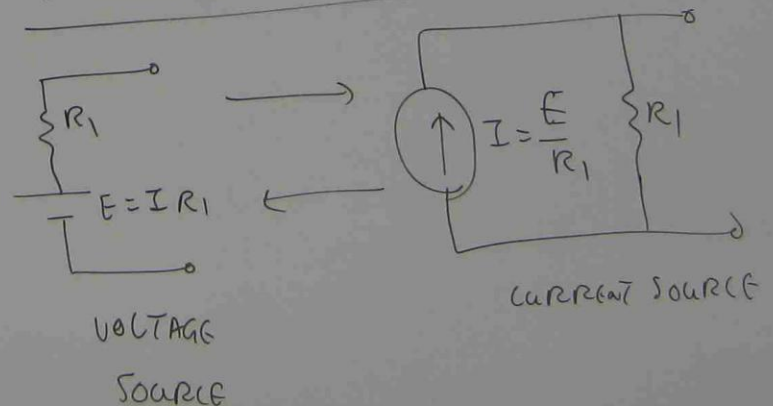


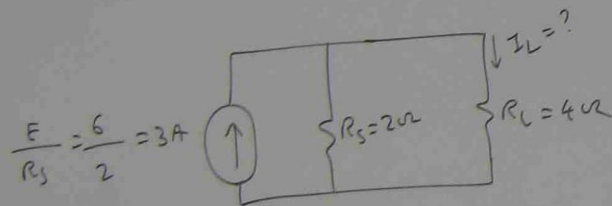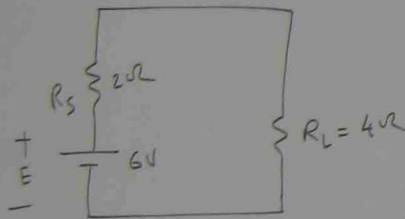Ex CONVERT THE VOLTAGE SOURCE OF GIVEN FIGURE TO A CURRENT SOURCE AND CALCULATE THE CURRENT THROUGH THE 4Ω LOAD




$$\begin{aligned}
 I_L &= I_T \times \frac{R_S}{R_S + R_L} \\
 &= 3 \times \frac{2}{2 + 4} \\
 &= \frac{12}{6} \\
 &= 2A
 \end{aligned}$$

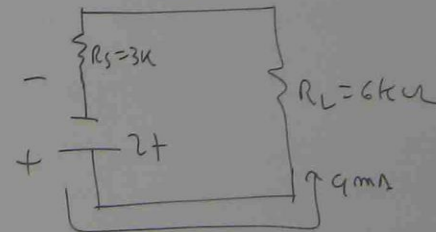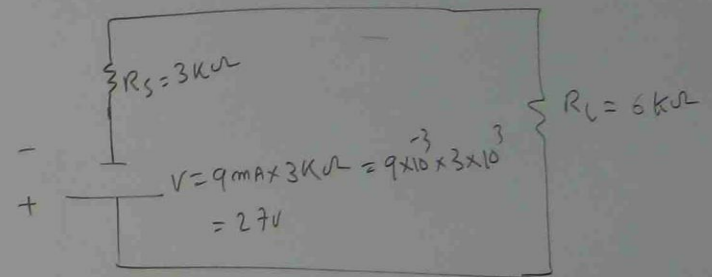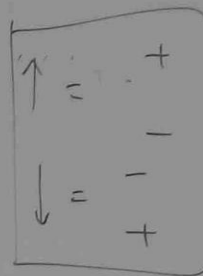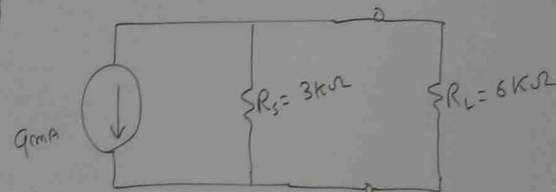Ex CONVERT THE GIVEN CURRENT SOURCE TO A VOLTAGE SOURCE AND FIND THE LOAD CURRENT FOR EACH SOURCE.



LOAD CURRENT = qmA


CURRENT SOURCES IN PARALLEL

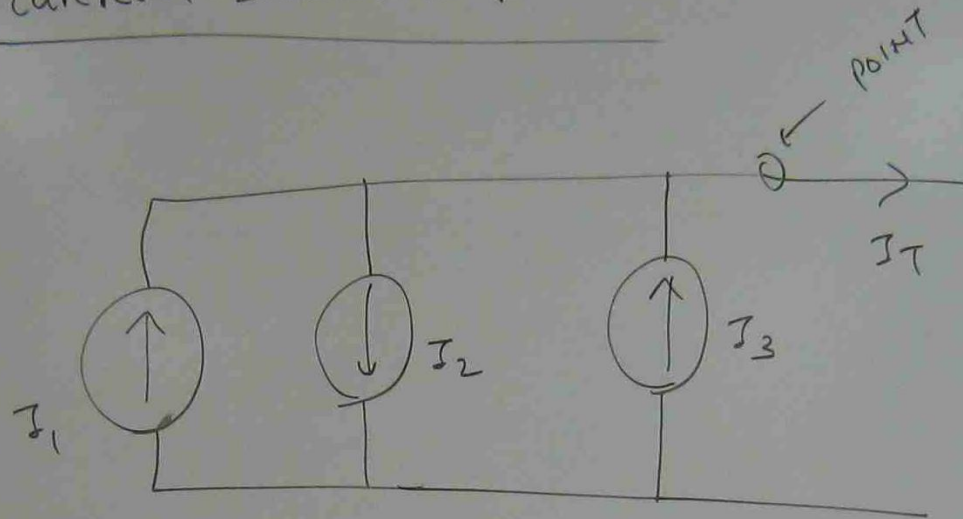


→ ○
flow in (+)

○ →
flow out (-)

$$I_T = +I_1 - I_2 + I_3$$

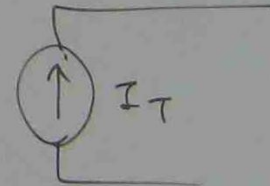

VOLTAGE SOURCES IN SERIES

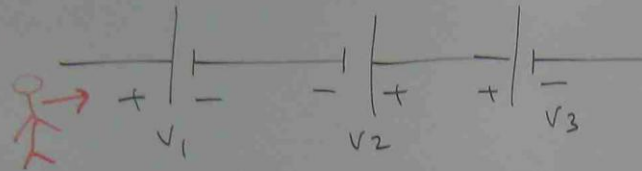


If $\xleftarrow{+}$ Then $\xrightarrow{-}$

If $\xleftarrow{-}$ Then $\xrightarrow{+}$





$$V_T = +V_1 + (-V_2) + (+V_3)$$

$$V_T = V_1 - V_2 + V_3$$

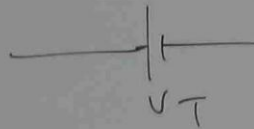

$$\frac{1}{R_T} = \frac{1}{R_T}$$

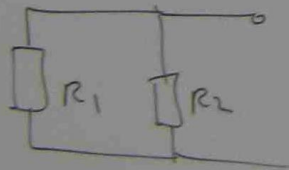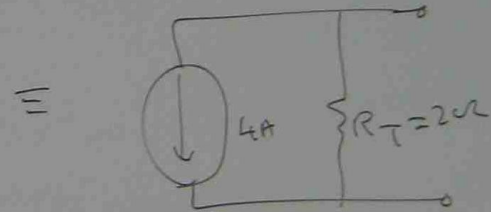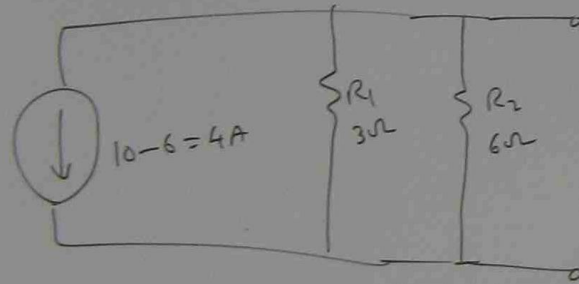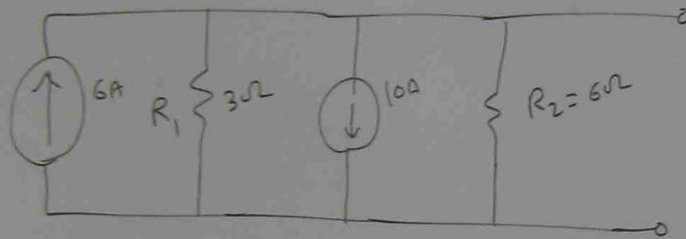Ex REDUCE THE PARALLEL CURRENT SOURCES OF GIVEN FIGURE TO A SINGLE CURRENT SOURCE.



$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_T = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2\Omega$$


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{R_1 + R_2}{R_1 R_2}$$

$$V_1 + (-V_2) + (+V_3)$$

$$-V_2 + V_3$$

KIRCHOFF'S VOLTAGE LAW

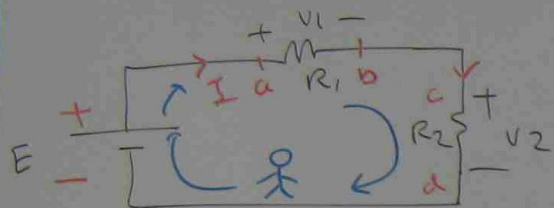

$$(-E) + (+V_1) + (+V_2) = 0$$

$$-E + V_1 + V_2 = 0$$

$$-E + IR_1 + IR_2 = 0$$

APPLICATION OF DETERMINANT TO
SOLVE THE EQUATIONS

2 unknowns

$$\begin{cases} a_1 I_1 + a_2 I_2 = m_1 \\ b_1 I_1 + b_2 I_2 = m_2 \end{cases}$$

$$I_1 = \frac{\begin{vmatrix} m_1 & a_2 \\ m_2 & b_2 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 \\ b_1 & b_2 \end{vmatrix}} = \frac{m_1 b_2 - m_2 a_2}{a_1 b_2 - b_1 a_2}$$

$$I_2 = \frac{\begin{vmatrix} a_1 & m_1 \\ b_1 & m_2 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 \\ b_1 & b_2 \end{vmatrix}} = \frac{a_1 m_2 - b_1 m_1}{a_1 b_2 - b_1 a_2}$$

3 unknown

$$a_1 I_1 + a_2 I_2 + a_3 I_3 = m_1$$

$$b_1 I_1 + b_2 I_2 + b_3 I_3 = m_2$$

$$c_1 I_1 + c_2 I_2 + c_3 I_3 = m_3$$

$$I_1 = \frac{\begin{vmatrix} m_1 & a_2 & a_3 \\ m_2 & b_2 & b_3 \\ m_3 & c_2 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$I_2 = \frac{\begin{vmatrix} a_1 & m_1 \\ b_1 & m_2 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 \\ b_1 & b_2 \end{vmatrix}} = \frac{a_1 m_2 - b_1 m_1}{a_1 b_2 - b_1 a_2}$$

3 unknown

$$a_1 I_1 + a_2 I_2 + a_3 I_3 = m_1$$

$$b_1 I_1 + b_2 I_2 + b_3 I_3 = m_2$$

$$c_1 I_1 + c_2 I_2 + c_3 I_3 = m_3$$

$$I_1 = \frac{\begin{vmatrix} m_1 & a_2 & a_3 \\ m_2 & b_2 & b_3 \\ m_3 & c_2 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$I_2 = \frac{\begin{vmatrix} a_1 & m_1 & a_3 \\ b_1 & m_2 & b_3 \\ c_1 & m_3 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$


$$I_3 = \frac{\begin{vmatrix} a_1 & a_2 & m_1 \\ b_1 & b_2 & m_2 \\ c_1 & c_2 & m_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$I_1 = \frac{\begin{vmatrix} m_1 & a_2 & a_3 \\ m_2 & b_2 & b_3 \\ m_3 & c_2 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$I_1 = \frac{\begin{vmatrix} m_1 & a_2 & a_3 & m_1 & a_2 \\ m_2 & b_2 & b_3 & m_2 & b_2 \\ m_3 & c_2 & c_3 & m_3 & c_2 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 & a_1 & a_2 \\ b_1 & b_2 & b_3 & b_1 & b_2 \\ c_1 & c_2 & c_3 & c_1 & c_2 \end{vmatrix}}$$

$$= \frac{(m_1 b_2 c_3 + a_2 b_3 m_3 + a_3 m_2 c_2) - (m_3 b_2 a_3 + c_2 b_3 m_1 + c_3 m_2 a_2)}{(a_1 b_2 c_3 + a_2 b_3 c_1 + a_3 b_1 c_2) - (c_1 b_2 a_3 + c_2 b_3 a_1 + c_3 b_1 a_2)}$$

ET

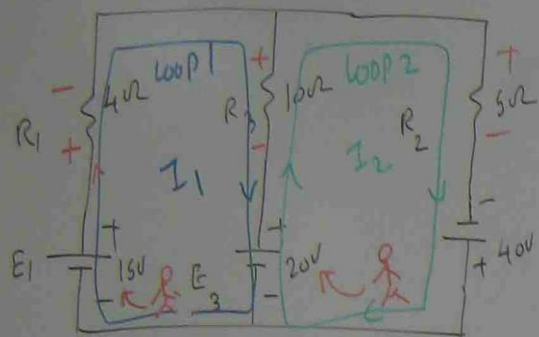

FIND CURRENT I_1 AND I_2

Loop (1)

$$(-15) + (+I_1 R_1) + (I_1 - I_2) R_3 + (+20) = 0$$

$$-15 + I_1 \times 4 + (I_1 - I_2) 10 + 20 = 0$$

$$-15 + 4I_1 + 10I_1 - 10I_2 + 20 = 0$$

$$14I_1 - 10I_2 + 5 = 0$$

$$14I_1 - 10I_2 = -5 \quad (1)$$

Loop (2)

$$(-20) + (I_2 - I_1)(-R_3) + (+I_2 R_2) + (-40) = 0$$

$$-20 + (I_2 - I_1)(-10) + I_2 \times 5 - 40 = 0$$

$$-20 - 10I_2 + 10I_1 + 5I_2 - 40 = 0$$

$$10I_1 - 5I_2 - 60 = 0$$

$$10I_1 - 5I_2 = 60 \quad (2)$$

$$14I_1 - 10I_2 = -5 \quad (1)$$

$$a_1 I_1 + a_2 I_2 = m_1$$

$$a_1 = 14, a_2 = -10, m_1 = -5$$

$$10I_1 - 5I_2 = 60 \quad \text{--- (2)}$$

$$b_1 I_1 + b_2 I_2 = m_2$$

$$b_1 = 10, \quad b_2 = -5, \quad m_2 = 60$$

$$I_1 = \frac{m_1 b_2 - m_2 a_2}{a_1 b_2 - b_1 a_2}$$

$$= \frac{(-5)(-5) - 60 \times (-10)}{14 \times (-5) - 10 \times (-10)}$$


$$= \frac{25 + 600}{-70 + 100} = \frac{625}{30}$$

$$I_2 = \frac{a_1 m_2 - b_1 m_1}{a_1 b_2 - b_1 a_2}$$

$$= \frac{14 \times 60 - 10 \times (-5)}{30}$$

$$= \frac{840 + 500}{30} = \frac{1340}{30}$$

KIRCHHOFF'S VOLTAGE LAW

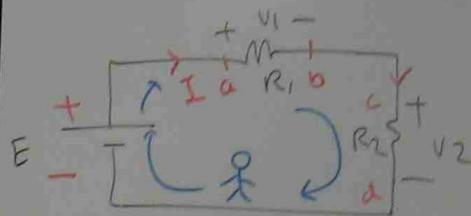

$$(-E) + (+V_1) + (+V_2) = 0$$

$$-E + V_1 + V_2 = 0$$

$$-E + IR_1 + IR_2 = 0$$

APPLICATION OF DETERMINANT TO
SOLVE THE EQUATIONS

$$\begin{cases} a_1 I_1 + a_2 I_2 = m_1 \\ b_1 I_1 + b_2 I_2 = m_2 \end{cases}$$

$$I_1 = \frac{\begin{vmatrix} m_1 & a_2 \\ m_2 & b_2 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 \\ b_1 & b_2 \end{vmatrix}} = \frac{m_1 b_2 - m_2 a_2}{a_1 b_2 - b_1 a_2}$$

$$I_2 = \frac{\begin{vmatrix} a_1 & m_1 \\ b_1 & m_2 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 \\ b_1 & b_2 \end{vmatrix}}$$

$$= \frac{a_1 m_2 - b_1 m_1}{a_1 b_2 - b_1 a_2}$$

3 unknown

$$a_1 I_1 + a_2 I_2 + a_3 I_3 = m_1$$

$$b_1 I_1 + b_2 I_2 + b_3 I_3 = m_2$$

$$c_1 I_1 + c_2 I_2 + c_3 I_3 = m_3$$

$$I_1 = \frac{\begin{vmatrix} m_1 & a_2 & a_3 \\ m_2 & b_2 & b_3 \\ m_3 & c_2 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$I_2 = \frac{\begin{vmatrix} a_1 & m_1 & a_3 \\ b_1 & m_2 & b_3 \\ c_1 & m_3 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$I_3 = \frac{\begin{vmatrix} a_1 & a_2 & m_1 \\ b_1 & b_2 & m_2 \\ c_1 & c_2 & m_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$


$$I_1 = \frac{\begin{vmatrix} m_1 & a_2 & a_3 \\ m_2 & b_2 & b_3 \\ m_3 & c_2 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$\frac{\left[11 \times 10 \times 0 + (-3)(0)(-8) + (15)(-3)(-5) \right] - \left[(-8) \times 10 \times 15 + (-5) \times 0 \times 11 + 0 \times (-3)(-3) \right]}{\left[11 \times 10 \times 23 + (-3)(-5) \times (-8) + (-8) \times (-3)(-5) \right] - \left[(-8)(10)(-8) + (-5)(-5) \times 11 + 23(-3)(-3) \right]}$$

$$= 1.22 \text{ Amp}$$

pb

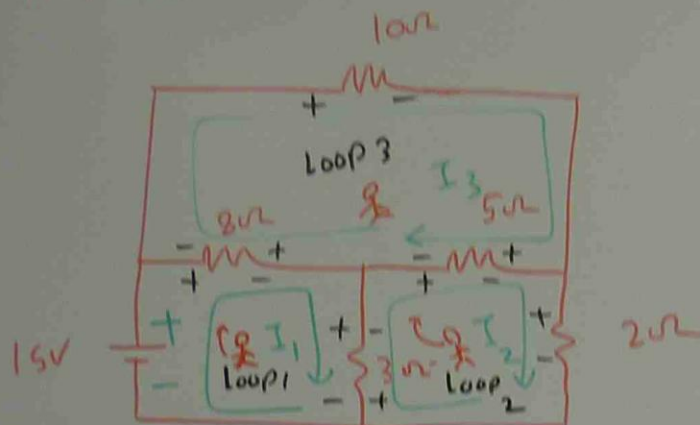FIND THE CURRENT THROUGH THE 10Ω RESISTOR OF THE NETWORK



Loop ①

$$-15 + \left[+(I_1 - I_3) \right] \times 8 + \left[+(I_1 - I_2) \right] \times 3 = 0$$

$$8I_1 - 8I_3 + 3I_1 - 3I_2 = 15$$

$$11I_1 - 3I_2 - 8I_3 = 15 \quad \text{--- (1)}$$

Loop ②

$$\left[+(I_2 - I_1) \right] \times 3 + \left[+(I_2 - I_3) \right] \times 5 + \left[+I_2 \right] \times 2 = 0$$

$$3I_2 - 3I_1 + 5I_2 - 5I_3 + 2I_2 = 0$$

$$-3I_1 + 10I_2 - 5I_3 = 0 \quad \text{--- (2)}$$

Loop ③ $\left[+ (I_3 - I_1) \right] \times 8 + \left[+ (I_3 \times 10) \right] + \left[+ (I_3 - I_2) \right] \times 5 = 0$

$$8I_3 - 8I_1 + 10I_3 + 5I_3 - 5I_2 = 0$$

$$-8I_1 - 5I_2 + 23I_3 = 0 \quad \text{--- (3)}$$

$$a_1 I_1 + a_2 I_2 + a_3 I_3 = m_1$$

$$b_1 I_1 + b_2 I_2 + b_3 I_3 = m_2$$

$$c_1 I_1 + c_2 I_2 + c_3 I_3 = m_3$$

$= 0$

$$I_1 = \frac{\begin{vmatrix} m_1 & a_2 & a_3 \\ m_2 & b_2 & b_3 \\ m_3 & c_2 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$I_2 = \frac{\begin{vmatrix} a_1 & m_1 & a_3 \\ b_1 & m_2 & b_3 \\ c_1 & m_3 & c_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$I_3 = \frac{\begin{vmatrix} a_1 & a_2 & m_1 \\ b_1 & b_2 & m_2 \\ c_1 & c_2 & m_3 \end{vmatrix}}{\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}}$$

$$I_1 = \begin{vmatrix} m_1 & a_2 & a_3 \\ m_2 & b_2 & b_3 \\ m_3 & c_2 & c_3 \end{vmatrix}$$

$$\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}$$

$$I_2 = \begin{vmatrix} a_1 & m_1 & a_3 \\ b_1 & m_2 & b_3 \\ c_1 & m_3 & c_3 \end{vmatrix}$$

$$\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}$$

$$I_3 = \begin{vmatrix} a_1 & a_2 & m_1 \\ b_1 & b_2 & m_2 \\ c_1 & c_2 & m_3 \end{vmatrix}$$

$$\begin{vmatrix} a_1 & a_2 & a_3 \\ b_1 & b_2 & b_3 \\ c_1 & c_2 & c_3 \end{vmatrix}$$

$$I_3 = \begin{vmatrix} 11 & -3 & 15 \\ -3 & 10 & 0 \\ -8 & -5 & 0 \end{vmatrix}$$

$$\begin{vmatrix} 11 & -3 & -8 \\ -3 & 10 & -5 \\ -8 & -5 & 23 \end{vmatrix}$$

$$I_3 = \begin{vmatrix} 11 & -3 & 15 & 11 & -3 \\ -3 & 10 & 0 & -3 & 10 \\ -8 & -5 & 0 & -8 & -5 \end{vmatrix}$$

$$\begin{vmatrix} 11 & -3 & -8 & 11 & -3 \\ -3 & 10 & -5 & -3 & 10 \\ -8 & -5 & 23 & -8 & -5 \end{vmatrix}$$

$$= [11 \times 11]$$

$$[11 \times 10]$$

$$=$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$= \frac{60 \times 60 + 60 \times 60 + 60 \times 60}{60}$$

$$= 180\Omega$$


$$R_2 = \frac{R_B \times R_C}{R_A + R_B + R_C} = \frac{20 \times 10}{60} = \frac{200}{60} = 3.33\Omega$$

$$R_3 = \frac{R_C \times R_A}{R_A + R_B + R_C} = \frac{10 \times 30}{60} = \frac{300}{60}$$

$$= 5\Omega$$



Ex CONVERT Δ OF GIVEN CIRCUIT TO λ

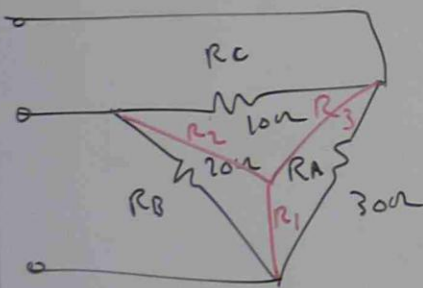

$$R_1 = \frac{R_A \times R_B}{R_A + R_B + R_C} = \frac{30 \times 20}{30 + 20 + 10}$$

$$= \frac{600}{60} = 10\Omega$$

