

- CALCULATE (a) ALL LINE CURRENTS IN POLAR FORM
 (b) READING OF WATT METER W_1 & W_2
 (c) TOTAL REAL POWER
 (d) TOTAL REACTIVE POWER

SEQUENCE A-B-C

$$\begin{aligned}
 E_{CA} &= 200 \angle +120^\circ \text{ V} \\
 E_{AB} &= 200 \angle 0^\circ \text{ V} \\
 E_{BC} &= 200 \angle -120^\circ \text{ V} \\
 A \rightarrow B \rightarrow C
 \end{aligned}$$

$$\begin{aligned}
 Z_{AB} &= 3 + j4 = \sqrt{3^2 + 4^2} \angle \tan^{-1} \frac{4}{3} = 5 \angle 53.1^\circ \Omega \\
 Z_{BC} &= 3 - j4 = \sqrt{3^2 + 4^2} \angle -\tan^{-1} \frac{4}{3} = 5 \angle -53.1^\circ \Omega \\
 Z_{CA} &= 5 + j6 = \sqrt{5^2 + 6^2} \angle \tan^{-1} \frac{6}{5} = 7.81 \angle 50.2^\circ \Omega
 \end{aligned}$$

$$\begin{aligned}
 I_{AB} &= \frac{E_{AB}}{Z_{AB}} = \frac{200 \angle 0^\circ}{5 \angle 53.1^\circ} = 40 \angle -53.1^\circ \text{ Amp} \\
 I_{BC} &= \frac{E_{BC}}{Z_{BC}} = \frac{200 \angle -120^\circ}{5 \angle -53.1^\circ} = 40 \angle 120 + 53.1^\circ \text{ Amp.} \\
 I_{CA} &= \frac{E_{CA}}{Z_{CA}} = \frac{200 \angle 120^\circ}{7.81 \angle 50.2^\circ} = 25.6 \angle 69.8^\circ \text{ Amp.}
 \end{aligned}$$

A point
 $I_{\text{flow out}} = \text{flow out}$

$$I_A + I_{CB} = I_{AB}$$

$$I_B = I_{AB} - I_{CB}$$

$$= 40 \angle -53.2^\circ - 25.6 \angle 69.8^\circ$$

$$= 40(\cos 53.2^\circ - j \sin 53.2^\circ) - 25.6 \left(\frac{\cos 69.8^\circ + j \sin 69.8^\circ}{1} \right)$$

$$= 24 - j 32 - 25.6(0.345 + j 0.438)$$

$$= 24 - j 32 - (8.83 + j 24)$$

$$= 24 - j 32 - 8.83 - j 24$$

$$\bar{I}_A = 15.17 - j 56 = \sqrt{15.17^2 + 56^2} \angle -\tan^{-1} \frac{56}{15.17}$$

$$= 58 \angle -74.2^\circ \text{ A amp.}$$

B point

$$I_0 + I_{AB} = I_{BC}$$

$$I_0 = I_{BC} - I_{AB} = 40 \angle -66.8^\circ - 40 \angle -53.2^\circ$$

$$= 40(\cos 66.8^\circ - j \sin 66.8^\circ) - (24 - j 32)$$

$$= 15.75 - j 36.75 - 24 + j 32$$

$$I_B = -8.25 - j4.76 = \sqrt{8.25^2 + 4.76^2} \angle \left(180 - \tan^{-1} \frac{-4.76}{8.25} \right)$$

$$= 9.52 \angle (-130 - 30)$$

$$= 9.52 \angle (-150) \text{ Amps}$$

~~IT~~
C POINT T

$$I_C + I_{BC} = I_{CA}$$

$$I_C = I_{CA} - I_{BC} = (8.25 + j24) - (15.76 - j36.76)$$

$$= 8.25 + j24 - 15.76 + j36.76$$

$$= -6.87 + j60.76$$

~~N~~
$$= \sqrt{6.87^2 + 60.76^2} \angle \left(180 - \tan^{-1} \frac{60.76}{6.87} \right)$$

$$= 61.147 \angle 180 - 83.54$$

$$I_C = 61.147 \angle 96.46^\circ \text{ A}$$

$$W_1 = E_{AB} I_A \cos \theta_{IA}^{E_{AB}}$$


$$E_{AB} = 200 \angle 0^\circ$$

$$I_A = 58$$

$$= 200 \times 58 \times \cos 74.8$$

$$= 11600 \times 0.262 = 3039.2 \text{ W}$$
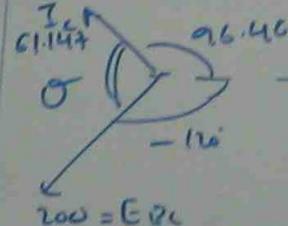
$$W_2 = E_{BC} I_C \cos \theta_{IC}^{E_{BC}}$$



$$\theta_{IC} = 360 - (96.46 + 120)$$

$$= 143.54$$

$$W_2 = 200 \times 61.147 \cos 143.54$$

$$= 12229.4 \times (-0.804)$$

$$= -9835 \text{ W}$$

$$W_T = |W_1| + |W_2| = |3039.2| + |-9835| = 3039.2 + 9835$$

$$= 12874 \text{ W}$$