

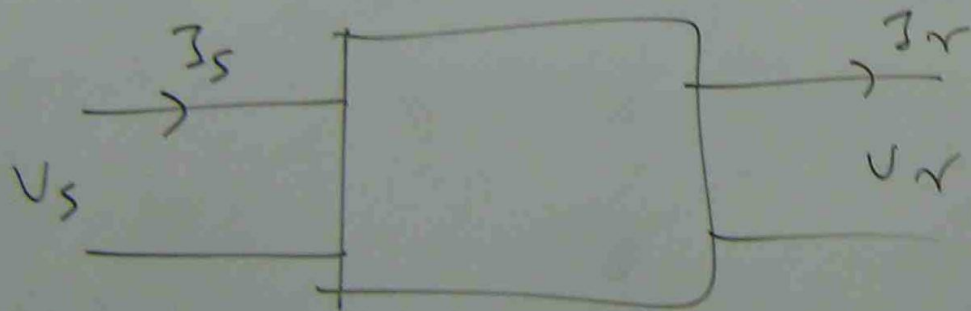
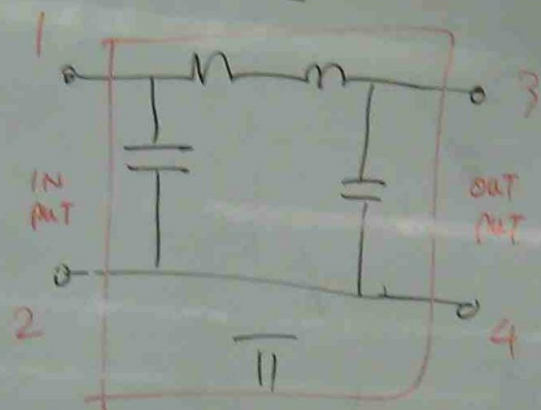


# FOUR TERMINAL NETWORKS ABCD CONSTANTS

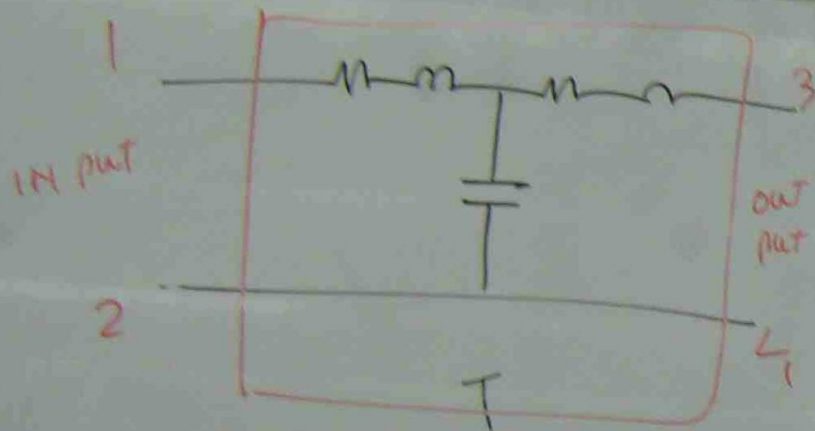

$$\overline{V_s} = A \overline{V_r} + B \overline{I_r}$$
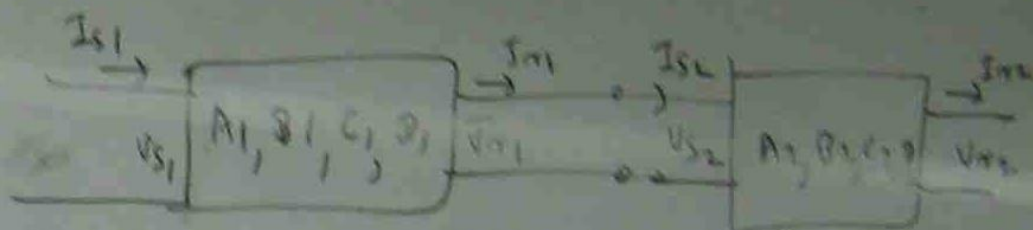
$$\overline{I_s} = C \overline{V_r} + D \overline{I_r}$$



$$A_{eq} = A_1 A_2 + B_1 C_2, \quad C_{eq} = C_1 A_2 + D_1 C_2$$


$$B_{eq} = A_1 B_2 + B_1 D_2, \quad D_{eq} = C_1 B_2 + D_1 D_2$$

$$\overline{V}_s = A_{eq} \overline{V}_r + B_{eq} \overline{I}_r$$

$$\overline{I}_s = C_{eq} \overline{V}_r + D_{eq} \overline{I}_r$$

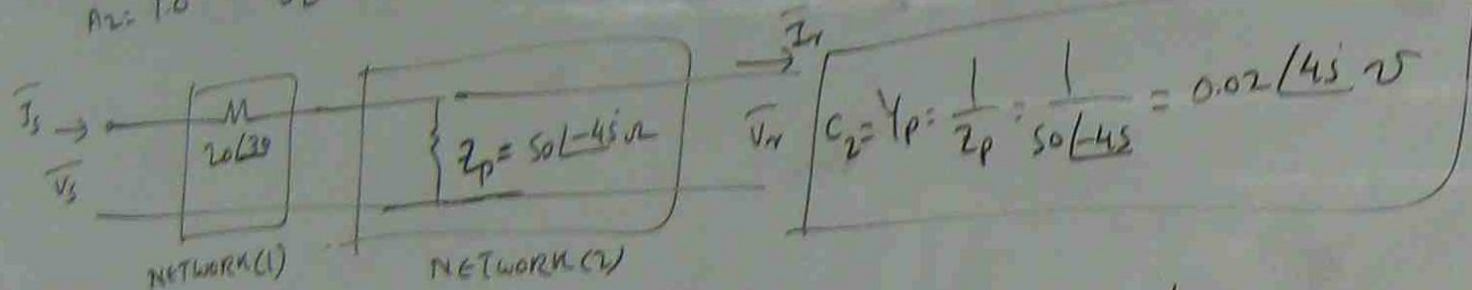PROBLEM: DETERMINE THE EQUIVALENT A, B, C, D CONSTANTS OF THE NETWORK AS SHOWN

$$\begin{aligned} A_1 &= 1.0 & B_1 &= 20 \angle 30^\circ \Omega & C_1 &= 0.01 \text{ S} & D_1 &= 1.0 \\ A_2 &= 1.0 & B_2 &= 0 & C_2 &= 0.02 \angle 45^\circ \text{ S} & D_2 &= 1.0 \end{aligned}$$



$$A_{eq} = A_1 A_2 + B_1 C_2 = 1.0 \times 1.0 + 20 \angle 30^\circ \times 0.02 \angle 45^\circ = 1.0 + 0.4 \angle 75^\circ$$

$$A_{eq} = 1.0 + 0.104 + j0.386 = 1.104 + j0.386 = 1.17 \angle 19.3^\circ$$

$$B_{eq} = A_1 B_2 + B_1 D_2 = 1.0 \times 0 + 20 \angle 30^\circ \times 1.0 = 20 \angle 30^\circ$$

$$C_{eq} = C_1 A_2 + D_1 C_2 = 0 \times 1.0 + 1.0 \times 0.02 \angle 45^\circ$$


$$C_{eq} = 0.02 \angle 45^\circ \text{ S}$$

$$D_{eq} = C_1 B_2 + D_1 D_2 = 0 \times 0 + 1.0 \times 1.0 = 1.0$$



# DETERMINATION OF A, B, C, D PARAMETERS BY EXPERIMENT

## TEST (1) OPEN CIRCUIT

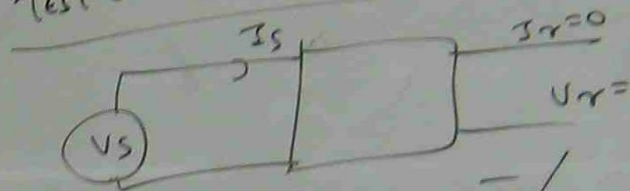

$$\bar{V}_S = A_{e0} \bar{V}_r + B_{e0} \cancel{\bar{I}_r}$$

$$\bar{V}_S = A_{e0} \times \bar{V}_r \longrightarrow A_{e0} = \frac{\bar{V}_S}{\bar{V}_r}$$


$$\bar{I}_S = C_{e0} \bar{V}_S + D_{e0} \cancel{\bar{I}_r}$$

$$\bar{I}_S = C_{e0} \bar{V}_S \longrightarrow C_{e0} = \frac{\bar{I}_S}{\bar{V}_S}$$

## TEST (2) SHORT CIRCUIT

$$\bar{V}_S = A_{s0} \cancel{\bar{V}_r} + B_{s0} \bar{I}_r$$

$$B_{s0} = \frac{\bar{V}_S}{\bar{I}_r}$$

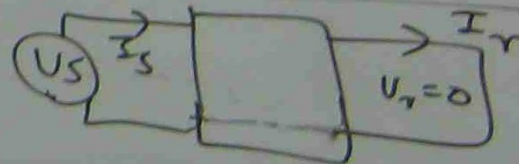

$$\bar{I}_S = C_{s0} \cancel{\bar{V}_r} + D_{s0} \bar{I}_r$$

$$D_{s0} = \frac{\bar{I}_S}{\bar{I}_r}$$

Qb

DETERMINE THE ABCD CONSTANTS OF THE NETWORK IN WHICH THE FOLLOWING TEST RESULTS HAVE BEEN OBSERVED.

RECEIVER OPEN CIRCUIT

$$\bar{V}_S = 100 \angle 0^\circ \text{ V}$$

$$\bar{V}_R = 70.7 \angle -45^\circ \text{ V}$$

$$\bar{I}_S = 1.41 \angle -45^\circ \text{ A}$$

$$\bar{I}_R = 0$$

RECEIVER SHORT CIRCUIT

$$\bar{V}_R = 0$$

$$\bar{V}_S = 100 \angle 0^\circ \text{ V}$$

$$\bar{I}_S = 2.0 \angle -90^\circ \text{ A}$$

$$\bar{I}_R = 2.0 \angle -90^\circ \text{ A}$$

OPEN  $A = \frac{V_S}{V_R} = \frac{100 \angle 0^\circ}{70.7 \angle -45^\circ} = 1.41 \angle 45^\circ$

$$C = \frac{I_S}{V_S} = \frac{1.41 \angle -45^\circ}{100 \angle 0^\circ} = 0.0141 \angle -45^\circ$$

SHORT

$$B = \frac{V_S}{I_R} = \frac{100 \angle 0^\circ}{2 \angle -90^\circ} = 50 \angle 90^\circ$$


$$D = \frac{I_S}{I_R} = \frac{2 \angle -90^\circ}{2 \angle -90^\circ} = 1$$

# APPLICATION OF ABCD CONSTANTS IN TRANSMISSION LINE

---

## II EQUIVALENT CIRCUIT

---

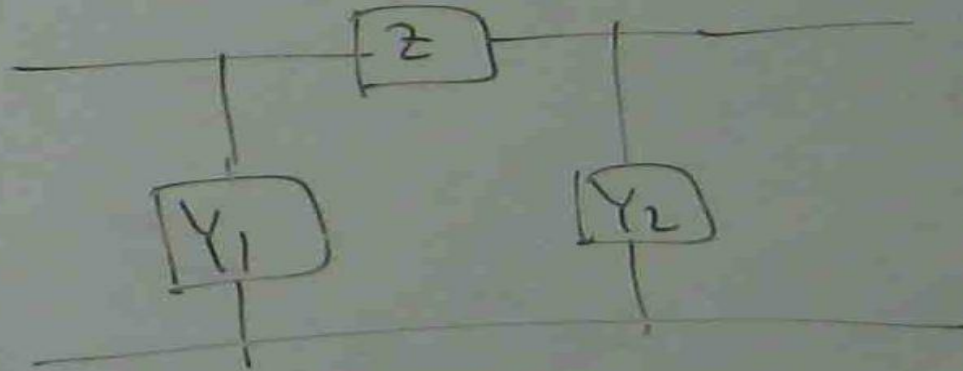

$$A = 1 + Y_1 Z$$

$$B = Z$$

$$C = Y_2 + Y_1 + Y_1 Y_2 Z$$

$$D = 1 + Z Y_1$$



\*\*\*  
RESOLVE THE FOLLOWING PHASORS IN TO THEIR SYMMETRICAL  
COMPONENTS TO DRAW THE PHASOR DIAGRAM OF SEPARATE  
COMPONENTS AND CHECK THAT THE SUM OF THE COMPONENTS IS  
EQUAL TO ORIGINAL SET OF PHASORS

$$I_A = 120 \angle 0^\circ \text{ Amp}, \quad I_B = 0 \text{ Amp}, \quad I_C = 0 \text{ Amp}.$$

$$\begin{matrix} I_{A0} & I_{A1} & I_{A2} \\ I_{B0} & I_{B1} & I_{B2} \\ I_{C0} & I_{C1} & I_{C2} \end{matrix} \left\{ \begin{array}{l} \text{SYMMETRICAL} \\ \text{COMPONENTS} \end{array} \right.$$

$$I_{A0} = I_{B0} = I_{C0} = \frac{1}{3} (I_A + I_B + I_C) \\ = \frac{1}{3} (120 \angle 0^\circ + 0 + 0) = 40 \angle 0^\circ \text{ Amp}.$$


$$I_{A1} = \frac{1}{3} (I_A + a I_B + a^2 I_C) \quad a = 1 \angle 120^\circ \\ = \frac{1}{3} (120 \angle 0^\circ + 1 \angle 120^\circ \times 0 + (1 \angle 120^\circ)^2 \times 0) = 40 \angle 0^\circ \text{ Amp}$$

$$I_{A2} = \frac{1}{3} (I_A + a^2 I_B + a I_C) = \frac{1}{3} (120 \angle 0^\circ + (1 \angle 120^\circ)^2 \times 0 + 1 \angle 120^\circ \times 0) \\ = 40 \angle 0^\circ \text{ Amp}$$

TRICAL  
TE  
S 15


$$I_{B1} = I_{A1} \times \frac{1 \angle -120^\circ}{1 \angle -120^\circ} = 40 \angle 0^\circ \times \frac{1 \angle -120^\circ}{1 \angle -120^\circ} = 40 \angle 0 - 120 = 40 \angle -120^\circ \text{ Amp}$$
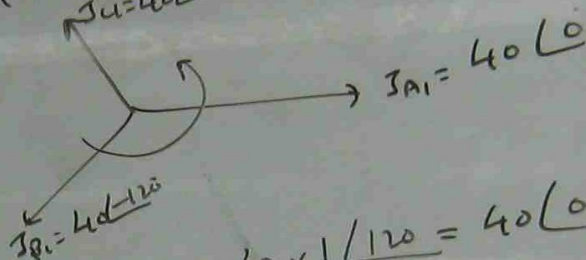
$$I_{C1} = I_{A1} \times \frac{1 \angle +120^\circ}{1 \angle +120^\circ} = 40 \angle 0^\circ \times \frac{1 \angle +120^\circ}{1 \angle +120^\circ} = 40 \angle 0 + 120 = 40 \angle 120^\circ \text{ Amp}$$



$$I_{B2} = I_{A2} \times \frac{1 \angle +120^\circ}{1 \angle +120^\circ} = 40 \angle 0^\circ \times \frac{1 \angle +120^\circ}{1 \angle +120^\circ} = 40 \angle 0 + 120 = 40 \angle 120^\circ \text{ Amp}$$
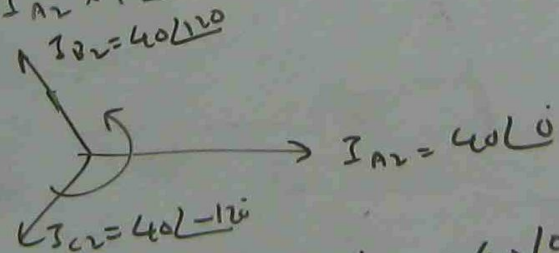
$$I_{C2} = I_{A2} \times \frac{1 \angle -120^\circ}{1 \angle -120^\circ} = 40 \angle 0^\circ \times \frac{1 \angle -120^\circ}{1 \angle -120^\circ} = 40 \angle 0 - 120 = 40 \angle -120^\circ \text{ Amp}$$



CHECK  $I_{A0} + I_{A1} + I_{A2} = 40 \angle 0 + 40 \angle 0 + 40 \angle 0 = 120 \angle 0 = I_A$

$$I_{B0} + I_{B1} + I_{B2} = 40 \angle 0 + 40 \angle -120 + 40 \angle +120$$

$$= 40 + 40(\cos 120 - j \sin 120) + 40(\cos 120 + j \sin 120)$$


$$= 40 + (-20) - j 40 \sin 120 + (-20) + j 40 \sin 120$$

$$= 0 = I_B$$

$$I_{C0} + I_{C1} + I_{C2} = 40 \angle 0 + 40 \angle 120 + 40 \angle -120 = 40 + 40(\cos 120 + j \sin 120) + 40(\cos 120 - j \sin 120)$$

$$= 0 = I_C$$



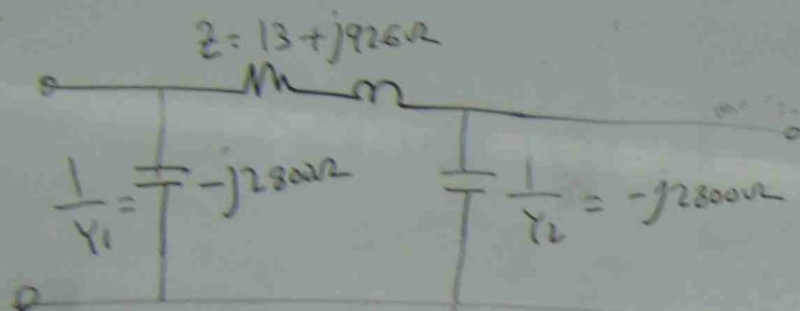

FIND A, B, C, D CONSTANTS OF ABOVE II CIRCUIT.

$$\begin{aligned}
 A &= 1 + Y_2 Z \\
 B &= Z \\
 C &= Y_1 + Y_2 + Y_1 Y_2 Z \\
 D &= A
 \end{aligned}$$

$$Z = 13 + j92.6 = 93.5 \angle 82^\circ \Omega$$

$$Y_1 = \frac{1}{-j2800} = 0.00357 \angle 90^\circ \text{ S}$$

$$Y_2 = \frac{1}{-j2800} = 0.00357 \angle 90^\circ \text{ S}$$

$$A = 1 + Y_2 Z = 1 + 0.00357 \angle 90^\circ \times 93.5 \angle 82^\circ$$

$$= 1 + 0.00334 \angle 172^\circ$$

$$= 1 + 0.00334 (\cos 172^\circ + j \sin 172^\circ)$$

$$= 0.967 + j 0.00465$$

$$A = 0.967 \angle 0.3^\circ$$

$$B = Z \rightarrow B = 93.5 \angle 82^\circ \Omega$$

$$C = Y_1 + Y_2 + Y_1 Y_2 Z = 0.00357 \angle 90^\circ + 0.00357 \angle 90^\circ + 0.00357 \angle 90^\circ \times 0.00357 \angle 90^\circ \times 93.5 \angle 82^\circ$$


$$= 0.00714 (\cos 90^\circ + j \sin 90^\circ) + (0.00357)^2 \times 93.5 \angle 262^\circ$$

$$= 0.00714 (0 + j1) + (0.00357)^2 \times 93.5 (\cos 262^\circ + j \sin 262^\circ)$$

$$= -0.0000017 + j 0.000702$$

$$C = 0.000702 \angle 90^\circ \text{ S}$$

$$D = A = 0.967 \angle 0.3^\circ$$

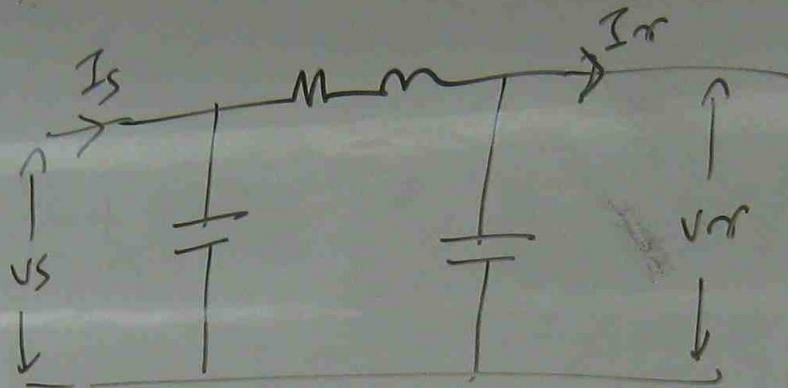

Amp.

$$\bar{V}_S = A \bar{V}_N + B \bar{I}_N$$

$$\bar{V}_S = 0.0967 \angle 0.3 \bar{V}_N + 93.5 \angle 82 \bar{I}_N \quad \text{--- (1)}$$


$$\bar{I}_S = C \bar{V}_S + D \bar{I}_N$$

$$\bar{I}_S = 0.000702 \angle 90 \bar{V}_S + 0.967 \angle 0.3 \bar{I}_N$$

(2)



ph

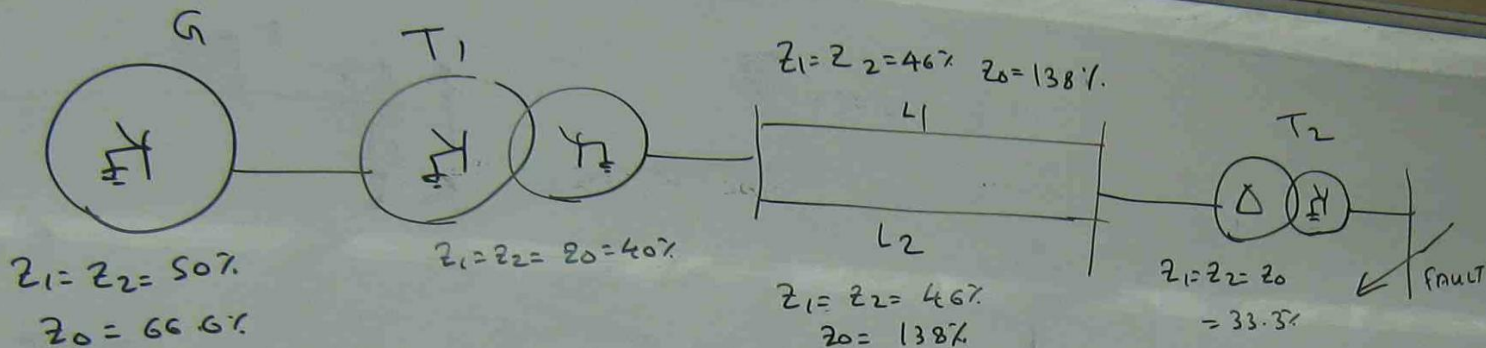

### PLANT DETAILS

GENERATOR 11KV, 30MVA,  $Z_1 = Z_2 = 15\%$ ,  $Z_0 = 20\%$

TRANSFORMER (1) 11KV/33KV 30MVA  $Z = 12\%$

TRANSFORMER (2) 33KV/11KV 30MVA  $Z = 10\%$

TRANSMISSION LINE (1) & (2)

LENGTH 5 km,  $Z_1 = Z_2 = j1 \Omega/\text{km}$   
 $Z_0 = j3 \Omega/\text{km}$

USE 100 MVA BASE

DRAW - POSITIVE, NEGATIVE AND ZERO  
SEQUENCE DIAGRAMS

CALCULATE (i) L → L FAULT

(ii) L → G FAULT

(iii) 2L → G FAULT

BASE  
MVA = 100  
BASE VOLTAGE = 33KV

$$Z_2 = \frac{\text{BASE MVA} \times Z_1}{\text{MVA}_1}$$

GENERATOR

$$Z_1 = Z_2 = \frac{100}{30} \times 15 = 50\%$$

$$Z_0 = \frac{100}{30} \times 20 = 66.6\%$$

TRANSFORMER (1)

$$Z_1 = Z_2 = Z_0 = \frac{100}{30} \times 12 = 40\%$$

TRANSFORMER (2)

$$Z_1 = Z_2 = Z_0 = \frac{100}{30} \times 10 = 33.3\%$$

LINE(1)(2)

LT

$$Z_1 = Z_2 = j1 \times 5 = j5 \Omega$$


$$Z_0 = j3 \times 5 = j15 \Omega$$

$$Z(\%) \text{ OR } Z(\text{pu}) = \frac{Z(\Omega) \times \text{MVA BASE}}{(\text{BASE KV})^2}$$

$$Z_1 = Z_2 = \frac{5 \times 100 \times 10^6}{(33 \times 10^3)^2} = 4.6\%$$

$$Z_0 = \frac{15 \times 100 \times 10^6}{(33 \times 10^3)^2} = 13.8\%$$

POSITIVE SEQUENCE DIAGRAM

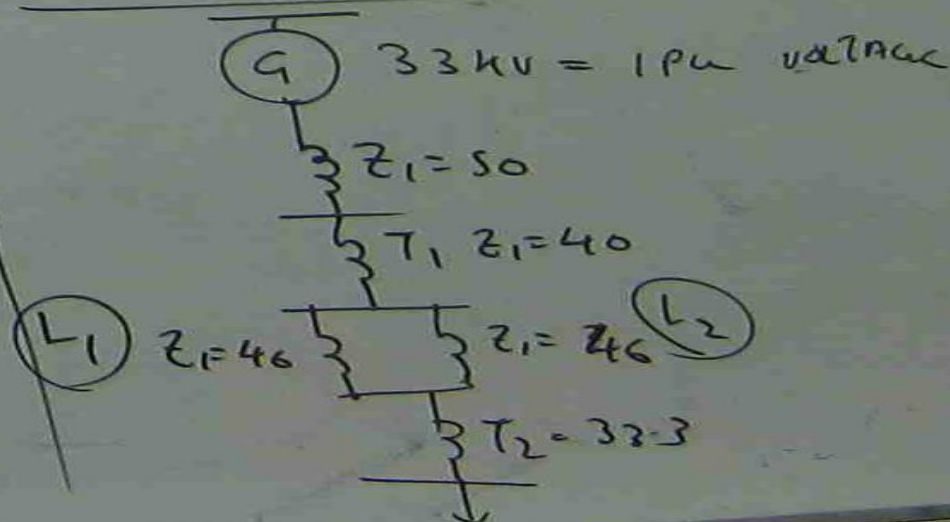




$$Z_{1 \text{ TOTAL}} = Z^+ = 50 + 40 + \frac{46 \times 46}{46 + 46} + 33.3$$



$$= 146.3 \%$$

NEGATIVE SEQUENCE DIAGRAM

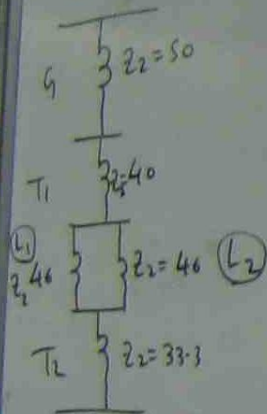


$$Z_{2 \text{ TOTAL}} = \bar{Z} = 50 + 40 + \frac{46 \times 46}{46 + 46} + 33.3$$

$$= 146.3 \%$$

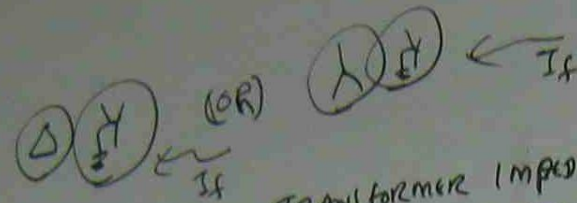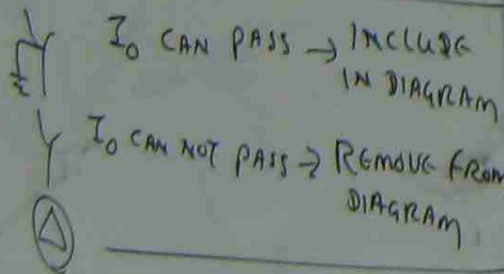

ONLY INCLUDE THE TRANSFORMER IMPEDANCE IN DIAGRAM. ELIMINATE ALL EQUIPMENTS BEYOND \$\Delta\$ & Y POINT OF THE TRANSFORMER

FAULT ZERO SEQUENCE DIAGRAM

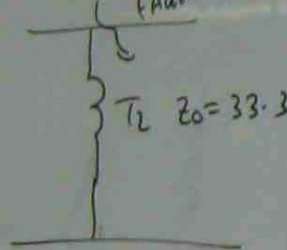

(ii) L \$\rightarrow\$ G FAULT

$$Z_T = Z^+ + \bar{Z} + Z_0 = 146.3 + 146.3 + 33.3$$

$$= 325.9 \text{ pu}$$



$$I_{A1} = I_{A2} = I_{A0} = \frac{\text{BASE MVA}}{Z_T \times \text{BASE} \times \sqrt{3}} \times 100$$

$$= \frac{100 \times 10^6}{325.9 \times 33 \times 10^3 \times 1.7321} \times 100 = 536.13 \text{ Amp}$$

$$I_A = 3 I_{A1} = 3 \times 536.13 = 1608 \text{ Amp}$$



(i)  $L \rightarrow L$  fault

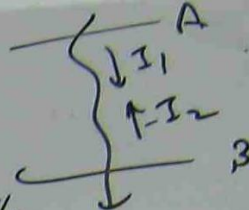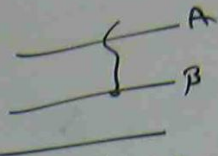


$$Z_T = Z^+ + Z^- = 146.3 + 146.3 = 292.6\%$$

$$I_1 = (-I_2) = \frac{\text{BASE MVA}}{Z_T \times \text{BASE VOLTAGE} \times \sqrt{3}} \times 100$$

$$= \frac{100 \times 10^6}{292.6 \times 33 \times 10^3 \times \sqrt{3}} \times 100 = 597 \text{ Amp}$$

$$I_A = I_B = \sqrt{3} I_1 = 1.732 \times 597 = 1034.06 \text{ Amp}$$

(ii)  $2L \rightarrow G$  fault

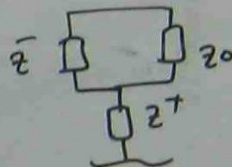

$$Z_T = Z^+ + \frac{Z^- \times Z_0}{Z^- + Z_0}$$

$$= 146.3 + \frac{146.3 \times 33.3}{146.3 + 33.3} = 173.4\%$$

$$I_1 = \frac{\text{BASE MVA}}{Z_T \times \text{BASE VOLTAGE} \times \sqrt{3}} \times 100 = \frac{100 \times 10^6 \times 100}{173.4 \times 33 \times 10^3 \times 1.7321} = 1008.9 \text{ Amp}$$

$$I_2 = I_1 \times \frac{Z_0}{Z_0 + Z^-} = 1008.9 \times \frac{33.3}{146.3 + 33.3} = 187.06 \text{ Amp}$$

$$I_0 = I_1 \times \frac{Z^-}{Z_0 + Z^-} = 1008.9 \times \frac{146.3}{146.3 + 33.3} = 821.83 \text{ Amp}$$

Amp

$$I_A = I_1 \angle 0^\circ + I_2 \angle 60^\circ + I_0 \angle -60^\circ$$

$$I_B = I_1 \angle 120^\circ + I_2 \angle 180^\circ + I_0 \angle -60^\circ$$

$$I_C = I_1 \angle 240^\circ + I_2 \angle -60^\circ + I_0 \angle -60^\circ$$

$$I_f = I_A + I_B + I_C$$

$$\begin{aligned}
 I_A &= I_1 \angle 0 + I_2 \angle 60 + I_0 \angle -60 \\
 &= 1008.9 \angle 0 + 187.06 \angle 60 + 821.83 \angle -60 \\
 &= 1008.9 + 93.4 + j161.5 + 410.9 - j770.6 \\
 &= 1511.45 - j549.1 \text{ Amp}
 \end{aligned}$$

$$\begin{aligned}
 I_B &= I_1 \angle 120 + I_2 \angle 180 + I_0 \angle -60 \\
 &= 1008.9 \angle 120 + 187.06 \angle 180 + 821.83 \angle -60 \\
 &= -503.82 + j872.62 + (-187.06 + j0) + 410.38 - j770.62 \\
 I_B &= -280.25 + j162 \text{ Amp}
 \end{aligned}$$

$$\begin{aligned}
 I_C &= I_1 \angle 120 + I_2 \angle -60 + I_0 \angle -60 \\
 &= 1008.9 \angle 120 + 187.06 \angle -60 + 821.83 \angle -60 \\
 &= -504.45 + j873.69 + 504.45 - j873.69 \\
 &= 0
 \end{aligned}$$

$$\begin{aligned}
 I_{\text{fault}} &= I_A + I_B + I_C \\
 (2L \rightarrow G)
 \end{aligned}$$

$$I_{\text{fault}} = 1511.45 - j549.1 + (-280.25 + j162) + 0$$

2L → G

$$= 1231.2 - j387.1$$

$$= 1290.61 \angle -17.45 \text{ Amp}$$

62