
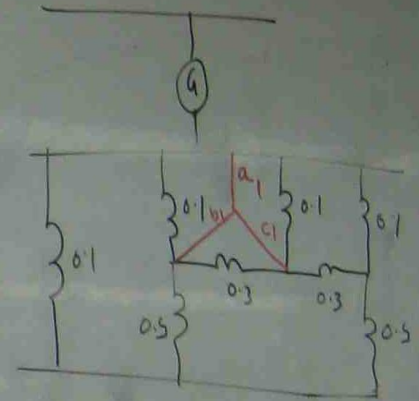
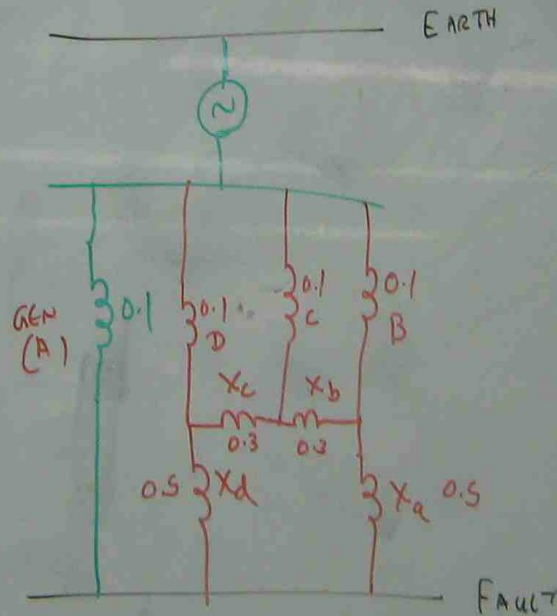


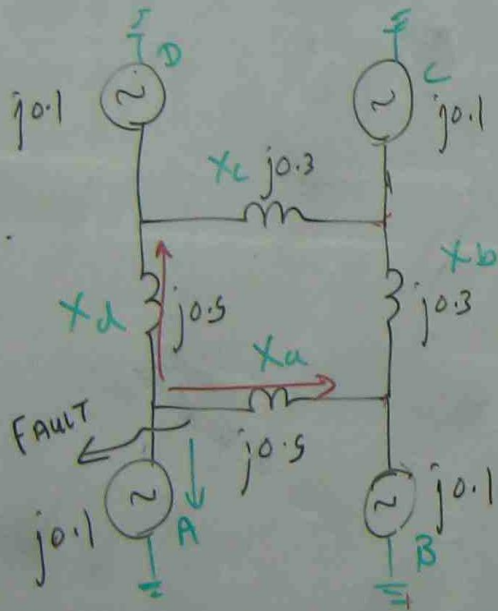
Q7 IN THE GIVEN NETWORK, 3 $\phi$  FAULT OCCURS AT POINT (F)  
 CALCULATE FAULT M.V.A THE PERUNIT VALUES OF REACTANCES  
 ALL REFER TO BASE OF 100 MVA. RESISTANCE MAY BE NEGLECTED





$$a_1 = \frac{0.1 \times 0.1}{0.1 + 0.1 + 0.3} = 0.2$$

$$b_1 = \frac{0.1 \times 0.3}{0.1 + 0.1 + 0.3} = 0.6$$
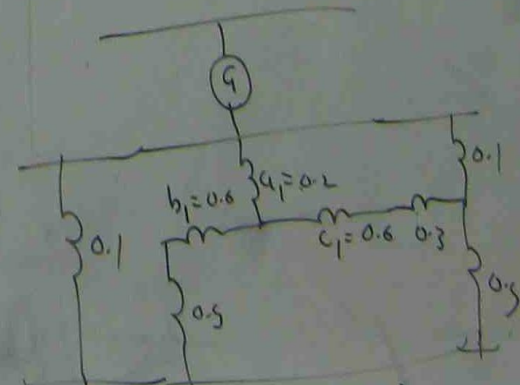
$$c_1 = \frac{0.1 \times 0.3}{0.1 + 0.1 + 0.3} = 0.6$$




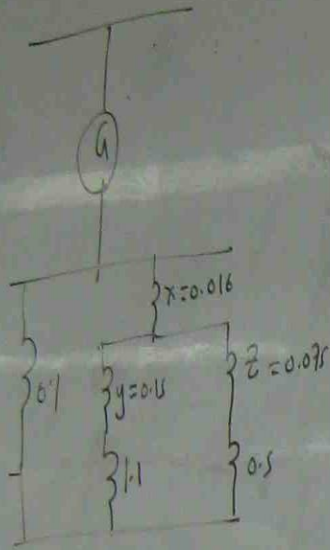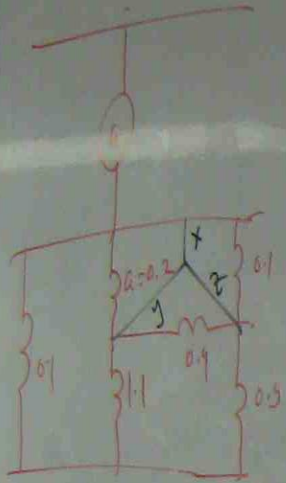


$$x = \frac{0.2 \times 0.1}{0.2 + 0.9 + 0.1} = 0.016$$

$$y = \frac{0.2 \times 0.9}{0.2 + 0.9 + 0.1} = 0.15$$
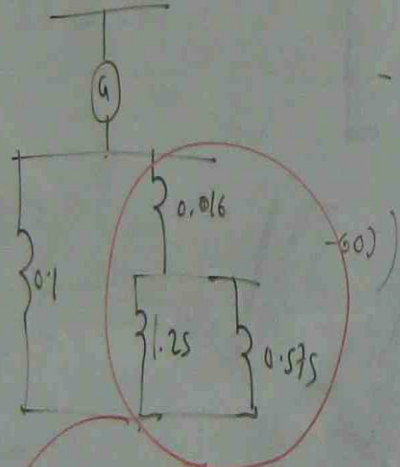
$$z = \frac{0.9 \times 0.1}{0.2 + 0.9 + 0.1} = 0.075$$


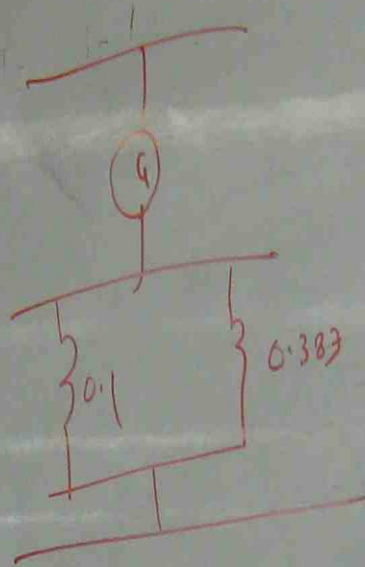
$$\frac{1.25 \times 0.575}{1.25 + 0.575} + 0.016 = 0.383$$





$$0.1 \parallel 0.383 = \frac{0.1 \times 0.383}{0.1 + 0.383} = 0.084$$

$$MVA_{sh} = \frac{MVA_{FL}}{Z_T} \times 100 = \frac{100}{0.084} \times 100$$


$$= 1190 \text{ MVA}$$

Ph

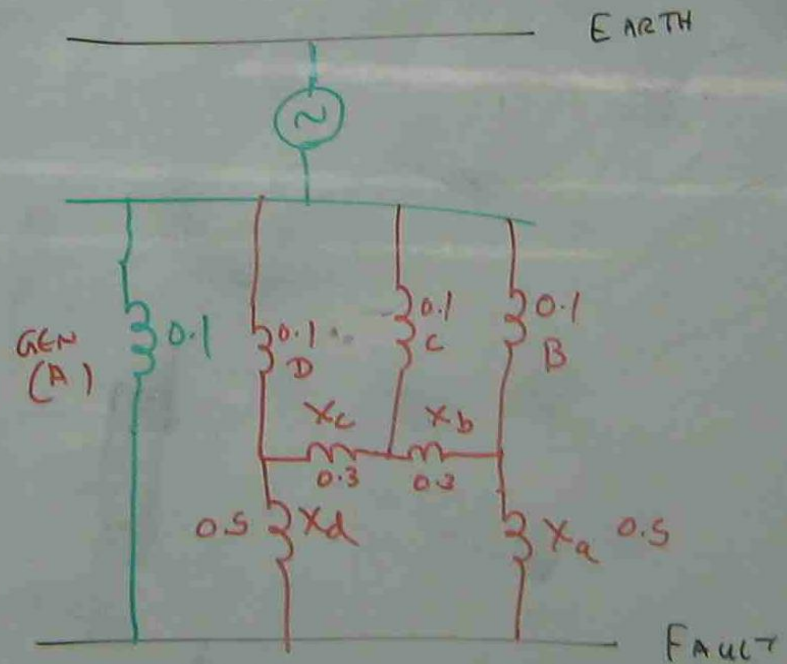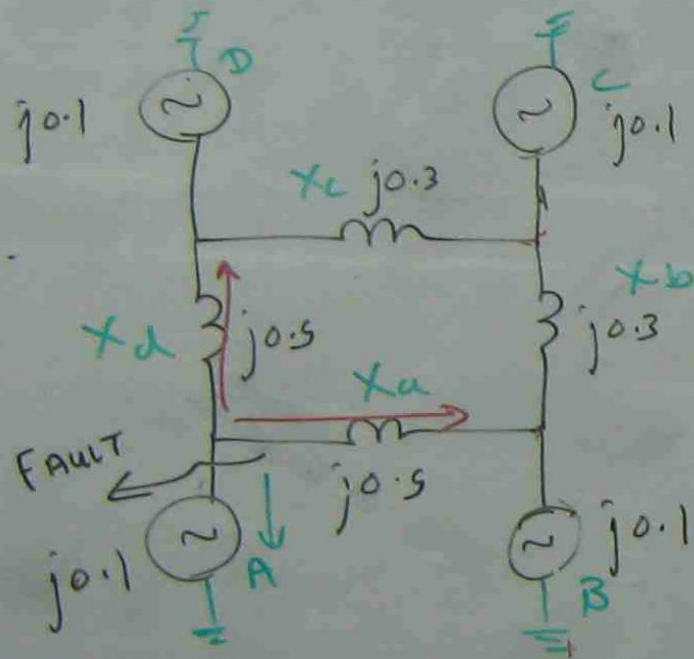IN THE GIVEN NETWORK, 3 $\phi$  FAULT OCCURS AT POINT (F)  
 CALCULATE FAULT M.V.A THE PER UNIT VALUES OF REACTANCES  
 ALL REFER TO BASE OF 100 MVA. RESISTANCE MAY BE NEGLECTED






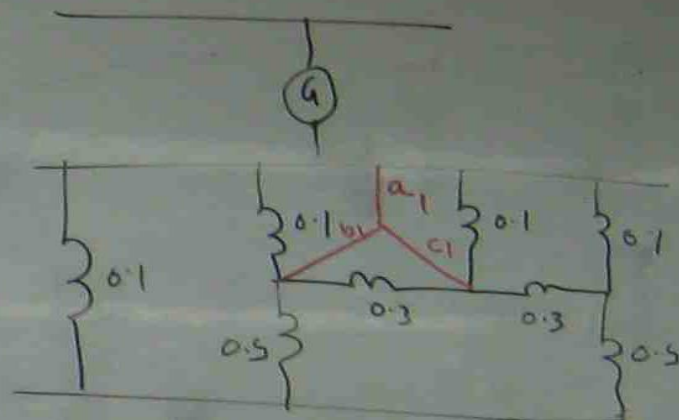


$$a_1 = \frac{0.1 \times 0.1}{0.1 + 0.1 + 0.3} = 0.2$$

$$b_1 = \frac{0.1 \times 0.3}{0.1 + 0.1 + 0.3} = 0.6$$
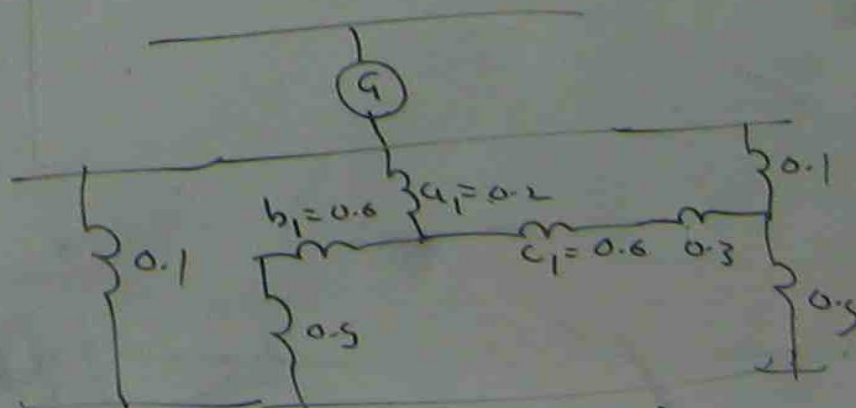
$$c_1 = \frac{0.1 \times 0.3}{0.1 + 0.1 + 0.3} = 0.6$$





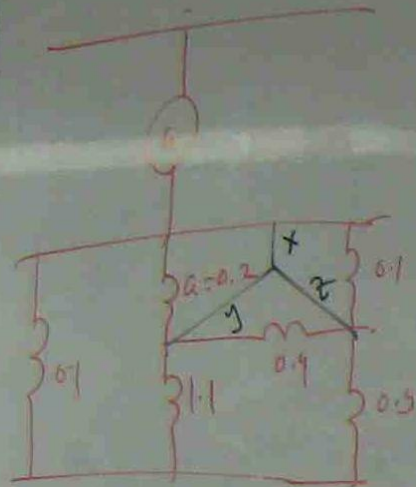

$$x = \frac{0.2 \times 0.1}{0.2 + 0.9 + 0.1} = 0.016$$

$$y = \frac{0.2 \times 0.9}{0.2 + 0.9 + 0.1} = 0.15$$

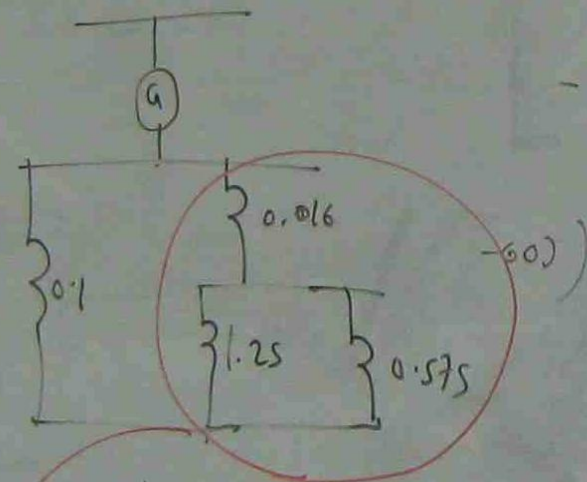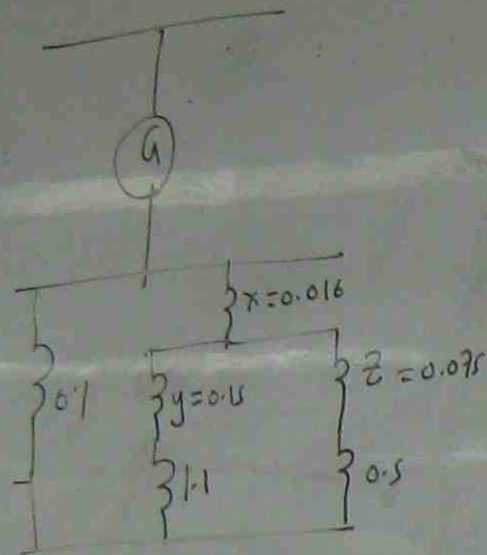
$$z = \frac{0.9 \times 0.1}{0.2 + 0.9 + 0.1} = 0.075$$



$$\frac{1.25 \times 0.575}{1.25 + 0.575} + 0.016$$

$$= 0.383$$

1-60

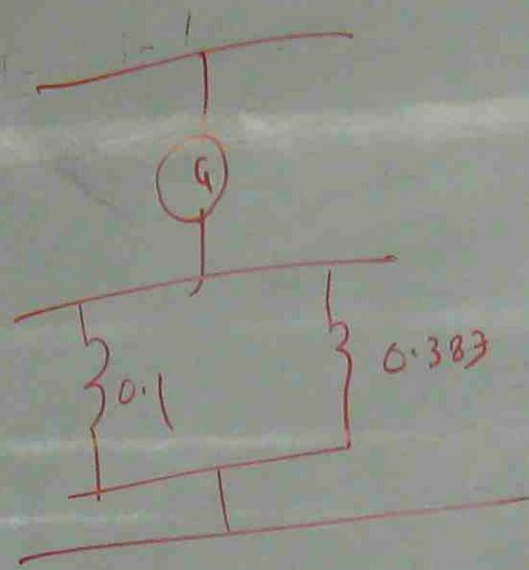

$$0.1 \parallel 0.383 = \frac{0.1 \times 0.383}{0.1 + 0.383} = 0.084$$

$$MVA_{Sh} = \frac{MVA_{FL}}{Z_T} \times 100$$

$$= \frac{100}{0.084} \times 100$$

$$= 1190 MVA$$