

CALCULATION OF POWER IN FOUR WIRE STAR CONNECTED UNBALANCED LOADS


FOR 3 ϕ BALANCED LOAD $3\phi \text{ power} = \sqrt{3} E I \cos\theta$

FOR 3 ϕ UNBALANCED LOAD, THE ABOVE FORMULA CAN NOT BE USED

$$3\phi \text{ power} = V_{AN} I_A \cos\theta_{IA} + V_{BN} I_B \cos\theta_{IB} + V_{CN} I_C \cos\theta_{IC}$$

ph 3 ϕ 208 v ABC, $Z_A = 10 \angle -60^\circ$, $Z_B = 6 \angle -90^\circ$, $Z_C = 12 \angle 30^\circ$. FIND 3 ϕ POWER
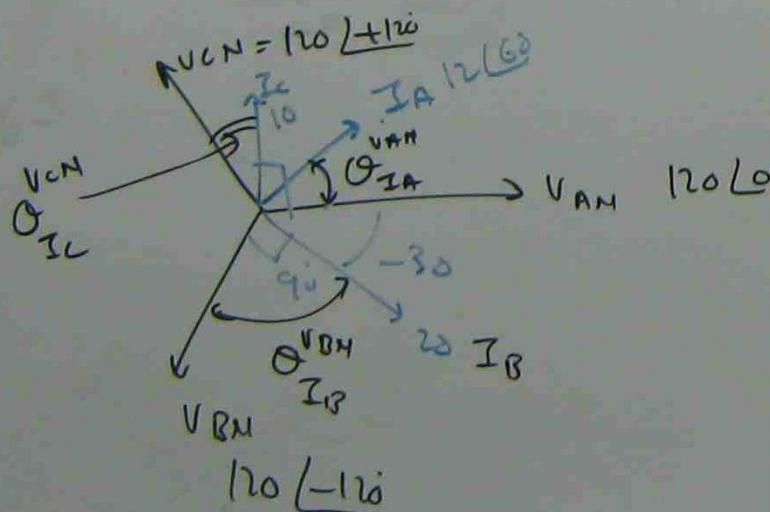
$$V_{AN} = \frac{208}{\sqrt{3}} = 120 \text{ V}$$



$$\bar{I}_A = \overline{\frac{V_{AN}}{Z_A}} = \overline{\frac{120 L 0}{10 \angle -60}} = 12 \angle 60^\circ \text{ A}$$

$$\bar{I}_B = \overline{\frac{V_{BN}}{Z_B}} = \overline{\frac{120 L 120}{6 \angle -90}} = 20 \angle -30^\circ \text{ A}$$

$$\bar{I}_C = \overline{\frac{V_{CN}}{Z_C}} = \overline{\frac{120 L 110}{12 \angle 30}} = 10 \angle 40^\circ \text{ A}$$

$$\theta_{I_n}^{UAN} = 60^\circ, \quad \theta_{I_B}^{UBN} = 90^\circ$$

$$\theta_{I_C}^{VCN} = 30^\circ$$

$$P_A = V_{AN} I_A \cos \theta_{IA}^{UAN}$$

$$= 120 \times 12 \times \cos 60^\circ = 720 \text{ WATT}$$

$$P_B = V_{BN} I_B \cos \theta_{IB}^{UBN}$$

$$= 120 \times 20 \times \cos 90^\circ = 0 \text{ WATT}$$

$$P_C = V_{CN} I_C \cos \theta_{IC}^{VCN}$$


$$= 120 \times 10 \times \cos 30^\circ = 1039 \text{ WATT}$$

$$P_T = P_A + P_B + P_C$$

$$= 720 + 0 + 1039$$

$$= 1759 \text{ WATT}$$

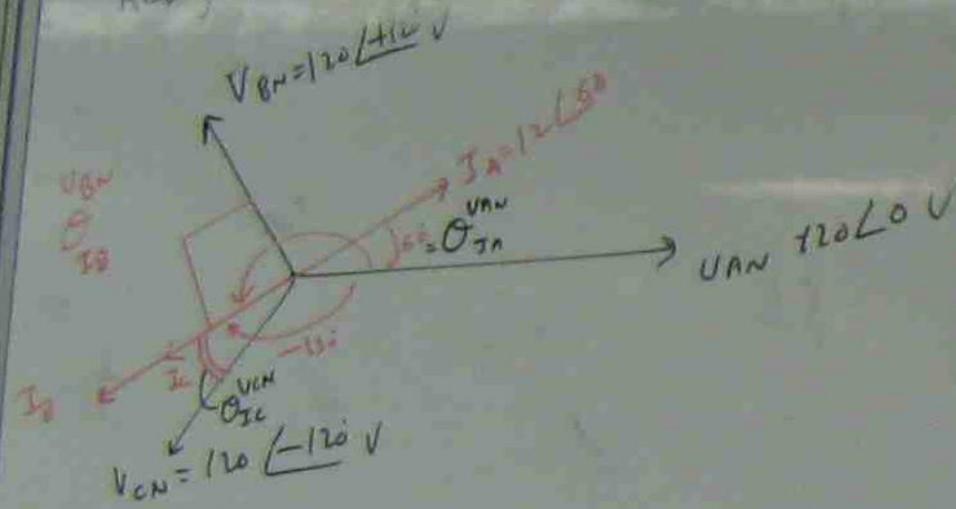Qb) IN ABOVE PROBLEM, IF THE PHASE SEQUENCE IS CHANGED TO
ACB, FIND TOTAL 3rd POWER



$$\bar{I}_A = \frac{\bar{V}_{AN}}{Z_A} = \frac{120\angle 0^\circ}{10\angle -60^\circ} = 12\angle 60^\circ \text{ A}$$

$$\bar{I}_B = \frac{\bar{V}_{BN}}{Z_B} = \frac{120\angle 120^\circ}{6\angle -90^\circ} = 20\angle 210^\circ \text{ A}$$

$$\bar{I}_C = \frac{\bar{V}_{CN}}{Z_C} = \frac{120\angle -120^\circ}{12\angle 30^\circ} = 10\angle -150^\circ \text{ A}$$

leads to

$$\theta_{IA}^{VAN} = 60^\circ$$

$$\theta_{IB}^{VCN} = 90^\circ$$

$$\theta_{IC}^{VCN} = 30^\circ$$

$$P_A = V_{AN} I_A \cos \theta_{IA}^{VAN} = 120 \times 12 \cos 60^\circ = 720 \text{ W}$$

$$P_B = V_{BN} I_B \cos \theta_{IB}^{VBN} = 120 \times 20 \cos 90^\circ = 0$$

$$P_C = V_{CN} I_C \cos \theta_{IC}^{VCN} = 120 \times 10 \cos 30^\circ = 1039 \text{ W}$$

$$P_T = P_A + P_B + P_C$$

$$= 720 + 0 + 1039$$

$$= 1759 \text{ W}$$

By reversing the phase sequence

(1) Line current magnitudes - the same / phase angles different

(2) Different neutral current

(3) The same total 3φ power.