
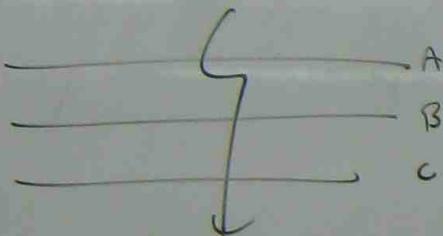


REASON TO DIVIDE POSITIVE, NEGATIVE AND ZERO SEQUENCE
COMPONENTS

BALANCED 3 ϕ SHORT CIRCUIT

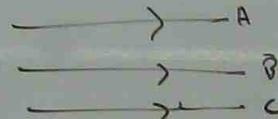


NORMAL



THERE IS ONLY POSITIVE SEQUENCE
COMPONENT


$$I_{A_1}, I_{B_1}, I_{C_1}$$

3 LINES TO GROUND

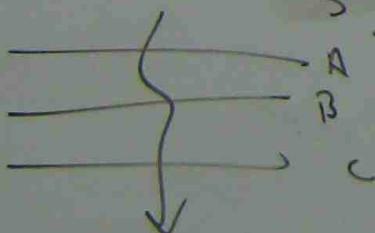

THERE IS ONLY ZERO SEQUENCE
COMPONENT

$$I_{A_0}, I_{B_0}, I_{C_0}$$

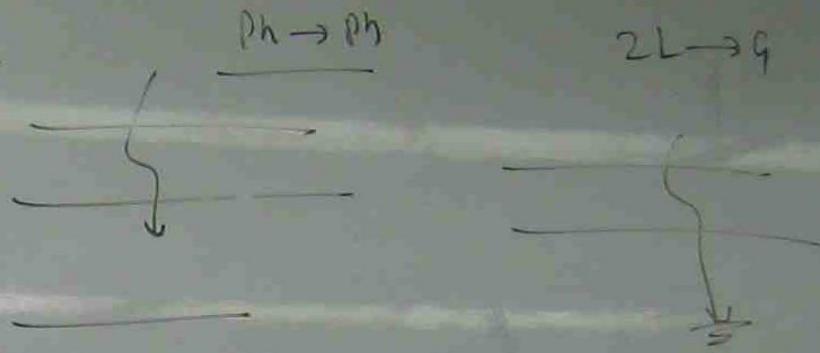

compose +IVE, -IVE & ZERO

SEQUENCE COMPONENTS

$I_{A1}, I_{B1}, I_{C1}, I_{A2}, I_{B2}, I_{C2}, I_{A0}, I_{B0}, I_{C0}$

Z_0 = ZERO SEQUENCE IMPEDANCE

H.V
EQUIPMENT

Z_1 = +IVE SEQUENCE IMPEDANCE

Z_2 = -IVE SEQUENCE IMPEDANCE

STATIC DEVICE

TRANS FOR MGR

O.H LING

CABLE

REACTOR

OVER HEAD

$$Z_1 = 22$$

I_{Co}

ROTATING MACHINING

GENERATOR, MOTOR

$$Z_1 \neq Z_2$$

To GENTS when THE DEVICE

IS CONNECTED TO EARTH

POSITIVE, NEGATIVE AND ZERO SEQUENCE EQUIVALENT DIAGRAMS

$$I_A = I_A^+ + I_A^- + I_A^0$$


$$I_B = I_B^+ + I_B^- + I_B^0$$

$$I_C = I_C^+ + I_C^- + I_C^0$$

$$I_{A1} = \frac{1}{3} (I_A + a I_B + a^2 I_C) \rightarrow I_{B1} = \underline{\underline{I_A - 120}}, \quad I_{C1} = \underline{\underline{I_A + 120}}$$

$$I_{A2} = \frac{1}{3} (I_A + a^2 I_B + a I_C) \rightarrow I_{B2} = \underline{\underline{I_A + 120}} \quad I_{C2} = \underline{\underline{I_A - 120}}$$
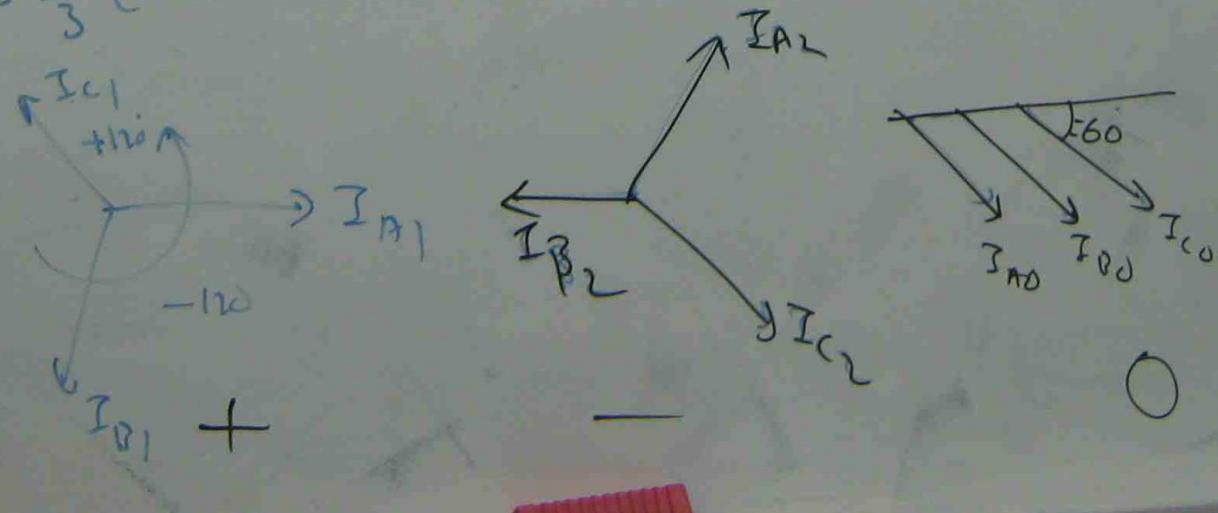
$$I_{A0} = \frac{1}{3} (I_A + I_B + I_C)$$



POSITIVE, NEGATIVE AND ZERO SEQUENCE EQUIVALENT DIAGRAMS

$$I_A = I_A^+ + I_A^- + I_A^0$$


$$I_B = I_B^+ + I_B^- + I_B^0$$

$$I_C = I_C^+ + I_C^- + I_C^0$$

$$I_{A1} = \frac{1}{3} (I_A + a I_B + a^2 I_C) \rightarrow I_{B1} = \underline{\Omega_A - 120}, \quad I_{C1} = \underline{\Omega_A + 120}$$

$$I_{A2} = \frac{1}{3} (I_A + a^2 I_B + a I_C) \rightarrow I_{B2} = \underline{\Omega_A + 120} \quad I_{C2} = \underline{\Omega_A - 120}$$
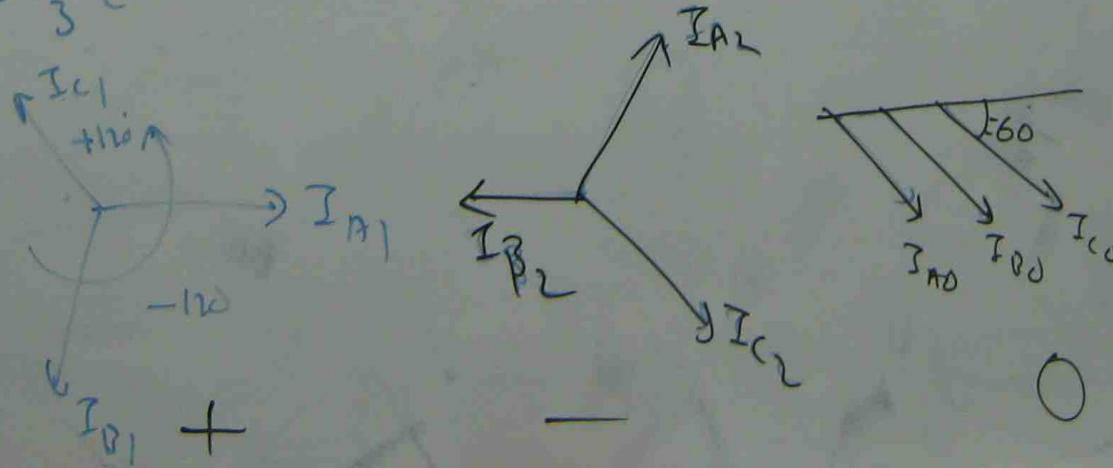
$$I_{A0} = \frac{1}{3} (I_A + I_B + I_C)$$



NOTE(1)


POSITIVE SEQUENCE DIAGRAM

ALL GENERATORS - VOLTAGE

SOURCES, THE VOLTAGE AND

IMPEDANCES ARE TO BE

INCLUDED.

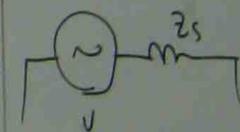


NEGATIVE SEQUENCE DIAGRAM


REMOVE THE VOLTAGE.

ONLY IMPEDANCE TO BE


INCLUDED.

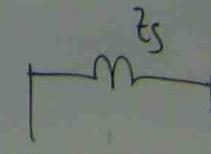

ZERO SEQUENCE DIAGRAM

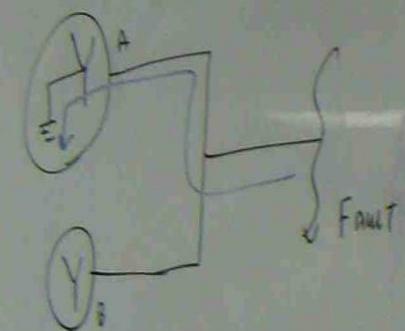


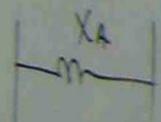INCLUDE ONLY THE EQUIPMENTS THAT
ALLOW THE FAULT CURRENT TO PASS THEM
TO THE GROUND.



PRACTICAL 12/05/09 PRACTICAL 02/06/09
TEST 2 26/05/09 TEST 3 - 16/06/09

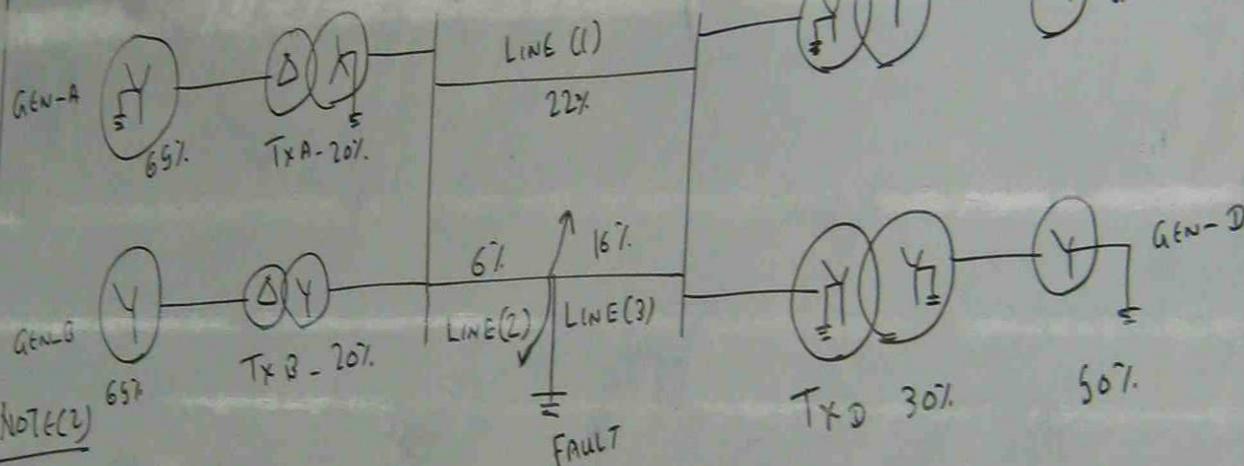DRAW POSITIVE SEQUENCE, NEGATIVE SEQUENCE AND ZERO SEQUENCE EQUIVALENT
DIAGRAM FOR THE FOLLOWING POWER SYSTEM.




→ CURRENT \vec{Y} \vec{Y}_0 INCLUDE BOTH EQUIPMENTS IN ZERO SEQUENCE DIAGRAM

→ CURRENT \vec{Y} $\vec{\Delta}$ REMOVE $\vec{\Delta}$ IN ZERO SEQUENCE DIAGRAM

→ \vec{Y} $\vec{\Delta}$ REMOVE BOTH IN ZERO SEQUENCE DIAGRAM

→ \vec{Y} \vec{Y}_0 REMOVE \vec{Y}_0 IN ZERO SEQUENCE DIAGRAM

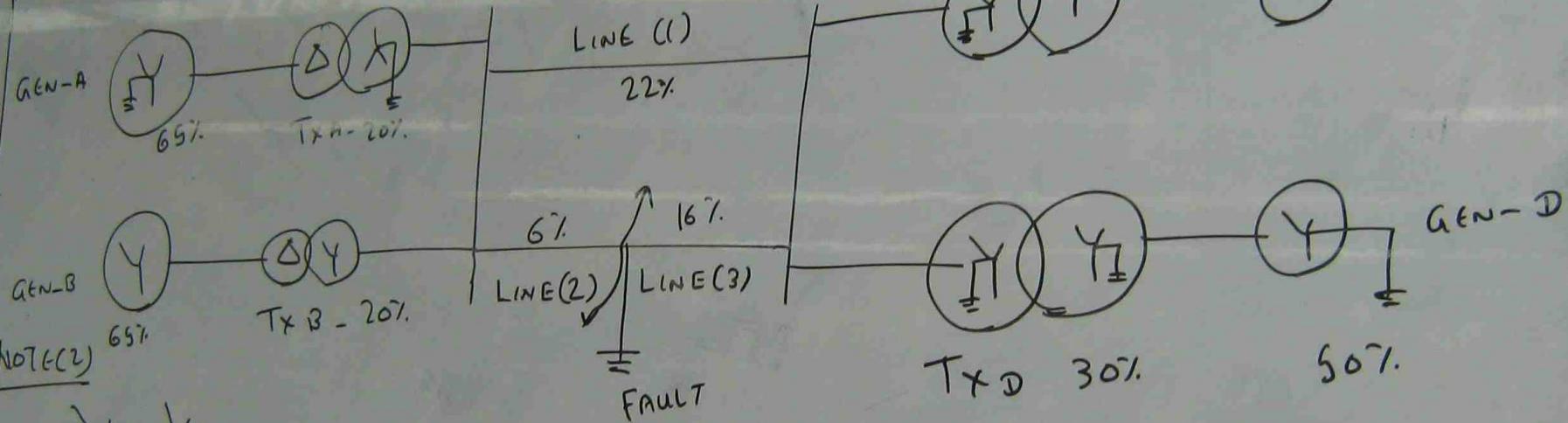Qn DRAW POSITIVE SEQUENCE, NEGATIVE SEQUENCE AND ZERO SEQUENCE EQUIVALENT DIAGRAM FOR THE FOLLOWING POWER SYSTEM.





→ Current \rightarrow $\begin{array}{c} Y \\ \Delta \\ Y \end{array}$ INCLUDE BOTH EQUIPMENTS IN ZERO SEQUENCE DIAGRAM

→ Current \rightarrow $\begin{array}{c} Y \\ \Delta \end{array}$ REMOVE $\begin{array}{c} Y \end{array}$ INCLUDING $\begin{array}{c} Y \end{array}$ IN ZERO SEQUENCE DIAGRAM

→ $\begin{array}{c} Y \\ \Delta \end{array}$ REMOVE BOTH IN ZERO SEQUENCE DIAGRAM

→ $\begin{array}{c} Y \\ \Delta \\ Y \end{array}$ REMOVE $\begin{array}{c} Y \end{array}$ INCLUDING $\begin{array}{c} Y \\ \Delta \\ Y \end{array}$


POSITIVE
SEQUENCE
DIAGRAM

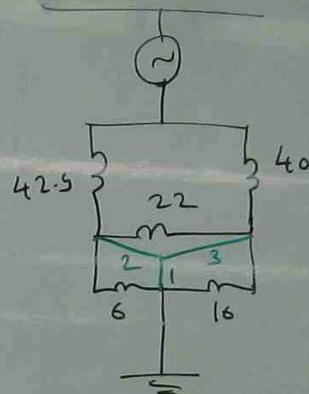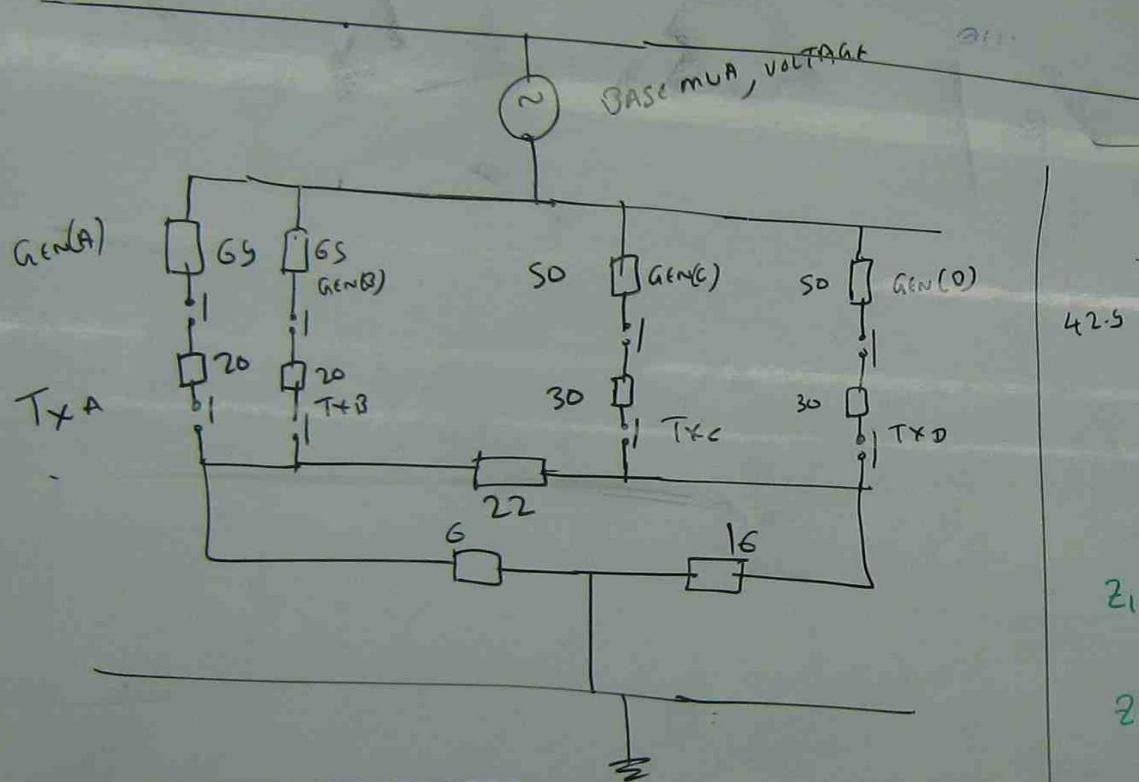

$$Z_1 = \frac{6 \times 16}{6 + 16 + 22} = 2.2$$


$$Z_2 = \frac{6 \times 22}{6 + 16 + 22} = 3$$
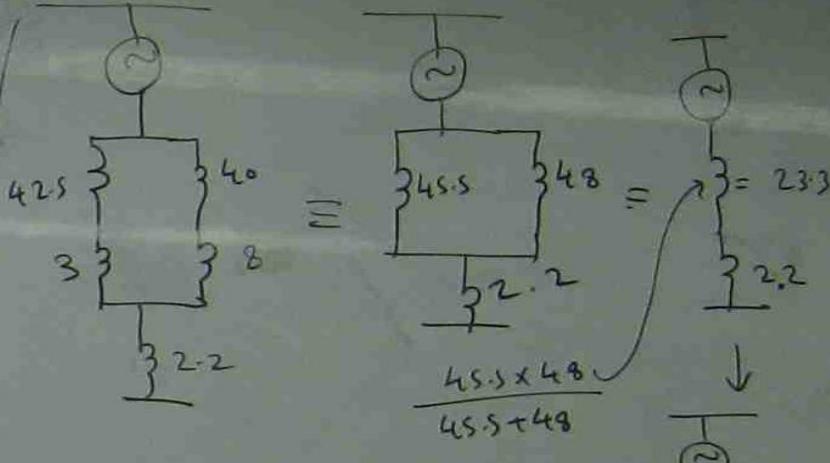
$$Z_3 = \frac{22 \times 16}{6 + 16 + 22} = 8$$






POSITIVE SEQUENCE EQUIVALENT DIAGRAM

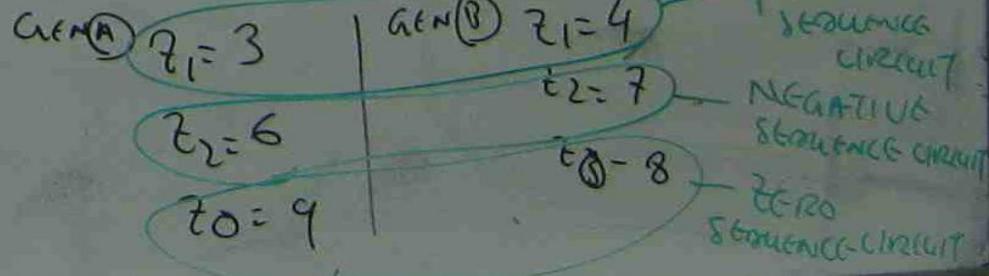IN THIS PROBLEM, THE SAME γ . IMPEDANCE IS GIVEN FOR BOTH POSITIVE, NEGATIVE AND ZERO SEQUENCE. IF THE DIFFERENT POSITIVE, NEGATIVE AND ZERO SEQUENCE IMPEDANCES ARE GIVEN, USE RESPECTIVE VALUE FOR RESPECTIVE EQUIVALENT CIRCUIT




POSITIVE
SEQUENCE
DIAGRAM

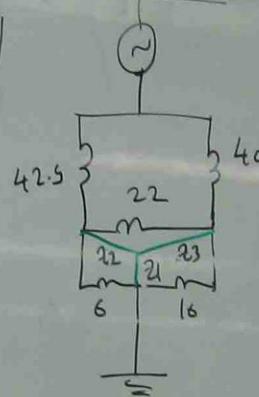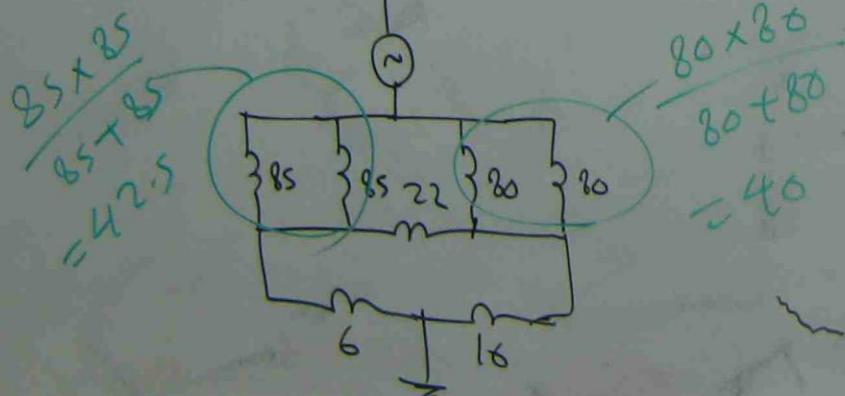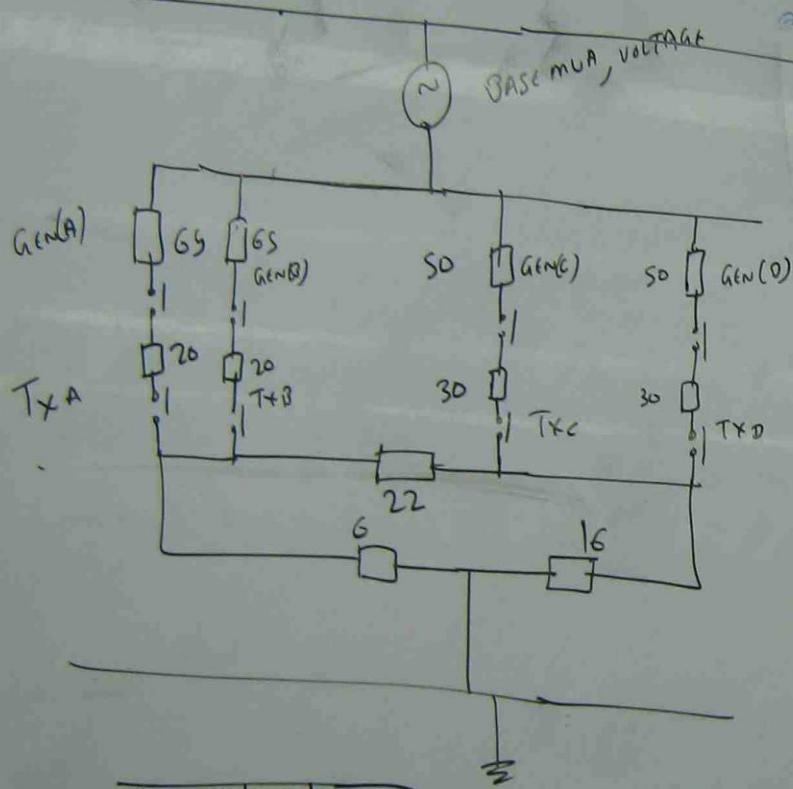


$$Z_1 = \frac{6 \times 16}{6 + 16 + 22} = 2.2$$

$$Z_2 = \frac{6 \times 22}{6 + 16 + 22} = 3$$
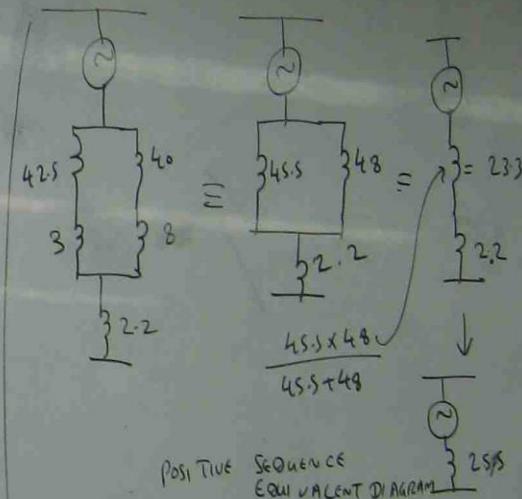
$$Z_3 = \frac{22 \times 16}{6 + 16 + 22} = 8$$



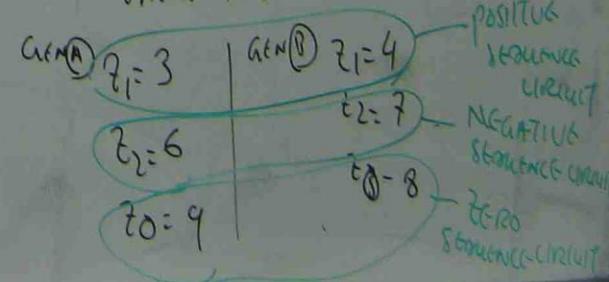IN THIS PROBLEM, THE SAME Z . IMPEDANCE IS GIVEN FOR BOTH POSITIVE, NEGATIVE AND ZERO SEQUENCE. IF THE DIFFERENT POSITIVE, NEGATIVE AND ZERO SEQUENCE IMPEDANCES ARE GIVEN, USE RESPECTIVE VALUE FOR RESPECTIVE EQUIPMENT CIRCUIT




NEGATIVE SEQUENCE EQUIVALENT CIRCUIT


CONSTANT VOLTAGE SOURCE, INCLUDE IMPEDANCE

233

2

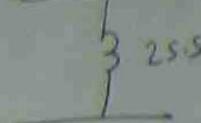

ZERO SEQUENCE EQUIVALENT DIAGRAM

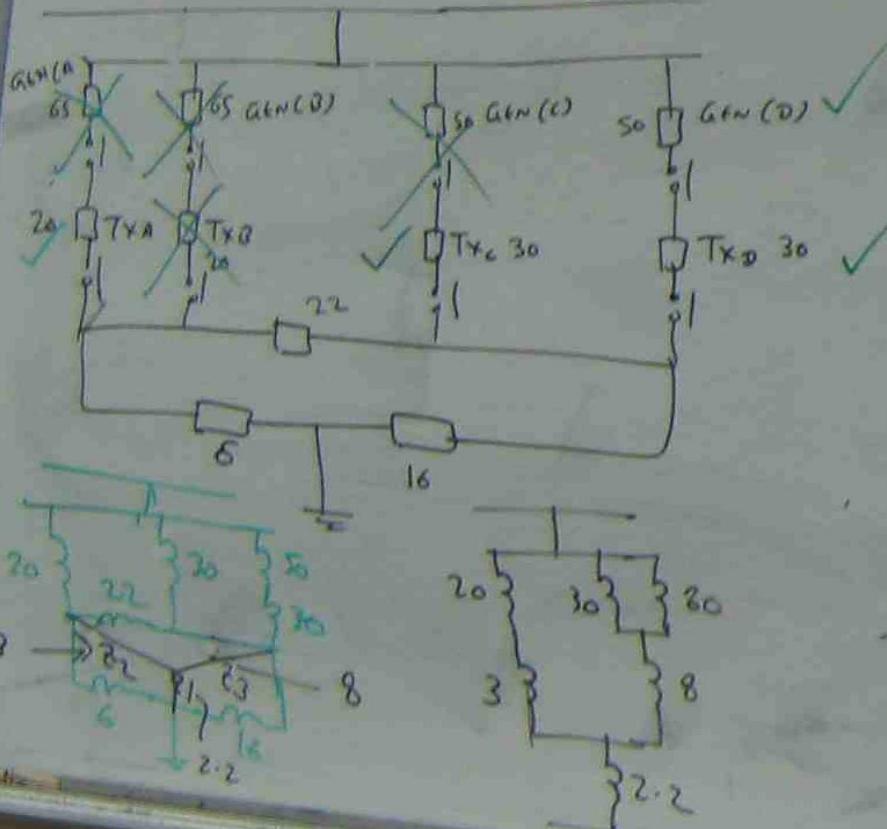

$$\begin{array}{c} \text{23} \\ \left\{ \begin{array}{l} 30+80 \\ 30+20 \end{array} \right\} 8 \\ \left\{ \begin{array}{l} 22 \\ 22 \end{array} \right\} \\ = 23 \end{array} \quad \begin{array}{c} 29.8 \\ \left\{ \begin{array}{l} 23+29.8 \\ 23+29.8 \end{array} \right\} \\ \left\{ \begin{array}{l} 12.9 \\ 2.2 \end{array} \right\} \\ = 15.1 \end{array}$$

POSITIVE
SEQUENCE
DIAGRAM

SELECT BASE MUA = 100 MUA

$$Z_{\text{NEW}} = \frac{\text{BASE MUA}}{\text{MUA OLD}} \times Z_{\text{OLD}}$$

GEN (A)

$$Z_1 = \frac{100}{50} \times 32.5 = 65\%$$

$$Z_2 = \frac{100}{50} \times 45 = 90\%$$

$$Z_0 = \frac{100}{50} \times 60 = 120\%$$

GEN (B)

$$Z_1 = \frac{100}{50} \times 32.5 = 65$$

$$Z_2 = \frac{100}{50} \times 45 = 90$$

$$Z_0 = \frac{100}{50} \times 60 = 120$$

OLD

Tx(A) $z_1 = z_2 = z_0 = \frac{100}{50} \times 10 = 20$

LINE (2)

$$\% z = \frac{Z(SL) \times \text{BASE mva}}{(KV)^2} \times 100$$

Tx(B) $z_1 = z_2 = z_0 = \frac{100}{50} \times 10 = 20$

LINE (1)

$$z_1 = z_2 = \frac{36.8 \times 100}{(132)^2} \times 100 = 22.7$$

Tx(C) $z_1 = z_2 = \frac{100}{40} \times 12 = 30$

$$z_0 = \frac{134 \times 100}{(132)^2} \times 100 = 77.7$$

$$z_0 = \frac{100}{40} \times 6 = 15$$

Tx(D) $z_1 = z_2 = \frac{100}{40} \times 12 = 30$

SIMILARLY
LINE (2)

$$z_0 = \frac{100}{40} \times 6 = 15$$

$$z_1 = z_2 = 67.$$

$$z_0 = 21.1$$


GEN (C) $z_1 = 50, z_2 = 30, z_0 = 25$

LINE (3) $z_1 = z_2 = 16$


$$z_0 = 86$$

GEN (D) $z_1 = 50, z_2 = 30, z_0 = 25$

POSITIVE

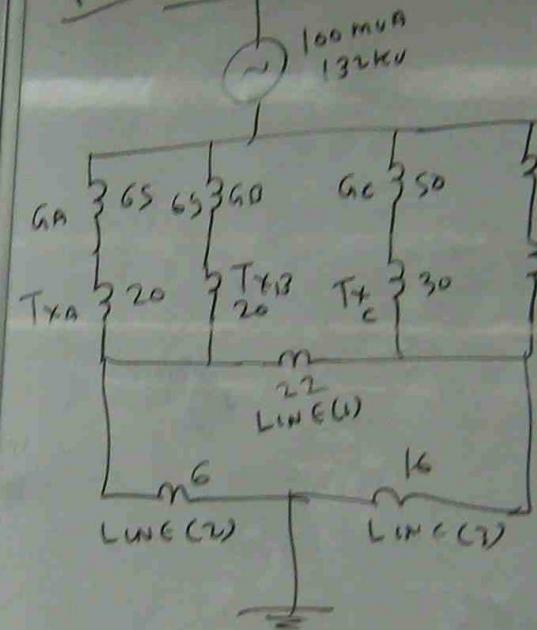

NEG GATING

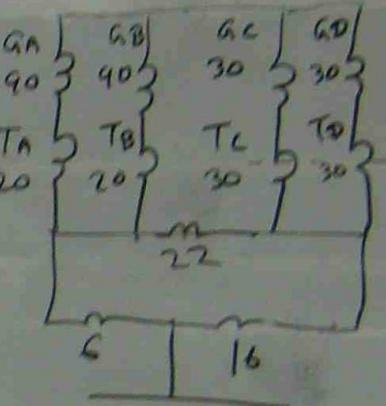

ZERO

