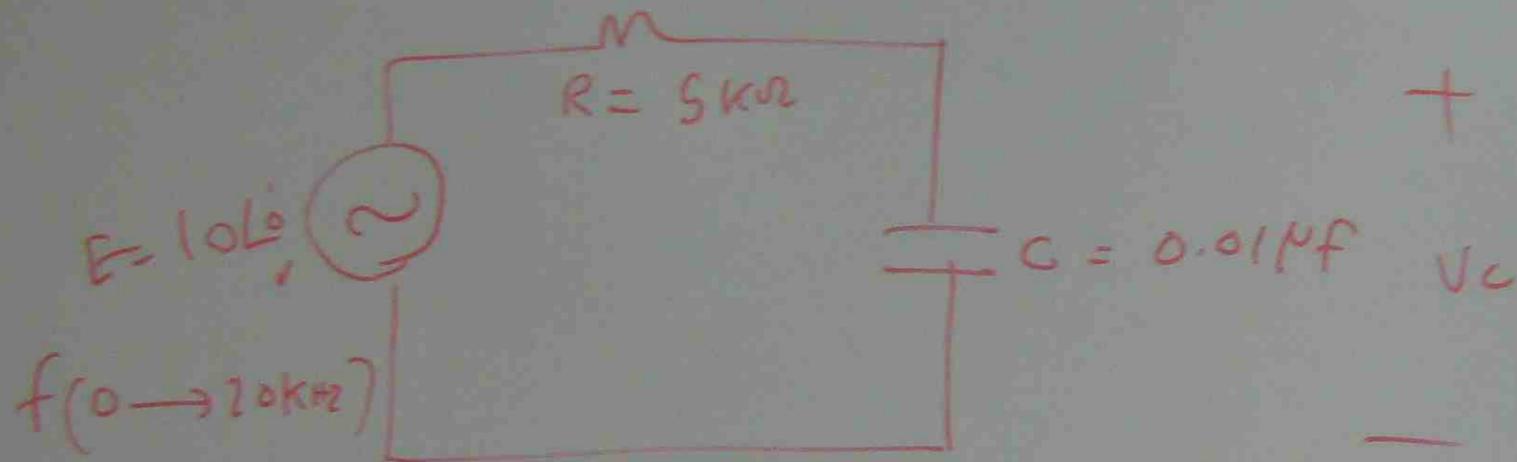


FREQUENCY RESPONSE OF SERIES RC CIRCUIT



$$X_c = \frac{1}{2\pi f C}$$

$$f = 0 \rightarrow X_c = \frac{1}{2\pi \times 0 \times C} = \infty \quad Z = \infty$$

$$f = 100\text{ Hz} \quad X_c = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.1416 \times 100 \times 0.01 \times 10^{-6}} = 159.16\text{ k}\Omega$$

$$Z_T = \sqrt{R^2 + X_c^2} = \sqrt{5^2 + 159.16^2} = 159.24\text{ k}\Omega$$


$$\theta_T = -\tan^{-1} \frac{X_c}{R} = -\tan^{-1} \frac{159.16}{5} = -88.2^\circ$$

$$f = 1 \text{ kHz} \Rightarrow X_C = \frac{1}{2 \times 3.1416 \times 1 \times 10^3 \times 0.01 \times 10^{-6}} = 15.92 \text{ k}\Omega$$

$$Z_T = \sqrt{5^2 + 15.92^2} = 16.69 \text{ k}\Omega$$

$$\theta_T = -\tan^{-1} \frac{X_C}{R} = -\tan^{-1} \frac{15.92}{5} = -72.54$$



f	Z_T	θ_T
0	∞	-90°
5 kHz	5.93 k Ω	-32.48
10 kHz	5.23 k Ω	-17.66
15 kHz	5.11 k Ω	-11.93
20 kHz	5.06 k Ω	-9.04

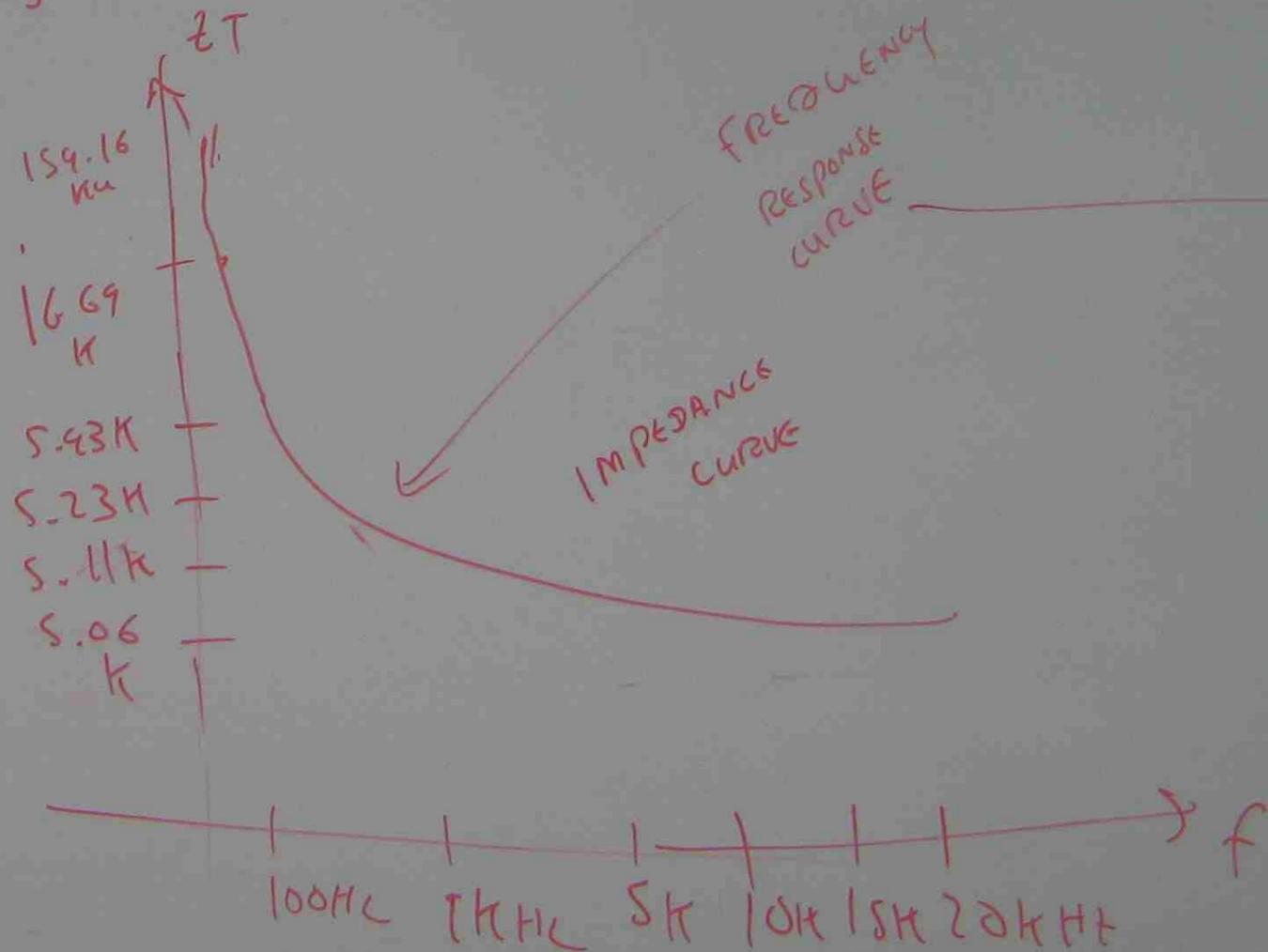

$$0.01 \times 10^{-6} = 15.92 \text{ k}\Omega$$


$$= 16.69 \text{ k}\Omega$$
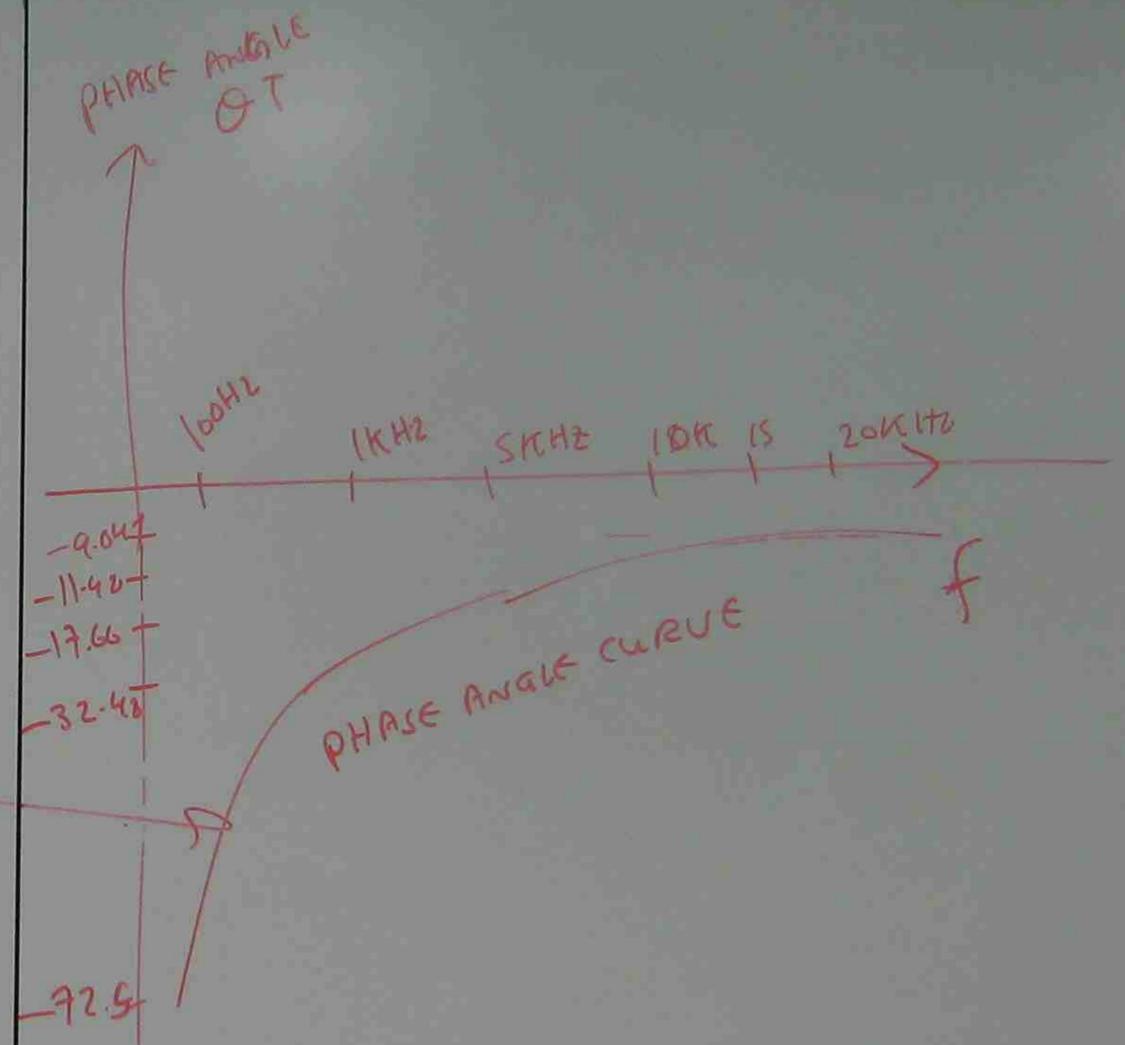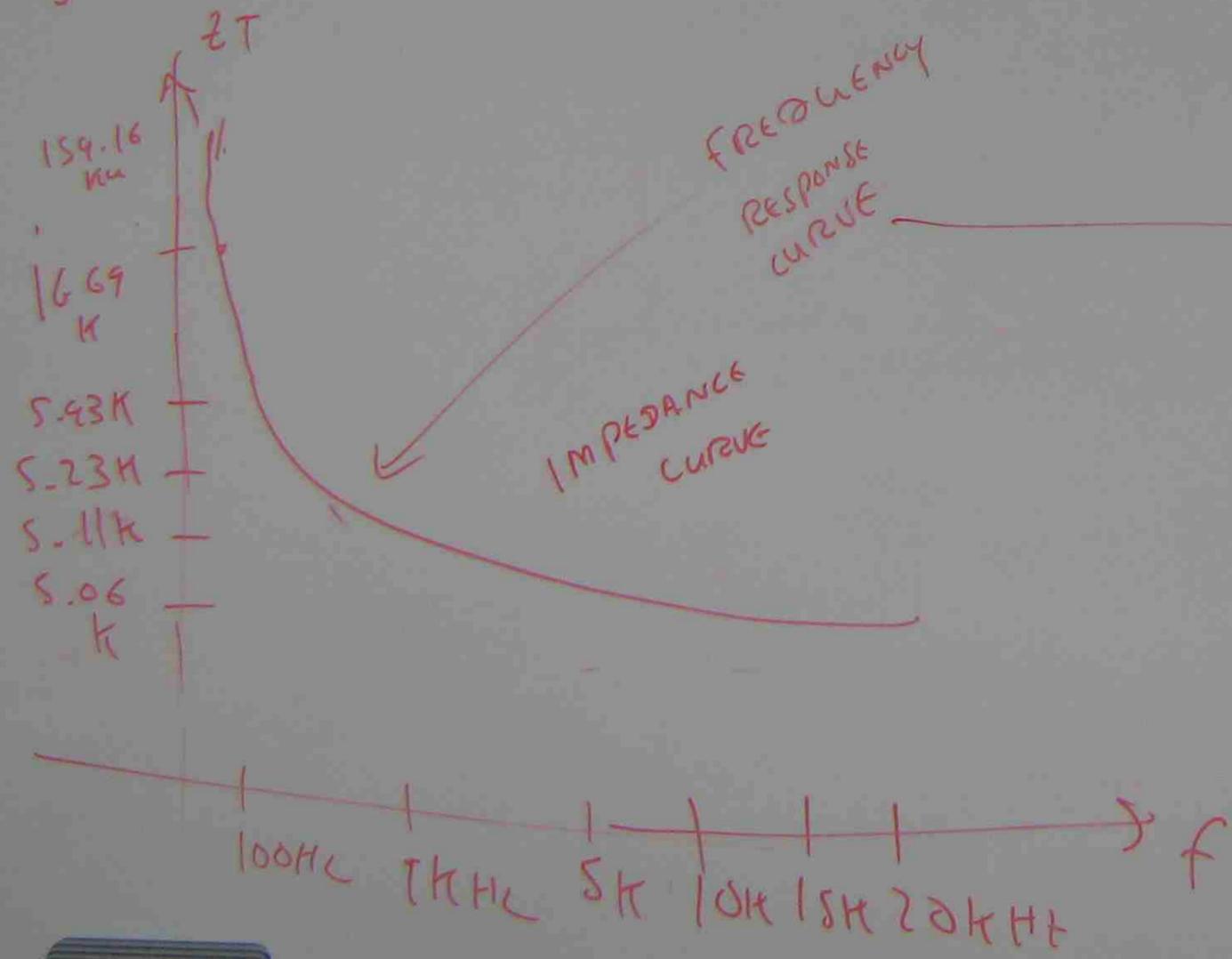
$$\frac{-1}{s} \frac{15.92}{s} = -72.54$$



FREQUENCY RESPONSE OF PARALLEL R-L NETWORK

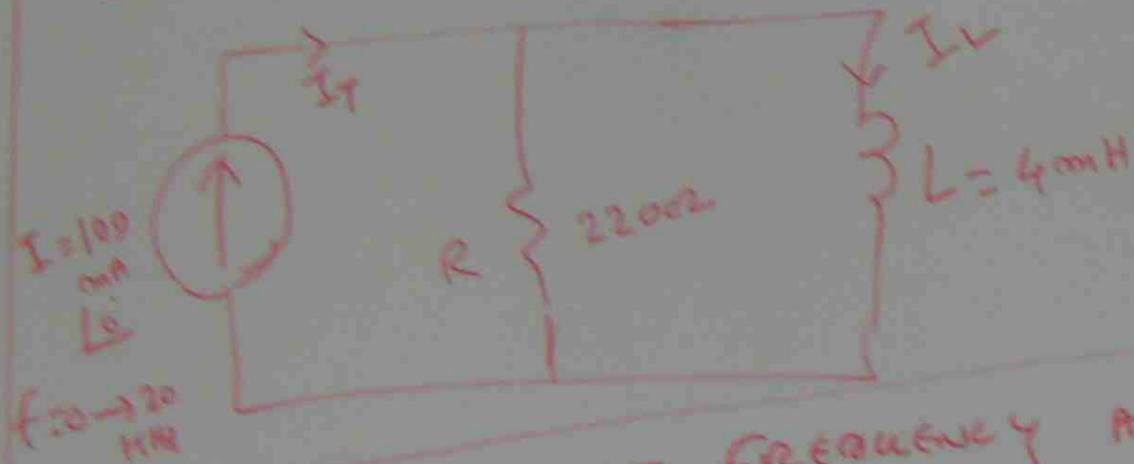DETERMINE THE FREQUENCY RESPONSE OF IMPEDANCE, PHASE ANGLE AND CURRENT OF THE FOLLOWING PARALLEL R-L NETWORK



CALCULATE RESONANT FREQUENCY AT WHICH CIRCUIT RESISTANCE AND INDUCTIVE REACTANCE ARE EQUAL

$$X_L = 2\pi fL, R$$

$$f = ? \Rightarrow R = X_L$$

$$220 = 2 \times 3.1416 \times f \times 4 \times 10^{-3}$$

$$f = \frac{220}{2 \times 3.1416 \times 4 \times 10^{-3}} = 8.75 \text{ kHz}$$

V_0
↓
1 kHz

8.75 kHz

5 kHz, 10 kHz, 15 kHz, 20 kHz

1 kHz

$$X_L = 2\pi fL = 2 \times 3.1416 \times 1 \times 10^3 \times 4 \times 10^{-3} = 25.12 \Omega$$



$$\frac{1}{Z_T} = \frac{1}{R} + \frac{1}{X_L}$$

$$\frac{1}{Z_T} = \frac{R + X_L}{R \cdot X_L}$$

$$Z_T = \frac{R(jX_L)}{R + jX_L} = \frac{220 \times j25.12}{220 + j25.12}$$

CURRENT

1 kHz, 15 kHz, 20 kHz

$$= 2 \times 3.1416 \times 1 \times 10^3 \times 4 \times 10^{-3}$$

$$\frac{1}{Z_T} = \frac{1}{R} + \frac{1}{jX_L}$$

$$= \frac{R + jX_L}{R \cdot jX_L}$$


$$= \frac{220 + j25.12}{220 \cdot j25.12}$$

$$Z_T = \frac{220 \angle 0^\circ \times 25.12 \angle 90^\circ}{\sqrt{220^2 + 25.12^2} \angle \tan^{-1} \frac{25.12}{220}}$$

$$= \frac{220 \times 25.12 \angle 90^\circ}{\sqrt{220^2 + 25.12^2} \angle 8.76^\circ}$$

$$Z_T = 24.96 \angle 90^\circ - 8.76^\circ$$

$$Z_T = 24.96 \angle 83.49^\circ$$

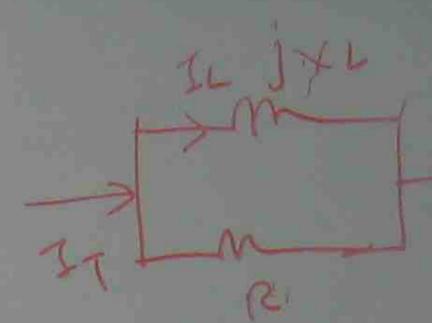

$$I_L = I_T \times \frac{R}{R + jX_L}$$


$$\text{1 kHz} = 100 \text{ mA} \times \frac{220}{220 + j25.12}$$

$$= 100 \times \frac{220}{\sqrt{220^2 + 25.12^2} \angle \tan^{-1} \frac{25.12}{220}} = 99.5 \angle -6.5^\circ$$

f	Z _T	θ _T	I	φ
1 kHz	24.96	83.49	99.35	-6.5
5	109.1	60.23	86.84	-29.74
10	168.5	41.21	65.88	-48.79
15	189.89	30.28	50.43	-59.72
20	201.53	23.65	40.11	-73.73

FREQUENCY RESPONSE OF PARALLEL R-L NETWORK

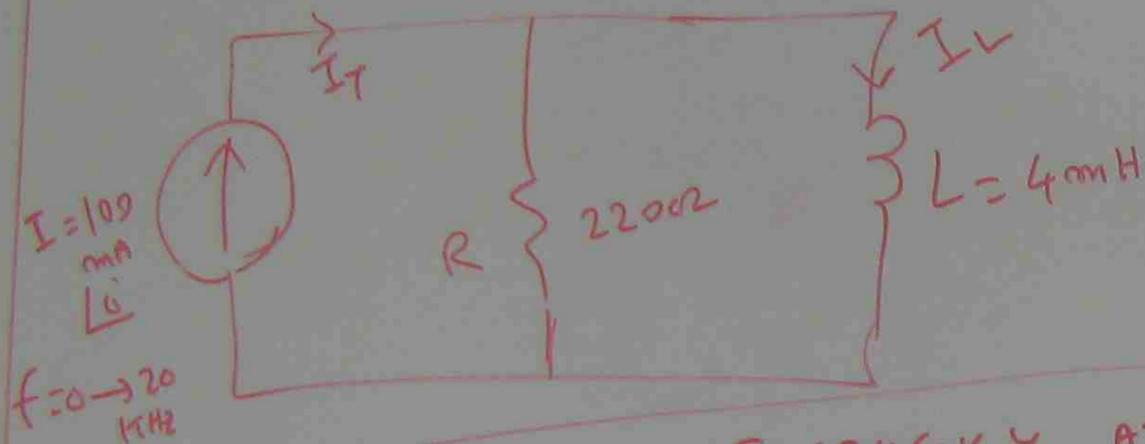Ph
DETERMINE THE FREQUENCY RESPONSE OF IMPEDANCE, PHASE ANGLE AND CURRENT OF THE FOLLOWING PARALLEL R-L NETWORK



V_s
↓
1 kHz 5 kHz, 10 kHz, 15 kHz, 20 kHz
8.75 kHz

CALCULATE RESONANT FREQUENCY AT WHICH CIRCUIT RESISTANCE AND INDUCTIVE REACTANCE ARE EQUAL

$$X_L = 2\pi fL, R$$

$$f = ? \Rightarrow R = X_L$$

$$220 = 2 \times 3.1416 f \times 4 \times 10^{-3}$$

$$f = \frac{220}{2 \times 3.1416 \times 4 \times 10^{-3}} = 8.75 \text{ kHz}$$

1 kHz

$$X_L = 2\pi fL = 2 \times 3.1416 \times 1 \times 10^3 \times 4 \times 10^{-3} = 25.12 \Omega$$



$$\frac{1}{Z_T} = \frac{1}{R} + \frac{1}{X_L}$$

$$\frac{1}{Z_T} = \frac{R + X_L}{R \cdot X_L}$$

$$Z_T = \frac{R(jX_L)}{R + jX_L} = \frac{220 \times j25.12}{220 + j25.12}$$

CURRENT

KHz

15 KHz, 20 KHz

$$= 2 \times 3.1416 \times 10^3 \times 4 \times 10^{-3}$$

$$= \frac{1}{R} + \frac{1}{jX_L}$$

$$= \frac{R + jX_L}{R \cdot jX_L}$$



$$= \frac{220 + j25.12}{220 \cdot j25.12}$$

$$Z_T = \frac{220 \angle 0^\circ \times 25.12 \angle 90^\circ}{\sqrt{220^2 + 25.12^2} \angle \tan^{-1} \frac{25.12}{220}}$$

$$= \frac{220 \times 25.12 \angle 90^\circ}{\sqrt{220^2 + 25.12^2} \angle 8.76^\circ}$$

$$= 24.96 \angle 90^\circ - 8.76^\circ$$

$$Z_T = 24.96 \angle 83.49^\circ$$



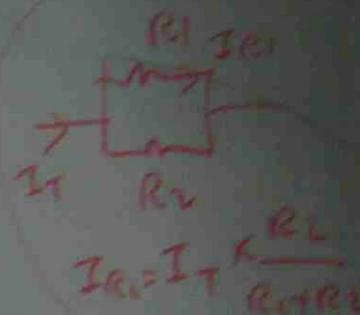
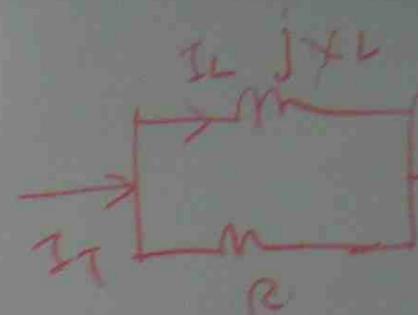


$$I_L = I_T \times \frac{R}{R + jX_L}$$

$$\text{1 KHz} = 100 \text{ mA} \times \frac{220}{220 + j25.12}$$



$$= 100 \times \frac{220}{\sqrt{220^2 + 25.12^2} \angle \tan^{-1} \frac{25.12}{220}} = 99.5 \angle -6.5^\circ$$

f	Z _T	θ _T	I	θ
1 KHz	24.96	83.49	99.35	-6.5
5	109.1	60.23	86.84	-29.74
10	168.5	41.21	65.88	-48.79
15	189.89	30.28	50.43	-59.72
20	201.83	23.65	40.11	-73.73

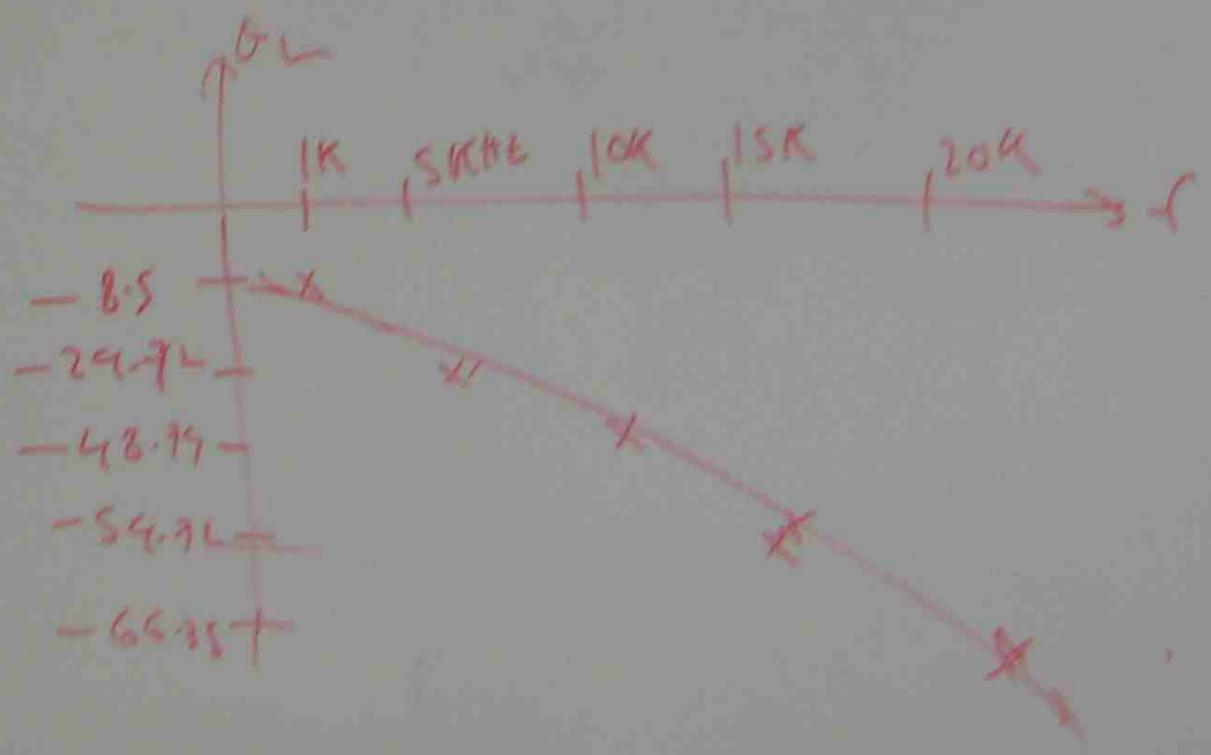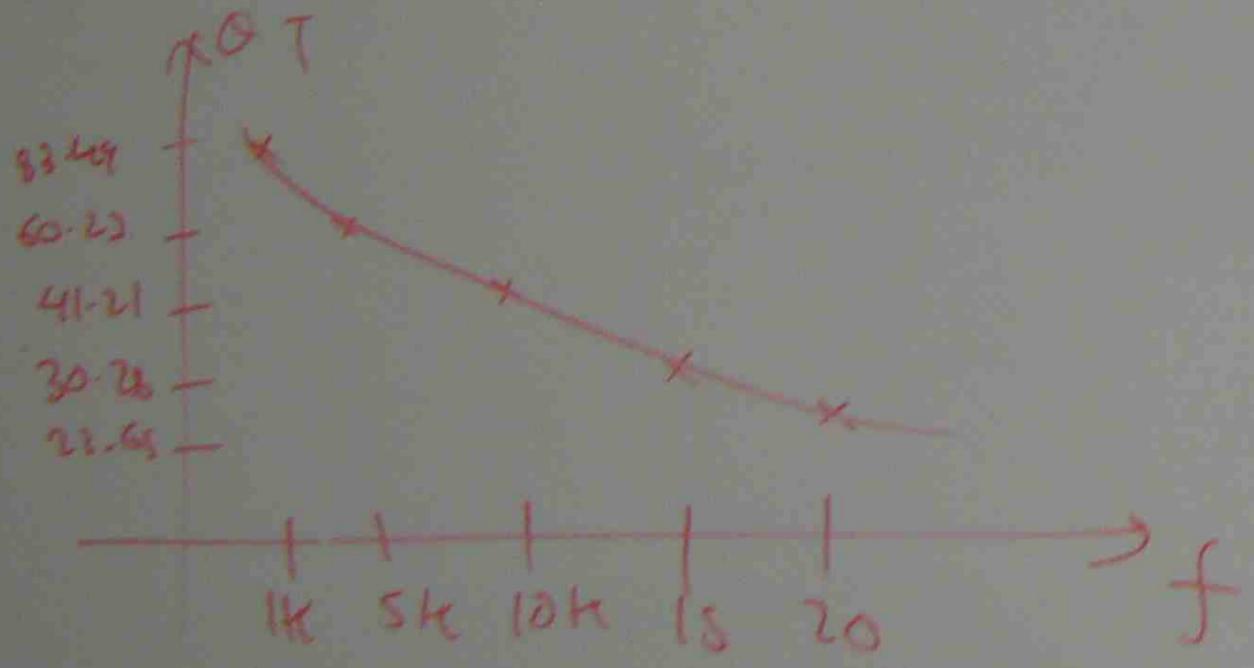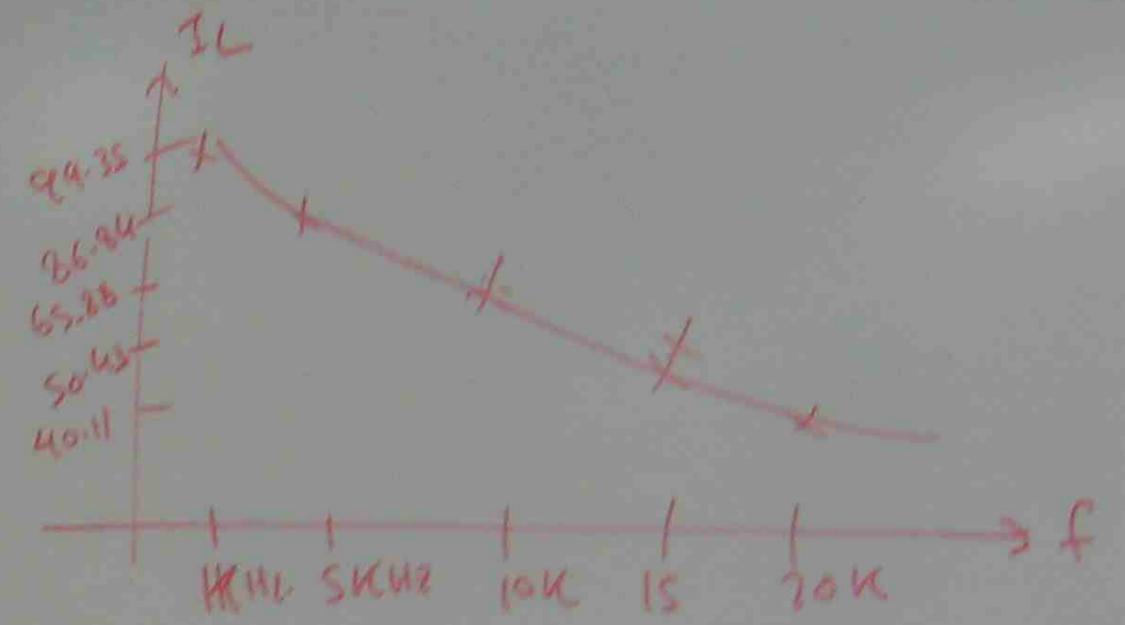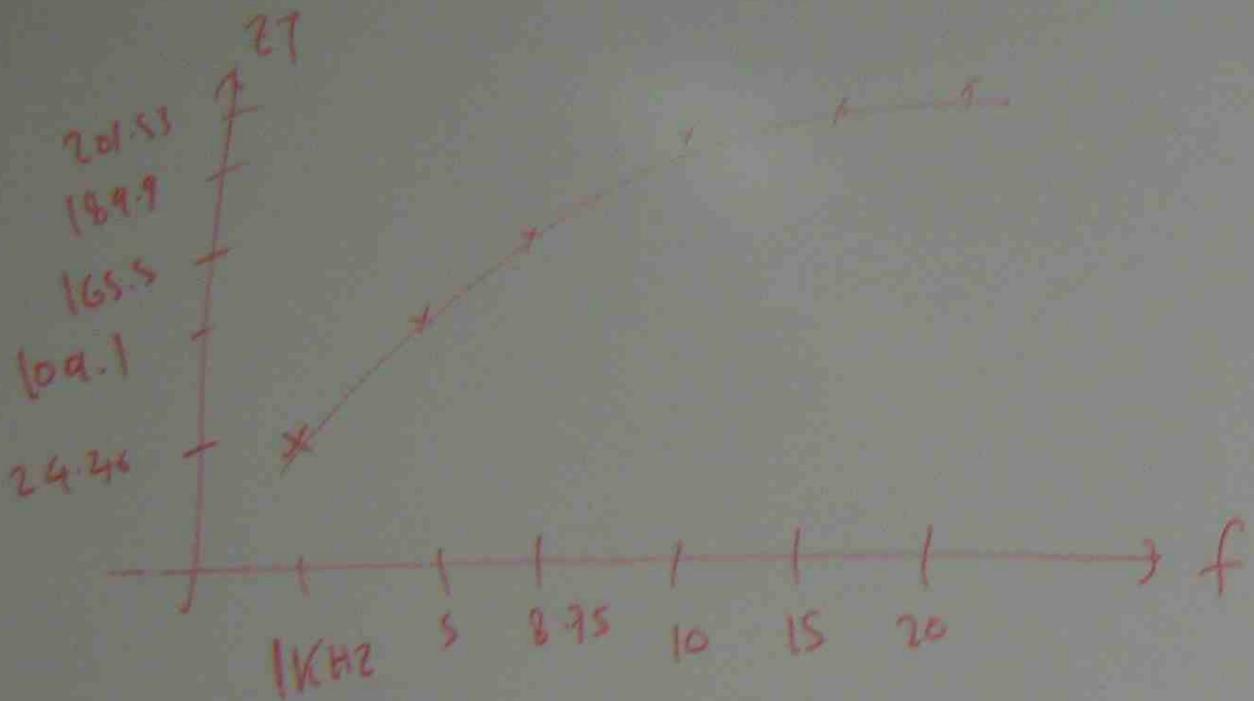

PLOTTING FREQUENCY RESPONSE CURVE FOR LOW PASS AND HIGH PASS FILTERS

HIGH PASS FILTER

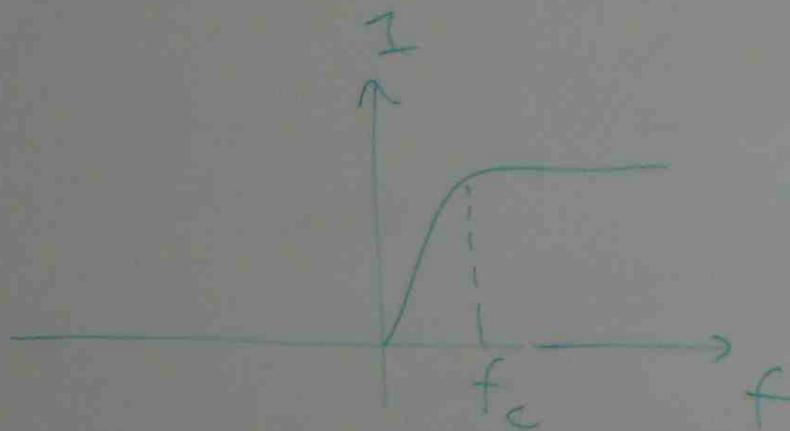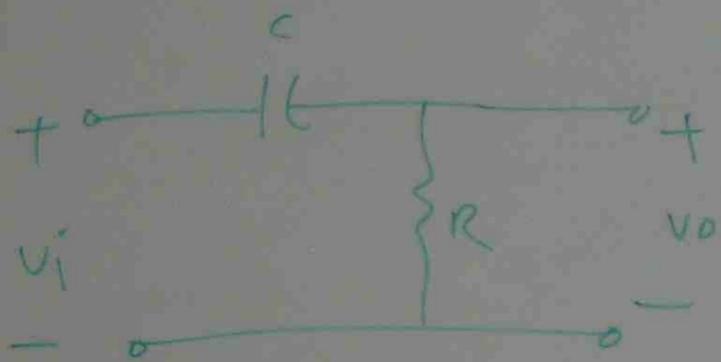

BODE PLOT

FREQUENCY GAIN (dB) = $-20 \log_{10} \frac{f_c}{f}$

FREQUENCY GAIN



f_c = CRITICAL FREQUENCY
(CUT-OFF FREQUENCY)

VOLTAGE GAIN

$$|A_{v dB}| = 20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{f_c}{f}\right)^2}}$$

PHASE ANGLE $\phi = -\tan^{-1} \frac{f_c}{f}$

LOW PASS FILTER (RC)

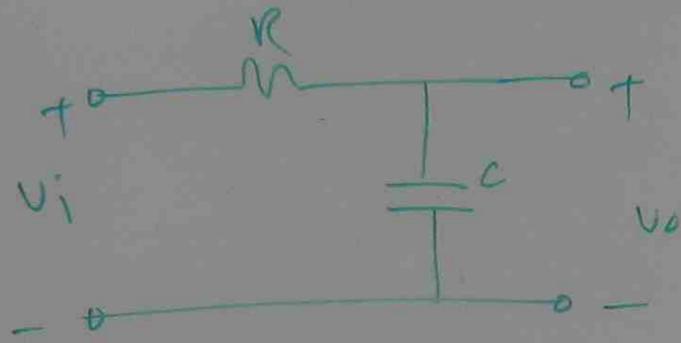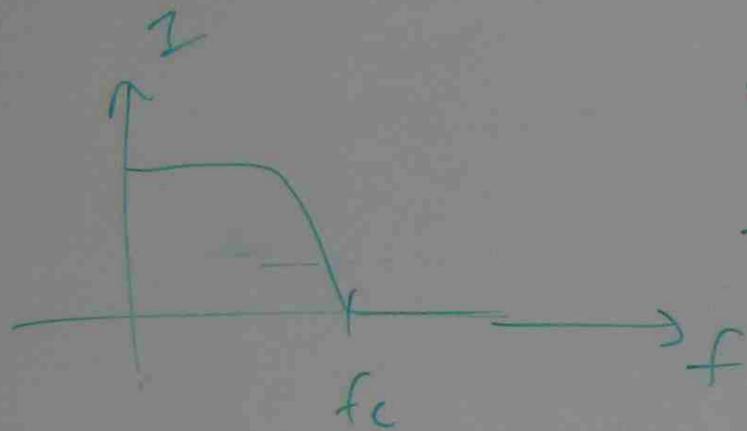

$$\text{FREQUENCY GAIN dB} = -20 \log_{10} \frac{f}{f_c}$$

VOLTAGE GAIN

$$|A_V \text{ dB}| = 20 \log_{10} \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$


PHASE ANGLE $\phi = \tan^{-1} \frac{f}{f_c}$

HIGH PASS FILTER WITH ADDITIONAL RESISTOR (HIGH PASS FILTER WITH ATTENUATED OUTPUT)



$$A_V = \frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} \left[\frac{1}{1 - j \frac{f_c}{f}} \right]$$

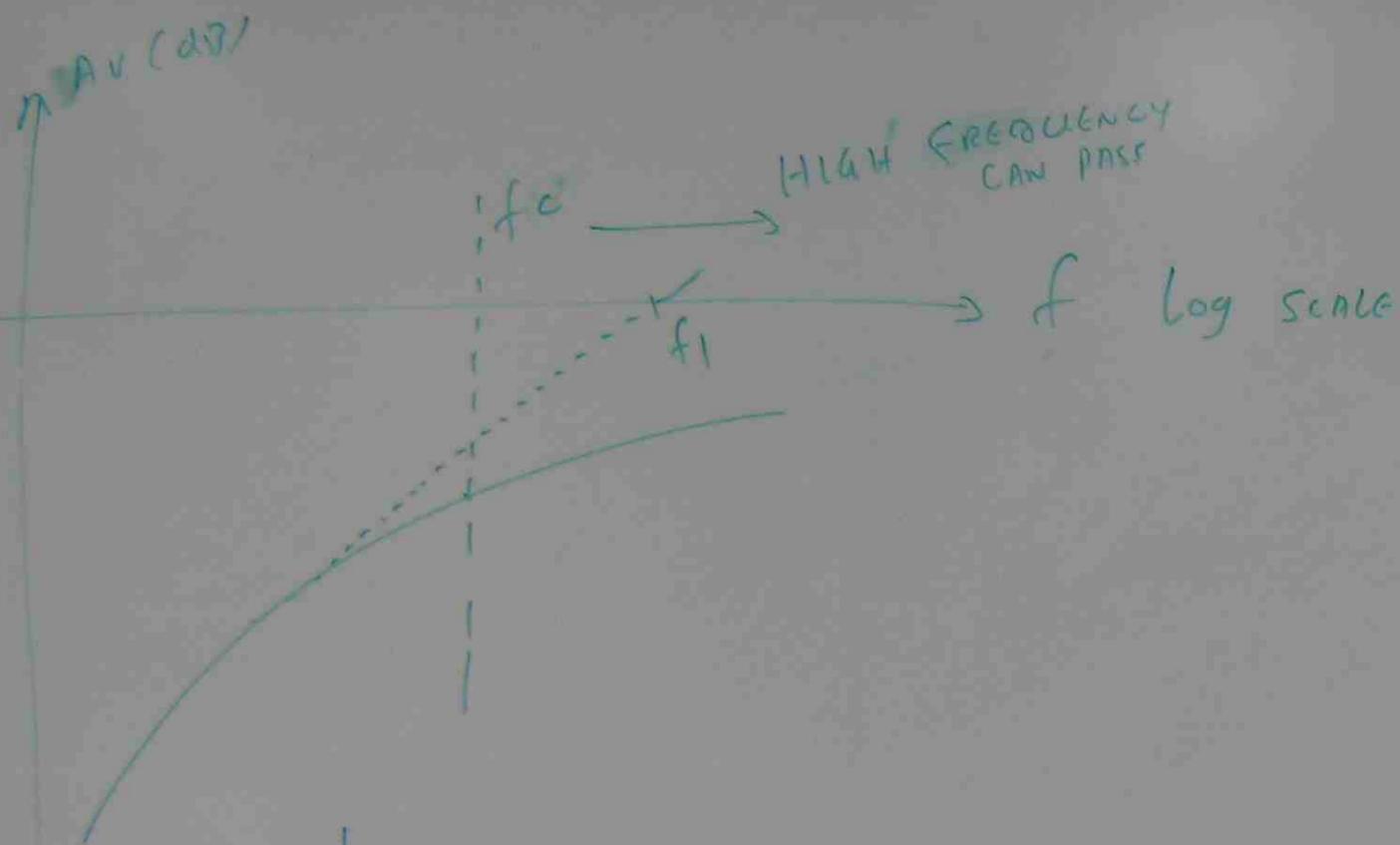
$$[A_V \text{ dB}] = -20 \log_{10} \frac{R_1 + R_2}{R_2}$$



$$f_1 = \frac{1}{2\pi R_2 C}$$

$$f_c = \frac{1}{2\pi (R_1 + R_2) C}$$

LOW PASS FILTER WITH LIMITED ATTENUATION

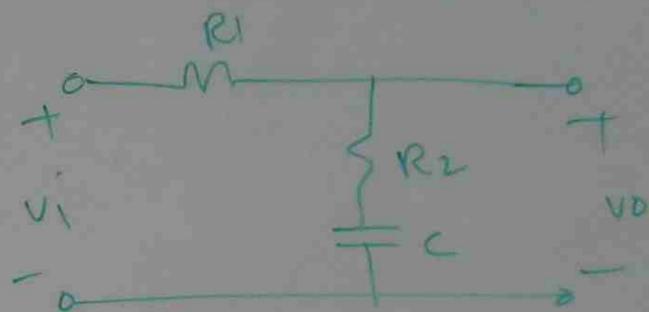


BY INSERTING R_2 , THE ATTENUATION LEVEL OF HIGH FREQUENCY IS LIMITED

$$V_o = \frac{R_2}{R_1 + R_2} V_i$$

$$A_v (\text{dB}) = -20 \log_{10} \frac{R_1 + R_2}{R_2}$$

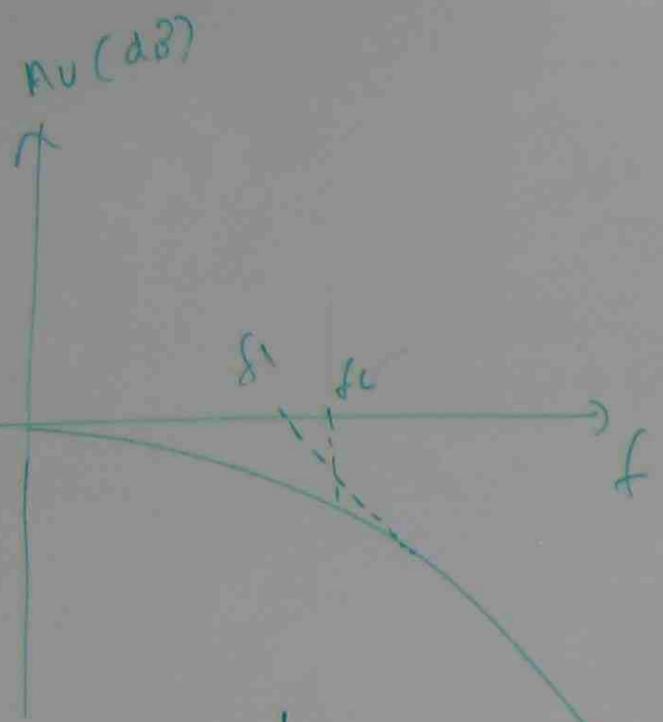
$$A_v = \frac{1 + j \frac{f}{f_1}}{1 + j \frac{f}{f_c}}$$



$$f_1 = \frac{1}{2\pi R_2 C}$$


$$f_c = \frac{1}{2\pi (R_1 + R_2) C}$$

PHASE ANGLE PLOT

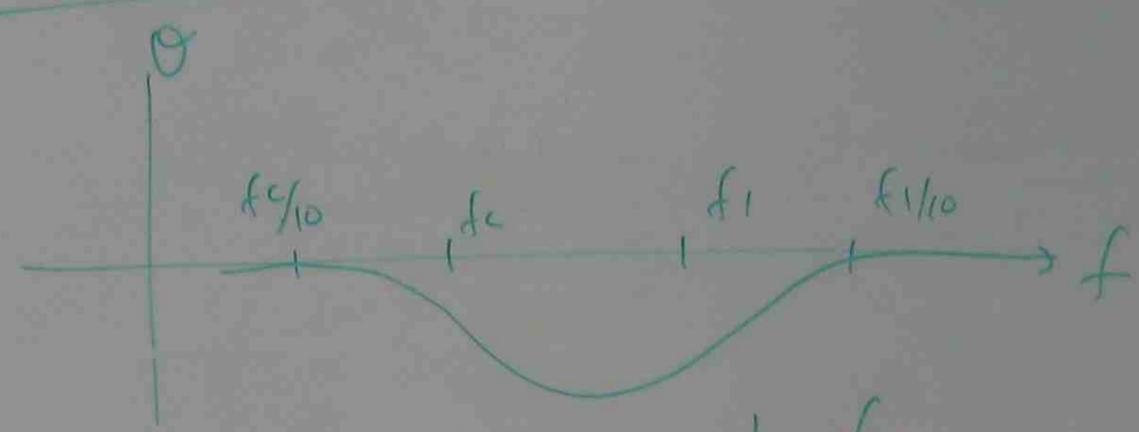


$$\theta = -\tan^{-1} \frac{f}{f_1} - \tan^{-1} \frac{f}{f_c}$$

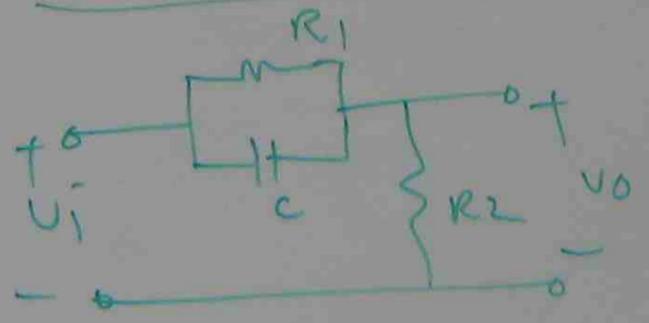HIGH PASS FILTER WITH LIMITED ATTENUATION




$$A_V = \frac{V_O}{V_I} = \frac{1 - j f_c/f}{1 - j f_c/f}$$

$$f_1 = \frac{1}{2\pi R_1 C}, \quad f_c = \frac{1}{2\pi (R_1 || R_2) C}$$

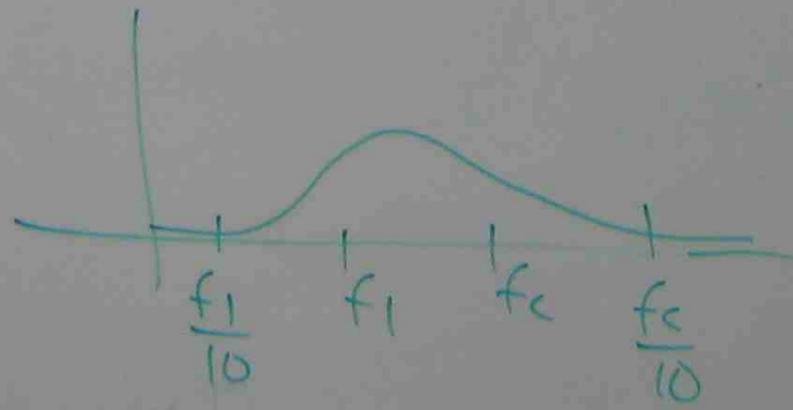

$$\theta = -\tan^{-1} \frac{f_1}{f} + \tan^{-1} \frac{f_c}{f}$$

ph

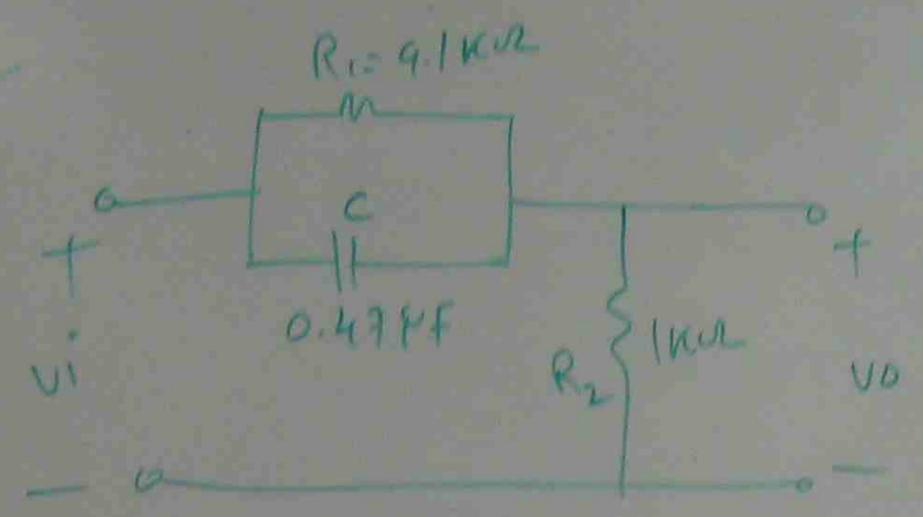

FOR THE ABOVE CIRCUIT,

(A) SKETCH $A_{v \text{ dB}}$ VS f USING LOG SCALE

(B) SKETCH ϕ VS f USING LOG SCALE

HIGH PASS FILTER WITH LIMITED ATTENUATION

BREAK FREQUENCIES

$$f_1 = \frac{1}{2\pi R_1 C}$$

$$= \frac{1}{2 \times 3.1416 \times 9.1 \times 10^3 \times 0.47 \times 10^{-6}}$$


$$= 37.2 \text{ Hz}$$

$$f_c = \frac{1}{2\pi \frac{R_1 R_2}{R_1 + R_2} C}$$

$$= \frac{1}{2 \times 3.1416 \times \frac{9.1 \times 10^3 \times 1 \times 10^3}{9.1 \times 10^3 + 1 \times 10^3} \times 0.47 \times 10^{-6}}$$

$$f_c = 376.25 \text{ Hz}$$

pb

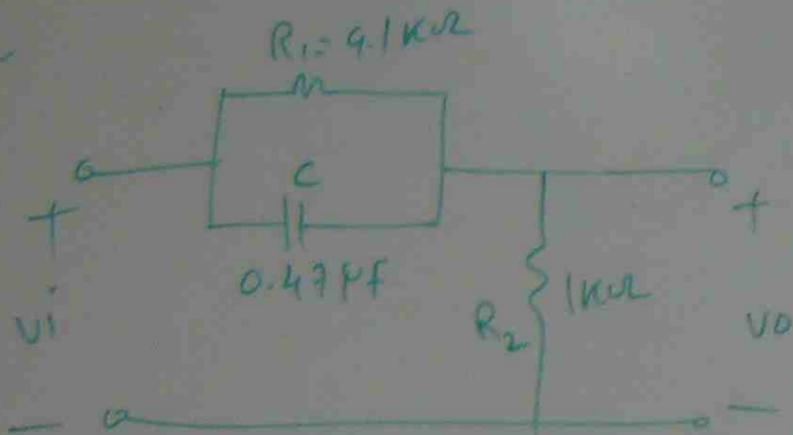

FOR THE ABOVE CIRCUIT,

(A) SKETCH $A_{v,dB}$ VS f USING LOG SCALE

(B) SKETCH ϕ VS f USING LOG SCALE

HIGH PASS FILTER WITH LIMITED ATTENUATION

BREAK FREQUENCIES

$$f_1 = \frac{1}{2\pi R_1 C}$$

$$= \frac{1}{2 \times 3.1416 \times 9.1 \times 10^3 \times 0.47 \times 10^{-6}}$$
$$= 37.2 \text{ Hz}$$


$$f_c = \frac{1}{2\pi \frac{R_1 R_2}{R_1 + R_2} C}$$

$$= \frac{1}{2 \times 3.1416 \times \frac{9.1 \times 10^3 \times 1 \times 10^3}{9.1 \times 10^3 + 1 \times 10^3} \times 0.47 \times 10^{-6}}$$

$$f_c = 376.25 \text{ Hz}$$

$$10^3 \times 0.47 \times 10^{-6}$$
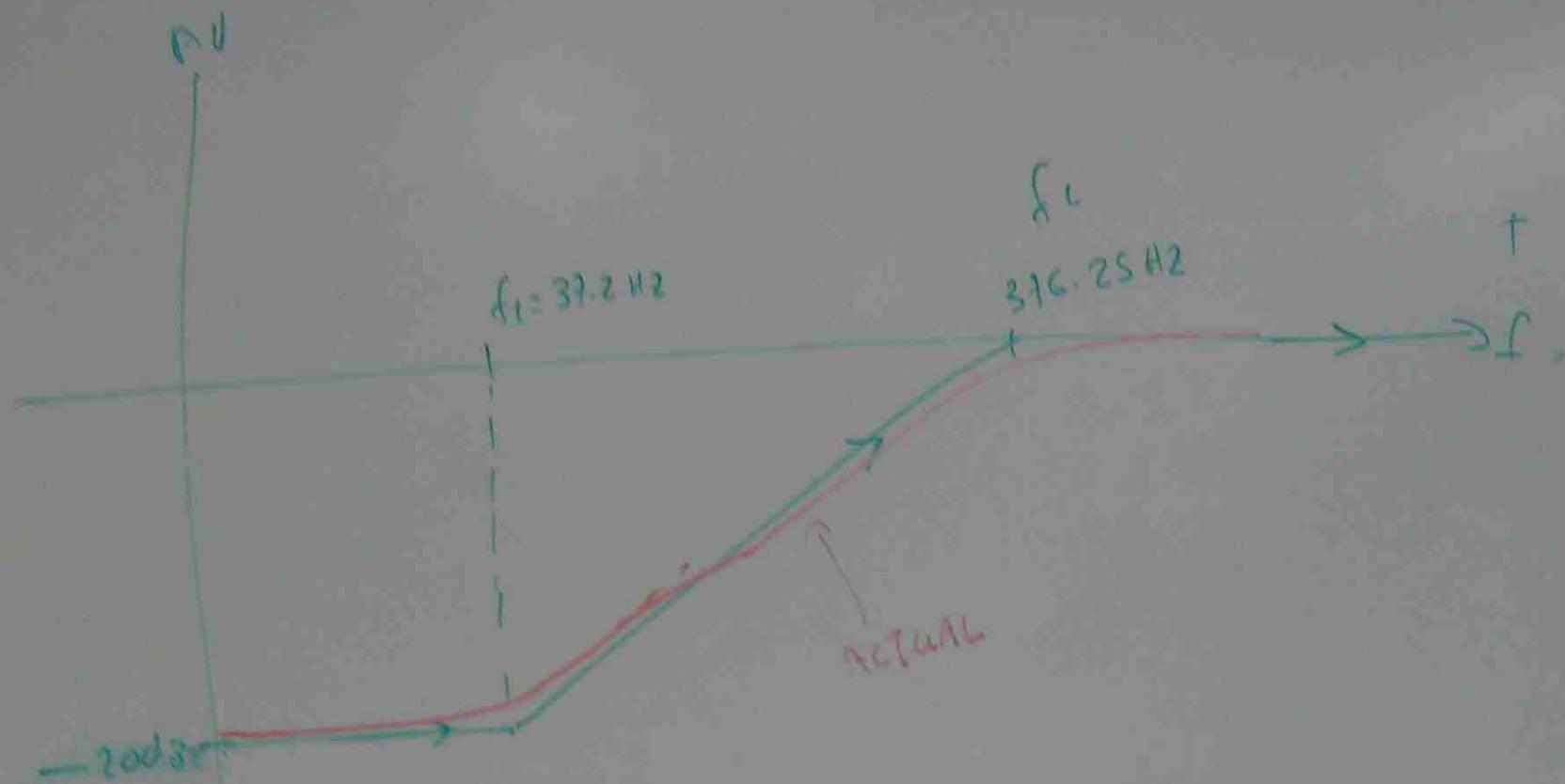
$$\frac{0.5 \times 10^3}{10^3 + 10^3} \times 0.47 \times 10^{-6}$$




MAXIMUM LEVEL

ATTENUATION =


$$\begin{aligned} A_{v dB} &= -20 \log_{10} \frac{R_1 + R_2}{R_2} \\ &= -20 \log_{10} \frac{9.1 + 1}{1} \\ &= -20.09 \text{ dB} \end{aligned}$$

HIGH PASS
RESISTOR
ATTENUA

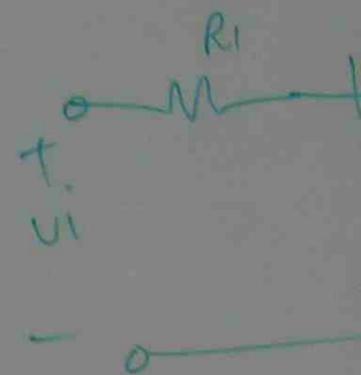

$$A_v = \frac{V_o}{V_i}$$

$$[A_{v dB}] =$$

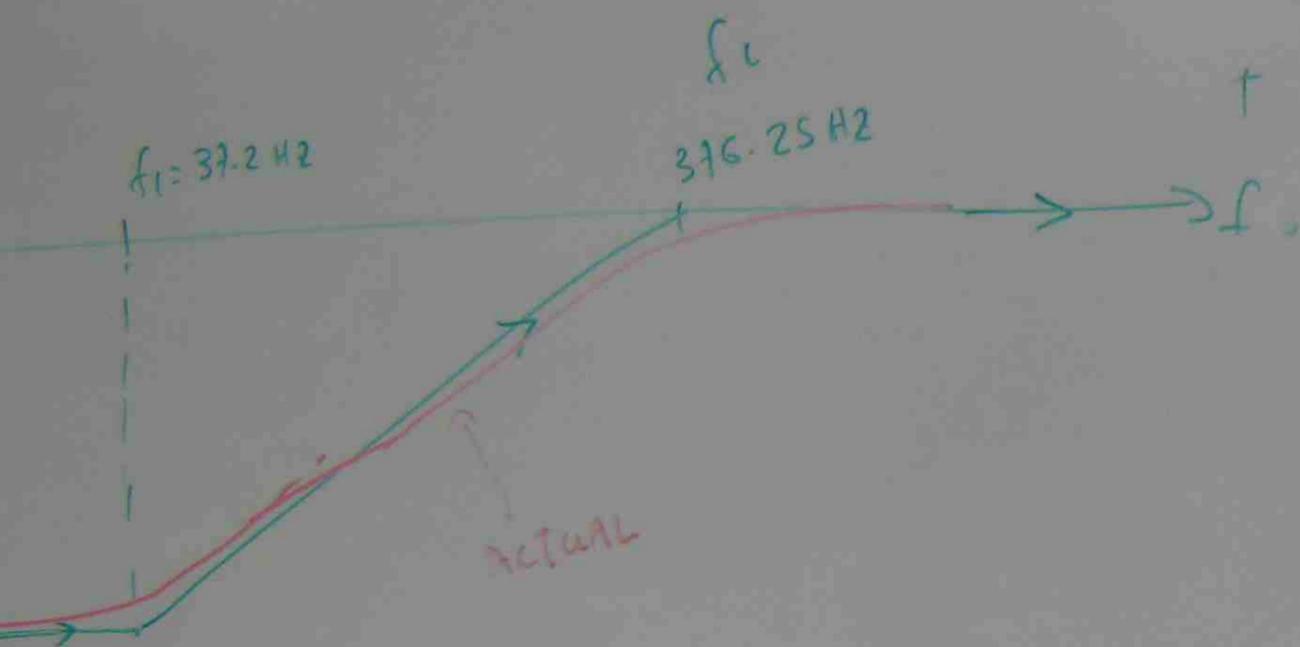

max LEVEL

ATTENUATION =

$$\begin{aligned}
 A_{V \text{ dB}} &= -20 \log_{10} \frac{R_1 + R_2}{R_2} \\
 &= -20 \log_{10} \frac{4.14 + 1}{1} \\
 &= -20.09 \text{ dB}
 \end{aligned}$$

$$(b) \quad \theta = -\tan^{-1} \frac{f_1}{f} + \tan^{-1} \frac{f_c}{f}$$


$$f = 37.2 \text{ Hz}$$

$$\theta = -\tan^{-1} \frac{37.2}{37.2} + \tan^{-1} \frac{376.25}{37.2}$$

$$= 39.35^\circ$$

SELECT FREQUENCY BETWEEN f_1 & f_c
IF WE SELECT 120 Hz
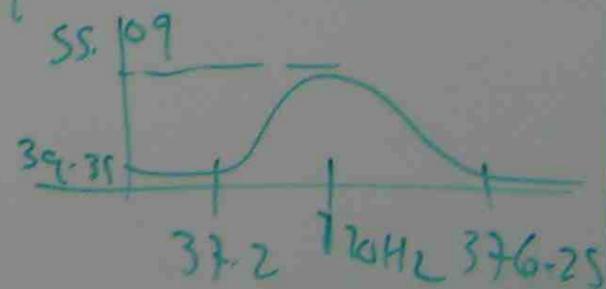
$$\begin{aligned}
 \theta &= -\tan^{-1} \frac{37.2}{120} + \tan^{-1} \frac{376.25}{120} \\
 &= 55.09^\circ
 \end{aligned}$$






$$(b) \quad \theta = -\tan^{-1} \frac{f_1}{f} + \tan^{-1} \frac{f_c}{f}$$


$$\begin{aligned} \text{f} = 37.2 \text{ Hz} \\ \theta = -\tan^{-1} \frac{37.2}{37.2} + \tan^{-1} \frac{376.25}{37.2} \\ = 39.35^\circ \end{aligned}$$

SELECT FREQUENCY BETWEEN f_1 & f_c
IF WE SELECT 170 Hz

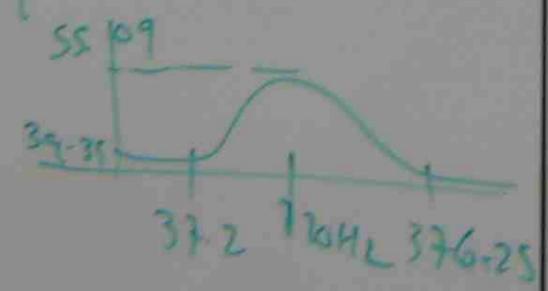
$$\begin{aligned} \theta = -\tan^{-1} \frac{37.2}{170} + \tan^{-1} \frac{376.25}{170} \\ = 55.09^\circ \end{aligned}$$



\uparrow Av (dB)

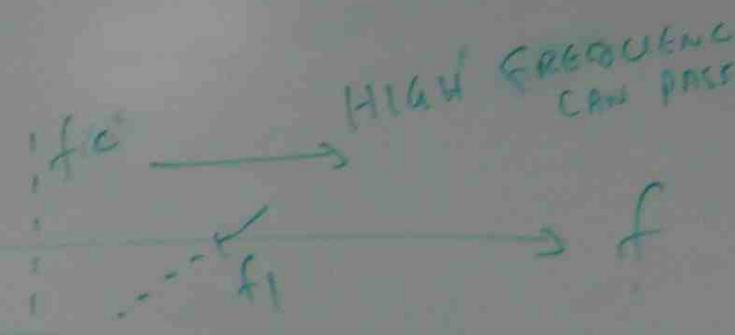
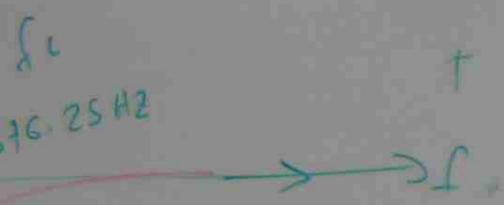
$$\begin{aligned} \text{f} = 376.25 \\ \theta = -\tan^{-1} \frac{37.2}{37.2} + \tan^{-1} \frac{376.25}{37.2} \\ = 39.35^\circ \end{aligned}$$



(b)

$$\theta = -\tan^{-1} \frac{f_1}{f} + \tan^{-1} \frac{f_c}{f}$$

$f = 37.2 \text{ Hz}$


$$\theta = -\tan^{-1} \frac{37.2}{37.2} + \tan^{-1} \frac{376.25}{37.2}$$

$$= 39.35^\circ$$


SELECT FREQUENCY BETWEEN f_1 & f_c
IF WE SELECT 120 Hz

$$\theta = -\tan^{-1} \frac{37.2}{120} + \tan^{-1} \frac{376.25}{120}$$

$$= 55.09^\circ$$

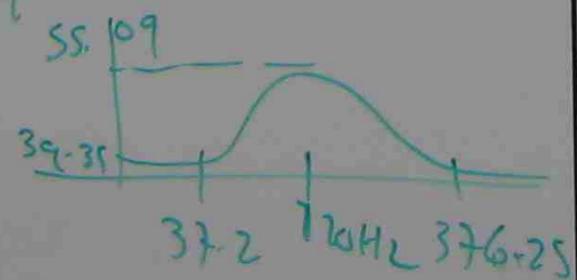

$\uparrow A_v \text{ (dB)}$


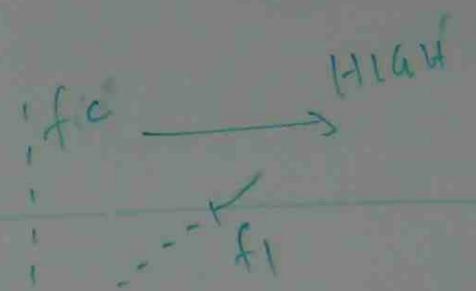


$f = 376.25$

$$\theta = -\tan^{-1} \frac{37.2}{376.25} + \tan^{-1} \frac{376.25}{376.25}$$


$$= 39.35^\circ$$

FREQUENCY RESPONSE OF RC CIRCUIT

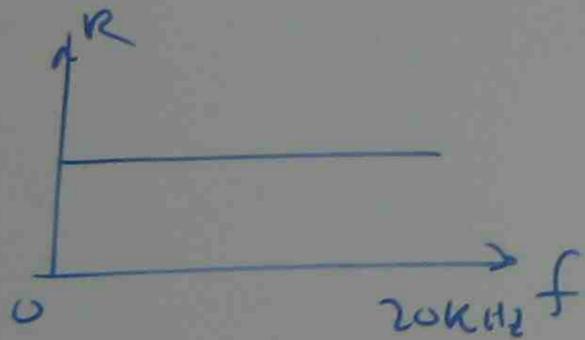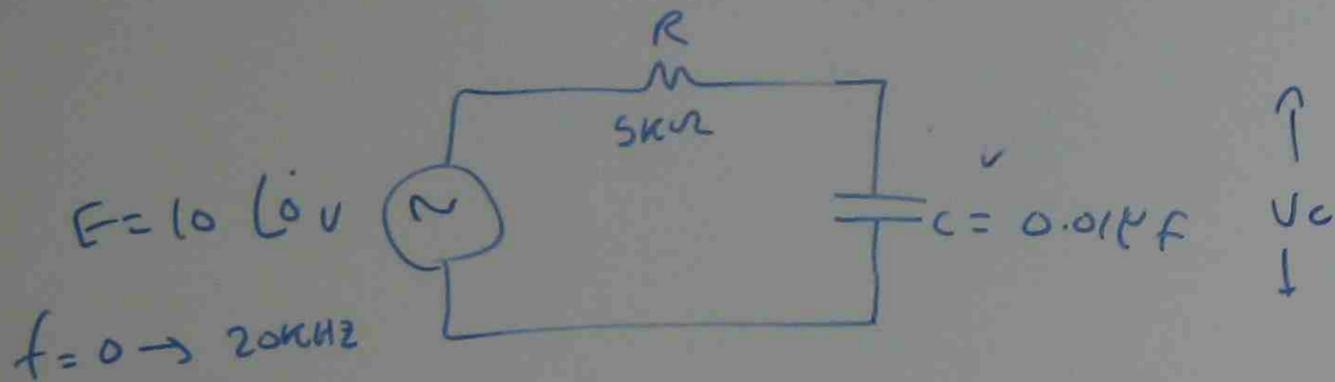

$$X_C = \frac{1}{2\pi f C}$$


$f \uparrow \quad X_C \downarrow$

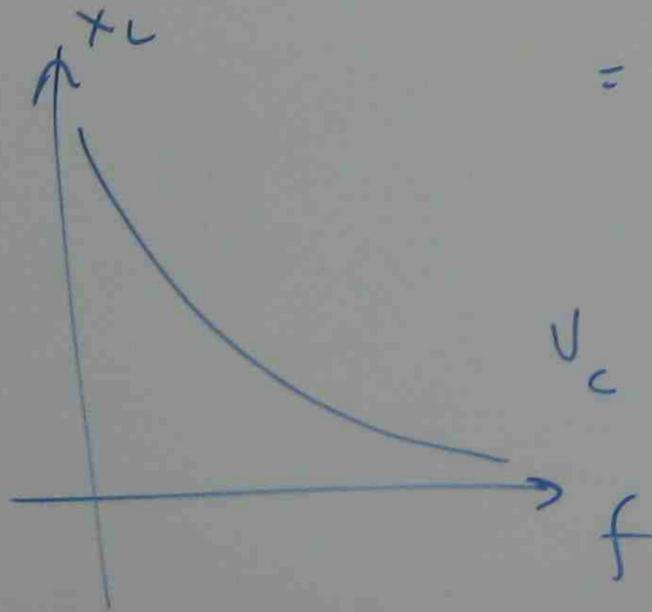


$$\begin{aligned}
 V_C &= E \times \frac{X_C}{R + X_C} \\
 &= E \times \frac{-jX_C}{R + (-jX_C)} \\
 &= \frac{E \times (-jX_C)}{R - jX_C}
 \end{aligned}$$

$$\begin{aligned}
 V_C &= \frac{E \times X_C \angle -90^\circ}{\sqrt{R^2 + X_C^2} \angle -\tan^{-1} \frac{X_C}{R}} \\
 \theta &= -\tan^{-1} \frac{X_C}{R}
 \end{aligned}$$




By change

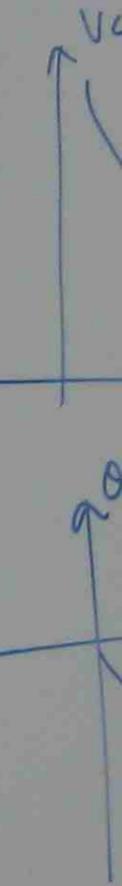

BY CHANGING "f", ϕ & V_L ALSO CHANGE


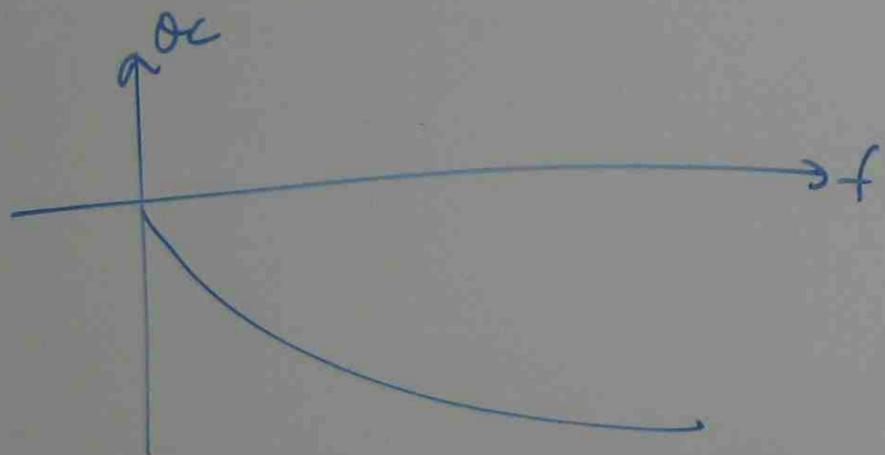


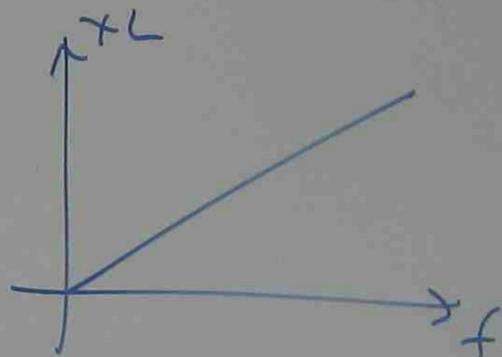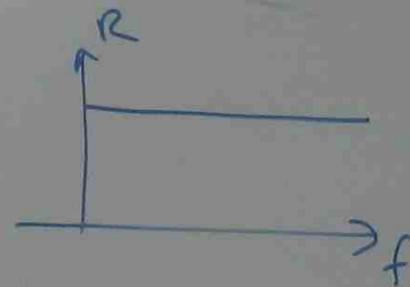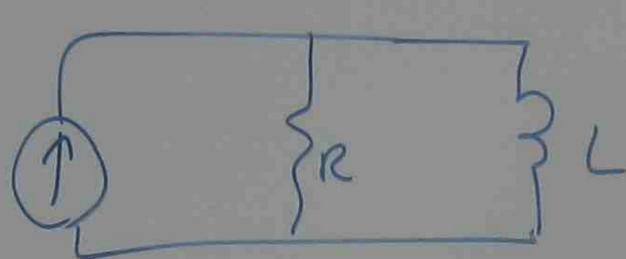FREQUENCY RESPONSE OF PARALLEL R-L NETWORK





$$X_L = 2\pi fL$$
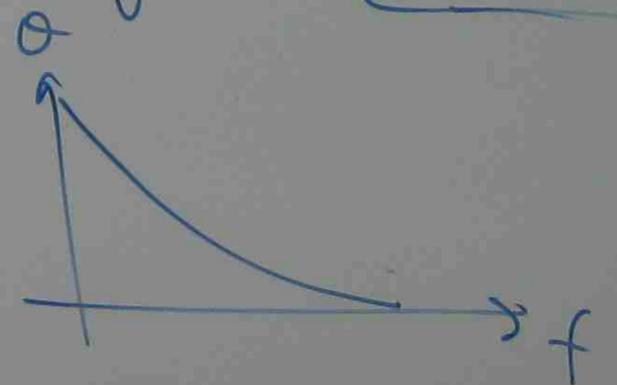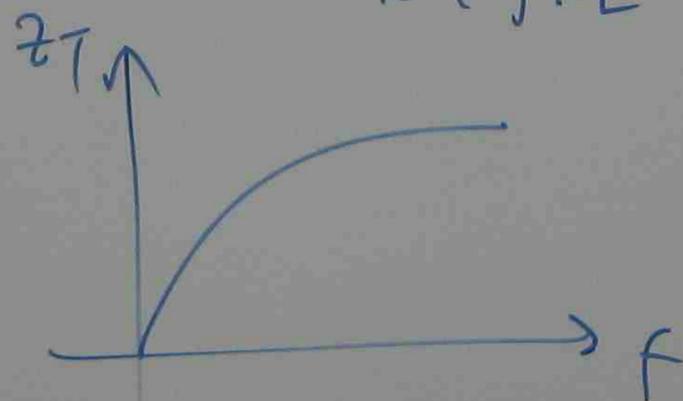
$$Z_T = \frac{R \times jX_L}{R + jX_L} = \frac{R \times X_L \angle +90^\circ}{\sqrt{R^2 + X_L^2} \angle \tan^{-1} \frac{X_L}{R}}$$



BRIDGE NETWORK (AC)

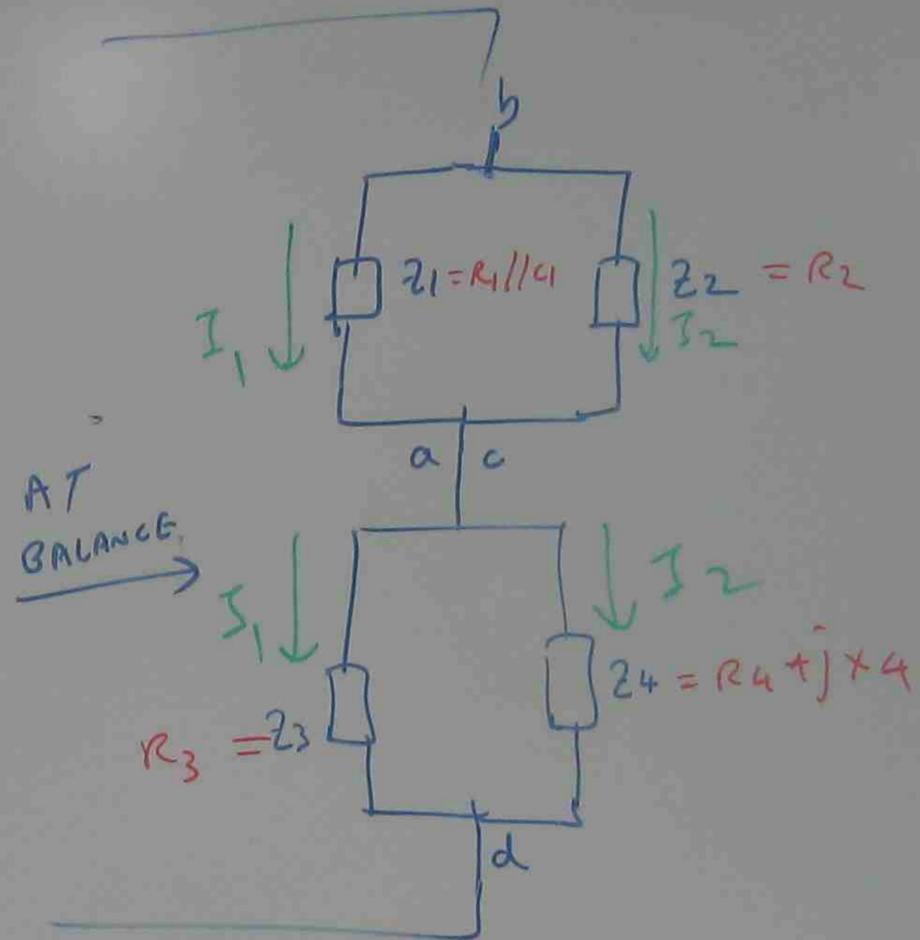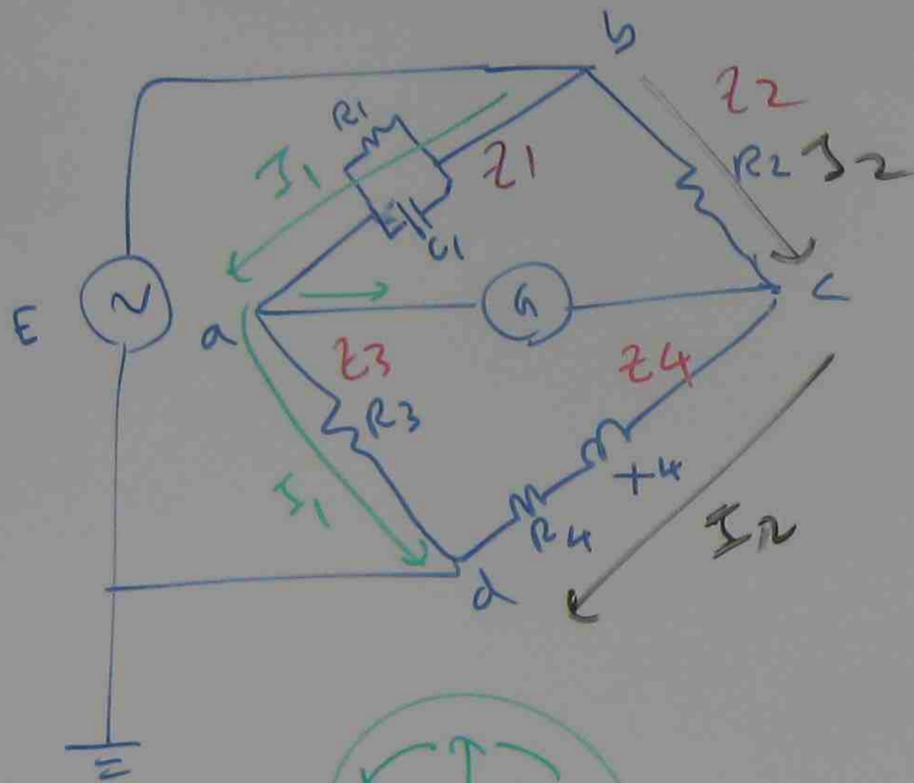

AT BALANCE

$$I_{ba} = I_{ad} = I_1$$


$$I_{bc} = I_{cd} = I_2$$

$$I_1 Z_1 = I_2 Z_2 \quad \text{--- (1)}$$

$$I_1 Z_3 = I_2 Z_4 \quad \text{--- (2)}$$

$$(1) \div (2) = \frac{I_1 Z_1}{I_1 Z_3} = \frac{I_2 Z_2}{I_2 Z_4}$$
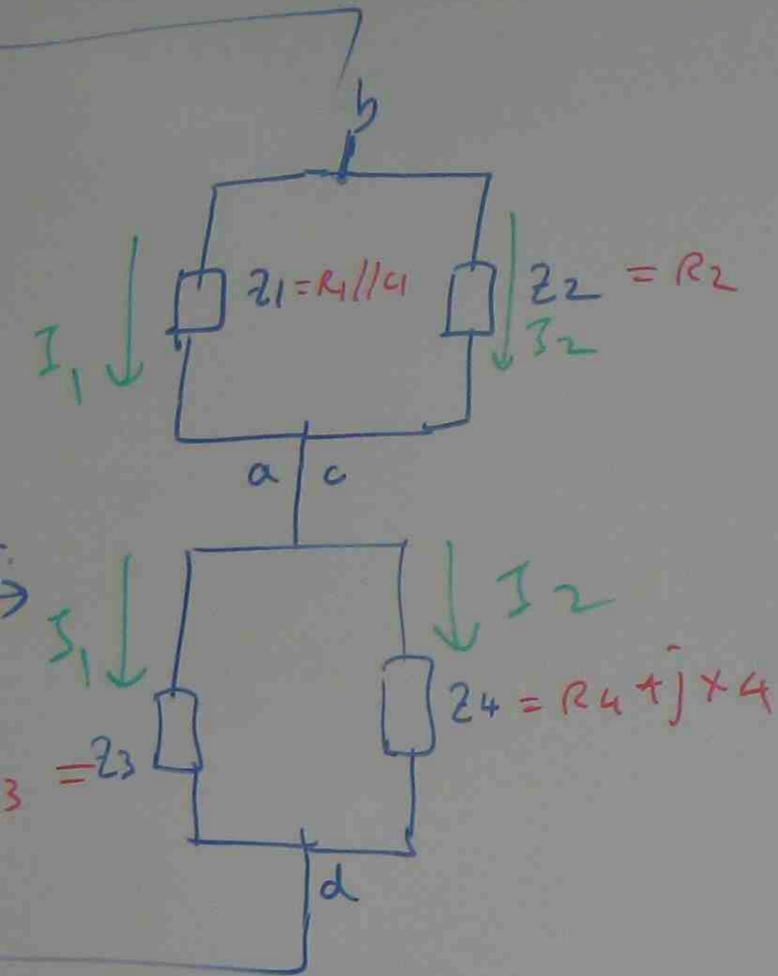
$$\frac{R_1 \times (-j \times \omega)}{R_3 + (-j \times \omega)} = \frac{R_2}{R_4 + j \times \omega}$$



$$I_1 z_1 = I_2 z_2 \quad \text{--- (1)}$$

$$I_1 z_3 = I_2 z_4 \quad \text{--- (2)}$$

$$\text{(1)} \div \text{(2)} \Rightarrow$$

$$\frac{I_1 z_1}{I_1 z_3} = \frac{I_2 z_2}{I_2 z_4}$$

$$\frac{z_1}{z_3} = \frac{z_2}{z_4}$$

$$z_1 z_4 = z_2 z_3$$

$$\frac{R_1 \times (-jX_4)}{R_1 + (-jX_4)} \times (R_4 + jX_4) = R_2 \times R_3$$

$$\frac{-jR_1 X_4 (R_4 + jX_4)}{R_1 - jX_4} = R_2 \times R_3$$

$$j = \sqrt{-1}, \quad j^2 = -1$$

$$\frac{-jR_1 X_4 R_4 + j^2 R_1 X_4^2}{R_1 - jX_4}$$

$$\frac{-jR_1 R_4 X_4 + R_1 X_4^2}{R_1 - jX_4}$$

$$\frac{R_1 X_4^2 - jR_1 R_4 X_4}{R_1 - jX_4}$$

$$\frac{(R_1 X_4^2 - jR_1 R_4 X_4)}{(R_1 - jX_4)}$$

$$\frac{R_1^2 X_4^2 - jR_1^2 X_4^2}{R_1^2 + X_4^2}$$

$$R_1^2 + X_4^2$$

$$j = \sqrt{-1}, \quad j^2 = -1$$

$$\frac{-jR_1 X_{C1} R_4 + j^2 R_1 X_{C1} X_4}{R_1 - jX_{C1}} = R_2 R_3$$

$$\frac{-jR_1 R_4 X_{C1} + R_1 X_{C1} X_4}{R_1 - jX_{C1}} = R_2 R_3$$

$$\frac{R_1 X_{C1} X_4 - jR_1 R_4 X_{C1}}{R_1 - jX_{C1}} = R_2 R_3$$

$$\frac{(R_1 X_{C1} X_4 - jR_1 R_4 X_{C1})(R_1 + jX_{C1})}{(R_1 - jX_{C1})(R_1 + jX_{C1})} = R_2 R_3$$

$$\frac{R_1^2 X_{C1} X_4 - jR_1^2 R_4 X_{C1} + jR_1 X_{C1}^2 X_4 + R_1 R_4 X_{C1}^2}{R_1^2 + X_{C1}^2} = R_2 R_3$$

$$R_1^2 + X_{C1}^2$$

$$\frac{R_1^2 X_{C1} X_4 + R_1 R_4 X_{C1}^2}{R_1^2 + X_{C1}^2} + j \frac{R_1 X_{C1}^2 X_4 - R_1^2 R_4 X_{C1}}{R_1^2 + X_{C1}^2}$$

$$\rightarrow = R_2 R_3$$

$$\frac{R_1^2 X_{C1} X_4 + R_1 R_4 X_{C1}^2}{R_1^2 + X_{C1}^2} = R_2 R_3$$

$$\frac{-R_1 X_{C1}^2 X_4 - R_1^2 R_4 X_{C1}}{R_1^2 + X_{C1}^2} = 0$$

$$j = \sqrt{-1}, \quad j^2 = -1$$

$$\frac{-jR_1 X_{C1} R_4 + j^2 R_1 X_{C1} X_4}{R_1 - jX_4} = R_2 R_3$$

$$\frac{-jR_1 R_4 X_{C1} + R_1 X_{C1} X_4}{R_1 - jX_4} = R_2 R_3$$

$$\frac{R_1 X_{C1} X_4 - jR_1 R_4 X_{C1}}{R_1 - jX_4} = R_2 R_3$$

$$\frac{(R_1 X_{C1} X_4 - jR_1 R_4 X_{C1})(R_1 + jX_4)}{(R_1 - jX_4)(R_1 + jX_4)} = R_2 R_3$$

$$\frac{R_1^2 X_{C1} X_4 - jR_1^2 R_4 X_{C1} + jR_1 X_{C1}^2 X_4 + R_1 R_4 X_{C1}}{R_1^2 + X_{C1}^2} = R_2 R_3$$

$$\frac{R_1^2 X_{C1} X_4 + R_1 R_4 X_{C1}^2}{R_1^2 + X_{C1}^2} + j \frac{R_1 X_{C1}^2 X_4 - R_1^2 R_4 X_{C1}}{R_1^2 + X_{C1}^2}$$

$$\rightarrow = R_2 R_3$$

$$\frac{R_1^2 X_{C1} X_4 + R_1 R_4 X_{C1}^2}{R_1^2 + X_{C1}^2} = R_2 R_3$$

$$\frac{R_1 X_{C1}^2 X_4 - R_1^2 R_4 X_{C1}}{R_1^2 + X_{C1}^2} = 0$$

$$R_1 X_{C1}^2 X_4 - R_1^2 R_4 X_{C1} = 0$$

$$R_1 X_{C1}^2 X_4 = R_1^2 R_4 X_{C1}$$


$$X_{C1} X_4 = R_1 R_4$$

#

$\times R_3$

$= R_2 \times R_3$

PD

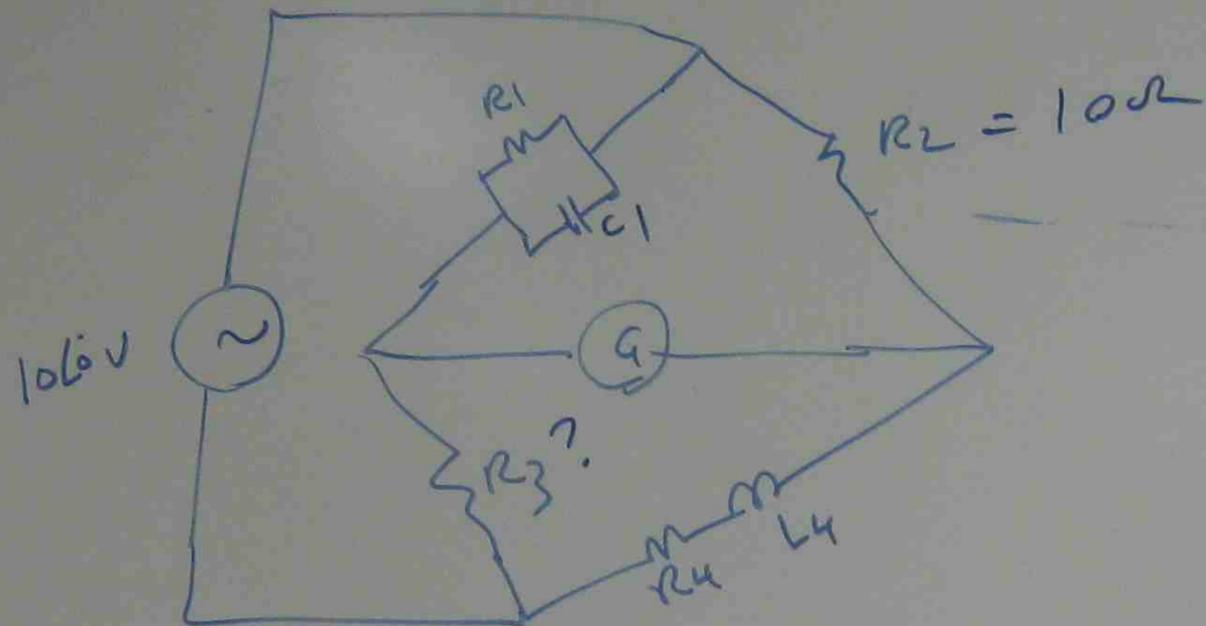

IF THE ABOVE CIRCUIT IS BALANCED

& $R_1 = 3\Omega$, $R_4 = 2\Omega$

$X_L = j5\Omega$ FIND X_{C1}

ALSO FIND R_3

BALANCED

$$X_{C1} \times X_L$$

$$X_{C1} \times j5$$

$$X_{C1} \times j5 =$$

$$X_{C1} = \frac{1}{j}$$

$$\frac{R_1^2 \times X_{C1} \times X_L}{R_1^2}$$

$$R_1^2$$

$$3^2 \times 1.2$$

$$3$$

$$(9 \times 1.2)$$

$$= 10\Omega$$

BALANCED

$$X_{C1} \times X_{C4} = R_1 \times R_4$$

$$X_{C1} \times j5 = 3 \times 2$$

$$X_{C1} \times j5 = 6$$

$$X_{C1} = \frac{6}{j5} = -j1.2\Omega$$

IS BALANCED

$$= 2\Omega$$


$$X_{C1}$$

$$\frac{R_1^2 X_{C1} X_{C4} + R_1 R_4 X_{C1}^2}{R_1^2 + X_{C1}^2} = R_2 R_3$$

$$\frac{3^2 \times 1.2 \times 5 + 3 \times 2 \times 1.2^2}{3^2 + (1.2)^2} = 10 \times R_3$$

$$\left(\frac{9 \times 1.2 \times 5 + 3 \times 2 \times 1.44}{9 + 1.44} \right) \times \frac{1}{10} = R_3$$

$$R_3 = 0.6\Omega$$

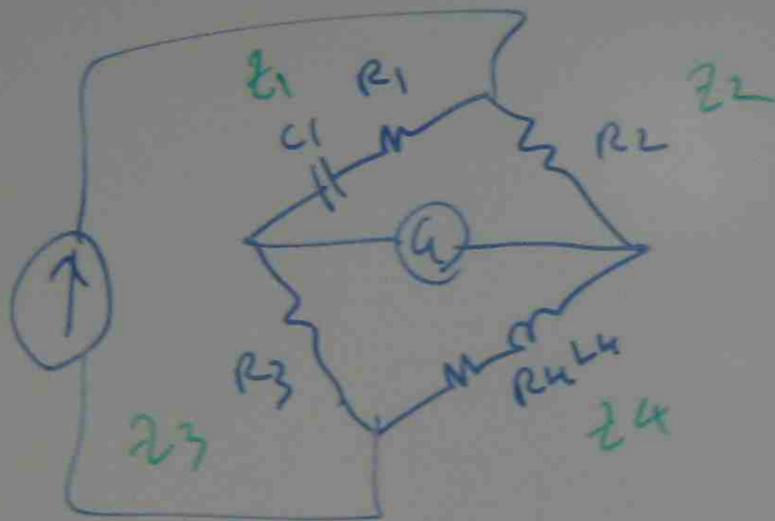

FIND THE EQUATIONS FOR ABOVE
BALANCED BRIDGE

$$Z_1 = R_1 - jX_{C1}$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_4 = R_4 + jX_{L4}$$

$$Z_1 Z_4 = Z_2 Z_3$$

$$(R_1 - jX_{C1})(R_4 + jX_{L4}) = R_2 R_3$$

$$R_1 R_4 - jX_{C1} R_4 + jR_1 X_{L4} + X_{C1} X_{L4} = R_2 R_3$$

$$R_1 R_4 + X_{C1} X_{L4} + j(R_1 X_{L4} - R_4 X_{C1}) = R_2 R_3$$

EQUATE REAL & J TERMS


$$R_1 R_4 + X_{C1} X_{L4} = R_2 R_3 \quad \text{--- (1)}$$

$$j(R_1 X_{L4} - R_4 X_{C1}) = 0$$

$$R_1 X_{L4} - R_4 X_{C1} = 0$$

$$R_1 X_{L4} = R_4 X_{C1} \quad \text{--- (2)}$$

STAR / DELTA & DELTA / STAR CONVERSION

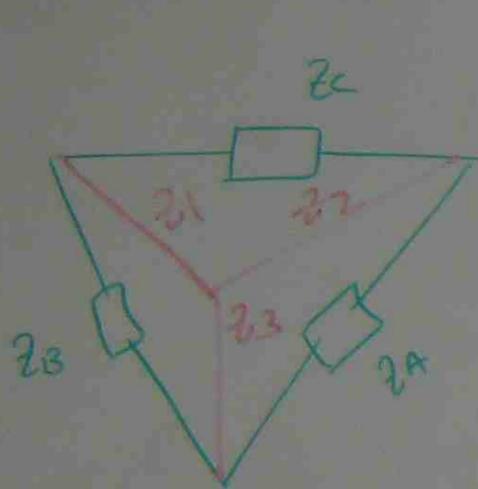

$\Delta \rightarrow \lambda$

$$z_1 = \frac{z_B z_C}{z_A + z_B + z_C}$$

$$z_2 = \frac{z_A z_C}{z_A + z_B + z_C}$$

$$z_3 = \frac{z_A z_B}{z_A + z_B + z_C}$$


$\lambda \rightarrow \Delta$

$$z_A = \frac{z_1 z_2 + z_2 z_3 + z_3 z_1}{z_1}$$

$$z_B = \frac{z_1 z_2 + z_2 z_3 + z_3 z_1}{z_2}$$

$$z_C = \frac{z_1 z_2 + z_2 z_3 + z_3 z_1}{z_3}$$

ph) CONVERT Δ TO λ FOR GIVEN CIRCUIT

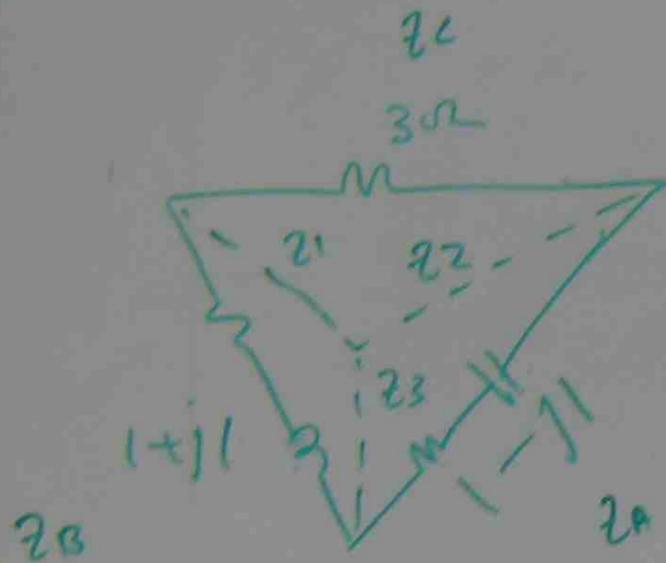

$$z_1 = \frac{z_b z_c}{z_a + z_b + z_c} = \frac{(1+j1) \times 3}{1-j1 + 1+j1 + 3} = \frac{3+j3}{5}$$

$$= 0.6 + j0.6$$

$$z_2 = \frac{z_a z_c}{z_a + z_b + z_c} = \frac{(1-j1) \times 3}{1-j1 + 1+j1 + 3} = \frac{3-j3}{5}$$

$$= 0.6 - j0.6$$

$$z_3 = \frac{z_a z_b}{z_a + z_b + z_c} = \frac{(1-j1)(1+j1)}{1-j1 + 1+j1 + 3}$$

$$= \frac{1 - j1 + j1 \times 1 - j1 \times j1}{5}$$


$$= \frac{1 - j1 + j1 - (-1)}{5}$$

$$= \frac{1+1}{5} = \frac{2}{5} = 0.4 \Omega$$

$$j = \sqrt{-1}$$

$$j \times j = \sqrt{-1} \times \sqrt{-1}$$

$$= -1$$

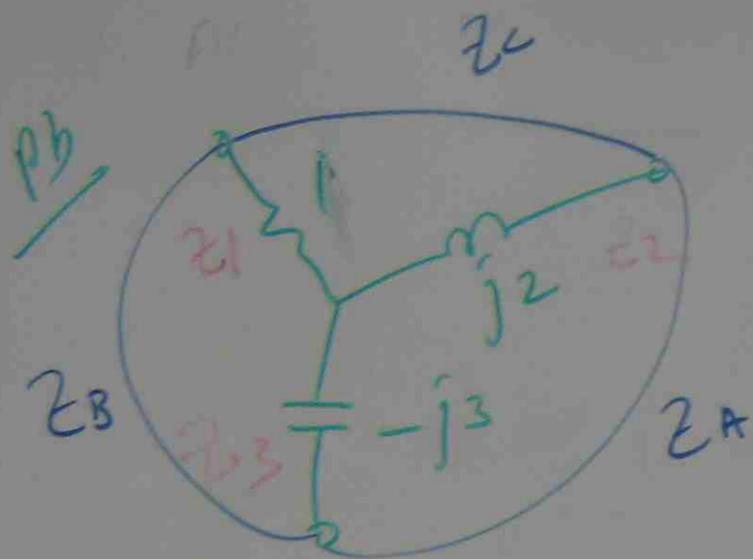

FIND Δ EQUIVALENT OF ABOVE CIRCUIT

$$\begin{aligned}
 Z_A &= \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1} \\
 &= \frac{1 \times j2 + j2 \times (-j3) + (-j3) \times 1}{1} \\
 &= \frac{j2 - (-1)6 - j3}{1} \\
 &= j2 + 6 - j3 \\
 &= 6 - j1 \quad \#
 \end{aligned}$$

$$\begin{aligned}
 Z_B &= \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2} \\
 &= \frac{1 \times j2 + j2(-j3) + (-j3) \times 1}{j2} \\
 &= \frac{6 - j1}{j2} \\
 &= \frac{6}{j2} - \frac{j1}{j2} \\
 &= \frac{6}{j2} \times \frac{j}{j} - \frac{1}{2} \\
 &= \frac{j6}{-2} - \frac{1}{2} \\
 &= -j3 - \frac{1}{2} = -\frac{1}{2} - j3 \quad \#
 \end{aligned}$$

$$Z_B = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$= \frac{1 \times j2 + j2(-j3) + (-j3) \times 1}{j2}$$

$$= \frac{6 - j1}{j2}$$

$$= \frac{6}{j2} - \frac{j1}{j2}$$

$$= \frac{6}{j2} \times \frac{j}{j} - \frac{1}{2}$$

$$= \frac{j6}{-2} - \frac{1}{2}$$

$$= -j3 - \frac{1}{2} = -\frac{1}{2} - j3 \quad \times$$

$$Z_C = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

$$= \frac{6 - j1}{-j3}$$

$$= \frac{6}{-j3} - \frac{j1}{-j3}$$

$$= -\frac{2}{j} + \frac{1}{3}$$

$$= -\frac{2}{j} \times \frac{j}{j} + \frac{1}{3}$$

$$= \frac{-j2}{-1} + \frac{1}{3}$$

$$= j2 + \frac{1}{3}$$

$$= \frac{1}{3} + j2 \quad \times$$

SYSTEM ANALYSIS

TWO PORTS NETWORKS

IMPEDANCE
PARAMETER

Z - PARAMETER

ADMITTANCE
PARAMETER


Y - PARAMETER

COMBINED IMPEDANCE & ADMITTANCE
PARAMETER

HYBRID PARAMETER


H - PARAMETER

IMPEDANCE PARAMETER (Z)

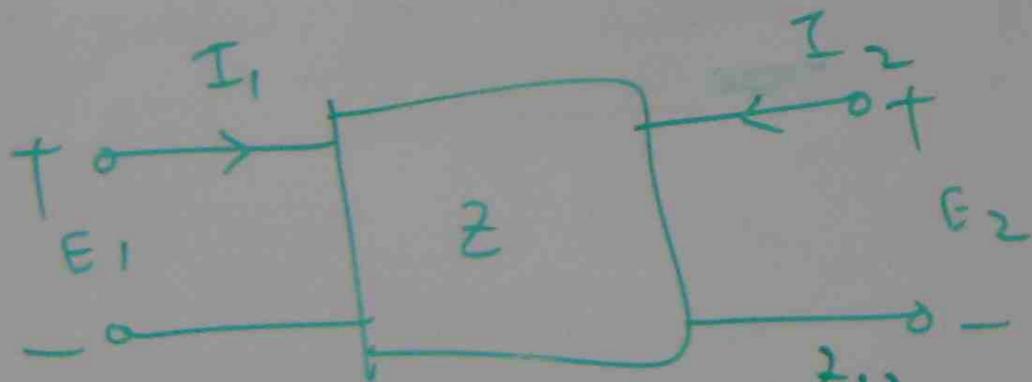


$$E_1 = Z_{11} I_1 + Z_{12} I_2$$


$$E_2 = Z_{21} I_1 + Z_{22} I_2$$

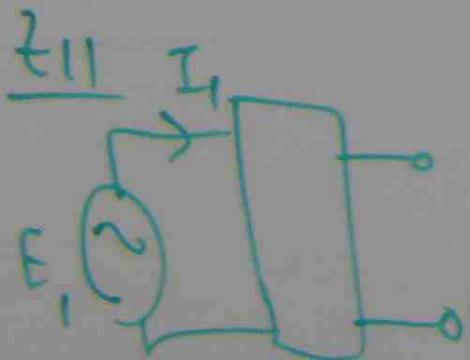

$$Z_{11} = \frac{E_1}{I_1}$$

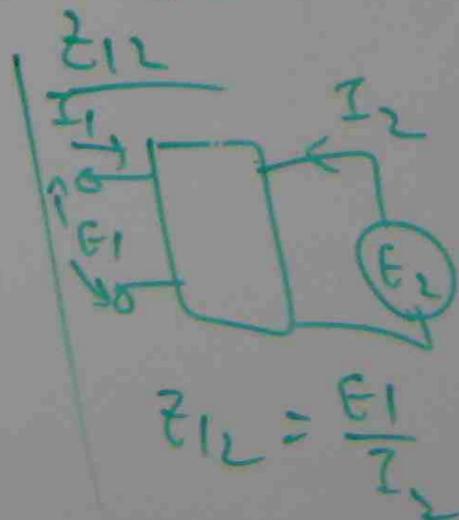

$$Z_{12} = \frac{E_1}{I_2}$$

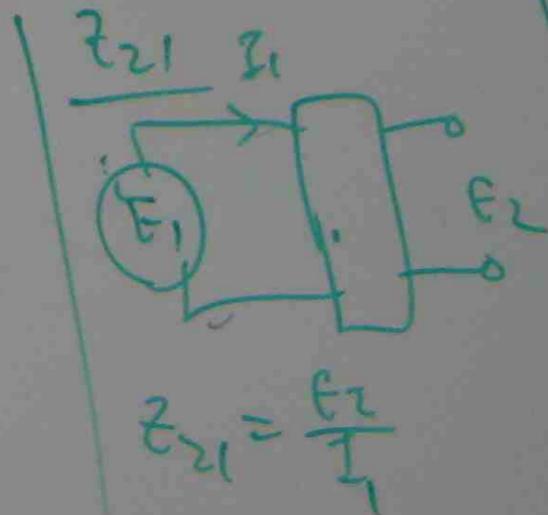

$$Z_{21} = \frac{E_2}{I_1}$$

$$Z_{22} = \frac{E_2}{I_2}$$

SYSTEM ANALYSIS

K

TWO PORTS NETWORKS

IMPEDANCE
PARAMETER

Z - PARAMETER

ADMITTANCE
PARAMETER


Y - PARAMETER

COMBINED IMPEDANCE & ADMITTANCE
PARAMETER

HYBRID PARAMETER


H - PARAMETER

IMPEDANCE PARAMETER (Z)

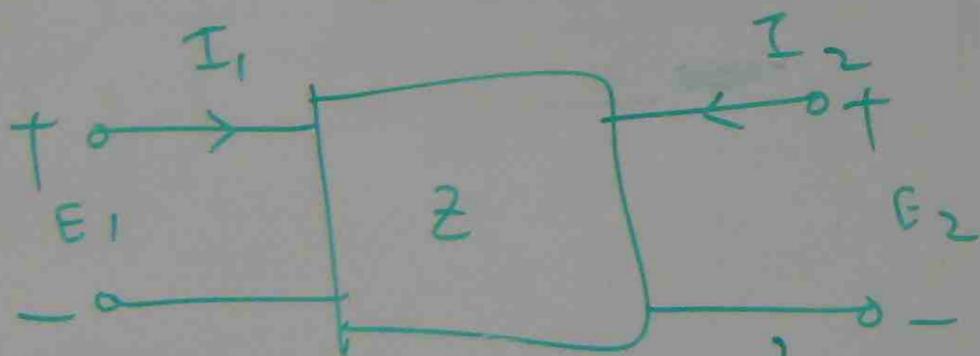


$$E_1 = Z_{11} I_1 + Z_{12} I_2$$


$$E_2 = Z_{21} I_1 + Z_{22} I_2$$

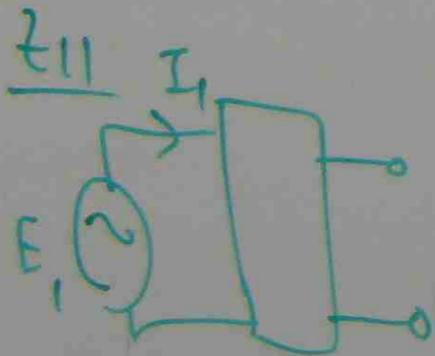

$$Z_{11} = \frac{E_1}{I_1}$$

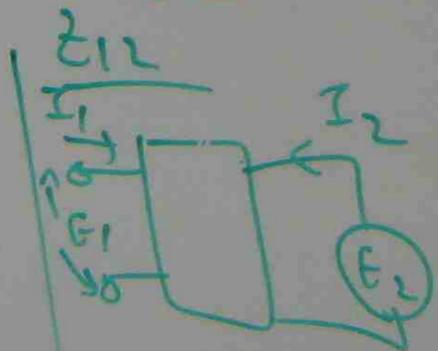

$$Z_{12} = \frac{E_1}{I_2}$$


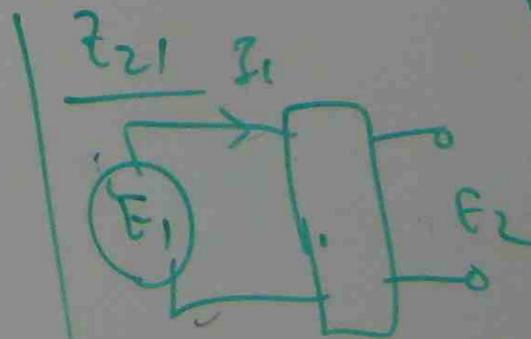


$$Z_{21} = \frac{E_2}{I_1}$$

$$Z_{22} = \frac{E_2}{I_2}$$

Ph

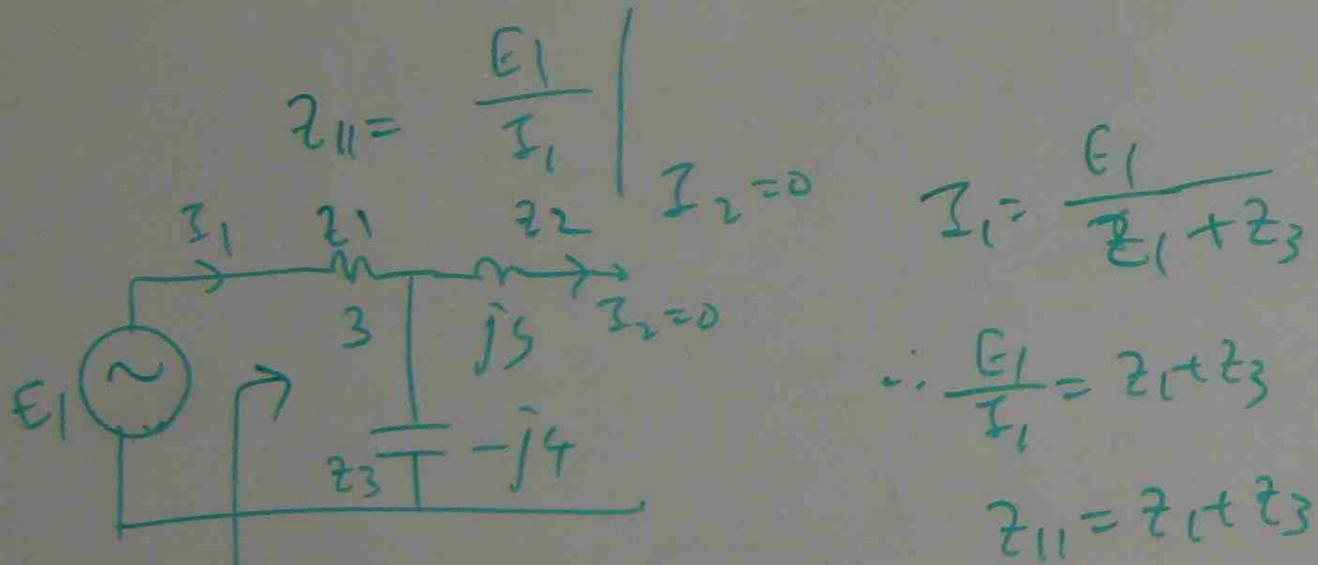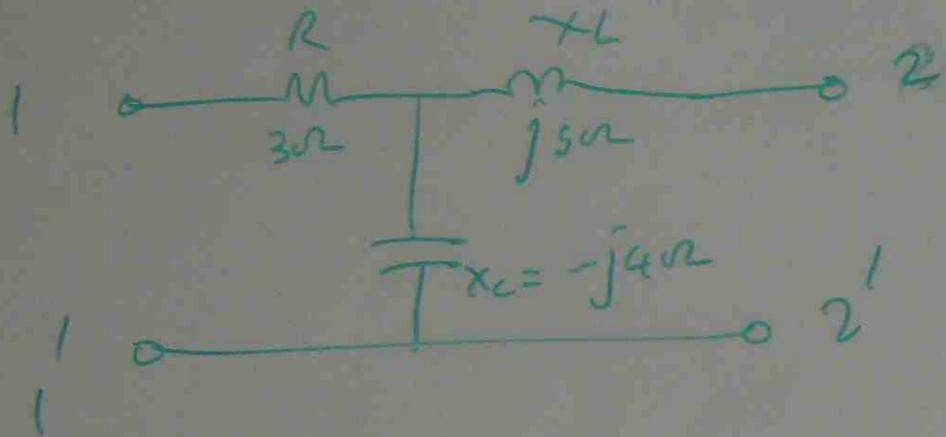DETERMINE IMPEDANCE (Z) PARAMETER FOR THE GIVEN CIRCUIT




$$Z_{11} = \frac{E_1}{I_1} \quad | \quad I_2 = 0$$

$$I_1 = \frac{E_1}{z_1 + z_3}$$

$$\therefore \frac{E_1}{I_1} = z_1 + z_3$$

$$Z_{11} = z_1 + z_3$$
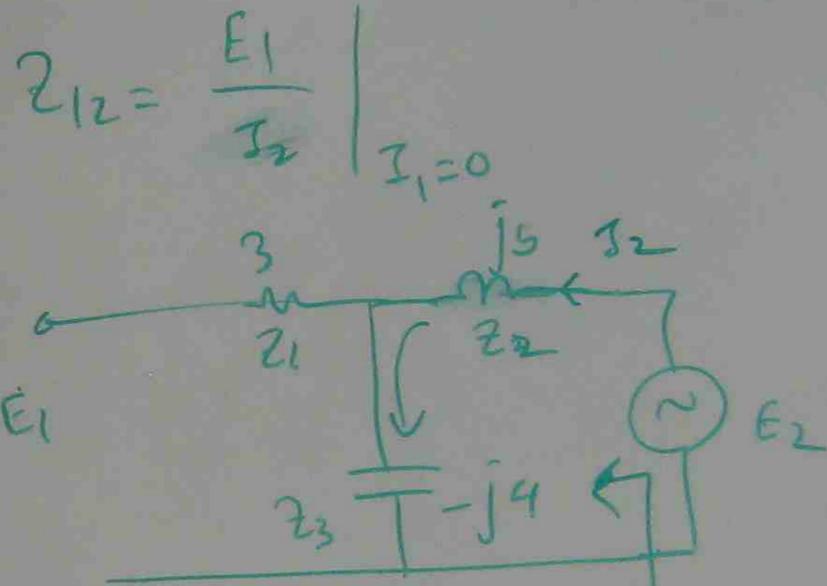
$$\begin{aligned} Z_{11} &= z_1 + z_3 \\ &= 3 + (-j4) \\ &= 3 - j4 \Omega \end{aligned}$$




$$Z_{12} = \frac{E_1}{I_2} \quad | \quad I_1 = 0$$

NO VOLTAGE DROP IN z_1

$$\therefore I_2 z_3 = E_1$$

$$Z_{12} = \frac{E_1}{I_2} = \frac{I_2 z_3}{I_2} = z_3 = -j4 \Omega$$

$$Z_{21} = \frac{E_2}{I_1} \Big|_{I_2=0}$$

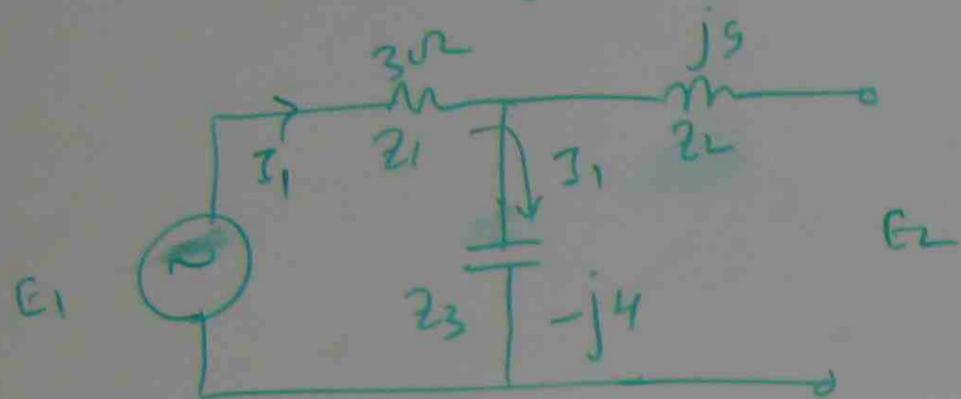


$$E_2 = I_1 z_3$$

$$Z_{21} = \frac{E_2}{I_1} = \frac{I_1 z_3}{I_1} = z_3$$

$$Z_{21} = z_3 = -j4$$

$$Z_{22} = \frac{E_2}{I_2} \Big|_{I_1=0}$$

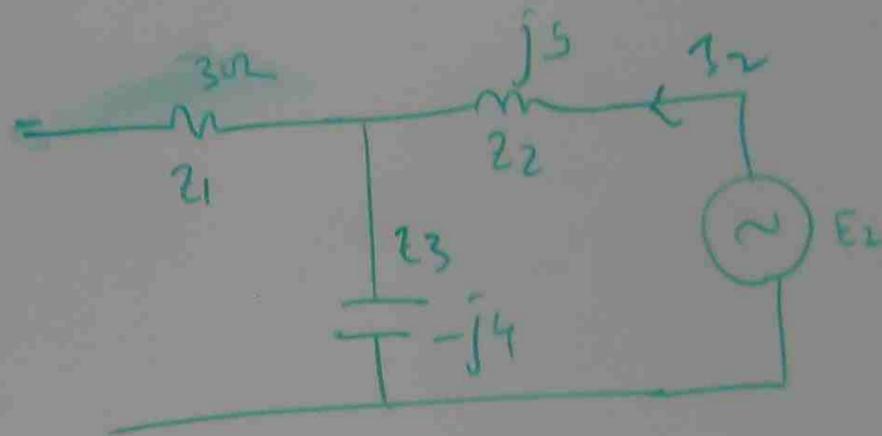


$$I_2 = \frac{E_2}{z_2 + z_3}$$

$$I_2 (z_2 + z_3) = E_2$$

$$z_2 + z_3 = \frac{E_2}{I_2} = Z_{22}$$
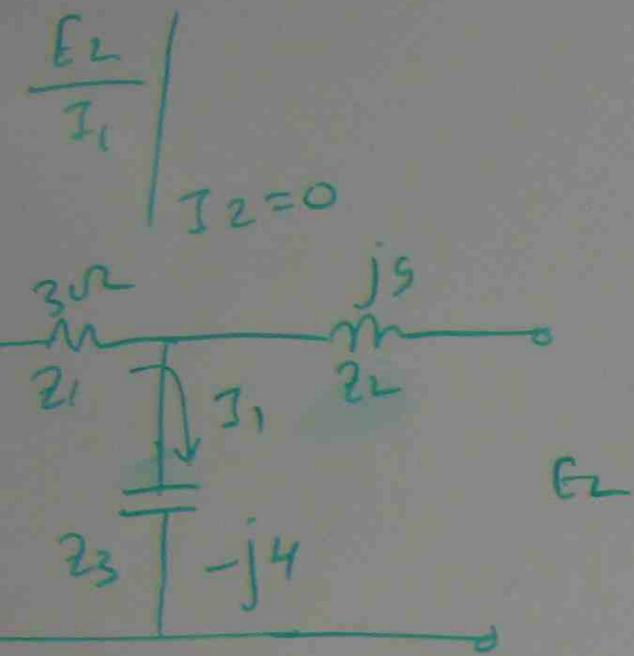
$$Z_{22} = z_2 + z_3 = j5 + (-j4) = j1 \Omega$$




z_3

$$\frac{I_1 z_3}{I_1} = z_3$$

$$z_3 = -j4$$

$$z_{22} = \frac{E_2}{I_2} \Big|_{I_1=0}$$

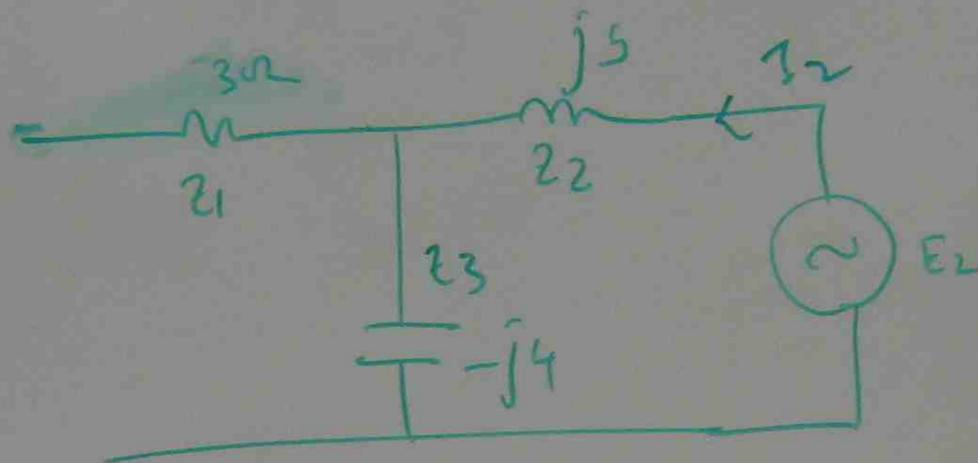

$$I_2 = \frac{E_2}{z_2 + z_3}$$

$$I_2 (z_2 + z_3) = E_2$$

$$z_2 + z_3 = \frac{E_2}{I_2} = z_{22}$$


$$z_{22} = z_2 + z_3 = j5 + (-j4) = j1 \Omega$$

$\frac{pb}{/}$


z_B

z_A

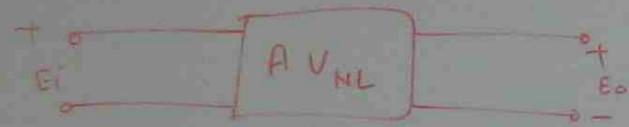NO LOAD VOLTAGE GAIN (A_{VNL}), LOADED VOLTAGE GAIN (A_V), TOTAL VOLTAGE GAIN (A_{VT})



$$A_{VNL} = \frac{E_o}{E_i}$$

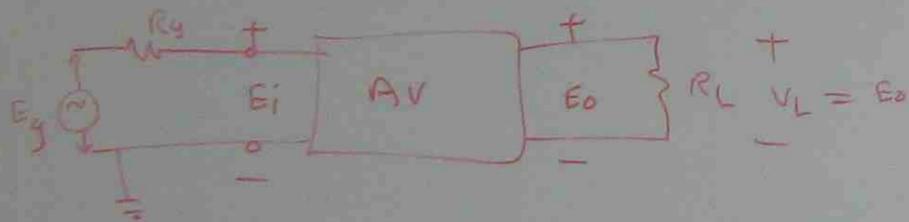

$$A_V = \frac{E_o}{E_i}$$

WITH R_L

$$A_{VT} = \frac{E_o}{E_g}$$

$$A_{VT} = A_V \times \frac{Z_i}{Z_i + R_g}$$


$$A_{VT} = A_{VNL} \times \frac{Z_i}{Z_i + R_g}$$

$$A_V = A_{VNL} \times \frac{R_L}{R_L + R_o}$$

$$R_o = R_L \left(\frac{A_{VNL}}{A_V} - 1 \right)$$

pb For THE following
AMPLIFIER

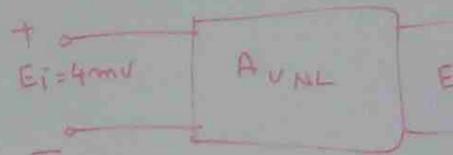- (a) DETERMINE THE
- (b) FIND THE LOADED
- (c) CALCULATE TOTAL
- (d) DETERMINE R_o



(a) (a)

$$A_{VNL} = \frac{E_o}{E_i} = \frac{-20}{4 \times 10^{-3}}$$

(b) $A_V = A_{VNL} \times \frac{R_L}{R_L + R_o}$

$$= (-5000) \times \frac{?}{?}$$

VOLTAGE GAIN (A_{VT})

$$= A_V \times \frac{Z_i}{Z_i + R_g}$$


$$= A_{VNL} \times \frac{Z_i}{Z_i + R_g}$$

$$A_{VNL} \times \frac{R_L}{R_L + R_o}$$

$$R_L \left(\frac{A_{VNL}}{A_V} - 1 \right)$$

pb For THE following system EMPLOYED IN THE LOADED AMPLIFIER

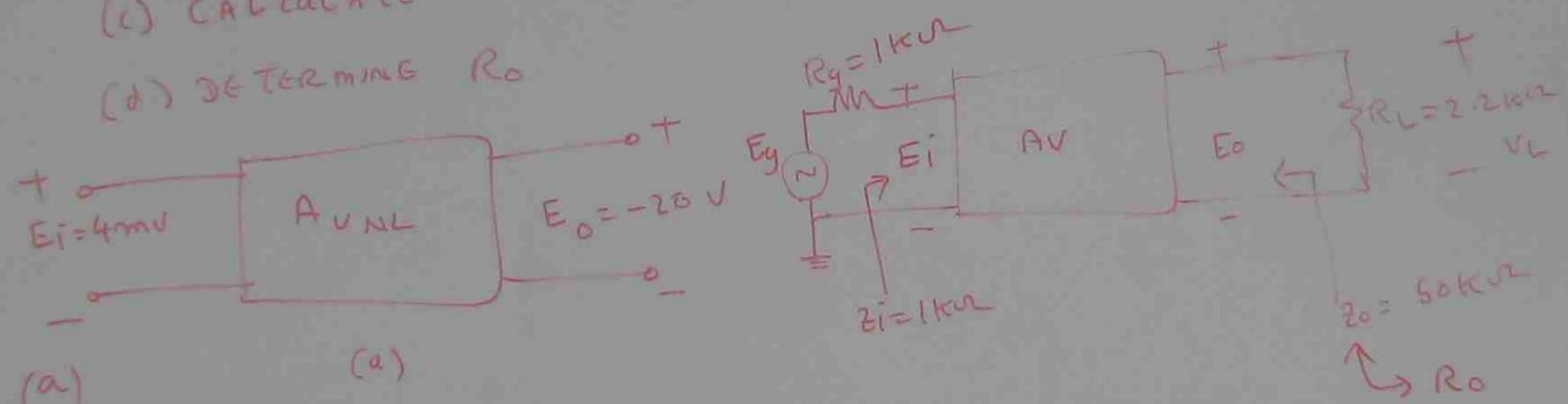- (a) DETERMINE THE NO LOAD VOLTAGE GAIN A_{VNL}
- (b) FIND THE LOADED VOLTAGE GAIN A_V
- (c) CALCULATE TOTAL LOADED VOLTAGE GAIN A_{VT}
- (d) DETERMINE R_o



(a)
$$A_{VNL} = \frac{E_o}{E_i} = \frac{-20}{4 \times 10^{-3}} = -5000$$

(b)
$$A_V = A_{VNL} \times \frac{R_L}{R_L + R_o}$$

$$= (-5000) \times \frac{2.2 \times 10^3}{2.2 \times 10^3 + 50 \times 10^3} = -210.73$$

(c)
$$A_{VT} = A_V \times \frac{Z_i}{Z_i + R_g}$$

$$= (-210.73) \times \frac{1k\Omega}{1k\Omega + 1k\Omega}$$


$$= -105.36$$

(d)
$$R_o = R_L \left(\frac{A_{VNL}}{A_V} - 1 \right)$$

$$= 2.2k \left(\frac{-5000}{-210.73} - 1 \right)$$

$$= 50k\Omega$$

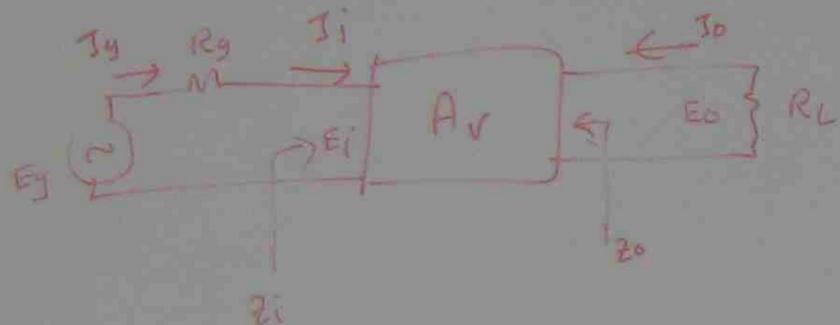CURRENT GAIN A_I , A_{IT} AND POWER GAIN A_G




$$I_o = - \frac{E_o}{R_L}$$

$$I_i = \frac{E_i}{z_i}$$

$$A_i = - A_v \times \frac{z_i}{R_L}$$

TOTAL LOADED CURRENT GAIN
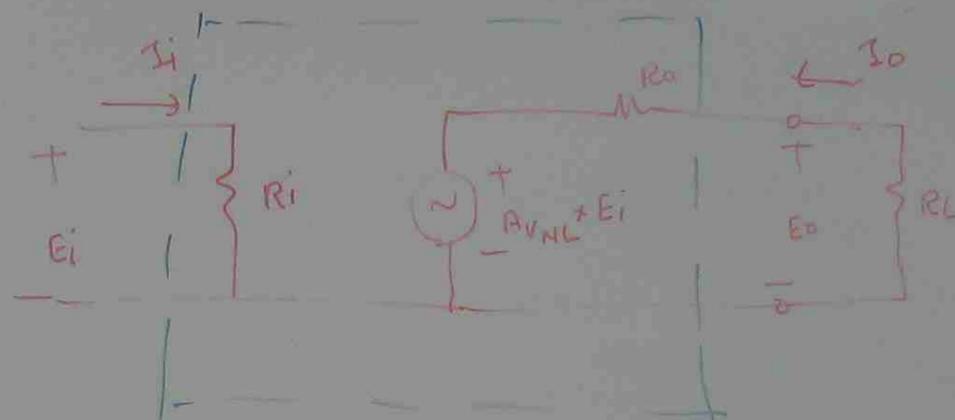
$$A_{IT} = - A_{VT} \left(\frac{R_g + z_i}{R_L} \right)$$



$$I_o = - \frac{A_{vNL} E_i}{R_L + R_o}$$

$$E_i = I_i R_i$$

$$I_o = - \frac{A_{vNL} (I_i R_i)}{R_L + R_o}$$

$$A_I = \frac{I_o}{I_i} = - A_{vNL} \times \frac{R_i}{R_L + R_o}$$

$A_G = \text{POWER GAIN}$


$$A_G = A_v^2 \times \frac{R_i}{R_L}$$

$$A_G = A_v \times (-A_i)$$

$$A_{GT} = - A_{VT} \times A_{IT}$$



CASCADED SYSTEM

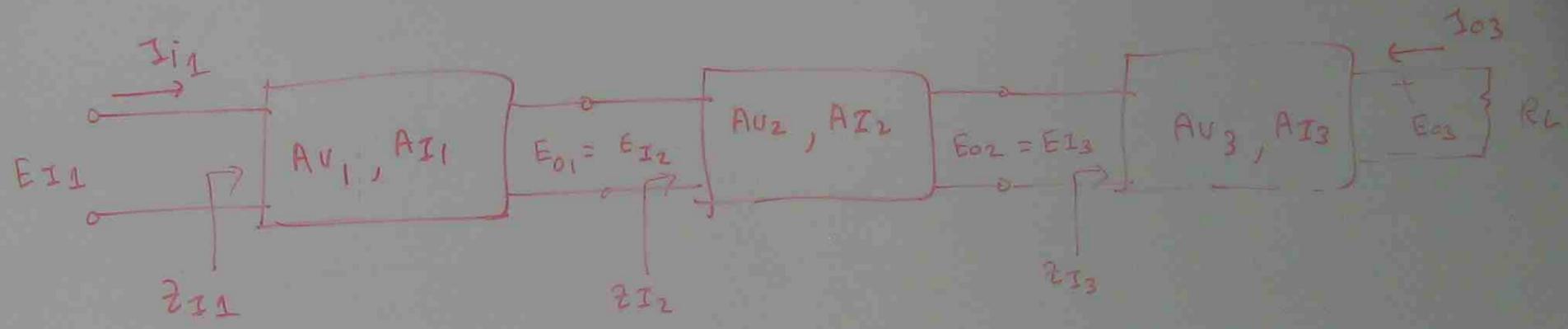

= POWER GAIN

$$G = A_v^2 \times \frac{R_i}{R_L}$$

$$G = A_v \times (-A_i)$$

$$G_{GT} = -A_{VT} \times A_{IT}$$

$$A_{VT} = A_{V1} \times A_{V2} \times A_{V3}$$

$$A_{IT} = A_{I1} \times A_{I2} \times A_{I3}$$


$$A_I = A_v \times \frac{Z_i}{R_L}$$

$$G_{GT} = A_{VT} \times A_{IT}$$

pb

FOR THE GIVEN CASCADED SYSTEM,

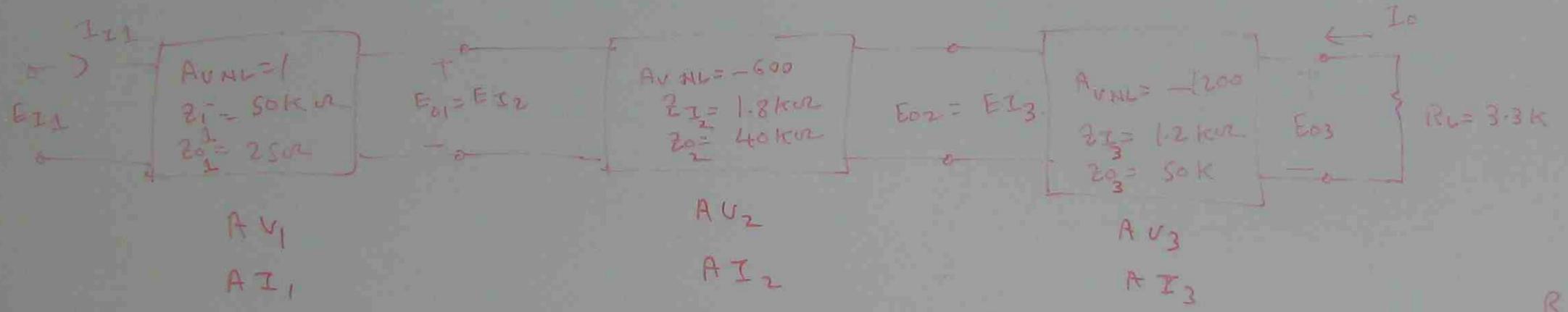- (a) DETERMINE THE LOADED VOLTAGE AND CURRENT GAIN FOR EACH STAGE
- (b) CALCULATE TOTAL VOLTAGE AND CURRENT GAIN
- (c) FIND TOTAL POWER GAIN.



(a)
$$A_{V1} = A_{VNL1} \times \frac{Z_{I2}}{Z_{I2} + Z_{O1}}$$

$$= 1 \times \frac{1.8}{1.8 + 25 \times 10^3}$$

$$= 0.986$$

$$A_{V2} = A_{VNL2} \times \frac{Z_{I3}}{Z_{I3} + Z_{O2}}$$


$$= (-600) \times \frac{1.2}{1.2 + 40}$$

$$= -17.476$$

$$A_{V3} = A_{VNL3} \times \frac{R_L}{R_L + Z_{O3}}$$

$$= (-1200) \times \frac{3.3}{3.3 + 50}$$

$$= -74.296$$

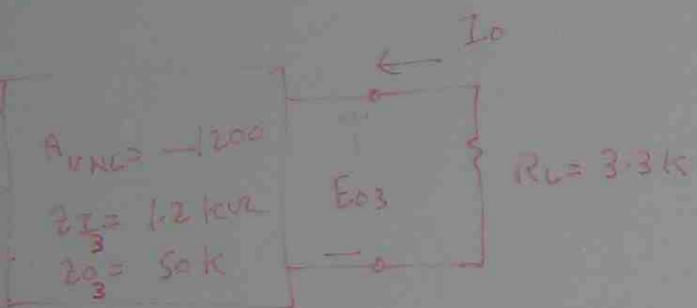

AV_3

AI_3

$$AV_3 = AV_{NL3} \times \frac{R_L}{R_L + Z_{O3}}$$

$$= (-1200) \times \frac{3.3}{3.3 + 50}$$

$$= -74.296$$

$$AI_1 = -AV_{NL1} \times \frac{Z_{I1}}{Z_{I2} + Z_{O1}} = -1 \times \frac{50k}{18k + 25 \times 10^3} = -27.397$$

$$AI_2 = -AV_{NL2} \times \frac{Z_{I2}}{Z_{I3} + Z_{O2}} = -(-600) \times \frac{1.8k}{1.2k + 40} = 26.214$$

$$AI_3 = -AV_{NL3} \times \frac{Z_{I3}}{R_L + Z_{O3}} = -(-1200) \times \frac{1.2k}{3.3k + 50k} = 27.017$$

$$(b) A_{VT} = AV_1 \times AV_2 \times AV_3 = (0.986) \times (-17.476) \times (-74.296) = 1280.22$$

$$AI_T = AI_1 \times AI_2 \times AI_3 = (-27.397) \times (26.214) \times (27.017) = -19403.20 \text{ Amp}$$

$$(c) A_{GT} = -A_{VT} \times AI_T = -1280.22 \times (-19403.2) = 24.84 \times 10^6$$