
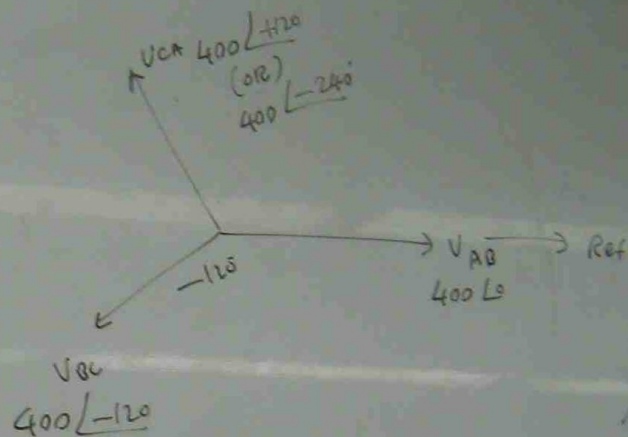
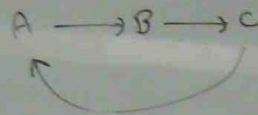


# BALANCED 3 $\phi$ DELTA

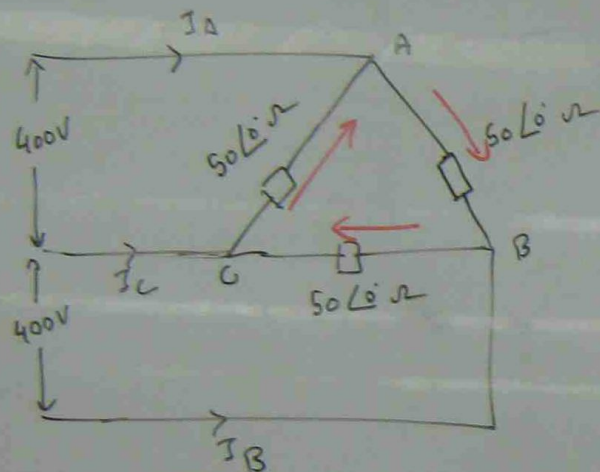

LINE VOLTAGE IS 400V

PHASE SEQUENCE IS ABC

FIND PHASE CURRENTS AND  
LINE CURRENTS.



PHASE VOLTAGE = LINE VOLTAGE

$$V_{AB} = 400V$$

$$V_{BC} = 400V$$

$$V_{CA} = 400V$$

$$I_{AB} = \frac{V_{AB}}{Z_{AB}} = \frac{400 L_0}{50 L_0} = 8 L_0 A$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}} = \frac{400 L_{-120}}{50 L_0} = 8 L_{-120} A$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}} = \frac{400 L_{120}}{50 L_0} = 8 L_{120} A$$

Flow IN CURRENTS = Flow OUT CURRENT

$$I_A + I_{CA} = I_{AB}$$

$$I_A = I_{AB} - I_{CA}$$

$$= 8 \angle 0 - 8 \angle 120$$

$$= 8(\cos 0 + j \sin 0) - 8(\cos 120 + j \sin 120)$$

$$= 8(1 + j0) - 8(-0.5 + j0.866)$$

$$= 8 - 8(-0.5 + j0.866)$$

$$= 8 + 4 - j7$$

$$= 12 - j7$$

$$I_A = \sqrt{12^2 + 7^2} \angle \tan^{-1} \frac{7}{12}$$

$$= 13.89 \angle -30.2^\circ \text{ A}$$

(B)

$$I_B + I_{AB} = I_{BC}$$

$$I_B = I_{BC} - I_{AB}$$

$$= 8 \angle -120 - 8 \angle 0$$

$$= 8(\cos(-120) + j \sin(-120)) - 8(\cos 0 + j \sin 0)$$

$$= 8(-0.5 - j0.866) - 8(1 + j0)$$

$$= -4 - j7 - 8$$

$$= -12 - j7$$


$$= \sqrt{12^2 + 7^2} \angle -(180 - \tan^{-1} \frac{7}{12})$$

$$I_B = 13.8 \angle -(180 - 30.2)$$

$$13.8 \angle -149.8^\circ \text{ A}$$

$$\tan^{-1} \frac{7}{12}$$

$$-(180 - \tan^{-1} \frac{7}{12})$$

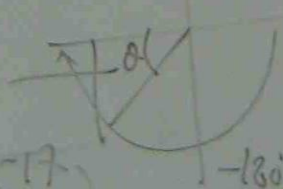

(C)

$$I_C + I_{BC} = I_{CA}$$

$$I_C = I_{CA} - I_{BC}$$

$$= 8 \angle 120 - 8 \angle -120$$

$$= 8(\cos 120 + j \sin 120) - 8(\cos(-120) + j \sin(-120))$$

$$= 8(-0.5 + j0.866) - 8(-0.5 - j0.866)$$

$$= -4 + j6.9 + 4 + j6.9$$

$$= j13.8$$

$$= j13.8$$

$$I_C = 13.8 \angle 90^\circ$$



A) Flow in arrows = Phasor current

$$I_A + I_{AC} = I_{AB}$$

$$I_{AC} = I_{AB} - I_{BA}$$

$$= 8 \angle -120^\circ - 8 \angle 120^\circ$$

$$= 8 [\cos(-120^\circ) + j \sin(-120^\circ)] - 8 (\cos 120^\circ + j \sin 120^\circ)$$


$$= 8(-0.5 - j0.866) - 8(-0.5 + j0.866)$$

$$= -4 - j6.9 - 4 + j6.9$$

$$= -8 - j0$$

$$= \sqrt{8^2 + 0^2} \angle -180^\circ$$

$$= 8 \angle -180^\circ$$

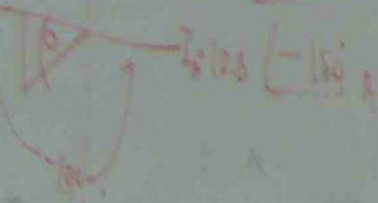

B)

$$I_B + I_{CB} = I_{BA}$$

$$I_{CB} = I_{BA} - I_{AB}$$

$$= 8 \angle 0^\circ - 8 \angle 120^\circ$$

$$= 8 (\cos 0^\circ + j \sin 0^\circ) - 8 (\cos 120^\circ + j \sin 120^\circ)$$

$$= 8(1 + j0) - 8(-0.5 + j0.866)$$

$$= 8 + 4 - j6.9$$

$$= 12 - j6.9$$

$$= \sqrt{12^2 + 6.9^2} \angle -\tan^{-1} \frac{6.9}{12}$$

$$I_B = 13.8 \angle -30.2^\circ$$

C)

$$I_C + I_{AC} = I_{CB}$$

$$I_C = I_{CB} - I_{AC}$$

$$= 8 \angle 120^\circ - 8 \angle -120^\circ$$

$$= 8 (\cos 120^\circ + j \sin 120^\circ) - 8 (\cos(-120^\circ) + j \sin(-120^\circ))$$

$$= 8(-0.5 + j0.866) - 8(-0.5 - j0.866)$$

$$= -4 + j6.9 + 4 + j6.9$$

$$= j13.8$$

$$I_C = 13.8 \angle 90^\circ \text{ Amp.}$$

