

PQ 34) 415 V STAR CONNECTED LOAD HAS THE FOLLOWING LOADS IN


A PHASE = 30Ω RESISTOR

B PHASE = 40Ω RESISTOR


C PHASE = 50Ω RESISTOR


FIND (a) LINE CURRENTS

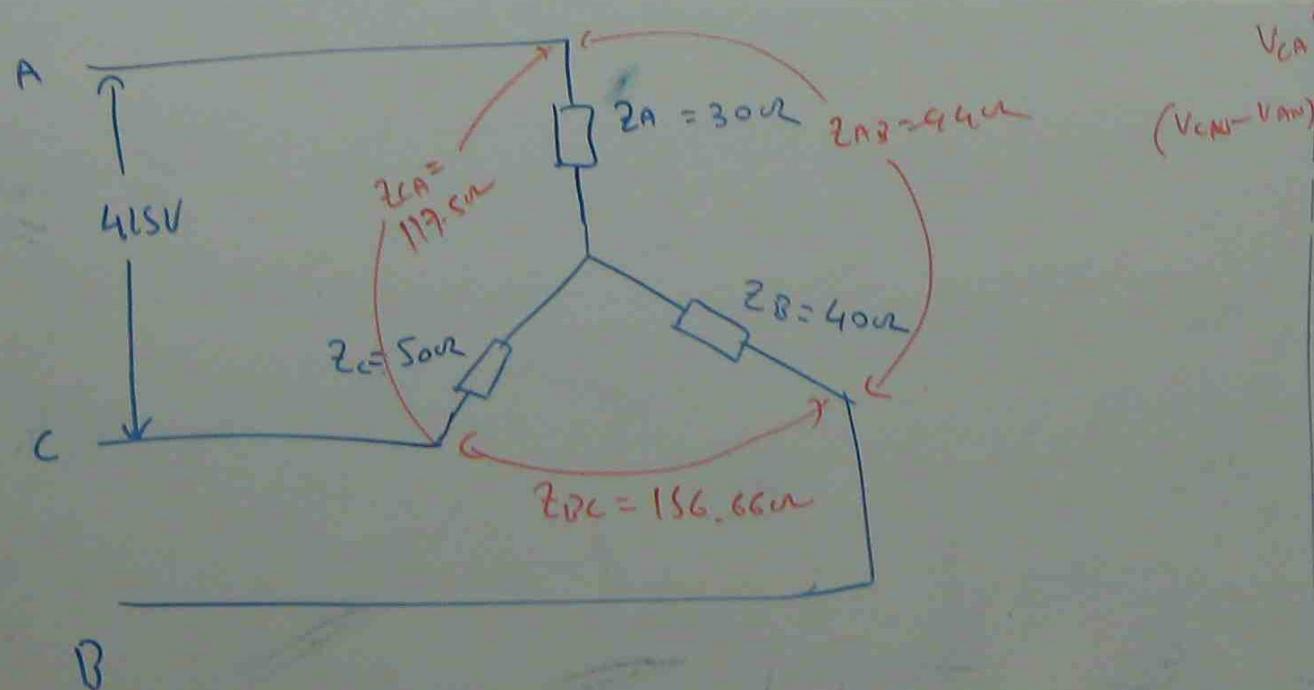(b) VOLTAGE BETWEEN NEW STAR POINT AND NEUTRAL POINT.



ING LOADS IN PHASE

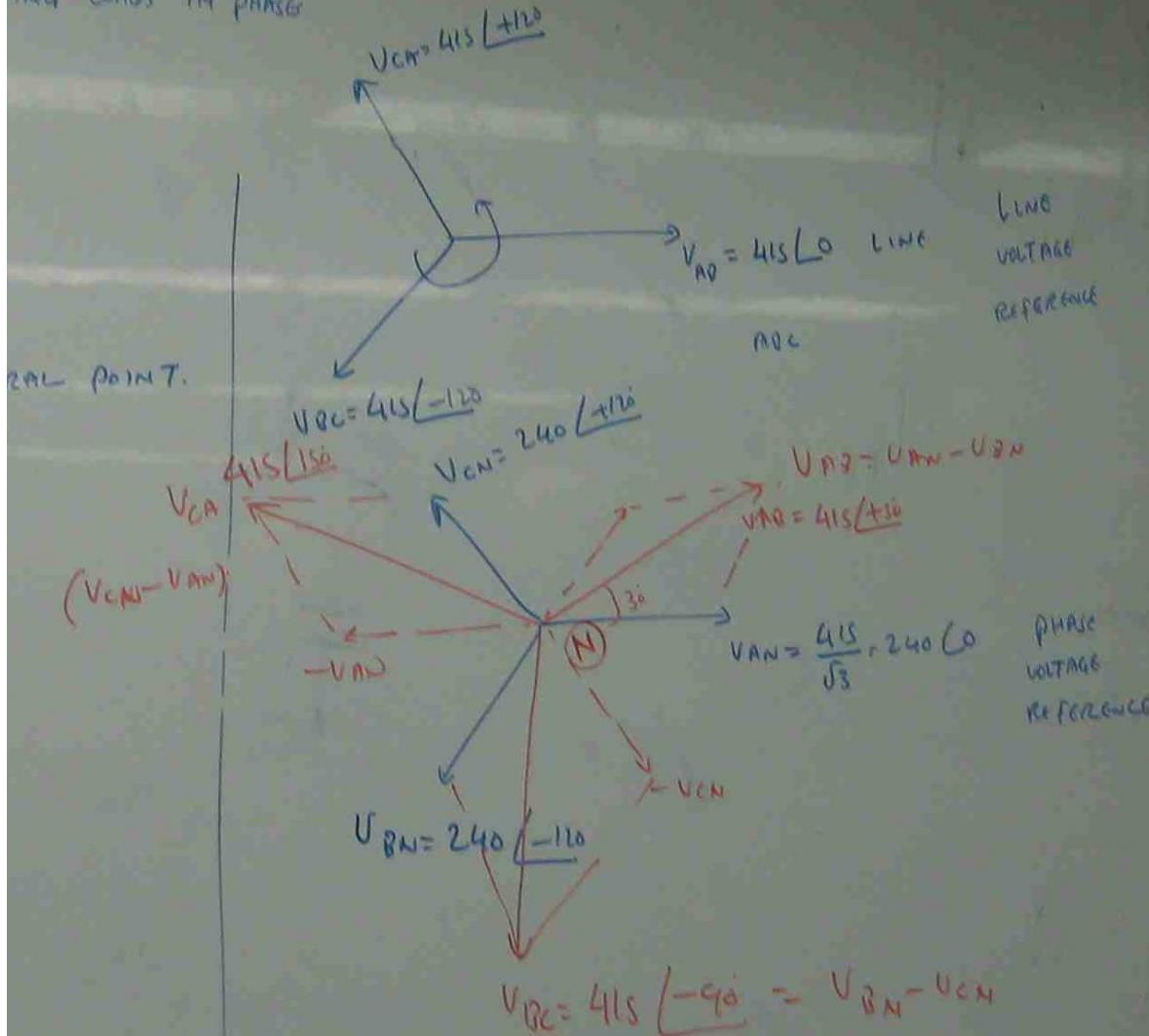

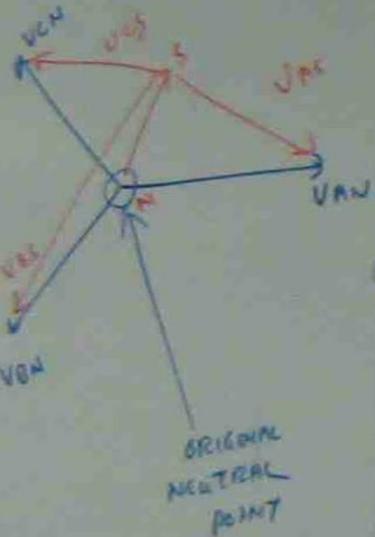

V_{NS} : VOLTAGE BETWEEN
NEW STAR POINT &
ORIGINAL
NEUTRAL POINT

(AT 3rd WIRE λ)

$$V_{NS} = V_{AN} - V_{AS}$$

$$V_{NS} = I_R \times Z_R$$

$$V_{AS} = I_B \times Z_B$$

$$V_{CS} = I_C \times Z_C$$

CONVERT TO \angle AND
FIND THE LINE CURRENTS

$$\lambda \rightarrow \Delta$$

$$Z_{AB} = \frac{2A 28 + 2B 2C + 2C 2A}{2C}$$

$$= \frac{30 \times 40 + 40 \times 50 + 50 \times 30}{50}$$


$$= \frac{4700}{50} = 94\Omega$$

$$Z_{BC} = \frac{2A 2B + 2B 2C + 2C 2A}{2A}$$

$$= \frac{4700}{30} = 156.66\Omega$$

$$Z_{CA} = \frac{2A 2B + 2B 2C + 2C 2A}{2B}$$

$$= \frac{4700}{40} = 117.5\Omega$$

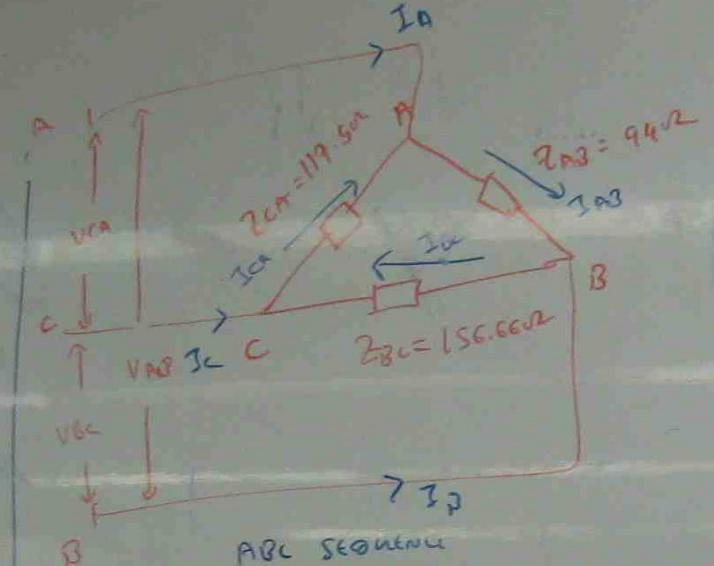

$$I_{AB} = \frac{V_{AB}}{Z_{AB}} = \frac{415 \angle 30}{94} = 4.414 \angle 30 \text{ A}$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}} = \frac{415 \angle -90}{156.66} = 2.65 \angle -90 \text{ A}$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}} = \frac{415 \angle 150}{117.5} = 3.53 \angle 150 \text{ A}$$

(A) point flow in = flow out

$$I_A + I_{CA} = I_{AB}$$

$$I_A = I_{AB} - I_{CA} = 4.414 \angle 30 - 3.53 \angle 150$$

$$= 4.414(\cos 30 + j \sin 30) - 3.53(\cos 150 + j \sin 150)$$

$$= 3.82 + j 2.207 - 3.53(-0.866 + j 0.5)$$

$$\begin{aligned} I_A &= 3.82 + j 2.207 + 3.05 - j 1.765 \\ &= 6.87 + j 0.442 \\ &= \sqrt{6.87^2 + 0.442^2} \angle \tan^{-1} \frac{0.442}{6.87} \\ &= 6.88 \angle 3.66^\circ \text{ A} \end{aligned}$$

$$U_{NS} = U_{PN} - U_{PS}$$

$$= 240 \angle 0 - I_A Z_A$$

$$= 240 \angle 0 - 6.88 \angle 3.66 \times 30$$

$$= 240 \angle 0 - 206.4 \angle 3.66$$

$$= 240 - 206.4(\cos 3.66 + j \sin 3.66)$$

$$= 240 - 206.4(0.947 + j 0.063)$$

$$= 240 - (205.7 + j 13)$$

$$= 240 - 205.7 - j 13$$

$$= 34.3 - j 13$$

$$\begin{aligned} U_{NS} &= \sqrt{34.3^2 + 13^2} \angle -\tan^{-1} \frac{13}{34.3} \\ &= 36.68 \angle -20.75^\circ \text{ V} \end{aligned}$$

AT ③

$$\text{Flow in} = \text{Flow out}$$

$$I_B + I_{AB} = I_{BC}$$

$$I_B = I_{BC} - I_{AB}$$

$$= 2.65 \angle -90^\circ - 4.414 \angle 30^\circ$$

$$= 2.65(\cos 90^\circ - j \sin 90^\circ) - 4.414(\cos 30^\circ + j \sin 30^\circ)$$

$$= 2.65(0 - j 1) - (3.82 + j 2.207)$$

$$= 0 - j 2.65 - 3.82 - j 2.207$$

$$I_B = -3.82 - j 4.857$$

$$I_B = \sqrt{3.82^2 + 4.857^2} \angle \left(-\left(180 - \tan^{-1} \frac{4.857}{3.82}\right) \right)$$


$$= 6.179 \angle \left(-\left(180 - 51.98\right) \right)$$

$$= 6.179 \angle \left(-128.22^\circ \right)$$

AT (c) Flow IN = Flow OUT

$$I_C + I_{BC} = I_{CA}$$

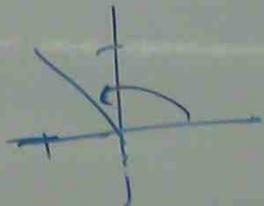
$$\begin{aligned} I_C &= I_{CA} - I_{BC} = 3.53 \angle 150^\circ - 2.65 \angle -90^\circ \\ &= 3.53 (\cos 150^\circ + j \sin 150^\circ) - (0 - j 2.65) \\ &= 3.53 (-0.866 + j 0.5) + j 2.65 \\ &= -3.05 + j 1.765 + j 2.65 \\ &= -3.05 + j 4.415 \end{aligned}$$



$$I_C = \sqrt{3.05^2 + 4.415^2} \angle \left(180 - \tan^{-1} \frac{4.415}{3.05} \right)$$

$$= 5.36 \angle -124.78^\circ$$
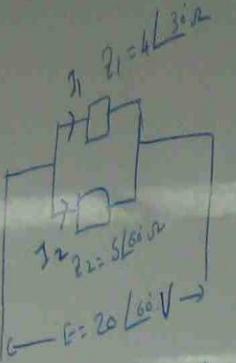
$$= 5.36 \angle -124.78^\circ \text{ A}$$




FIND TOTAL power TAKEN BY THE CIRCUIT.

$$I_1 = \frac{E}{Z_1} = \frac{20 L 60}{4 L 30} = 5 L 60 - 30 = 5 L 30 \text{ A}$$

$$I_2 = \frac{E}{Z_2} = \frac{20 L 60}{5 L 60} = 4 L 0 \text{ A}$$

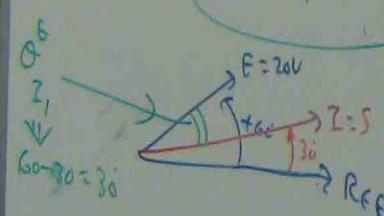POWER IN Z_1 = $E \times I_1 \cos \theta_{I_1}$



$$\begin{aligned} P_{Z_1} &= 20 \times 5 \times \cos 30 \\ &= 100 \times 0.866 \\ &\approx 86.6 \text{ W} \end{aligned}$$

POWER IN Z_2 = $E I_2 \cos \theta_{I_2}$


$$Z_2 = \frac{E}{I_2} = \frac{20 L 60}{4 L 0} = 5 L 60 \text{ ohms}$$

$$\begin{aligned} P_{Z_2} &= 20 \times 4 \times \cos 60 \\ &= 80 \times 0.5 \\ &= 40 \text{ W} \end{aligned}$$

TOTAL power = $P_{Z_1} + P_{Z_2} = 86.6 + 40 = 126.6 \text{ W}$

3φ POWER IN UNBALANCED LOAD

2 WATT METER METHOD

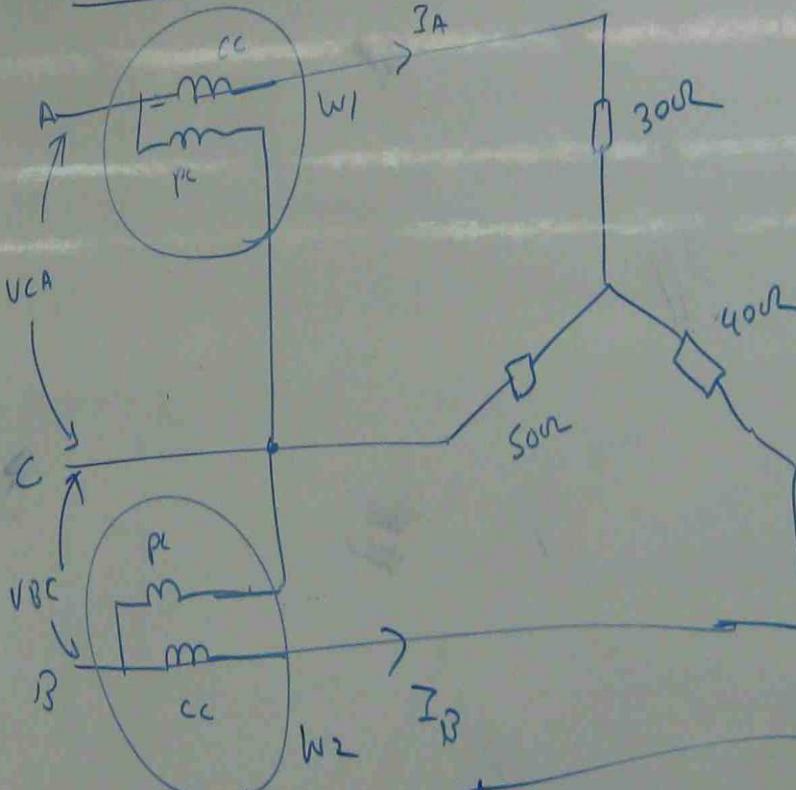

$$W_1 = I_A \times V_{CA} \cos \theta_{I_A}$$

$$W_2 = I_B \times V_{BC} \cos \theta_{I_B}$$

$$W_T = W_1 + W_2$$