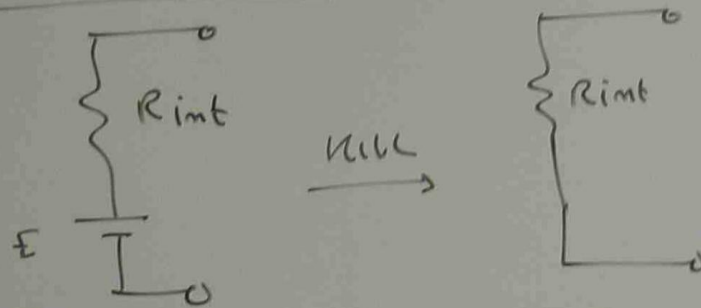



## SUPER POSITION THEOREM


ALTERNATIVELY KILL THE THE SOURCE. FIND THE CURRENT FLOWS IN BRANCHES AND ALGEBRICALLY ADD THE CURRENTS.

### VOLTAGE SOURCE




### CURRENT SOURCE

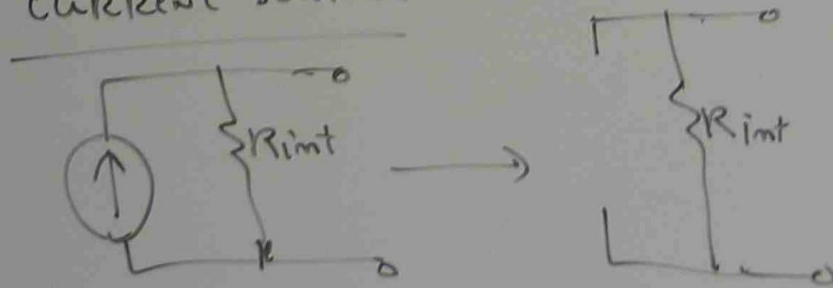

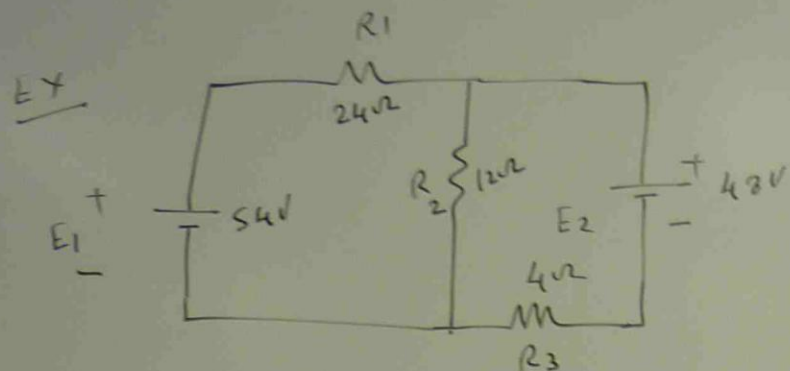

USE SUPERPOSITION THEOREM AND DETERMINE THE CURRENT THROUGH THE 4Ω RESISTOR.

KILL 48V

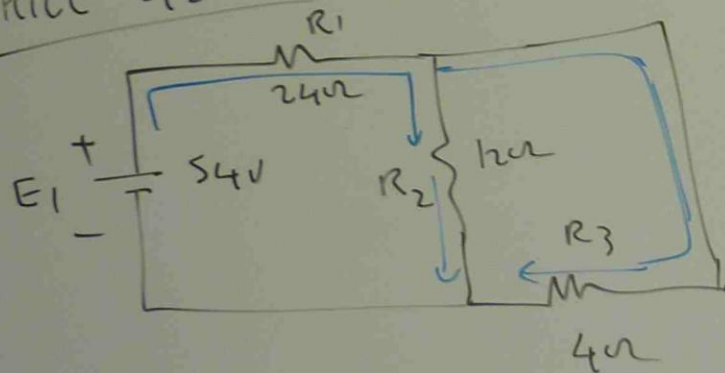

$$R_T = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 24 + \frac{12 \times 4}{12 + 4}$$

$$= 24 + \frac{48}{16} = 27\Omega$$

$$I_T = \frac{E_1}{R_T} = \frac{54}{27} = 2 \text{ Amps}$$


$$I_{R_3} (4\Omega) = I_T \times \frac{R_2}{R_2 + R_3}$$

$$= 2 \times \frac{12}{12 + 4}$$

$$= 2 \times \frac{12}{16}$$

$$I_{R_3} = 1.5 \text{ A}$$

KILL 54V

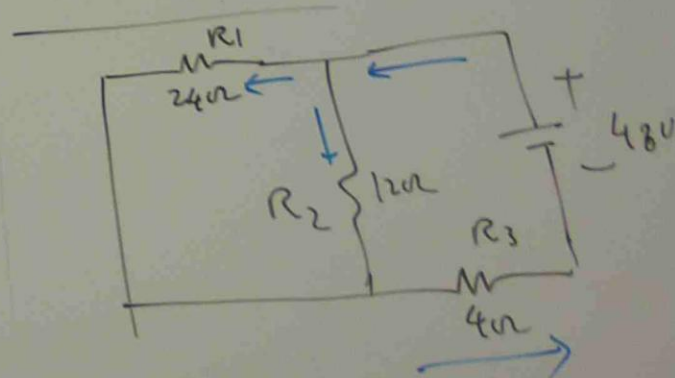


$$\begin{aligned}
 R_T &= R_3 + \frac{R_1 R_2}{R_1 + R_2} \\
 &= 4 + \frac{24 \times 12}{24 + 12} \\
 &= 4 + \frac{24 \times 12}{36} \\
 &= 4 + 8 = 12 \Omega
 \end{aligned}$$


$$I_{R_3} = \frac{E_2}{R_T} = \frac{48}{12} = 4A$$

$$\begin{aligned}
 I_{R_3} &= I_{R_3}^I - I_{R_3}^{II} \\
 &= 4 - 1.5 = 2.5A
 \end{aligned}$$

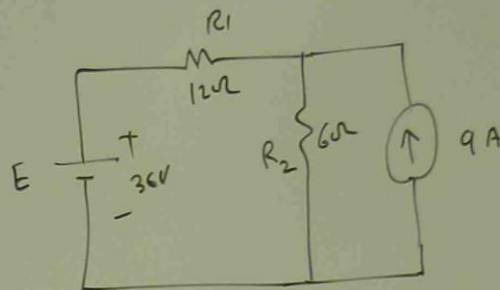Ex USING SUPERPOSITION, FIND THE CURRENT THROUGH  $6\Omega$  RESISTOR OF THE GIVEN NETWORK.



KILL 36V SOURCE

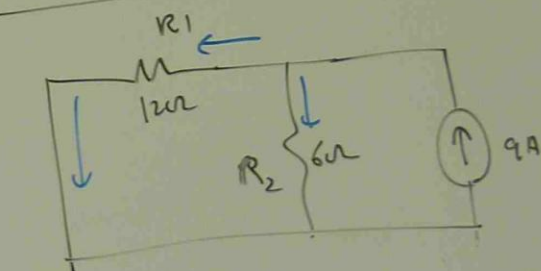


$$I_{R_2}^I = I_T \times \frac{R_1}{R_1 + R_2}$$

$$= 9 \times \frac{12}{12 + 6}$$

$$= 9 \times \frac{12}{18} = 6A$$

KILL 9A SOURCE

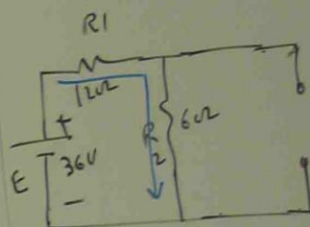

$$I_{R_2}^{II} = \frac{E}{R_1 + R_2}$$


$$= \frac{36}{12 + 6}$$

$$= \frac{36}{18} = 2A$$


$$I_{R_2} = I_{R_2}^I + I_{R_2}^{II}$$

$$= 6 + 2 = 8A$$


# THEVENIN'S THEOREM

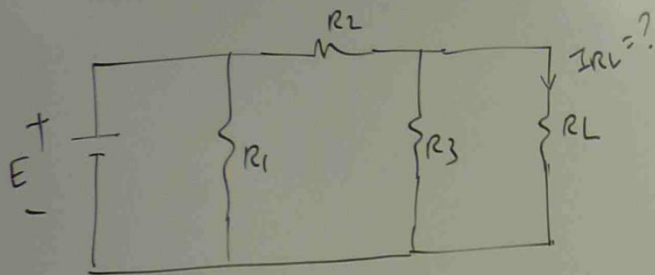

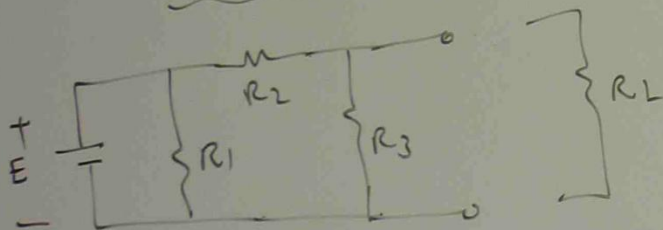STEP (1) REMOVE THE BRANCH IN WHICH THE CURRENT NEEDS TO BE CALCULATED



STEP (2) KILL THE SOURCES

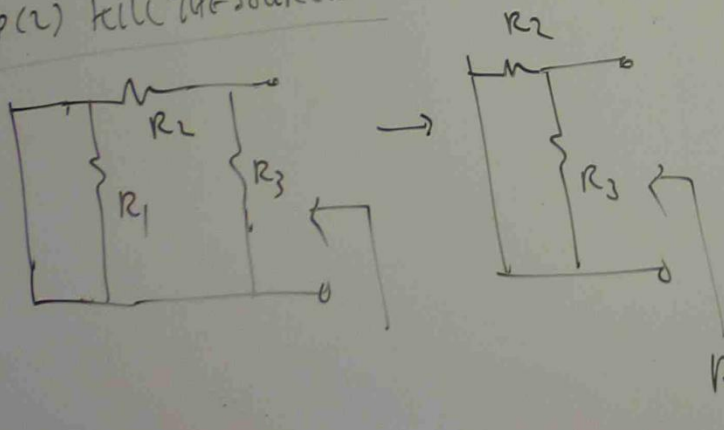


STEP (3) DETERMINE THE RESISTANCE ACROSS TERMINAL

$$R_{th} = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3}$$

STEP (4)

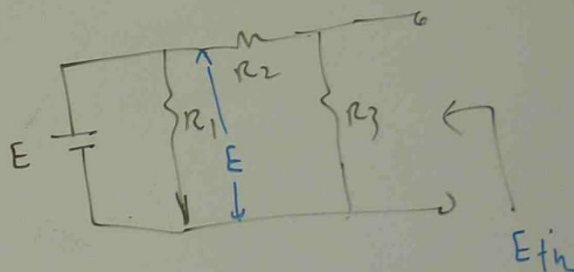RECONNECT THE SOURCES, FIND THE VOLTAGE ACROSS TERMINAL




$$E_{th} = E \times \frac{R_3}{R_2 + R_3}$$

STEP (5)


$$I_{RL} = \frac{E_{th}}{R_{th} + R_L} = \frac{\frac{E R_3}{R_2 + R_3}}{\frac{R_2 R_3}{R_2 + R_3} + R_L}$$



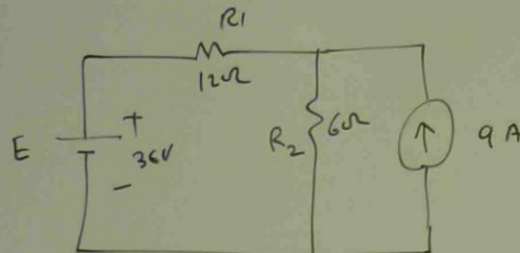Ex USING SUPERPOSITION, FIND THE CURRENT THROUGH  $6\Omega$  RESISTOR OF THE GIVEN NETWORK.



KILL 36V SOURCE

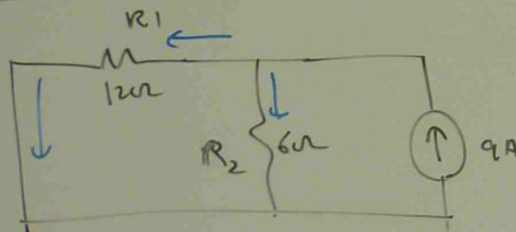


$$I_{R2} = I_T \times \frac{R_1}{R_1 + R_2}$$

$$= 9 \times \frac{12}{12+6}$$

$$= 9 \times \frac{12}{18} = 6A \downarrow$$

KILL 9A SOURCE

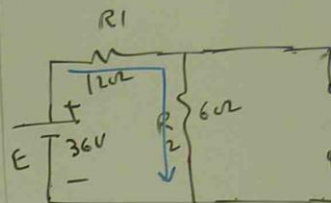

$$I_{R2}'' = \frac{E}{R_1 + R_2}$$


$$= \frac{36}{12+6}$$

$$= \frac{36}{18} = 2A \downarrow$$


$$I_{R2} = I_{R2}' + I_{R2}''$$

$$= 6 + 2 = 8A \downarrow$$


# THEVENIN'S THEOREM

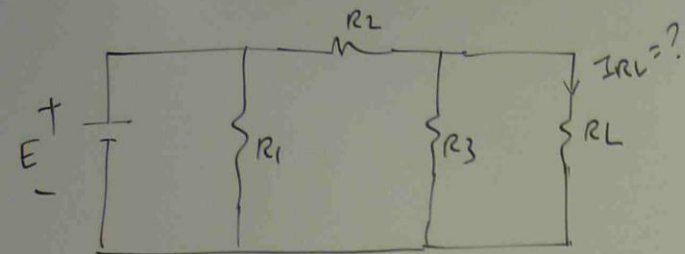

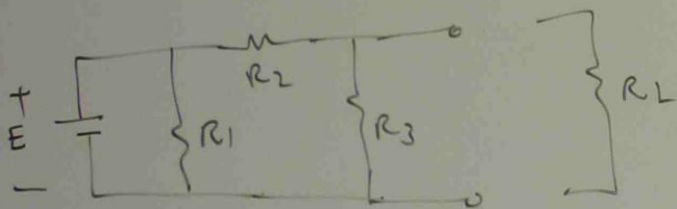STEP (1) REMOVE THE BRANCH IN WHICH THE CURRENT NEEDS TO BE CALCULATED



STEP (2) KILL THE SOURCES

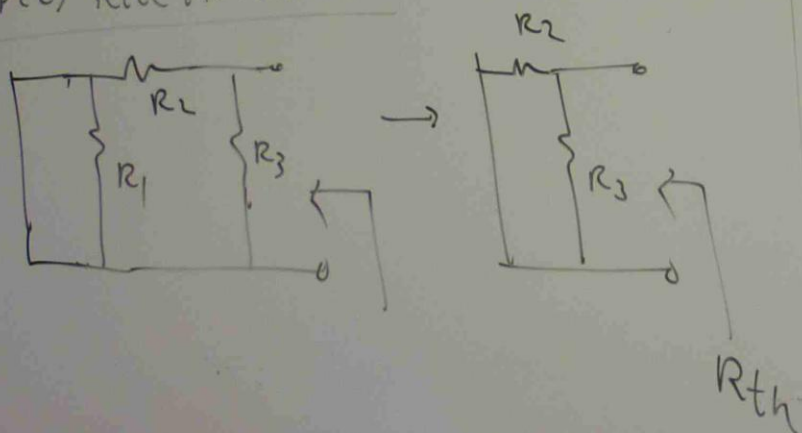


STEP (3) DETERMINE THE RESISTANCE ACROSS TERMINAL

$$R_{th} = R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3}$$

STEP (4)

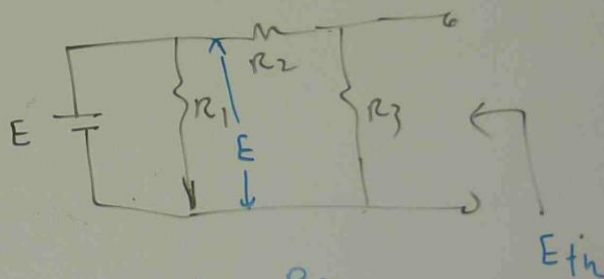RECONNECT THE SOURCES, FIND THE VOLTAGE ACROSS TERMINAL




$$E_{th} = E \times \frac{R_3}{R_2 + R_3}$$



STEP (5)

$$I_{RL} = \frac{E_{th}}{R_{th} + R_L} = \frac{\frac{E R_3}{R_2 + R_3}}{\frac{R_2 R_3}{R_2 + R_3} + R_L}$$

EX

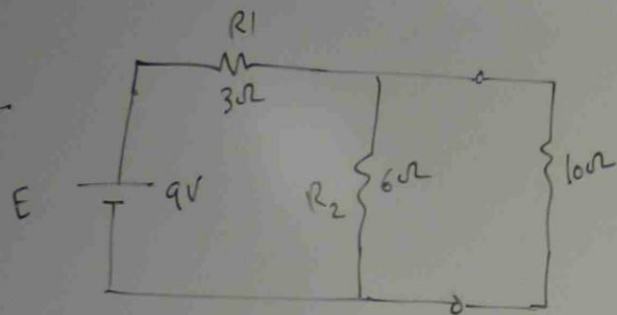


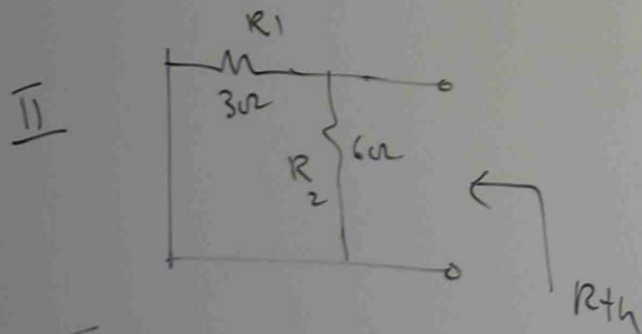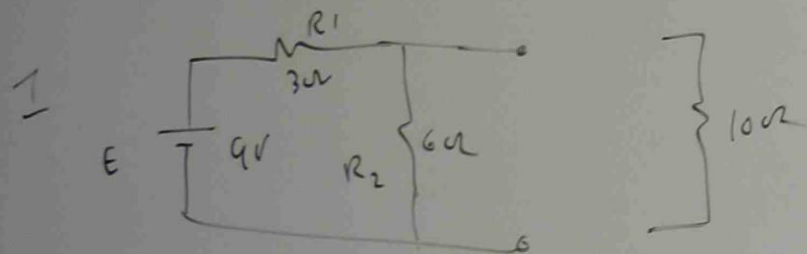FIND THE CURRENT THROUGH  $10\Omega$  RESISTOR  
BY USING THEVENIN'S THEOREM.



III

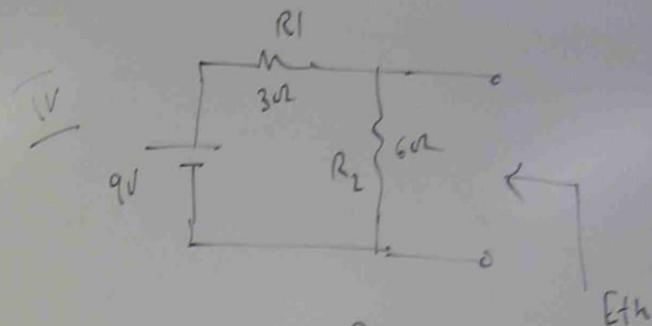
$$R_{th} = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2\Omega$$



$$\begin{aligned} E_{th} &= 9V \times \frac{R_2}{R_1 + R_2} \\ &= 9 \times \frac{6}{3 + 6} \\ &= 9 \times \frac{6}{9} = 6V \end{aligned}$$




V
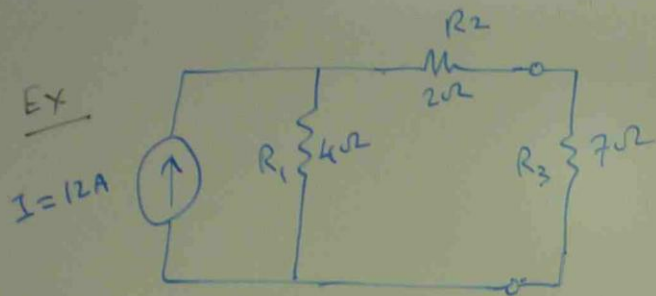
$$\begin{aligned} I_{10\Omega} &= \frac{E_{th}}{10\Omega + R_{th}} \\ &= \frac{6}{10 + 2} \\ &= \frac{6}{12} = 0.5A \end{aligned}$$




FIND THEVENIN'S EQUIVALENT CIRCUIT ACROSS  $R_3$

THEVENIN'S EQUIVALENT

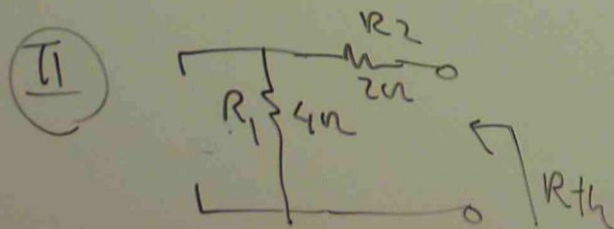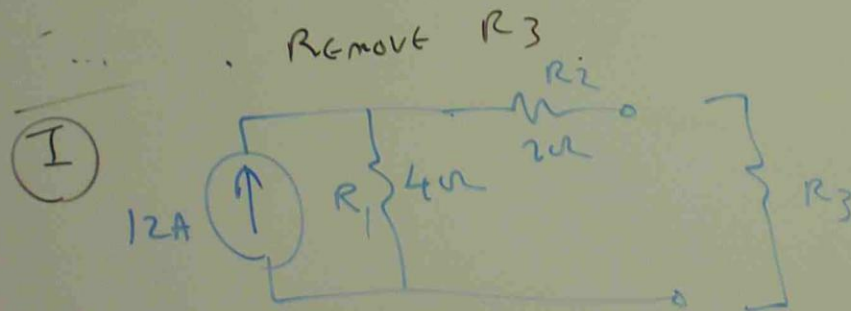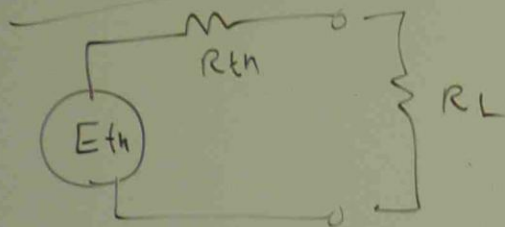


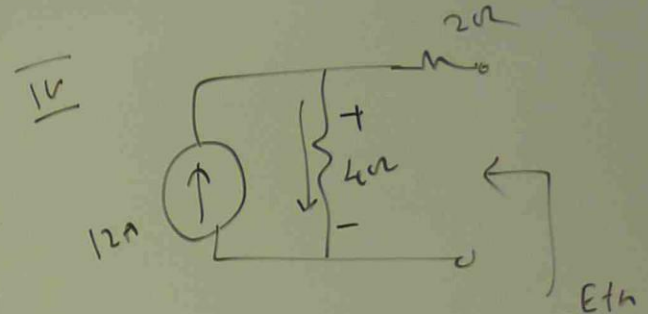III  $R_{th} = R_1 + R_2 = 4 + 2 = 6\Omega$



$V_{4\Omega} = 12 \times 4 = 48V$


$V_{4\Omega} = E_{th} = 48V$

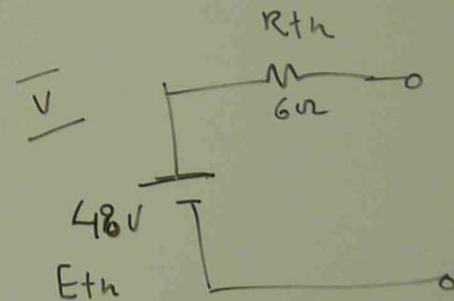



THEVENIN'S EQUIVALENT.



Ex

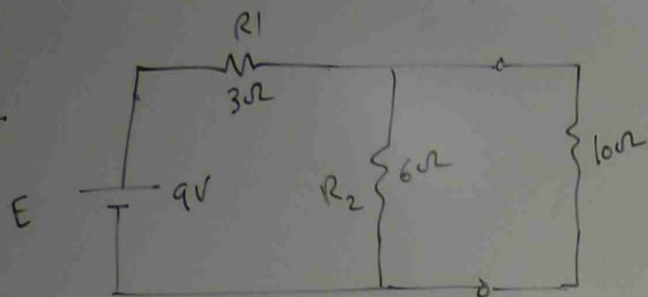


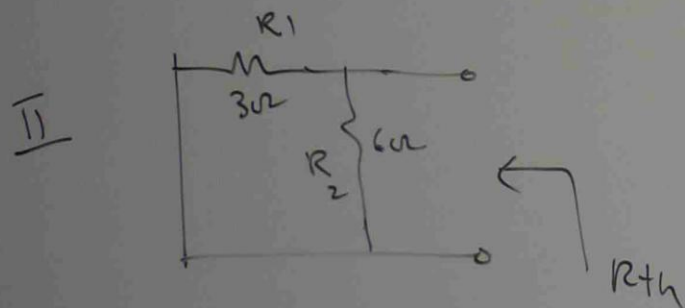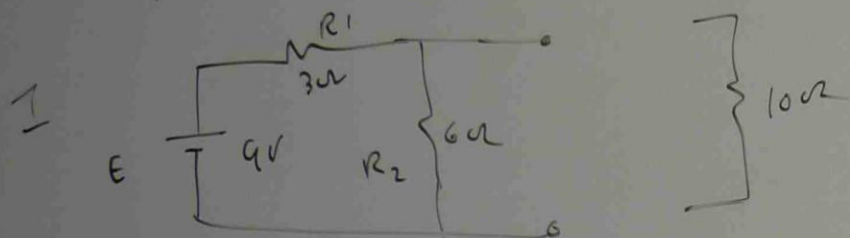FIND THE CURRENT THROUGH  $10\Omega$  RESISTOR BY USING THEVENIN'S THEOREM.



III
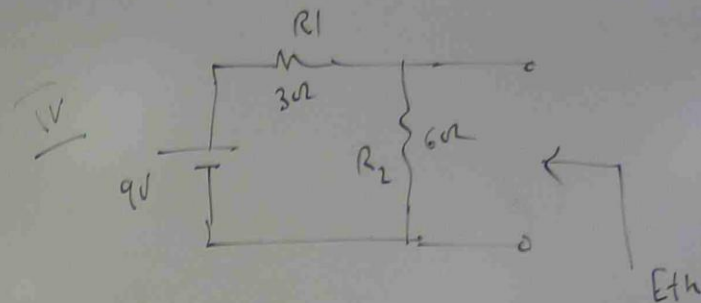
$$R_{th} = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2\Omega$$



$$E_{th} = 9V \times \frac{R_2}{R_1 + R_2}$$

$$= 9 \times \frac{6}{3 + 6}$$


$$= 9 \times \frac{6}{9} = 6V$$

V

$$I_{10\Omega} = \frac{E_{th}}{10\Omega + R_{th}}$$


$$= \frac{6}{10 + 2}$$

$$= \frac{6}{12} = 0.5A$$


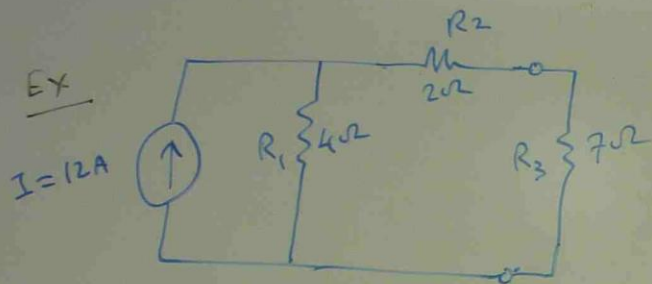


FIND THEVENIN'S EQUIVALENT CIRCUIT ACROSS  $R_3$

THEVENIN'S EQUIVALENT

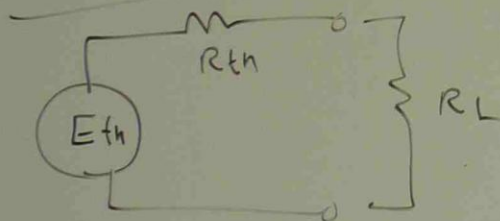


REMOVE  $R_3$

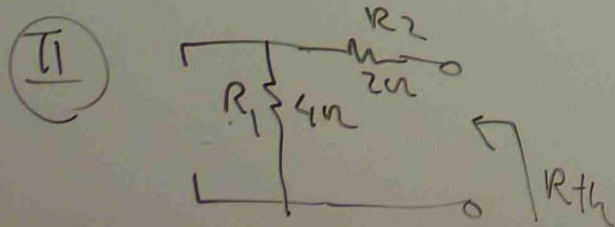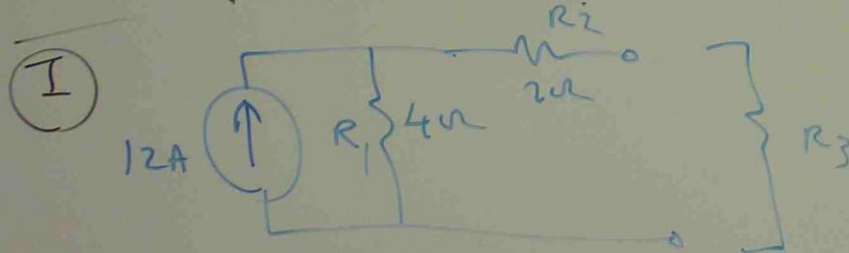


III

$$R_{th} = R_1 + R_2 = 4 + 2 = 6\Omega$$

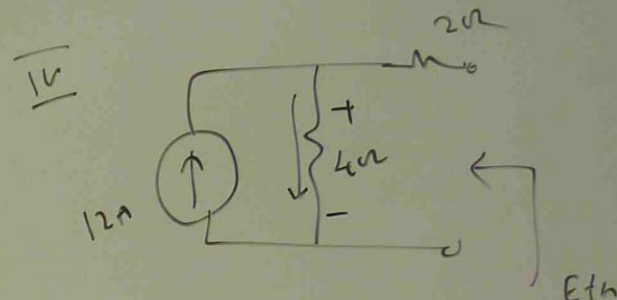


$$V_{4\Omega} = 12 \times 4 = 48V$$

$$V_{4\Omega} = E_{th} = 48V$$


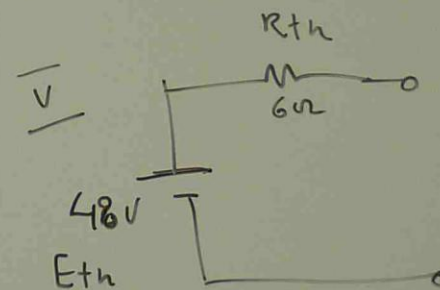


THEVENIN'S EQUIVALENT


# NORTON THEOREM

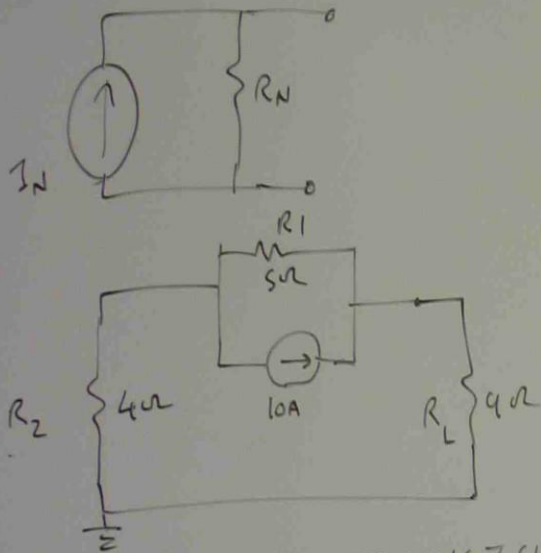

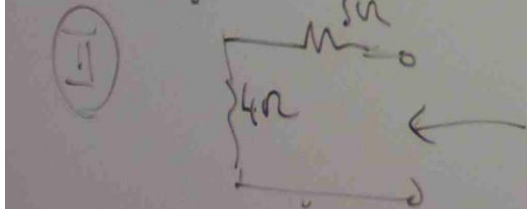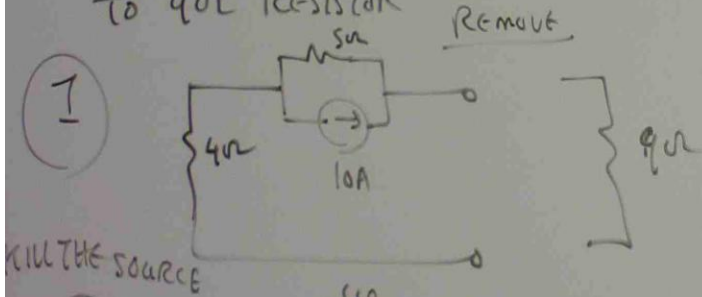
FIND THE NORTON EQUIVALENT CIRCUIT EXTERNAL TO 9Ω RESISTOR



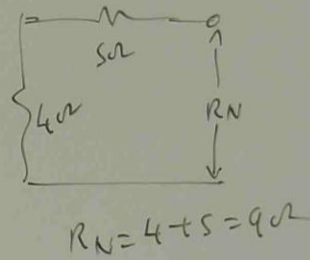III FIND THE EQUIVALENT RESISTANCE ACROSS TERMINAL



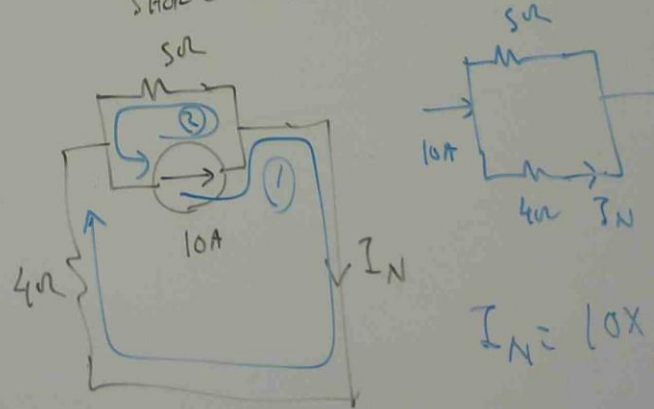IV FIND NORTON CURRENT RE-CONNECT THE SOURCE SHORT CIRCUIT THE TERMINAL



$$I_N = 10 \times \frac{5}{5+4} = \frac{50}{9} = 5.55A$$