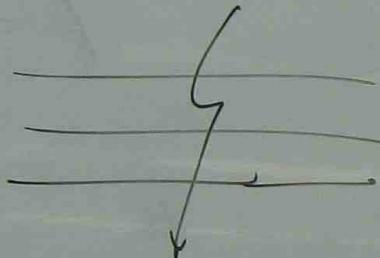


APPLICATION OF POSITIVE, NEGATIVE AND ZERO SEQUENCE IMPEDANCE IN FAULT CALCULATION

BALANCED FAULT




TYPE OF FAULT

$1\phi \rightarrow G$ FAULT




UNBALANCED FAULT


(1) $L \rightarrow G$ FAULT

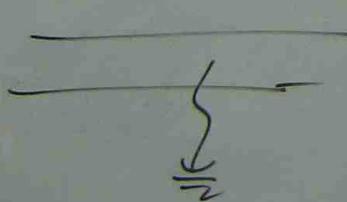


(2) $L-L$ FAULT

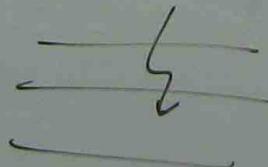


(3) $2L \rightarrow G$ FAULT

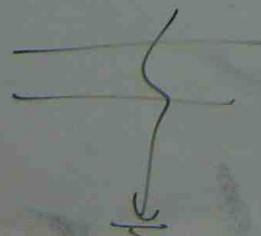



FAULT CURRENT CALCULATION TABLE

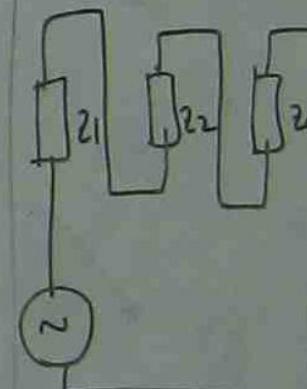TYPE OF FAULT	COMPONENT	CIRCUIT	Z _T	FAULT CURRENT
$1\phi \rightarrow G$ FAULT	+ive, -ive, zero		$Z_T = Z_1 + Z_2 + Z_0$ $I_{A1} = I_{A2} = I_{AO}$	$\Rightarrow \frac{V_{BASE}}{\sqrt{3} V_{LINE}} \times 1.7$

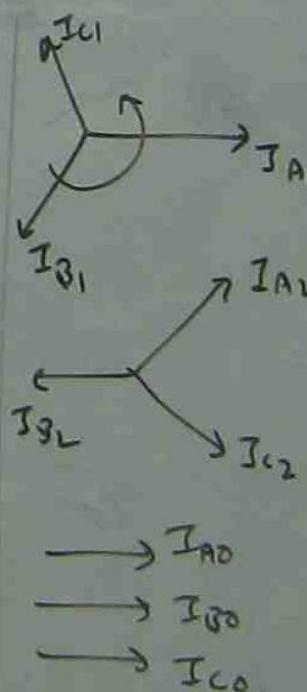


$$I_A = I_{A1} + I_{A2} + I_{A0}$$

$$I_A = 3 I_{A1}$$

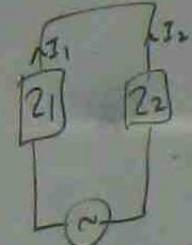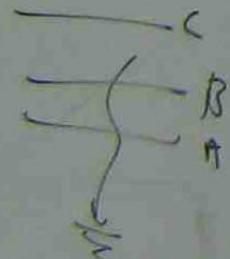Type of Fault	Component	Circuit	ZT	Fault Current
L → L FAULT	positive, -ive	$I_1 = -I_2$ 	$Z_T = Z_1 + Z_2$	$I_1 = \frac{V_A \text{ BASE}}{\sqrt{3} V_{\text{LINE}}} \times \frac{100}{Z_T}$ $(-I_2) = \frac{V_A \text{ BASE}}{\sqrt{3} V_{\text{LINE}}} \times \frac{100}{Z_T}$ $I_A = I_3 = \sqrt{3} I_1$
34	ONLY POSITIVE SEQUENCE	$I_A = I_3 = I_C = \frac{V_A \text{ BASE}}{\sqrt{3} V_{\text{LINE}}} \times \frac{100}{Z_T}$	$Z_T = Z_1$	
2L + G FAULT				

$2L \rightarrow G$ fault

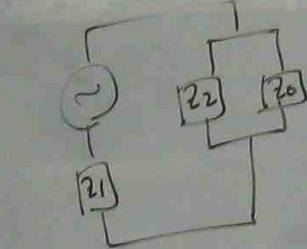


$$Z_T = Z_1 + \frac{Z_2 Z_0}{Z_2 + Z_0}$$

$$I_1 = \frac{V_R \text{ BASE}}{\sqrt{3} V_{\text{LINE}}} \times \frac{100}{1.2T}$$

$$I_2 = \frac{I_1 Z_0}{Z_0 + Z_2}$$

$$I_0 = I_1 \frac{Z_2}{Z_0 + Z_2}$$

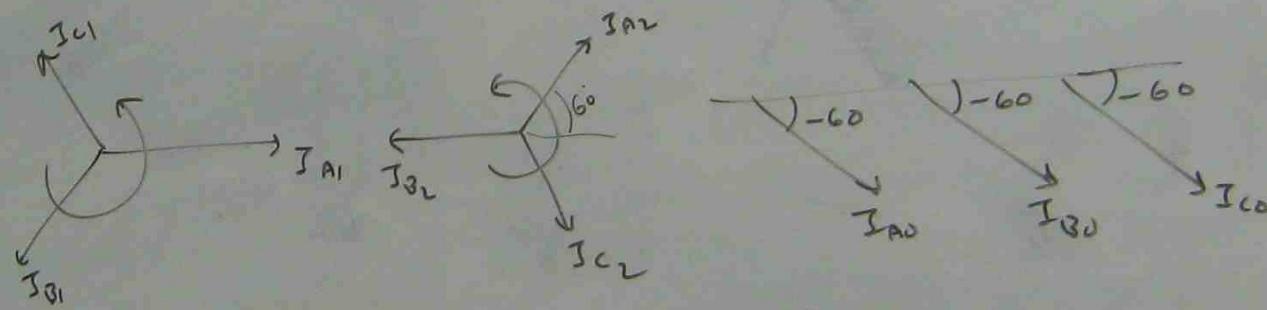

$$I_A = I_1 [0] + I_2 [-60] + I_0 [-60]$$

$$I_B = I_1 [-120] + I_2 [120] + I_0 [-60]$$

$$I_C = I_1 [120] + I_2 [-60] + I_0 [-60]$$

$$I_{\text{FAULT}} = I_A + I_B + I_C$$

Pb

$Z_1 = 10\%$, $Z_2 = 12\%$, 100 MVA BASE, A To B FAULT AT 66 KV.

FIND FAULT CURRENT.

L → L FAULT

$$Z_T = Z_1 + Z_2 = 10 + 12 = 22 \%$$

$$I_1 = -I_2 = \frac{U_A \text{ BASE}}{\sqrt{3} U_{LINE}} \times \frac{100}{22}$$

$$= \frac{100 \times 10^6}{\sqrt{3} \times 66 \times 10^3} \times \frac{100}{22}$$

$$= 3976 \text{ Amp}$$

$$I_A = I_B = \sqrt{3} I_1 = 1.7321 \times 3976 \\ = 6886 \text{ Amp}$$

Pb

$$Z_1 = 6\%, \quad Z_2 = 7\%, \quad Z_0 = 10\%. \quad 100 \text{ mua.} \quad 132 \text{ kV}$$

LINE TO GROUND FAULT. FIND FAULT CURRENT.

$$Z_T = Z_1 + Z_2 + Z_0 = 6 + 7 + 10 = 23\%$$

$$I_{A_1} = I_{A_2} = I_{A_0} = \frac{\text{V.U. BASE}}{\sqrt{3} \text{ V LINE}} \times \frac{100}{7.27}$$

$$= \frac{100 \times 10^6}{1.732 \times 132 \times 10^3} \times \frac{100}{23} = 1902 \text{ Amp}$$

$$I_A = 3 I_{A_1} = 3 \times 1902 = 5706 \text{ Amp}$$

Pb

$$Z_1 = 65\%, \quad Z_2 = 69\%, \quad Z_0 = 40\%.$$

$$\text{BASE MUA} = 100 \text{ mua.} \quad E = 132 \text{ kV}$$

Ph-Ph-E FAULT

CALCULATE FAULT CURRENT.

$$Z_T = Z_1 + \frac{Z_2 Z_0}{Z_2 + Z_0} = 69 + \frac{69 \times 40}{69 + 40} = 90\Omega$$

$$I_1 = \frac{\text{VA BASE}}{\sqrt{3} V_{\text{LINE}}} \times \frac{100}{Z_T} = \frac{100 \times 10^6}{1.93218 / 32 \times 10^3} \times \frac{100}{90} = 4.36 \text{ Amp}$$

$$I_2 = \frac{I_1 Z_0}{Z_0 + Z_2} = \frac{4.36 \times 40}{40 + 69} = 1.183 \text{ Amp}$$

$$I_0 = \frac{I_1 Z_2}{Z_0 + Z_2} = \frac{4.36 \times 69}{69 + 40} = 3.076 \text{ Amp}$$

$$\begin{aligned} I_A &= I_{A1} \angle 0^\circ + I_{A2} \angle 60^\circ + I_{A0} \angle -60^\circ \\ &= I_1 \angle 0^\circ + I_2 \angle 60^\circ + I_0 \angle -60^\circ \\ &= 4.36 \angle 0^\circ + 1.183 \angle 60^\circ + 3.076 \angle -60^\circ \\ &= 4.36(\cos 0 + j \sin 0) + 1.183(\cos 60 + j \sin 60) + 3.076 (\cos(-60) + j \sin(-60)) \\ &= 728.95 - j 111.98 \end{aligned}$$

$$= \sqrt{728.95^2 + 111.98^2} \angle \tan \frac{-111.98}{728.95}$$

$$= 737.4 \angle -8.7^\circ \text{ Amp.}$$

$$I_B = I_{B1} \angle -120^\circ + I_{B2} \angle 180^\circ + I_{B3} \angle -60^\circ$$

$$= I_1 \angle -120^\circ + I_2 \angle 180^\circ + I_o \angle -60^\circ$$

$$= 486 \angle -120^\circ + 178.3 \angle 180^\circ + 307.6 \angle -60^\circ$$

$$I_B = 740.7 \angle -111.9^\circ \text{ Amp}$$

$$I_C = I_{C1} \angle 120^\circ + I_{C2} \angle -60^\circ + I_{Co} \angle -60^\circ$$

$$= I_1 \angle 120^\circ + I_2 \angle -60^\circ + I_o \angle -60^\circ$$

$$= 486 \angle 120^\circ + 178.3 \angle -60^\circ + 307.6 \angle -60^\circ$$

$$= 0$$

$$I_{FAULT} = I_A + I_B + I_C = 737.4 \angle -8.7^\circ + 740.7 \angle -111.9^\circ + 0$$

$$= 737.4 \left(\cos(-8.7) + j \sin(-8.7) \right) + 740.7 \left(\cos(-111.9) + j \sin(-111.9) \right)$$

$$= 918.3 \angle -60.5^\circ \text{ Amp}$$

