
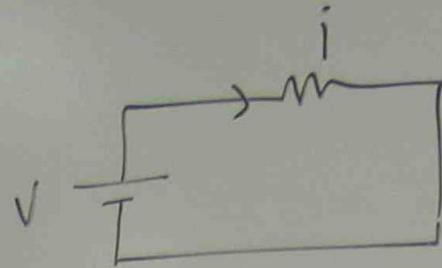






RESISTOR

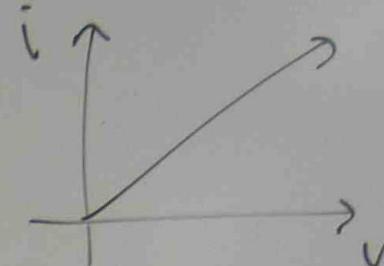

TRANSIENT



CAPACITOR

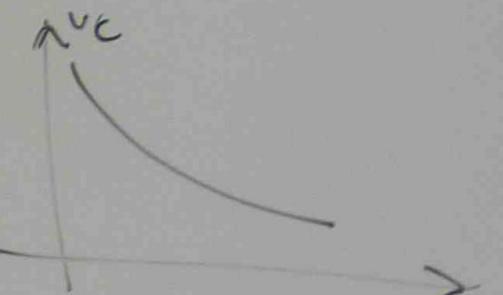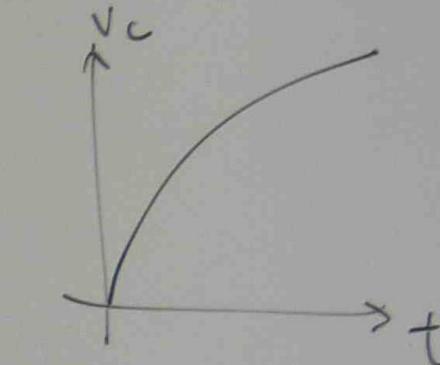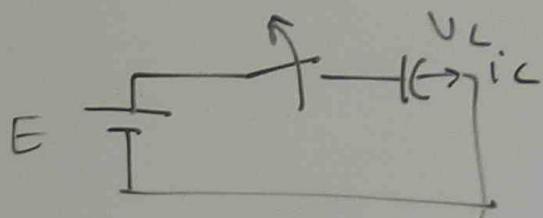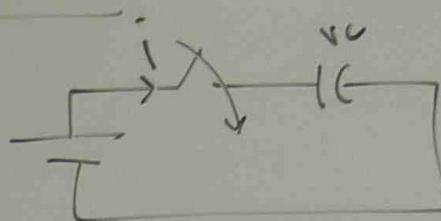


$i_C$  = CHARGING current

FOR CAPACITOR
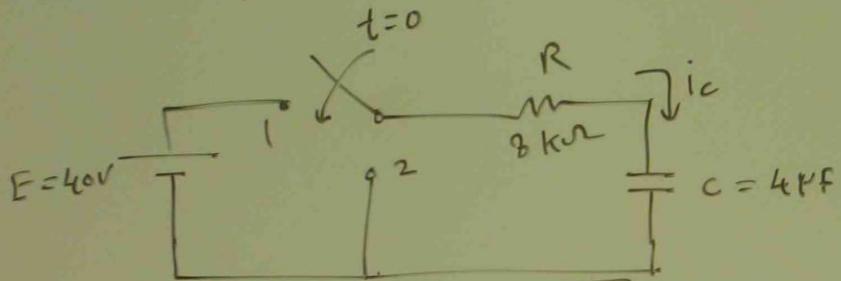
## CHARGING - RC CIRCUIT

Pb

FIND THE MATHEMATICAL EXPRESSIONS FOR THE TRANSIENT BEHAVIOUR OF  $V_C$ ,  $i_C$  AND  $V_R$  FOR THE GIVEN CIRCUIT WHEN THE SWITCH IS MOVED TO POSITION 1. PLOT THE CURVES OF  $V_C$ ,  $i_C$  AND  $V_R$



$$V_C = E \left( 1 - e^{-\frac{t}{RC}} \right)$$

$$= 40 \left( 1 - e^{-\frac{t}{8 \times 10^3 \times 4 \times 10^{-6}}} \right)$$

$$= 40 \left( 1 - e^{-\frac{t}{32 \times 10^{-3}}} \right) \text{ V}$$

$$i_C = \frac{E}{R} e^{-\frac{t}{RC}}$$


$$= \frac{40}{8 \times 10^3} e^{-\frac{t}{32 \times 10^{-3}}}$$

$$= 5 \times 10^{-3} e^{-\frac{t}{32 \times 10^{-3}}} \text{ Amp}$$

$$V_R = E e^{-\frac{t}{RC}}$$

$$= 40 e^{-\frac{t}{32 \times 10^{-3}}} \text{ V}$$


# DISCHARGING RC CIRCUIT

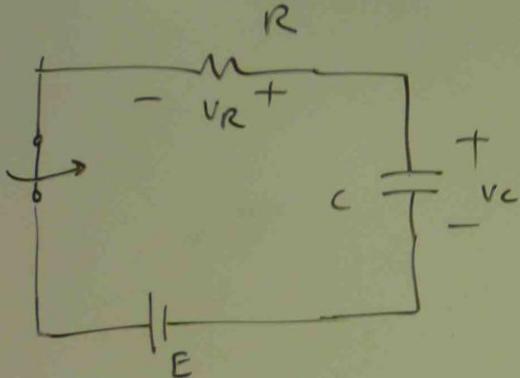

$$V_c = E e^{-t/Rc}$$

$$i_c = \frac{E}{R} e^{-t/Rc}$$

$$V_R = E e^{-t/Rc}$$

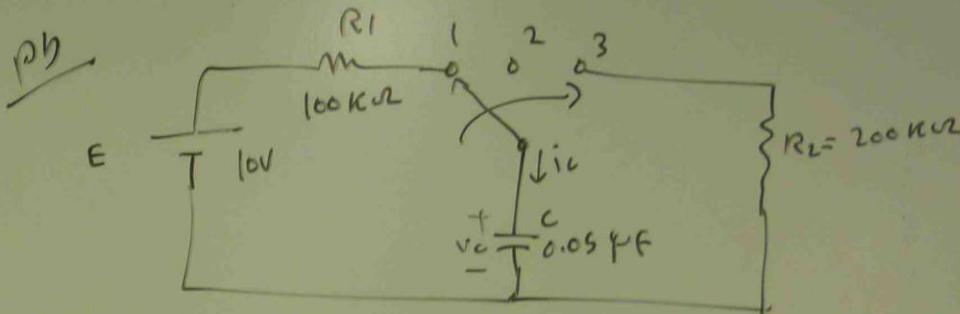

(a) FIND THE MATHEMATICAL EXPRESSION FOR THE TRANSIENT BEHAVIOUR OF THE VOLTAGE ACROSS THE CAPACITOR IF THE SWITCH IS THROWN INTO POSITION 1 AT  $t = 0$  SEC.

(b) REPEAT PART (a) FOR  $i_c$ .

(c) FIND THE MATHEMATICAL EXPRESSIONS FOR THE RESPONSE OF  $V_c$  AND  $i_c$  IF THE SWITCH IS THROWN INTO POSITION 2 AT  $30\text{ ms}$ .

(d) FIND THE MATHEMATICAL EXPRESSION FOR THE VOLTAGE  $V_c$  AND CURRENT  $i_c$  IF THE SWITCH IS THROWN INTO POSITION 3 AT  $t = 4.8\text{ ms}$ .

(e) PLOT THE WAVEFORMS OBTAINED IN PART (a) THROUGH (d).

SWITCH AT POSITION "1"

CAPACITOR CHARGING


(a)

$$V_C = E \left( 1 - e^{-\frac{t}{\tau}} \right)$$

$$= 10 \left( 1 - e^{-\frac{t}{R_1 C}} \right)$$

$$= 10 \left( 1 - e^{-\frac{t}{100 \times 10^3 \times 0.05 \times 10^{-6}}} \right)$$
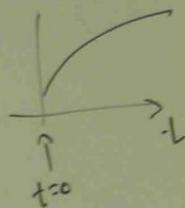
$$= 10 \left( 1 - e^{-\frac{t}{5 \times 10^3}} \right) V$$



(c)

SWITCH AT POSITION "2"

OFF CIRCUIT

$$V_C = 10V$$

$$i_C = 0$$

(d) SWITCH AT POSITION "3"

DISCHARGE

$$\tau = R_C$$

$$V_C = E e^{-\frac{t}{\tau}}$$

$$= 10 e^{-\frac{t}{R_2 C}}$$

$$= 10 e^{-\frac{t}{200 \times 10^3 \times C}}$$

$$= 10 e^{-\frac{t}{10 \times 10^3}} V$$

(b)

$$i_C = \frac{E}{R_1} e^{-\frac{t}{R_1 C}}$$

$$= \frac{10}{100 \times 10^3} e^{-\frac{t}{100 \times 10^3 \times 0.05 \times 10^{-6}}}$$

$$= 0.1 \times 10^{-3} e^{-\frac{t}{5 \times 10^3}} \text{ Amp}$$

$$i_C = -\frac{E}{R_2} e^{-\frac{t}{R_2 C}}$$

$$= -\frac{10}{200 \times 10^3} e^{-\frac{t}{10 \times 10^3}} A$$

A

$$= -0.05 \times 10^{-3} e^{-\frac{t}{10 \times 10^3}} A$$

A

SWITCH AT POSITION "2"

(c)  $V_C = 10V$

OFF CIRCUIT

$i_C = 0$

SWITCH AT POSITION "3"

DISCHARGE

$T = RC$

$$V_C = E e^{-t/\tau}$$



$$= -\frac{t}{R_2 C}$$

$$= 10 e^{-\frac{t}{200 \times 10^3 \times C}}$$

$$= 10 e^{-\frac{t}{10 \times 10^3}}$$


$$i_C = -\frac{E}{R_2} e^{-t/\tau}$$
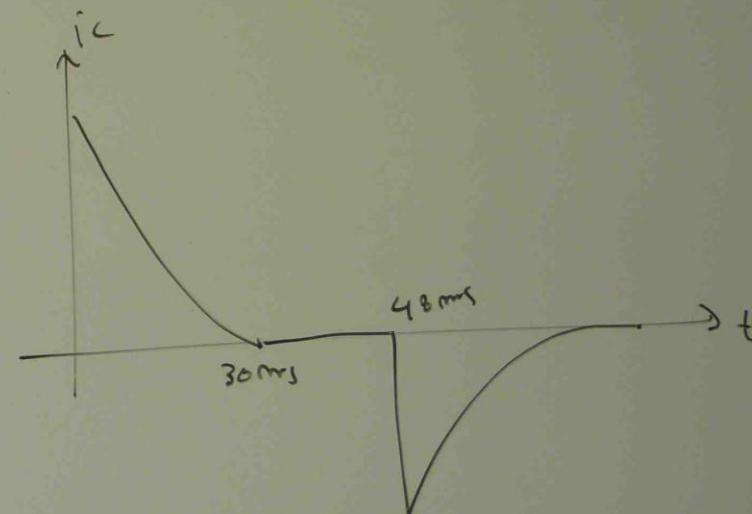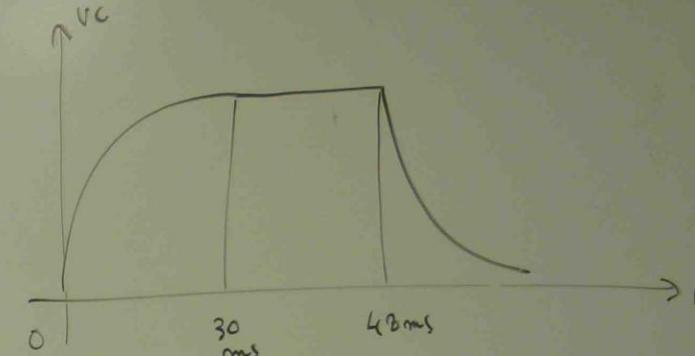
$$= -\frac{10}{200 \times 10^3} e^{-\frac{t}{10 \times 10^3}}$$



PB

FOR THE NETWORK GIVEN IN FIGURE :

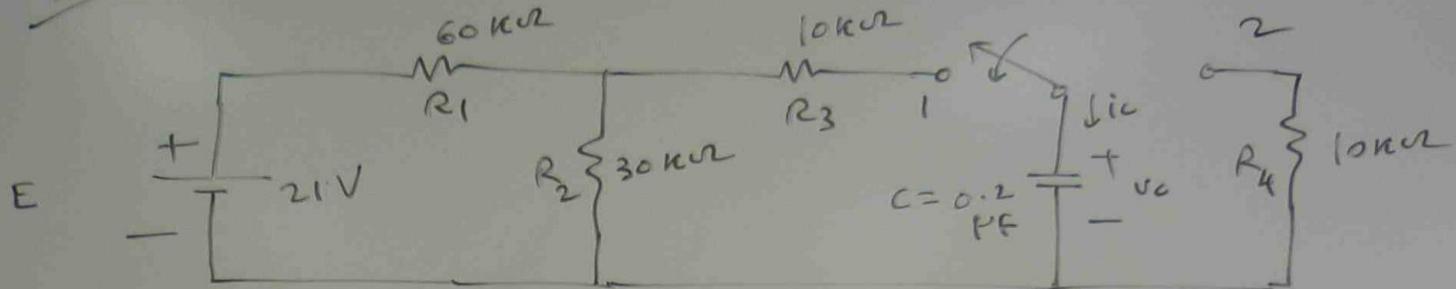


(a) FIND THE MATHEMATICAL EXPRESSION FOR THE TRANSIENT BEHAVIOUR OF THE VOLTAGE  $v_c$  AND THE CURRENT  $i_c$  FOLLOWING THE CLOSING OF THE SWITCH POSITION 1 AT  $t = 0$  SEC.

(b) FIND THE MATHEMATICAL EXPRESSION FOR THE VOLTAGE  $v_c$  AND CURRENT  $i_c$  AS A FUNCTION OF TIME IF THE SWITCH IS THROWN INTO POSITION 2 AT  $t = 9\text{ ms}$

(c) DRAW THE RESULTANT WAVEFORMS.


(a)

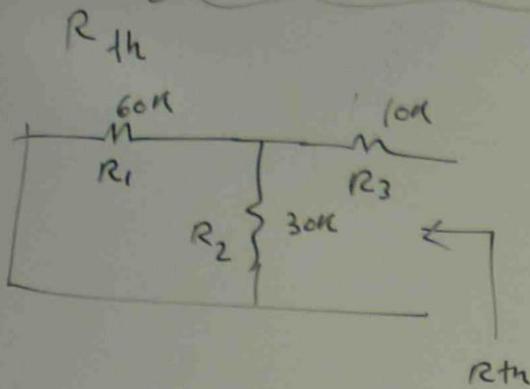SWITCH AT POSITION (1) CHARGING

$$R_{th} = R_1 \parallel (R_2 + R_3)$$

$$= \frac{60 \times 30}{60+30} + 10$$

$$R_{th} = 30 \text{ k}\Omega$$

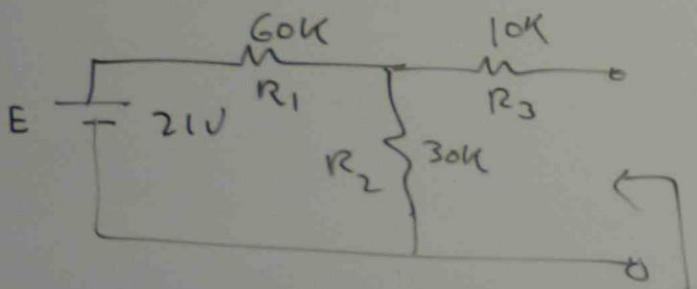

$$V_{R2} = E \times \frac{R_2}{R_1 + R_2} = 21 \times \frac{30}{60+30} = 7V$$

$$E_{th} = V_{R2} = 7V$$

$$\begin{aligned} V_C &= E_{th} \left( 1 - e^{-\frac{t}{RC}} \right) \\ &= 7 \left( 1 - e^{-\frac{t}{R_{th} C}} \right) \\ &= 7 \left( 1 - e^{-\frac{t}{30 \times 10^3 \times 0.2 \times 10^{-6}}} \right) \end{aligned}$$

$$i_C = \frac{E_{th}}{R} e^{-\frac{t}{R_{th} C}} = \frac{7}{30 \times 10^3} e^{-\frac{t}{6 \times 10^3}}$$

(b) SWITCH AT POSITION (2)  
DISCHARGING

CHARGING VOLTAGE UP TO 9ms

$$V_C = 7 \left( 1 - e^{-\frac{t}{6 \times 10^3}} \right) V$$

$$\begin{aligned} \text{AT } t &= 9 \text{ ms} \quad - \frac{9 \times 10^{-3}}{6 \times 10^3} \\ V_C &= 7 \left( 1 - e^{-\frac{9 \times 10^{-3}}{6 \times 10^3}} \right) \end{aligned}$$

$$E_{th} = V_{R2} = 7V$$

$$V_c = E_{th} \left( 1 - e^{-\frac{t}{RC}} \right)$$

$$= 7 \left( 1 - e^{-\frac{t}{R_{th}C}} \right)$$

$$= 7 \left( 1 - e^{-\frac{t}{30 \times 10^3 \times 0.2 \times 10^{-6}}} \right)$$

$$i_c = \frac{E_{th}}{R} e^{-\frac{t}{RC}} = \frac{7}{30k\Omega} e^{-\frac{t}{6 \times 10^{-3}}} \\ = (0.233 \times 10^3) e^{-\frac{t}{6 \times 10^{-3}}}$$

(b) SWITCH AT POSITION "2"  
DISCHARGING

CHARGING VOLTAGE UP TO 9ms

$$V_c = 7 \left( 1 - e^{-\frac{t}{6 \times 10^{-3}}} \right) V$$

$$\text{AT } t = 9 \text{ ms} \quad - \frac{9 \times 10^{-3}}{6 \times 10^{-3}}$$

$$V_c = 7 \left( 1 - e^{-\frac{t}{6 \times 10^{-3}}} \right)$$

$$V_c = 7 \left( 1 - e^{-\frac{t}{6 \times 10^{-3}}} \right) = 5.44V$$

$$(9 \text{ ms}) \quad - \frac{9 \times 10^{-3}}{6 \times 10^{-3}}$$

$$i_c (9 \text{ ms}) = 0.233 \times 10^3 \times e^{-\frac{9 \times 10^{-3}}{6 \times 10^{-3}}} \\ = 0.233 \times 10^3 \times e^{-1.5}$$

$$i_c (9 \text{ ms}) = 0.052 \text{ mA}$$

$$V_c = E e^{-\frac{t}{RC}}$$

$$= V_c (9 \text{ ms}) e^{-\frac{t}{RC}}$$

$$= 5.44 e^{-\frac{t}{R \cdot C}}$$

$$= 5.44 e^{-\frac{t}{10 \times 10^{-3} \times 0.2 \times 10^{-6}}}$$

$$= 5.44 e^{-\frac{t}{2 \times 10^{-3}}} \quad \checkmark$$

$$-\frac{t}{2 \times 10^{-3}}$$


$$i_c = -\frac{V_c (9 \text{ ms})}{R} e^{-\frac{t}{R \cdot C}}$$

$$= -\frac{5.44}{10 \times 10^{-3}} e^{-\frac{t}{2 \times 10^{-3}}}$$

$$i_c = -0.054 e^{-\frac{t}{2 \times 10^{-3}}}$$

A

Q3 FOR THE NETWORK GIVEN IN FIGURE:

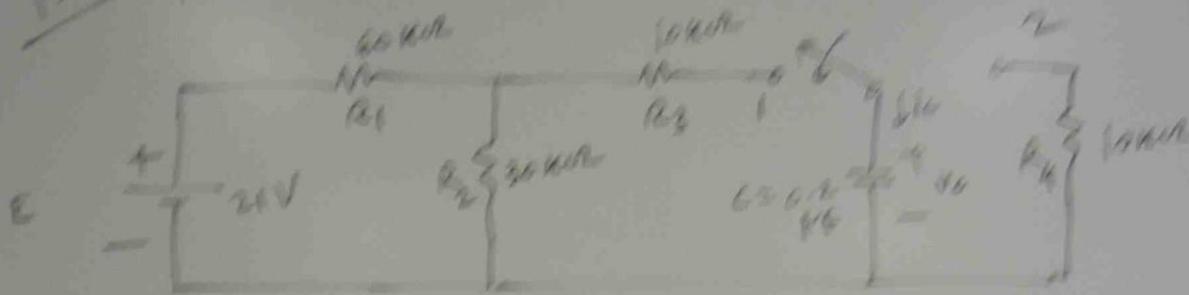


(a) FIND THE MATHEMATICAL EXPRESSION FOR THE TRANSIENT BEHAVIOR OF THE VOLTAGE  $V_C$  AS A FUNCTION OF TIME FOLLOWING THE CLOSING OF THE SWITCH POSITION 1 AT  $t = 0$  sec.

(b) FIND THE MATHEMATICAL EXPRESSION FOR THE VOLTAGE  $V_C$  AND CURRENT  $I_C$  AS A FUNCTION OF TIME IF THE SWITCH IS THROWN INTO POSITION 2 AT  $t = 9$  sec.

(c) DRAW THE RESULTANT WAVEFORMS.

(a)


SWITCH AT POSITION (1) CHARGING

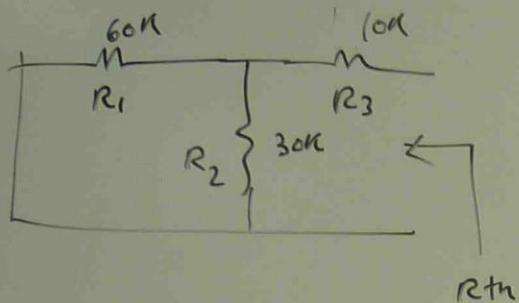 $R_{th}$ 

$$R_{th} = R_1 \parallel (R_2 + R_3)$$

$$= \frac{60 \times 30}{60+30} + 10$$

$$R_{th} = 30 \text{ k}\Omega$$

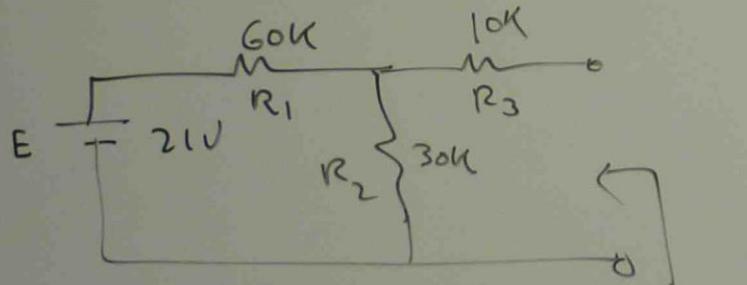

$$V_{R2} = E \times \frac{R_2}{R_1 + R_2} = 21 \times \frac{30}{60+30} = 7 \text{ V}$$

$$E_{th} = V_{R2} = 7 \text{ V}$$

$$\begin{aligned} V_C &= E_{th} \left( 1 - e^{-\frac{t}{\tau}} \right) \\ &= 7 \left( 1 - e^{-\frac{t}{R_{th} C}} \right) \\ &= 7 \left( 1 - e^{-\frac{t}{30 \times 10^3 \times 0.2 \times 10^{-6}}} \right) \\ i_C &= \frac{E_{th}}{R} e^{-\frac{t}{R_{th} C}} = \frac{7}{30 \times 10^3} e^{-\frac{t}{6 \times 10^{-3}}} \end{aligned}$$

(b) SWITCH AT POSITION (2)  
DISCHARGING

CHARGING VOLTAGE UP TO 9ms

$$V_C = 7 \left( 1 - e^{-\frac{t}{6 \times 10^{-3}}} \right) \text{ V}$$

$$\text{AT } t = 9 \text{ ms} \quad -\frac{9 \times 10^{-3}}{6 \times 10^{-3}}$$

$$V_C = 7 \left( 1 - e^{-\frac{9 \times 10^{-3}}{6 \times 10^{-3}}} \right)$$

$$E_{fh} = V_{R2} = 7V$$

$$V_c = E_{fh} \left( 1 - e^{-\frac{t}{R_{fh} C}} \right)$$

$$= 7 \left( 1 - e^{-\frac{t}{R_{fh} C}} \right)$$

$$= 7 \left( 1 - e^{-\frac{t}{30 \times 10^3 \times 0.2 \times 10^{-6}}} \right)$$

$$i_C = \frac{E_{fh}}{R} e^{-\frac{t}{R C}} = \frac{7}{30 \times 10^3} e^{-\frac{t}{6 \times 10^{-3}}}$$

$$= (0.233 \times 10^3) e^{-\frac{t}{6 \times 10^{-3}}}$$

(a) SWITCH AT POSITION "2")  
DISCHARGING

CHARGING VOLTAGE UP TO 9ms

$$V_c = 7 \left( 1 - e^{-\frac{t}{6 \times 10^{-3}}} \right) V$$

$$\text{AT } t = 9 \text{ ms} \quad - \frac{9 \times 10^{-3}}{6 \times 10^{-3}}$$

$$V_c = 7 \left( 1 - e^{-\frac{9 \times 10^{-3}}{6 \times 10^{-3}}} \right)$$

$$V_c = 7 \left( 1 - e^{-\frac{1.5}{6 \times 10^{-3}}} \right) = 5.44V$$

$$i_C(9 \text{ ms}) = 0.233 \times 10^3 \times e^{-\frac{1.5}{6 \times 10^{-3}}}$$

$$= 0.233 \times 10^3 \times e^{-1.5}$$

$$i_C(9 \text{ ms}) = 0.052 \text{ mA}$$

$$V_c = E \bar{e}^{-\frac{t}{R C}}$$

$$= V_c(9 \text{ ms}) \bar{e}^{-\frac{t}{R C}}$$

$$= 5.44 \bar{e}^{-\frac{t}{R C}}$$

$$= 5.44 \bar{e}^{-\frac{t}{10 \times 10^3 \times 0.2 \times 10^{-6}}}$$

$$= 5.44 \bar{e}^{-\frac{t}{2 \times 10^3}}$$

$$i_C = - \frac{V_c(9 \text{ ms})}{R} \bar{e}^{-\frac{t}{R C}}$$


$$= - \frac{5.44}{10 \times 10^3} \bar{e}^{-\frac{t}{2 \times 10^3}}$$

$$- \frac{t}{2 \times 10^3}$$

A


## CAPACITORS IN SERIES & PARALLEL

PARALLEL

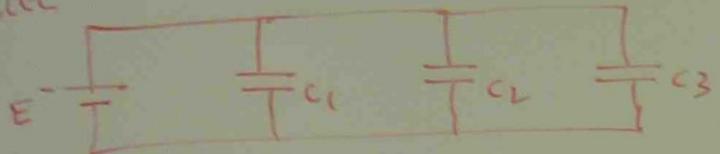


$$C_T = C_1 + C_2 + C_3$$

SERIES

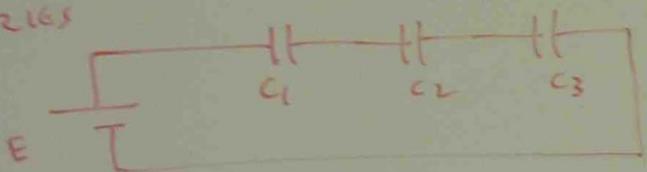

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

ph

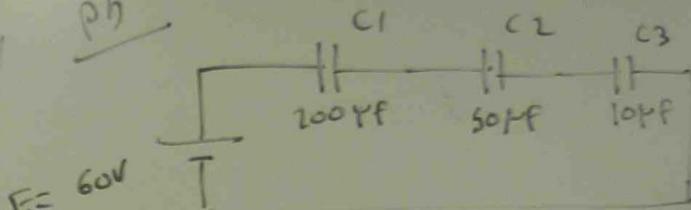


- FIND (a) TOTAL CAPACITANCE  
 (b) DETERMINE THE CHARGE ON EACH PLATE  
 (c) FIND VOLTAGE ACROSS EACH CAPACITOR.

$$\begin{aligned}\frac{1}{C_T} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \\ &= \frac{1}{200} + \frac{1}{50} + \frac{1}{10}\end{aligned}$$

$$\frac{1}{C_T} = 0.125$$

$$C_T = \frac{1}{0.125} = 8 \mu F$$

ph

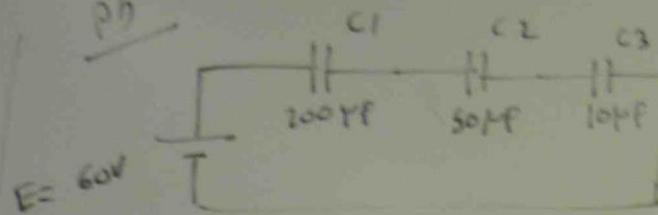

- FIND  
 (a) TOTAL CAPACITANCE  
 (b) DETERMINE THE CHARGE ON  
 EACH PLATE  
 (c) FIND VOLTAGE ACROSS  
 EACH CAPACITOR.

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$= \frac{1}{200} + \frac{1}{50} + \frac{1}{10}$$

$$\frac{1}{C_T} = 0.125$$

$$C_T = \frac{1}{0.125} = 8 \mu F$$

SAME CHARGE

$$Q_T = Q_1 = Q_2 = Q_3$$

$$Q_T = C_T E$$

$$Q_T = 8 \times 10^{-6} \times 60 = 480 \times 10^{-6} C$$

$$V_1 = \frac{Q_T = Q_1}{C_1} = \frac{480 \times 10^{-6}}{200 \times 10^{-6}} = 2.4 V$$

$$V_2 = \frac{Q_2}{C_2} = \frac{480 \times 10^{-6}}{50 \times 10^{-6}} = 9.6 V$$

$$V_3 = \frac{Q_3}{C_3} = \frac{480 \times 10^{-6}}{10 \times 10^{-6}} = 48 V$$

SAME CHARGE

$$Q_T = Q_1 = Q_2 = Q_3$$

$$Q_T = C_T E$$

$$Q_T = 8 \times 10^{-6} \times 60 = 480 \times 10^{-6} C$$

$$V_1 = \frac{Q_T = Q_1}{C_1} = \frac{480 \times 10^{-6}}{200 \times 10^{-6}} = 2.4 V$$

$$V_2 = \frac{Q_2}{C_2} = \frac{480 \times 10^{-6}}{50 \times 10^{-6}} = 9.6 V$$

$$V_3 = \frac{Q_3}{C_3} = \frac{480 \times 10^{-6}}{10 \times 10^{-6}} = 48 V$$

$$\text{ENERGY STORED IN CAPACITOR} = \frac{1}{2} C V^2$$

(Joules)

$$\text{ENERGY STORED IN CAPACITOR } C_1 = \frac{1}{2} C_1 V_1^2$$

$$= \frac{1}{2} \times 200 \times 10^{-6} \times 2.4^2$$

$$= 576 \times 10^{-6}$$

$$= 0.576 \text{ mJ}$$

XX