

Fault Analysis

- **Fault types:**
 - ◆ balanced faults
 - three-phase
 - ◆ unbalanced faults
 - single-line to ground
 - double-line to ground
 - line-to-line faults
- **Unbalance fault analysis requires new tools**
 - ◆ symmetrical components
 - ◆ augmented component models


Percentage of total faults

| |
|--------|
| <5% |
| 60-75% |
| 15-25% |
| 5-15% |


Symmetrical Components

- Allow unbalanced three-phase phasor quantities to be replaced by the sum of three separate but balanced symmetrical components
 - ◆ applicable to current and voltages
 - ◆ permits modeling of unbalanced systems and networks

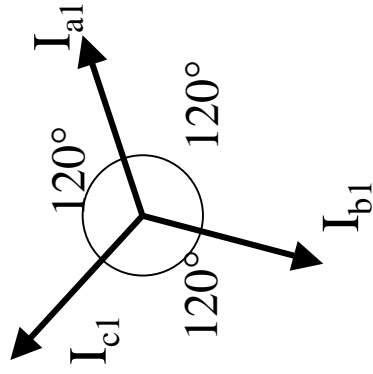
- **Representative symmetrical components**



abc sequence
positive sequence

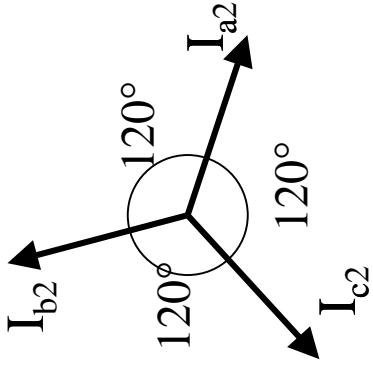

acb sequence
negative sequence

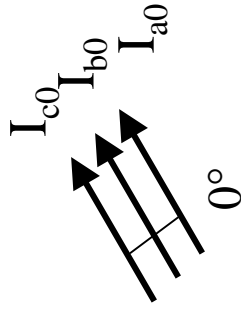

zero sequence

Symmetrical Components

- **Positive sequence phasors**

$$I_{a1} = |I_{a1}| \angle (\delta + 0^\circ) = I_{a1}$$

$$I_{b1} = |I_{a1}| \angle (\delta + 240^\circ) = a^2 I_{a1}$$

$$I_{c1} = |I_{a1}| \angle (\delta + 120^\circ) = a I_{a1}$$

- **Operator a identities**

$$a = 1 \angle 120^\circ = -0.5 + j0.866$$

$$a^2 = 1 \angle 240^\circ = -0.5 - j0.866$$

$$a^3 = 1 \angle 0^\circ = 1 + j0$$

$$1 + a + a^2 = 0$$

Power Systems I

Symmetrical Components

- **Negative sequence phasors**

$$I_{a2} = |I_{a2}| \angle (\delta + 0^\circ) = I_{a2}$$

$$I_{b2} = |I_{a2}| \angle (\delta + 120^\circ) = a I_{a2}$$

$$I_{c2} = |I_{a2}| \angle (\delta + 240^\circ) = a^2 I_{a2}$$

- **Zero sequence phasors**

$$I_{a0} = |I_{a0}| \angle (\delta + 0^\circ) = I_{a0}$$

$$I_{b0} = |I_{a0}| \angle (\delta + 0^\circ) = I_{a0}$$

$$I_{c0} = |I_{a0}| \angle (\delta + 0^\circ) = I_{a0}$$

Symmetrical Components

- Relating unbalanced phasors to symmetrical components

$$I_a = I_{a0} + I_{a1} + I_{a2} = I_{a0} + I_{a1} + I_{a2}$$

$$I_b = I_{b0} + I_{b1} + I_{b2} = I_{a0} + a^2 I_{a1} + a I_{a2}$$

$$I_c = I_{c0} + I_{c1} + I_{c2} = I_{a0} + a I_{a1} + a^2 I_{a2}$$

- In matrix notation

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

Symmetrical Components

- [A] is known as the symmetrical components transformation matrix
- Solving for the symmetrical components leads to

$$\mathbf{I}_{abc} = \mathbf{A} \mathbf{I}_{012} \qquad \mathbf{A} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$\mathbf{I}_{012} = \mathbf{A}^{-1} \mathbf{I}_{abc}$$

$$\mathbf{A}^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} = \frac{1}{3} \mathbf{A}^*$$

Symmetrical Components

- In component form, the calculation for symmetrical components are

$$I_{a0} = \frac{1}{3} (I_a + I_b + I_c)$$

$$I_{a1} = \frac{1}{3} (I_a + aI_b + a^2 I_c)$$

$$I_{a2} = \frac{1}{3} (I_a + a^2 I_b + aI_c)$$

Symmetrical Components

- Similar expressions exist for voltages

$$\mathbf{V}_{abc} = \mathbf{A} \mathbf{V}_{012}$$

$$\mathbf{V}_{012} = \mathbf{A}^{-1} \mathbf{V}_{abc}$$

- The apparent power may also be expressed in terms of symmetrical components

$$S_{3\phi} = \mathbf{V}_{abc}^T \mathbf{I}_{abc}^*$$

$$S_{3\phi} = (\mathbf{A} \mathbf{V}_{012})^T (\mathbf{A} \mathbf{I}_{012})^*$$

$$S_{3\phi} = \mathbf{V}_{012}^T \mathbf{A}^T \mathbf{A}^* \mathbf{I}_{012}^* \quad \mathbf{A}^T \mathbf{A}^* = 3$$

$$S_{3\phi} = 3 \mathbf{V}_{012}^T \mathbf{I}_{012}^* = 3 V_{a0} I_{a0}^* + 3 V_{a1} I_{a1}^* + 3 V_{a2} I_{a2}^*$$

Power Systems I

Example

- Obtain the symmetrical components of a set of unbalanced currents

$$I_a = 1.6 \angle 25^\circ$$

$$I_b = 1.0 \angle 180^\circ$$

$$I_c = 0.9 \angle 132^\circ$$

- **Solution**





$$I_{a0} = \frac{(1.6 \angle 25^\circ) + (1.0 \angle 180^\circ) + (0.9 \angle 132^\circ)}{3} = 0.45 \angle 96.5^\circ$$

$$I_{a1} = \frac{(1.6 \angle 25^\circ) + a(1.0 \angle 180^\circ) + a^2(0.9 \angle 132^\circ)}{3} = 0.94 \angle -0.1^\circ$$

$$I_{a2} = \frac{(1.6 \angle 25^\circ) + a^2(1.0 \angle 180^\circ) + a(0.9 \angle 132^\circ)}{3} = 0.60 \angle 22.3^\circ$$

Power Systems I

Example

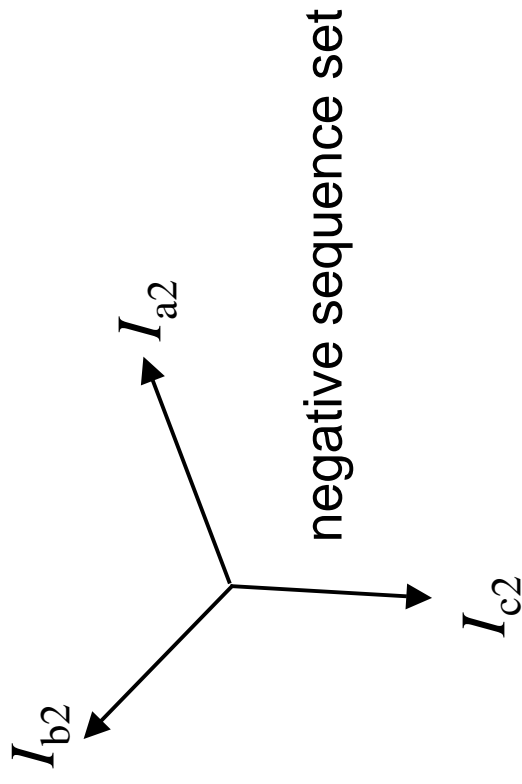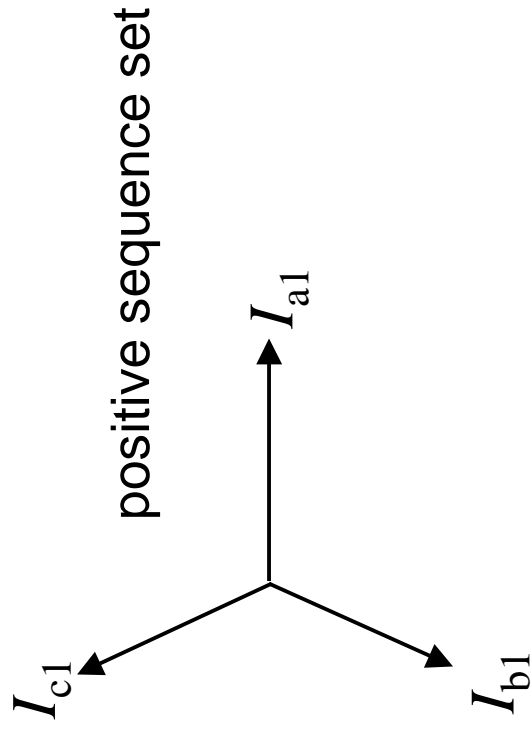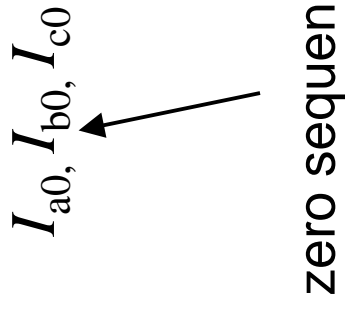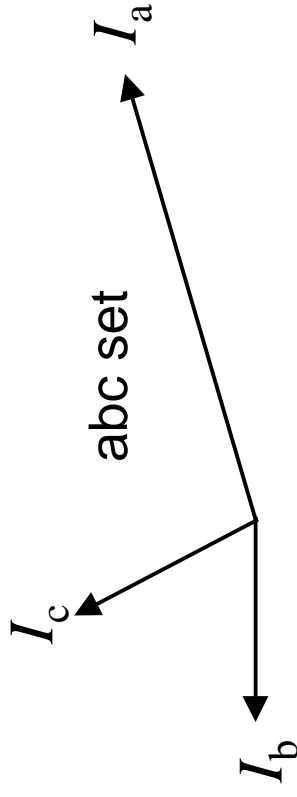

Example

- The symmetrical components of a set of unbalanced voltages are

$$V_{a0} = 0.6 \angle 90^\circ$$

$$V_{a1} = 1.0 \angle 30^\circ$$

$$V_{a2} = 0.8 \angle -30^\circ$$

Obtain the original unbalanced voltages:

$$V_a = (0.6 \angle 90^\circ) + (1.0 \angle 30^\circ) + (0.8 \angle -30^\circ) = 1.7088 \angle 24.2^\circ$$

$$V_b = (0.6 \angle 90^\circ) + a^2(1.0 \angle 30^\circ) + a(0.8 \angle -30^\circ) = 0.4 \angle 90^\circ$$

$$V_c = (0.6 \angle 90^\circ) + a(1.0 \angle 30^\circ) + a^2(0.8 \angle -30^\circ) = 1.7088 \angle 155.8^\circ$$

Example

V_{a0}, V_{b0}, V_{c0}

V_{c1} V_{a1}

zero sequence set

positive sequence set

V_{b1}

V_{b2} V_{c2} V_{a2}

negative sequence set

V_c V_b V_a


abc set

Power Systems I

Sequence Impedances

- The impedance offered to the flow of a sequence current creating sequence voltages
 - ◆ positive, negative, and zero sequence impedances
- **Augmented network models**
 - ◆ wye-connected balanced loads
 - ◆ transmission line
 - ◆ 3-phase transformers
 - ◆ generators

Balanced Loads

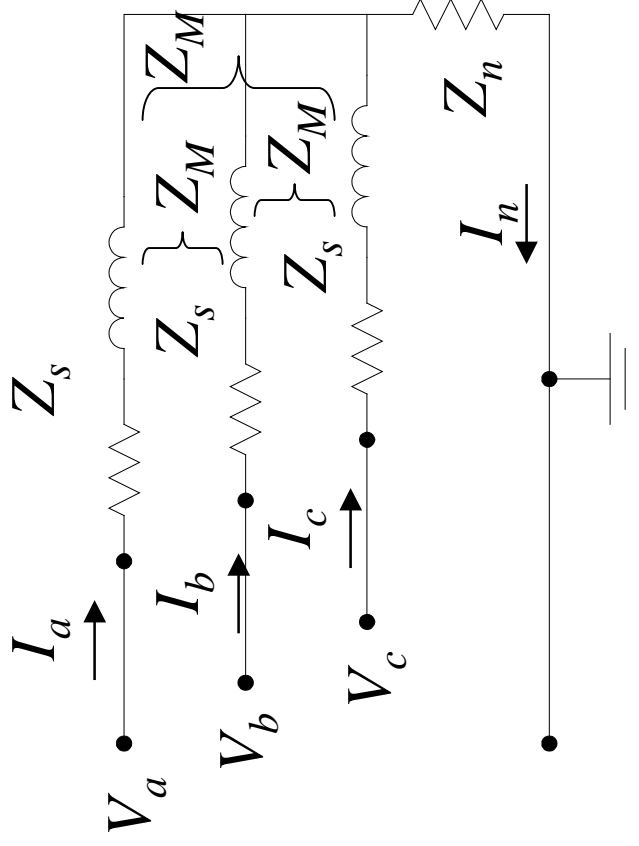

Model and governing equations

$$V_a = Z_S I_a + Z_M I_b + Z_M I_c + Z_n I_n$$

$$V_b = Z_M I_a + Z_S I_b + Z_M I_c + Z_n I_n$$

$$V_c = Z_M I_a + Z_M I_b + Z_S I_c + Z_n I_n$$

$$I_n = I_a + I_b + I_c$$

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} Z_S + Z_n & Z_M + Z_n & Z_M + Z_n \\ Z_M + Z_n & Z_S + Z_n & Z_M + Z_n \\ Z_M + Z_n & Z_M + Z_n & Z_S + Z_n \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$\mathbf{V}_{abc} = \mathbf{Z}_{abc} \mathbf{I}_{abc}$$

Power Systems I

Balanced Loads

$$\mathbf{V}_{abc} = \mathbf{Z}_{abc} \mathbf{I}_{abc} \rightarrow (\mathbf{A} \mathbf{V}_{012}) = \mathbf{Z}_{abc} (\mathbf{A} \mathbf{I}_{012})$$

$$\mathbf{V}_{012} = [\mathbf{A}^{-1} \mathbf{Z}_{abc} \mathbf{A}] \mathbf{I}_{012} \rightarrow \mathbf{V}_{012} = \mathbf{Z}_{012} \mathbf{I}_{012}$$


$$\mathbf{Z}_{012} = [\mathbf{A}^{-1} \mathbf{Z}_{abc} \mathbf{A}]$$

$$= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} Z_S + Z_n & Z_M + Z_n & Z_M + Z_n \\ Z_M + Z_n & Z_S + Z_n & Z_M + Z_n \\ Z_M + Z_n & Z_M + Z_n & Z_S + Z_n \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$= \begin{bmatrix} Z_S + 3Z_n + 2Z_M & 0 & 0 \\ 0 & Z_S - Z_M & 0 \\ 0 & 0 & Z_S - Z_M \end{bmatrix}$$

Power Systems I

Transmission Line

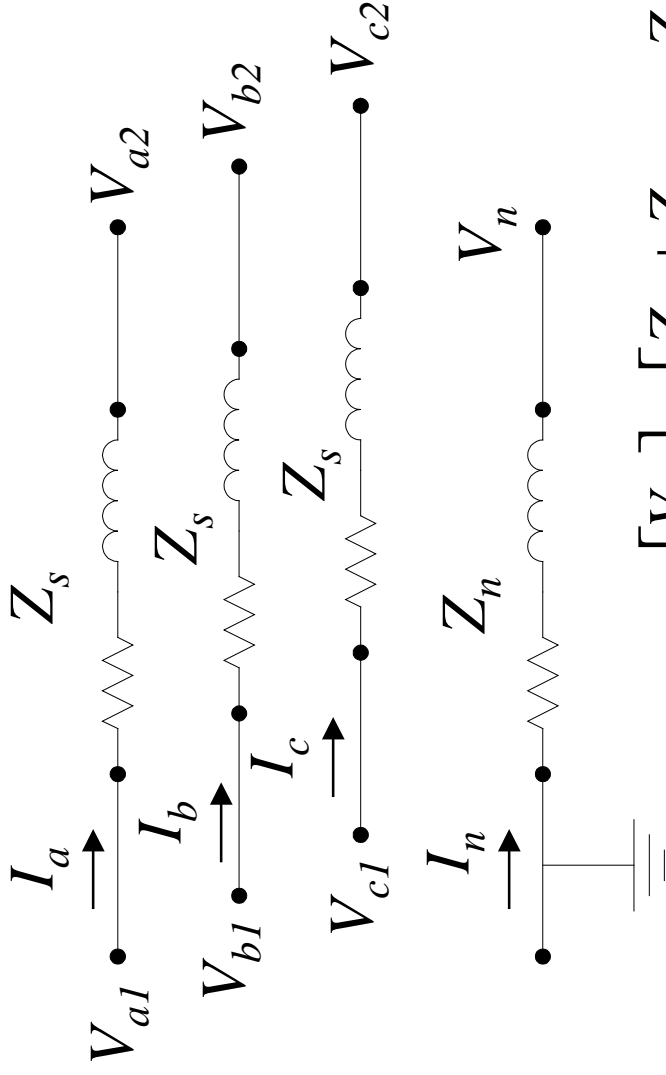

$$\begin{aligned} V_{a1} &= Z_s I_a - Z_n I_n + V_{a2} \\ V_{b1} &= Z_s I_b - Z_n I_n + V_{b2} \\ V_{c1} &= Z_s I_c - Z_n I_n + V_{c2} \\ V_n &= 0 + Z_n I_n \\ I_n + I_a + I_b + I_c &= 0 \end{aligned}$$

$$\begin{bmatrix} V_{a1} \\ V_{b1} \\ V_{c1} \end{bmatrix} = \begin{bmatrix} Z_s + Z_n & Z_n & Z_n \\ Z_n & Z_s + Z_n & Z_n \\ Z_n & Z_n & Z_s + Z_n \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} + \begin{bmatrix} V_{a2} \\ V_{b2} \\ V_{c2} \end{bmatrix}$$

$$\mathbf{V}_{abc1} = \mathbf{Z}_{abc} \mathbf{I}_{abc} + \mathbf{V}_{abc2}$$

Power Systems I

Transmission Line

$$\mathbf{V}_{abc1} = \mathbf{Z}_{abc} \mathbf{I}_{abc} + \mathbf{V}_{abc2} \rightarrow \mathbf{A} \mathbf{V}_{012-1} = \mathbf{Z}_{abc} \mathbf{A} \mathbf{I}_{012} + \mathbf{A} \mathbf{V}_{012-2}$$

$$\mathbf{V}_{012-1} = \mathbf{A}^{-1} \mathbf{Z}_{abc} \mathbf{A} \mathbf{I}_{012} + \mathbf{V}_{012-2} = \mathbf{Z}_{012} \mathbf{I}_{012} + \mathbf{V}_{012-2}$$

$$\mathbf{Z}_{012} = \mathbf{A}^{-1} \mathbf{Z}_{abc} \mathbf{A}$$

$$= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} Z_S + Z_n & Z_n & Z_n \\ Z_n & Z_S + Z_n & Z_n \\ Z_n & Z_n & Z_S + Z_n \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$


$$= \begin{bmatrix} Z_S + 3Z_n & 0 & 0 \\ 0 & Z_S & 0 \\ 0 & 0 & Z_S \end{bmatrix}$$

Power Systems I

Generators


- **Similar modeling of impedances to sequence impedances**
- **Typical values for common generators**
 - ◆ remember that the transient fault impedance is a function of time
 - ◆ positive sequence values are the same as X_d , X_d' , and X_d''
 - ◆ negative sequence values are affected by the rotation of the rotor
 - $X_2 \sim X_d''$
 - ◆ zero sequence values are isolated from the airgap of the machine
 - the zero sequence reactance is approximated to the leakage reactance
 - $X_0 \sim X_L$

Generator Model

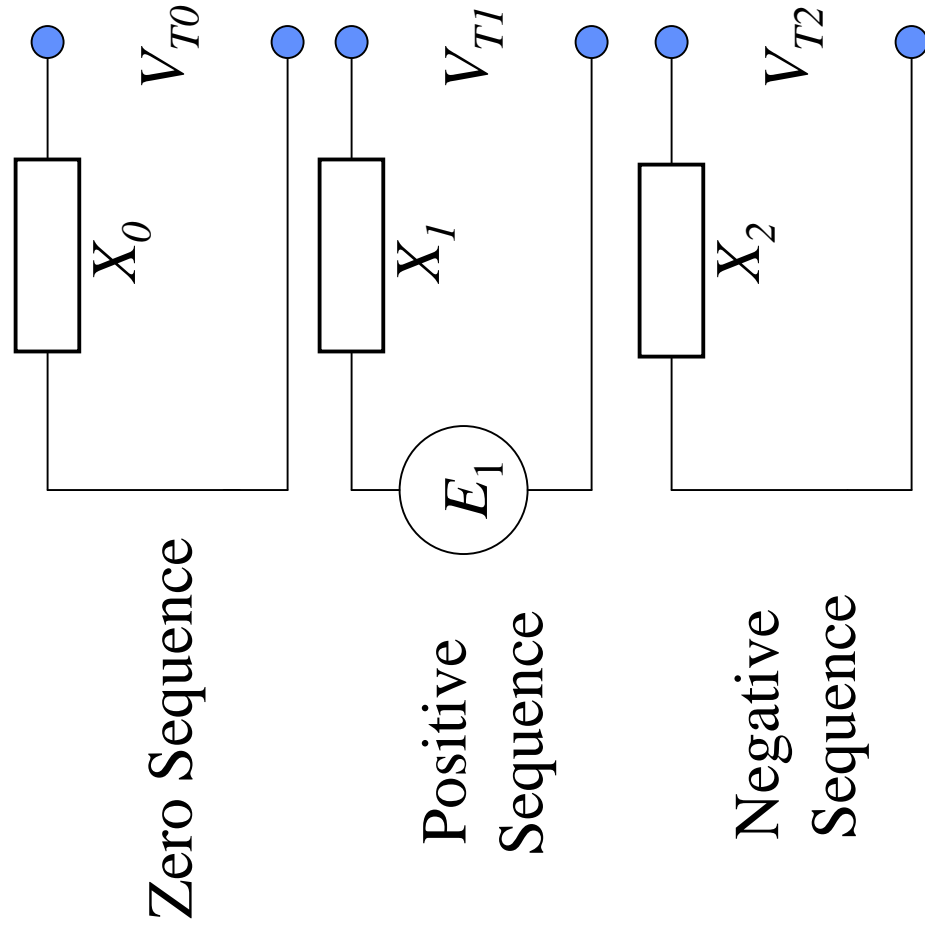

Power Systems I

Impedance Grounded Generators

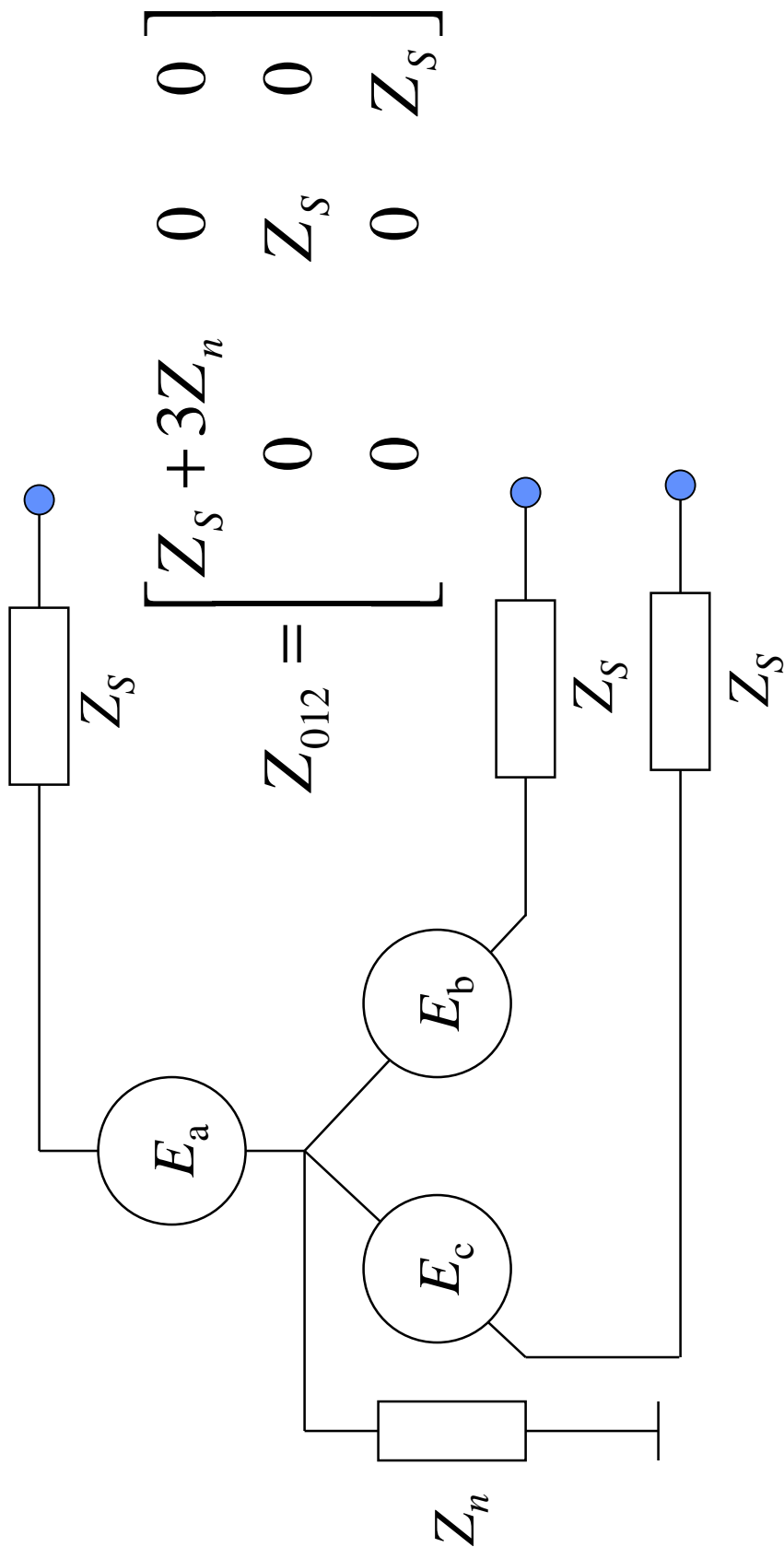

Transformers

- **Series Leakage Impedance**
 - ◆ the magnetization current and core losses represented by the shunt branch are neglected (they represent only 1% of the total load current)
 - ◆ the transformer is modeled with the equivalent series leakage impedance
- **Three single-phase units & five-legged core three-phase units**
 - ◆ the series leakage impedance is the same for all the sequences $Z_0 = Z_1 = Z_2 = Z_\ell$
- **Three-legged core three-phase units**
 - ◆ the series leakage impedance is the same for the positive and negative sequence only $Z_1 = Z_2 = Z_\ell$


Transformers

- **Wye-delta transformers create a phase shifting pattern for the various sequences**
 - ◆ the positive sequence quantities rotate by +30 degrees
 - ◆ the negative sequence quantities rotate by -30 degrees
 - ◆ the zero sequence quantities can not pass through the transformer
- **USA standard**
 - ◆ independent of the winding order (Δ -Y or Y- Δ)
 - ◆ the positive sequence line voltage on the HV side leads the corresponding line voltage on the LV side by 30°
 - ◆ consequently, for the negative sequence voltages the corresponding phase shift is -30°


Transformers

- Zero-sequence network connections of the transformer depends on the winding connection
 - ◆ primary winding - wye / wye-grounded / delta
 - ◆ secondary winding - wye / wye-grounded / delta

Transformers

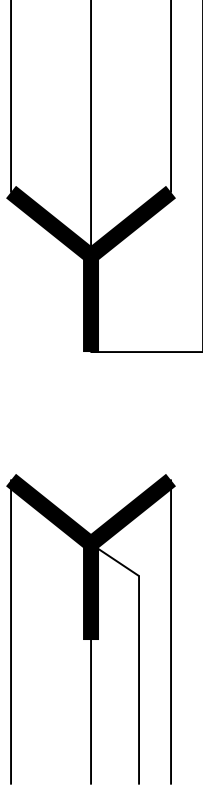


wye-grounded wye-grounded

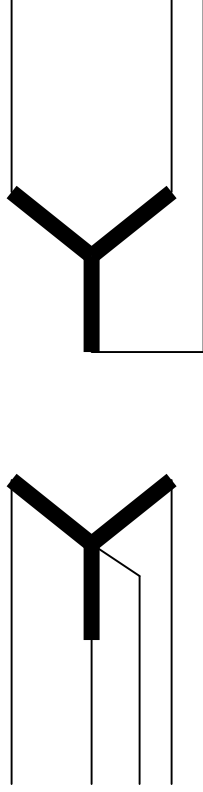




wye-grounded

wye

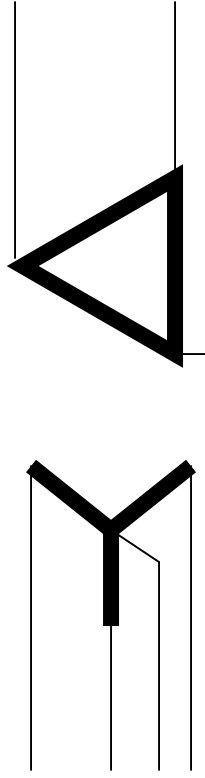


wye-grounded


delta

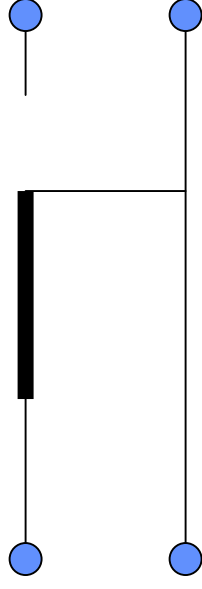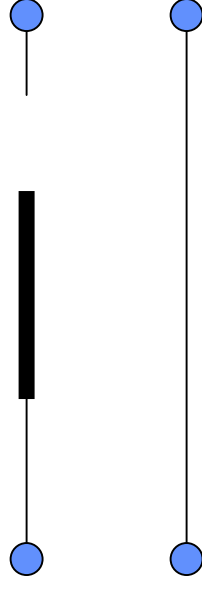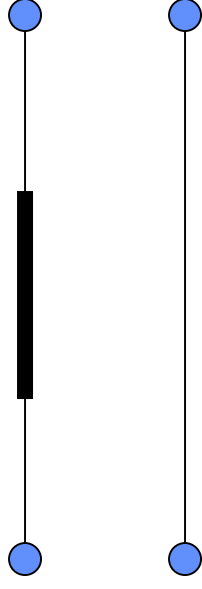



Transformers

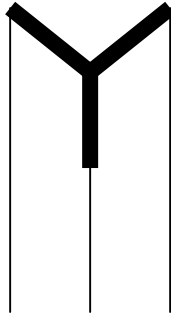


wye

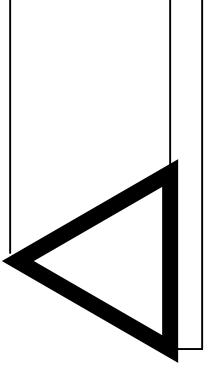

delta

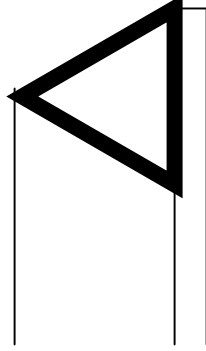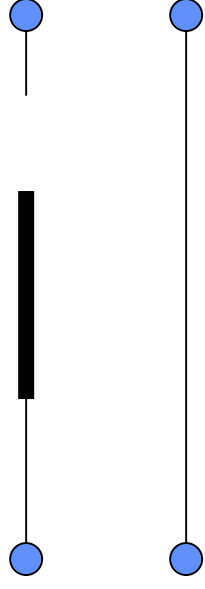

delta

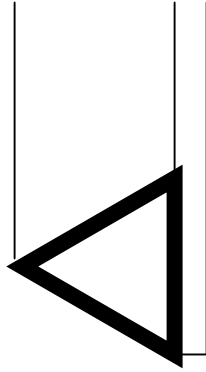

delta

