

The Bus Impedance Matrix

- **Definition**


$$\mathbf{Z}_{bus} = \mathbf{Y}_{bus}^{-1}$$

- **Direct formation of the matrix**

- ◆ inversion of the bus admittance matrix is a n^3 effort
- ◆ for small and medium size networks, direct building of the matrix is less effort
- ◆ for large size networks, sparse matrix programming with gaussian elimination technique is preferred


Forming the Bus Impedance Matrix

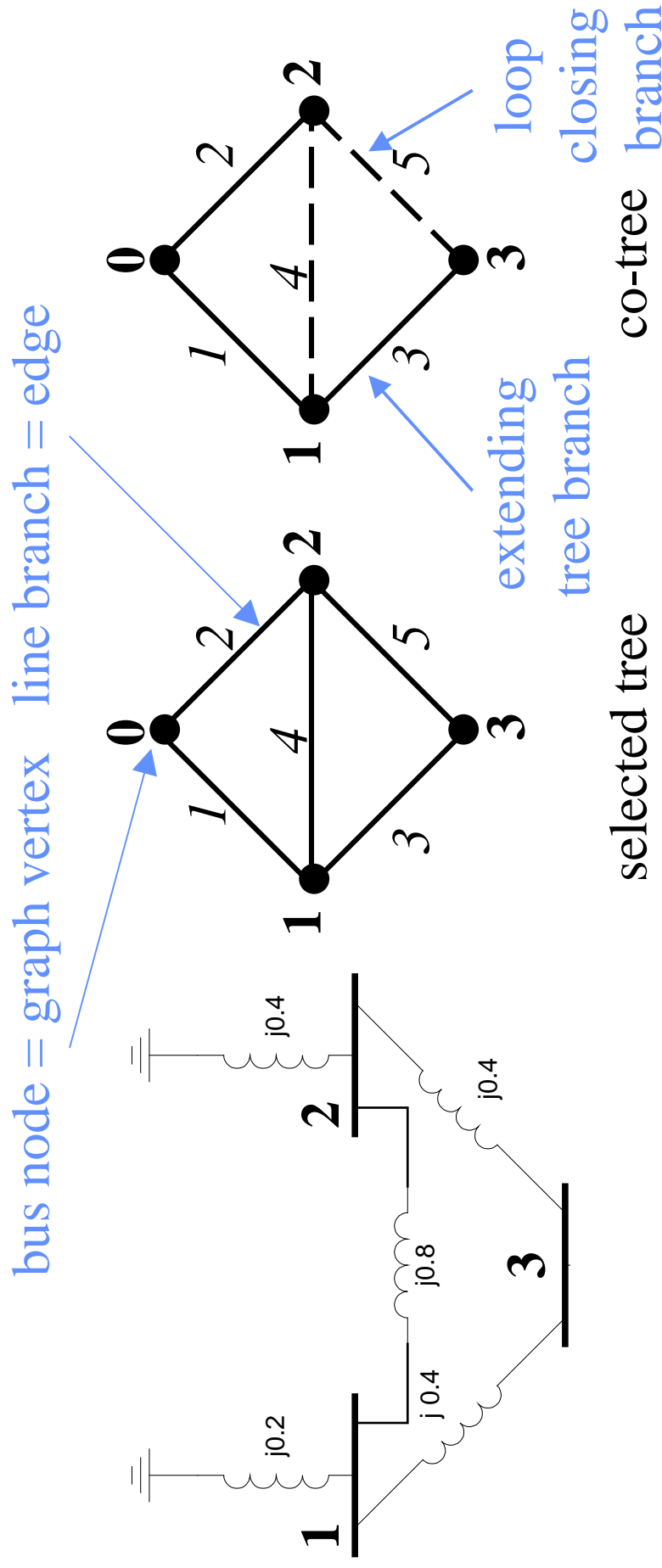- Graph theory techniques helps explain the building process




Forming the Bus Impedance Matrix

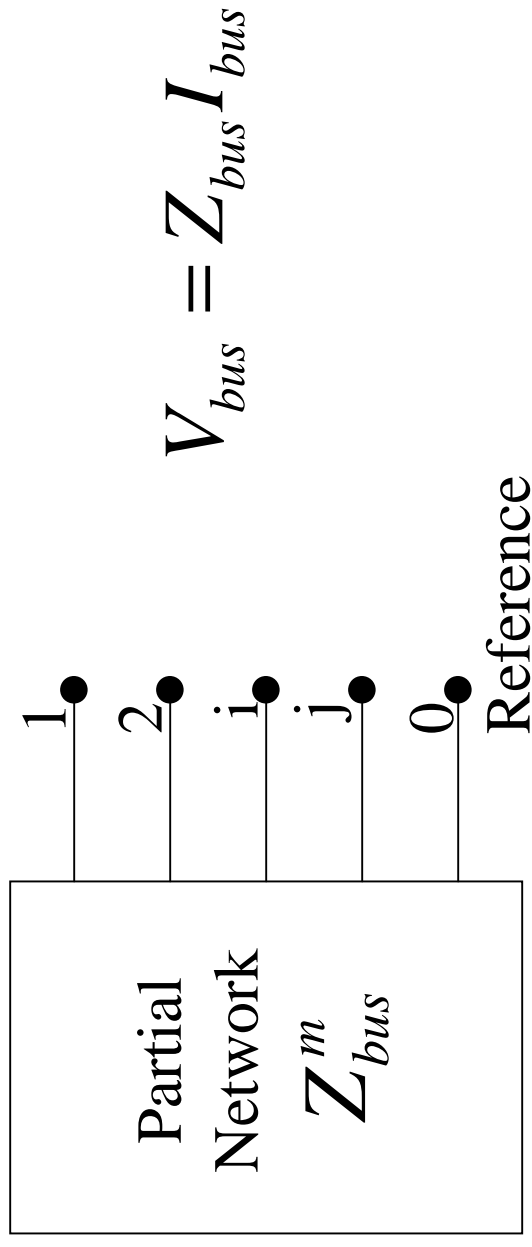
- Basic construction of the network and the matrix



Adding a Line

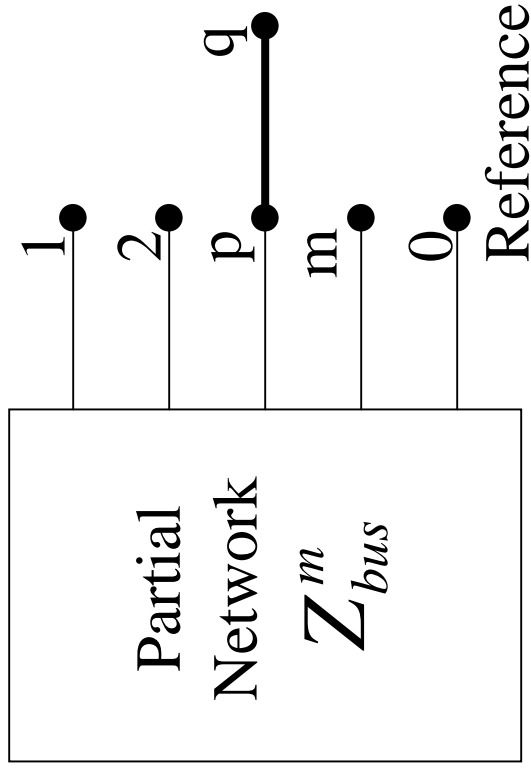

$$V_q = V_p + Z_{qp} I_q$$

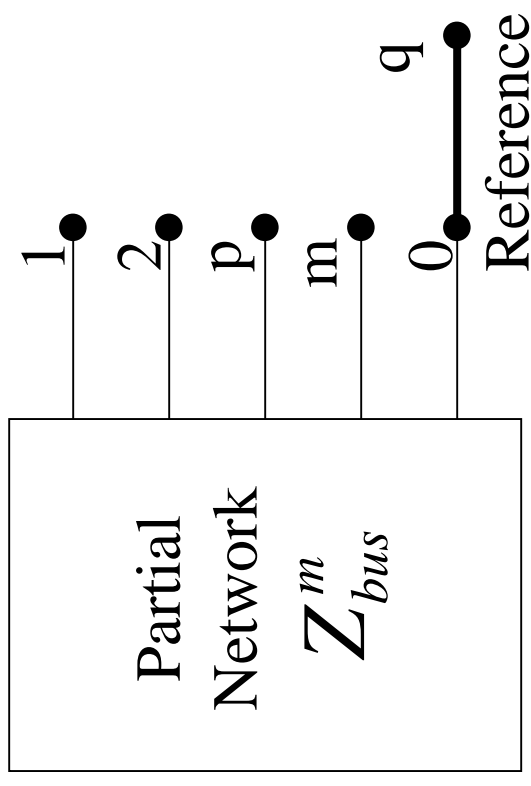

$$V_q = 0 + Z_{q0} I_q$$

Power Systems I

Adding a Line to an Existing Line

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_p \\ \vdots \\ V_m \\ V_q \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{21} & \cdots & Z_{1p} & \cdots & Z_{1m} \\ Z_{21} & Z_{22} & \cdots & Z_{2p} & \cdots & Z_{2m} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{p1} & Z_{p2} & \cdots & Z_{pp} & \cdots & Z_{pm} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{m1} & Z_{m2} & \cdots & Z_{mp} & \cdots & Z_{mm} \\ = Z_{p1} & = Z_{p2} & \cdots & = Z_{pp} & \cdots & = Z_{pm} \\ V_q & & & = Z_{pq} + Z_{pp} & & \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_p \\ \vdots \\ I_m \\ I_q \end{bmatrix}$$


The diagram illustrates the process of adding a new line (p) to an existing system. The impedance matrix is partitioned into two parts: the first part represents the existing system (lines 1 to m), and the second part represents the new line (line p). The new line is added as a new row and column in the matrix. The diagonal element Z_{pp} is updated to include the self-impedance of the new line. The off-diagonal elements Z_{pj} and Z_{jp} are updated to include the mutual impedances between the new line and the existing lines.

Adding a Line from Reference

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_p \\ \vdots \\ V_m \\ V_q \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{21} & \cdots & Z_{1p} & \cdots & Z_{1m} \\ Z_{21} & Z_{22} & \cdots & Z_{2p} & \cdots & Z_{2m} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{p1} & Z_{p2} & \cdots & Z_{pp} & \cdots & Z_{pm} \\ \vdots & \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{m1} & Z_{m2} & \cdots & Z_{mp} & \cdots & Z_{mm} \\ =0 & =0 & \cdots & =0 & \cdots & =0 \end{bmatrix} \begin{bmatrix} =0 \\ =0 \\ \vdots \\ =0 \\ \vdots \\ =0 \\ =Z_{0q} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_p \\ \vdots \\ I_m \\ I_q \end{bmatrix}$$


Power Systems I

Closing a Loop

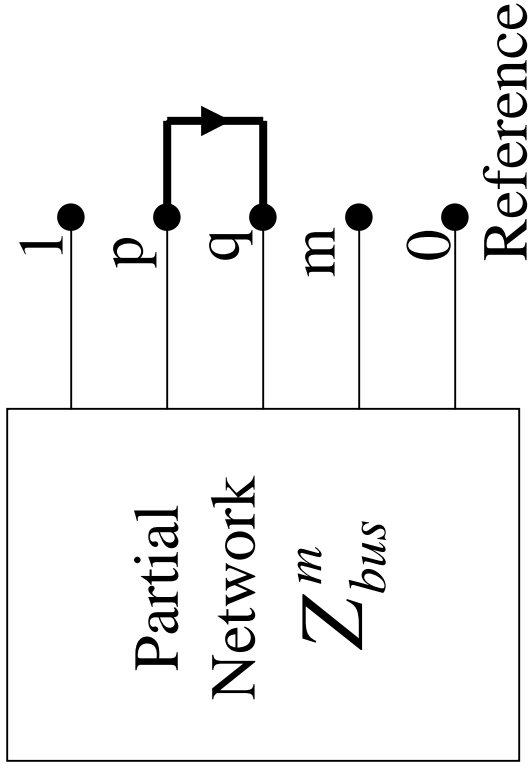

$$Z_{pq} I_l = V_p - V_q \rightarrow$$

$$Z_{pq} I_l + V_q - V_p = 0$$

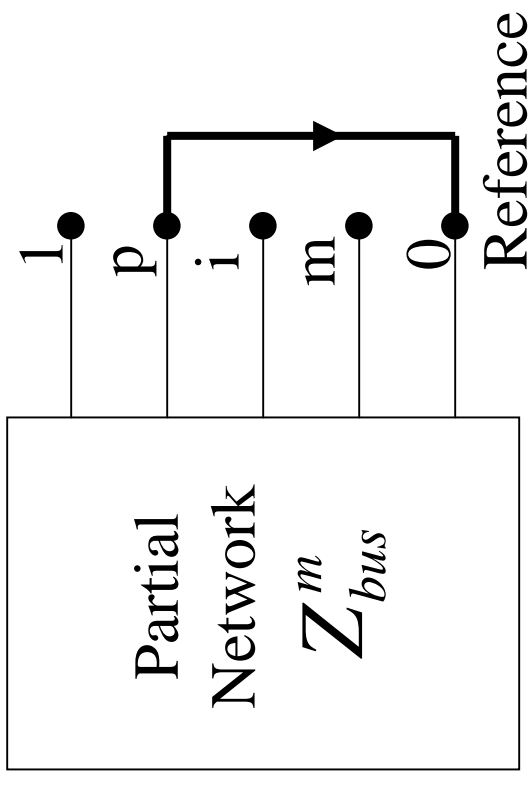

$$Z_{p0} I_l = V_p - 0 \rightarrow$$

$$Z_{p0} I_l - V_p = 0$$

Kron Reduction

Eliminating a node from the system

$$\begin{bmatrix} V_{bus [1 \times n]} \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{bus [n \times n]}^{old} & \Delta Z_{[1 \times n]} \\ \Delta Z_{[n \times 1]}^T & Z_{ll [1 \times 1]} \end{bmatrix} \begin{bmatrix} I_{bus [1 \times n]} \\ I_l \end{bmatrix}$$

$$V_{bus [1 \times n]} = Z_{bus [n \times n]}^{old} I_{bus [1 \times n]} + \Delta Z_{[1 \times n]} I_l$$

$$0 = \Delta Z_{[n \times 1]}^T I_{bus [1 \times n]} + Z_{ll [1 \times 1]} I_l \rightarrow I_l = -\frac{\Delta Z_{[n \times 1]}^T I_{bus [1 \times n]}}{Z_{ll}}$$

$$V_{bus [1 \times n]} = Z_{bus [n \times n]}^{old} I_{bus [1 \times n]} - \frac{\Delta Z_{[1 \times n]} \Delta Z_{[n \times 1]}^T}{Z_{ll}} I_{bus [1 \times n]} = \left[Z_{bus}^{old} - \frac{\Delta Z \Delta Z^T}{Z_{ll}} \right] I_{bus}$$

Power Systems I

Adding a Line between two Lines

$$\begin{bmatrix} V_1 \\ \vdots \\ V_p \\ V_q \\ \vdots \\ V_m \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{11} & \dots & Z_{1p} & Z_{1q} & \dots & Z_{1m} \\ \vdots & \ddots & \vdots & \vdots & \ddots & \vdots \\ Z_{p1} & \dots & Z_{pp} & Z_{pq} & \dots & Z_{pm} \\ Z_{q1} & \dots & Z_{qp} & Z_{qq} & \dots & Z_{qm} \\ \vdots & \ddots & \vdots & \vdots & \ddots & \vdots \\ Z_{m1} & \dots & Z_{mp} & Z_{mq} & \dots & Z_{mm} \end{bmatrix} \begin{bmatrix} Z_{1q} - Z_{1p} \\ \vdots \\ Z_{pq} - Z_{pp} \\ Z_{qq} - Z_{qp} \\ \vdots \\ Z_{mq} - Z_{mp} \\ Z_{ll} \end{bmatrix} \begin{bmatrix} I_1 \\ \vdots \\ I_p \\ I_q \\ \vdots \\ I_m \\ I_l \end{bmatrix}$$

$Z_{ll} = Z_{pq} + Z_{pp} + Z_{qq} - 2Z_{pq}$

Then execute Kron reduction on Z_{ll}

Power Systems I

Adding a Line from a Line to Reference

$$\begin{bmatrix} V_1 \\ \vdots \\ V_p \\ V_i \\ \vdots \\ V_m \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{11} & \cdots & Z_{1p} & Z_{1i} & \cdots & Z_{1m} \\ \vdots & \ddots & \vdots & \vdots & \ddots & \vdots \\ Z_{p1} & \cdots & Z_{pp} & Z_{pi} & \cdots & Z_{pm} \\ Z_{i1} & \cdots & Z_{ip} & Z_{ii} & \cdots & Z_{im} \\ \vdots & \ddots & \vdots & \vdots & \ddots & \vdots \\ Z_{m1} & \cdots & Z_{mp} & Z_{mi} & \cdots & Z_{mm} \\ -Z_{p1} & \cdots & -Z_{pp} & -Z_{pi} & \cdots & -Z_{pm} \end{bmatrix} \begin{bmatrix} I_1 \\ \vdots \\ I_p \\ I_q \\ \vdots \\ I_m \\ I_l \end{bmatrix}$$

$$Z_{ll} = Z_{p0} + Z_{pp}$$

Then execute Kron reduction on Z_{ll}

Power Systems I

Kron Reduction

- Kron reduction removes an axis (row & column) from a matrix while retaining the axis's numerical influence

$$\begin{bmatrix} V_1 \\ \vdots \\ V_p \\ V_i \\ \vdots \\ V_m \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{11} & \cdots & Z_{1p} & Z_{1i} & \cdots & Z_{1l} \\ \vdots & & \vdots & \vdots & & \vdots \\ Z_{p1} & \cdots & Z_{pp} & \textcircled{Z_{pi}} & \cdots & \textcircled{Z_{pl}} \\ Z_{i1} & \cdots & Z_{ip} & Z_{ii} & \cdots & Z_{il} \\ \vdots & & \vdots & \vdots & & \vdots \\ Z_{m1} & \cdots & Z_{mp} & Z_{mi} & \cdots & Z_{ml} \\ Z_{l1} & \cdots & Z_{lp} & \textcircled{Z_{li}} & \cdots & \textcircled{Z_{ll}} \end{bmatrix} \begin{bmatrix} I_1 \\ \vdots \\ I_p \\ I_q \\ \vdots \\ I_m \\ I_l \end{bmatrix}$$

$$Z_{jk}^{new} = Z_{jk}^{old} - \frac{Z_{jl}Z_{lk}}{Z_{ll}}$$

Z-Bus Building Rules

- **Rule 1: Addition of a branch to the reference**
 - ◆ start with existing network matrix $[m \times m]$
 - ◆ create a new network matrix $[(m+1) \times (m+1)]$ with
 - the new off-diagonal row and column filled with (0)
 - the diagonal element $(m+1),(m+1)$ filled with the element impedance Z_{q0}

Z-Bus Building Rules

- **Rule 2: Addition of a branch to an existing bus**
 - ◆ connecting to existing bus p
 - ◆ start with existing network matrix $[m \times m]$
 - ◆ create a new network matrix $[(m+1) \times (m+1)]$ with
 - the new off-diagonal row and column filled with a copy of row p and column p
 - the diagonal element $(m+1),(m+1)$ filled with the element impedance Z_{pq} plus the diagonal impedance Z_{pp}



Z-Bus Building Rules

- **Rule 3: Addition of a linking branch**
 - ◆ connecting to existing buses p and q
 - ◆ start with existing network matrix $[m \times m]$
 - ◆ create a new network matrix $[(m+1) \times (m+1)]$ with
 - the new off-diagonal row and column filled with a copy of row q minus row p and column q minus column p
 - the diagonal element $(m+1),(m+1)$ filled with $Z_{pq} + Z_{pp} + Z_{qq} - 2 Z_{pq}$
 - ◆ perform Kron reduction on the m+1 row and column

Z-Bus Building Rules

- **Rule 4: Addition of a linking branch**
 - ◆ connecting to existing bus p and reference
 - ◆ start with existing network matrix $[m \times m]$
 - ◆ create a new network matrix $[(m+1) \times (m+1)]$ with
 - the new off-diagonal row and column filled with a copy of the negative of row p and the negative of column p
 - the diagonal element $(m+1),(m+1)$ filled with $Z_{p0} + Z_{pp}$
 - ◆ perform Kron reduction on the $m+1$ row and column

Example

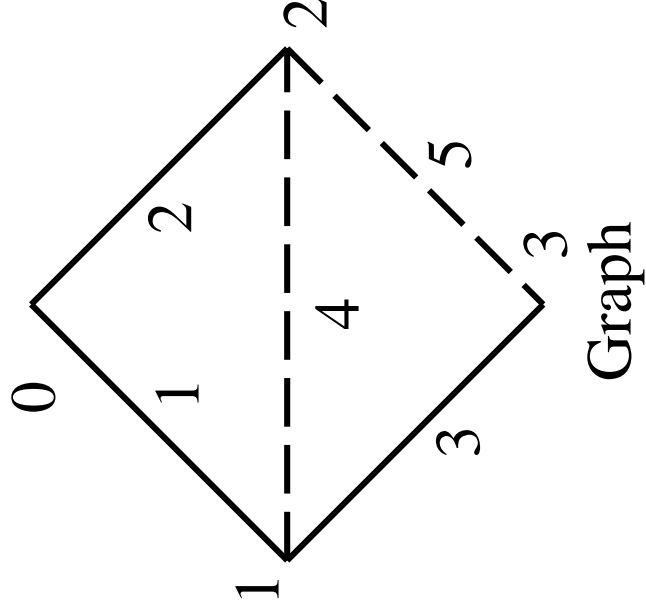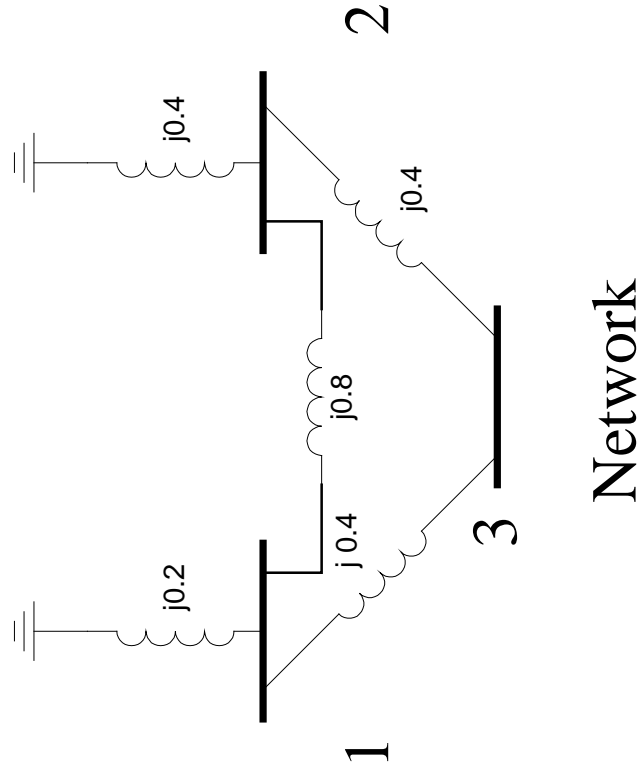

Line adding order: 1-0, 2-0, 1-3, 1-2, then 2-3

Example

0. $[\]$

1. $[j0.2]$

2. $\begin{bmatrix} j0.2 & 0 \\ 0 & j0.4 \end{bmatrix}$

3. $\begin{bmatrix} j0.2 & 0 & j0.2 \\ 0 & j0.4 & 0 \\ j0.2 & 0 & j0.6 \end{bmatrix}$

4.

$$\begin{bmatrix} j0.2 & 0 & j0.2 & j0.2 \\ 0 & j0.4 & 0 & -j0.4 \\ j0.2 & 0 & j0.6 & j0.2 \\ j0.2 & -j0.4 & j0.2 & j1.4 \end{bmatrix}$$

$$Z_{11} = j0.2 - \frac{(j0.2)(j0.2)}{j1.4} = j0.17$$

$$\begin{bmatrix} j0.171 & j0.057 & j0.171 \\ j0.057 & 0.285 & j0.057 \\ j0.171 & j0.057 & j0.571 \end{bmatrix}$$

Example

$$5. \quad \begin{bmatrix} j0.171 & j0.057 & j0.171 & j0.114 \\ j0.057 & j0.285 & j0.057 & -j0.228 \\ j0.171 & j0.057 & j0.571 & j0.514 \\ j0.114 & -j0.228 & j0.514 & j1.14 \end{bmatrix}$$
$$\begin{bmatrix} j0.16 & j0.08 & j0.12 \\ j0.08 & j0.24 & j0.16 \\ j0.12 & j0.16 & j0.34 \end{bmatrix}$$