

Fault Analysis

- **Analysis types**
 - ◆ power flow - evaluate normal operating conditions
 - ◆ fault analysis - evaluate abnormal operating conditions
- **Fault types:**
 - ◆ balanced faults
 - three-phase
 - ◆ unbalanced faults
 - single-line to ground and double-line to ground
 - line-to-line faults
- **Results used for:**
 - ◆ specifying ratings for circuit breakers and fuses
 - ◆ protective relay settings
 - ◆ specifying the impedance of transformers and generators

Power Systems I

Fault Analysis

- **Magnitude of fault currents depend on:**
 - ◆ the impedance of the network
 - ◆ the internal impedances of the generators
 - ◆ the resistance of the fault (arc resistance)
- **Network impedances are governed by**
 - ◆ transmission line impedances
 - ◆ transformer connections and impedances
 - ◆ grounding connections and resistances
- **Generator behavior is divided into three periods**
 - ◆ sub-transient period, lasting for the first few cycles
 - ◆ transient period, covering a relatively longer time
 - ◆ steady state period

Power Systems I

Fault Studies


- **Sub-transient period, $X_G = X_d''$**
 - ◆ determine the interrupting capacity of HV circuit breakers
 - ◆ determine the operation timing of the protective relay system for high-voltage networks
- **Transient period, $X_G = X_d'$**
 - ◆ determine the interrupting capacity of MV circuit breakers
 - ◆ determine the operation timing of the protective relay system for medium-voltage networks
 - ◆ transient stability studies

Fault Representation

- **A fault represents a structural network change**
 - ◆ equivalent to the addition of an impedance at the place of the fault
 - ◆ if the fault impedance is zero, the fault is referred to as a bolted fault or solid fault
- **First order method**
 - ◆ the faulted network can be solved conveniently by Thévenin's method
 - ◆ network resistances are neglected
 - ◆ generators are modeled as an emf behind the sub-transient or transient reactance
 - ◆ shunt capacitances are neglected
 - ◆ system is considered as having no-load

Thévenin's Method

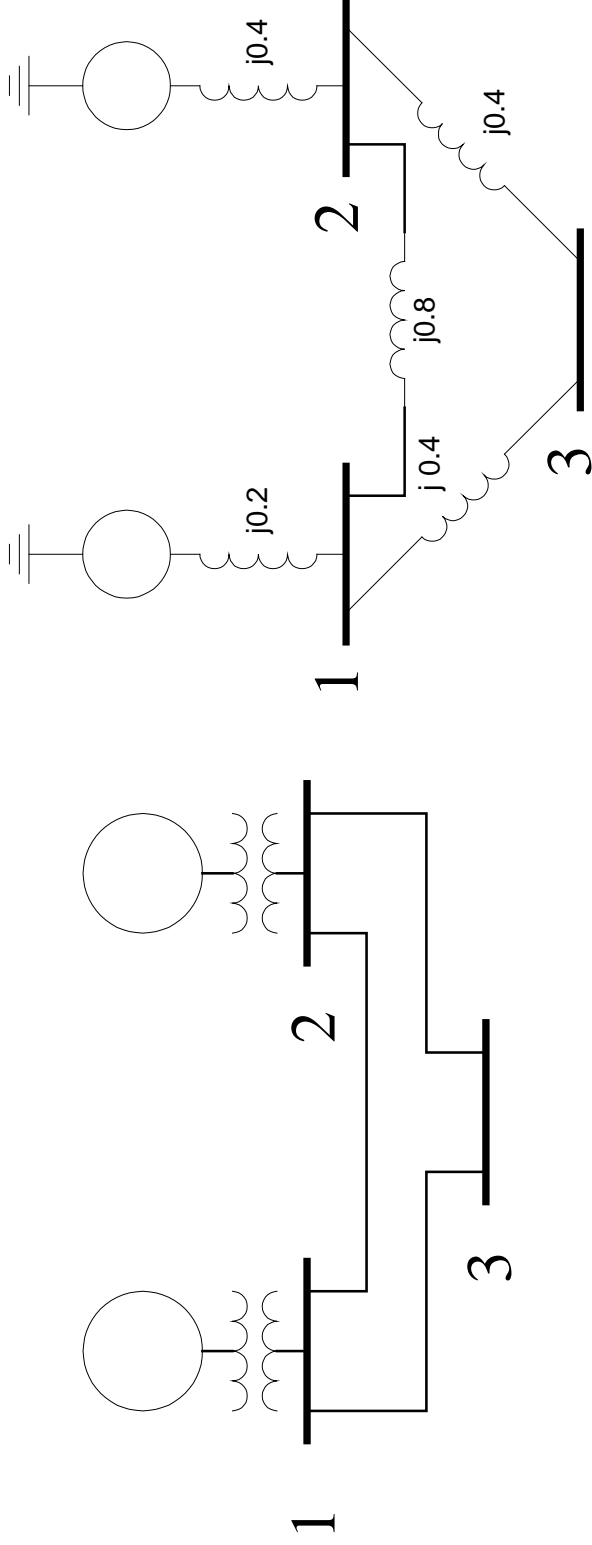
- The fault is simulated by switching a fault impedance at the faulted bus
- The change in the network voltages is equivalent to adding the prefault bus voltage with all other sources short circuited




Power Systems I

Thévenin's Method

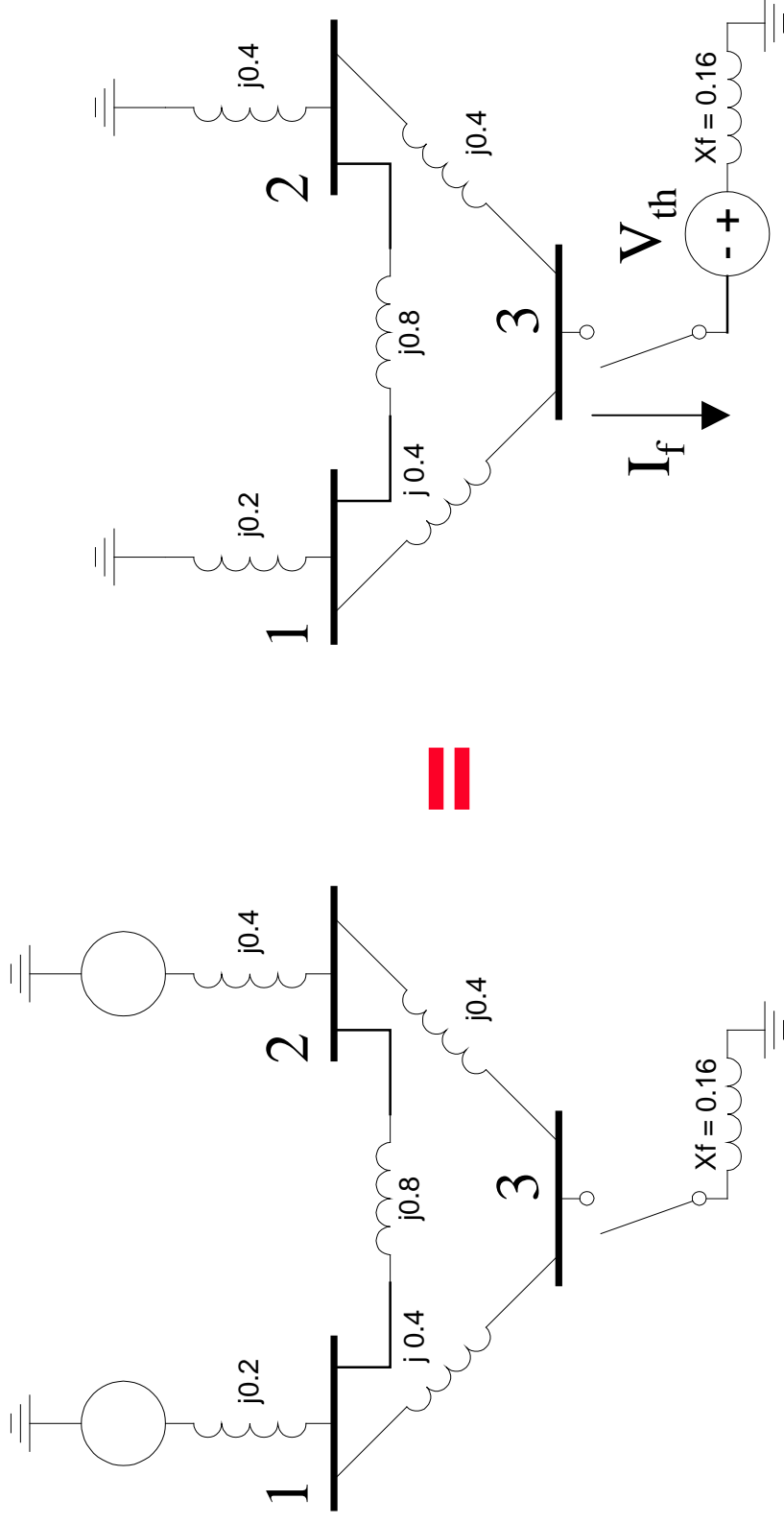- 3-phase fault with $Z_f = j0.16$ on bus 3



Thévenin's Method

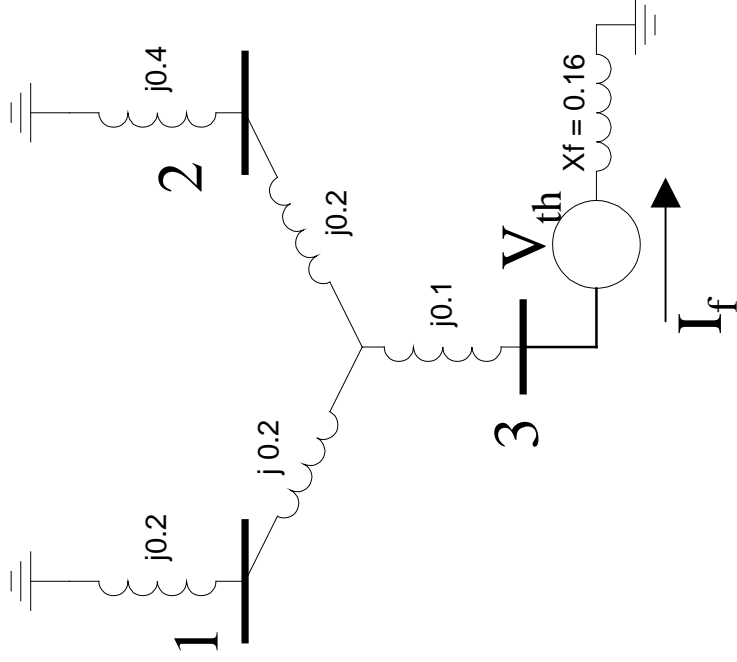

$$I_3^{[f]} = \frac{V_3^{[0]}}{Z_{33} + Z_f}$$


$$V_1^{[0]} = V_2^{[0]} = V_3^{[0]} = 1.0$$

$$Z_{1s} = Z_{2s} = \frac{(j0.4)(j0.8)}{(j1.6)} = j0.2$$


$$Z_{3s} = \frac{(j0.4)(j0.4)}{(j1.6)} = j0.1$$

$$Z_{33} = \frac{(j0.4)(j0.6)}{j0.4 + j0.6} + j0.1$$

$$Z_{33} = j0.34$$

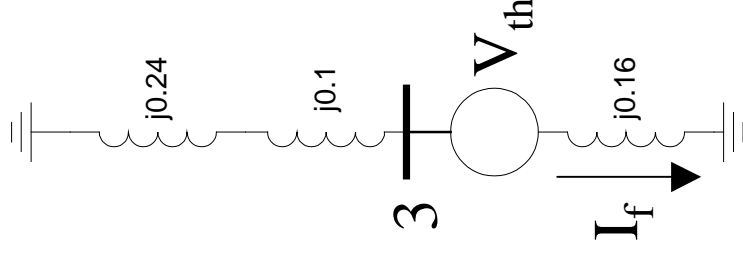

Thévenin's Method

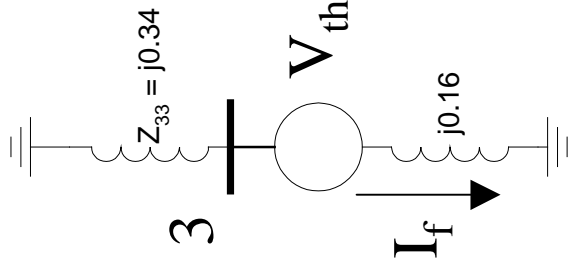

$$Z_{33} = j0.34$$
$$I_3^{[f]} = \frac{V_3^{[0]}}{Z_{33} + Z_f} = \frac{1.0}{j0.34 + j0.16} = -j2.0$$

Thévenin's Method

- **For more accurate solutions**
 - ◆ use the pre-fault bus voltages which can be obtained from the results of a power flow solution
 - ◆ include loads - to preserve linearity, convert loads to constant impedance model
 - ◆ Thevenin's theorem allows the changes in the bus voltages to be obtained
 - ◆ bus voltages are obtained by superposition of the pre-fault voltages and the changes in the bus voltages
 - ◆ current in each branch can be solved

Short Circuit Capacity (SCC)

- Measures the electrical strength of the bus
- Stated in MVA
- Determines the dimension of bus bars and the interrupting capacity of circuit breakers

- **Definition:**

$$SCC = \sqrt{3} V_{L-L,k}^{[pre-f]} I_k^{[f]}$$


- ♦ in per unit:

$$I_k^{[f]} = \frac{V_k^{[pre-f]}}{X_{kk}}$$

$$SCC = \frac{S_B}{X_{kk}}$$

Short Circuit Capacity (SCC)

- Find the SCC for bus #3

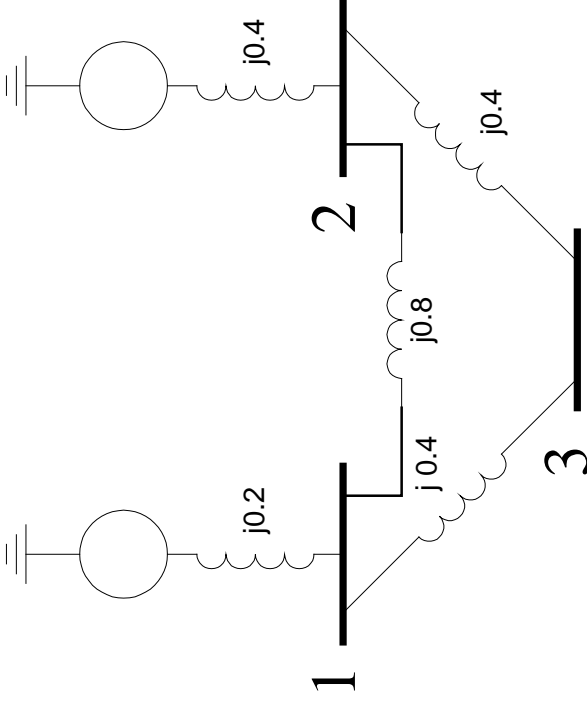


$$Z_{33} = j0.34$$

$$S_{base} = 100 \text{ MVA}$$

$$SCC_3 = \frac{S_{base}}{|Z_{33}|} = \frac{100 \text{ MVA}}{0.34} = 294 \text{ MVA}$$

Fault Analysis Using Impedance Matrix

- **Network reduction by Thévenin's method is not efficient**
 - ◆ difficult to apply to large networks
- **Matrix algebra formation**
 - ◆ seek a matrix where the diagonal elements represent the source impedance for the buses
 - ◆ consider the following system
 - operating under balanced conditions
 - each generator represented by a constant emf behind a proper reactance (X_d , X'_d , or X''_d)
 - lines represented by their equivalent π model

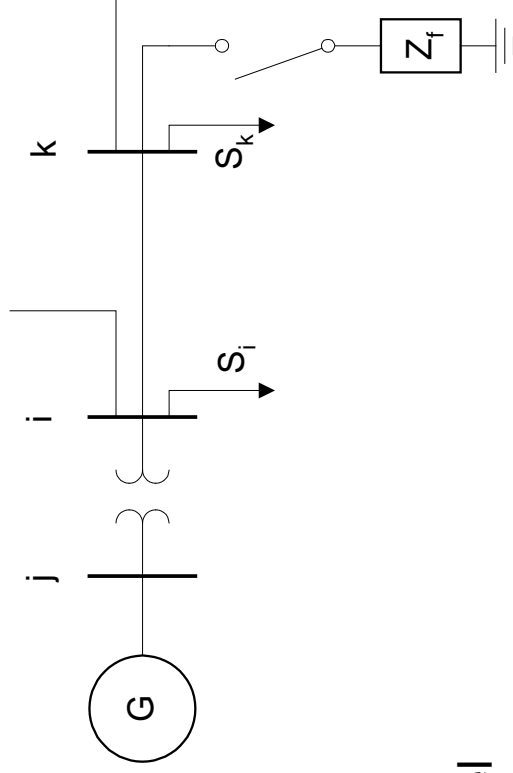

Power Systems I

Fault Analysis Using Impedance Matrix


- Place the prefault voltages into a vector

$$\mathbf{V}_{bus}^{[pre-f]} = \begin{bmatrix} V_1^{[pre-f]} \\ \vdots \\ V_k^{[pre-f]} \\ \vdots \\ V_n^{[pre-f]} \end{bmatrix}$$

- Replace the loads by a constant impedance model using the prefault bus voltages

$$Z_{i-load} = \frac{|V_i^{[pre-f]}|^2}{S_{i-load}^*}$$

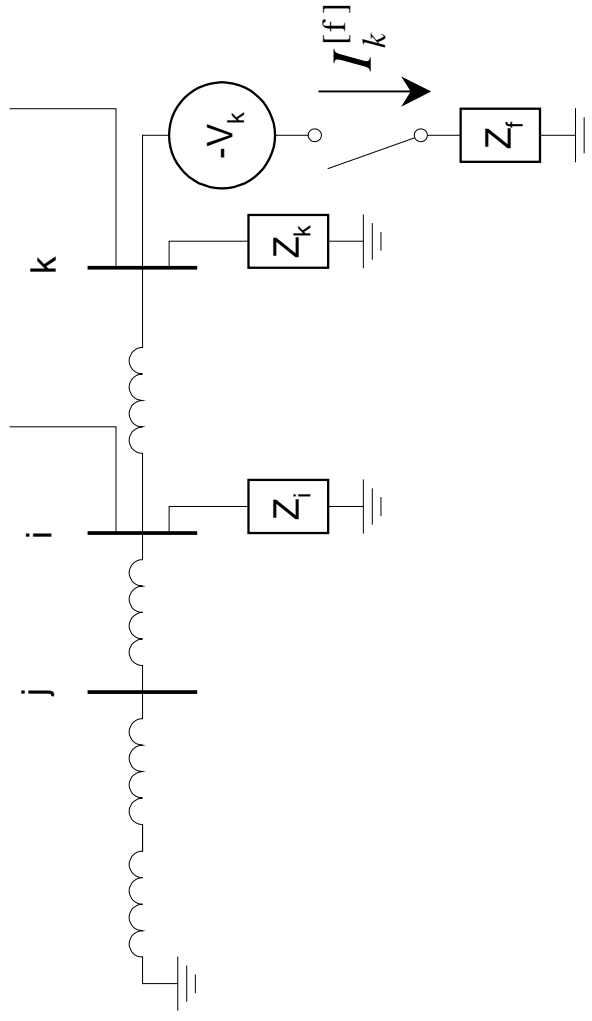- The change in the network voltage caused by the fault is equivalent to placing a fault voltage at the faulted bus with all the other sources short-circuited



Fault Analysis Using Impedance Matrix

- Using superpositioning, the fault voltages are calculated from the prefault voltages by adding the change in bus voltages due to the fault

$$\mathbf{V}_{bus}^{[f]} = \mathbf{V}_{bus}^{[pre-f]} + \Delta \mathbf{V}_{bus} = \begin{bmatrix} \Delta V_1 \\ \vdots \\ \Delta V_k \\ \vdots \\ \Delta V_n \end{bmatrix}$$

- The change in bus voltages can be calculated from the network matrix

$$\begin{aligned} \mathbf{I}_{bus} &= \mathbf{Y}_{bus} \mathbf{V}_{bus} \\ \mathbf{I}_{bus}^{[Fault]} &= \mathbf{Y}_{bus} \Delta \mathbf{V}_{bus} \\ \mathbf{I}_{bus}^{[Fault]} &= \begin{bmatrix} 0 \\ \vdots \\ -I_k^{[Fault]} \\ \vdots \\ 0 \end{bmatrix} \end{aligned}$$

Fault Analysis Using Impedance Matrix

$$\mathbf{I}_{bus}^{[Fault]} = \mathbf{Y}_{bus} \Delta \mathbf{V}_{bus}$$

$$\begin{bmatrix} 0 \\ \vdots \\ -I_k^{[f]} \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} y_{11} & \cdots & y_{1k} & \cdots & y_{1n} \\ \vdots & \ddots & \vdots & \ddots & \vdots \\ y_{k1} & \cdots & y_{kk} & \cdots & y_{kn} \\ \vdots & \ddots & \vdots & \ddots & \vdots \\ y_{n1} & \cdots & y_{nk} & \cdots & y_{nn} \end{bmatrix} \begin{bmatrix} \Delta V_1 \\ \vdots \\ \Delta V_k \\ \vdots \\ \Delta V_n \end{bmatrix}$$

$$\Delta \mathbf{V}_{bus} = \mathbf{Y}_{bus}^{-1} \mathbf{I}_{bus}^{[Fault]}$$

$$\mathbf{Z}_{bus} = \mathbf{Y}_{bus}^{-1}$$

$$\Delta \mathbf{V}_{bus} = \mathbf{Z}_{bus} \mathbf{I}_{bus}^{[Fault]}$$

Power Systems I

Fault Analysis Using Impedance Matrix

$$\begin{bmatrix} \Delta V_1 \\ \vdots \\ \Delta V_k \\ \vdots \\ \Delta V_n \end{bmatrix} = \begin{bmatrix} Z_{11} & \cdots & Z_{1k} & \cdots & Z_{1n} \\ \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{k1} & \cdots & Z_{kk} & \cdots & Z_{kn} \\ \vdots & \ddots & \vdots & \ddots & \vdots \\ Z_{n1} & \cdots & Z_{nk} & \cdots & Z_{nn} \end{bmatrix} \begin{bmatrix} 0 \\ \vdots \\ -I_k^{[f]} \\ \vdots \\ 0 \end{bmatrix}$$

$$\mathbf{V}_{bus}^{[f]} = \mathbf{V}_{bus}^{[pre-f]} + \Delta \mathbf{V}_{bus}$$

$$\mathbf{V}_{bus}^{[f]} = \mathbf{V}_{bus}^{[pre-f]} + \mathbf{Z}_{bus} \mathbf{I}_{bus}^{[f]}$$

$$V_k^{[f]} = V_k^{[pre-f]} + Z_{kk} I_k^{[f]} \quad \& \quad V_k^{[f]} = Z_f I_k^{[f]}$$


$$I_k^{[f]} = \frac{V_k^{[pre-f]}}{Z_{kk} + Z_f}$$

Power Systems I

Example

- 3-phase fault with $Z_f = j0.16$ on

♦ bus 3

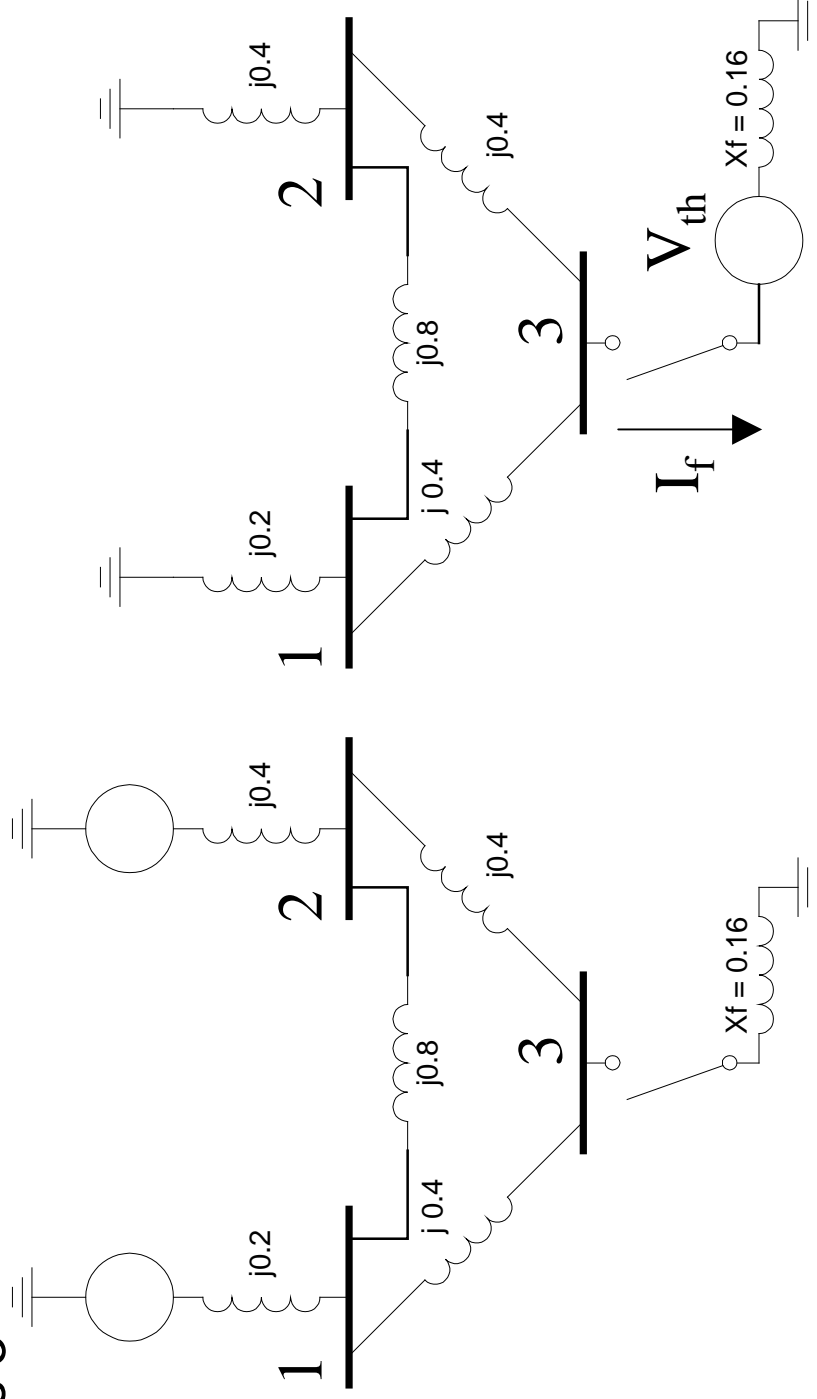

Power Systems I

Example

$$Y_{bus} = \begin{bmatrix} -j8.75 & j1.25 & j2.50 \\ j1.25 & -j6.25 & j2.50 \\ j2.50 & j2.50 & -j5.00 \end{bmatrix}$$

$$Z_{bus} = \begin{bmatrix} j0.16 & j0.08 & j0.12 \\ j0.08 & j0.24 & j0.16 \\ j0.12 & j0.16 & j0.34 \end{bmatrix}$$

$$I_3^{[f]} = \frac{V_3^{[pre-f]}}{Z_{33} + Z_f} = \frac{1.0 pu}{j0.34 + j0.16} = -j2.0 pu$$

Example

$$V_1^{[f]} = V_1^{[pre-f]} - Z_{13} I_3^{[f]} = 1.0 pu - (j0.12)(-j2.0) = 0.76 pu$$

$$V_2^{[f]} = V_2^{[pre-f]} - Z_{23} I_3^{[f]} = 1.0 pu - (j0.16)(-j2.0) = 0.68 pu$$

$$V_3^{[f]} = V_3^{[pre-f]} - Z_{33} I_3^{[f]} = 1.0 pu - (j0.34)(-j2.0) = 0.32 pu$$