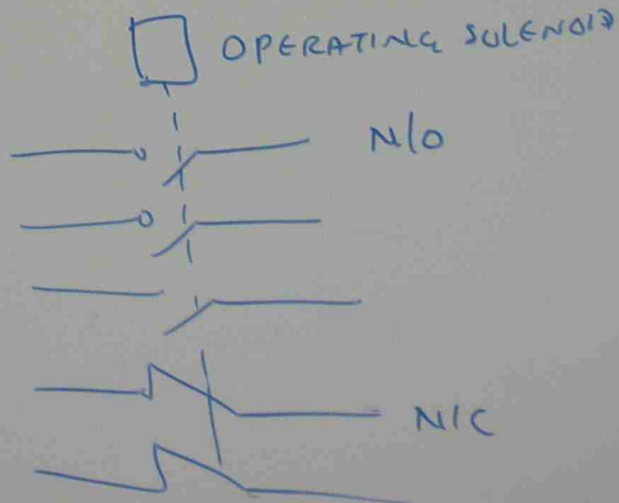


CURRENT & VOLTAGE  
 TORQUE & (VOLTAGE)<sup>2</sup>


CONTACTORS



$$\text{LOCKED ROTOR CURRENT} = \frac{1}{0.5} \times \text{MEASURED CURRENT}$$

$$\text{LOCKED ROTOR TORQUE} = \frac{1}{(0.5)^2} \times \text{MEASURED TORQUE}$$


(i) STAND STILL

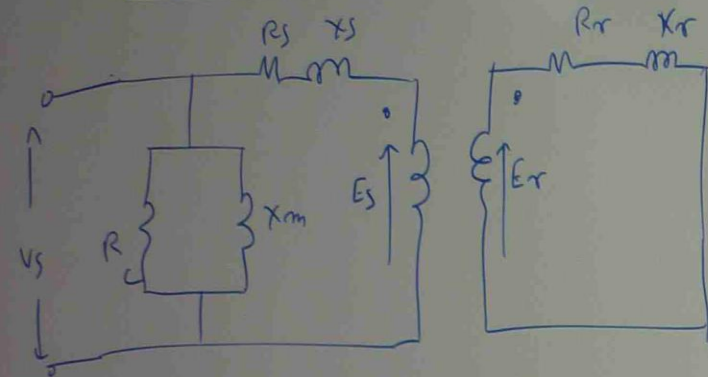

$$I_r = \frac{\textcircled{S} E_r}{R_r + j \textcircled{S} X_r} = \frac{E_r}{\frac{R_r}{\textcircled{S}} + j X_r} = \frac{E_m}{(R_r + j X_r) + R_r \left( \frac{1-\textcircled{S}}{\textcircled{S}} \right)}$$

$I_r$  = ROTOR WINDING CURRENT

(ii) ANY SLIP

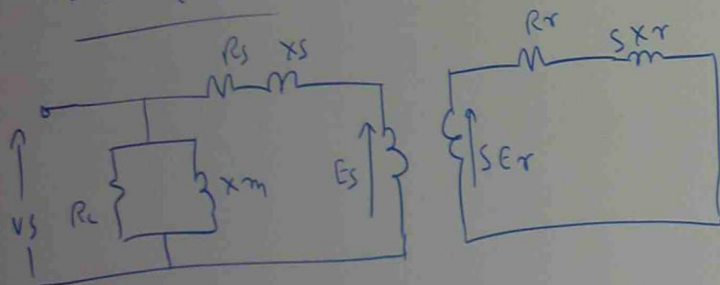

ANY SLIP

$\textcircled{S}$  = SLIP

$E_s$  = STATOR VOLTAGE

$E_r$  = ROTOR VOLTAGE

$R_c$  = CORE RESISTANCE


$X_m$  = CORE INDUCTIVE REACTANCE

$R_r$  = ROTOR WINDING RESISTANCE


$X_r$  = ROTOR WINDING INDUCTIVE REACTANCE

$R_s$  = STATOR WINDING RESISTANCE

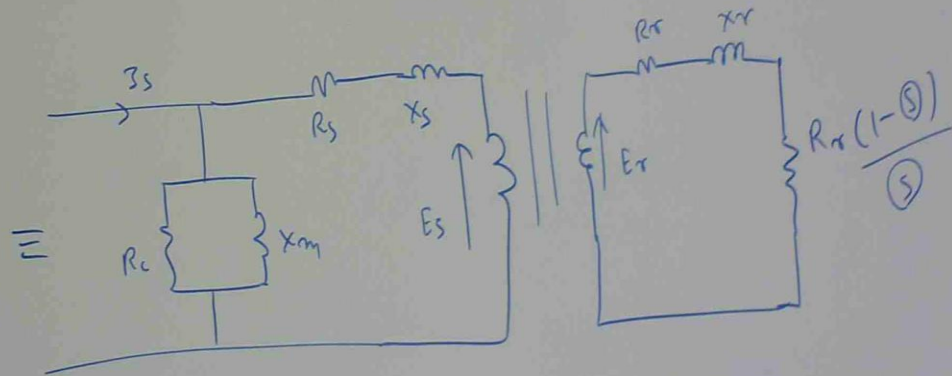$X_s$  = STATOR WINDING INDUCTIVE REACTANCE



### OVER ALL EQUIVALENT CIRCUIT

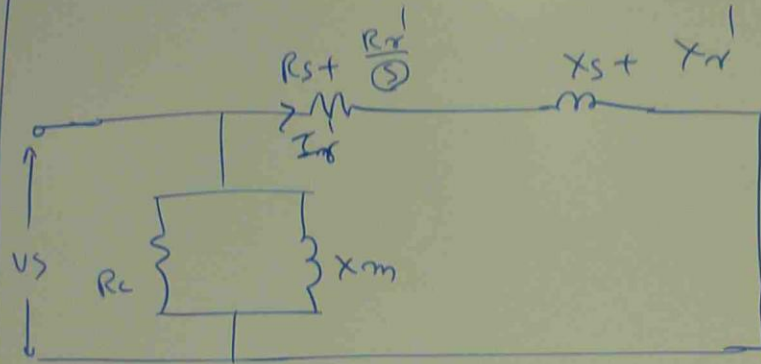

$$\frac{R_r'}{5} = (\text{TURN RATIO})^2 \times \frac{R_r}{5}$$

$$X_r' = (\text{TURN RATIO})^2 \times X_r$$

$$\text{TURN RATIO} = \frac{\text{STATOR TURNS / PHASE}}{\text{ROTOR TURNS / PHASE}}$$

$$I_r' = \frac{V_s}{\sqrt{\left(R_s + \frac{R_r'}{5}\right)^2 + (X_s + X_r')^2}}$$

E+ (20)

A 440V 4 POLE 3 $\phi$  50 HZ SLIP RING INDUCTION MOTOR HAS IT'S WINDING MESH ( $\Delta$ ) CONNECTED AND IT'S ROTOR WINDING STAR CONNECTED.

THE STANDSTILL VOLTAGE MEASURED BETWEEN SLIP RINGS WITH THE ROTOR OPEN CIRCUIT IS 216V. THE STATOR RESISTANCE / PHASE

IS 0.6 $\Omega$  AND THE STATOR REACTANCE / PHASE


IS 3 $\Omega$ . THE ROTOR RESISTANCE / PHASE IS 0.05 $\Omega$  AND ROTOR REACTANCE / PHASE IS

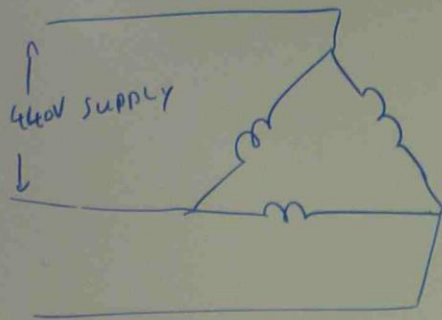0.25 $\Omega$ . CALCULATE THE ROTOR CURRENT AND STATOR CURRENT WHEN SLIP RINGS


ARE SHORT CIRCUITED TO START THE MOTOR.

CALCULATE ROTOR POWER FACTOR AND STATOR POWER FACTOR.





STATOR

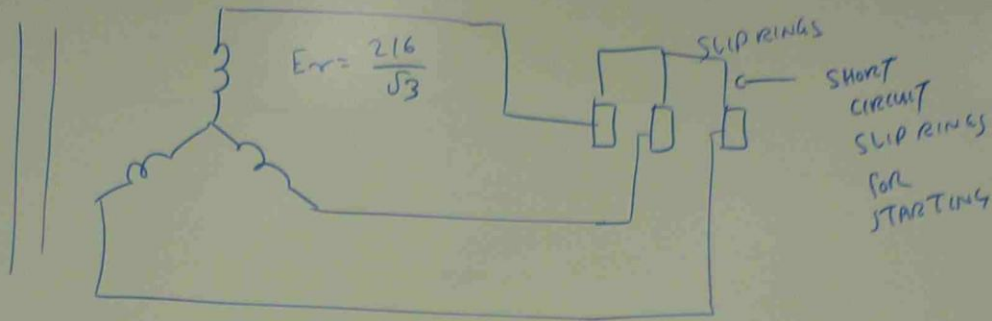

$$\text{TURN RATIO } K_s = \frac{E_s / \text{ph}}{E_r / \text{ph}} = \frac{440}{216 / \sqrt{3}} = \frac{440}{126} = 3.49$$

$$\text{ROTOR CURRENT } I_r = \frac{E_r / \text{ph}}{R_r + j X_r} = \frac{E_r / \text{ph}}{\frac{R_r}{\text{③}} + j X_r} = \frac{E_r / \text{ph}}{\sqrt{\left(\frac{R_r}{\text{③}}\right)^2 + X_r^2}} = \frac{126}{\sqrt{\left(\frac{0.05}{1}\right)^2 + (0.25)^2}} = 504 \text{ Amp}$$

$$\text{STATOR CURRENT } I_s = \frac{1}{\sqrt{\left(R_s + \frac{R_r'}{\text{③}}\right)^2 + \left(X_s + X_r'\right)^2}} = \frac{440}{\sqrt{(0.6 + 0.609)^2 + (3 + 3.045)^2}}$$

$$R_s = 0.6 \Omega$$

$$X_s = 3 \Omega$$

$$\frac{R_r'}{\text{③}} = K_s^2 \times \frac{R_r}{\text{③}} = 3.49^2 \times \frac{0.05}{1} = 0.609 \Omega$$

$$X_r' = K_s^2 \times X_r = 3.49^2 \times 0.25 = 3.045$$

$$= 71.42 \text{ Amp}$$

$$\text{STATOR P.F} = \cos \left( \tan^{-1} \frac{X_s + X_r}{R_s + \frac{R_r}{s}} \right)$$


$$= \cos \left( \tan^{-1} \frac{3 + 3.045}{0.6 + 0.69} \right)$$

$$= \cos \tan^{-1} 5$$

$$= \cos 78.6 = 0.196 \text{ LAGGING}$$

Ex (2)

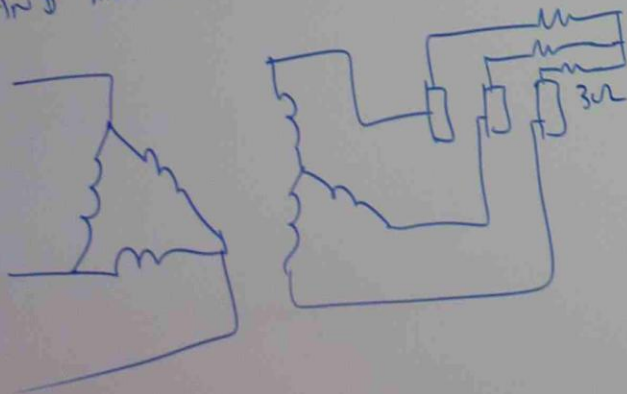IN ABOVE PROBLEM, CALCULATE ROTOR CURRENT AND STATOR CURRENT WHEN SLIP RINGS ARE CONNECTED TO  $3\Omega$  EXTERNAL RESISTANCE AND MOTOR IS RUNNING AT 0.03 SLIP



ROTOR CURRENT

$$I_r = \frac{E_r}{\sqrt{\left(\frac{R_r}{s} + R_{ext}\right)^2 + (X_r)^2}}$$

$$= \frac{126}{\sqrt{\left(\frac{0.05}{0.3} + 3\right)^2 + (0.25)^2}}$$

$$= 39.6 \text{ Amp}$$

$$\text{ROTOR P.F} = \cos \tan^{-1} \frac{X_r}{\frac{R_r}{s} + R_{ext}}$$

$$= \cos \tan^{-1} \frac{0.25}{3.166} = 0.996 \text{ LAGGING}$$

$$\text{STATOR PF} = \cos \tan^{-1} \frac{X_s + X_r}{R_s + K_s^2 \left(\frac{R_r}{s} + R_{ext}\right)}$$

$$= \cos \tan^{-1} \frac{3.045 + 3}{0.6 + 3.49^2 \left(\frac{0.05}{0.3} + 3\right)}$$

$$= \cos \tan^{-1} 0.154$$

$$= \cos 8.77$$

$$= 0.988 \text{ LAGGING}$$


$$\text{STATOR CURRENT} = I_s = \frac{V_s / \text{ph}}{\sqrt{R_s + K_s^2 \left(\frac{R_r}{s} + R_{ext}\right)^2 + (X_s + X_r)^2}}$$

$$I_s = \frac{440}{\sqrt{\left(0.6 + 3.49^2 \left(\frac{0.05}{0.3} + 3\right)\right)^2 + (3 + 3.49^2 \times 0.25)^2}}$$


$$= 11.11 \text{ Amp}$$

# POWER TRANSFER IN INDUCTION MACHINE



## MOTOR MODE

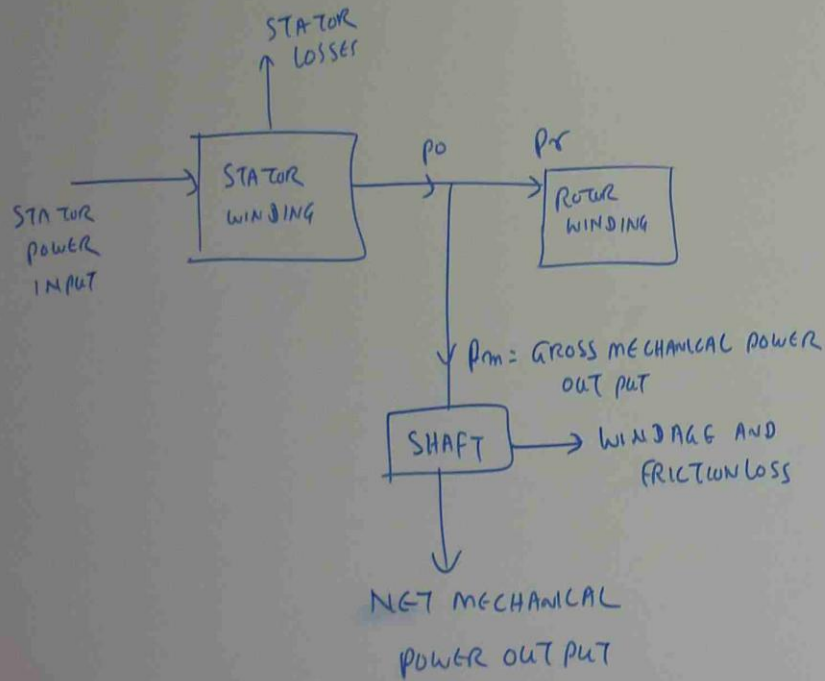

## GENERATOR MODE

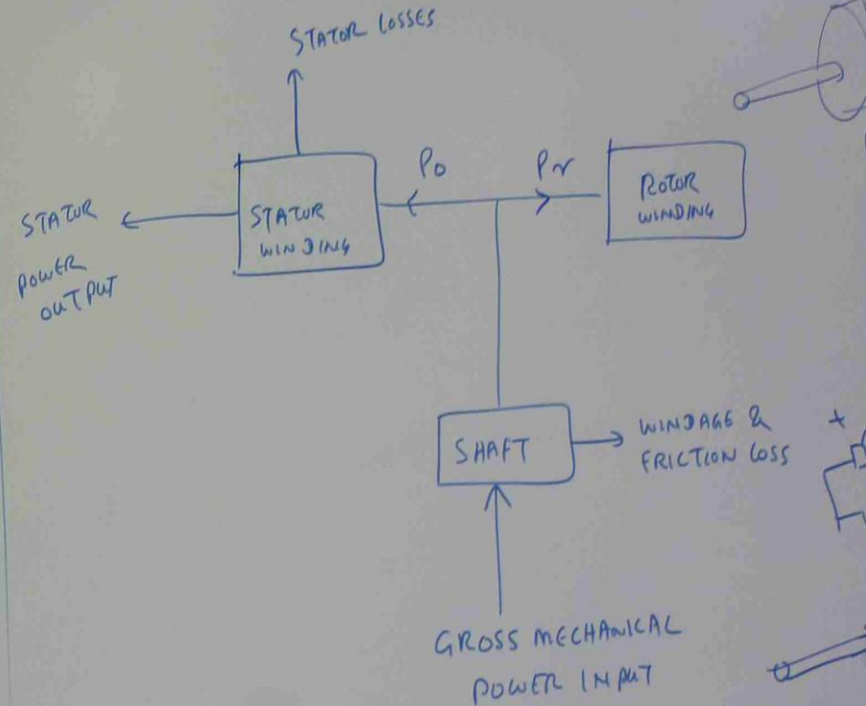



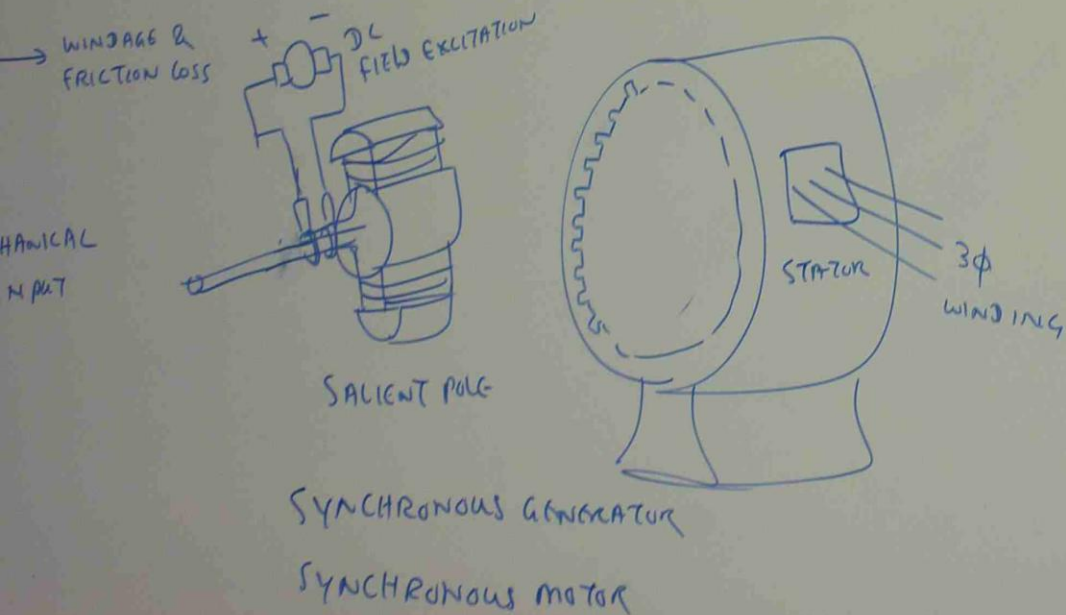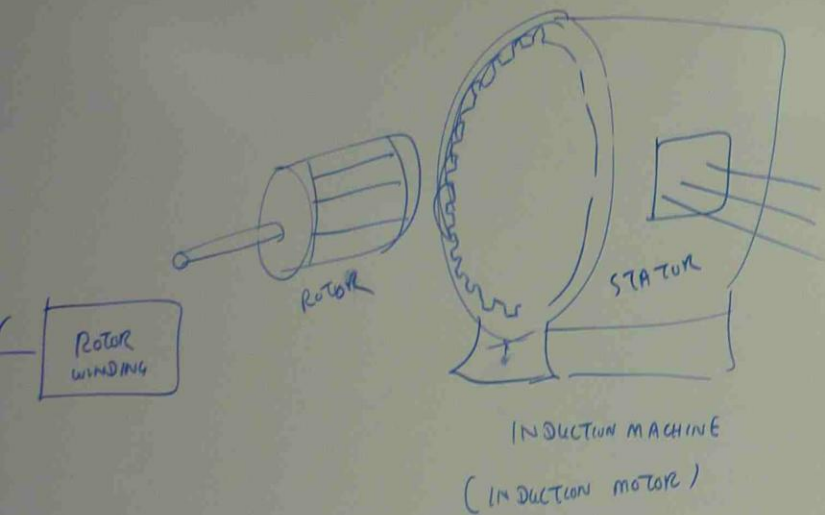

FOR MOTOR CASE (3φ)

POWER ABSORBED BY IDEAL STATOR WINDING  $P_o = 3 E_s I_r \cos \phi_r$

POWER DISSIPATED IN THE ROTOR CIRCUIT  $= 3 \textcircled{S} E_r I_r \cos \phi_r$   
(OR)  
 $3 \textcircled{S} E_s I_r \cos \phi_r$

MECHANICAL POWER ( $P_m$ )  $= P_o - P_r$   
 $= P_o - \textcircled{S} P_o$   
 $P_m = P_o (1 - \textcircled{S})$

POWER DISSIPATED IN ROTOR RESISTANCE  $= 3 I_r^2 R_r \left( \frac{1 - \textcircled{S}}{\textcircled{S}} \right)$

ROTOR CIRCUIT POWER LOSS  $= 3 \left( I_r \right)^2 R_r$

POWER ABSORBED BY IDEAL STATOR WINDING  $= 3 \left( I_r \right)^2 \frac{R_r}{\textcircled{S}}$

$$\text{GROSS MECHANICAL POWER OUTPUT} = P_m = 3 (I_r')^2 R_r \frac{(1-s)}{s}$$

$$\text{GROSS TORQUE DEVELOPED } T = \frac{3}{2\pi n_r} (I_r')^2 R_r \frac{(1-s)}{s}$$

$$n_o = \frac{f}{p/2}$$

$$n_r = \text{ROTOR SPEED (RPM)} = (1-s) \text{ Rotor speed AT NO LOAD}$$

$$n_r = (1-s) n_s$$

$$s = \text{SLIP}$$

$$\text{ANY TORQUE} \rightarrow T = \frac{3 V_s^2}{4\pi n_o} \frac{s R_r'}{[(s R_s + R_r')^2 + s^2 (X_s + X_r')^2]}$$

$$\text{MAXIMUM TORQUE} \rightarrow T_{\max} = \frac{3 V_s^2}{4\pi n_o} \times \frac{s}{(s R_s + R_r')}$$


SLIP AT maximum  
TORQUE

$$s_m = \frac{R_r'}{\sqrt{R_s^2 + (X_s + X_r')^2}}$$



Ex 22

A 440V 4poles 3 $\phi$  50Hz slip ring induction motor has its stator winding delta connected and rotor winding star connected. The stand still voltage measured between slip rings with the rotor open circuited is 218V. The stator resistance per phase is 0.6 $\Omega$  and the stator reactance per phase is 3 $\Omega$ . The rotor resistance per phase is 0.05 $\Omega$  and the rotor reactance per phase is 0.25 $\Omega$ . Calculate the maximum torque and the slip at which it occurs.

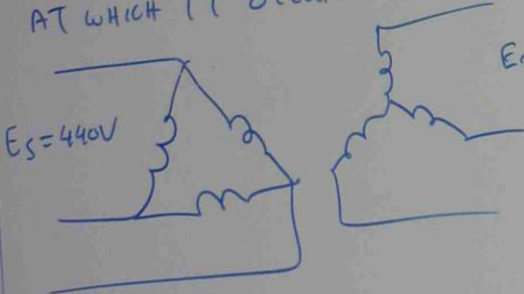

$$E_r(\text{ph}) = \frac{218}{\sqrt{3}} = 126\text{V}$$

$$k_t = \frac{E_s(\text{ph})}{E_r(\text{ph})} = \frac{440}{126} = 3.49$$

$$R_r' = k_t^2 \times R_r = 3.49^2 \times 0.05 = 0.61\Omega$$

$$X_r' = k_t^2 \times X_r = 3.49^2 \times 0.25 = 3.05\Omega$$

$$s_m = \frac{R_r'}{\sqrt{R_s^2 + (X_s + X_r')^2}} = \frac{0.61}{\sqrt{0.6^2 + (3 + 3.05)^2}} = 0.1$$

$$m_0 = \frac{f}{P/2} = \frac{50}{4/2} = \frac{50}{2} = 25$$

$$T_{\text{max}} = \frac{3 V_s^2}{4 \pi m_0} \frac{R_r'}{\sqrt{(\sum R_s) + R_r'}^2 + (\sum X_s + X_r')^2}$$

$$= \frac{3 \times 440^2 \times 1 \times 0.61}{4 \times 3.1416 \times 25 \sqrt{(1 \times 0.6 + 0.61)^2 + 1^2 (3 + 3.05)^2}}$$

$$= 277 \text{ N-m}$$