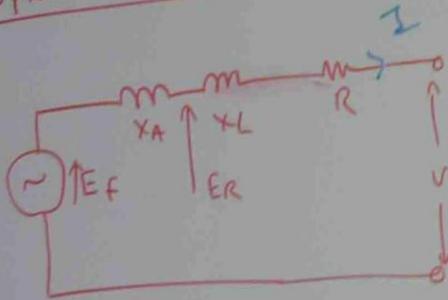


EQUIVALENT CIRCUIT AND VECTOR DIAGRAM OF SYNCHRONOUS MACHINE

TEST (1) Q

- Plot (i) VECTOR DIAGRAM FOR SYNCHRONOUS GENERATOR
 (ii) VECTOR DIAGRAM FOR SYNCHRONOUS MOTOR

SYNCHRONOUS GENERATOR



X_A = SERIES CONNECTED REACTANCE OF VOLTAGE WINDING

X_L = LEAKAGE REACTANCE OF VOLTAGE WINDING

R = RESISTANCE OF VOLTAGE WINDING

V = TERMINAL VOLTAGE

E_f = GENERATED VOLTAGE

$$E_f = V + I Z_s$$

$$E_f = V + I (R + j(X_L + X_A))$$

$$Z_s = R + j(X_L + X_A)$$

$$= \sqrt{R^2 + (X_L + X_A)^2}$$

SYNCHRONOUS IMPEDANCE (Ω)

$$E_f = 4.44 \phi f T_p K_p K_d$$

T_p = TURNS / PHASE

ϕ = FLUX / (wb) / POLE


f = FREQUENCY

K_p = PITCH FACTOR
 K_d = DISTRIBUTION FACTOR
 } WINDING CONSTANT


$$N_s = \frac{120 f}{P}$$

P = NO. OF POLES

N_s = SYNCHRONOUS SPEED (RPM)

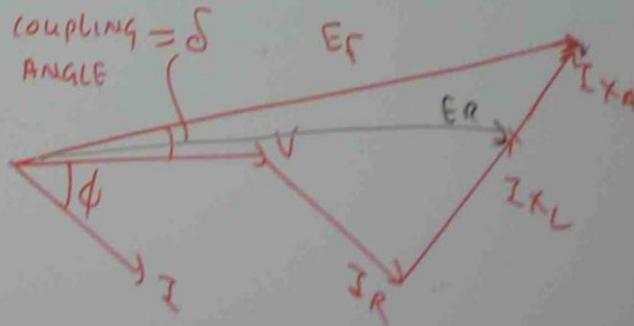

SYNCHRONOUS MOTOR

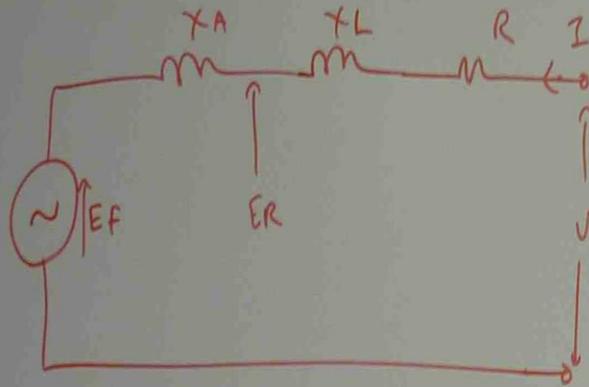

$E_f =$ BACK EMF
(OR)
EXCITATION
EMF

$$E_f = V - I Z_s$$

(OR)

$$V = E_f + I Z_s$$

$$V = E_f + I (R + j(X_L + X_A))$$

