
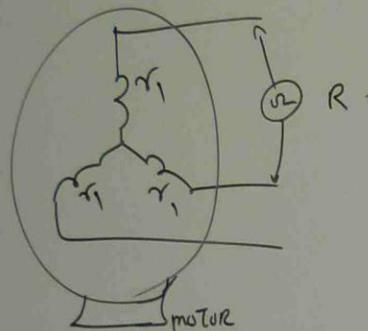


TESTS TO DETERMINE THE EQUIVALENT
CIRCUIT OF 3 ϕ MOTOR

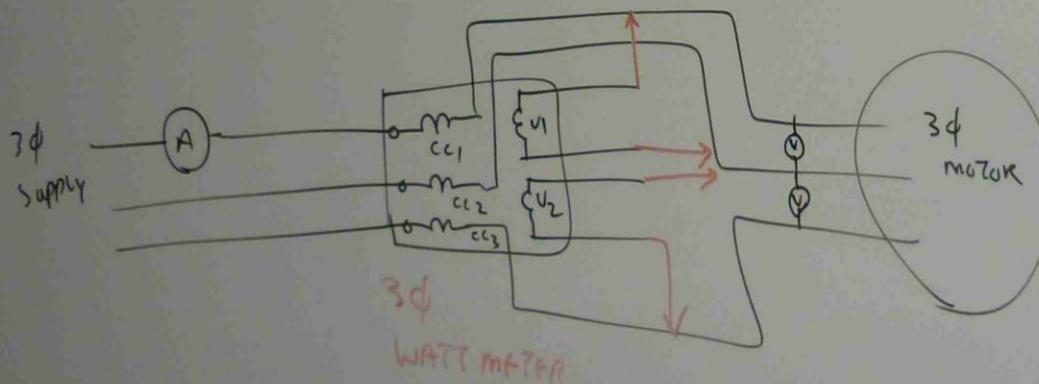No load test → To determine magnetizing reactance
and core resistance




$$r_1 = \frac{R}{2}$$



RUN THE MOTOR AT NO LOAD

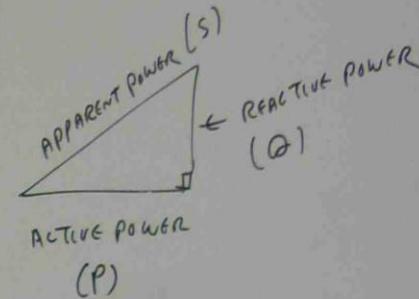- MEASURE RATED LINE TO LINE VOLTAGE (E_{NL})
- MEASURE NO LOAD CURRENT (I_{NL})
- MEASURE TOTAL 3 ϕ POWER (P_{NL})



$$\text{APPARENT POWER AT NO LOAD} = S_{NL}$$

$$\text{ACTIVE POWER AT NO LOAD} = P_{NL}$$

$$\text{REACTIVE POWER AT NO LOAD} = Q_{NL}$$

$$3\phi \text{ WATT METER READING} = P_{NL}$$

DETERMINATION

R_m

$R_m =$

$X_m =$

R

AT NO LOAD

TOTAL LINE TO LINE VOLTAGE (E_{NL})

LOAD CURRENT (I_{NL})


TOTAL 3 ϕ POWER (P_{NL})

- REACTIVE POWER
(Q)

$$S_{NL} = \sqrt{3} E_{NL} I_{NL}$$

$$\Omega_{NL} = \sqrt{S_{NL}^2 - P_{NL}^2}$$

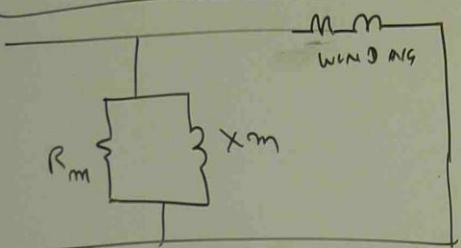DETERMINATION OF CORE RESISTANCE &
REACTANCE



$$= S_{NL}$$

$$= P_{NL}$$

$$= \Omega_{NL}$$

$$= P_{NL}$$

$$R_m = \frac{E_{NL}^2}{WINDAGE + FRICTION + IRONLOSS}$$

AT NO LOAD

TOTAL NO LOAD
ACTIVE POWER (P_{NL}) =

COPPER
LOSS IN
WINDING
+ (WINDAGE
+ FRICTION +
IRON LOSS)


$$\text{WINDAGE + FRICTION + IRON LOSS} = P_{NL} - \text{COPPER LOSS
IN
WINDING}$$

$$= P_{NL} - 3 I_{NL}^2 r$$

$$X_m = \frac{E_{NL}^2}{\Omega_{NL}}$$

DETERMINATION OF WINDING RESISTANCE AND
REACTANCE

LOCKED ROTOR TEST

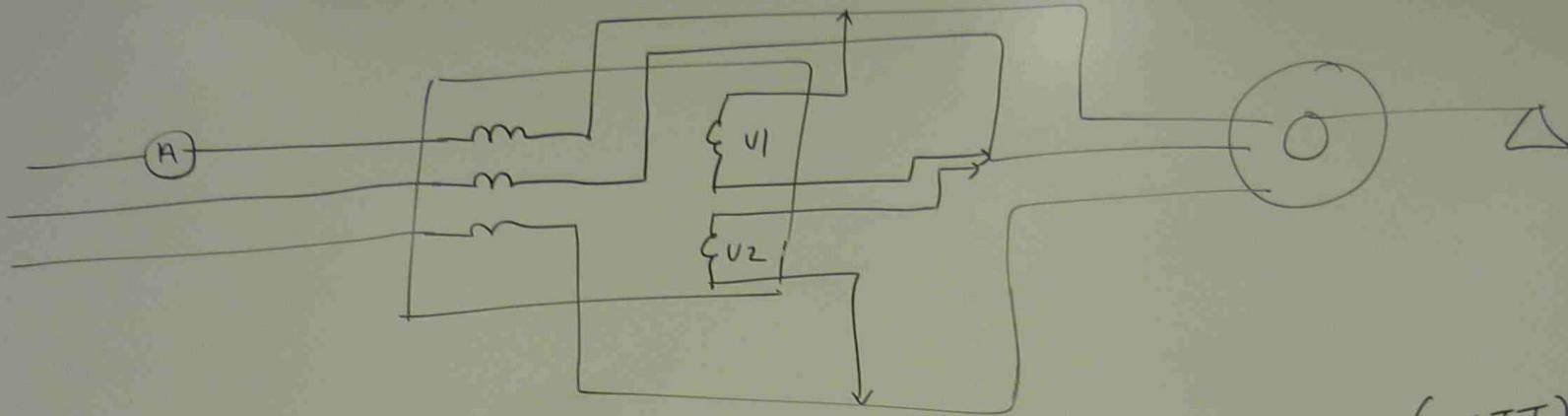

3ϕ WATT METER READING = P_{LF} (Locked rotor active (WATT) power)

E_{LF} = locked rotor voltage

I_{LF} = locked rotor current

$$S_{LF} = \text{locked rotor apparent power} = \sqrt{3} E_{LF} I_{LF}$$

Q_{LF} = locked rotor reactive power (VAR)

$$Q_{LF} = \sqrt{S_{LF}^2 - P_{LF}^2}$$

$$X = \frac{Q_{LF}}{\sqrt{3} I_{LF}^2}$$

WINDING
REACTANCE

$$r_2 = \frac{P_{LF}}{\sqrt{3} I_{LF}^2} - r$$

WINDING
RESISTANCE

Pb A NO LOAD TEST CONDUCTED ON A 30 HP, 835 RPM 440V 3Φ 60Hz SQUIRREL CAGE INDUCTION MOTOR YIELD THE FOLLOWING RESULTS.

NL NO LOAD VOLTAGE (LINE TO LINE) = 440V

NO LOAD CURRENT = 14 A

NO LOAD POWER = 1470 W

RESISTANCE MEASURED BETWEEN TWO TERMINALS = 0.5Ω

LF THE LOCKED ROTOR TEST CONDUCTED AT REACTANCE VOLTAGE GAVE THE FOLLOWING RESULTS.

LOCKED ROTOR VOLTAGE (L-L) = 163V

LOCKED ROTOR POWER = 7200W

LOCKED ROTOR CURRENT = 60 A

DETERMINING THE EQUIVALENT CIRCUIT OF THE MOTOR

NO LOAD TEST

$$r_1 = \frac{R}{2} = \frac{0.5}{2} = 0.25\Omega$$

$E_{NL} = 440V$, $I_{NL} = 14A$, $P_{NL} = 1470W$

$$S_{NL} = \sqrt{3} E_{NL} I_{NL} = \sqrt{3} \times 440 \times 14 = 10669 \text{ VA}$$

$$Q_{NL} = \sqrt{S_{NL}^2 - P_{NL}^2} = \sqrt{10669^2 - 1470^2} = 10586 \text{ VAR}$$

$$X_m = \frac{E_{NL}^2}{\alpha_{NL}} = \frac{440^2}{10586} = 18.3 \Omega$$

$$R_m = \frac{\frac{E_{NL}^2}{\alpha_{NL}}}{P_{NL} - 3 I_{NL}^2 \gamma_1} = \frac{440^2}{(470 - 3 \times 14^2 \times 0.25)} = 146 \Omega$$

locked rotor test


$$S_{LF} = \sqrt{3} E_{LF} I_{LF} = 1.7321 \times 60 \times 163 = 16939 \text{ VA}$$

$$P_{LF} = 7200 \text{ WATT}$$

$$Q_{LF} = \sqrt{S_{LF}^2 - P_{LF}^2} = \sqrt{16939^2 - 7200^2} = 15333 \text{ VAR}$$


$$X = \frac{Q_{LF}}{3 I_{LF}^2} = \frac{15333}{3 \times 60^2} = 1.42 \Omega$$
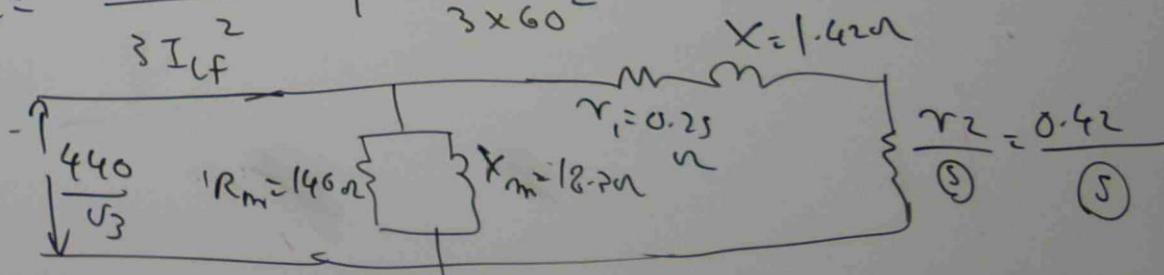
$$\gamma_2 = \frac{P_{LF}}{3 I_{LF}^2} - \gamma_1 = \frac{7200}{3 \times 60^2} - 0.25 = 0.42 \Omega$$



CALCULATING TORQUE, LINE CURRENT, POWER, POWER FACTOR,
SLIP AND EFFICIENCY FOR THE MOTOR USING EQUIVALENT
CIRCUIT PARAMETERS FOR GIVEN LOAD

Ex(29)

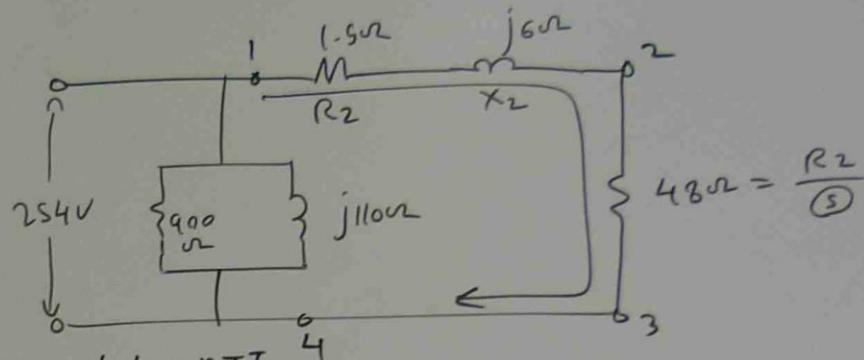

$$\text{STATOR COPPER LOSS} = 44 \text{ WATT}$$

CALCULATE (a) ACTIVE POWER DELIVERED TO ROTOR

(b) MECHANICAL POWER INPUT TO SHAFT

(c) STATOR POWER INPUT

(d) INPUT CURRENT AND P.F

(e) IF WINDAGE & FRICTION LOSS IS 70WATT

FIND OUTPUT TORQUE AND EFFICIENCY

$$SPEED = 1884 \text{ RPM.}$$

$$R_{1234} = 1.5 + 48 = 49.5 \Omega$$

$$Z_{1234} = \sqrt{R_{1234}^2 + X^2}$$

$$= \sqrt{49.5^2 + 6^2} = 49.86 \Omega$$

$$I_{1234} = \frac{V}{Z_{1234}} = \frac{254}{49.86} = 5.09 \text{ Amp.}$$

(a) ACTIVE POWER DELIVERED TO ROTOR = $I^2 \frac{R_2}{\textcircled{S}}$

COPPER LOSS = $5.09^2 \times 48$
 $= 1243.5 \text{ WATT}$

(b) MECHANICAL POWER INPUT TO SHAFT = $(I^2 R_{\text{loss, IN ROTOR}}) + \text{ACTIVE POWER DELIVERED TO ROTOR}$

$$\approx I^2 R_2 + 1243.5$$

$$\approx (5.09)^2 \times 1.5 + 1243.5 = 1282.3 \text{ WATT}$$

(c) STATOR

(d)

T

$$(c) \text{ STATOR POWER INPUT} = \text{CORE LOSS} + \frac{\text{STATOR COPPER LOSS}}{\text{COPPER LOSS}} + \text{MECHANICAL POWER INPUT TO SHAFT}$$

$$= \left(\frac{\text{TERMINAL VOLTAGE}}{\text{CORE RESISTANCE}} \right)^2 + 44 + 1282.3$$

$$= \frac{(254)^2}{900} + 44 + 1282.3$$

$$= 1398.04 \text{ WATT}$$

$$(d) \text{ INPUT CURRENT} = \frac{\text{TOTAL APPARENT POWER}}{\text{SUPPLY VOLTAGE}}$$

ACTIVE POWER = $\sqrt{\text{ACTIV POWER}^2 + \text{REACTIV POWER}^2}$

STATOR POWER INPUT = $\frac{\text{SUPPLY VOLTAGE}^2}{\text{CORE REACTANCE}}$

TOTAL APPARENT POWER = $\sqrt{\text{ACTIV POWER}^2 + \text{REACTIV POWER}^2}$

ACTIVE POWER
LIVERED TO
STATOR

$$\text{ACTIVE POWER} = \frac{\text{STATOR POWER INPUT}}{\text{STATOR POWER INPUT}} = 1398.04 \text{ W}$$

1282.3 WATT

$$\text{REACTIVE POWER} = \frac{(\text{SUPPLY VOLTAGE})^2}{\text{CORE REACTANCE}} = \frac{(254)^2}{110} = 585 \text{ VAR}$$

$$\text{TOTAL APPARENT POWER} = \sqrt{1398.04^2 + 986^2} = 1515.8 \text{ VA}$$

$$\text{INPUT LINE CURRENT} = \frac{\text{APPARENT POWER}}{\text{SUPPLY VOLTAGE}} = \frac{1515.8}{254} = 5.96 \text{ AMP}$$


$$\text{POWER FACTOR (PF) OF MOTOR} = \frac{\text{ACTIVE POWER}}{\text{APPARENT POWER}} = \frac{1398.04}{1515.8} = 0.922 \text{ LAGGING}$$

$$(e) \text{ POWER OUTPUT TO SHAFT} = \frac{\text{ACTIVE POWER DELIVERED TO ROTOR} - \text{WINDAGE \& FRICTION LOSS}}{} \\ = 1243.5 - 70 = 1173.5 \text{ WATT}$$

$$\text{SHAFT TORQUE} = \frac{9.55 \times \text{POWER OUTPUT TO SHAFT}}{\text{SPEED}}$$

$$= \frac{9.55 \times 1173.5}{1854} = 6.04 \text{ N-mm}$$
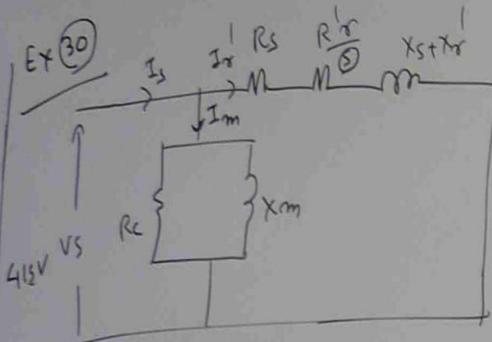
$$\text{EFFICIENCY} = \frac{\text{OUTPUT POWER TO LOAD}}{\text{INPUT ELECTRICAL POWER}} \times 100 = \frac{1173.5}{1398.04} \times 100 = 83.9\%$$



IN THE APPROPRIATE EQUIVALENT CIRCUIT OF ONE PHASE OF A 3 ϕ MESH CONNECTED INDUCTION MOTOR SHOWN IN FIGURE. $V_S = 415V$, $R_C = 25\Omega$, $R_S = 0.1\Omega$

$$R_r^1 = 0.2\Omega, X_m = 25\Omega$$

$X_{st} + X_r = 10\Omega$. DETERMINE THE INPUT CURRENT, POWER FACTOR, INPUT POWER AND EFFICIENCY IF THE FULL LOAD SLIP IS 0.03 WHEN THE MACHINE IS CONNECTED TO A 3 ϕ , 415V, 50Hz SUPPLY

$$Z_S = \sqrt{\left(R_s + \frac{R_r^1}{S}\right)^2 + (X_{st} + X_r)^2} \quad \boxed{\tan \frac{-1(X_{st} + X_r)}{(R_s + \frac{R_r^1}{S})}}$$

$$= \sqrt{\left(0.1 + \frac{0.2}{0.03}\right)^2 + (1)^2} \quad \boxed{\tan \frac{1}{0.1 + \frac{0.2}{0.03}}}$$

$$= 6.83 \underline{8.4} \Omega$$

$$I_s = \frac{V_S}{Z_S} = \frac{415}{6.83 \underline{8.4}} = 60.76 \underline{-8.4} \text{ amp}$$

$$\begin{aligned} \text{WINDING current} \\ I_m &= \frac{V_S}{R_C} - j \frac{V_S}{X_m} = \frac{415}{25} - j \frac{415}{25} = 1.66 - j 16.6 \text{ Amp.} \end{aligned}$$

$$\begin{aligned} \bar{I}_s &= \bar{I}_m + \bar{I}_{cm} = 60.76 \underline{-8.4} + 1.66 - j 16.6 \text{ Amp} \\ &= 60.76 (\cos(-8.4) + j \sin(-8.4)) + 1.66 - j 16.6 \end{aligned}$$

$$\begin{aligned} &= 60.1 - j 8.67 + 1.66 - j 16.6 \\ &= 61.76 - j 25.47 = \sqrt{61.76^2 + 25.47^2} \quad \boxed{- \tan \frac{1}{61.76} \underline{25.47}} = 66.75 \underline{22.4} \text{ A} \end{aligned}$$

$$\Delta I_{ph} = 66.75 \text{ Amp}, \quad I_{line} = \sqrt{3} I_{ph} = \sqrt{3} \times 66.75 = 115.6 \text{ Amp.}$$

$$\text{MECHANICAL power output} = 3 \left(I_s^2 \right) \times R_r^1 \times \frac{(1-S)}{S}$$

$$= 3 \times 60.76^2 \times 0.2 \times \frac{(1-0.03)}{0.03} = 71100 \text{ WATT}$$

$$\text{INPUT power to motor} = \sqrt{3} E I \cos \phi = \sqrt{3} \times 415 \times 115.6 \times \cos(-22.4)$$

$$\text{EFFICIENCY} = \frac{\text{Output Power}}{\text{Input Power}} \times 100 = \frac{71100}{76822} \times 100 = 92.1\%$$


$$= 76822 \text{ WATT}$$


Ex (3)

AN 8 POLE 50Hz 3ϕ SLIP RING INDUCTION MOTOR HAS A TOTAL
LEAKAGE IMPEDANCE $(2 + j 5.4) \Omega$ PER PHASE REFERRED TO THE STATOR
THE STATOR RESISTANCE PER PHASE IS 1.1Ω .

WHEN 415V IS APPLIED TO MESH CONNECTED STATOR WINDING,
THE VOLTAGE BETWEEN ANY PAIR OF OPEN CIRCUITED SLIP RING TO
WHICH THE STAR CONNECTED ROTOR WINDING IS CONNECTED IS 239V.

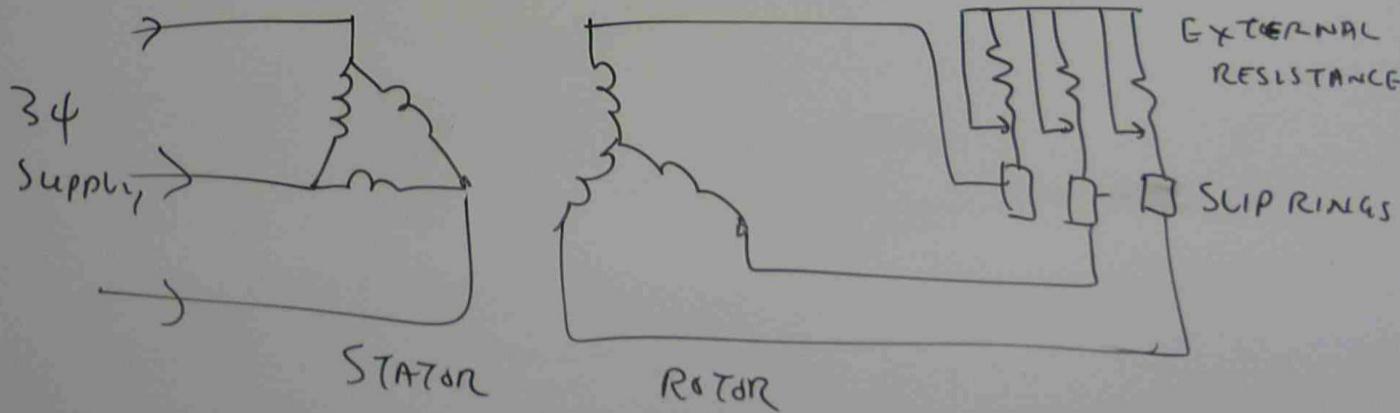- (a) WHEN SLIP RINGS ARE SHORT CIRCUTED, THE SLIP IS 0.04, CALCULATE TORQUE
(b) WHEN SLIP RINGS ARE CONNECTED TO EXTERNAL RESISTOR $0.5 \Omega / \text{ph}$,
SLIP IS 0.05, CALCULATE TORQUE



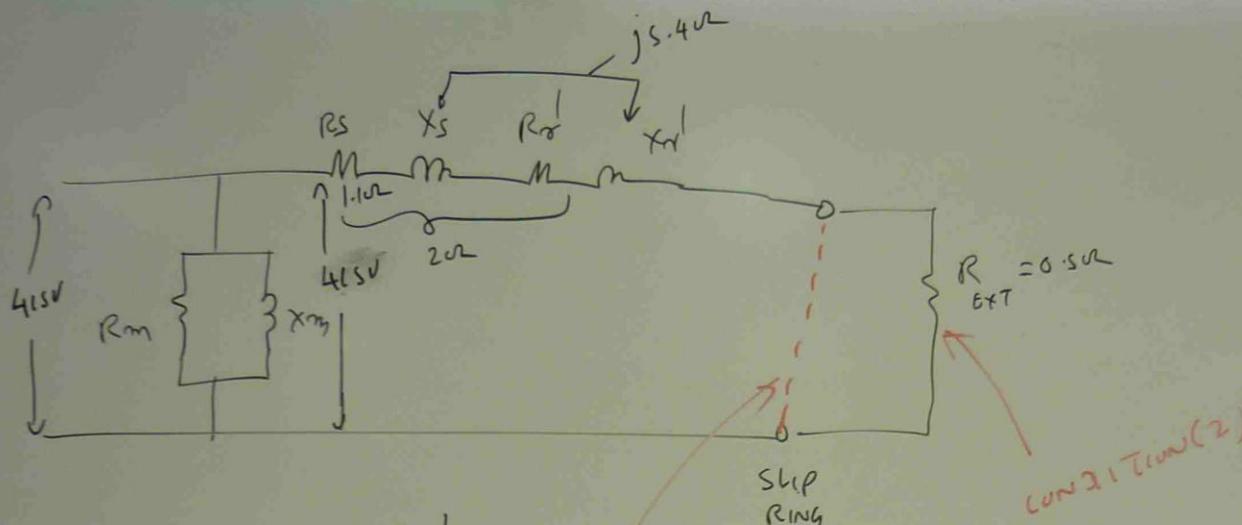

$$R_S + R_R^1 = 2 \Omega \rightarrow R_R^1 = 2 - 1 \cdot 1 \\ = 0.9$$

Condition
(1)

$$X_S + X_R^1 = 5.4 \Omega$$

$$T = \frac{3 v s^2}{2 \pi m} \times \frac{1}{(S R_s + R_r^1)^2 + S^2 (x_s + x_r^1)^2}$$

$$n = n_s(1 - \textcircled{5})$$


$$n_S = \frac{120f}{P} = \frac{120 \times 50}{6} = 750$$

$$n = 750 \left(1 - 0.04\right)^8 = 750 \times 0.96 = 720 \text{ RPM}$$

$$T = \frac{3 \times 415^2}{2 \times 3.1416 \times 720} \left(\frac{0.04 \times 0.9}{(0.04 \times 1.1 + 0.9)^2 + 0.04 \times (5.4)^2} \right)$$

$$= 114.2 \times \frac{0.036}{(0.891 + 0.0466)}$$
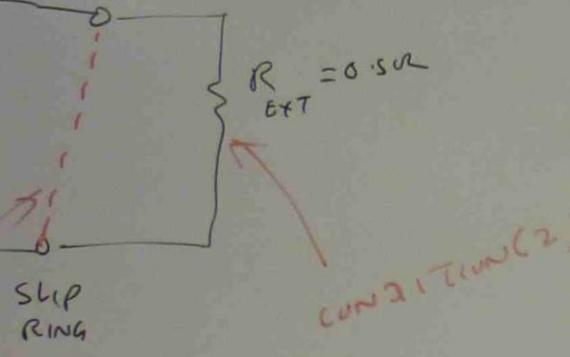
$$= \frac{114.2 \times 0.036}{0.9376} = 4.38 N$$



SLIP RINGS ARE CONNECTED TO 0.5Ω

$$T = \frac{3 \times V_s^2}{2 \pi n} \times \frac{\left(R_r + R_{load} \right)}{\left(R_s + R_r + R_{load} \right)^2 + \left(\omega_s + \omega_r \right)^2}$$

$$= \frac{3 \times 415^2}{2 \times 3.1416 \times 750 (1 - 0.05)} \times \frac{0.05 (0.9 + 0.5)}{(0.05 \times 1.1 + 0.9 + 0.5)^2 + 0.05^2 (5.4)^2}$$

$$= \frac{115.4 \times 0.07}{(1.455)^2 + 0.0729}$$

$$= \frac{115.4 \times 0.07}{2.899}$$

$$= 2.78 N$$

$$- \textcircled{S}^2 (x_s + x_r^1)^2$$

$$T = \frac{3 \times 415^2}{2 \times 3.1416 \times 720} \times \frac{0.04 \times 0.9}{(0.04 \times 1.1 + 0.9)^2 + 0.04^2 \times (5.4)^2}$$

$$= 114.2 \times \frac{0.036}{(0.891 + 0.0466)}$$


$$= \frac{114.2 \times 0.036}{0.9376} = 4.38 N$$


Ex (3)

AN 8 POLE 50Hz 3 ϕ SLIP RING INDUCTION MOTOR HAS A TOTAL LEAKAGE IMPEDANCE $(2 + j5.4)\Omega$ PER PHASE REFERRED TO THE STATOR. THE STATOR RESISTANCE PER PHASE IS 1.1Ω .

WHEN 415V IS APPLIED TO MESH CONNECTED STATOR WINDING, THE VOLTAGE BETWEEN ANY PAIR OF OPEN CIRCUITED SLIP RING TO WHICH THE STAR CONNECTED ROTOR WINDING IS CONNECTED IS 239V.

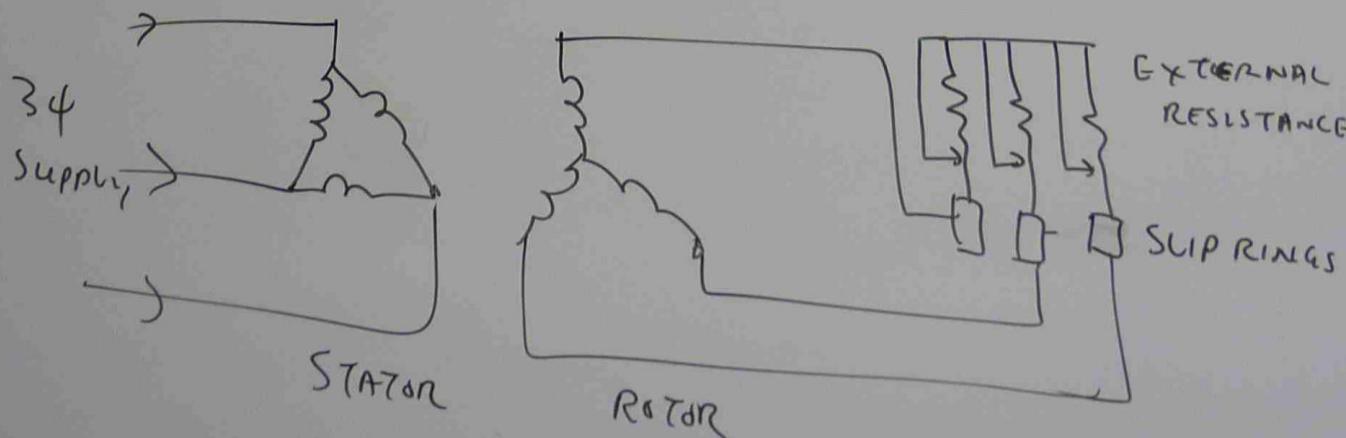- WHEN SLIP RINGS ARE SHORT CIRCUTED, THE SLIP IS 0.04, CALCULATE TORQUE
- WHEN SLIP RINGS ARE CONNECTED TO EXTERNAL RESISTOR $0.5\Omega/\text{ph}$, SLIP IS 0.05, CALCULATE TORQUE



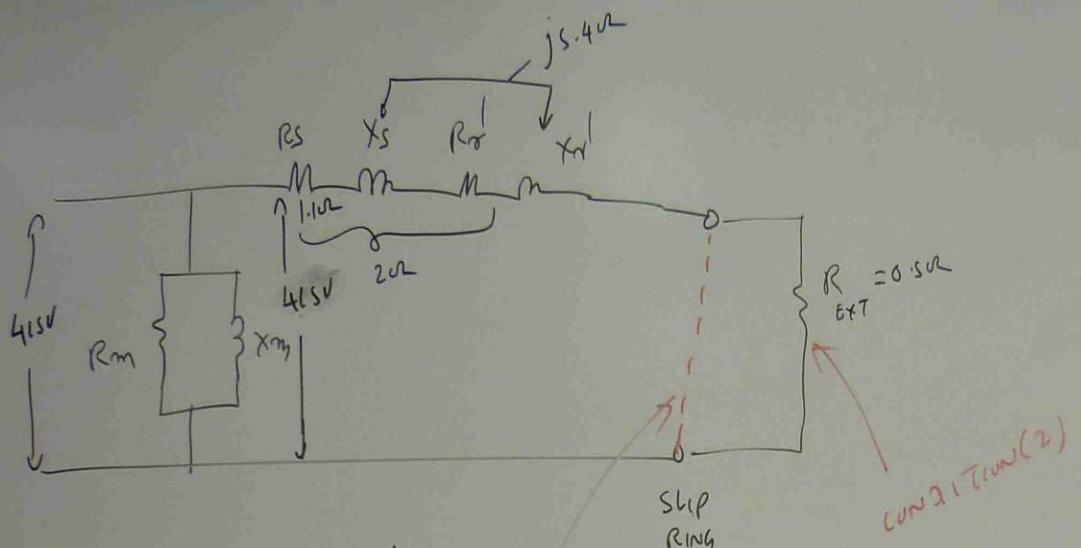

$$R_s + R_r^1 = 2\Omega \rightarrow R_r^1 = 2 - 1.1 = 0.9 \text{ (connection 1)}$$

$$X_s + X_r^1 = 5.4\Omega$$

$$T = \frac{3 vs^2}{2\pi m} \times \frac{\circledS R_r^1}{(\circledS R_s + R_r^1)^2 + \circledS (X_s + X_r^1)^2}$$

$$n = n_s(1 - \circledS)$$

$$n_s = \frac{120f}{P} = \frac{120 \times 50}{8} = 750$$

$$n = 750(1 - 0.04) = 750 \times 0.96 = 720 \text{ RPM}$$

SLIP RINGS ARE CONNECTED TO 0.5Ω

$$T = \frac{3 vs^2}{2\pi m} \times \frac{\circledS (R_r^1 + R_{load})}{(\circledS R_s + R_r^1 + R_{load})^2 + \circledS (X_s + X_r^1)^2}$$

$$= \frac{3 \times 415^2}{2 \times 3.1416 \times 720 (1 - 0.05)} \times \frac{0.05(0.9 + 0.5)}{(0.05 \times 1.1 + 0.9 + 0.5)^2 + 0.05^2}$$

$$= \frac{115.4 \times 0.07}{(1.455)^2 + 0.0729}$$

$$= \frac{115.4 \times 0.07}{2.899}$$

$$= 2.78 \text{ N}$$

$$T = \frac{3 \times 415^2}{2 \times 3.1416 \times 720} \times \frac{0.04 \times 0.9}{(0.04 \times 1.1 + 0.9)^2 + 0.04^2 \times (5.4)^2}$$

$$= 114.2 \times \frac{0.036}{(0.891 + 0.0466)}$$

$$= \frac{114.2 \times 0.036}{0.9376} = 4.38 \text{ N}$$

E+32

A SINGLE PHASE 230V 4 POLES 50Hz, 0.5kW INDUCTION MOTOR

GAVE THE FOLLOWING TEST RESULTS.

LOCKED ROTOR TEST = 60V, 1.5A, PF 0.6 LAGGING

NO LOAD TEST = 230V, 0.535A, PF 0.174 LAGGING

DETERMINE THE APPROPRIATE EQUIVALENT CIRCUIT OF THE MACHINE.

FIND ALSO THE TORQUE DEVELOPED, THE POWER OUTPUT, INPUT CURRENT AND POWER FACTOR WHEN THE MACHINE RUNS WITH A SLIP OF 0.05.

LOCKED ROTOR TEST

$$S_{LF} = E_{LF} \times I_{LF} = 60 \times 1.5 = 90 \text{ VA}$$

$$P_{LF} = E_{LF} \times I_{LF} \times PF = 60 \times 1.5 \times 0.6 = 54 \text{ WATT}$$

$$Q_{LF} = \sqrt{S_{LF}^2 - P_{LF}^2} = \sqrt{90^2 - 54^2} = 72 \text{ VAR}$$

$$X = \frac{Q_{LF}}{3 I_{LF}^2} = \frac{72}{3 \times 1.5^2} = 10.66 \Omega$$

$$r_2 = \frac{P_{LF}}{3 I_{LF}^2} - r_1 = \frac{54}{3 \times (1.5)^2} - 0 = 8 \Omega$$

NO LOAD TEST


$$S_{NL} = E_{NL} \times I_{NL} = 230$$

$$P_{NL} = E_{NL} \times I_{NL} \times PF =$$

$$Q_{NL} = \sqrt{S_{NL}^2 - P_{NL}^2} =$$

$$X_m = \frac{E_{NL}^2}{Q_{NL}} = \frac{230^2}{72} = 121$$
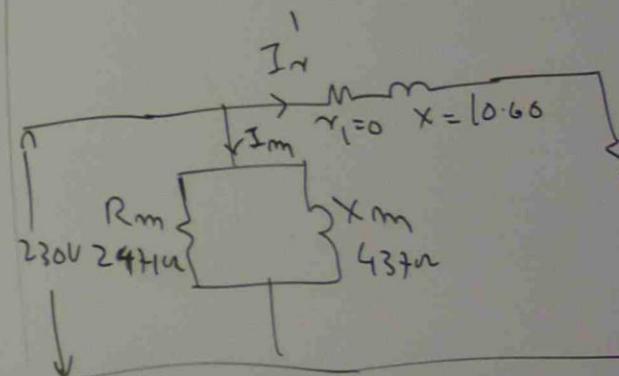
$$R_m = \frac{E_{NL}^2}{P_{NL} - 3 I_{NL}^2 \tau_1}$$



motor

NO LOAD TEST

$$S_{NL} = E_{NL} \times I_{NL} = 230 \times 0.535 = 123 \text{ VA}$$

$$P_{NL} = E_{NL} \times I_{NL} \times PF = 230 \times 0.535 \times 0.74 = 21.4 \text{ WATT}$$


RENT

S.

$$\emptyset_{NL} = \sqrt{S_{NL}^2 - P_{NL}^2} = \sqrt{123^2 - 21.4^2} = 121 \text{ VAR}$$

$$X_m = \frac{E_{NL}^2}{\emptyset_{NL}} = \frac{230^2}{121} = 437 \Omega$$
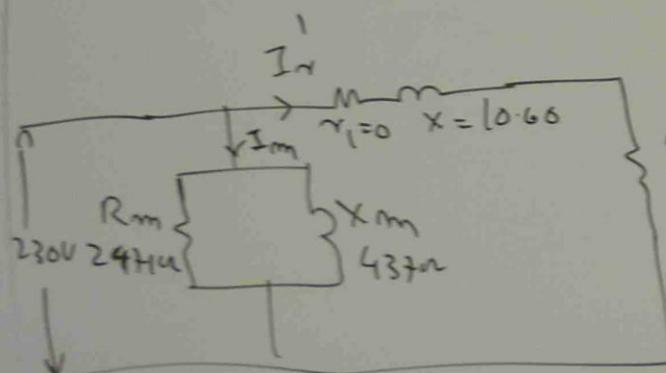
$$R_m = \frac{E_{NL}^2}{P_{NL} - 3 \cdot I_{NL}^2 \gamma_1} = \frac{230^2}{21.4 - 3 \times (0.535)^2 \times 0} = 2471 \Omega$$



$$\frac{\gamma_2}{\gamma_1} = \frac{8}{5}$$

$$\begin{aligned} \gamma_2 &= \frac{230}{\sqrt{\left(R_s + \frac{R_1}{\gamma_1}\right)^2 + (X_s + X_1)^2}} \\ &= \frac{230}{\sqrt{\left(0 + \frac{8}{0.05}\right)^2 + (10.66)^2}} \\ &= 1.434 \quad [3.81 \text{ Amp}] \end{aligned}$$

Mechanical
output

T =

TO CARRY THE SECOND LOAD IN STARTING, MOTOR ROTOR RESISTANCE
MUST BE CHANGED & NEW CHARACTERISTICS CURVE IS TO BE ACHIEVED.

THE OPERATING POINT BEYOND THE ORIGINAL CURVE WILL CREATE
UNSTABILITY.

AT WORST MOTOR WILL FOLLOW THE RUN AWAY CURVE.

MOTOR OPERATES FLUCTUATING BETWEEN STABLE & UNSTABLE
IS CRAWLING WHICH IS THE EARLY SIGN OF RUN AWAY.

INDUCTION MOTOR CHARACTERISTICS UNDER VARIOUS LOAD CONDITIONS

AT THE RATED FREQUENCY

SLIP (s), TORQUE (T), LINE VOLTAGE (E), MOTOR RESISTANCE (R)

ARE RELATED TO MOTOR CONSTANT

$$K = \frac{s E^2}{T R}$$

$$K = \frac{s_1 E_1^2}{T_1 R_1} = \frac{s_2 E_2^2}{T_2 R_2} = \frac{s_3 E_3^2}{T_3 R_3} = \dots$$

s_{NE}
 s_{OL}

T_{NL}
 T_0

SISTANCE (R)

ONCE WE KNOW THE CHARACTERISTICS OF A MOTOR
FOR GIVEN LOAD CONDITION, WE CAN PREDICT SPEED,
TORQUE, POWER FOR OTHER LOADS.

$$\frac{s_{\text{NEW}}}{s_{\text{OLD}}} = \left[\frac{T_{\text{NEW}}}{T_{\text{OLD}}} \right] \left[\frac{R_{\text{NEW}}}{R_{\text{OLD}}} \right] \left[\frac{E_{\text{OLD}}}{E_{\text{NEW}}} \right]^2$$

s_{NEW} = NEW SLIP

s_{OLD} = OLD SLIP

T_{NEW} = NEW TORQUE

T_{OLD} = OLD TORQUE


R_{NEW} = NEW ROTOR RESISTANCE

R_{OLD} = OLD ROTOR RESISTANCE

E_{OLD} = OLD ROTOR VOLTAGE

E_{NEW} = NEW ROTOR VOLTAGE

TORQUE - SPEED CURVE

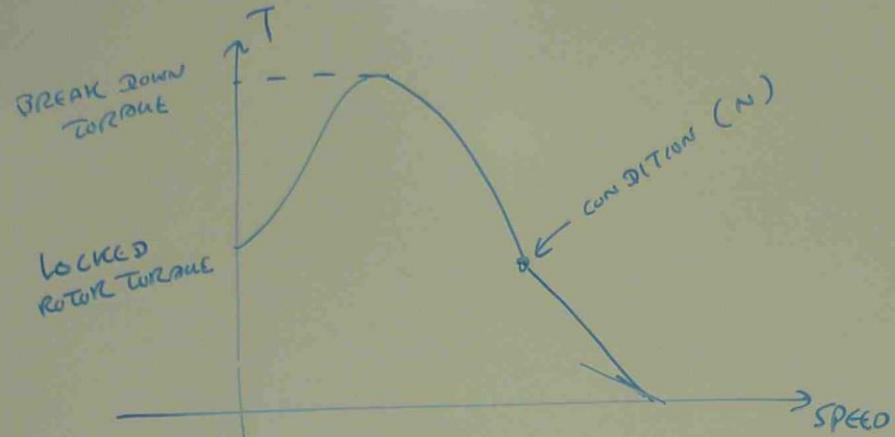

Ex(33)

A 3 PHASE, 208 V INDUCTION MOTOR HAVING A SYNCHRONOUS SPEED OF 1200 RPM RUNS AT 1140 RPM WHEN CONNECTED TO A 215 V LINE AND DRIVING A CONSTANT TORQUE LOAD. CALCULATE THE SPEED IF THE VOLTAGE INCREASES TO 240 V.

$$N_S = 1200 \text{ RPM}$$

$$N = 1140 \text{ RPM}$$

$$\begin{aligned} \textcircled{S}_1 &= \frac{N_S - N}{N_S} = \frac{1200 - 1140}{1200} \\ &= 0.05 \end{aligned}$$

$$E_1 = 215 \text{ V}$$

$$E_2 = 240 \text{ V}$$

$$\textcircled{S}_2 = ? \rightarrow \text{NEW SPEED.}$$

$$k = \frac{\textcircled{S}_1 E^2}{T R}$$

$$\frac{\textcircled{S}_1 E_1^2}{T_1 R_1} = \frac{\textcircled{S}_2 E_2^2}{T_2 R_2}$$

$$T_1 = T_2, R_1 = R_2$$

$$\frac{0.05 \times 215^2}{T_1 R_1} = \frac{s_2 \times 240^2}{T_2 R_2}$$

$$s_2 = \frac{0.05 \times 215^2}{240^2}$$

$$= 0.04$$

$$\text{NEW SPEED} = [1 - s_2] \times N_s$$

$$= [1 - 0.04] \times 1200$$

$$= 1152 \text{ RPM}$$

Ex 34

A 3φ 8 pole induction motor driving a compressor runs at 873 RPM, immediately after it is connected to a fixed 460V, 60 Hz line. The initial cold rotor temperature is 23°C. The speed drops to 864 RPM after the machine has run for several hours.

CALCULATE (a) THE HOT ROTOR RESISTANCE IN TERM OF THE COLD RESISTANCE

(b) THE APPROPRIATE HOT TEMPERATURE OF THE ROTOR BARS, KNOWING THEY ARE MADE OF COPPER.

$$N_s = \text{SYNCHRONOUS SPEED} = \frac{120f}{P} = \frac{120 \times 60}{8} = 900 \text{ RPM}$$

$$N_1 = 873 \text{ RPM} \quad s_1 = \frac{N_s - N_1}{N_s} \quad s_1 = \frac{900 - 873}{900} = 0.03$$

$$N_2 = 864 \text{ RPM}$$

$$s_2 = \frac{900 - 864}{900} = 0.04$$

HOT / CUP
ROTOR
RESISTANCE

COLD $\rightarrow R_1 = ?$ $R_2 = ?$ $\frac{R_2}{R_1} = ?$

$$K = \frac{S_1 E_1^2}{T_1 R_1}$$

$$\underline{T_1 = T_2}$$

$$\frac{S_1 E_1^2}{T_1 R_1} = \frac{S_L E_2^2}{T_2 R_2}$$

$$\frac{0.03 \times 460^2}{T_1 \times R_1} = \frac{0.04 \times 460^2}{T_2 \times R_2}$$

$$\frac{0.03}{R_1} = \frac{0.04}{R_2}$$

$$\frac{R_2}{R_1} = \frac{0.04}{0.03} = 1.33$$

COPPER

$$t_2 = \frac{R_2}{R_1} (234 + t_1) - 234$$

$$t_2 = 1.333 (234 + 23) - 234$$

$$= 108 \text{ C} \times$$

Ex 35

A 3φ 4 pole wound rotor induction motor has a rating of 110 kW, 1760 RPM, 2.3 kV, 60 Hz. Three external resistances of 2Ω are connected in star (WYE) across the rotor slip rings. Under these conditions, the motor develops a torque of 300 N-m at a speed of 1000 RPM.

(a) Calculate the speed for a torque of 400 N-m

(b) Calculate the value of external resistances so that the motor develops 10 kW at 200 RPM.

Ex(35)

A 3 ϕ 4 POLE WOUND ROTOR INDUCTION MOTOR HAS A RATING OF 110 KW, 1760 RPM, 2.3 KV, 60 Hz. THREE EXTERNAL RESISTANCES OF 2Ω ARE CONNECTED IN STAR (WYE) ACROSS THE ROTOR SLIP RINGS. UNDER THESE CONDITIONS, THE MOTOR DEVELOPS A TORQUE OF 300 N-m AT A SPEED OF 1000 RPM.

(a) CALCULATE THE SPEED FOR A TORQUE OF 400 N-m

(b) CALCULATE THE VALUE OF EXTERNAL RESISTANCES SO THAT THE MOTOR DEVELOPS 10 KW AT 200 RPM.

$$T_1 = 300 \text{ N-m}$$

$$T_2 = 400 \text{ N-m}$$

$$N_1 = 1000 \text{ RPM}$$

$$N_2 = ?$$

$$N_s = \frac{120f}{P} = \frac{120 \times 60}{4} = 1800 \text{ RPM}$$

$$\textcircled{S}_1 = \frac{N_s - N_1}{N_s} = \frac{1800 - 1000}{1800} = 0.444$$

$$\begin{aligned} \textcircled{S}_2 &= ? \\ \text{Assume} \\ E_1 &= F_2 \\ R_1 &= R_2 \end{aligned}$$

$$K = \frac{\textcircled{S} E^2}{TR}$$

$$\frac{\textcircled{S}_1 E_1^2}{T_1 R_1} = \frac{\textcircled{S}_2 E_2^2}{T_2 R_2}$$

$$\frac{0.444 \times E_1^2}{300 \times R_1} = \frac{\textcircled{S}_2 E_2^2}{400 \times R_2}$$

$$\textcircled{S}_2 = \frac{0.444 \times 400}{300}$$

$$= 0.592$$

$$N_{r(2)} = (1 - \textcircled{S}) N_S$$

$$= (1 - 0.592) \times 1800$$

$$= 734.4 \text{ RPM}$$

(b) 10 kw, 200 RPM

$$T = \frac{9.55 \times \text{POWER (WATT)}}{\text{RPM}}$$

$$T = \frac{9.55 \times 10,000}{200}$$

$$= 478 \text{ N-m}$$

$$S_{UP} = \frac{N_S - N_r}{N_S} = \frac{1800 - 200}{1800} = 0.89$$

$$R_1 = 2 \Omega, T_1 = 300 \text{ N-m}, \textcircled{S}_1 = 0.444 \quad E_1 = E_2$$

$$R_2 = ? \quad T_2 = 478 \text{ N-m} \quad \textcircled{S}_2 = 0.89$$


$$K = \frac{\textcircled{S} E^2}{TR}$$

$$\frac{S_1}{T_1 R_1} E_1^2 = \frac{S_2}{T_2 R_2} E_2^2$$

$$\frac{0.444 \times E_1^2}{300 \times 2} = \frac{0.89 \times E_2^2}{478 \times R_2}$$

$$R_2 = \frac{0.89 \times 300 \times 2}{0.444 \times 478}$$

$$= 2.53\Omega$$

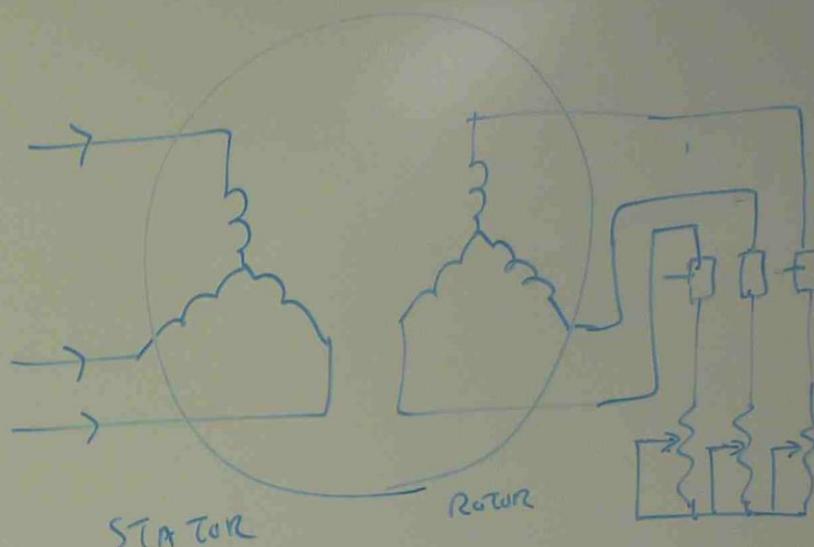


WOUND ROTOR INDUCTION
MOTOR

BY ADJUSTING THE ROTOR EXTERNAL RESISTANCE, THE
SPEED AND TORQUE OF WOUND ROTOR INDUCTION MOTOR
CAN BE REGULATED.

Ex(36)

A 3φ WOUND ROTOR INDUCTION MOTOR HAS A RATING OF 150HP (110kW) 1760RPM
2.3 KV, 60 Hz. UNDER LOCKED ROTOR CONDITION, THE OPEN CIRCUIT ROTOR VOLTAGE BETWEEN
 THE SLIP RING IS 500V. THE ROTOR IS DRIVEN BY A VARIABLE SPEED DC MOTOR.

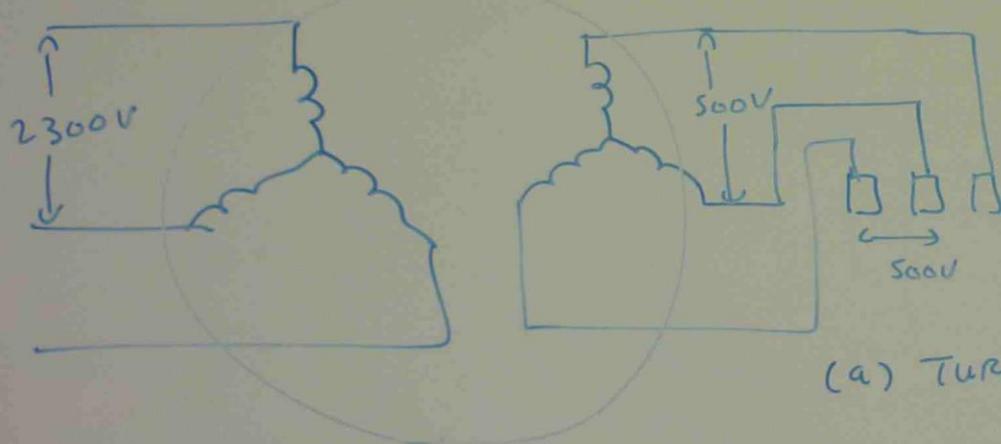- CALCULATE (a) THE TURN RATIO OF THE STATOR TO ROTOR WINDING
 (b) THE ROTOR VOLTAGE AND FREQUENCY WHEN THE ROTOR IS DRIVEN AT
 720 RPM IN THE SAME DIRECTION AS THE REVOLVING FIELD.
 (c) THE ROTOR VOLTAGE AND FREQUENCY WHEN THE ROTOR IS DRIVEN
 AT 720 RPM OPPOSITE TO THE REVOLVING FIELD.



WOUND ROTOR MOTOR

ALL SLIP RINGS ARE TO
 BE SHORT CIRCUTED SO THAT
 MOTOR CAN START.

$$(a) \text{ TURN RATIO} = \frac{V_1}{V_2} = \frac{2300}{500} = 4.6$$

$$(b) \text{ ROTOR VOLTAGE AT } 720 \text{ RPM} = \text{SLIP} \times f_2 \quad (\text{STATOR FREQUENCY})$$

$$f_r = \text{ROTOR FREQUENCY}\br/>AT ANY RPM$$

$$f_s = \text{STATOR FREQUENCY}$$

$$f_r = \text{SLIP} \times f_s$$

720 RPM \rightarrow 1300 RPM

$$N = \frac{120 f}{P}$$

$$1300 = \frac{120 \times 60}{P} \Rightarrow P = 4$$

$$\text{SLIP} = \frac{N_s - N_r}{N_s}$$

$$= \frac{1300 - 720}{1300} = 0.6$$

$$\text{ROTOR VOLTAGE AT } 720 \text{ RPM} = \text{SLIP} \times E_2 \text{ STANDBY}$$
$$= 0.6 \times 500 = 300 \text{ V}$$


$$f_r = \textcircled{S} f_s = 0.6 \times 60 = 36 \text{ Hz}$$

$$(c) \quad \text{SLIP} = \frac{N_s - N_r}{N_s} = \frac{1300 - (-720)}{1300} = 1.4$$

$$\textcircled{S} E_2 = 1.4 \times 500 = 700 \text{ V}$$

$$f_r = \textcircled{S} f_s = 1.4 \times 60 = 84 \text{ Hz}$$

FREQuency CONVERTER SET

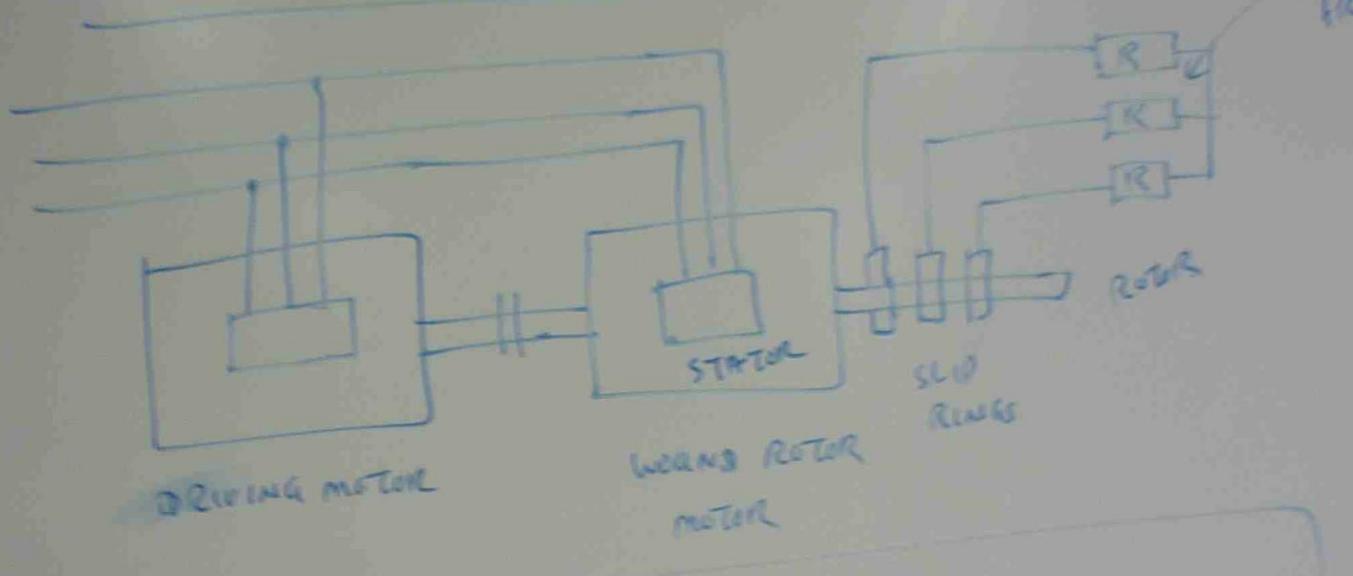

POWER TRANSFERRED FROM
STATOR TO ROTOR OF
WOUND ROTOR MOTOR

=

POWER GENERATED
SLIP


TABLE
FREQUENCY

E+37)

WE WISH TO USE A 30kW, 880 RPM, 60Hz WOUND ROTOR
MOTOR AS A FREQUENCY CONVERTER TO GENERATE 60kW
AT AN APPROXIMATE FREQUENCY OF 180Hz.

IF THE SUPPLY LINE FREQUENCY IS 60Hz, CALCULATE
THE FOLLOWINGS.

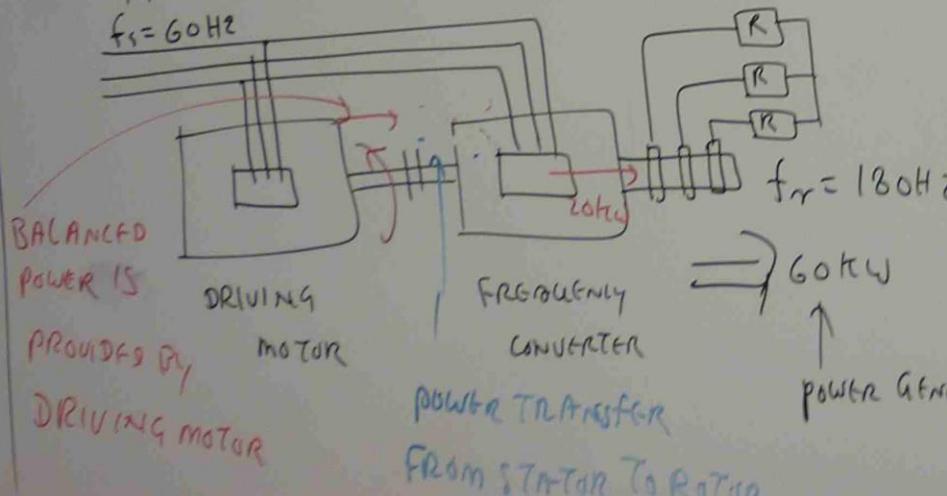- THE SPEED OF THE INDUCTION MOTOR THAT DRIVES THE FREQUENCY CONVERTER
- THE ACTIVE POWER DELIVERED TO THE STATOR OF THE FREQUENCY CONVERTER
- THE POWER OF THE INDUCTION MOTOR (M)
- WILL THE FREQUENCY CONVERTER OVER HEAT UNDER THESE CONDITIONS.



POWER TRANSFERRED

$$\text{FROM STATOR TO ROTOR} = \frac{\text{POWER GENERATED}}{\text{SLIP}}$$

$$f_r = S f_s$$

$$180 = S \times 60 \rightarrow S = \frac{180}{60} = 3$$


$$(b) \text{POWER TRANSFERRED} = \frac{60}{3} = 20 \text{kW}$$

$$(c) \text{DRIVING MOTOR} = \frac{\text{POWER GENERATED}}{\text{POWER TRANSFERRED}} - \text{POWER TRANSFERRED FROM STATOR TO ROTOR}$$

$$= 60 - 20 = 40 \text{kW}$$

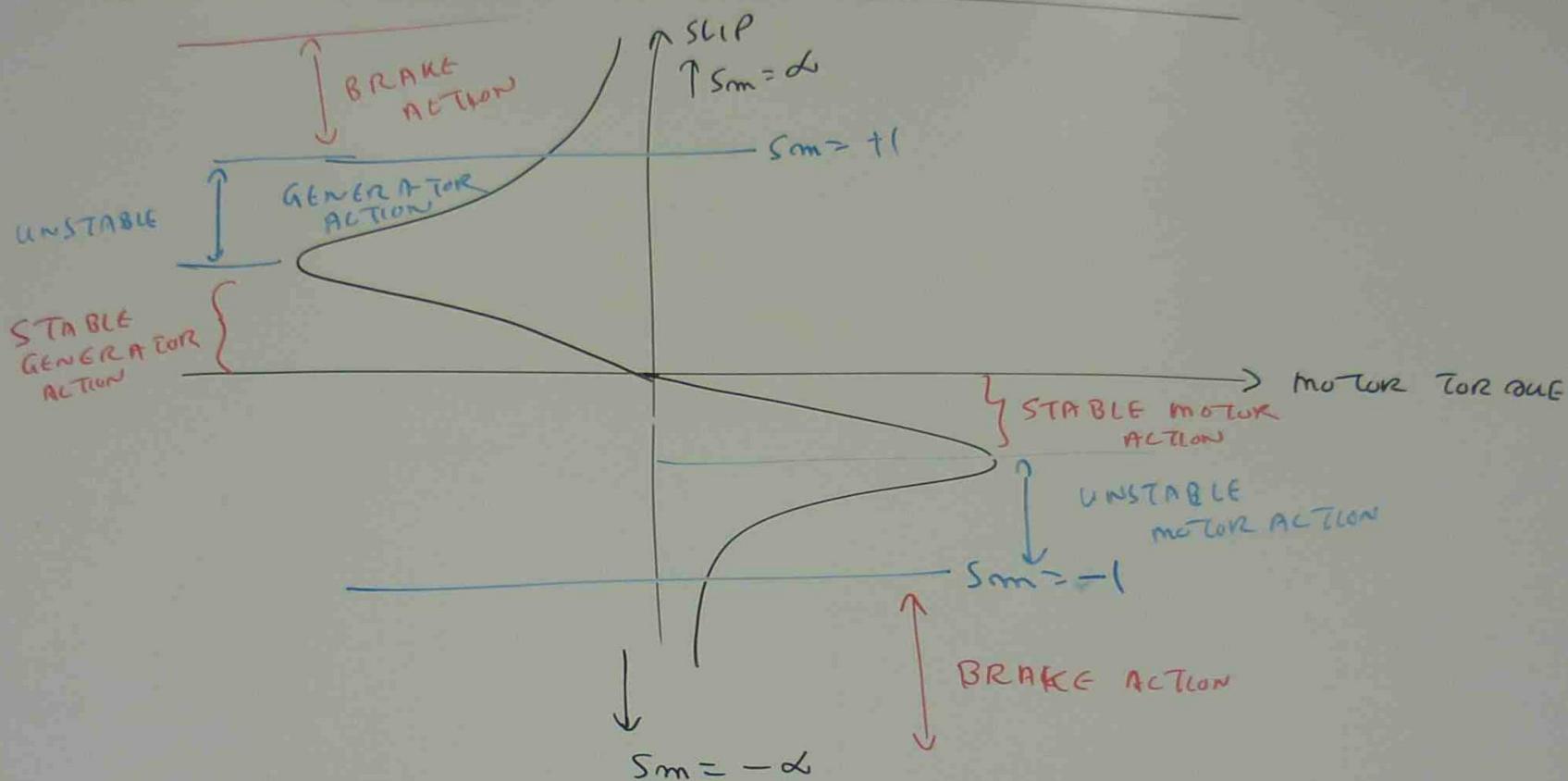(d) IT WILL BE OVER HEATED


SLIP TORQUE CHARACTERISTICS OF INDUCTION MACHINE





STABILITY AND DRAWING

STABILITY

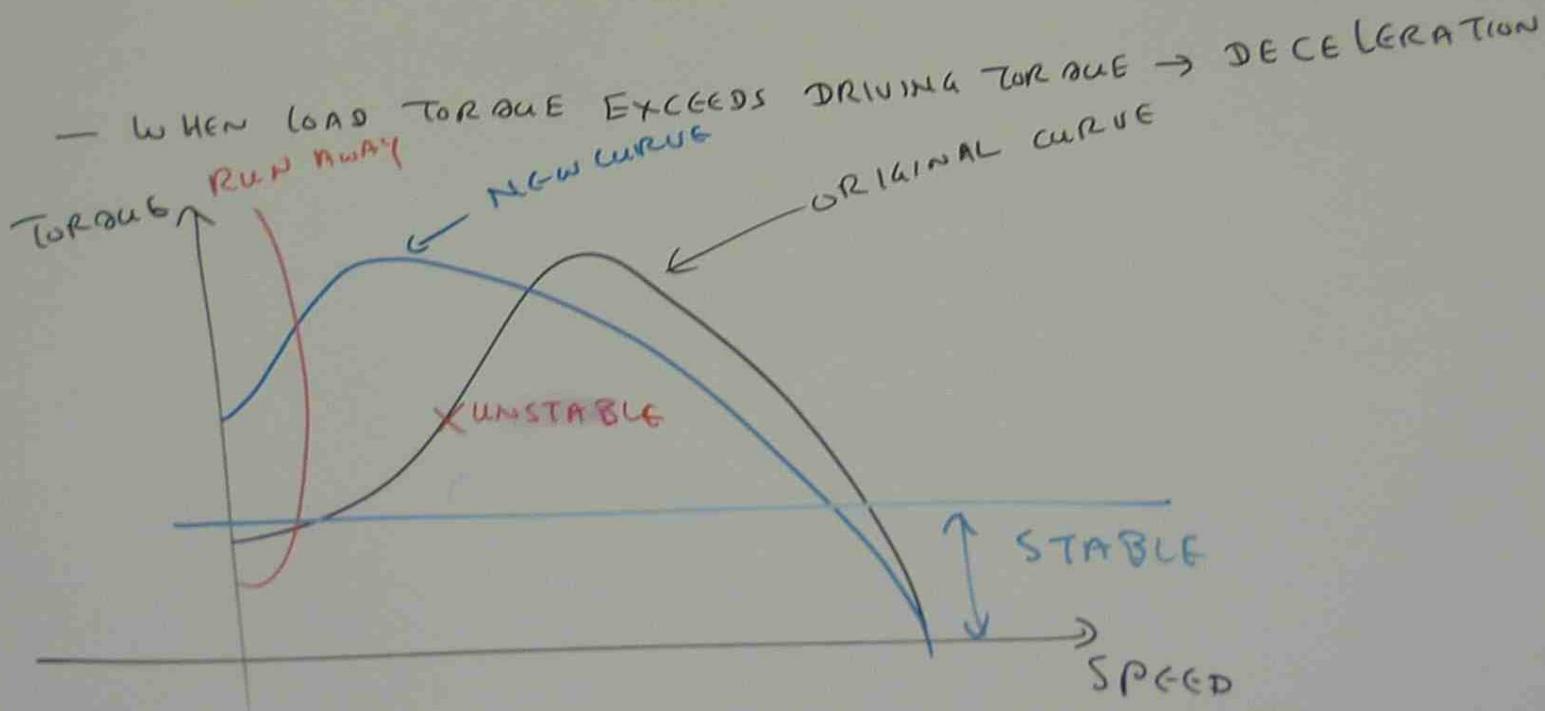- STARTING TORQUE IS GREATER THAN LOAD TORQUE
- ACCELERATION AT ANY SPEED \propto TORQUE DIFFERENCE
- WHEN THE ACCELERATION IS ZERO \rightarrow STEADY SPEED IS OBTAINED
 \downarrow
STABLE OPERATING POINT.



MODIFIED CIRCUIT

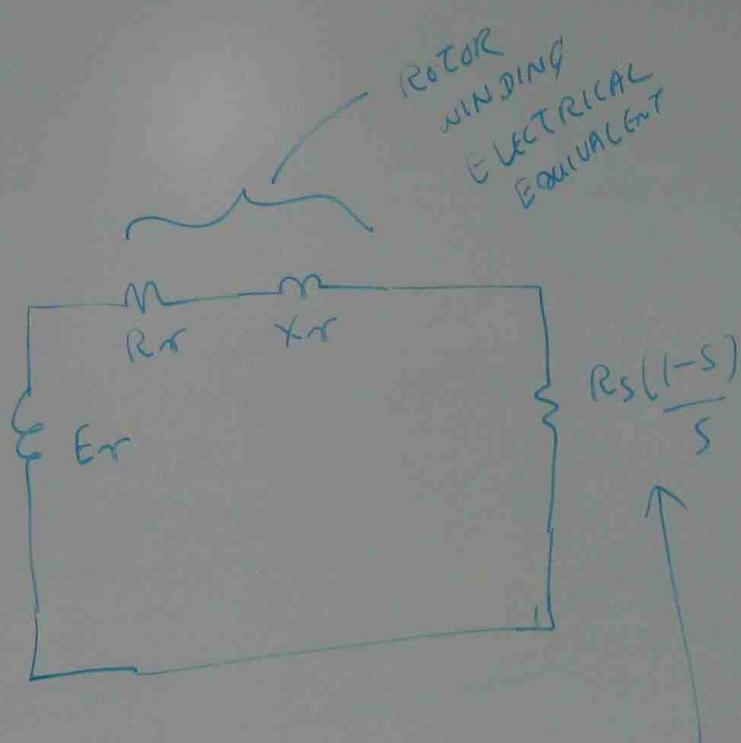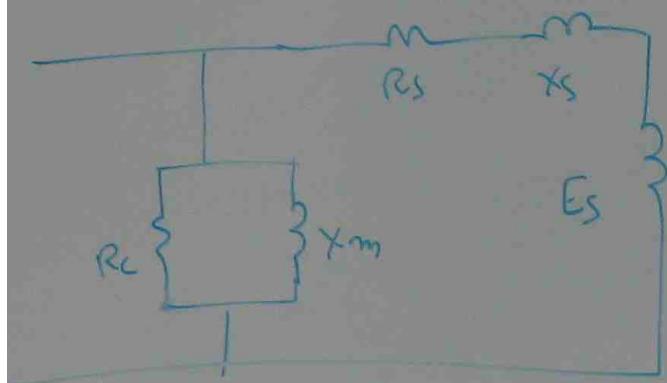

$$I_r = \frac{E_r}{(R_r + jX_r) + R_s \left(\frac{1-s}{s}\right)}$$

ROTOR LOAD
ELECTRICAL
EQUIVALENT