

Pb A TEST ON A $\frac{1}{4}$ HP, 120V, 60Hz, 1725 RPM 1φ MOTOR

REVEALS THE FOLLOWING RESULTS

R_{s1} STATOR RESISTANCE = 2Ω (1Ω) ← DIVIDED BY (2)

R_r ROTOR RESISTANCE REFERRED TO STATOR = 4Ω (2Ω)

X_{s1} STATOR LEAKAGE REACTANCE = 3Ω (j1.5Ω)

X_r ROTOR LEAKAGE REFERRED TO STATOR = 3Ω (j1.5Ω)

R_{h+e} RESISTANCE CORRESPONDING TO WINDAGE, FRICTION, IRON LOSSES = 600Ω (300Ω)

X_m MAGNETIZING REACTANCE = 60Ω (j300Ω)

DRAW THE EQUIVALENT DIAGRAM AND DETERMINE THE POWER OUTPUT,

EFFICIENCY AND POWER FACTOR OF THE MOTOR WHEN IT RUNS

AT 1725 RPM.


N_r 1725 N_s ≈ 1800 rpm

$$\text{SLIP } (\delta) = \frac{N_s - N_r}{N_s} = \frac{1800 - 1725}{1800} = 0.0417$$

1780 × 0.982


9.55

= 177W

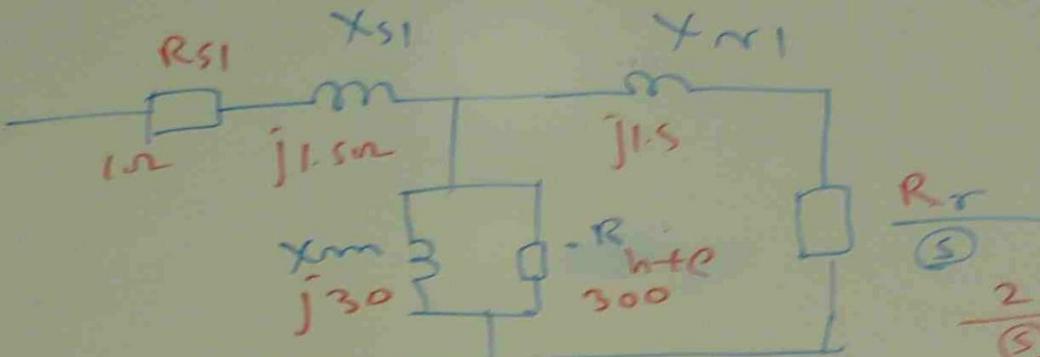

STAR WINDING
WINDING (1)

$$\frac{2}{S} = \frac{2}{0.0417} = 46$$

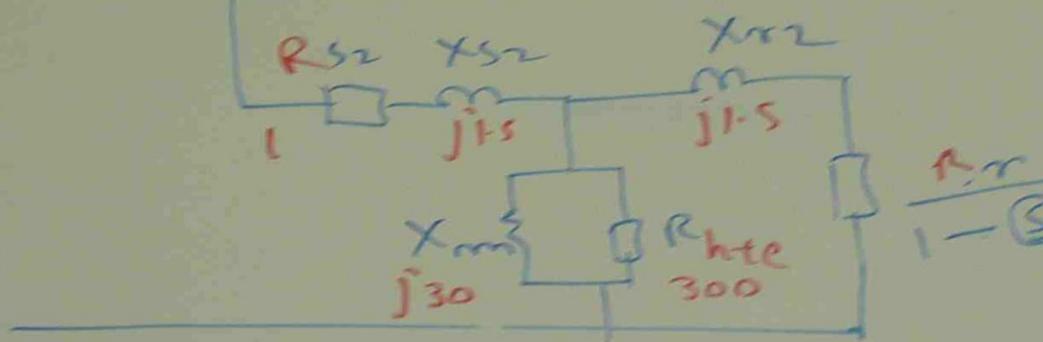


DELTA WINDING (2)

$$\frac{2}{1-0.0417} = 1.07$$


$$R_m, X_m, R_s1, X_s1, X_m, X_s2, Z_{s2} = \frac{\text{Given Value}}{2}$$

14 motor equivalent diagrams

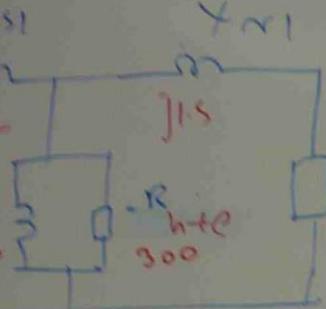

$$\frac{R_r}{S} = \frac{2}{0.0417} = 46$$

STARTING WINDING(1)

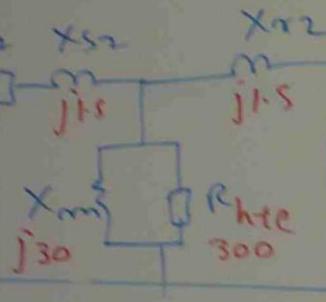


$$\frac{R_r}{1-S} = \frac{2}{1-0.0417} = 1.07$$

RUNNING WINDING (2)

$$X_{r1}, X_{r2}, S_2 = \frac{\text{GIVEN VALUE}}{2}$$

MOTOR EQUIVALENT DIAGRAM

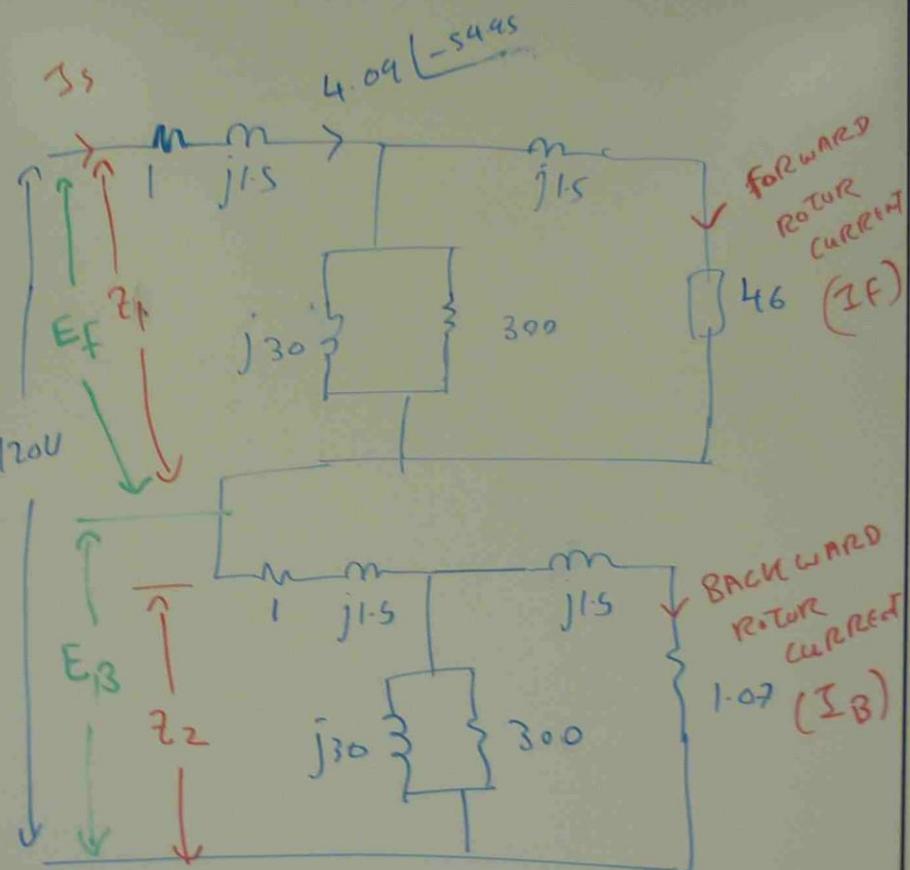

$$\begin{aligned}
 Z_P &= 1 + j1.5 + \frac{1}{\frac{1}{46+j1.5} + \frac{1}{300} + \frac{1}{j30}} \\
 &= 1 + j1.5 + \frac{300 \times j30 + (46+j1.5) \times j30 + 300(46+j1.5)}{(46+j1.5)(300)(j30)} \\
 &= 1 + j1.5 + \frac{(46+j1.5)(300) j30}{300 \times j30 + (46+j1.5) \times j30 + 300(46+j1.5)} \\
 &= 1 + j1.5 + \frac{j46 \times 300 \times 30 - 300 \times 1.5 \times 30}{j46000 + j46 \times 30 - 1.5 \times 30 + 46 \times 300 + j1.5 \times 300} \\
 &= 1 + j1.5 + \frac{-1.5 \times 30 \times 300 + j46 \times 300 \times 30}{46 \times 300 - 1.5 \times 30 + j(46000 + 46 \times 30 + 1.5 \times 300)}
 \end{aligned}$$

$$\begin{aligned}
 Z_1 &= 1 + j1.5 + (3.89 + j19.53) \\
 &= 14.89 + j21.03 = \sqrt{14.89^2 + 21.03^2} \left(\tan^{-1} \frac{21.03}{14.89} \right) = 25.77 \angle 54.7^\circ
 \end{aligned}$$

$$\begin{aligned}
 Z_2 &= 1 + j1.8 + \frac{1}{100 + j1.8} + \frac{1}{300} + \frac{1}{j30} \\
 &= 1 + j1.8 + 0.93 + j1.45 \\
 &= 1.93 + j2.95 \Omega = \sqrt{1.93^2 + 2.95^2} \left(\angle \frac{2.95}{1.93} \right) = 3.52 \angle 55.3^\circ
 \end{aligned}$$

$$\begin{aligned}
 \text{Short current } I_s &= \frac{E}{Z_1 + Z_2} = \frac{120}{14.82 + j21.03 + 1.93 + j2.95} \\
 I_s &= \frac{120}{16.82 + j23.98} \\
 &= \frac{120}{\sqrt{16.82^2 + 23.98^2}} \left(\angle -\frac{23.98}{16.82} \right)
 \end{aligned}$$

$$I_s = \frac{120}{19.75 \angle 54.93^\circ} = 4.09 \angle -54.93^\circ$$

$$E_F = I_S \times Z_1 = 4.09 \left[-54.95 \times 25.77 \right] \left[\frac{1}{54.7} \right] = 105.6 \left[-0.25 \right]$$

$$E_B = I_S \times Z_2 = 4.09 \left[-54.95 \times 3.52 \right] \left[\frac{1}{54.8} \right] = 14.42 \left[1.85 \right]$$

$$I_F = \frac{4.09 \left[-54.95 \right]}{\frac{1}{300} + \frac{1}{j30}} \\ 46 + j1.5 + \frac{1}{\frac{1}{300} + \frac{1}{j30}}$$

$$= \frac{4.09 \left[-54.95 \right]}{48.02 \left(1.79 \right)} \left(13.84 + j19.5 \right)$$

$$= \frac{4.09 \left[-54.95 \right] \times 23.96 \left[\frac{54.58}{54.58} \right]}{48.02 \left(1.79 \right) \left| 1 \right|} = 2.044 \left[2.16 \right]$$

$$I_B = \frac{4.09 \left[-54.95 \right] \times \frac{\frac{1}{300} + \frac{1}{j30}}{1.07 + j1.5 + \frac{1}{\frac{1}{300} + \frac{1}{j30}}}}{1.81 \left[\frac{55.78}{55.78} \right]}$$

$$= \frac{4.09 \left[-54.95 \right] \times (0.93 + j1.45)}{1.81 \left[55.78 \right]} = 3.89 \left[-53.4 \right]$$

FORWARD POWER

$$P_F = I_f^2 \times R$$
$$= 2.044^2 \times 48 = 200.5 \text{ W}$$

$$P_B = I_B^2 \times R$$
$$= 3.89^2 \times 1.07$$
$$= 15.4 \text{ W}$$

$$T = \frac{q_{ss}}{m} (P_F - P_B)$$

$$= \frac{q_{ss}}{17800} (200.5 - 15.4)$$

$$= 0.982 \text{ N-m}$$

$$\text{POWER} = \frac{nT}{q_{ss}} = \frac{1780 \times 0.982}{q_{ss}}$$
$$= 177 \text{ W}$$

Pb
RE UEN
RSI S

RN R
XS1 S
XR

Rh+e
Xam

FORWARD POWER

$$P_F = I_F^2 \times R \left(\frac{R^2}{r^2} \right)$$
$$= 2.044^2 \times 48 = 200.5 \text{ W}$$

$$P_B = I_S^2 \times R \left(\frac{r^2}{r^2 - \sigma^2} \right)$$
$$= 3.69^2 \times 1.09$$
$$= 15.4 \text{ W}$$

$$T = \frac{q_{ss}}{m_s} (P_F - P_B)$$

$$= \frac{q_{ss}}{1600} (200.5 - 15.4)$$
$$= 0.982 \text{ N-m}$$

$$\frac{\text{POWER}}{\text{O/P}} = \frac{n_f T}{q_{ss}} = \frac{1780 \times 0.982}{q_{ss}}$$
$$= 177 \text{ W}$$

$$I_S = 4.09 \angle -54.95^\circ$$

$$PF = \cos 54.95^\circ = 0.57 \text{ LAGGING}$$

$$\text{INPUT POWER} = E I_S \cos \phi = 110 \times 4.09 \times 0.57 = 282.3 \text{ W}$$

$$\text{OUT PUT POWER} = 177 \text{ W}$$

$$\text{EFFICIENCY} = \frac{\text{OUT PUT}}{\text{IN PUT}} \times 100 = \frac{177}{282.3} \times 100 = 62.7\%$$

Pb

A RESISTANCE SPLIT PHASE MOTOR IS RATED AT $\frac{1}{4}$ HP
(187 W) 1725 RPM, 115V, 60 Hz

WHEN THE ROTOR IS LOCKED, A TEST AT REDUCED VOLTAGE
ON MAIN AND AUXILIARY WINDINGS YIELDS THE FOLLOWING
RESULTS.

	MAIN WINDING	AUXILIARY WINDING
APPLIED VOLTAGE	$E = 23V$	$E = 23V$
CURRENT	$I_s = 4A$	$I_a = 1.5A$
ACTIVE POWER	$P_s = 60W$	$P_a = 30W$

CALCULATE (a) PHASE ANGLE BETWEEN I_s AND I_a

(b) LOCKED ROTOR CURRENT DRAWN FROM
THE LINE AT 115V

Pb

A RESISTANCE SPLIT PHASE MOTOR IS RATED AT $\frac{1}{4}$ HP

(187 W) 1725 RPM, 115V, 60 Hz

WHEN THE ROTOR IS LOCKED, A TEST AT REDUCED VOLTAGE
ON MAIN AND AUXILIARY WINDINGS YIELDS THE FOLLOWING
RESULTS.

	MAIN WINDING	AUXILIARY WINDING
APPLIED VOLTAGE	$E = 23V$	$E = 23V$
CURRENT	$I_s = 4A$	$I_a = 1.5A$
ACTIVE POWER	$P_s = 60W$	$P_a = 30W$

CALCULATE (a) PHASE ANGLE BETWEEN I_s AND I_a

(b) LOCKED ROTOR CURRENT DRAWN FROM
THE LINE AT 115V

(a)

MAIN WINDING

$$\text{APPARENT POWER } S_s = EI_s = 23 \times 4 = 92 \text{ VA}$$

$$\text{POWER FACTOR} = \frac{P_s}{S_s} = \frac{60}{92} = 0.65$$

$$\phi_s = \cos^{-1} 0.65 = 49.6^\circ$$

AUXILIARY WINDING

$$\text{APPARENT POWER} = S_a = EI_a = 23 \times 1.5 = 34.5 \text{ VA}$$

$$\text{POWER FACTOR} = \frac{P_a}{S_a} = \frac{30}{34.5} = 0.87$$

$$\phi_a = \cos^{-1} 0.87 = 29.6^\circ$$

$$\text{ANGLE DIFFERENCE: } \phi_s - \phi_a = 49.6 - 29.6 = 20^\circ$$

(b) TOTAL ACTIVE POWER ABSORBED BY
MAIN AND AUXILIARY WINDING = $60 + 30 = 90 \text{ W}$

REACTIVE POWER

$$Q_s = \sqrt{s_s^2 - P_s^2} = \sqrt{92^2 - 60^2} = 69.7 \text{ VAR}$$

$$Q_a = \sqrt{s_a^2 - P_a^2} = \sqrt{34.5^2 - 30^2} = 17 \text{ VAR}$$


$$Q_T = Q_s + Q_a = 69.7 + 17 = 86.7 \text{ VAR}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \sqrt{90^2 + 86.7^2} = 125 \text{ VA}$$

LOCKED ROTOR CURRENT = $\frac{S_T}{E} = \frac{125}{23} = 5.44 \text{ A}$


LOCKED ROTOR CURRENT = $\frac{115}{23} \times 5.44 = 27.2 \text{ A}$

SYNCHRONOUS MOTOR CONTROL

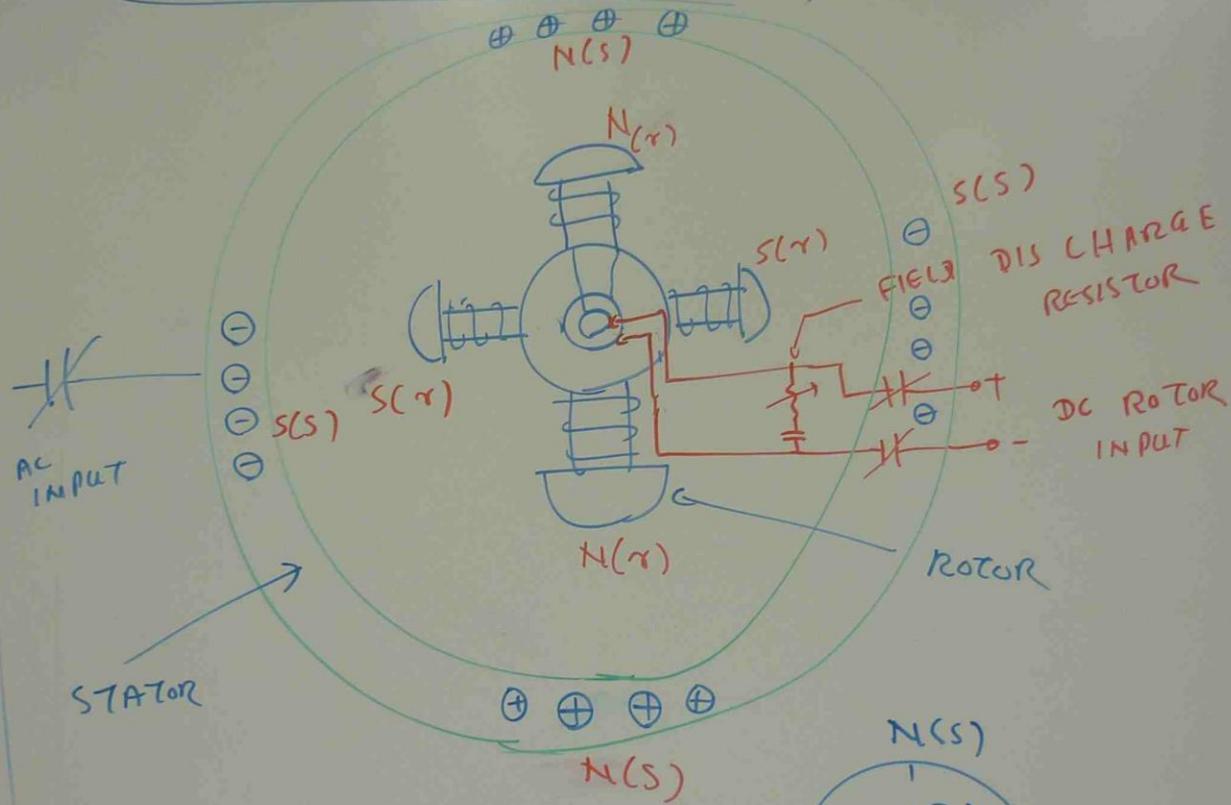


$$P = \frac{E_s \times F_r}{X_s} \sin \delta$$

δ = COUPLING ANGLE

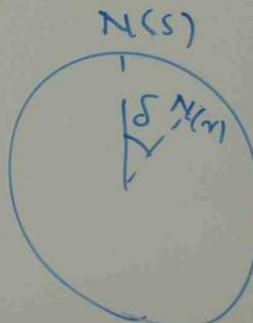

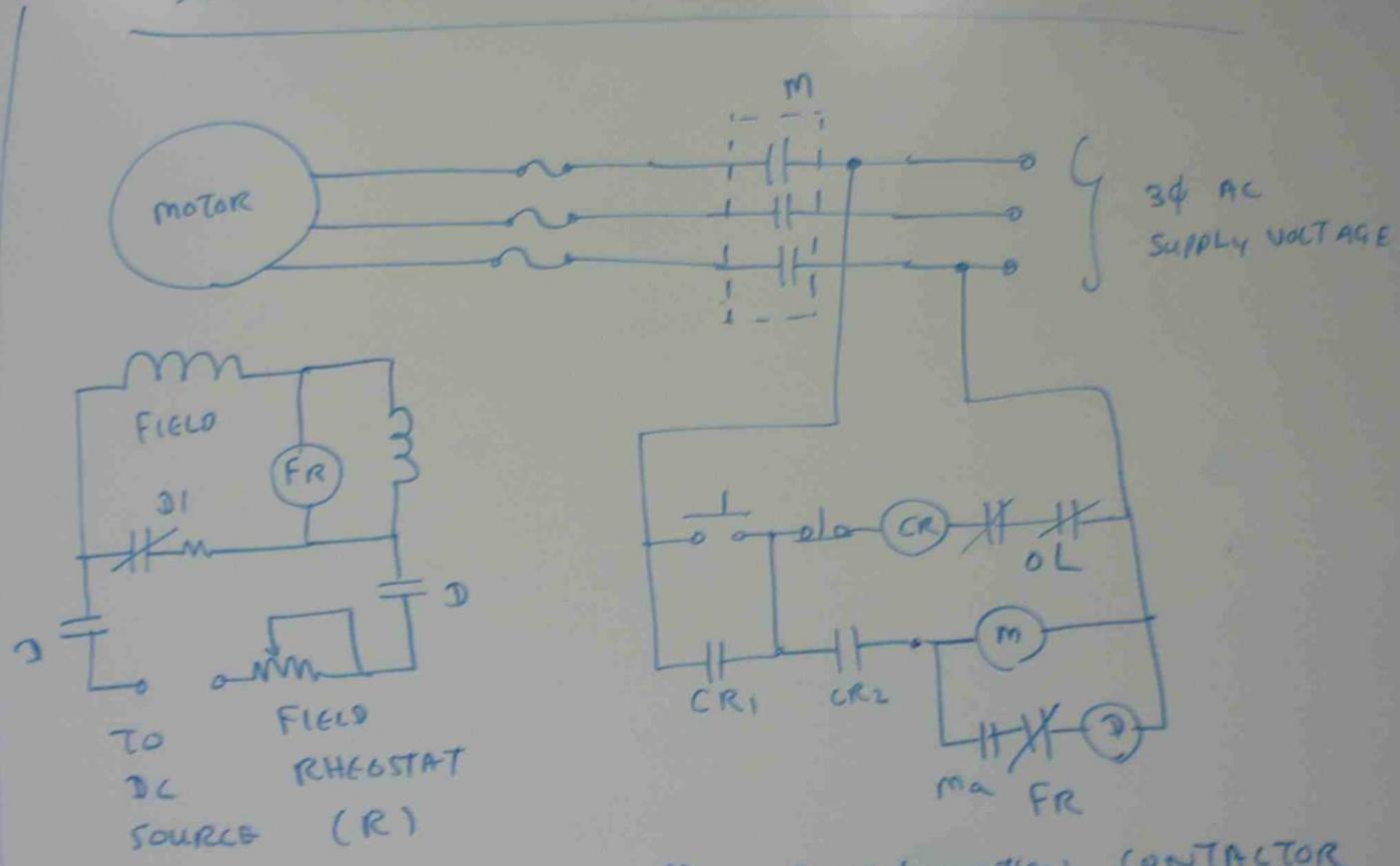STARTER CONNECTION DIAGRAM OF SYNCHRONOUS MOTOR



OPERATION

- (1) WHEN THE START BUTTON IS PRESSED, CR RELAY WILL ENERGIZE CAUSING CONTACT CR₁ AND CR₂. M COIL TO ENERGIZE
- (2) M CONTACTS CLOSE, MOTOR STARTS
- (3) EMF IS INDUCED IN FIELD WINDING
- (4) THE CURRENT WILL FLOW THROUGH THE FIELD.
- (5) IT DEVELOPS THE VOLTAGE ACROSS FR COIL.
FR COIL ENERGIZES AND FR CONTACTS ARE OPEN
M_a IS CLOSED
- (6) THE ROTOR FIELD WILL START TO ROTATE BECAUSE
THE FIELD IS CONNECTED THROUGH D₁.
- (7) AS THE SPEED OF ROTATING FIELD INCREASE
THE VOLTAGE ACROSS FR IS DECREASED.

(8) FR RELAY DROPS OUT

(4) FR CONTACT TO CLOSE


(10) D RELAY ENERGIZES

(11) D, CONTACT OPENS

D CONTACTS CLOSED.

(12) ROTOR FIELD EXcitation

COMB GUTN

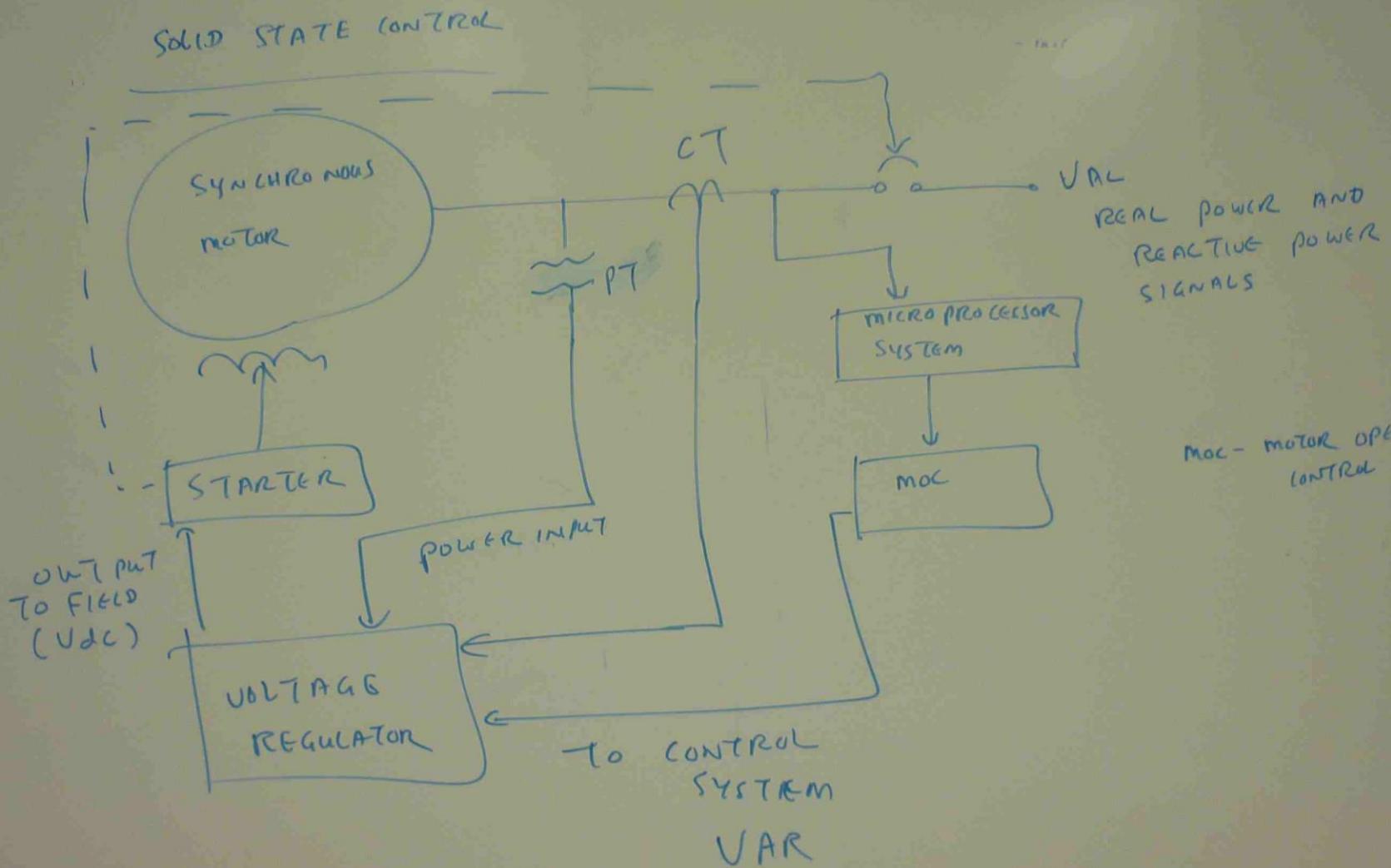


THE MICRO PROCESSOR SENSES OUTPUT ACTIVE & REACTIVE POWER AND PROVIDES THE SUPERVISORY SIGNAL TO MOTOR OPERATED CONTROL MOC. MOC THEN ADJUSTS THE VOLTAGE REGULATOR WHICH CHANGES THE AMOUNT OF FIELD EXCITATION CURRENT.

UNDER EXCITATION CAN DEVELOP LAGGING POWER FACTOR AND OVER EXCITATION CAN DEVELOP LEADING POWER FACTOR OF SYNCHRONOUS MOTOR.

DEPENDING ON THE WHOLE SYSTEM ACTIVE AND REACTIVE POWER FLOW, THE SYNCHRONOUS MOTOR PROVIDES APPROPRIATE POWER FACTOR CORRECTION


EXCITATION SYSTEM WORKING INTO THE FIELD OF A SYNCHRONOUS MOTOR

(SCHEMATIC)

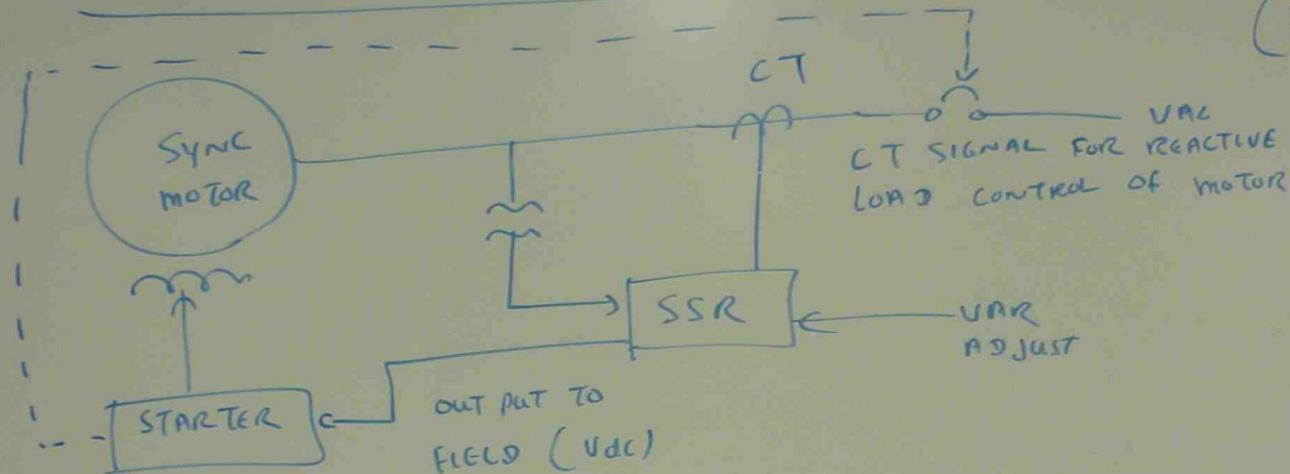

MANUAL VOLTAGE CONTROL WORKING INTO THE FIELD OF
A SYNCHRONOUS MOTOR



(SCHEMATIC)

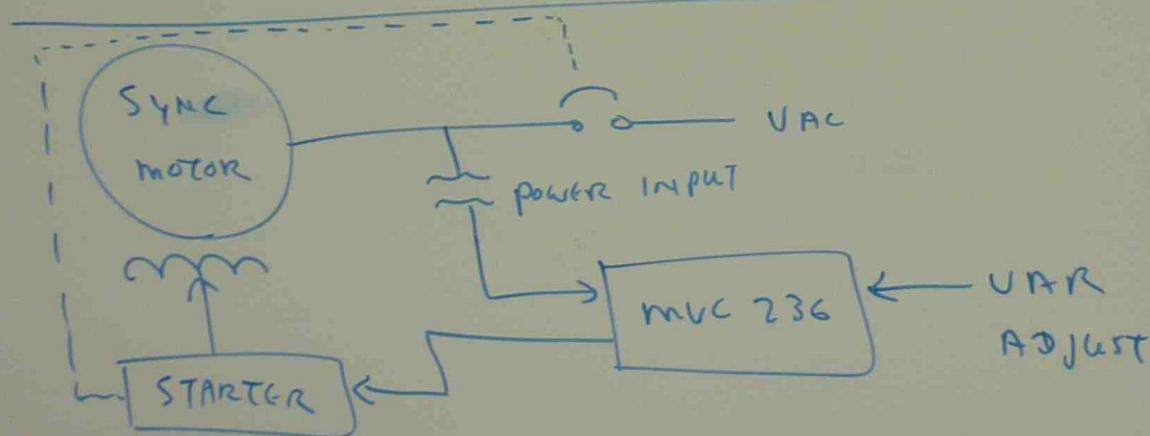



SYNCHRONOUS MOTOR
(SCHEMATIC)

VAR
REACTIVE
OF MOTOR



FIELD OF
(SCHEMATIC)

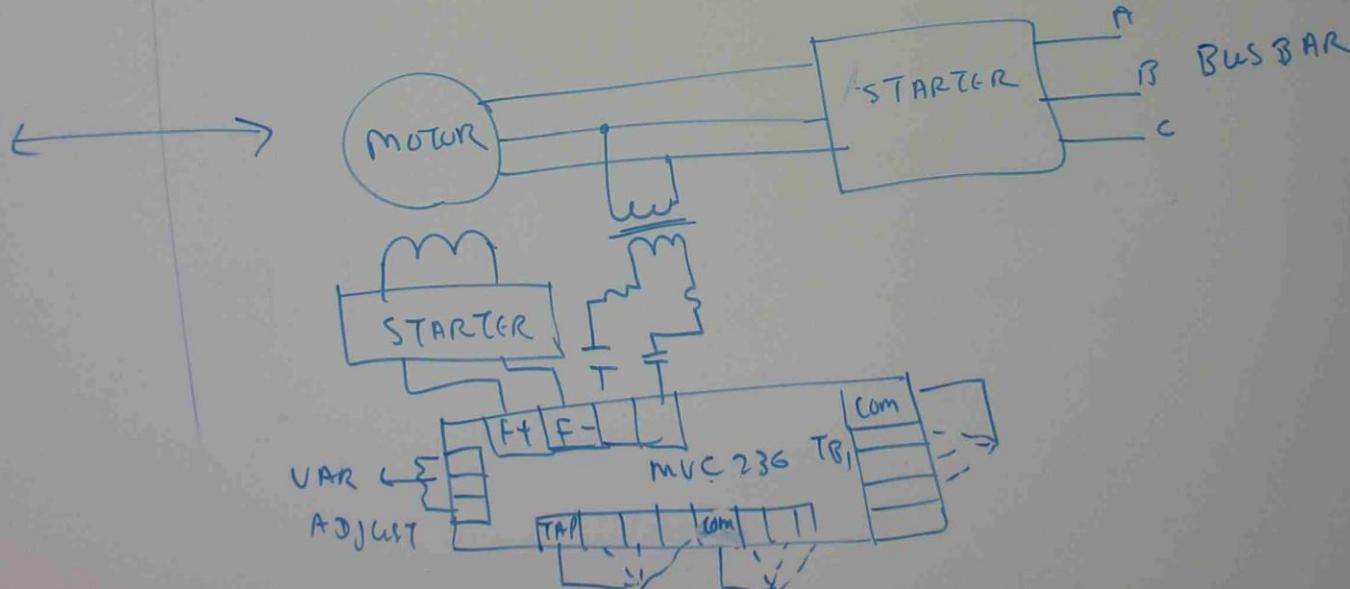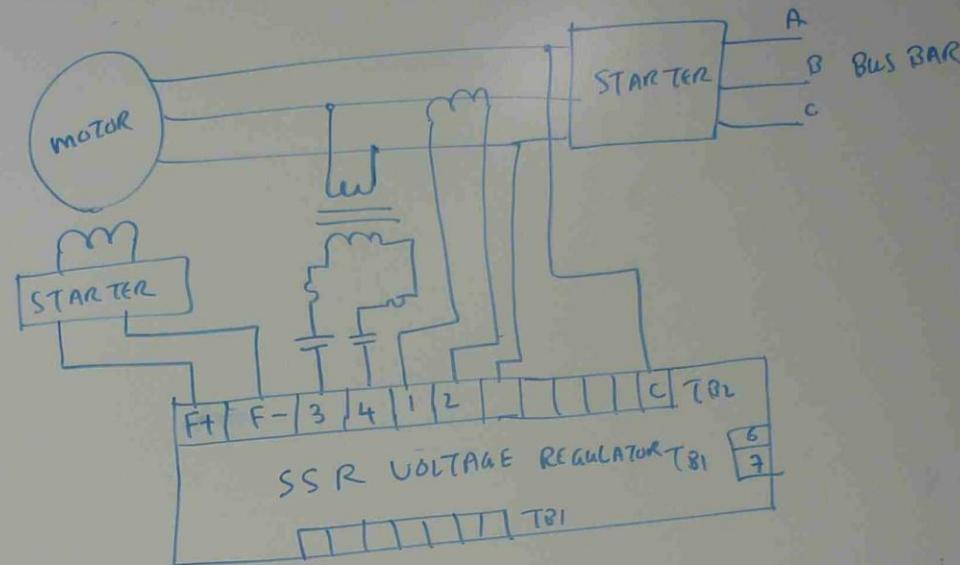


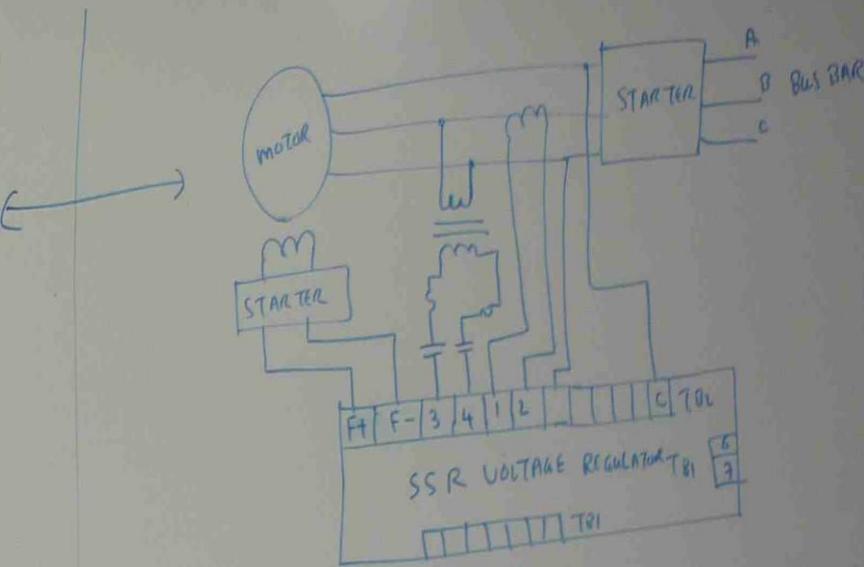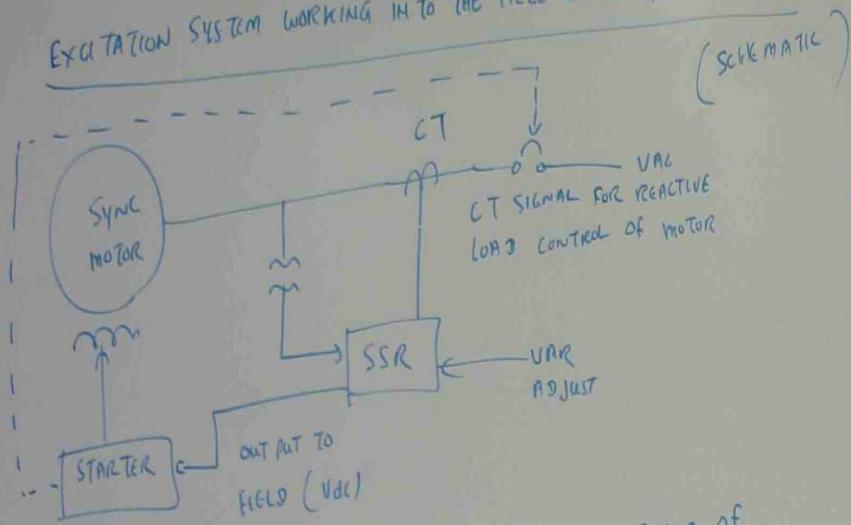EXCITATION SYSTEM WORKING INTO THE FIELD OF A SYNCHRONOUS MOTOR



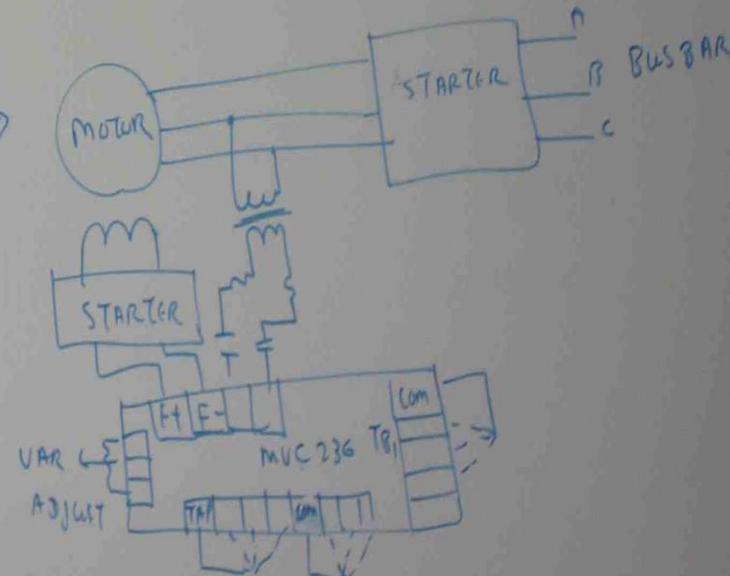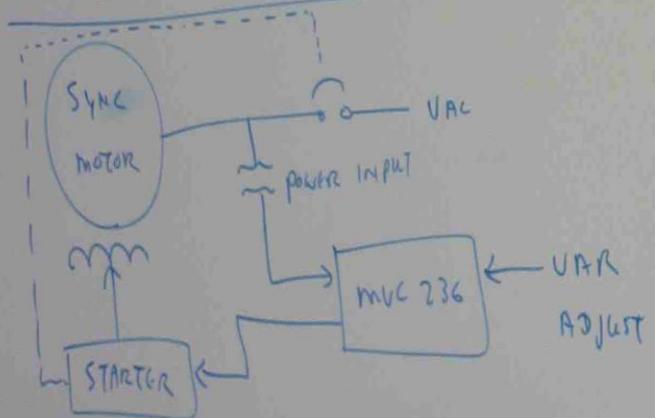MANUAL VOLTAGE CONTROL WORKING INTO THE FIELD OF
A SYNCHRONOUS MOTOR




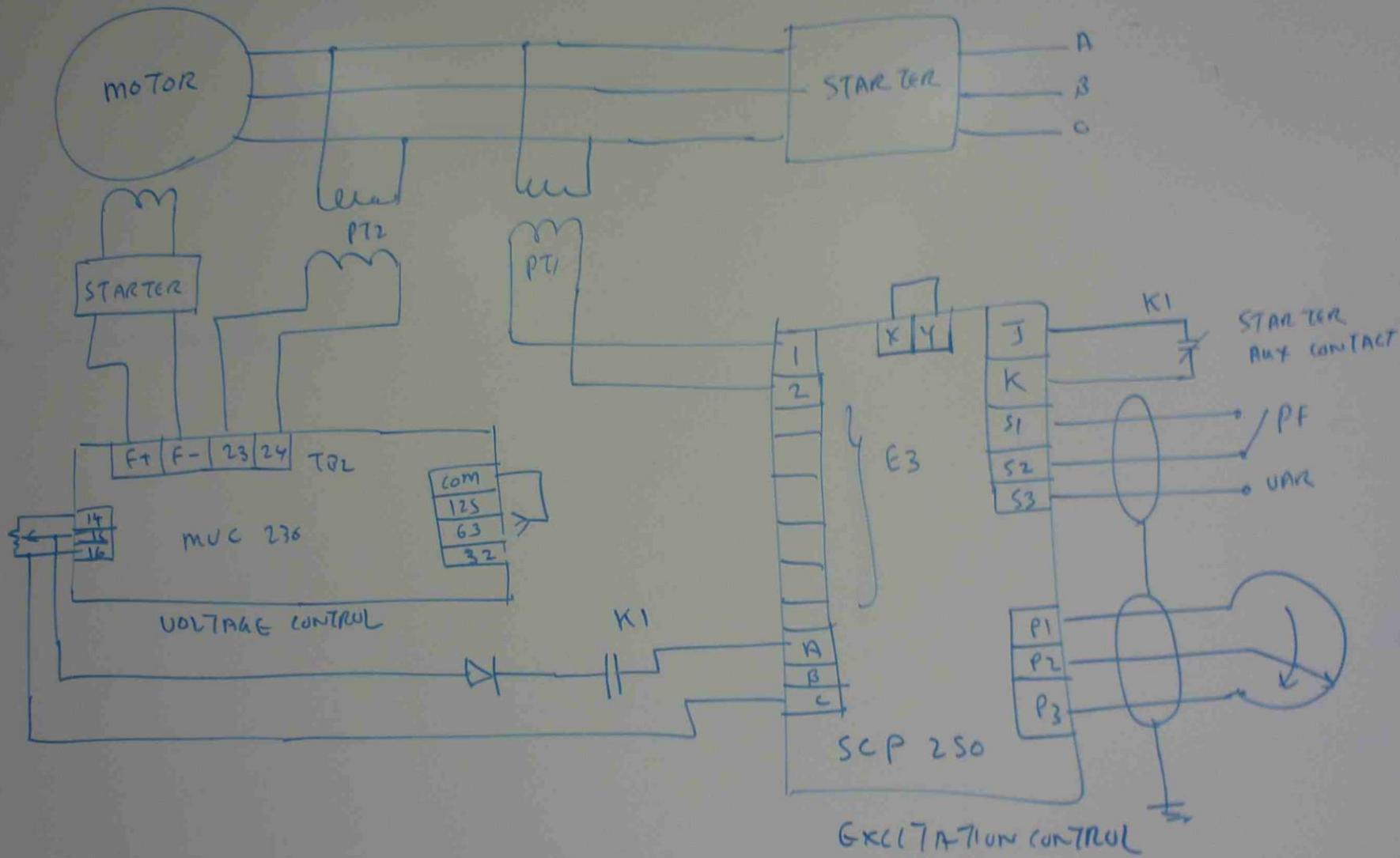


PF CONTROL

TYPIC
POWER

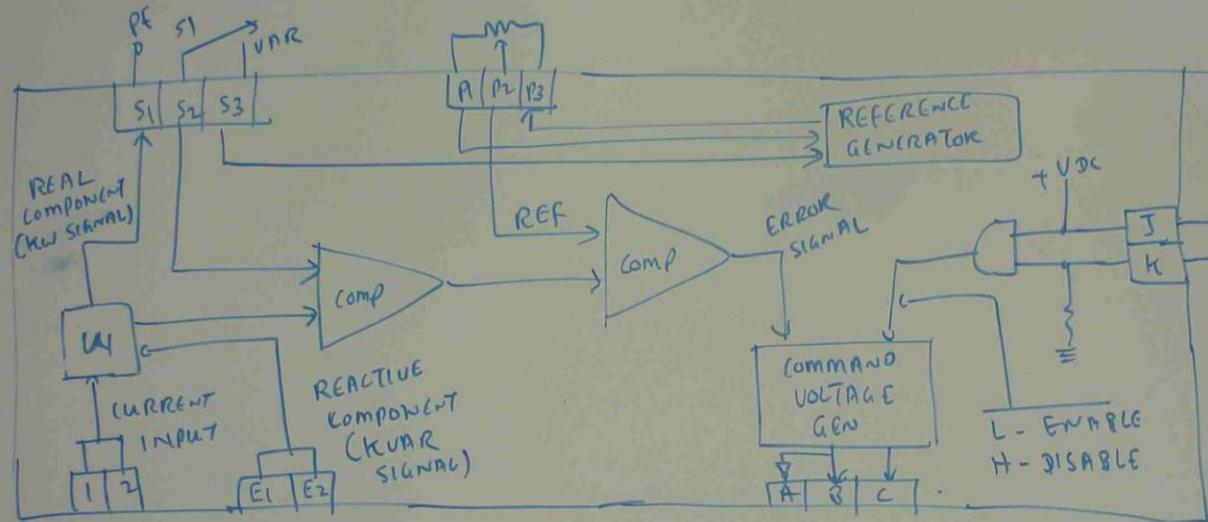EXCITATION CONTROL BLOCK INTERNAL
CONNECTION DIAGRAM (SCP 250)



TER
CONTACT

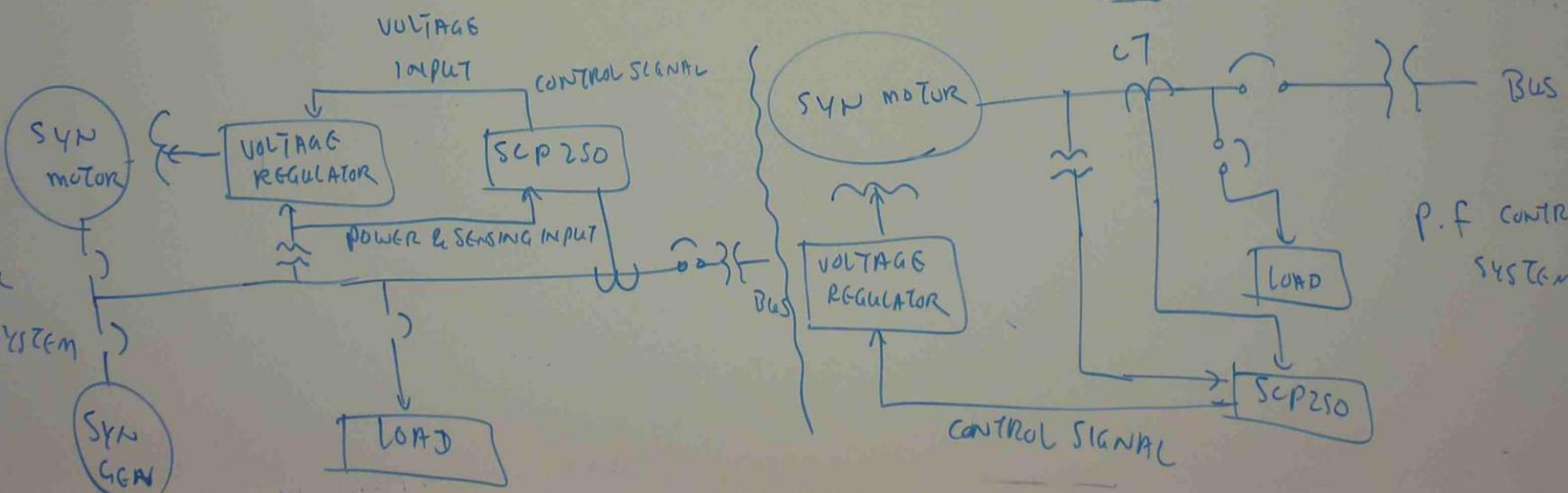

TYPICAL
POWER SYSTEM



P. F
control
system

