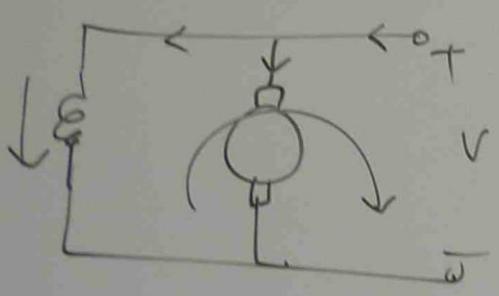



## EFFECT OF CHANGING FLUX AND SPEED ON VOLTAGE

$$E_g \propto \phi N$$

$$\frac{E_{g1}}{E_{g2}} = \frac{\phi_1 N_1}{\phi_2 N_2}$$



DC MOTOR

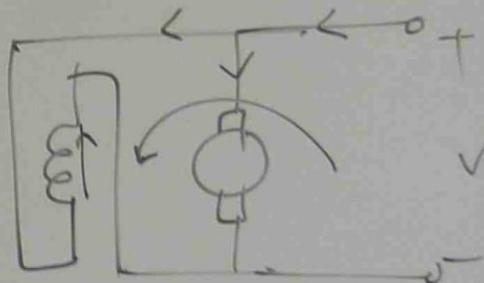

By changing the field connection,  
MOTOR ROTATION DIRECTION CAN BE  
REVERSED.

Pb motor PARTICULARS  $\rightarrow$  3.75 kW, 230V, 10 Amp, 1750 RPM

$R_a = 0.3 \Omega$ , BRUSH DROP = 2V ON LOAD.

CALCULATE

(a) FULL LOAD TORQUE

(b) INITIAL RUSH OF ARMATURE CURRENT AND  
CORRESPONDING TORQUE AT THE INSTANT THE FIELD  
RESISTANCE IS INCREASING TO REDUCE THE  
FIELD FLUX TO 0.96 OF ORIGINAL VALUE

(c) FINAL ARMATURE CURRENT, SPEED AND POWER  
CONSUMPTION

(a)

$$\text{WATT} = \frac{2\pi NT}{60}$$

$$3.75 \times 10^3 = \frac{2 \times 3.1416 \times 1750 \times T}{60}$$


$$T = \frac{3.75 \times 10^3 \times 60}{2 \times 3.1416 \times 1750} = 20.47 \text{ N-m}$$

(b)

$$T = k \phi I_a$$

MOTOR TORQUE
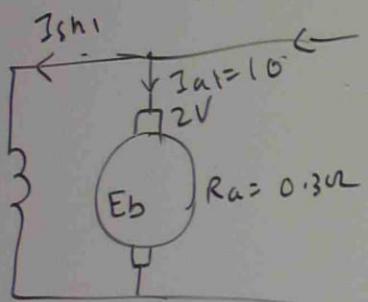
$$\frac{T_1}{T_2} = \frac{\phi_1 I_{a1}}{\phi_2 I_{a2}}$$



$$I_{FL} = \frac{\text{POWER}}{\text{VOLTAGE}}$$

$$= \frac{3750}{230} \\ = 16.3 \text{ Amp.}$$

$$I_{sh1} = 16.3 - 10 = 6.3 \text{ Amp.}$$

FLUX FLUX IS REDUCED

$$R_{\text{Brush}} = \frac{2V}{I_a} \\ = \frac{2}{10} = 0.2 \Omega$$

$$E_{b1} = V - (I_a R_a + R_{\text{Brush}} + \text{Drop}) \\ = 230 - (10 \times 0.3 + 2) \\ = 228 \text{ V}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\frac{225}{E_{b2}} = \frac{\phi_1 \times N_1}{0.96 \phi_1 \times N_2}$$

$$E_{b2} = 0.96 \times 225 \\ = 216 \text{ V}$$

$$E_{b2} = V - (I_{a2} R_a + \text{Brush Drop})$$

$$216 = 230 - (I_{a2} \times 3 + I_{a2} \times R_b)$$

$$216 = 230 - (I_{a2} \times 0.3 + I_{a2} \times 0.2)$$

$$0.5 I_{a2} = 230 - 216 = 14$$

$$I_{a2} = \frac{14}{0.5} = 28 \text{ Amp.}$$

$$\frac{T_1}{T_2} = \frac{\phi_1 \tau_{a1}}{\phi_2 \tau_{a2}}$$

$$\frac{20.467}{T_2} = \frac{\phi_1}{0.96\phi_1} \times \frac{10}{22}$$

$$T_2 = \frac{20.467 + 0.96 \times 22}{10}$$

$$55 \text{ N-m}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\frac{225}{216} = \frac{\phi_1 \times 1750}{0.96 \phi_1 \times N_2}$$

$$N_2 = \frac{216 \times 1750}{225 \times 0.96}$$

$$= 1750 \text{ RPM}$$

$$P = 2\pi N_2 T$$

$$= \frac{2 \times 3.1416 \times 1750 \times 55}{60}$$

$$= 10079 \text{ WATT}$$

$$= 10.079 \text{ kW } \times$$

7.46 kW, 230V, 1750 RPM SHUNT MOTOR.

ARMATURE RESISTANCE 0.35Ω. SHUNT FIELD  
RESISTANCE 62.2Ω.

(a) NO LOAD CURRENT IS 7.7 AMP. FULL LOAD  
EFFICIENCY 86%. BRUSH DROP 3 VOLT AT  
FULL LOAD

CALCULATE % REGULATION

) A 2.65Ω RESISTANCE IS PLACED IN  
SERIES WITH ARMATURE CIRCUIT, CALCULATE


NEW SPEED, % REGULATION, % POWER

LOSS IN SERIES RESISTANCE IN RESPECT  
OF TOTAL POWER INPUT.

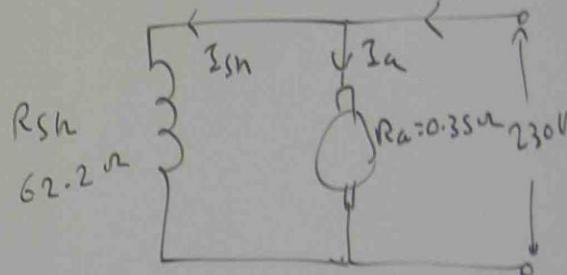(a)  $I_{FL} = \frac{\text{OUTPUT POWER}}{\text{VOLTAGE} \times \text{EFFICIENCY}}$

$$= \frac{7.46 \times 10^3}{230 \times 0.86}$$

$$= 37.7 \text{ AMP.} \quad 37.7 \text{ AMP} = I_{FL}$$



$$I_{sh} = \frac{V}{R_{sh}} = \frac{230}{62.2} = 3.7 \text{ AMP.}$$

$$I_a = I_{FL} - I_{sh} = 37.7 - 3.7 = 34 \text{ AMP}$$

$$N_{FL} = 1750 \text{ RPM}$$

$$I_{aFL} = 34 \text{ Amp}$$

$$N_{NL} = ?$$

$$\begin{aligned} I_{aNL} &= I_{NL} - I_{SN NL} \\ &= 7.7 - 3.7 \\ &= 4 \text{ Amp.} \end{aligned}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\frac{V - (I_{aFL} R_{at} + \text{BRUSH DROP})}{V - (I_{aNL} R_{at} + \text{BRUSH DROP})} = \frac{\phi_1 N_1}{\phi_2 N_2} \quad \phi_1 = \phi_2$$

$$\frac{230 - (34 \times 0.35 + 3)}{230 - (4 \times 0.35 + 3)} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\frac{215.1}{225.6} = \frac{1750}{N_2}$$

$$N_2 = \frac{1750 \times 225.6}{215.1} = 1850 \text{ RPM}$$

$$\% \text{ SPEED REGULATION} = \frac{N_{NL} - N_{FL}}{N_{FL}} \times 100$$

$$\begin{aligned} &= \frac{1250 - 1750}{1750} \times 100 \\ &= 5.7\% \end{aligned}$$

(b)

$$E_{b_3} = V - (I_a R_a + \text{BRUSH} + \text{PROP})$$

$$= 230 - [34(0.35 + 2.65) + 3]$$

$$= 125 \text{ V}$$

$$\frac{E_{b_2}}{E_{b_3}} = \frac{d_2 N_2}{d_3 N_3}$$

$$\frac{225.6}{125} = \frac{1850}{N_3}$$

$$N_3 = \frac{1850 \times 125}{225}$$

$$= 1020 \text{ RPM}$$

$$\% \text{ REGA} = \frac{N_{NL} - N_3}{N_3} \times 100$$

$$= \frac{1850 - 1020}{1020} \times 100 \\ = 61.3\%$$

$$2.65 \text{ per unit power loss} = I_a^2 \times 2.65$$

$$= 34^2 \times 2.65 = 3060 \text{ W}$$

$$\% \text{ of power input} = \frac{3060}{V_L \times I_{FL}} \times 100$$

$$= \frac{3060}{230 \times 37.7} \times 100 = 39.2\%$$

7.46 kW, 230V, 1750 RPM SHUNT MOTOR.

ARMATURE RESISTANCE 0.35Ω. SHUNT FIELD  
RESISTANCE 62.2Ω.

(a) NO LOAD CURRENT IS 7.7 AMP. FULL LOAD  
EFFICIENCY 86%. BRUSH DROP 3 VOLT AT

FULL LOAD


CALCULATE % REGULATION

) A 2.65Ω RESISTANCE IS PLACED IN  
SERIES WITH ARMATURE CIRCUIT, CALCULATE  
NEW SPEED, % REGULATION, % POWER  
LOSS IN SERIES RESISTANCE IN RESPECT  
OF TOTAL POWER INPUT.

$$(a) I_{FL} = \frac{\text{OUTPUT POWER}}{\text{VOLTAGE} \times \text{EFFICIENCY}}$$

$$= \frac{7.46 \times 10^3}{230 \times 0.86}$$

$$= 37.7 \text{ Amp.}$$

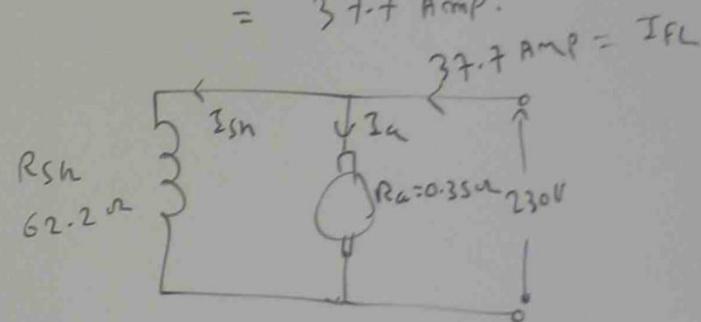

$$I_{sh} = \frac{V}{R_{sh}} = \frac{230}{62.2} = 3.7 \text{ Amp.}$$

$$I_a = I_{FL} - I_{sh} = 37.7 - 3.7 = 34 \text{ Amp}$$

$$N_{FL} = 1750 \text{ RPM}$$

$$I_{aFL} = 34 \text{ Amp}$$

$$N_{NL} = ?$$

$$\begin{aligned} I_{aNL} &= I_{NL} - I_{aNL} \\ &= 7.7 - 3.7 \\ &= 4 \text{ Amp} \end{aligned}$$

$$\frac{E_{t1}}{E_{t2}} = \frac{q_1 N_1}{q_2 N_2}$$

$$\frac{V - (I_{aFL} R_{at} + \text{BUSH DROP})}{V - (I_{aNL} R_{at} + \text{BUSH DROP})} = \frac{q_1 N_1}{q_2 N_2}$$

$$q_1 = q_2$$

$$\frac{230 - (34 \times 0.35 + 3)}{230 - (4 \times 0.35 + 3)} = \frac{q_1 N_1}{q_2 N_2}$$

$$\% \text{ SPEED REGULATION} = \frac{N_{NL} - N_{FL}}{N_{FL}} \times 100$$

$$\frac{215-1}{223.6} = \frac{1750}{N_2}$$

$$\begin{aligned} &= \frac{1750 - 1750}{1750} \times 100 \\ &= 3.7\% \end{aligned}$$

$$N_2 = 1750 \times \frac{223.6}{215-1} \approx 1830 \text{ RPM}$$

(b)

$$E_{b3} = V - (I_a R_a + \text{BRUSH DROP})$$

$$= 230 - [34(0.35 + 2.65) + 3]$$

$$= 125 \text{ V}$$

$$\frac{E_{b2}}{E_{b3}} = \frac{\phi_2 N_2}{\phi_3 N_3}$$

$$\frac{225.6}{125} = \frac{1850}{N_3}$$

$$N_3 = \frac{1850 \times 125}{225}$$

$$= 1020 \text{ RPM}$$

$$\% \text{ REG} = \frac{N_{NL} - N_3}{N_3} \times 100$$

$$= \frac{1850 - 1020}{1020} \times 100$$

$$= 61.3\%$$

$$2.65 \Omega \text{ power loss} = I_a^2 \times 2.65$$

$$= 34^2 \times 2.65 = 3060 \text{ W}$$

$$\% \text{ of power input} =$$

$$\frac{3060}{V_I \times I_{FL}} \times 100$$

$$= \frac{3060}{230 \times 37.7} \times 100 = 37.2\%$$