
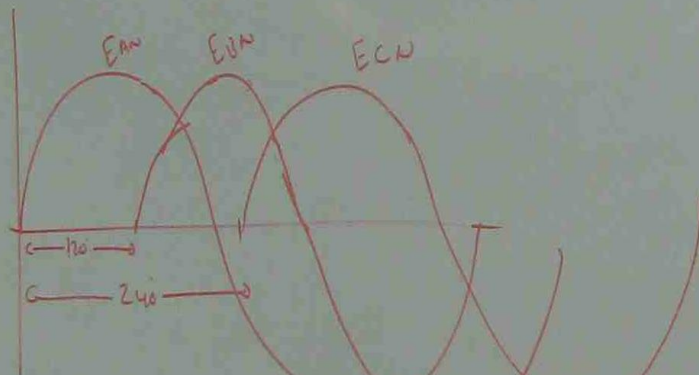
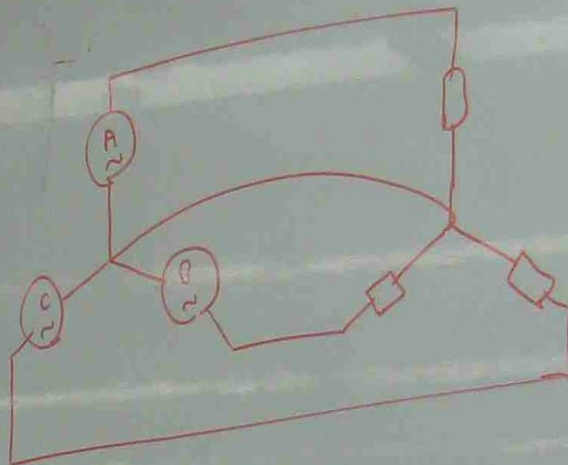


Exercise

CONSTRUCT A PHASOR DIAGRAM OF TWO  
VECTORS  $V_{CN} = 200 \angle 120^\circ$  V AND  
 $V_{BN} = 200 \angle -120^\circ$  V  
WHERE N IS COMMON TO BOTH  
ORIGINAL VOLTAGES.

FIND THE MAGNITUDE AND ANGLE OF  
VOLTAGE  $V_{BC}$

### 3 $\phi$ VOLTAGE GENERATION

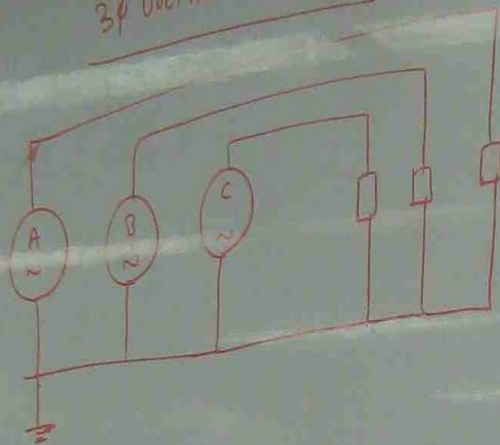

$$e_A = E_{AN} \sin \omega t \longrightarrow E \angle 0$$

$$e_B = E_{BN} \sin (\omega t - 120) \longrightarrow E \angle -120$$

$$e_C = E_{CN} \sin (\omega t - 240) \longrightarrow E \angle -240$$

$$E_{AN} + E_{BN} + E_{CN} = E \angle 0 + E \angle -120 + E \angle 120$$


$$= E (\cos 0 + j \sin 0) + E (\cos 120 - j \sin 120) + E (\cos 120 + j \sin 120)$$

$$= E (1 + j0) + E (-0.5 + j0.866) + E (0.5 - j0.866)$$

$$= 0$$

3 $\phi$  STAR

MODEL TO

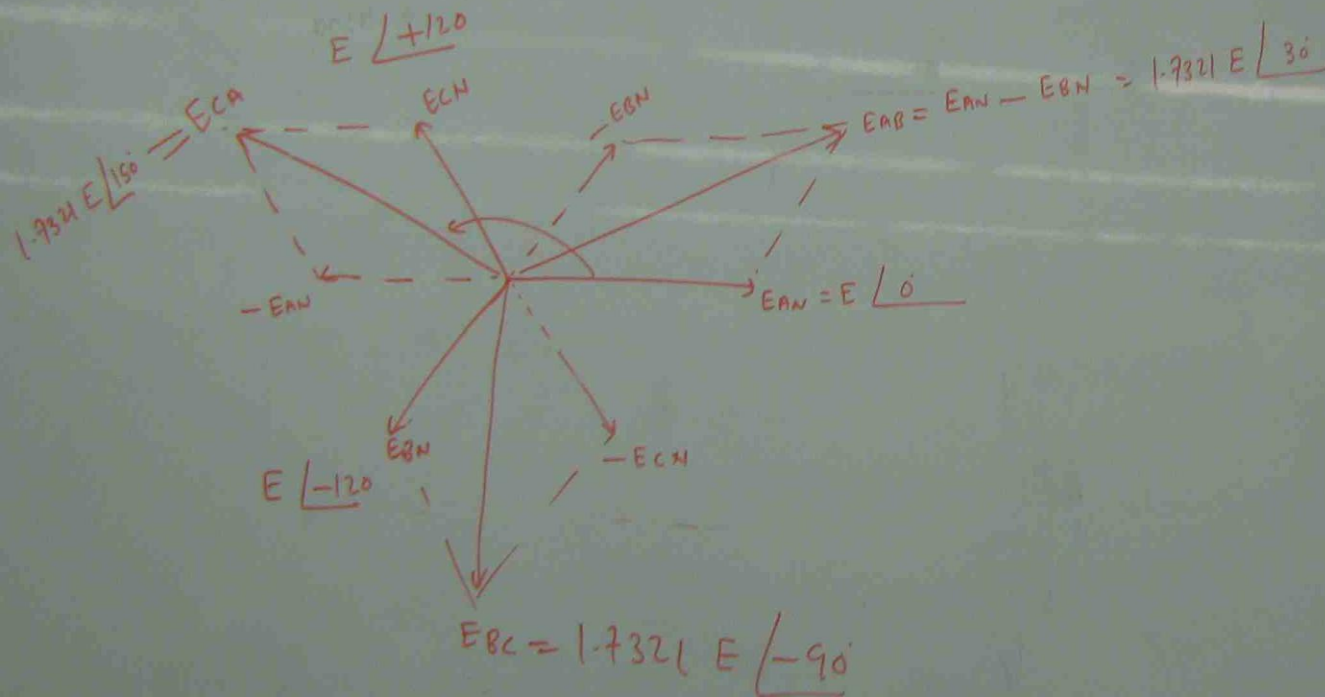

$$E_{AN} = E \angle 0$$

$$E_{BN} = E \angle -120$$

$$E_{CN} = E \angle +120$$

$$E_{AB} = 1.7321 E \angle 30$$


$$E_{BC} = 1.7321 E \angle -90$$

$$E_{CA} = 1.7321 E \angle +150$$




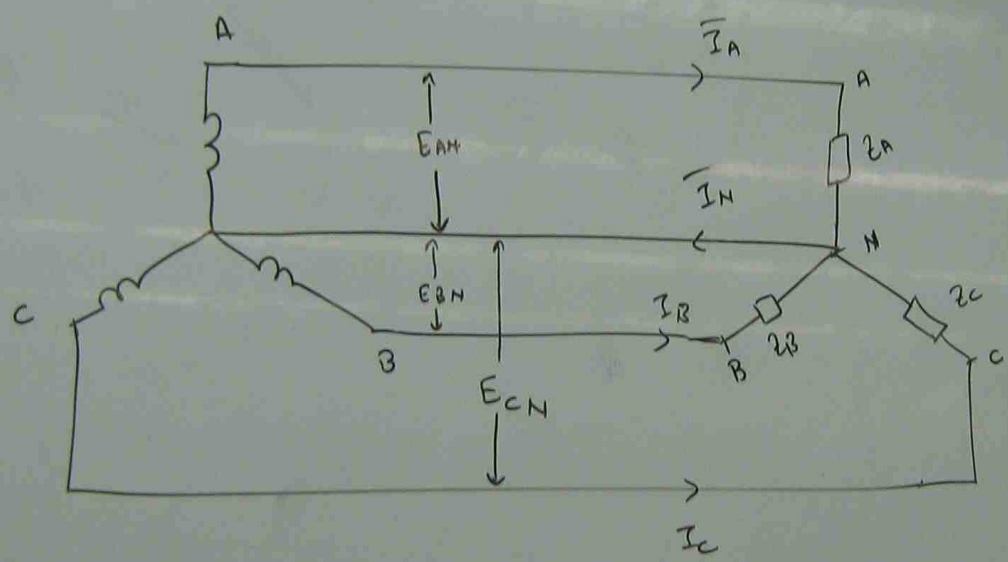
# CALCULATION OF CURRENTS IN STAR CONNECTED BALANCED LOAD



GENERATOR

LOAD

$$I_A = \frac{E_{AN}}{Z_A} = \frac{E \angle 0}{Z_A \angle \theta} = \frac{E}{Z_A} \angle -\theta$$

$$I_B = \frac{E_{BN}}{Z_B} = \frac{E \angle -120}{Z_B \angle \theta} = \frac{E}{Z_B} \angle -120 - \theta$$

$$I_C = \frac{E_{CN}}{Z_C} = \frac{E \angle -240}{Z_C \angle \theta} = \frac{E}{Z_C} \angle -240 - \theta$$

$$I_N = I_A + I_B + I_C = 0$$

← Polar/Rectangular Conversions  
(Some Pb in Network)

THEVENIN'S THEOREM  
SUPERPOSITION  
THEOREM

X-Δ TRANSFORMATION



POWER  
SYSTEM  
ANALYSIS

FAULT  
CALCULATION

24/3/09 T1

PRACTICAL AFTER TEST

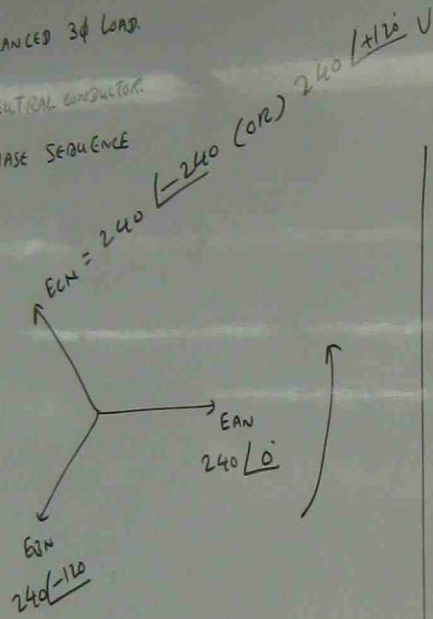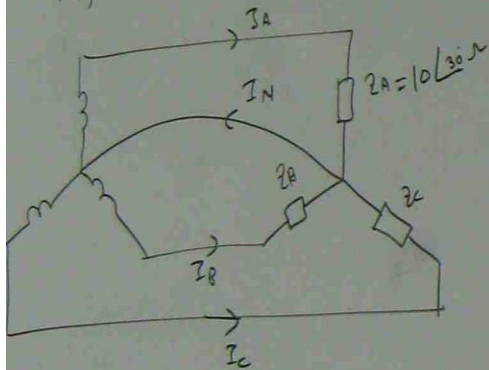ph  
A 4 WIRES 3 $\phi$  SUPPLY IS CONNECTED TO A BALANCED 3 $\phi$  LOAD.  
THE CONNECTION BEING THE THREE PHASE PLUS A NEUTRAL CONDUCTOR.  
IF  $V_{AN} = 240 \angle 0^\circ$   $Z_A = 10 \angle 30^\circ \Omega$ . PHASE SEQUENCE  
ABC, FIND  $I_A, I_B, I_C$  AND  $I_N$



$$I_A = \frac{E_{AN}}{Z_A} = \frac{240 \angle 0^\circ}{10 \angle 30^\circ} = 24 \angle 0 - 30 = 24 \angle -30^\circ \text{ A}$$


$$I_B = \frac{E_{BN}}{Z_B} = \frac{240 \angle -120^\circ}{10 \angle 30^\circ} = 24 \angle -120 - 30 = 24 \angle -150^\circ \text{ A}$$

$$I_C = \frac{E_{CN}}{Z_C} = \frac{240 \angle +120^\circ}{10 \angle 30^\circ} = 24 \angle 120 - 30 = 24 \angle 90^\circ \text{ A}$$

$$\begin{aligned} I_N &= I_A + I_B + I_C \\ &= 24 \angle -30^\circ + 24 \angle -150^\circ + 24 \angle 90^\circ \\ &= 24 (\cos(-30^\circ) + j \sin(-30^\circ)) + 24 (\cos(-150^\circ) + j \sin(-150^\circ)) \\ &\quad + 24 (\cos 90^\circ + j \sin 90^\circ) \end{aligned}$$


$$= 20.78 - j12 + (-20.78 - j12) + j24$$

$$= 0$$

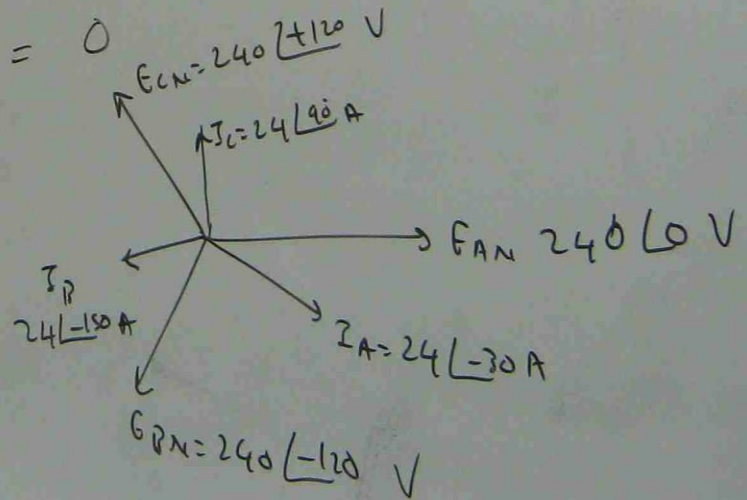



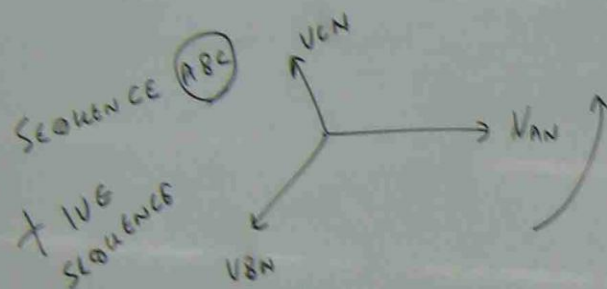
# EFFECT OF PHASE REVERSAL ON STAR LOAD CURRENTS



$$V_{AN} = V \angle 0$$

$$V_{BN} = V \angle -120$$

$$V_{CN} = V \angle +120$$

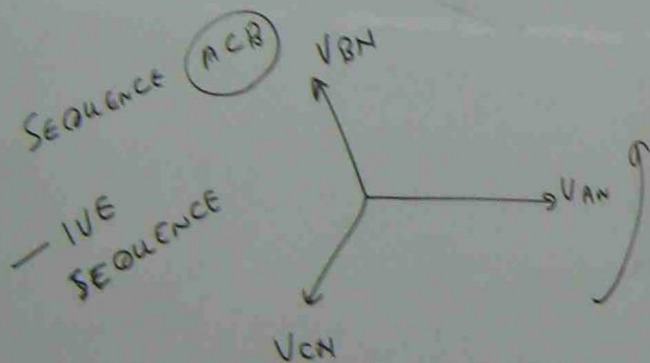

$$V_{AN} = V \angle 0$$

$$V_{BN} = V \angle +120$$

$$V_{CN} = V \angle -120$$


IF NEGATIVE SEQUENCE HAPPENS IN PREVIOUS PROBLEM, DETERMINE

THE PHASOR DIAGRAM OF LINE CURRENTS.

$$V_{AN} = 240 \angle 0$$

$$Z_A = 10 \angle 30 \Omega$$

NEGATIVE SEQUENCE  $\rightarrow$  ACB

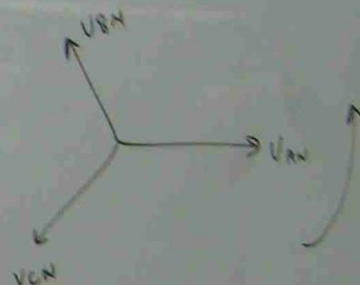

$$V_{AN} = V \angle 0 = 240 \angle 0$$


$$V_{CN} = 240 \angle -120$$

$$V_{BN} = 240 \angle +120$$

$$I_A = \frac{V_{AN}}{Z_A} = \frac{240 \angle 0}{10 \angle 30} = 24 \angle 0-30 = 24 \angle -30^\circ \text{ A}$$

$$I_B = \frac{V_{BN}}{Z_B} = \frac{240 \angle 120}{10 \angle 30} = 24 \angle 120-30 = 24 \angle 90^\circ \text{ A}$$
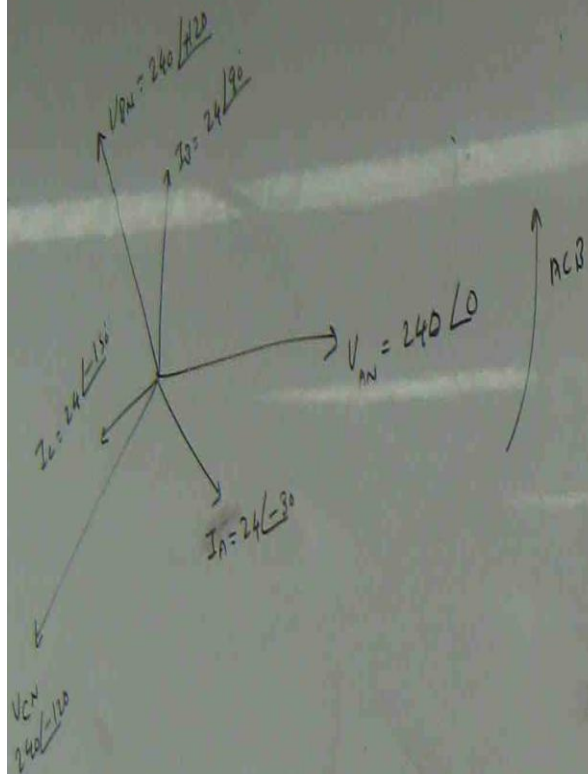
$$I_C = \frac{V_{CN}}{Z_C} = \frac{240 \angle -120}{10 \angle 30} = 24 \angle -120-30 = 24 \angle -150^\circ \text{ A}$$



### HOME WORK EXERCISE

- ① 3 IDENTICAL IMPEDANCES OF  $17 \angle -30^\circ \Omega$  ARE CONNECTED TO A 415V 3 $\phi$  4 WIRE SUPPLY. THE LOAD IS CONNECTED IN STAR AND PHASE SEQUENCE IS ABC. FIND THE LINE CURRENT AND DRAW THE PHASOR DIAGRAM.