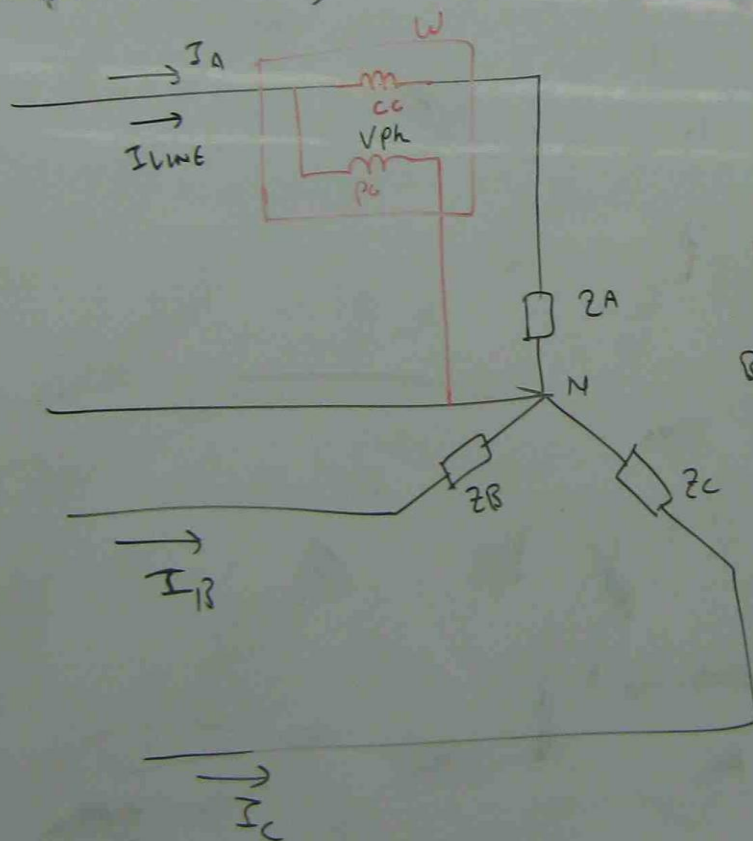


# CALCULATION OF POWER IN STAR CONNECTED BALANCED LOAD

## POWER MEASUREMENT BY ONE WATT METER METHOD

3 $\phi$  BALANCED LOAD  $\rightarrow$  TOTAL 3 $\phi$  POWER = 3 $\times$  1 $\phi$  POWER



CC - CURRENT COIL  
PC - POTENTIAL COIL  
W - WATT METER

BALANCED

3 $\phi$  POWER = 3 $\times$  WATT METER READING  
BALANCED

$$V_{PHASE} = \frac{V_{LINE}}{\sqrt{3}}$$

$$I_{LINE} = I_{PH}$$

$$1\phi \text{ POWER} = V_{PH} I_{PH} \cos \phi$$


$$1\phi \text{ POWER} = \frac{V_{LINE}}{\sqrt{3}} \times I_{LINE} \times \cos \phi$$

$$3\phi \text{ POWER} = 3 \times 1\phi \text{ POWER}$$

$$= 3 \times \frac{V_{LINE}}{\sqrt{3}} \times I_{LINE} \cos \phi$$

$$3\phi \text{ POWER} = \sqrt{3} V_{LINE} \times I_{LINE} \cos \phi$$

# POWER TRIANGLE

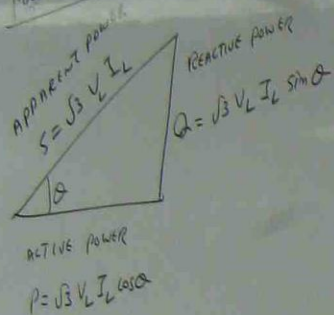

IN 3 $\phi$  SYSTEM THE FOLLOWINGS ARE VOLTAGE AND CURRENT

$$I_A = 24 \angle -30^\circ \text{ A}, I_B = 24 \angle -150^\circ \text{ A}, I_C = 24 \angle 90^\circ \text{ A}$$

$$V_{AN} = 240 \angle 0^\circ \text{ V}, V_{BN} = 240 \angle -120^\circ \text{ V}, V_{CN} = 240 \angle +120^\circ \text{ V}$$



FIND TOTAL POWER IN TWO WAYS.

## METHOD (1)

$$P_{\text{TOTAL}} = 3 P_{\text{ph}} = 3 V_{\text{ph}} I_{\text{ph}} \cos \phi$$

$$= 3 V_{AN} I_{AN} \cos \phi$$

$$I_{AN} = I_A = 24 \text{ A}$$

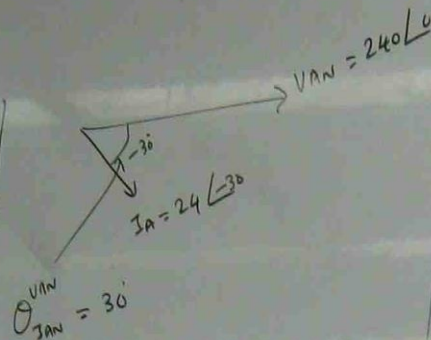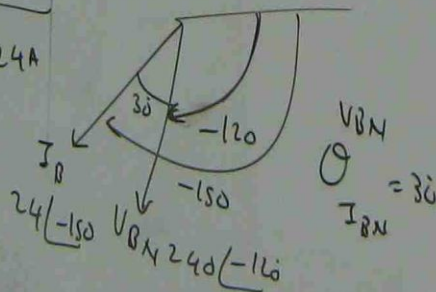

$$P_A = 240 \times 24 \cos 30^\circ$$


$$= 5760 \times 0.866$$

$$P_A = 4988 \text{ W}$$

$$P_B = V_{BN} I_{BN} \cos \phi$$

$$P_B = 240 \times 24 \cos 30^\circ$$

$$= 4988 \text{ W}$$

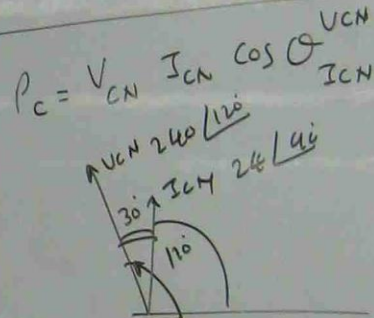

$$P_C = V_{CN} I_{CN} \cos \phi$$

$$= 240 \times 24 \times \cos 30^\circ$$

$$P_C = 4988 \text{ W}$$

$$P_T = P_A + P_B + P_C = 4988 + 4988 + 4988$$

$$= 14964 \text{ W}$$


## METHOD (2)

$$P_T = \sqrt{3} V_{\text{LINE}} I_{\text{LINE}} \cos \phi$$


$$= 1.7321 \times (\sqrt{3} V_{\text{ph}}) \times 24 \times \cos 30^\circ$$

$$= 1.7321 (1.7321 \times 240) \times 24 \times 0.866$$

$$= 14964 \text{ W}$$

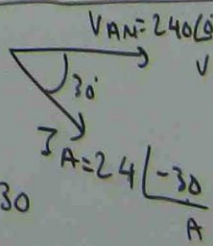

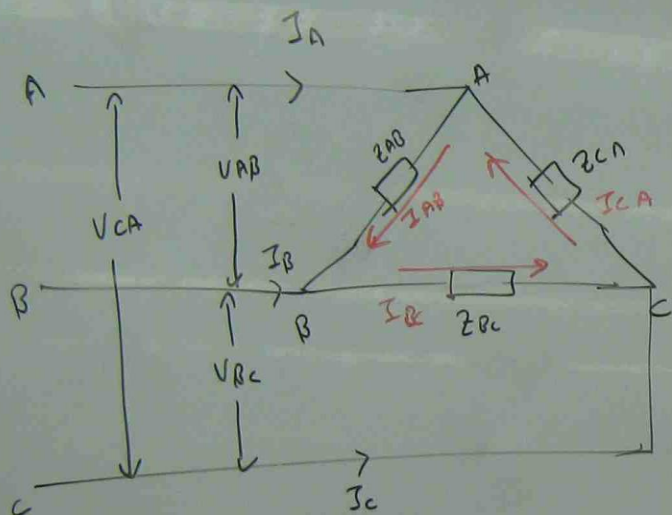
# THREE PHASE DELTA CONNECTED BALANCED LOADS



SEQUENCE

A B C

A → B → C

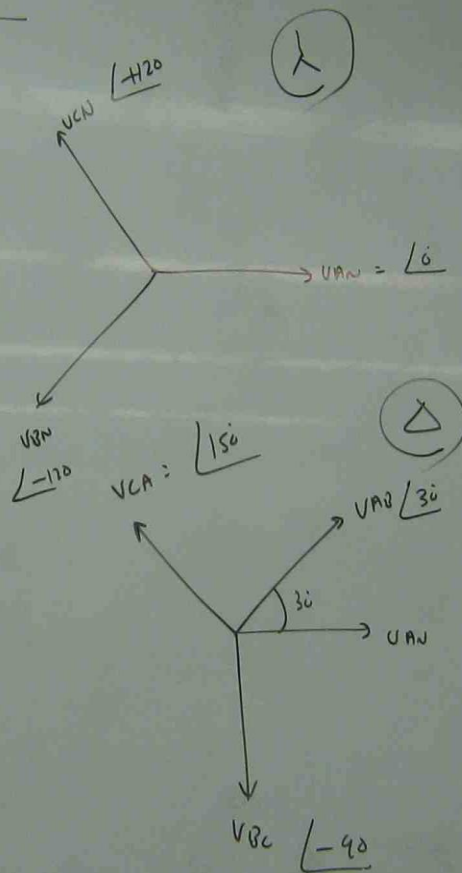

$$I_{AB} = \frac{V_{AB}}{Z_{AB}}$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}}$$

A POINT

$$I_A + I_{CA} = I_{AB}$$

$$I_A = I_{AB} - I_{CA}$$

B POINT

$$I_B + I_{AB} = I_{BC}$$

$$I_B = I_{BC} - I_{AB}$$

C POINT

$$I_C + I_{BC} = I_{CA}$$

$$I_C = I_{CA} - I_{BC}$$



Ph 3d 3WIRE 415V ABC SYSTEM SUPPLIES A  $\Delta$  CONNECTED LOAD WHOSE PHASE IMPEDANCE IS  $60 \angle 45^\circ \Omega$ .  
FIND PHASE CURRENT & LINE CURRENT.  
DRAW PHASOR DIAGRAM.

METHOD 1)  
 $Z_{AB} = Z_{BC} = Z_{CA} = 60 \angle 45^\circ \Omega$

$$V_{AB} = 415 \angle 30^\circ \text{ V}$$

$$V_{BC} = 415 \angle -90^\circ \text{ V}$$

$$V_{CA} = 415 \angle +150^\circ \text{ V}$$


$$I_{AB} = \frac{V_{AB}}{Z_{AB}} = \frac{415 \angle 30^\circ}{60 \angle 45^\circ} = 6.9 \angle 30 - 45 = 6.9 \angle -15^\circ \text{ A}$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}} = \frac{415 \angle -90^\circ}{60 \angle 45^\circ} = 6.9 \angle -90 - 45 = 6.9 \angle -135^\circ \text{ A}$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}} = \frac{415 \angle 150^\circ}{60 \angle 45^\circ} = 6.9 \angle 150 - 45 = 6.9 \angle 105^\circ \text{ A}$$

$$I_A = I_{AB} - I_{CA} = 6.9 \angle -15^\circ - 6.9 \angle 105^\circ$$
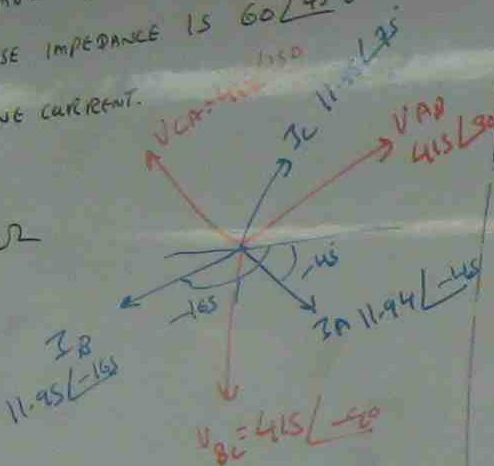
$$= 6.9 (\cos(-15) + j \sin(-15)) - 6.9 (\cos 105 + j \sin 105)$$



$$I_A = 6$$

$$I_B = 3$$

$$I_{AB} = 6.66 - j1.78 + 1.78 - j6.66 = 8.44 - j8.44 = \sqrt{8.44^2 + 8.44^2} \angle -\tan^{-1} \frac{8.44}{8.44} = 11.94 \angle -45^\circ \text{ A}$$

$$I_B = I_{BC} - I_{AB} = 6.9 \angle -135^\circ - 6.9 \angle -15^\circ$$

$$= 6.9 (\cos(-135^\circ) + j \sin(-135^\circ)) - 6.9 (\cos 15^\circ - j \sin 15^\circ)$$

$$= -4.88 - j4.88 - 6.66 + j1.78$$

$$= -11.54 - j3.1 = \sqrt{11.54^2 + 3.1^2} \angle -(180^\circ - \tan^{-1} \frac{3.1}{11.54})$$

$$I_B = 11.95 \angle -165^\circ \text{ A}$$

$$I_C = I_{CA} - I_{BC} = 6.9 \angle 105^\circ - 6.9 \angle -135^\circ$$

$$= 6.9 (\cos 105^\circ + j \sin 105^\circ) - 6.9 (\cos(-135^\circ) + j \sin(-135^\circ))$$

$$= -1.78 + j6.66 + 4.88 + j4.88$$

$$= 3.1 + j11.54 = \sqrt{3.1^2 + 11.54^2} \angle \tan^{-1} \frac{11.54}{3.1}$$

$$= 11.95 \angle 75^\circ \text{ A}$$

$$\text{PHASE CURRENT} = 6.9 \text{ A}$$

$$\text{LINE CURRENT} = \sqrt{3} \times I_{\text{PHASE}} = 1.732 \times 6.9 = 11.95 \text{ A}$$

$j \sin 105^\circ$



Pb ①

A DELTA CONNECTED LOAD HAS THREE IMPEDANCES

$Z_a = 300\Omega$  IN SERIES WITH  $500\text{mH}$  INDUCTOR.


$Z_b = 150\Omega$  IN SERIES WITH  $20\mu\text{F}$  CAPACITOR

$Z_c = 600\text{mH}$  INDUCTOR

LINE VOLTAGE =  $415\text{V}$

FREQUENCY =  $50\text{Hz}$ . USE  $E_{ab}$  AS REFERENCE

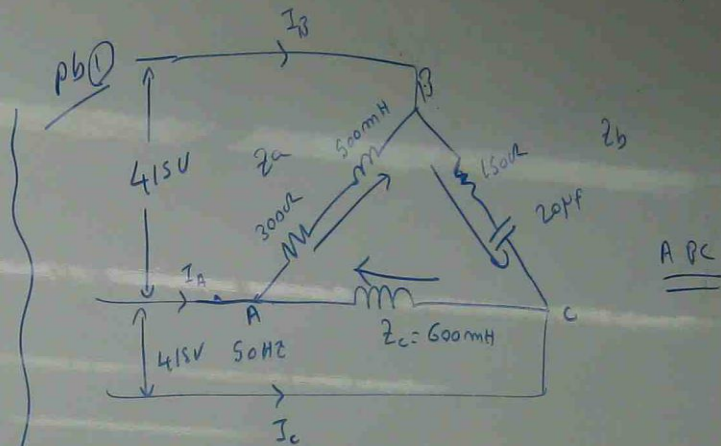CALCULATE ALL LINE CURRENTS IN POLAR FORM



Pb ②

A VOLTAGE  $V = 300 \sin 3000t$  IS APPLIED TO RESISTANCE  $250\Omega$  IN SERIES WITH  $5\mu\text{F}$  CAPACITOR.

CALCULATE (a) APPARENT POWER IN VA

(b) REAL POWER IN WATT

(c) REACTIVE POWER VAR

(d) CIRCUIT POWER FACTOR

(e) POWER TRIANGLE

$$Z_a = 300 + j2\pi fL = 300 + j2 \times 3.1416 \times 50 \times 500 \times 10^{-3}$$

$$(Z_{ab}) = 300 + j157 = \sqrt{300^2 + 157^2} \angle \tan^{-1} \frac{157}{300}$$

$$Z_a = 338.5 \angle 27.6^\circ \Omega$$

$$Z_b = 150 - j \frac{1}{2\pi fC} = 150 - j \frac{1}{2 \times 3.1416 \times 50 \times 20 \times 10^{-6}}$$

$$(Z_{bc}) = 150 - j \frac{10^6}{314.16 \times 20} = 150 - j159 \Omega$$

$$= \sqrt{150^2 + 159^2} \angle \tan^{-1} \frac{159}{150}$$


$$Z_b = 218.5 \angle -46.6^\circ \Omega$$

$$Z_c = \int 2\pi f L = \int 2\pi \times 3.1416 \times 50 \times 600 \times 10^{-3}$$

$$= \int 3/4.16 \times 600 \times 10^{-3}$$

$$= j188.49$$

$$Z_c = 188.49 \angle 90^\circ \Omega$$

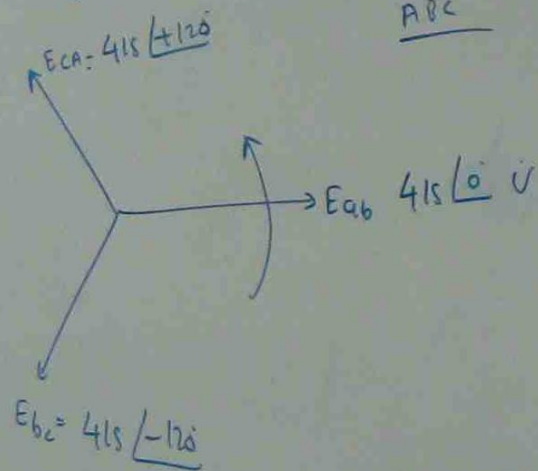

$$I_{AB} = \frac{E_{AB}}{Z_{AB}} = \frac{415 \angle 0^\circ}{218.5 \angle -46.6^\circ} = \frac{415 \angle 0^\circ}{338.5 \angle -27.6^\circ}$$

$$= 1.225 \angle -27.6^\circ \text{ Amp}$$

$$I_{BC} = \frac{E_{BC}}{Z_{BC}} = \frac{415 \angle -120^\circ}{218.5 \angle -46.6^\circ} = \frac{415 \angle -120^\circ}{218.5 \angle -46.6^\circ}$$

$$= 1.9 \angle -120 + 46.66$$

$$= 1.9 \angle -73.34^\circ \text{ Amp}$$

$$I_{CA} = \frac{E_{CA}}{Z_{CA}} = \frac{415 \angle +120^\circ}{188.49 \angle 90^\circ} = \frac{415 \angle 120^\circ}{188.49 \angle 90^\circ}$$

$$= 2.2 \angle 30^\circ \text{ Amp}$$

AT (A) Flow in = Flow out

$$I_A + I_{CA} = I_{AB}$$

$$I_A = I_{AB} - I_{CA}$$

$$= 1.225 \angle -27.6^\circ - 2.2 \angle 30^\circ$$

$$I_A = 1.225 (\cos 27.6^\circ - j \sin 27.6^\circ) - 2.2 (\cos 30^\circ + j \sin 30^\circ)$$

$$= 1.225 (0.886 - j0.463) - 2.2 (0.866 + j0.5)$$



$$\begin{aligned}
 I_A &= (1.085 - j0.567) - (1.9 + j1.1) = 1.085 - j0.567 - 1.9 - j1.1 \\
 &= -0.815 - j1.667 = \sqrt{0.815^2 + 1.667^2} \angle -(180 - \tan^{-1} \frac{1.667}{0.815}) \\
 &= 1.855 \angle -(180 - 63.94) \\
 &= 1.855 \angle -116.06 \text{ Amp}
 \end{aligned}$$

AT (B)  $I_B + I_{AB} = I_{BC}$

$$\begin{aligned}
 I_B &= I_{BC} - I_{AB} = 1.9 \angle -73.34 - 1.225 \angle -27.6 \\
 &= 1.9 (\cos 73.34 - j \sin 73.34) - (1.085 - j0.567) \\
 &= 1.9 (0.286 - j0.958) - 1.085 + j0.567 \\
 &= 0.543 - j1.82 - 1.085 + j0.567 \\
 &= -0.542 - j1.253 \\
 &= \sqrt{0.542^2 + 1.253^2} \angle -(180 - \tan^{-1} \frac{1.253}{0.542}) \\
 &= 1.365 \angle -(180 - 66.6) = 1.365 \angle -113.4 \text{ A}
 \end{aligned}$$

AT (C)  $I_C + I_{BC} = I_{CA} \rightarrow I_C = I_{CA} - I_{BC}$


$$\begin{aligned}
 I_C &= 2.2 \angle 30 - 1.9 \angle -73.34 \\
 &= (1.9 + j1.1) - (0.543 - j1.82) \\
 &= 1.9 + j1.1 - 0.543 + j1.82 = 1.357 + j2.92 \\
 I_C &= \sqrt{1.357^2 + 2.92^2} \angle \tan^{-1} \frac{2.92}{1.357} = 3.22 \angle 65^\circ \text{ A}
 \end{aligned}$$

+j sin 30)  
j0.5)



pb 2

$$V = 300 \sin 3000t$$

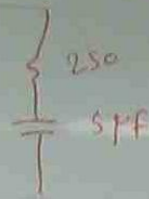

$$V = \frac{300}{\sqrt{2}} \angle 0$$

$$= \frac{300}{1.4142} \angle 0 = 212.13 \angle 0 \text{ V}$$

$$300 \sin 3000t + 30^\circ = \frac{300}{\sqrt{2}} \angle 30^\circ$$

$$300 \sin 3000t - 20^\circ = \frac{300}{\sqrt{2}} \angle -20^\circ$$

$$\omega = 2\pi f = 3000$$

$$250 - j \frac{1}{2\pi f C} = 250 - j \frac{1}{3000 \times 5 \times 10^{-6}}$$

$$= 250 - j \frac{10^6}{15000} = 250 - j 66.66$$

$$Z = \sqrt{250^2 + 66.66^2} \angle -\tan^{-1} \frac{66.66}{250}$$

$$Z = 258.73 \angle -14.9^\circ \Omega$$


$$I = \frac{V}{Z} = \frac{212.13 \angle 0^\circ}{258.73 \angle -14.9^\circ} = 0.819 \angle 14.9^\circ \text{ A}$$

$$(a) \text{ APPARENT POWER} = V I = 212.13 \times 0.819 \\ = 173.73 \text{ VA}$$

$$(b) \text{ REAL POWER} = \text{APPARENT POWER} \cos \phi \\ = 173.73 \cos 14.9^\circ \\ = 173.73 \times 0.966 \\ = 167.88 \text{ WATT}$$

$$(c) \text{ REACTIVE POWER} = \text{APPARENT POWER} \sin \phi \\ = 173.73 \sin 14.9^\circ \\ = 173.73 \times 0.257 \\ = 44.67 \text{ VAR}$$
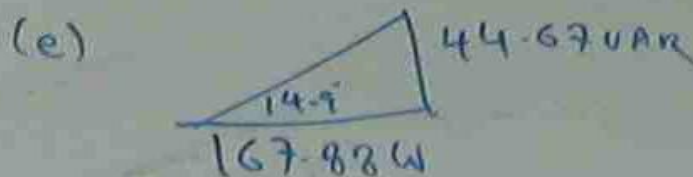
$$(d) \text{ pf} = \cos \phi = \cos 14.9^\circ = 0.966 \\ \text{LEADING (CAPACITIVE LOAD)}$$





$$I_{AB} = \frac{E_{AB}}{Z_{AB}} = \frac{415 \angle 0}{2a} = \frac{415 \angle 0}{338.5 \angle 27.6}$$

$$= 1.225 \angle -27.6 \text{ Amp}$$

$$I_{BC} = \frac{E_{BC}}{Z_{BC}} = \frac{415 \angle -120}{2b} = \frac{415 \angle -120}{218.5 \angle -46.66}$$

$$= 1.9 \angle -120 + 46.66$$

$$= 1.9 \angle -73.34 \text{ Amp}$$

$$I_{CA} = \frac{E_{CA}}{Z_{CA}} = \frac{415 \angle +120}{2c} = \frac{415 \angle 120}{188.49 \angle 46}$$

$$= 2.2 \angle 30 \text{ Amp}$$

AT (A) Flow in = Flow out

$$I_A + I_{CA} = I_{AB}$$

$$I_A = I_{AB} - I_{CA}$$

$$= 1.225 \angle -27.6 - 2.2 \angle 30$$

$$I_A = 1.225 (\cos 27.6 - j \sin 27.6) - 2.2 (\cos 30 + j \sin 30)$$

$$= 1.225 (0.885 - j 0.463) - 2.2 (0.866 + j 0.5)$$

$$I_A = (1.085 - j 0.567) - (1.9 + j 1.1) =$$

$$= -0.815 - j 1.667 = \sqrt{0.815^2 + 1.667^2}$$



$$= 1.855 \angle -109$$

$$= 1.855 \angle -$$

AT (B)  $I_B + I_{AB} = I_{BC}$

$$I_B = I_{BC} - I_{AB} = 1.9 \angle -73.34$$

$$= 1.9 (\cos 73.34 - j \sin 73.34) =$$

$$= 1.9 (0.288 - j 0.958) =$$

$$= 0.543 - j 1.82 = 1.085$$

$$= -0.542 - j 1.253$$

$$= \sqrt{0.542^2 + 1.253^2} \angle -$$

$$= 1.365 \angle -110.66$$

AT (C)  $I_C + I_{BC} = I_{CA}$

$$I_C = 2.2 \angle 30 - 1.9 \angle$$

$$= (1.9 + j 1.1) - (0.543 - j 1.82)$$

$$= 1.9 + j 1.1 - 0.543 + j 1.82$$

$$I_C = \sqrt{1.357^2 + 2.92^2} \angle \tan^{-1}$$

pb(3)

SOLVE THE FOLLOWING

$$3 + j5 + \frac{(5+j3)(4+j6) + (7-j3)^2}{8+j10}$$

$$3 + j5 + \frac{\left(\sqrt{5^2+3^2} \angle \tan^{-1} \frac{3}{5}\right) \left(\sqrt{4^2+6^2} \angle \tan^{-1} \frac{6}{4}\right) + \left(\sqrt{7^2+3^2} \angle \tan^{-1} \frac{3}{7}\right)^2}{\sqrt{8^2+10^2} \angle \tan^{-1} \frac{10}{8}}$$

$$3 + j5 + \frac{5.83 \angle 31^\circ \times 7.21 \angle -56.3^\circ + \left(7.615 \angle -23.17^\circ\right)^2}{12.8 \angle 51.3^\circ}$$

$$3 + j5 + \frac{42.03 \angle 31 - 56.3^\circ + 7.615^2 \angle -23.17 \times 2}{12.8 \angle 51.3^\circ} = 3 + j5 + \frac{42.03 \angle -25.3^\circ + 58 \angle -46.34^\circ}{12.8 \angle 51.3^\circ}$$

$$\boxed{\left(a \angle \theta\right)^n = a^n \angle n\theta}$$



$$3 + j5 + \frac{42.03(\cos 25.3 - j \sin 25.3) + 58(\cos 46.34 - j \sin 46.34)}{12.8 \angle 51.3}$$

$$3 + j5 + \frac{42.03(0.904 - j0.427) + 58(0.69 - j0.72)}{12.8 \angle 51.3}$$

$$3 + j5 + \frac{38 - j18 + 40 - j41.76}{12.8 \angle 51.3}$$

$$3 + j5 + \frac{78 - j59.76}{12.8 \angle 51.3}$$

$$3 + j5 + \frac{\sqrt{78^2 + 59.76^2} \angle -\tan^{-1} \frac{59.76}{78}}{12.8 \angle 51.3}$$

$$3 + j5 + \frac{98.26 \angle -37.45}{12.8 \angle 51.3}$$

$$3 + j5 + 7.67 \angle -37.45 - 51.3$$

$$3 + j5 + 7.67 \angle -88.75$$

$$3 + j5 + 7.67 (\cos 88.75 - j \sin 88.75)$$

$$3 + j5 + 7.67 (0.0218 - j0.999)$$

$$3 + j5 + 0.167 - j7.6$$


$$3.167 - j2.6$$

$$\sqrt{3.167^2 + 2.6^2} \angle -\tan^{-1} \frac{2.6}{3.167}$$

$$4.1 \angle -39.35$$

//


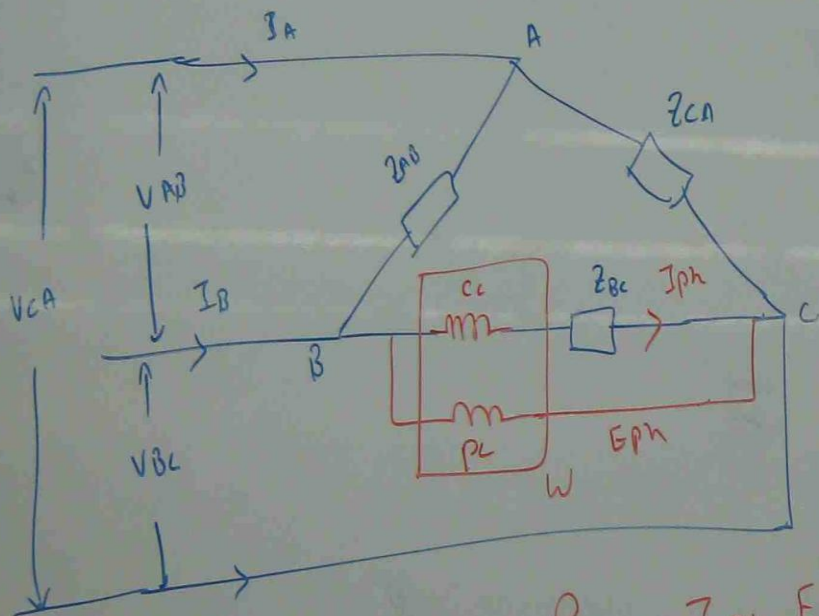
## CALCULATION OF POWER IN DELTA CONNECTED BALANCE LOADS



1  $\phi$  power  $P_{ph} = I_{ph} E_{ph} \cos \theta_{E_{ph}}$

3  $\phi$  power =  $3 \times P_{ph}$

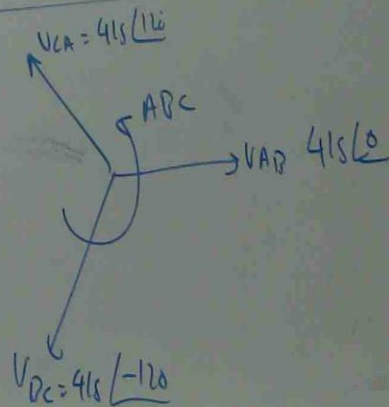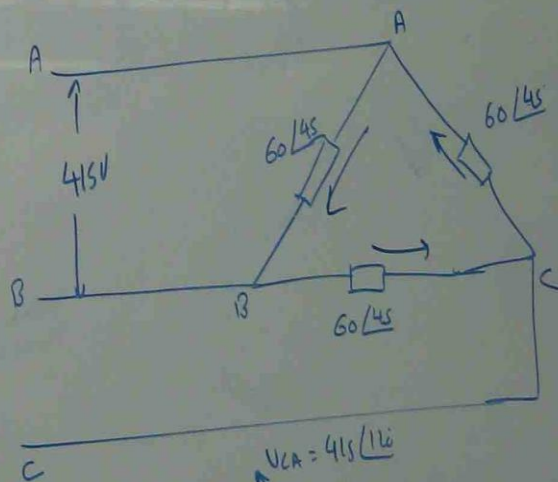Ex A 3  $\phi$  3W 1125 415V ABC system supplies  
A DELTA CONNECTED LOAD WHOSE IMPEDANCE IS  
 $60 \angle 45^\circ \Omega$ . CALCULATE 3  $\phi$  POWER





$$I_{\text{avg}} = I_{\text{ph}} = \frac{V_{\text{ph}}}{Z_{\text{avg}}} = \frac{415 \angle 0}{60 \angle 45} = 6.91 \angle -45 \text{ amp}$$

$$V_{\text{ph}} = V_{\text{avg}} (\text{line}) = 415 \text{ V}$$

$$I_{\text{ph}} = 6.91 \angle -45$$

$$\cos \theta = \cos 45 = 0.707$$

$$P_{\text{ph}} = V_{\text{ph}} I_{\text{ph}} \cos \theta$$

$$= 415 \times 6.91 \times 0.707$$



$$= 2027.42 \text{ WATT}$$

$$3\phi \text{ POWER} = 3 \times P_{\text{ph}} = 3 \times 2027.42$$

$$= 6082.28 \text{ WATT}$$

$$= 6.082 \text{ kW}$$

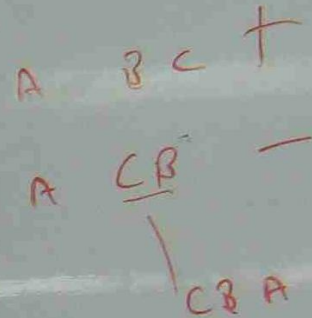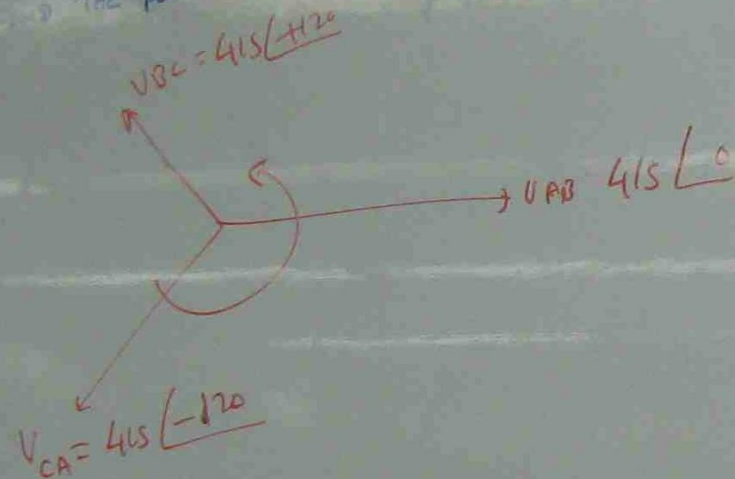Q IN PREVIOUS PROBLEM, IF PHASE SEQUENCE IS ACB (OR) CBA,  
FIND THE POWER AND LINE CURRENT.



$$I_{AB} = I_{ph} = \frac{V_{AB}}{Z_{AB}} = \frac{415 \angle 0}{60 \angle 45} = 6.91 \angle -45 \leftarrow I_{ph}$$

$$P_{ph} = V_{ph} I_{ph} \cos \theta = 415 \times 6.91 \cos 45 = 2027.41$$

$$3\phi \text{ power} = 3 P_{ph} = 3 \times 2027.41 = 6082.23$$

$$= 6.082 \text{ kW}$$

3 $\phi$  BALANCED  $\Delta$

$$I_{LINE} = \sqrt{3} \times I_{ph} = 1.7321 \times 6.91 = 11.95 \text{ Amp}$$



