

ENERGY CONVERSION PROCESS

EACH FORM OF ENERGY MAY BE CONVERTED TO ANOTHER FORM SO THAT THE DESIRED RESULT IS ACHIEVED

CAR ENGINE

CHEMICAL ENERGY \Rightarrow HEAT ENERGY \Rightarrow MECHANICAL ENERGY + WASTE HEAT ENERGY

HYDRO ELECTRIC POWER STATION

WATER IN RESERVOIR (POTENTIAL ENERGY) \Rightarrow FLOWING WATER (KINETIC ENERGY) \Rightarrow WATER TURBINE (MECHANICAL ENERGY) \Rightarrow GENERATOR (ELECTRICAL ENERGY)

$$\text{EFFICIENCY} = \frac{\text{OUTPUT}}{\text{INPUT}} \times 100$$

ph IF process INPUT IS 60KW, OUTPUT IS 55 KW, CALCULATE THE EFFICIENCY

$$\text{Efficiency} = \frac{\text{OUT PUT}}{\text{INPUT}} \times 100 = \frac{55}{60} \times 100 = 91.66\%$$

ENERGY SOURCES

COAL
PETROLEUM (OIL) - PETROL
DIESEL FUEL
KEROSENE
GAS
HEAVY OIL


SUN - DIRECT CONVERSION TO
ELECTRICITY OR HEAT

GRAVITY - WATER STORAGE (DAM)
TIDAL

NUCLEAR - FUSION
FISSION

pb1

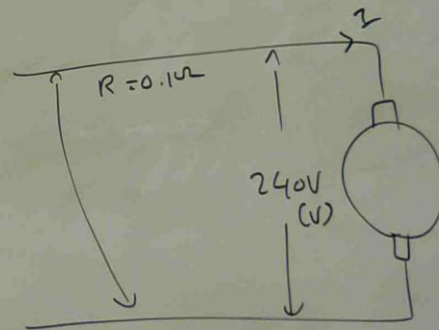1 KW, 240V MOTOR CALCULATE CURRENT.
IF WIRES TO MOTOR HAVE A RESISTANCE OF
0.1Ω HOW MUCH VOLTAGE IS LOST IN WIRES?



$$1 \text{ KW} = P$$

$$\text{WIRE VOLTAGE DROP} = I R$$

$$P = V I$$

$$1000 = 240 \times I$$

$$I = \frac{1000}{240} = 4.16 \text{ Amp}$$

$$= 4.16 \times 0.1$$


$$= 0.416 \text{ V}$$

pb ②

A power station may be providing 100 MW along a particular transmission line (wire), if the voltage is 240 V, what is the current?

(b) If the transmission line has $0.1 \Omega/\text{km}$ and 300 km long, what is voltage drop in line?

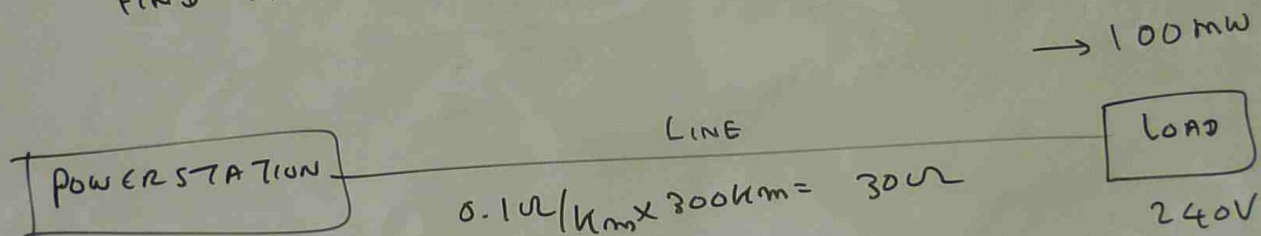(c) If the load voltage is changed from 240 V to 500 kV, find the ampere and voltage drop in wire.



$$(a) P = V \times I \rightarrow I = \frac{P}{V} = \frac{100 \times 10^6}{240} = 416666 \text{ Amp}$$

$$(b) \text{VOLTAGE DROP IN LINE} = I R = 416666 \times 30 \\ = 12500000 \text{ V}$$


$$\begin{aligned}
 (c) \quad I &= \frac{P}{V} \\
 &= \frac{100 \times 10^6}{500 \times 10^3} \\
 &= 200 \text{ Amp}
 \end{aligned}$$

$$\begin{aligned}
 \text{VOLTAGE DROP IN LINE} &= IR \\
 &= 200 \times 30 \\
 &= 6000 \text{ V}
 \end{aligned}$$

STEP UP TRANSFORMERS ARE UTILIZED TO CHANGE THE LOW VOLTAGE TO HIGH VOLTAGE LEVEL.

ONLY AC CAN BE CHANGED TO LEVEL. TO CHANGE THE DC VOLTAGE TO ANOTHER LEVEL IS DIFFICULT. IT IS WHY AC IS USED IN TRANSMISSION

AC CIRCUIT THEORY

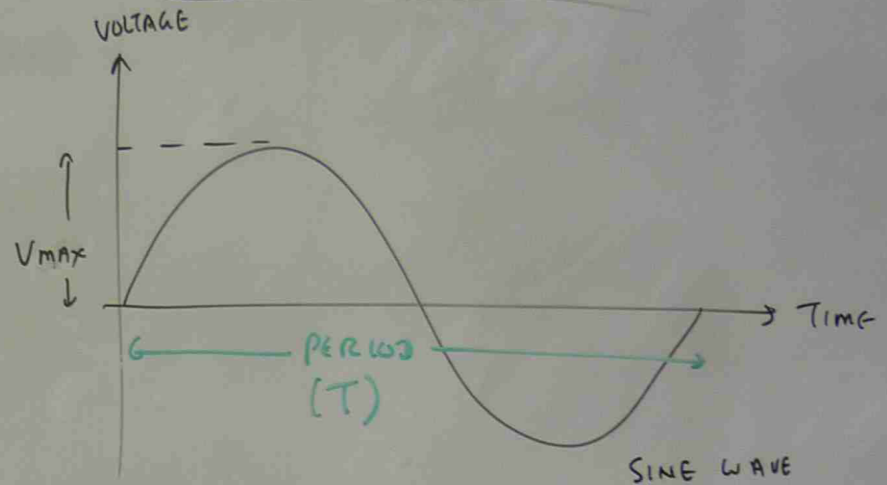


$$V = V_{\text{max}} \sin 2\pi ft$$

V_{max} = MAXIMUM VOLTAGE

f = FREQUENCY

$$\pi = 3.1416$$

t = TIME

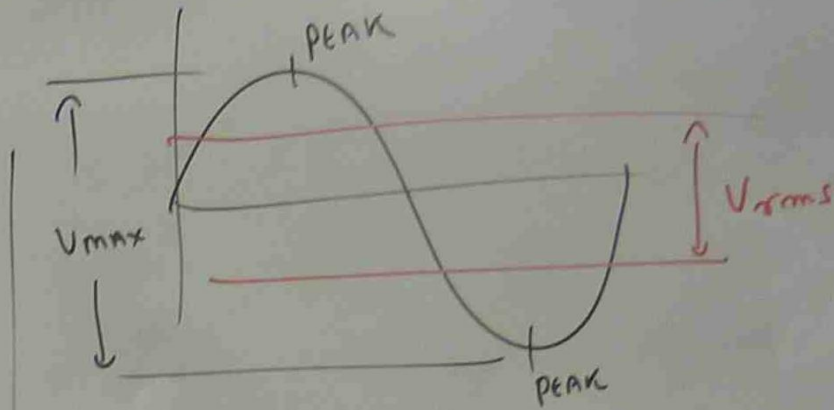

V_{MAX} = PEAK TO PEAK VOLTAGE


V_{RMS} = ROOT MEAN SQUARE VOLTAGE

$$V_{MAX} = \sqrt{2} V_{RMS}$$

$$V_{RMS} = \frac{V_{MAX}}{\sqrt{2}} = \frac{V_{MAX}}{1.4142}$$

PERIOD (T)

TIME TAKEN TO PASS ONE WAVEFORM.

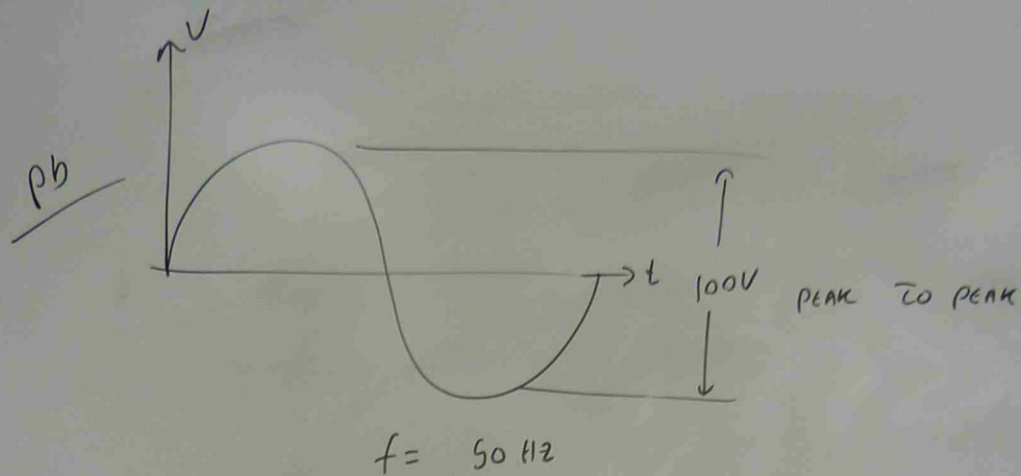

- (a) WRITE THE EQUATION FOR THE GIVEN WAVE FORM
 (b) CALCULATE PERIOD (T)
 (c) FIND RMS VALUE OF VOLTAGE.

$$(a) \quad V = V_{\text{MAX}} \sin 2\pi f t$$

(OR)

$$V = V_{\text{MAX}} \sin \omega t$$

$$\begin{aligned} V &= 100 \sin 2\pi f t \\ &= 100 \sin 2 \times 3.1416 \times 50 t \\ &= 100 \sin 314.16 t \end{aligned}$$

$$\omega = 2\pi f$$

ω = RADIANS
VELOCITY
(rad/sec)

f = FREQUENCY
(Hz)




$$(b) \quad T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ sec} \\ = 20 \text{ ms}$$

$$50 \text{ Hz} = 50 \text{ cycle/sec}$$


$$(c) \quad V_{\text{rms}} = \frac{V_{\text{max}}}{\sqrt{2}} = \frac{100}{1.4142} = 70.7 \text{ V}$$

PHASOR

(a) PURE
RESISTANCE

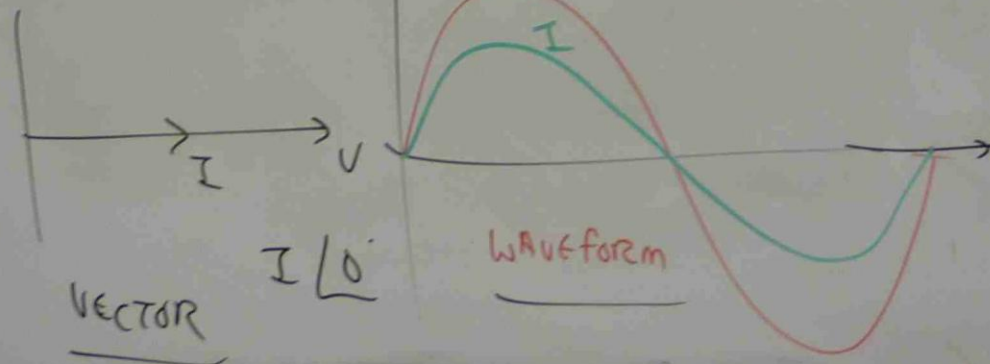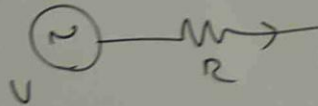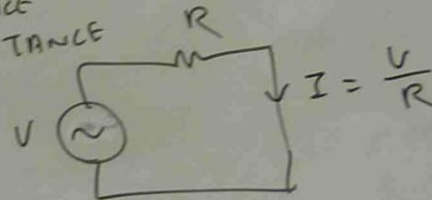


(b) PURE INDUCTANCE

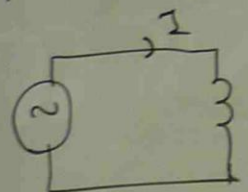


$$I = \frac{V}{X_L}$$

INDUCTIVE
REACTANCE
(Ω)

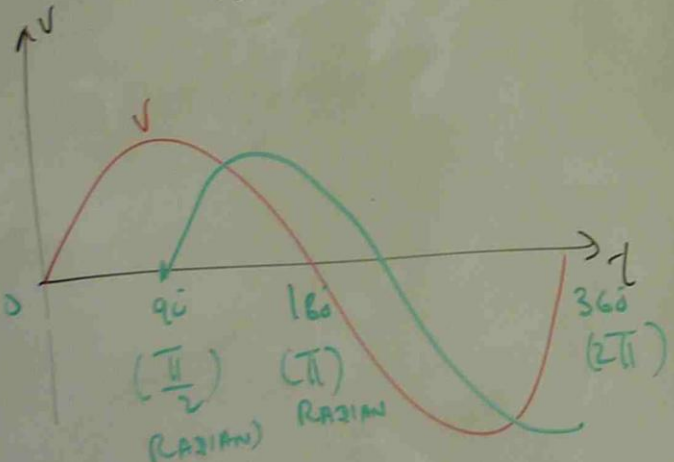
INDUCTANCE (H) $\Rightarrow X_L = 2\pi fL$



CURRENT LAGS VOLTAGE BY 90°


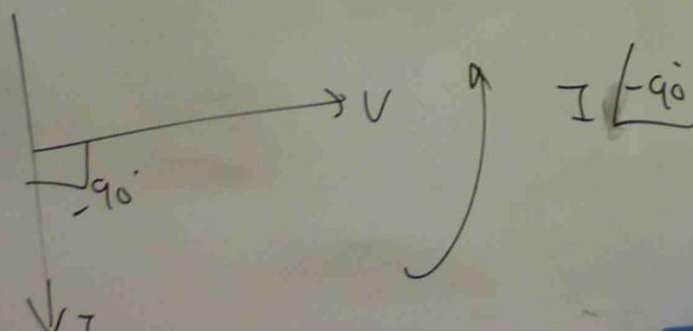


(c) RESISTOR + INDUCTOR

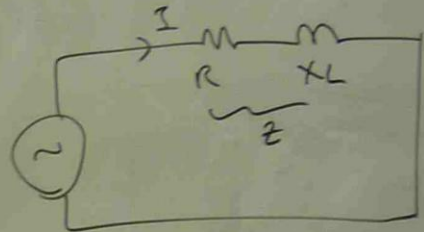


$$Z = \sqrt{R^2 + X_L^2}$$



$$I = \frac{V}{Z}$$

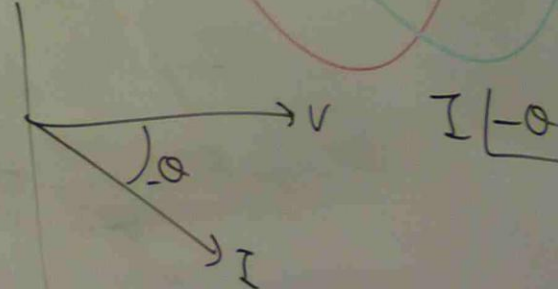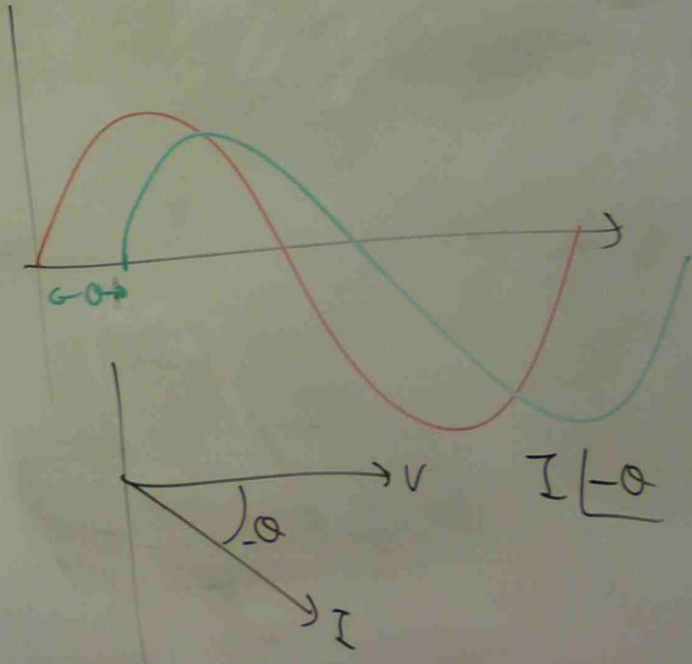


(d) PURE CAPACITANCE

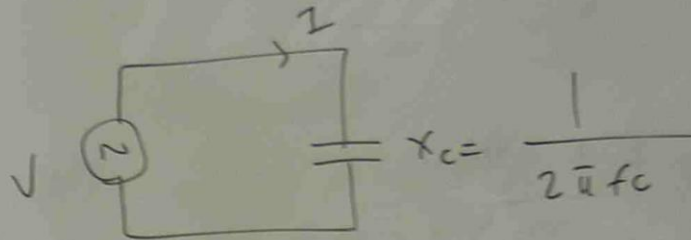

$$I = \frac{V}{X_c}$$

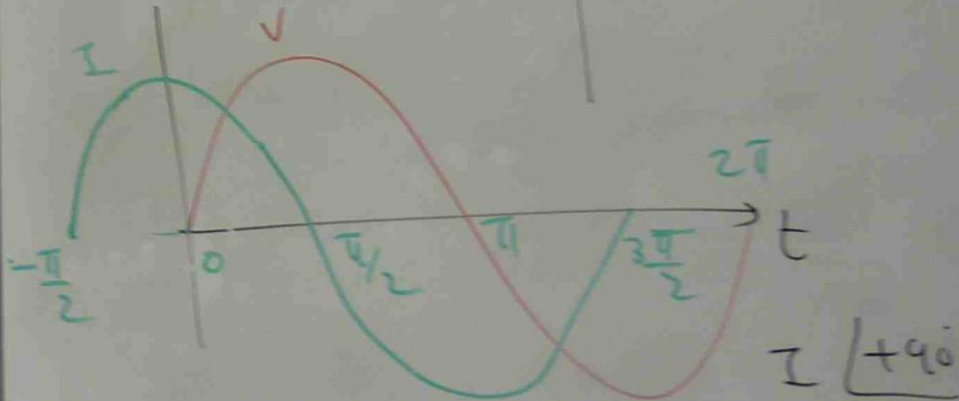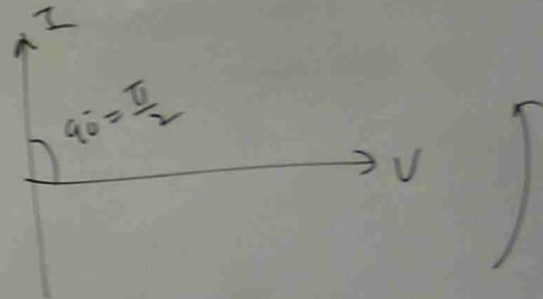


(c) RESISTOR + CAPACITOR

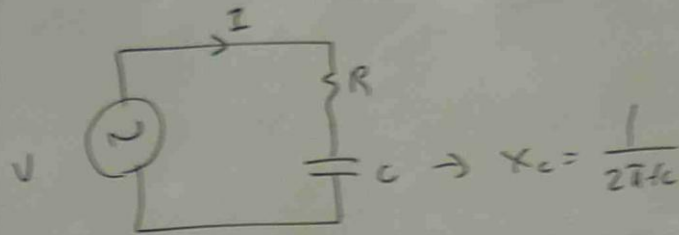


$$Z = \sqrt{R^2 + X_C^2}$$
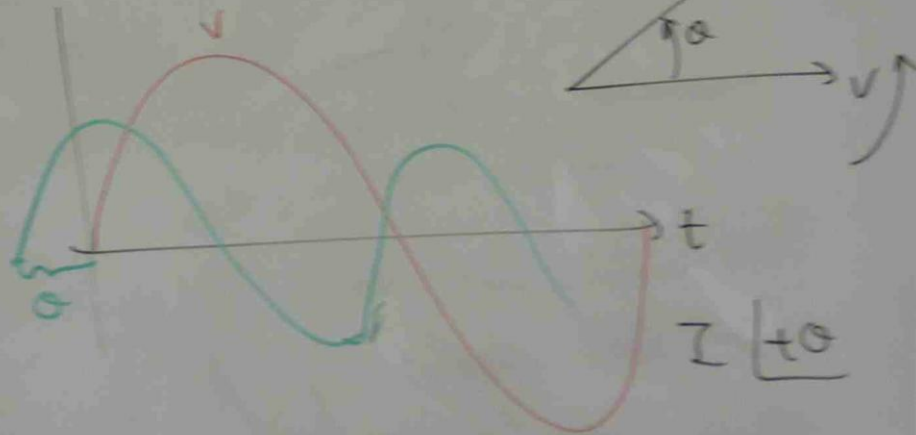
$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + X_C^2}}$$



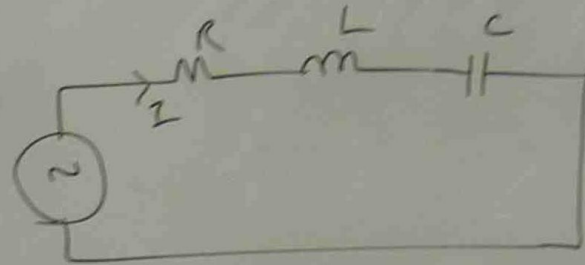(f) RESISTOR + INDUCTOR + CAPACITOR (RLC)




$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

If $X_L > X_C$: IT follows R + L circuit

If $X_C > X_L$: IT follows R + C circuit

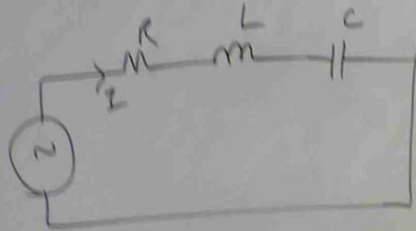(f) RESISTOR + INDUCTOR + CAPACITOR (RLC)



$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

If $X_L > X_C$: IT follows R + L circuit


If $X_C > X_L$: IT follows R + C circuit

CALCULATION OF POWER



SINGLE PHASE

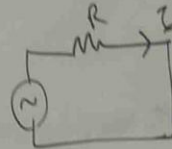

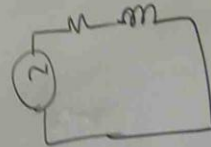
$$P = V \times I \text{ (or)} I^2 R \text{ (or)} \frac{V^2}{R}$$



$$P = VI \cos \phi$$

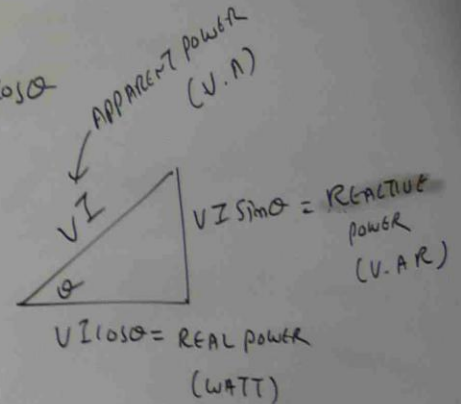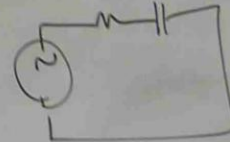
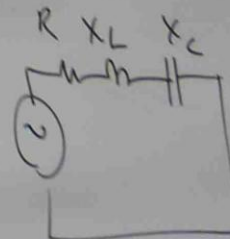
$$\phi = \tan^{-1} \frac{X_L}{R} \text{ (or)} \tan^{-1} \frac{X_C}{R}$$



$$\phi = \tan^{-1} \frac{X_L - X_C}{R}$$

