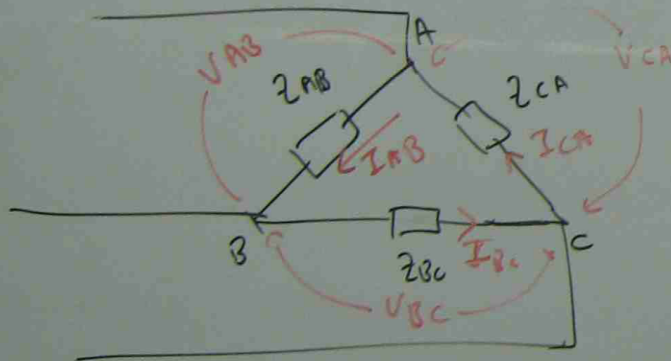



CALCULATION OF 3 ϕ POWER




$$3\phi \text{ power for UNBALANCED } = V_{AB} I_{AB} \cos \theta_{I_{AB}} + V_{BC} I_{BC} \cos \theta_{I_{BC}} + V_{CA} I_{CA} \cos \theta_{I_{CA}}$$

Δ LOAD

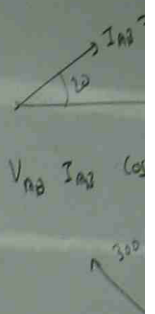
$$\begin{aligned} V_{AB} &= 300 \angle 0^\circ & I_{AB} &= 20 \angle 20^\circ \\ V_{BC} &= 300 \angle 120^\circ & I_{BC} &= 30 \angle 95^\circ \\ V_{CA} &= 300 \angle -120^\circ & I_{CA} &= 12 \angle -120^\circ \end{aligned}$$



TOTAL
POWER

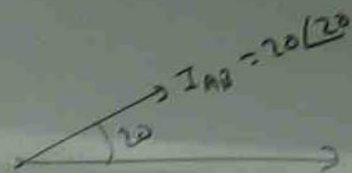

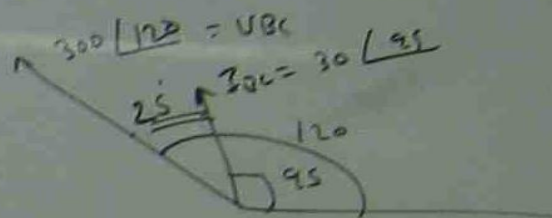
$$V_{AB} I_{AB} \cos \theta_{I_{AB}} = 300 \times 20 \cos 20 = 5638 \text{ W}$$



$$\begin{aligned} V_{BC} I_{BC} \cos \theta_{I_{BC}} &= 300 \times 30 \cos 25 \\ &= 9000 \times 0.906 \\ &= 8156 \text{ W} \end{aligned}$$

$$V_{CA} I_{CA} \cos \theta_{I_{CA}}$$

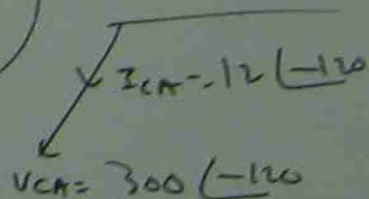

$$V_{CA} I_{CA} \cos \theta_{I_{CA}} = 300 \times 12 \cos 0 = 3600 \text{ W}$$

$$\begin{aligned} \text{TOTAL POWER} &= 5638 + 8156 + 3600 = 17394 \text{ W} \end{aligned}$$

WHEN PHASE SEQUENCE IS REVERSED, LINE CURRENT WILL CHANGE BUT TOTAL POWER IS UNCHANGED.

EXERCISE

A 3ϕ 3 WIRE 240 V ACB SEQUENCE
IS CONNECTED TO A DELTA LOAD. THE IMPEDANCES OF
THE LOAD ARE

$$Z_{AB} = 10 \angle 30^\circ \Omega$$

$$Z_{BC} = 20 \angle 90^\circ \Omega$$


$$Z_{CA} = 15 \angle -45^\circ \Omega$$

FIND (a) PHASE CURRENT



(b) LINE CURRENT

METHOD (?) USE KIRCHHOFF'S LAW

3W SWIRE X CONNECTED UNBALANCED LOAD

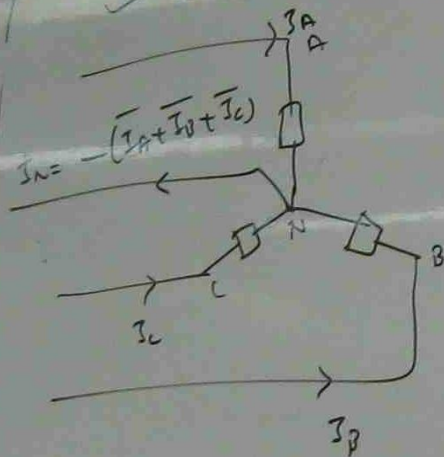

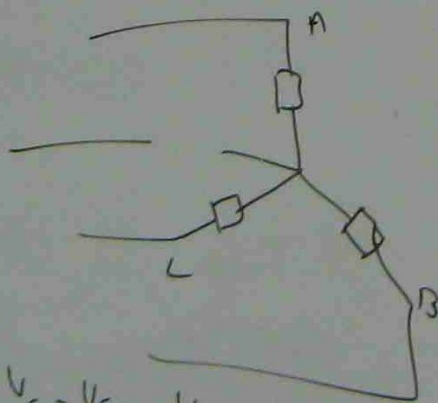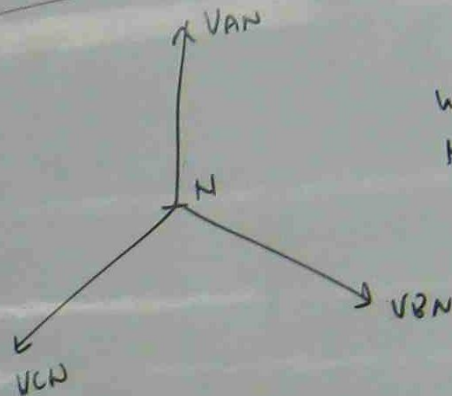
$$\begin{aligned} V_{AN} &= E \\ V_{BN} &= E \\ V_{CN} &= E \end{aligned}$$



$$\begin{aligned} V_{CO} &= V_{CN} - V_{NO} \\ I_C &= V_{CO} \times Y_C \end{aligned}$$
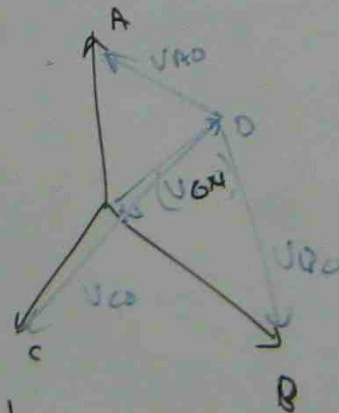
$$\begin{aligned} Y_A &= \frac{1}{Z_A} \\ Y_B &= \frac{1}{Z_B} \\ Y_C &= \frac{1}{Z_C} \end{aligned}$$



METHOD (1)


$\lambda \rightarrow \Delta$

CALCULATE
PHASE &
LINE
CURRENT

METHOD (2)



$$V_{ON} = \frac{V_{AN} Y_A + V_{BN} Y_B + V_{CN} Y_C}{Y_A + Y_B + Y_C}$$
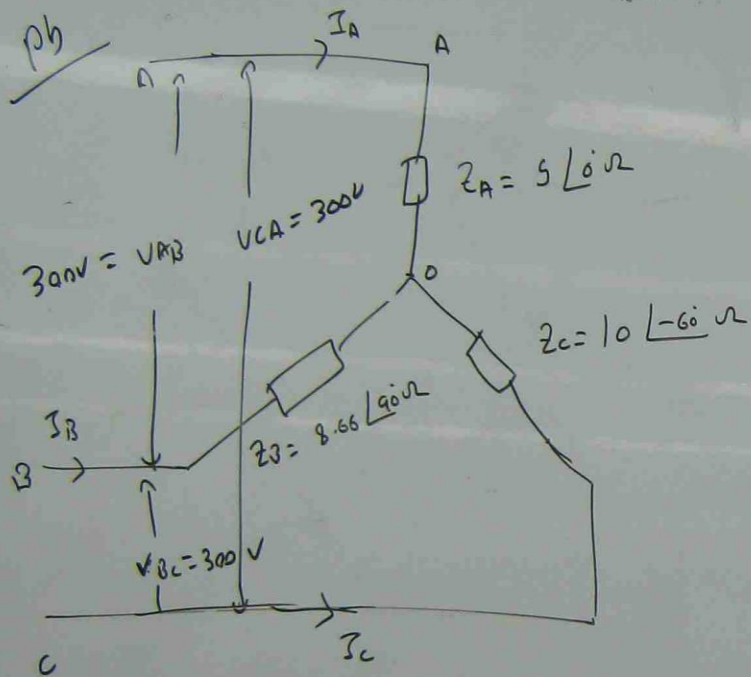
$$\begin{aligned} V_{AO} &= V_{AN} - V_{ON} \rightarrow I_A = V_{AO} \times Y_A \\ V_{BO} &= V_{BN} - V_{ON} \rightarrow I_B = V_{BO} \times Y_B \end{aligned}$$



- CALCULATE (i) V_{ON}
 (ii) UNBALANCED PHASE VOLTAGES
 (iii) LINE CURRENTS.

SEQUENCE ACB

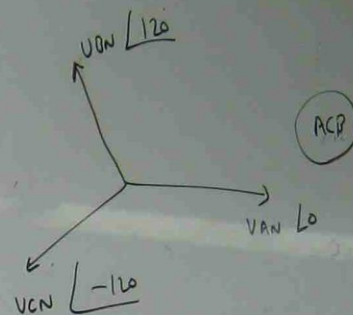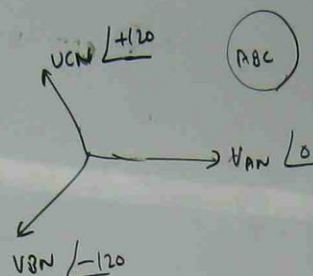

$$V_{AN} = \frac{\text{LINE VOLTAGE}}{\sqrt{3}} = \frac{300}{1.7321} = 173.2 \angle 0^\circ$$

$$V_{BN} = 173.2 \angle +120^\circ, \quad V_{CN} = 173.2 \angle -120^\circ$$

$$Y_A = \frac{1}{Z_A} = \frac{1}{5 \angle 0^\circ} = 0.2 \angle 0^\circ$$

$$Y_B = \frac{1}{Z_B} = \frac{1}{8.66 \angle 90^\circ} = 0.115 \angle -90^\circ$$

$$Y_C = \frac{1}{Z_C} = \frac{1}{10 \angle -60^\circ} = 0.1 \angle 60^\circ$$

$$\begin{aligned}
 V_{ON} &= \frac{V_{AN} Y_A + V_{BN} Y_B + V_{CN} Y_C}{Y_A + Y_B + Y_C} \\
 &= \frac{173.2 \angle 0^\circ \times 0.2 \angle 0^\circ + 173.2 \angle -120^\circ \times 0.115 \angle -90^\circ + 173.2 \angle +120^\circ \times 0.1 \angle 60^\circ}{0.2 \angle 0^\circ + 0.115 \angle -90^\circ + 0.1 \angle 60^\circ}
 \end{aligned}$$

$$V_{ON} = \frac{34.6 \angle 0^\circ + 19.9 \angle 30^\circ + 17.3 \angle 60^\circ}{0.2 + j0 + 0 - j0.115 + 0.05 + j0.087}$$

$$\begin{aligned}
 &34.6 + 19.9(\cos 30^\circ + j \sin 30^\circ) \\
 &+ 17.3(\cos 60^\circ - j \sin 60^\circ) \\
 &0.25 - j0.28
 \end{aligned}$$

$$\begin{aligned}
 &60.66 \angle -47^\circ \\
 &0.25 \angle -64^\circ
 \end{aligned}$$

$$V_{ON} = 242.6 \angle 1.7^\circ$$

$$\begin{aligned}
 V_{AO} &= V_{AN} - V_{ON} = 173.2 \angle 0 - 242.6 \angle 1.7 \\
 &= 173.2 - 242.6 (\cos 1.7 + j \sin 1.7) \\
 &= 173.2 - (242.5 + j 7.2) \\
 &= -69.3 - j 7.2 \\
 &= \sqrt{69.3^2 + 7.2^2} \angle \left(-180 - \tan^{-1} \frac{7.2}{69.3} \right) \\
 &= 69.9 \angle -174^\circ \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_{BO} &= V_{BN} - V_{ON} = 173.2 \angle 120 - 242.6 \angle 1.7 \\
 &= 173.2 (\cos 120 + j \sin 120) - (242.5 + j 7.2) \\
 &= -329 + j 142.6 \\
 &= 358.6 \angle 156^\circ \text{ V}
 \end{aligned}$$


$$\begin{aligned}
 V_{CO} &= V_{CN} - V_{ON} = 173.2 \angle -120 - 242.6 \angle 1.7 \\
 &= -66.5 - j 149.8 - (242.5 + j 7.2) \\
 &= -329 - j 157
 \end{aligned}$$

$$V_{CO} = 364.5 \angle -154.5^\circ \text{ V}$$

$$I_A = V_{AO} Y_A = 69.9 \angle -174^\circ \times 0.2 \angle 0 = 14 \angle -174^\circ \text{ A}$$

$$I_B = V_{BO} Y_B = 358.6 \angle 156^\circ \times 0.115 \angle -90 = 41.2 \angle 66^\circ \text{ A}$$
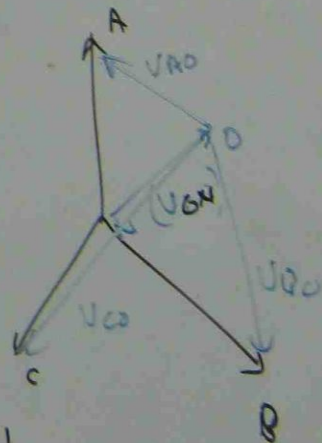
$$I_C = V_{CO} Y_C = 364.5 \angle -154.5^\circ \times 0.1 \angle 60 = 36.5 \angle -94^\circ \text{ A}$$



$$Y_A = \frac{1}{Z_A}$$

$$Y_B = \frac{1}{Z_B}$$

$$Y_C = \frac{1}{Z_C}$$

$$V_{ON} = \frac{V_{AN} Y_A + V_{BN} Y_B + V_{CN} Y_C}{Y_A + Y_B + Y_C}$$

$$V_{AO} = V_{AN} - V_{ON}$$