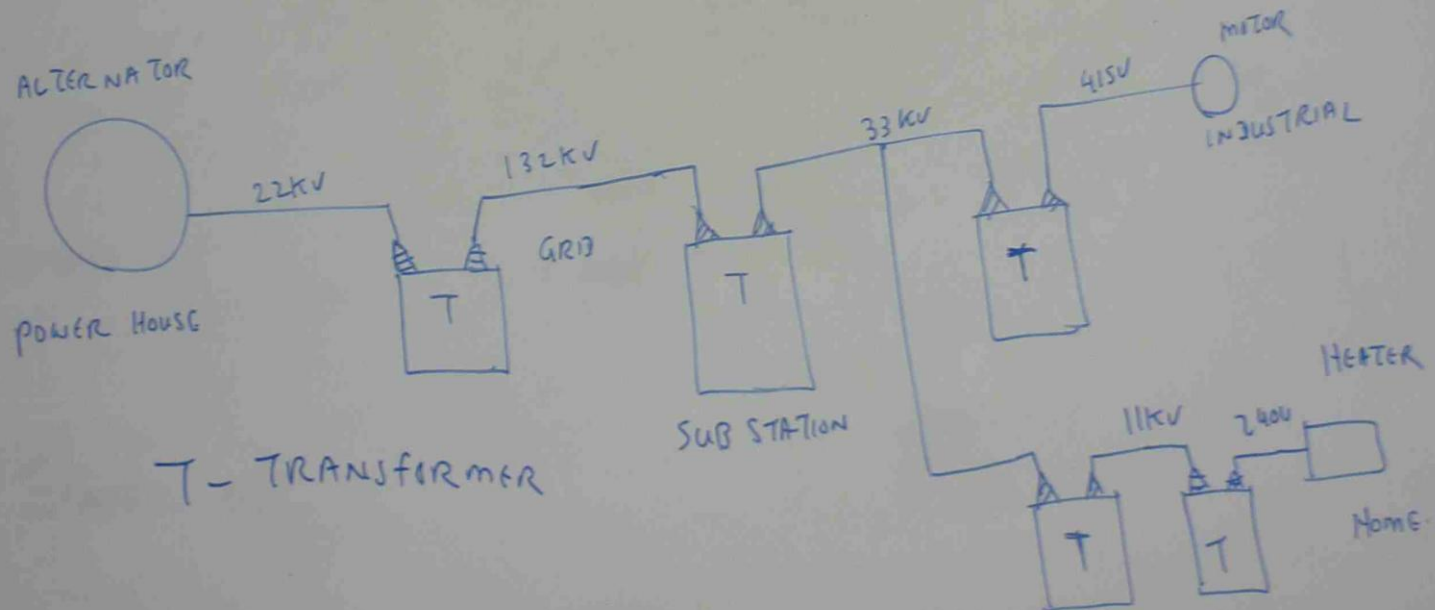


## TRANSFORMER

A TRANSFORMER IS A SPECIAL INDUCTOR THAT ALLOWS A CHANGE OF VOLTAGE TO SUIT THE PURPOSE. AN IMPORTANT EXAMPLE IS THAT OF DISTRIBUTION OF ELECTRICAL ENERGY FROM THE POWER STATION TO DOMESTIC AND INDUSTRIAL SITES.


### DISTRIBUTION

SIMPLIFIED VIEW OF POWER DISTRIBUTION.



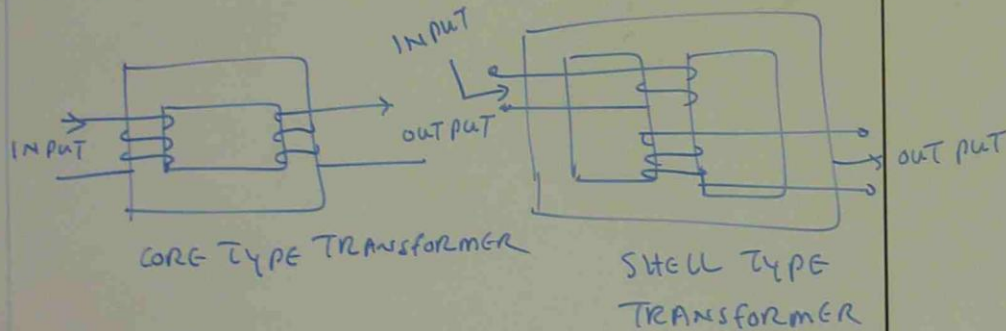
### CONSTRUCTION

A TRANSFORMER IS CONSTRUCTED OF TWO INDUCTORS. THE INPUT INDUCTOR OF TRANSFORMER IS CALLED PRIMARY WINDING. THE OUTPUT INDUCTOR IS CALLED SECONDARY WINDING. THE TWO WINDINGS ARE MAGNETICALLY COUPLED BY CORE.



THE CORE IS GENERALLY MADE OF LAMINATED IRON AND IS NOT SOLID, BUT IS LAMINATED OF MANY THIN PARTS. THIS IS BECAUSE OF CIRCULATING CURRENT THAT ARE GENERATED BY CORE. THEY ARE CALLED EDDY CURRENT WHICH CAUSES POWER LOSS IN CORE.

### SYMBOL

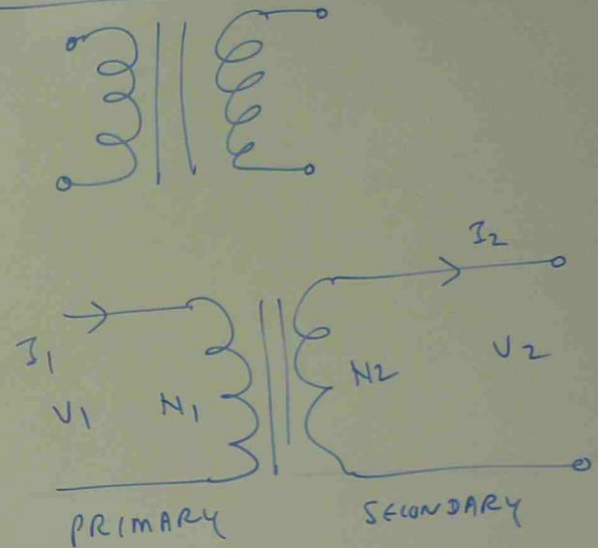


$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2}$$

$$\boxed{\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}}$$

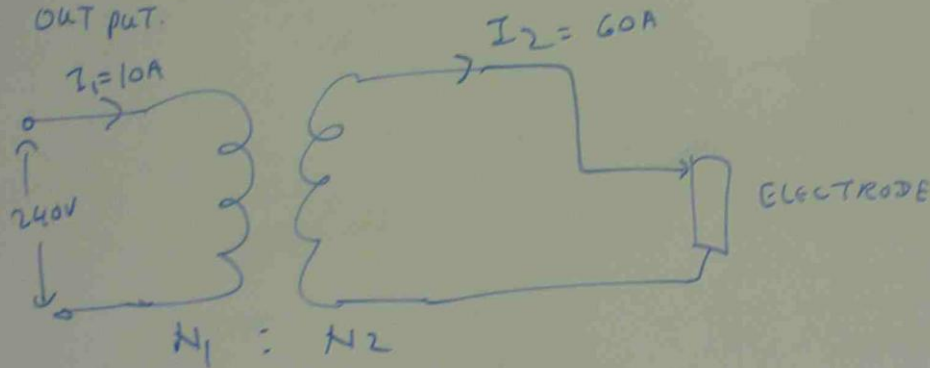pb A WELDER NEEDS TO HAVE 60 AMP OUTPUT AND IS TO BE CONNECTED TO A 240V, 10 A SUPPLY.  
 WHAT TURN RATIO IS NEEDED? WHAT VOLTAGE WOULD BE SUPPLIED TO THE ELECTRODE AT  
 OUTPUT.



$$\frac{N_1}{N_2} = a = \text{TURN RATIO}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = a$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = a$$


$$\frac{240}{V_2} = 6$$

$$\frac{60}{10} = a = 6$$


$$6V_2 = 240$$

$$V_2 = \frac{240}{6} = 40V$$

## VOLTAGE REGULATION

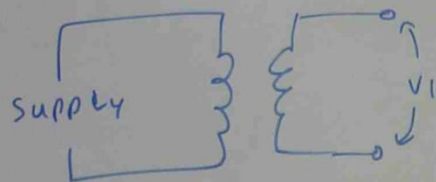

OPEN CIRCUIT  
VOLTAGE  
 $V_{NL}$

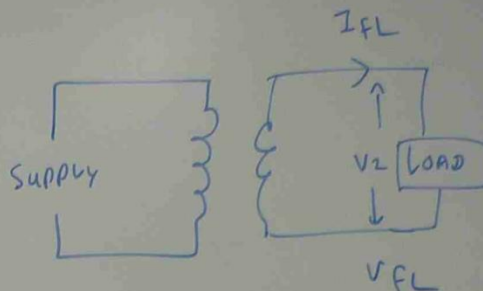

$$\text{VOLTAGE REGULATION } V_R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 \%$$

IF THE SECONDARY VOLTAGE VARIES TOO MUCH, A MOTOR (OR) OTHER LOAD MAY NOT OPERATE PROPERLY. TO ASSESS THIS OUTPUT STABILITY, REGULATION IS CALCULATED.

$$\text{VOLTAGE REGULATION} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 \%$$


Pb THE SECONDARY VOLTAGE OF A TRANSFORMER IS MEASURED AS 20 VOLT AT FULL LOAD AND 20.9 VOLT AT NO LOAD. WHAT IS THE VOLTAGE REGULATION.

$$V_R = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 = \frac{20.9 - 20}{20} \times 100 = \frac{0.9 \times 100}{20} = \frac{90}{20} = 4.5 \%$$




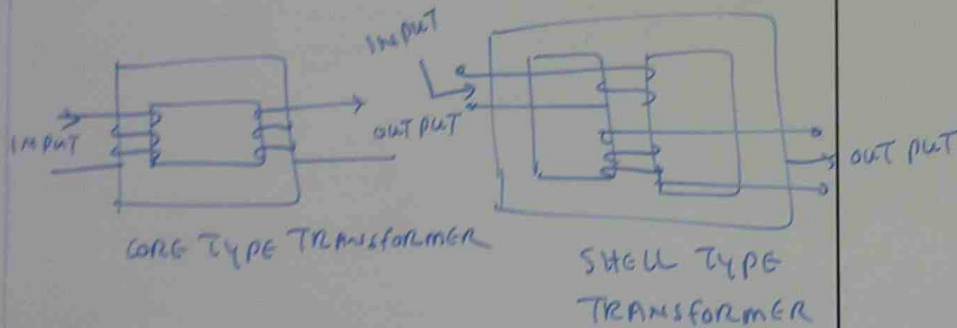
### CONSTRUCTION

A TRANSFORMER IS CONSTRUCTED OF TWO INDUCTORS. THE INPUT INDUCTOR OF TRANSFORMER IS CALLED PRIMARY WINDING. THE OUTPUT INDUCTOR IS CALLED SECONDARY WINDING. THE TWO WINDINGS ARE MAGNETICALLY COUPLED BY CORE.



THE CORE IS GENERALLY MADE OF LAMINATED IRON AND IS NOT SOLID, BUT IS LAMINATED OF MANY THIN PARTS. THIS IS BECAUSE OF CIRCULATING CURRENT THAT ARE GENERATED BY CORE. THEY ARE CALLED EDDY CURRENT WHICH CAUSES POWER LOSS IN CORE.

### SYMBOL

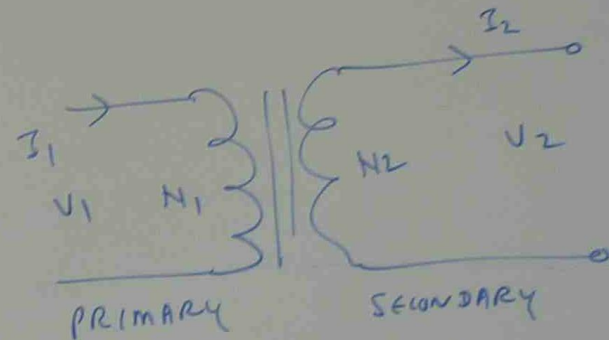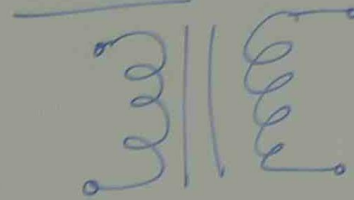


$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2}$$

$$\boxed{\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}}$$

Pb A WELDER NEEDS TO HAVE 60 AMP OUTPUT AND IS TO BE CONNECTED TO A 240V, 10 A SUPPLY.

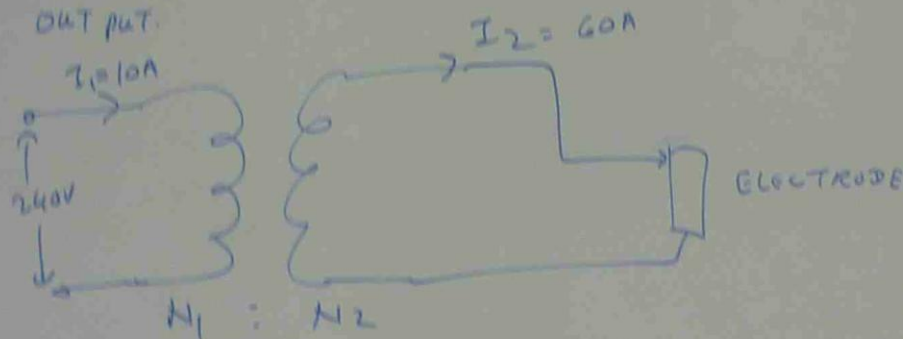WHAT TURN RATIO IS NEEDED? WHAT VOLTAGE WOULD BE SUPPLIED TO THE ELECTRODE AT OUTPUT.



$$\frac{N_1}{N_2} = a = \text{TURN RATIO}$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = a$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = a$$

$$\frac{240}{V_2} = 6$$

$$\frac{60}{10} = a = 6$$

$$6V_2 = 240$$


$$V_2 = \frac{240}{6} = 40V$$

## CONNECTION OF RESISTORS, INDUCTORS AND CAPACITORS

### RESISTOR




$$R_T = R_1 + R_2 + R_3$$

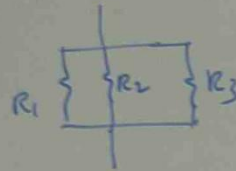

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


### INDUCTOR

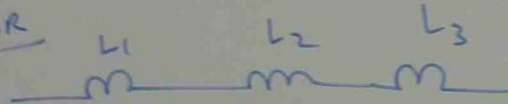

$$L_T = L_1 + L_2 + L_3$$

$$X_{L_T} = X_{L_1} + X_{L_2} + X_{L_3}$$


$$X_L = 2\pi f L$$

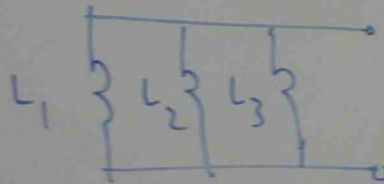

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$\frac{1}{X_{L_T}} = \frac{1}{X_{L_1}} + \frac{1}{X_{L_2}} + \frac{1}{X_{L_3}}$$


## CAPACITOR

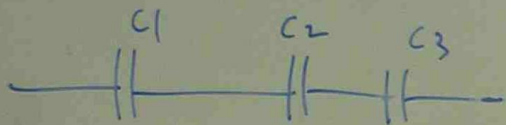

$$X_c = \frac{1}{2\pi f c}$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$
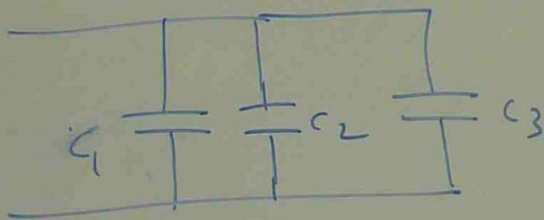
$$\frac{1}{X_{cT}} = \frac{1}{X_{c1}} + \frac{1}{X_{c2}} + \frac{1}{X_{c3}}$$



$$C_T = C_1 + C_2 + C_3$$

$$X_{cT} = X_{c1} + X_{c2} + X_{c3}$$




## CONNECTION OF RESISTORS, INDUCTORS AND CAPACITORS

### RESISTOR




$$R_T = R_1 + R_2 + R_3$$

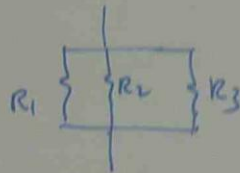

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


### INDUCTOR

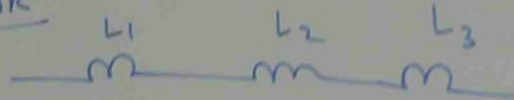

$$L_T = L_1 + L_2 + L_3$$

$$X_{L_T} = X_{L_1} + X_{L_2} + X_{L_3}$$


$$X_L = 2\pi f L$$

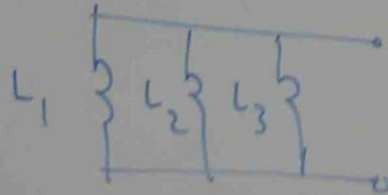

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$\frac{1}{X_{L_T}} = \frac{1}{X_{L_1}} + \frac{1}{X_{L_2}} + \frac{1}{X_{L_3}}$$


## CAPACITOR

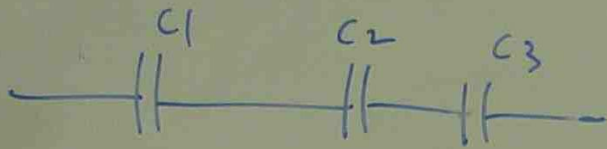

$$X_c = \frac{1}{2\pi f c}$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

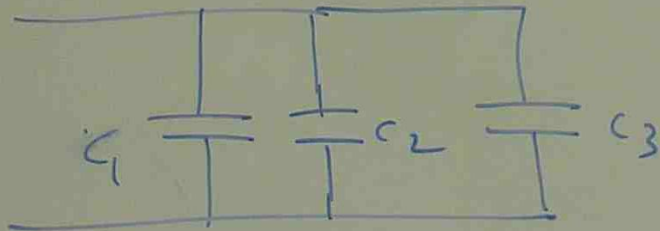
$$\frac{1}{X_{cT}} = \frac{1}{X_{c1}} + \frac{1}{X_{c2}} + \frac{1}{X_{c3}}$$



$$C_T = C_1 + C_2 + C_3$$

$$X_{cT} = X_{c1} + X_{c2} + X_{c3}$$


## POWER IN COMBINED CIRCUITS

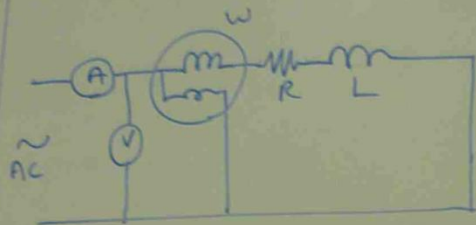

$$V = 200 \text{ V}$$

$$I = 2 \text{ Amp}$$

$$W = 300 \text{ WATT}$$

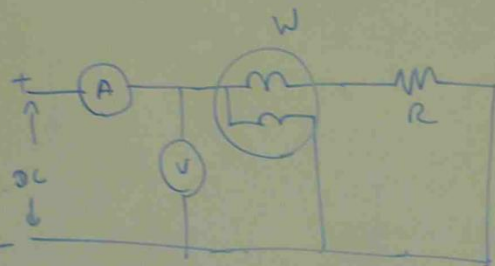

$$V = 200 \text{ V}$$

$$I = 2 \text{ Amp}$$

$$W = 400 \text{ WATT}$$


$$\text{DC power } W = V \times I$$

$$\text{AC power } W < V I$$


$$\text{AC power } W = V \times I \times \text{PF}$$

PF = POWER FACTOR

$$W = V \times I \times \cos \phi$$

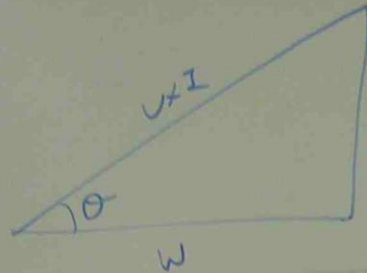

$$\cos \theta = PF = \frac{W}{VI}$$

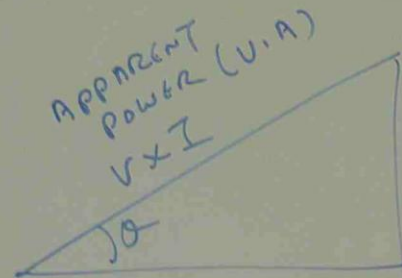

REAL POWER

$$W = VI \cos \theta$$

(WATT)



REACTING  
POWER =  $VI \sin \theta$   
(VAR)

$$(\text{APPARENT POWER})^2 = (\text{REAL POWER})^2 + (\text{REACTIVE POWER})^2$$





## LEADING & LAGGING power

### LAGGING

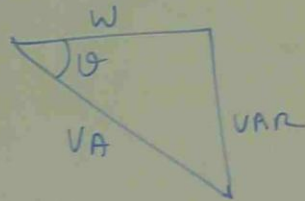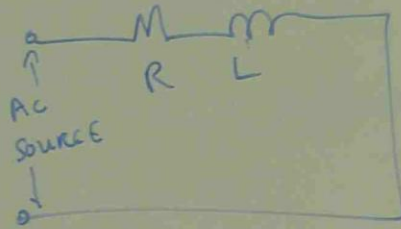


$$PF = \cos \theta = \text{LAGGING POWER FACTOR}$$

### LEADING

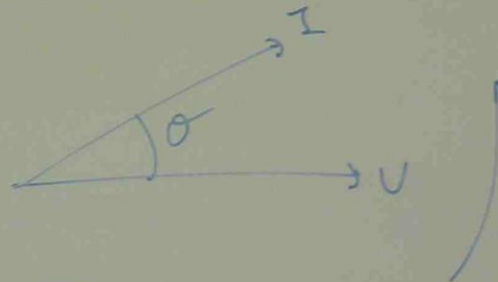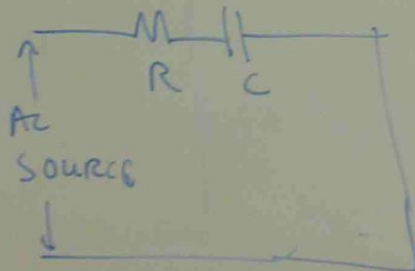
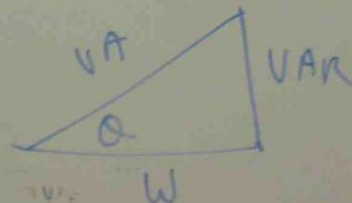
$$PF = \cos \theta = \text{LEADING POWER FACTOR}$$



ph For A supply voltage of 240 volts, 2 kW load, calculate the current needed for

$$\phi = 0^\circ, 25^\circ, 60^\circ$$


$$W = VI \cos \phi \rightarrow I = \frac{W}{V \cos \phi}$$

$$\phi = 0^\circ \rightarrow I = \frac{2 \times 10^3}{240 \times \cos 0} = 8.33 \text{ Amp}$$

$$\phi = 25^\circ \rightarrow I = \frac{2 \times 10^3}{240 \cos 25} = \frac{2000}{240 \times 0.906} = 9.19 \text{ Amp}$$

$$\phi = 60^\circ \rightarrow I = \frac{2 \times 10^3}{240 \cos 60} = \frac{2000}{240 \times 0.5} = 16.67 \text{ Amp}$$

$\phi$	$\cos \phi$	I
0	1	8.33
25	0.906	9.13
60	0.5	16.67

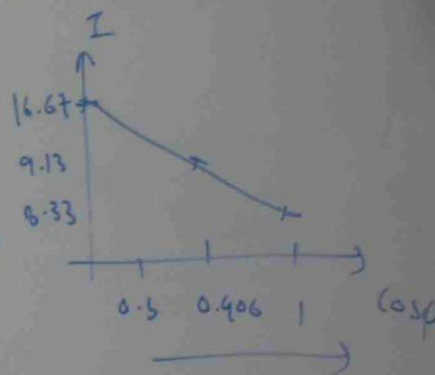

$$I \propto \frac{1}{\text{PF}}$$

## EFFECT OF POWER FACTOR ON SUPPLY CURRENT

IF THERE ARE A LOT OF INDUCTIVE LOADS, THE POWER FACTOR IS LAGGING AND POOR CAUSING A HIGH CURRENT FLOWS IN LINE.

TO REDUCE THE CURRENT, THE POWER FACTOR NEEDS TO BE INCREASED BY CONNECTING A PARALLEL CAPACITOR.