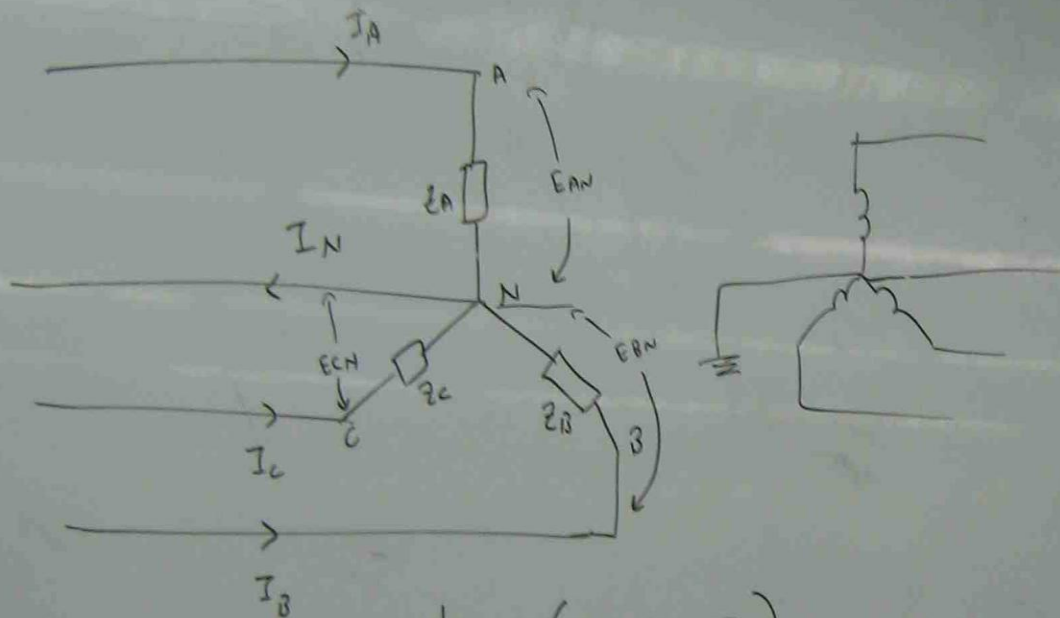


THREE PHASE FOUR WIRE STAR CONNECTED UNBALANCED LOAD



$$I_A = \frac{E_{AN}}{Z_A}$$

$$I_B = \frac{E_{BN}}{Z_B}$$

$$I_C = \frac{E_{CN}}{Z_C}$$

$$I_N = -(I_A + I_B + I_C)$$

Ph A 3φ 4 WIRE 208 V SUPPLIES A STAR CONNECTED UNBALANCED LOAD WHOSE IMPEDANCES ARE


$$Z_A = 10 \angle -60^\circ \Omega$$

$$Z_B = 6 \angle -90^\circ \Omega$$


$$Z_C = 12 \angle 30^\circ \Omega$$

CALCULATE I_A, I_B, I_C, I_N

DRAW THE COMPLETE PHASOR DIAGRAM.

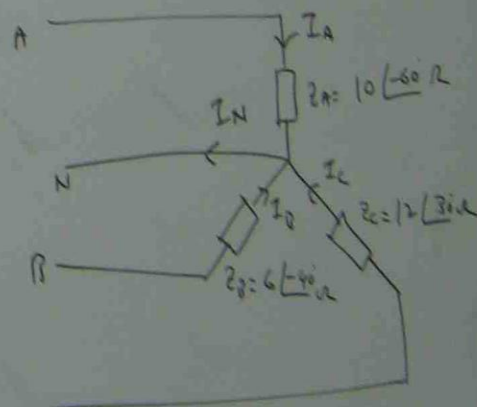
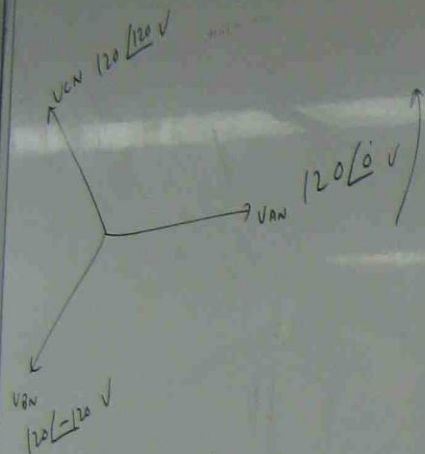
$$V_{AN} = \frac{208}{\sqrt{3}} = 120 \text{ V}$$



$$\bar{I}_A = \frac{\bar{V}_{AN}}{\bar{Z}_A} = \frac{120 \angle 0}{10 \angle -60} = 12 \angle 0 - (-60) = 12 \angle 60 \text{ A}$$


$$\bar{I}_B = \frac{\bar{V}_{BN}}{\bar{Z}_B} = \frac{120 \angle -120}{6 \angle -90} = 20 \angle -120 - (-90) = 20 \angle -120 + 90 = 20 \angle -30 \text{ A}$$


$$\bar{I}_C = \frac{\bar{V}_{CN}}{\bar{Z}_C} = \frac{120 \angle 120}{12 \angle 30} = 10 \angle 120 - 30 = 10 \angle 90 \text{ A}$$

$$\begin{aligned} \bar{I}_N &= -(\bar{I}_A + \bar{I}_B + \bar{I}_C) \\ &= -(12 \angle 60 + 20 \angle -30 + 10 \angle 90) \\ &= -(12(\cos 60 + j \sin 60) + 20(\cos 30 - j \sin 30) + 10(\cos 90 + j \sin 90)) \\ &= -(6 + j10.39 + 17.32 - j10 + j10) \\ &= -(23.32 + j10.39) \\ &= -23.32 - j10.39 \end{aligned}$$

$$= \sqrt{23.32^2 + 10.39^2} \angle -(180 - \tan^{-1} \frac{10.39}{23.32})$$

$$= 25.53 \angle -156' \text{ Amp}$$


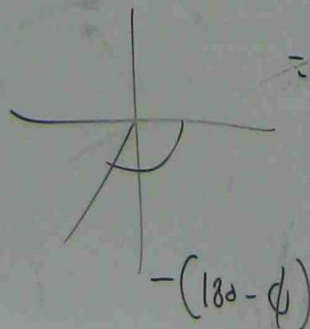


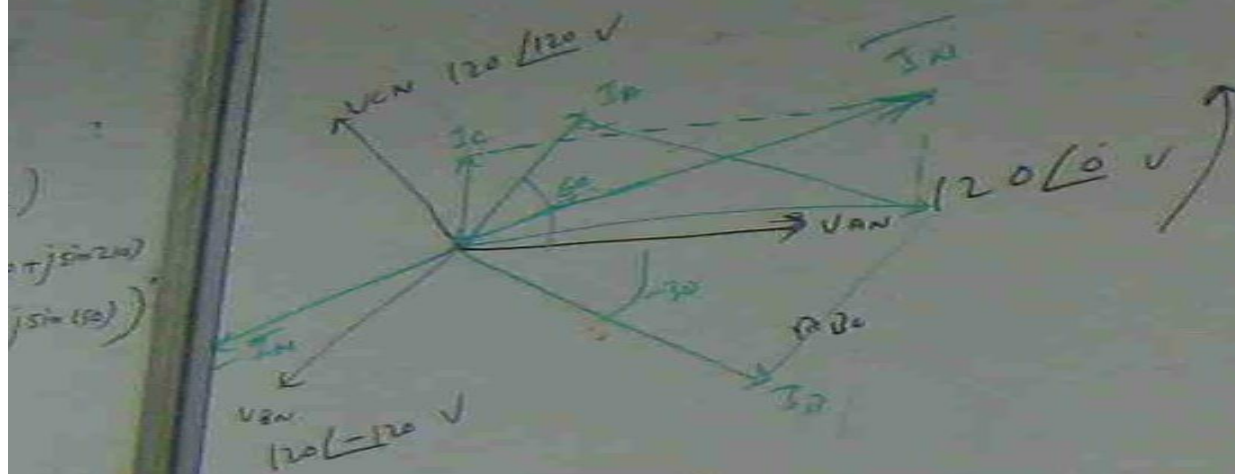

$$\bar{I}_A = \frac{\bar{V}_{AN}}{\bar{Z}_A} = \frac{120 \angle 0}{10 \angle -60} = 12 \angle 0 - (-60)$$

$$\bar{I}_B = \frac{\bar{V}_{BN}}{\bar{Z}_B} = \frac{120 \angle -120}{6 \angle -90}$$

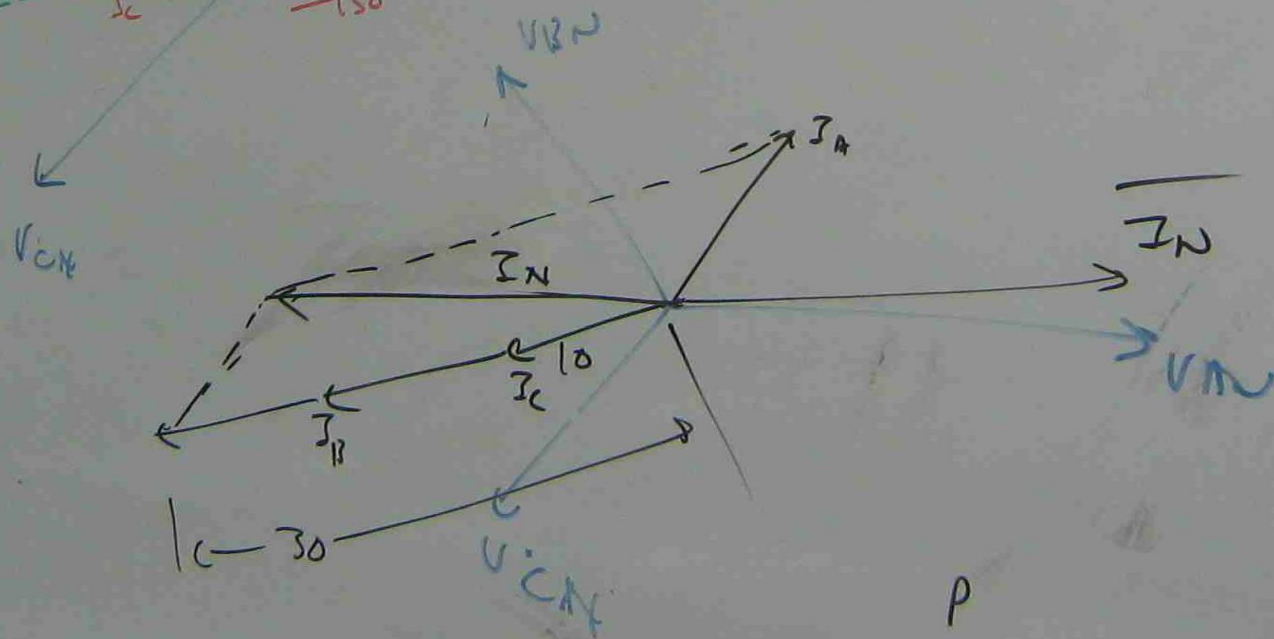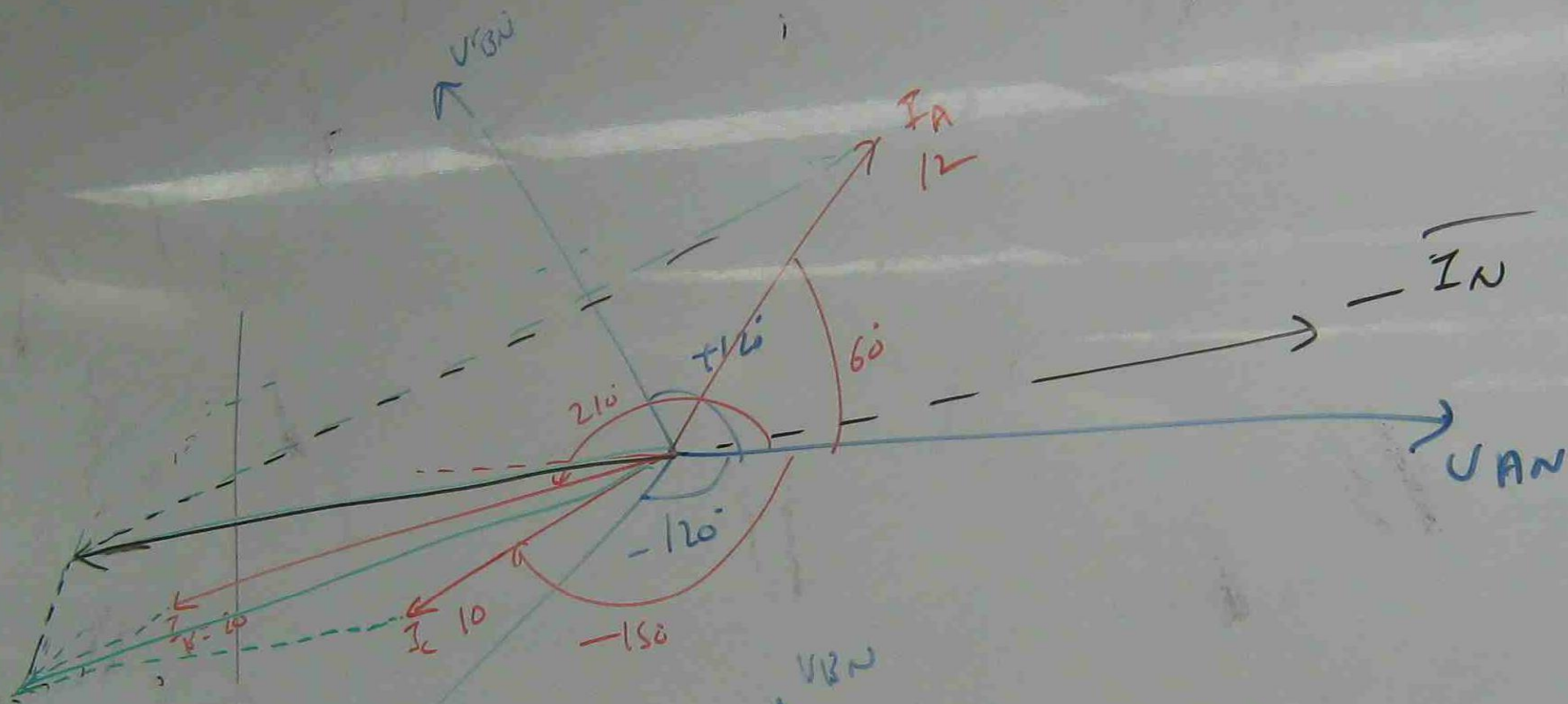
$$\bar{I}_C = \frac{\bar{V}_{CN}}{\bar{Z}_C} = \frac{120 \angle 120}{12 \angle 30}$$



EFFECT OF PHASE REVERSAL ON LOAD CURRENTS

ph

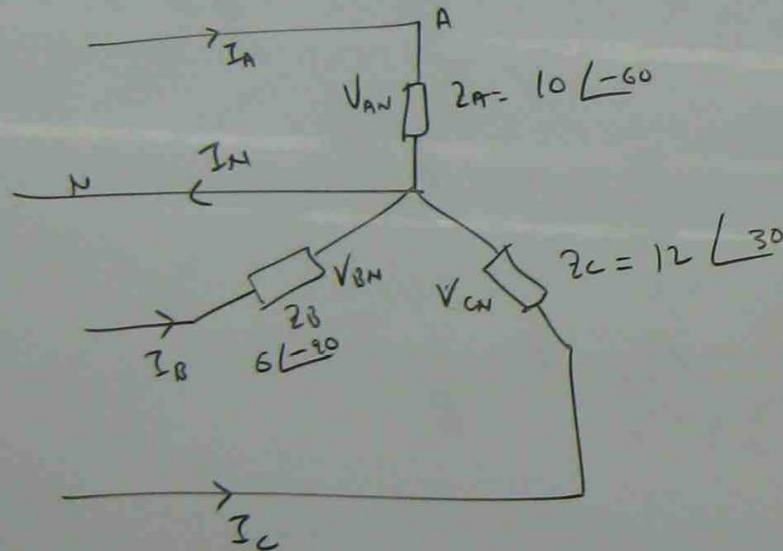IN ABOVE PROBLEM, IF PHASE SEQUENCE IS ACB (OR) CBA, WHAT WILL HAPPEN TO LINE CURRENTS AND NEUTRAL CURRENT?



$$V_{AN} = \frac{208}{\sqrt{3}} = 120$$

$$V_{BN} = 120 \angle +120^\circ$$

$$V_{CN} = 120 \angle -120^\circ$$

ACB (OR) CBA

$$\bar{I}_A = \frac{\bar{V}_{AN}}{\bar{Z}_A} = \frac{120 \angle 0^\circ}{10 \angle -60^\circ} = 12 \angle 60^\circ \text{ A}$$

$$\bar{I}_B = \frac{\bar{V}_{BN}}{\bar{Z}_B} = \frac{120 \angle +120^\circ}{6 \angle -90^\circ} = 20 \angle (120 - (-90)) = 20 \angle 210^\circ \text{ A}$$

$$\bar{I}_C = \frac{\bar{V}_{CN}}{\bar{Z}_C} = \frac{120 \angle -120^\circ}{12 \angle 30^\circ} = 10 \angle -150^\circ \text{ A}$$

$$\bar{I}_{IN} = -(\bar{I}_A + \bar{I}_B + \bar{I}_C)$$

$$= - (12 \angle 60^\circ + 20 \angle 240^\circ + 10 \angle -150^\circ)$$


$$= - (12 (\cos 60^\circ + j \sin 60^\circ) + 20 (\cos 240^\circ + j \sin 240^\circ) + 10 (\cos 150^\circ - j \sin 150^\circ))$$

$$= - (-20 - j4.6)$$

$$= 20 + j4.6$$

$$= \sqrt{20^2 + 4.6^2} \angle \tan^{-1} \frac{4.6}{20}$$

$$= 20.5 \angle 13^\circ \text{ A}$$

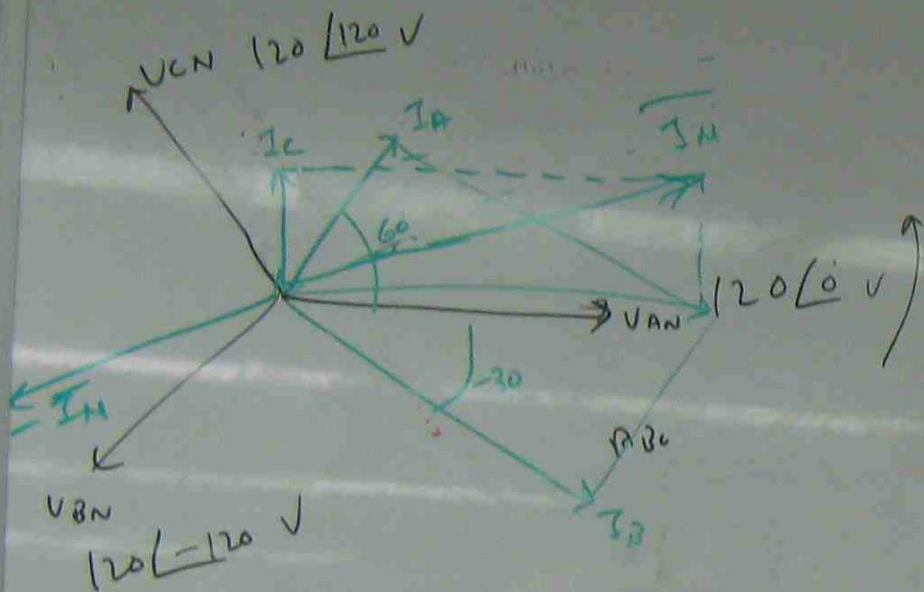

$$\overline{I_A} = \frac{\overline{V_{AN}}}{\overline{Z_A}} = \frac{120 \angle 0}{10 \angle -60} = 12 \angle 0 - (-60) = 12 \angle 60 \text{ A}$$

$$\overline{I_B} = \frac{\overline{V_{BN}}}{\overline{Z_B}} = \frac{120 \angle -120}{6 \angle -90} = 20 \angle -120 - (-90) = 20 \angle -120 + 90 = 20 \angle -30 \text{ A}$$

$$\overline{I_C} = \frac{\overline{V_{CN}}}{\overline{Z_C}} = \frac{120 \angle 120}{12 \angle 30} = 10 \angle 120 - 30 = 10 \angle 90 \text{ A}$$

$$\bar{I}_N = -(\bar{I}_A + \bar{I}_B + \bar{I}_C)$$

$$= - (12 \angle 60^\circ + 20 \angle -30^\circ + 10 \angle 90^\circ)$$

$$= - (12(\cos 60^\circ + j \sin 60^\circ) + 20(\cos 30^\circ - j \sin 30^\circ) + 10(\cos 90^\circ + j \sin 90^\circ))$$

$$= - (6 + j10.39 + 17.32 - j10 + j10)$$

$$= - (23.32 + j10.39)$$

$$= -23.32 - j10.39$$

$$= \sqrt{23.32^2 + 10.39^2} \angle - (180 - \tan^{-1} \frac{10.39}{23.32})$$

$$= 25.53 \angle -156^\circ \text{ Amp}$$

