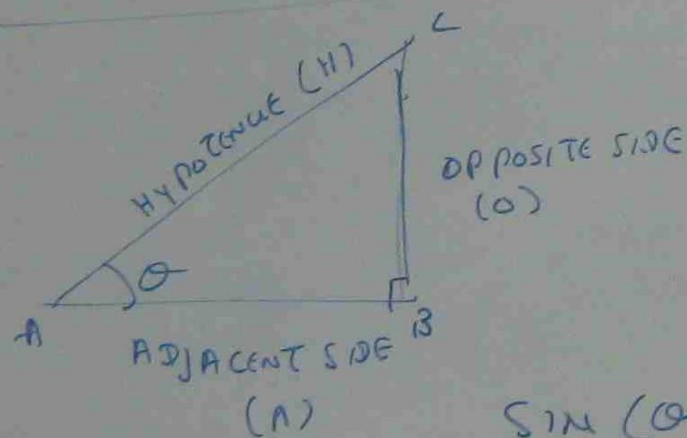


# WEE NEE G 002 B SOLVE PROBLEMS IN LOW VOLTAGE SINGLE PHASE AND THREE PHASE CIRCUIT

## BASIC TRIGONOMETRY



SIN	COS	TAN	COT	SEC	Cosec
O	A	O	A	H	H
H	H	A	O	A	O

$$\sin(\theta) = \frac{BC}{AC}$$

$$\cos \theta = \frac{AB}{AC}$$

$$\tan \theta = \frac{BC}{AB}$$

$$\cot \theta = \frac{AB}{BC}$$

$$\sec \theta = \frac{AC}{AB}$$

$$\csc \theta = \frac{AC}{BC}$$

2

$\sin = +$   
 $\cos = -$   
 $\tan = -$

1

$\sin = +$   
 $\cos = +$   
 $\tan = +$

$\sin = -$

$\cos = -$

$\tan = +$

$\sin = -$

$\cos = +$


$\tan = -$

3

4

$$180^\circ = \pi \text{ RADIANS}$$

PHASOR

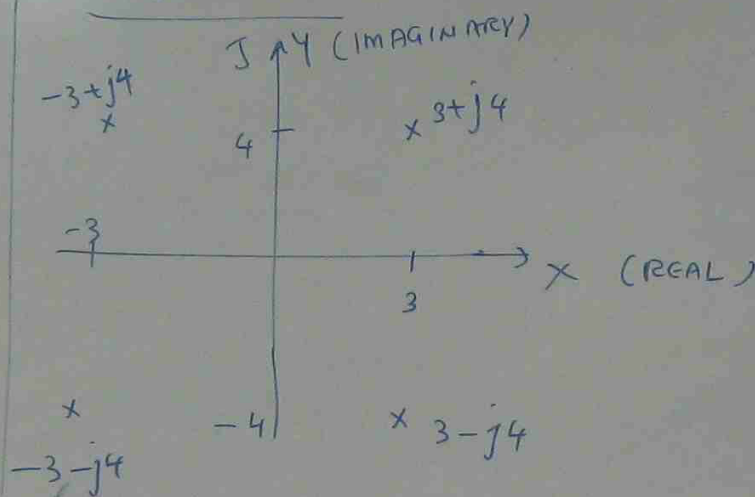

$$\hat{j} = \sqrt{-1}$$

$3+j4 = \text{RECTANGULAR FORM}$


$$\sqrt{3^2+4^2} \angle \tan^{-1} \frac{4}{3} = 5 \angle 53.2^\circ$$

← POLAR FORM

$$3 - j4 = \sqrt{3^2 + 4^2} \angle -\tan^{-1} \frac{4}{3} = 5 \angle -53.2^\circ$$


$$-3 + j4 = \sqrt{3^2 + 4^2} \angle 180 - \tan^{-1} \frac{4}{3} = 5 \angle 180 - 53.2^\circ$$

$$= 5 \angle 126.8^\circ$$

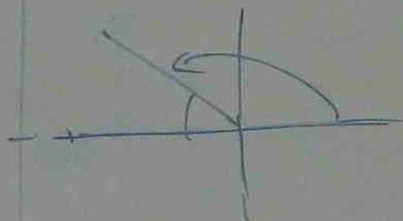

$$-3 - j4 = \sqrt{3^2 + 4^2} \angle -(180 - \tan^{-1} \frac{4}{3})$$

$$= 5 \angle -126.8^\circ$$

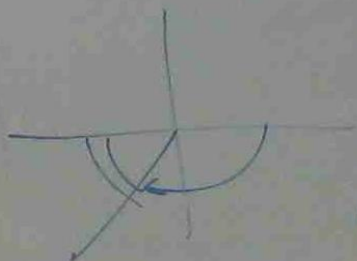

POLAR  $\rightarrow$  RECTANGULAR


$$Z \angle \theta = Z \cos \theta + j Z \sin \theta$$

$$5 \angle 53.2^\circ = 5 (\cos 53.2^\circ) + j 5 (\sin 53.2^\circ)$$

$$5 \angle -126.8^\circ = 5 (\cos (-126.8^\circ)) + j 5 (\sin (-126.8^\circ))$$


2.  
CAR Form

# PARSER DIAGRAM

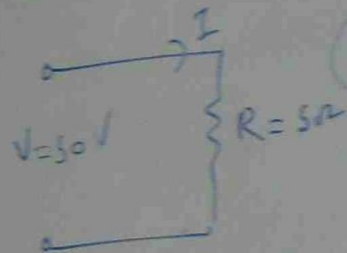


RESISTIVE CIRCUIT

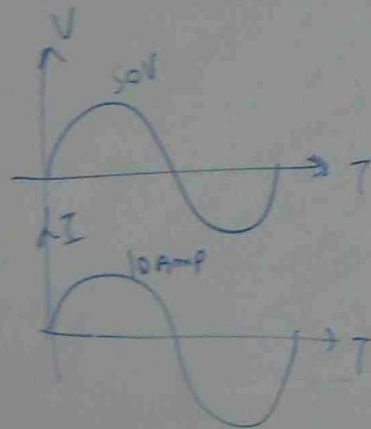
$$I = \frac{50V}{5\Omega} = 10 \text{ Amp}$$



WAVE FORM

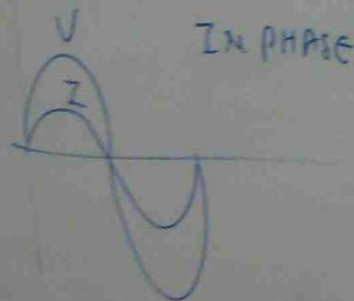




# VECTOR | PARSER DIAGRAM

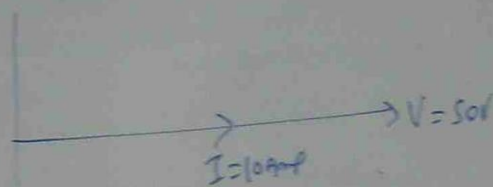

$$Z = \frac{V}{I} = \frac{50 \angle 0}{10 \angle 0} = 5 \angle 0$$

POLAR FORM

INDUCTIVE CIRCUIT

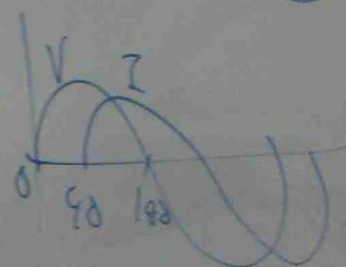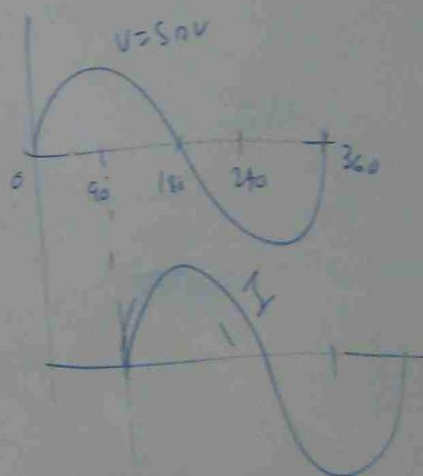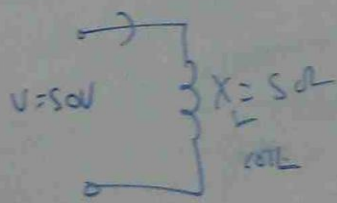

CURRENT IS 90 LAG



$$V = 50 \angle 0$$

$$X_L = \frac{V}{I}$$


$$Z_1 \angle \theta_1$$

$$Z_2 \angle \theta_2$$

$$Z_1 \angle \theta_1 \times Z_2 \angle \theta_2$$



CURRENT IS  $90^\circ$  LAGGING VOLTAGE

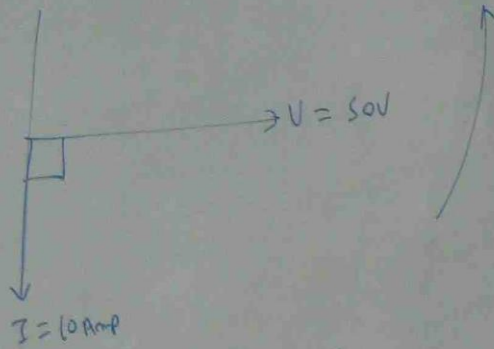




$$V = 50 \angle 0^\circ \text{ V}, \quad I = 10 \angle -90^\circ \text{ Amp.}$$

$$X_L = \frac{V}{I} = \frac{50 \angle 0^\circ}{10 \angle -90^\circ} = 5 \angle 0 - (-90) = 5 \angle 90^\circ$$

$$\frac{Z_1 \angle \theta_1}{Z_2 \angle \theta_2} = \left( \frac{Z_1}{Z_2} \right) \angle \theta_1 - \theta_2$$

$$Z_1 \angle \theta_1 \times Z_2 \angle \theta_2 = (Z_1 Z_2) \angle \theta_1 + \theta_2$$

CAPACITIVE CIRCUIT

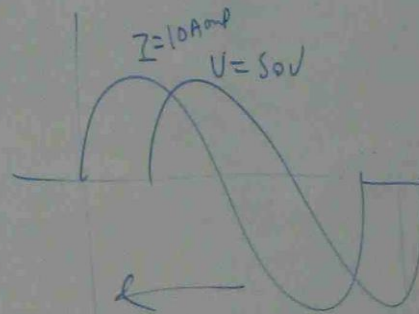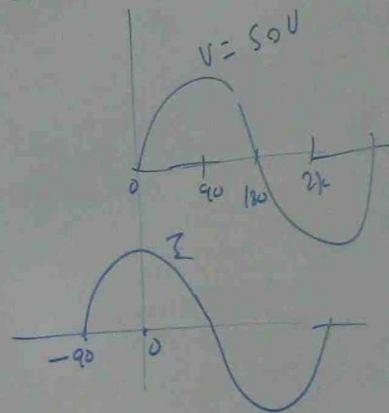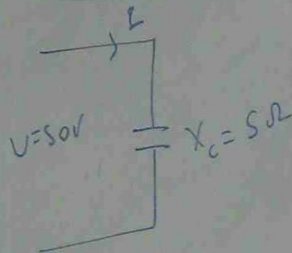


CURRENT LEADS VOLTAGE BY  $90^\circ$


$$V = 50 \angle 0^\circ$$

$$X_C = 5 \angle -90^\circ$$

$$I = \frac{V}{X_C} = \frac{50 \angle 0^\circ}{5 \angle -90^\circ} = 10 \angle +90^\circ \text{ Amp}$$


$$I = 10 \text{ Amp}$$

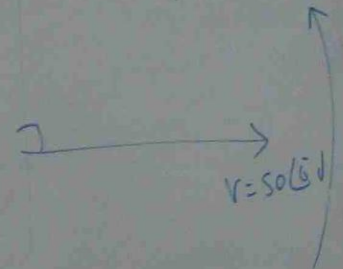

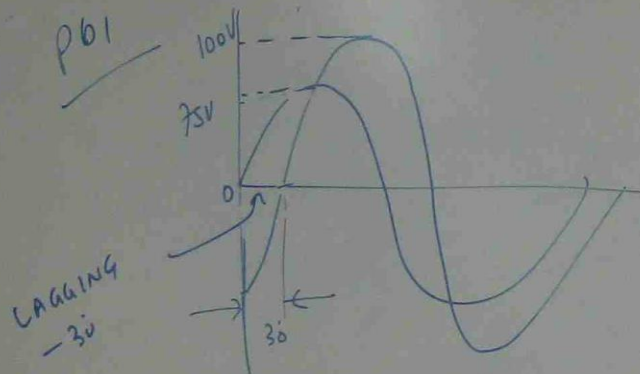


DRAW THE VECTOR DIAGRAM FOR ABOVE WAVE FORM


$$75 \angle 0 \quad 100 \angle -30$$

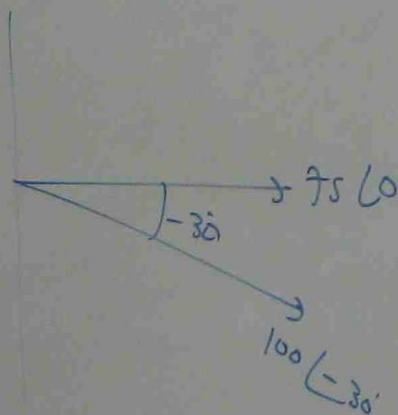

Pb 2

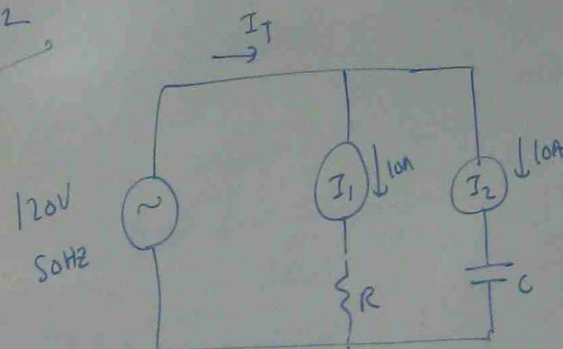


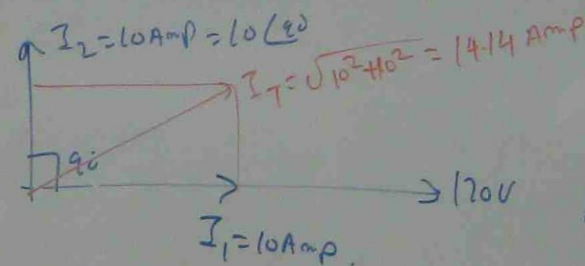DRAW THE VECTOR DIAGRAM FOR GIVEN CIRCUIT






pb (3)


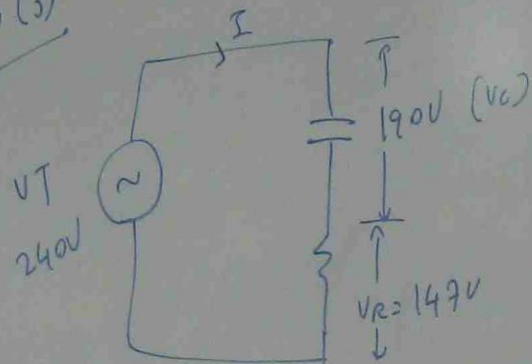


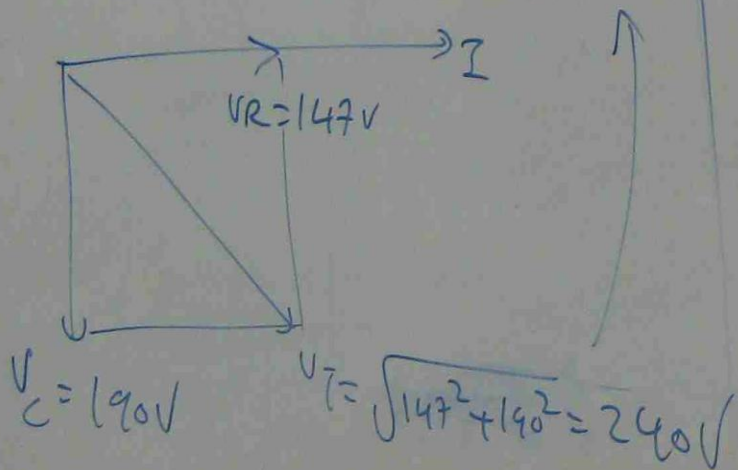DRAW THE VECTOR DIAGRAM FOR GIVEN CIRCUIT.




pb (4)

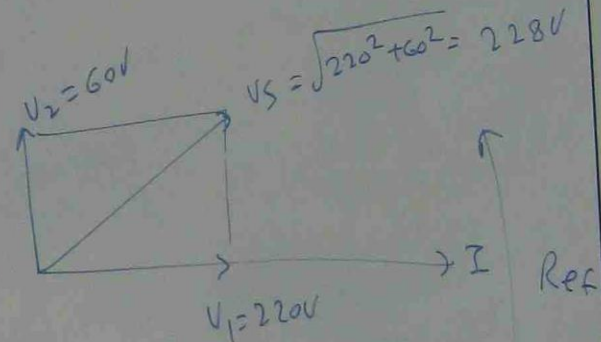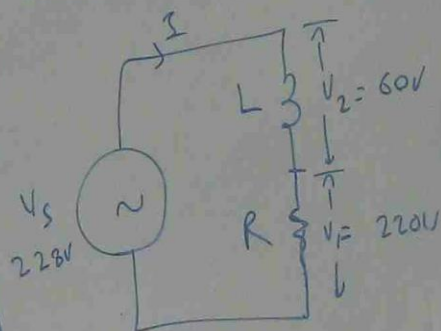THE CIRCUIT SHOWS A CHOKE (INDUCTOR) IN SERIES WITH A RESISTIVE INDUSTRIAL OVEN. THE VOLTAGE ACROSS THE RESISTOR IS IN PHASE WITH THE CURRENT AND THE VOLTAGE ACROSS THE INDUCTOR LEADS THE CURRENT BY  $90^\circ$ . DRAW A PHASOR DIAGRAM FOR THE CIRCUIT SHOWING  $V_1$ ,  $V_2$  AND  $V_S$ .



# AC THEORY

## ALTERNATING QUANTITIES

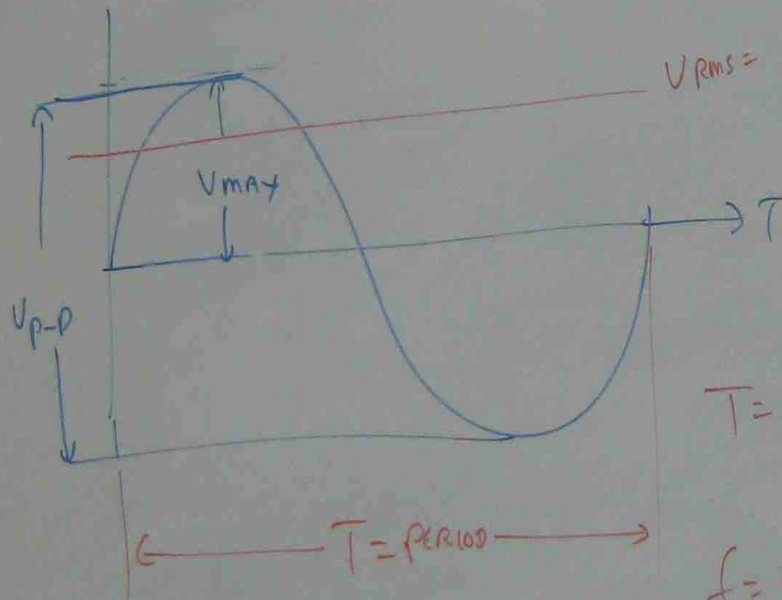


$$V_{RMS} = \frac{V_{max}}{\sqrt{2}} = \frac{V_{max}}{1.4142}$$

$$T = \frac{1}{f}$$

$f$  = Frequency

$T$  = Second

TIME DOMAIN  $\omega = 2\pi f$

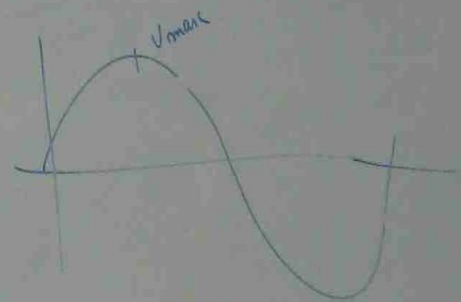


$$V(t) = V_{max} (\sin \omega t)$$



$$V(t) = V_{max} \sin(\omega t + \theta)$$



$$\omega = 2\pi f$$

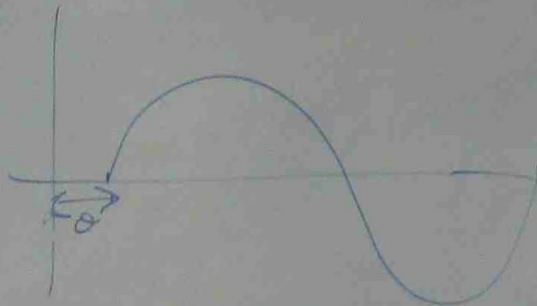

$$V(t) = V_{\max} \sin(\omega t - \phi)$$

$$\text{Average value} = \frac{V_{\max}}{\sqrt{2}}$$

FREQUENCY DOMAIN


$$V(t) = V_{\max} \sin \omega t \rightarrow \frac{V_{\max}}{\sqrt{2}} \angle 0$$

$$V(t) = V_{\max} \sin(\omega t + \phi) \rightarrow \frac{V_{\max}}{\sqrt{2}} \angle +\phi$$

$$V(t) = V_{\max} \sin(\omega t - \phi) \rightarrow \frac{V_{\max}}{\sqrt{2}} \angle -\phi$$

Q1 THE VALUE OF LINE VOLTAGE WHICH IS USED ON APPLIANCE RATING PLATE FOR AC SUPPLY IS RMS VALUE.

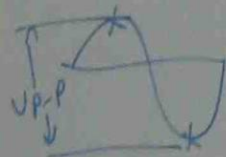Q2 THE VOLTAGE MEASURED BETWEEN THE MAXIMUM POSITIVE AND NEGATIVE VALUE OF SINE WAVE IS PEAK TO PEAK VOLTAGE.



Q3 THE FREQUENCY OF A SINE WAVE THAT HAS A PERIOD OF 10 MILLISECOND IS

$$f = \frac{1}{T} = \frac{1}{10 \times 10^{-3}} \\ = \frac{10^3}{10} = 100 \text{ Hz}$$

Q4 IF THE INSTANTANEOUS VALUE OF CURRENT IS 10 AMP AT ANGLE OF  $30^\circ$

THE RMS VALUE OF CURRENT IS \_\_\_\_\_

$$I_{\text{sin } \theta} = \text{INSTANTANEOUS VALUE} \quad \left| \quad I_{\text{max}} = \frac{10}{\sin 30} = \frac{10}{0.5} = 20 \text{ Amp}$$

$$I_{\text{max}} \quad I_{\text{sin } 30} = 10 \quad \left| \quad I_{\text{Rms}} = \frac{I_{\text{max}}}{\sqrt{2}} = \frac{20}{1.4142} = 14.14 \text{ Amp}$$

Q5 A SINE WAVE HAS PEAK VALUE 390V. DETERMINE

(a) RMS VOLTAGE

(b) AVERAGE VOLTAGE

$$(a) U_{\text{Rms}} = \frac{U_{\text{max}}}{\sqrt{2}} = \frac{390}{1.4142} = 275 \text{ V}$$

$$(b) U_{\text{Avg}} = \frac{U_{\text{max}}}{\pi} = \frac{390}{3.1416} = 124.14 \text{ V}$$

Q6 A SINE WAVE HAS A MAXIMUM VALUE OF 100V AND FREQUENCY OF 50Hz  
DETERMINE THE VALUE OF WAVE FORM AT

(a) 30 ELECTRICAL DEGREE (b) 90 ELECTRICAL DEGREE (c) 270 ELECTRICAL DEGREE

(c) AFTER TIME LAPSE OF 4 milli seconds.


(a)  $V_{max} \sin 30 = 100 \times 0.5 = 50V$

(b)  $V_{max} \sin 90 = 100 \times 1 = 100V$

(c)  $V_{max} \sin 270 = 100 \times (-1) = -100V$

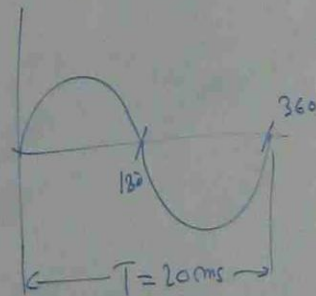(d)  $T = \frac{1}{f} = \frac{1}{50} = \frac{1000 \text{ ms}}{50} = 20 \text{ ms}$

$\frac{20 \text{ ms}}{4} \rightarrow \frac{360}{?} = \frac{360 \times 4}{20} = 72$



$V_{max} \sin 72 = 100 \sin 72 = 95V$

Q7 DETERMINE THE PERIODIC TIME FOR THE FOLLOWING WAVE FORMS

(a) 50Hz SINE WAVE (b) 125 Hz SQUARE WAVE

(c) 1000 Hz TRIANGULAR WAVE

(a)  $T = \frac{1}{f} = \frac{1}{50} = 0.02s$  (b)  $T = \frac{1}{125} = 8 \text{ ms}$

(c)  $T = \frac{1}{1000} = 1 \text{ ms}$

Q8 CALCULATE THE FREQUENCIES FOR THE FOLLOWING PERIODIC TIMES.

(a) 0.02 sec

(b) 0.0167 sec

(c) 0.2 millisecond

(a)  $f = \frac{1}{T} = \frac{1}{0.02} = 50 \text{ Hz}$


(b)  $f = \frac{1}{T} = \frac{1}{0.0167} = 60 \text{ Hz}$

(c)  $f = \frac{1}{T} = \frac{1}{0.2 \times 10^{-3}} = \frac{10^3}{0.2} = \frac{10^4}{2} = 5000 \text{ Hz}$



Q9 FOR THE WAVE FORM SHOWN IN FIGURE  
DETERMINE THE

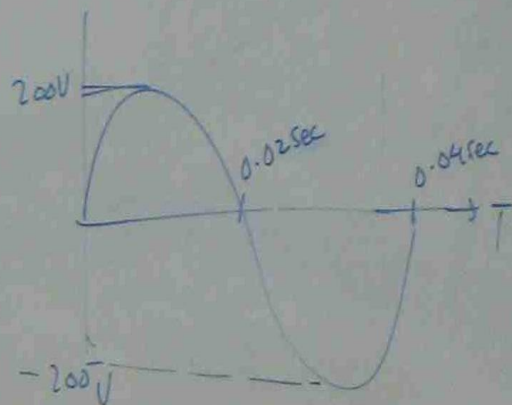- (a) MAXIMUM VOLTAGE
- (b) FREQUENCY
- (c) PERIOD
- (d) PEAK TO PEAK VALUE
- (e) RMS VALUE



$$(a) 200V$$

$$(b) f = \frac{1}{T} = \frac{1}{0.04}$$

$$= \frac{100}{4}$$

$$= 25 \text{ Hz}$$

$$(c) T = 0.04 \text{ sec}$$

$$(d) V_{p-p} = 400V$$

$$(e) V_{RMS} = \frac{V_{MAX}}{\sqrt{2}}$$

$$= \frac{200}{1.4142}$$

$$= 141.42V$$


Q10

A SINGLE CONDUCTOR OF LENGTH 1.5m IS MOVING THROUGH A MAGNETIC FIELD OF 0.5 TESLA AT VELOCITY OF 2 m/s. DETERMINE THE INDUCED VOLTAGE OF THE CONDUCTOR IN THE MAGNETIC FIELD AT

- (a) 90° (b) 45° (c) 60°

$$B = 0.5 \text{ T} \quad L = 1.5 \text{ m} \quad U = 2 \text{ m/s}$$

VELOCITY

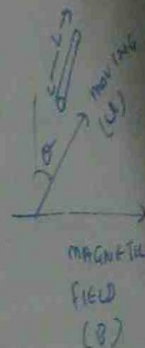

$$\text{INDUCED VOLTAGE IN MOVING CONDUCTOR} = B L U \sin \theta$$

$$V = B L U \sin \theta$$


$$(a) V = 0.5 \times 1.5 \times 2 \sin 90^\circ = 1.5V$$

$$(b) V = 0.5 \times 1.5 \times 2 \sin 45^\circ = 1.5 \times 0.707 = 1.06V$$

$$(c) V = 0.5 \times 1.5 \times 2 \sin 60^\circ = 1.5 \times 0.866 = 1.3V$$

## REVIEW QUESTIONS

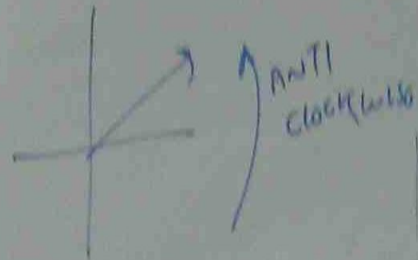(1) PHASOR NORMALLY ROTATE IN ANTI CLOCK WISE



(2) IN PRACTICE, AC QUANTITIES BY PHASOR DIAGRAM.

THE PHASORS ARE NORMALLY DRAWN TO SCALE TO

REPRESENT RMS VALUE

(3) PHASORS ARE QUANTITIES WHICH VARY IN MAGNITUDE AND DIRECTION

(4) THE RESULTANT OF TWO VOLTAGES HAVING THE SAME ANGLE OF LAG BUT DIFFERENT NUMERICAL VALUES CAN BE DETERMINED BY —


NUMERICAL SUBTRACTION

$$\overbrace{\quad}^3 \overbrace{\quad}^4 = 4 - 3$$

NUMERICAL ADDITION

$$\overbrace{\quad}^4 \overbrace{\quad}^3 = 4 + 3$$

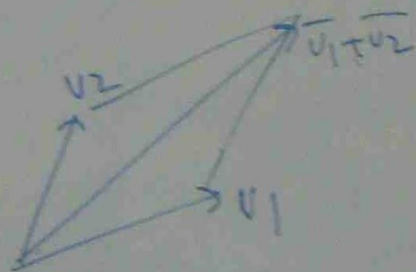(5) THE RESULTANT OF TWO OR MORE VOLTAGES DIFFERING IN PHASE MAY BE DETERMINED BY ALGEBRAIC ADDITION (OR) SUBTRACTION



$$V_1 - V_2 = V_1 + (-V_2)$$

