
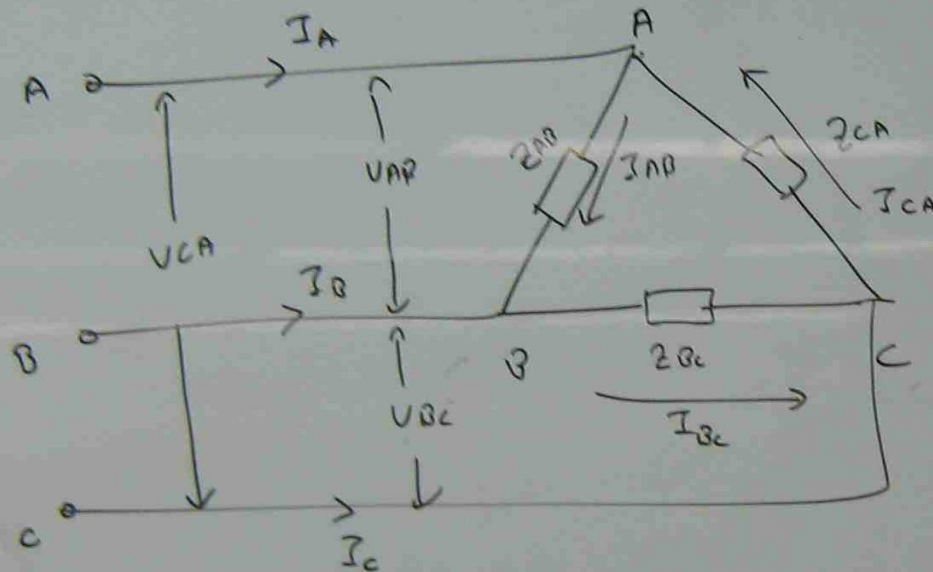


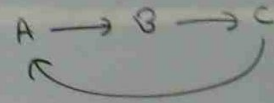CALCULATION OF CURRENTS IN DELTA CONNECTED UNBALANCED LOAD



SEQUENCE ABC



$$I_{AB} = \frac{V_{AB}}{Z_{AB}}$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}}$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}}$$

A POINT Flow in = Flow out

$$I_A + I_{CA} = I_{AB} \Rightarrow I_A = I_{AB} - I_{CA}$$

B POINT


$$I_B + I_{AB} = I_{BC} \Rightarrow I_B = I_{BC} - I_{AB}$$

C POINT

$$I_C + I_{BC} = I_{CA}$$


$$I_C = I_{CA} - I_{BC}$$

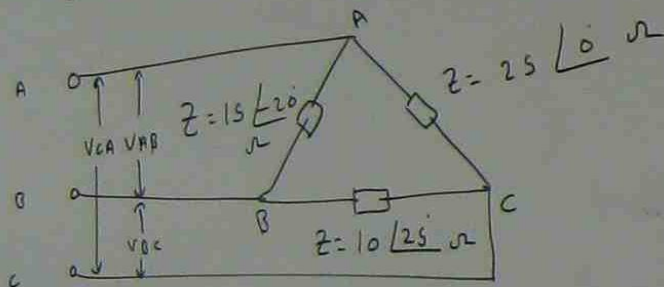ph CALCULATE THE LINE CURRENTS FOR THE LOAD SHOWN IN FIGURE.



SUPPLY VOLTAGE = 300V

PHASE SEQUENCE = A, B, C

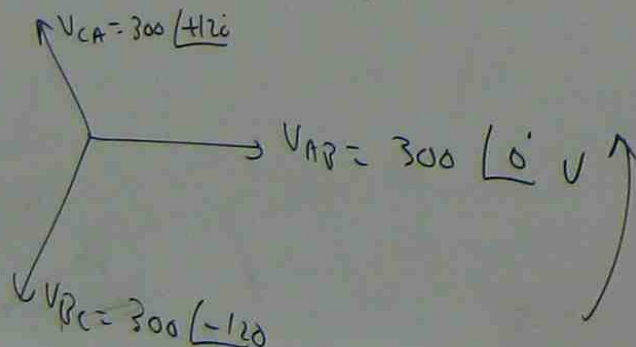

$$I_{AB} = \frac{V_{AB}}{Z_{AB}} = \frac{300 \angle 0}{15 \angle -20} = 20 \angle 20 \text{ A}$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}} = \frac{300 \angle -120}{10 \angle 25} = 30 \angle -145 \text{ A}$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}} = \frac{300 \angle +120}{25 \angle 0} = 12 \angle 120 \text{ A}$$

$$I_A = I_{AB} - I_{CA}$$

$$= 20 \angle 20 - 12 \angle 120$$


$$= 20 (\cos 20 + j \sin 20) - 12 (\cos 120 + j \sin 120)$$

$$= 18.79 + j 6.84 + 6 - j 10.39$$

$$= 24.79 - j 3.55$$

$$= \sqrt{24.79^2 + 3.55^2} \angle -\tan^{-1} \frac{3.55}{24.79}$$

$$= 25 \angle -81 \text{ A}$$
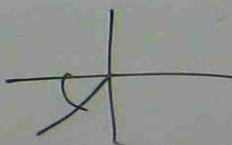
$$\begin{aligned}
 I_B &= I_{BC} - I_{AB} = 30 \angle -145^\circ - 20 \angle 20^\circ \\
 &= 30 (\cos(-145^\circ) + j \sin(-145^\circ)) - 20 (\cos 20^\circ + j \sin 20^\circ) \\
 &= -24.57 - j17.2 - 13.79 - j6.84 \\
 &= -43.36 - j24.04 \\
 &= \sqrt{43.36^2 + 24.04^2} \angle -(180^\circ - \tan^{-1} \frac{24.04}{43.36}) \\
 &= 49.6 \angle -151^\circ \text{ A}
 \end{aligned}$$


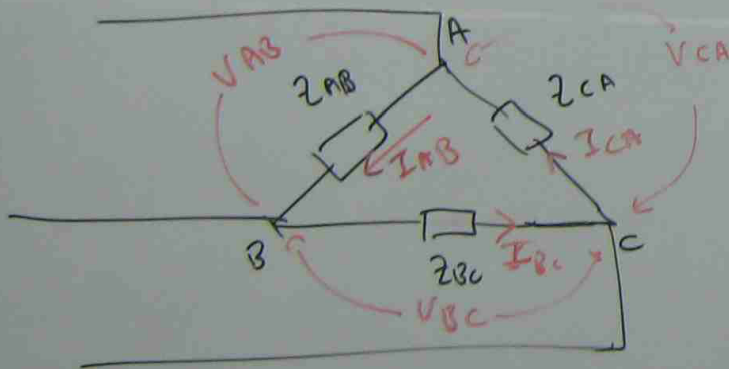
$$\begin{aligned}
 I_C &= I_{CA} - I_{BC} \\
 &= 12 \angle 120^\circ - 30 \angle -145^\circ \\
 &= 12 (\cos 120^\circ + j \sin 120^\circ) - 30 (\cos(-145^\circ) + j \sin(-145^\circ)) \\
 &= -6 + j10.39 - 30 (\cos 145^\circ - j \sin 145^\circ) \\
 &= -6 + j10.39 + 24.57 + j17.2 \\
 &= 18.57 + j27.6 \\
 &= \sqrt{18.57^2 + 27.6^2} \angle \tan^{-1} \frac{27.6}{18.57} \\
 &= 33.3 \angle 56^\circ \text{ A}
 \end{aligned}$$

CALCULATION OF POWER IN DELTA CONNECTED UNBALANCED LOAD

CALCULATE 3ϕ power for ABOVE PROBLEM.

FOR BALANCED LOAD, 3ϕ power = $\sqrt{3} E_L I_L \cos\theta$

FOR UNBALANCED LOAD, THIS FORMULA CAN NOT BE USED.



$$3\phi \text{ power for UNBALANCED} = V_{AB} I_{AB} \cos\theta_{I_{AB}} + V_{BC} I_{BC} \cos\theta_{I_{BC}} + V_{CA} I_{CA} \cos\theta_{I_{CA}}$$

Δ LOAD

$$V_{AB} = 300 \angle 0^\circ$$


$$V_{BC} = 300 \angle -120^\circ$$

$$V_{CA} = 300 \angle +120^\circ$$

$$I_{AB} = 20 \angle 20^\circ$$


$$I_{BC} = 30 \angle -145^\circ$$

$$I_{CA} = 12 \angle 120^\circ$$

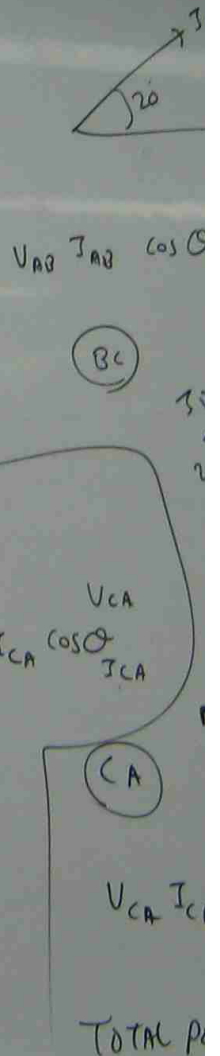


TOTAL P

(AB)

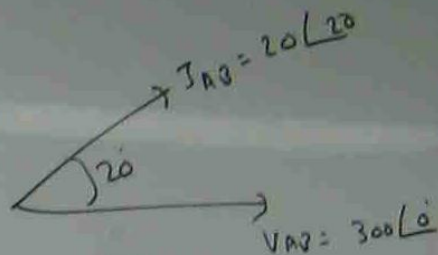

$$V_{AB} I_{AB} \cos \theta_{I_{AB}}^{V_{AB}} = 300 \times 20 \cos 20^\circ = 5638 \text{ W}$$


(BC)

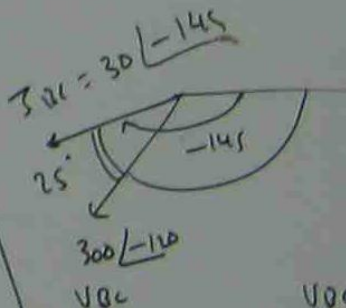

$$V_{BC} I_{BC} \cos \theta_{I_{BC}}^{V_{BC}} = 300 \times 30 \cos 25^\circ = 8156.8 \text{ W}$$

$$+ V_{CA} I_{CA} \cos \theta_{I_{CA}}^{V_{CA}}$$

(CA)

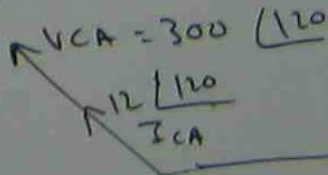


$$V_{CA} I_{CA} \cos \theta_{I_{CA}}^{V_{CA}} = 300 \times 12 \times \cos 0^\circ = 3600 \text{ W}$$

$$\text{TOTAL POWER} = 5638 + 8156.8 + 3600 = 17395 \text{ W}$$

EFFECT OF PHASE REVERSAL ON LOAD CURRENTS

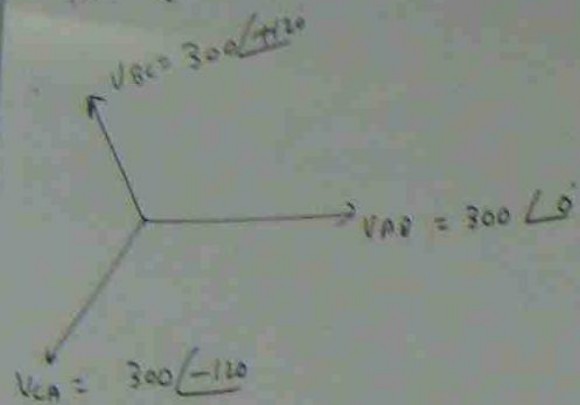Q IN ABOVE PROBLEM IF PHASE SEQUENCE IS CHANGED TO ACB (CBA), WHAT WILL BE LINE CURRENTS AND POWER?



$$I_{AB} = \frac{V_{AB}}{Z_{AB}} = \frac{300 \angle 0^\circ}{15 \angle -20^\circ} = 20 \angle 20^\circ \text{ A}$$

$$I_{BC} = \frac{V_{BC}}{Z_{BC}} = \frac{300 \angle 120^\circ}{10 \angle 25^\circ} = 30 \angle 95^\circ \text{ A}$$

$$I_{CA} = \frac{V_{CA}}{Z_{CA}} = \frac{300 \angle -120^\circ}{25 \angle 0^\circ} = 12 \angle -120^\circ \text{ A}$$

$$I_A = I_{AB} - I_{CA} = 20 \angle 20^\circ - 12 \angle -120^\circ = 20(\cos 20^\circ + j \sin 20^\circ) - 12(\cos(-120^\circ) + j \sin(-120^\circ))$$

$$= 18.77 + j6.84 - 6 + j10.39 = 24.77 + j17.32$$

$$= \sqrt{24.77^2 + 17.32^2} \angle \tan^{-1} \frac{17.32}{24.77}$$

$$I_B = I_{BC} - I_{AB} = 30 \angle 95^\circ - 20 \angle 20^\circ = 30(\cos 95^\circ + j \sin 95^\circ) - 20(\cos 20^\circ + j \sin 20^\circ)$$

$$= -2.61 + j29.89 - 18.77 - j6.84$$

$$= -21.4 + j23.05$$

$$= \sqrt{21.4^2 + 23.05^2} \angle 180^\circ - \tan^{-1} \frac{23.05}{21.4}$$

$$= 31.45 \angle 132.9^\circ \quad A$$

$$I_C = I_{CA} - I_{BC} = 12 \angle -120^\circ - 30 \angle 95^\circ$$

$$= 12(\cos(-120^\circ) + j \sin(-120^\circ)) - 30(\cos 95^\circ + j \sin 95^\circ)$$

$$= -6 - j10.39 + 2.61 - j29.89$$

$$= -3.4 - j40.28 = \sqrt{3.4^2 + 40.28^2} \angle \left(180^\circ + \tan^{-1} \frac{40.28}{3.4} \right)$$

$$= 40.4 \angle -94.8^\circ$$

A

