



FIND THE VOLTAGE AT A
FIND CURRENT FLOW TO Z

$$V_B = ?$$

$$V_B = \sqrt{\left(V_c + \frac{Q X_{BC}}{V_c}\right)^2 + \left(\frac{P X_{BC}}{V_c}\right)^2}$$

$$V_B = \sqrt{\left(1 + \frac{0.2 \times 0.5}{1}\right)^2 + \left(\frac{0.5 \times 0.5}{1}\right)^2}$$

$$V_B = \sqrt{(1.1)^2 + (0.25)^2}$$

$$= 1.12 \text{ pu}$$



$$V_A = \sqrt{\left(V_B + \frac{Q_1 X_{AB}}{V_B}\right)^2 + \left(\frac{P_1 X_{AB}}{V_B}\right)^2}$$

$$(P_1, \theta_1) = \text{Power Flow To Z} + \text{Power Loss IN BC} + \text{Power Flow To Load}$$

$$P_2 = \frac{V_B^2}{Z} \cos \theta_2 \quad Q_2 = \frac{V_B^2}{Z} \sin \theta_2 \quad + \quad 0.5 = P \quad 0.2 = Q$$

$$\theta_2 = \frac{V_B^2}{Z} \sin \theta_2$$

$$P_2 = \frac{V_B^2}{Z} \cos \theta_2 = \frac{1.12^2}{2} \cos 36.8^\circ = 0.5 \text{ pu}$$

$$Q_2 = \frac{V_B^2}{Z} \sin \theta_2 = \frac{1.12^2}{2} \sin 36.8^\circ = 0.37 \text{ pu}$$

$$I_{BC} = \frac{P + jQ}{V_c} = \frac{0.5 + j0.2}{1} = \sqrt{0.5^2 + 0.2^2} = 0.53$$

$$Q_{BC} = I_{BC}^2 X_{BC} = (0.53)^2 \times 0.5 = 0.145$$

$$P_1 = P_2 + P = 0.5 + 0.5 = 1 \text{ pu}$$

$$Q_1 = Q_2 + Q_{gc} + Q = 0.37 + 0.145 + 0.2$$

$$= 0.72 \text{ pu}$$

$$E_A = \sqrt{\left(V_B + \frac{Q_1 \times AB}{V_B} \right)^2 + \left(\frac{P_1 \times AB}{V_B} \right)^2}$$

$$= \sqrt{\left(1.12 + \frac{0.72 \times 0.25}{1.12} \right)^2 + \left(\frac{1 \times 0.25}{1.12} \right)^2}$$

