
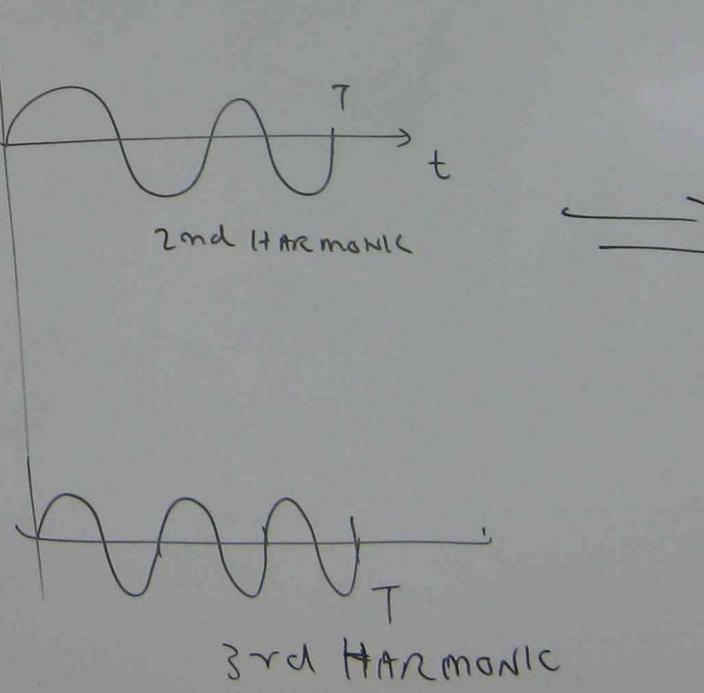


## HARMONICS IN TRANSFORMERS

WHEN ELECTRICAL SUPPLY IS PROVIDED TO TRANSFORMER, THE INDUCTANCE RESISTS THE BUILDING UP OF MAGNETIC FLUX AND MAIN VOLTAGE.


THE TRANSFORMER VOLTAGE OUT PUT CONSISTS OF THE VOLTAGES WHICH FREQUENCIES ARE HIGHER THAN FUNDAMENTAL.

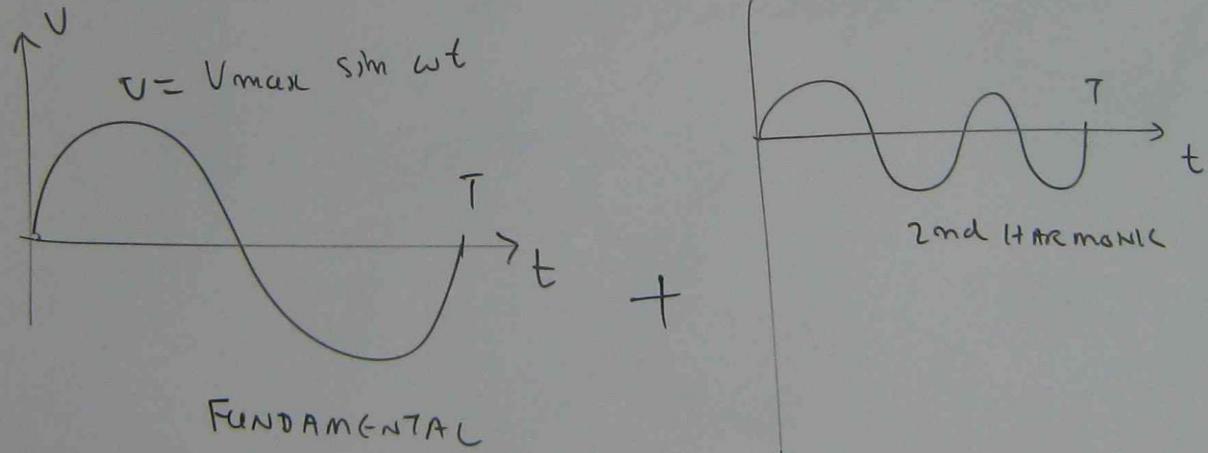DUE TO HARMONICS EFFECT, THE MAIN VOLTAGE WAVE FORM IS DISTORTED



Transformer can distort the output wave form. It is required to provide appropriate transformer core and winding design (or) harmonics filter to eliminate the harmonic.

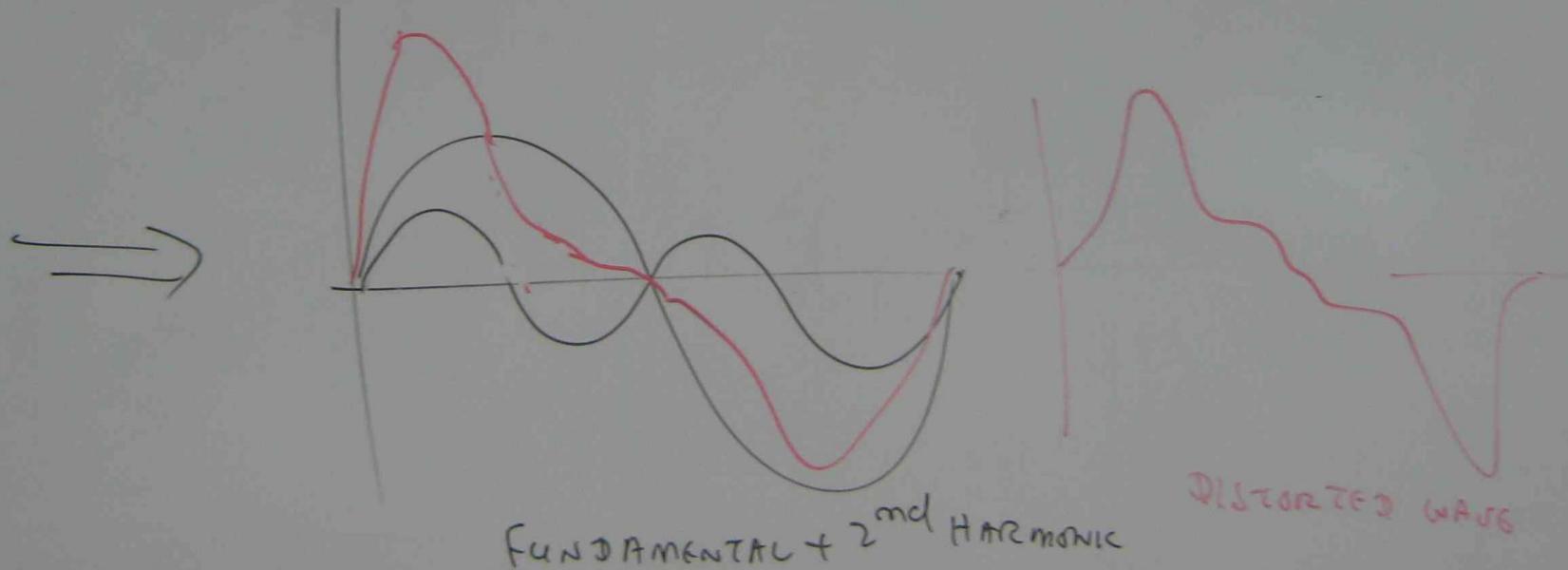Harmonic wave can degrade the quality of transformer insulation dielectric strength.



HARMONIC CAUSES DISTORTION OF WAVE FORM

CORE LOSS IS INCREASED

CORE LOSS  $\propto$  FREQUENCY

FREQUENCY ↑ → CORE LOSS ↑

PHASE RELATIONSHIP

3<sup>rd</sup>, 9<sup>th</sup> - IN PHASE WITH EACH OTHER IN  
EACH PHASE

WAVE

5<sup>th</sup>, 7<sup>th</sup>, 11<sup>th</sup>, 13<sup>th</sup> - DISPLACED BY 120°


HARMONIC EFFECT DEPENDS ON

- (i) WHETHER PHASES ARE MAGNETICALLY SEPARATED (OR) LINKED
- (ii) WHETHER PHASES ARE ELECTRICALLY SEPARATED (OR) LINKED.

EFFECT OF TRANSFORMER CONNECTION ON HARMONIC


△ CONNECTION

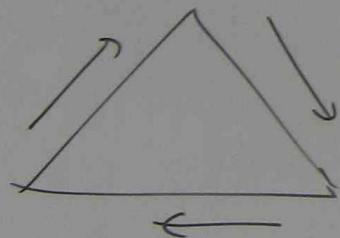HARMONIC CURRENT CAN ONLY FLOW IN  $\Delta$  CONNECTION, CAN NOT FLOW IN  $\lambda$ .



PATH FOR HARMONIC IN TRANSFORMER WINDING.

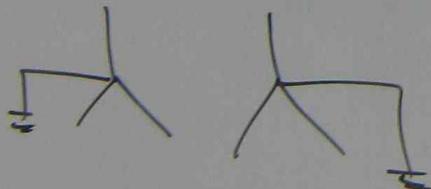HARMONIC CURRENT CIRCULATES IN  $\Delta$ .  
NO HARMONIC CURRENT FLOWS IN TO LINE



$\lambda | \lambda$  WITH NEUTRAL

NEUTRAL WIRE CAN CARRY HARMONIC CURRENT.  
HARMONIC IMPACT ON LOAD CAN BE REDUCED.

## ~~X~~ X WITHOUT NEUTRAL

NO WAY TO FLOW OUT THE HARMONIC CURRENT.



HARMONIC IS COMBINED WITH MAIN CURRENT  
AND MAIN CURRENT WAVE FORM IS DISTORTED.

LOAD SUFFERS THE IMPACT OF HARMONIC.

THE WAYS TO REDUCE / ELIMINATE HARMONIC  
IN POWER TRANSFORMERS


### CORE DESIGN


#### 3 LIMBS CORE

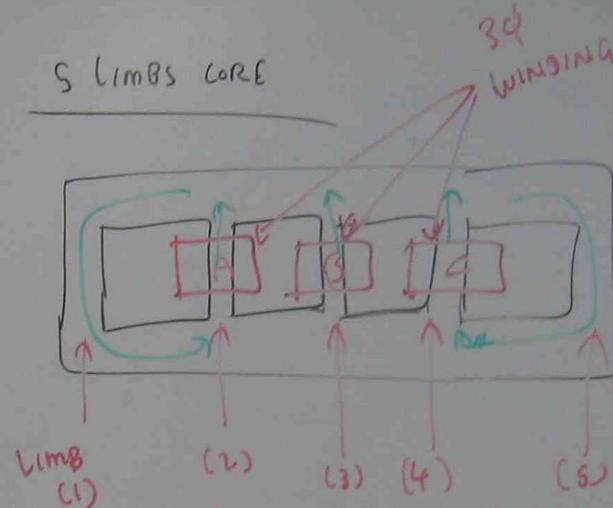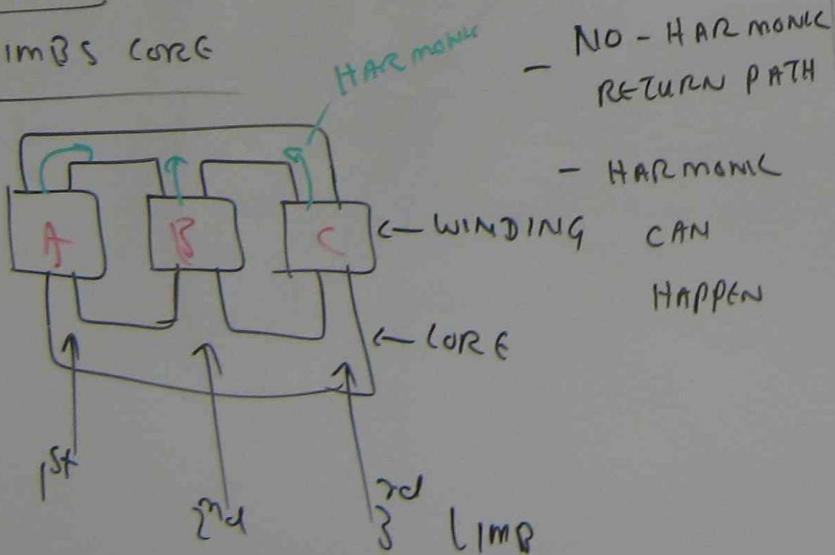

OUTER TWO LIMBS PROVIDE  
HARMONIC RETURN PATH.



### WINDING DESIGN

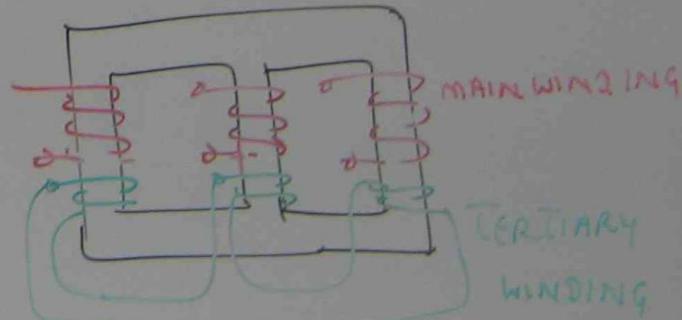

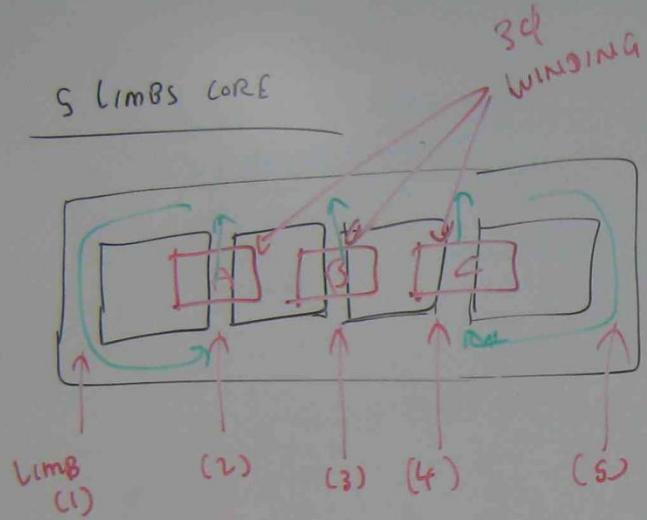

OUTER TWO LIMBS PROVIDE  
HARMONIC RETURN PATH.

WINDING DESIGN

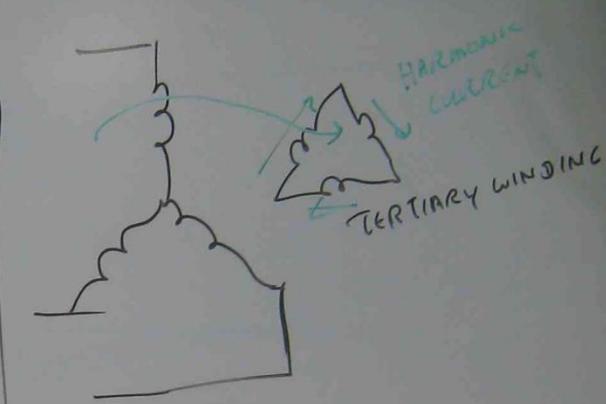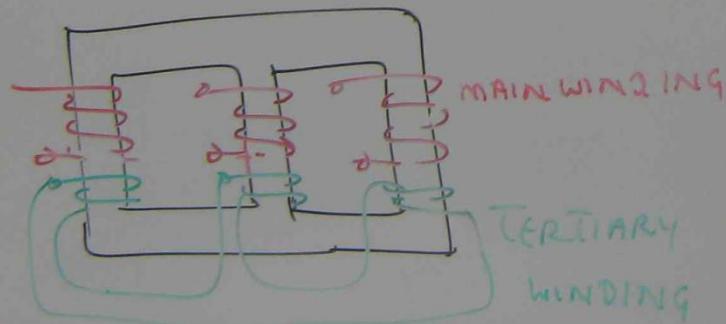

INTERCONNECTED TERTIARY WINDING IS INCLUDED IN POWER TRANSFORMER WINDING. TERTIARY WINDING PROVIDES HARMONIC RETURN PATH SO THAT HARMONIC CURRENT CAN NOT COMBINE WITH MAIN VOLTAGE CURRENT.

## EFFECT OF TRANSFORMER HARMONIC

Q2

- POSITIONAL  $I^2R$  LOSSES OCCUR
- CORE LOSS IS INCREASED
- MAGNETICALLY INTERFERENCE WITH COMMUNICATION CIRCUITS

HARMONIC CAN ALSO CAUSE → (i) DECREASE IN DIELECTRIC STRENGTH  
(ii) ELECTROSTATIC INTERFERENCE WITH  
COMMUNICATION LINES


(iii) RESONANCE OCCURS BETWEEN  
INDUCTANCE OF TRANSFORMER  
WINDING AND CAPACITANCE OF  
FEEDERS.

## HARMONIC GENERATORS


(1) HYSTERESIS EFFECT

$$B = \text{FLUX INTENSITY} = \frac{d \text{ FLUX (wb)}}{A \text{ (CUSA - mm²)}}$$


B-H  
CURVE

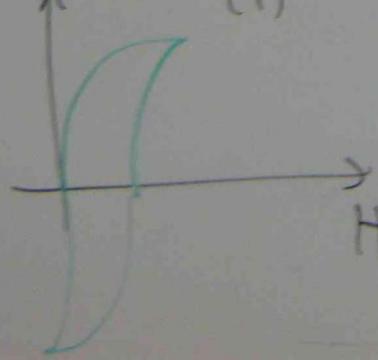

$$Hz \text{ AmpxTURN} = I \times N$$

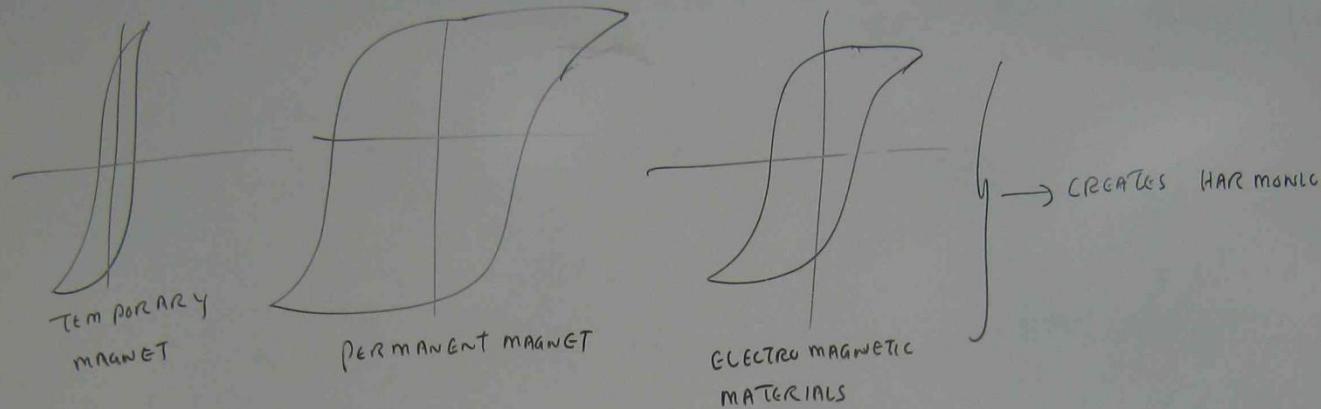

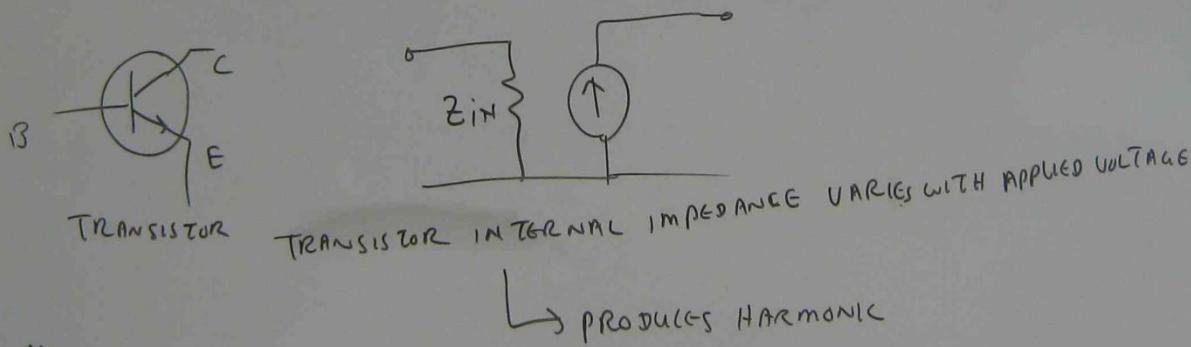
(ii) ELECTRONIC DEVICES WHICH IMPEDANCE VARIES WITH APPLIED E.M.F



(iii) NON SINUSOIDAL WAVE PRODUCERS

OSCILLATOR - SQUARE WAVE

↓ SAW TOOTH WAVE


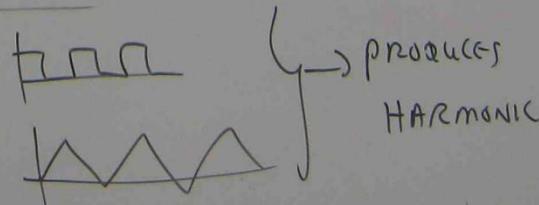


## DEVICES THAT PRODUCE HARMONIC

- ROTATING ELECTRICAL MACHINES
- GASEOUS DISCHARGE LAMPS
- ARC FURNACES
- RECTIFIERS

- LONG ANGLES OF FIRING

THYRISTORS

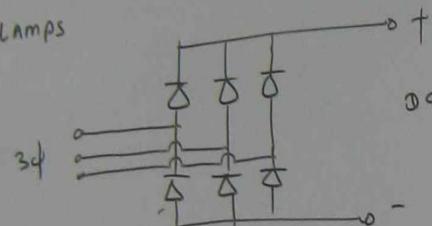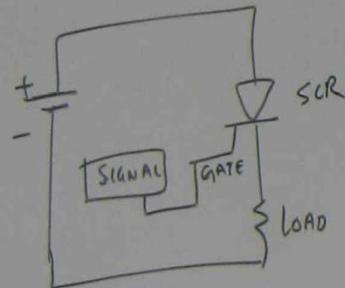

## TUTORIAL (14)

Q1 IN THE FOLLOWING CONNECTIONS OF 3 $\phi$  TRANSFORMER, WHICH ONE CAN CARRY HARMONIC CURRENT AND WHICH ONE CAN NOT CARRY IT ?

D d, Y d, D Y, YY WITHOUT NEUTRAL, YY WITH NEUTRAL

Q2 WHAT ARE DISADVANTAGES OF HARMONIC ?

Q3 SKETCH 3<sup>rd</sup> HARMONIC FLUX

Q1  $\Delta\Delta(\Delta d)$  CARRY HARMONIC

$\lambda\Delta(Yd)$  ONLY  $\Delta$  SIDE CARRIES HARMONIC

$\Delta Y(DY)$

YY WITHOUT NEUTRAL  $\rightarrow$  CAN NOT CARRY HARMONIC

YY WITH NEUTRAL  $\rightarrow$  NEUTRAL WIRE CARRIES HARMONIC

TUTORIAL (14)

Q1 IN THE FOLLOWING CONNECTIONS OF 3 $\phi$  TRANSFORMER, WHICH ONE CAN CARRY HARMONIC CURRENT AND WHICH ONE CAN NOT CARRY IT?

D<sub>d</sub>, Y<sub>d</sub>, D<sub>y</sub>, YY WITHOUT NEUTRAL, YY WITH NEUTRAL

Q2 WHAT ARE DISADVANTAGES OF HARMONIC?

Q3 SKETCH 3<sup>rd</sup> HARMONIC FLUX


Q1  $\Delta\Delta$  (D<sub>d</sub>) CARRY HARMONIC

$\lambda\Delta$  (Y<sub>d</sub>) ONLY  $\Delta$  SIDE CARRIES HARMONIC

$\Delta Y$  (D<sub>y</sub>)

YY WITHOUT NEUTRAL  $\rightarrow$  CAN NOT CARRY HARMONIC

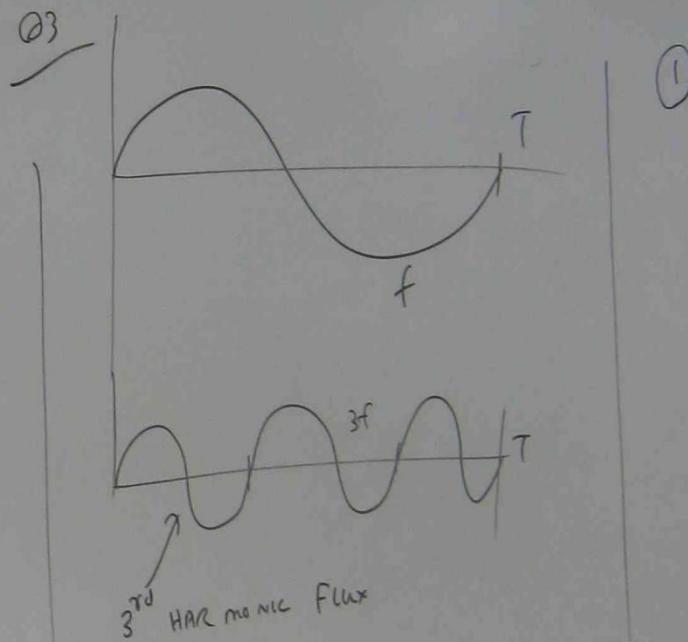YY WITH NEUTRAL  $\rightarrow$  NEUTRAL WIRE CARRIES HARMONIC




REVIEW QUESTIONS FOR SECTION (6)

1. WITH THE AID OF SIMPLE WAVE FORM EXPLAIN THE FORMATION OF HARMONIC IN THE SECONDARY OF TRANSFORMER

2. SKETCH THE EFFECT OF ODD HARMONIC ON SECONDARY VOLTAGE OF A TRANSFORMER

3. SKETCH THE EFFECT OF EVEN HARMONIC ON SECONDARY VOLTAGE OF TRANSFORMER

①

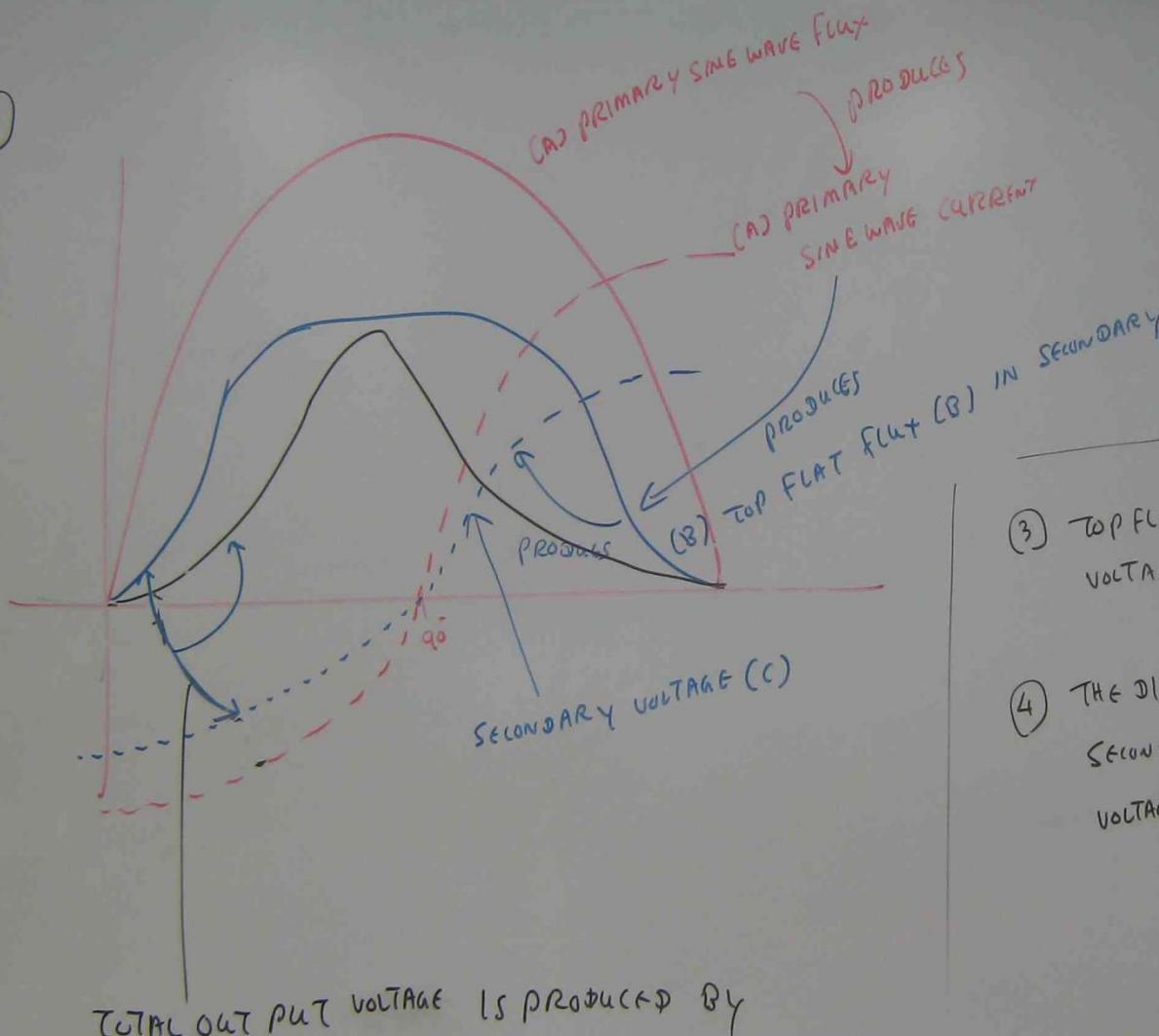

(A) PRIMARY SINE WAVE FLUX

PRODUCES

(A) PRIMARY  
SINE WAVE CURRENT

PRODUCES

(B)

TOP FLAT FLUX (B) IN SECONDARY

SECONDARY VOLTAGE (C)

TOTAL OUT PUT VOLTAGE IS PRODUCED BY

PRIMARY & SECONDARY VOLTAGE


① PRIMARY SINE WAVE FLUX (A) PRODUCES  
PRIMARY SINE WAVE CURRENT (A)

② PRIMARY SINE WAVE CURRENT (A)  
PRODUCES TOP FLAT FLUX IN SECONDARY  
(B)


③ TOP FLAT FLUX IN SECONDARY PRODUCES SECONDARY  
VOLTAGE (C)

④ THE DIFFERENCE BETWEEN PRIMARY AND  
SECONDARY FLUXES PRODUCE HARMONIC OUTPUT  
VOLTAGE.

②

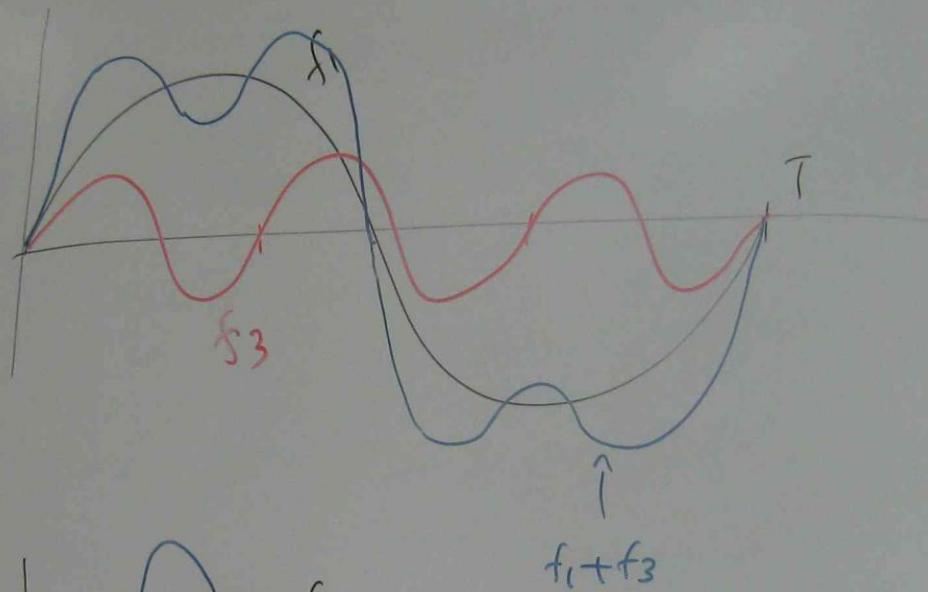

③

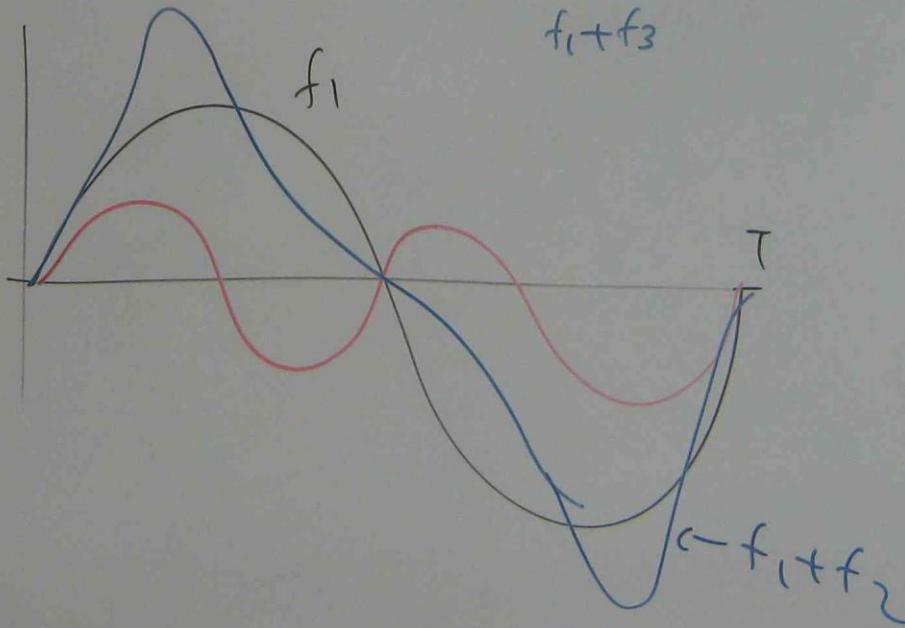


Q4 EXPLAIN THE EFFECT OF THREE WIRE STAR CONNECTION ON THIRD HARMONIC

Q5 EXPLAIN THE EFFECT OF FOUR WIRE STAR CONNECTION ON THIRD HARMONIC

Q6 EXPLAIN THE EFFECT OF DELTA CONNECTION ON THIRD HARMONIC

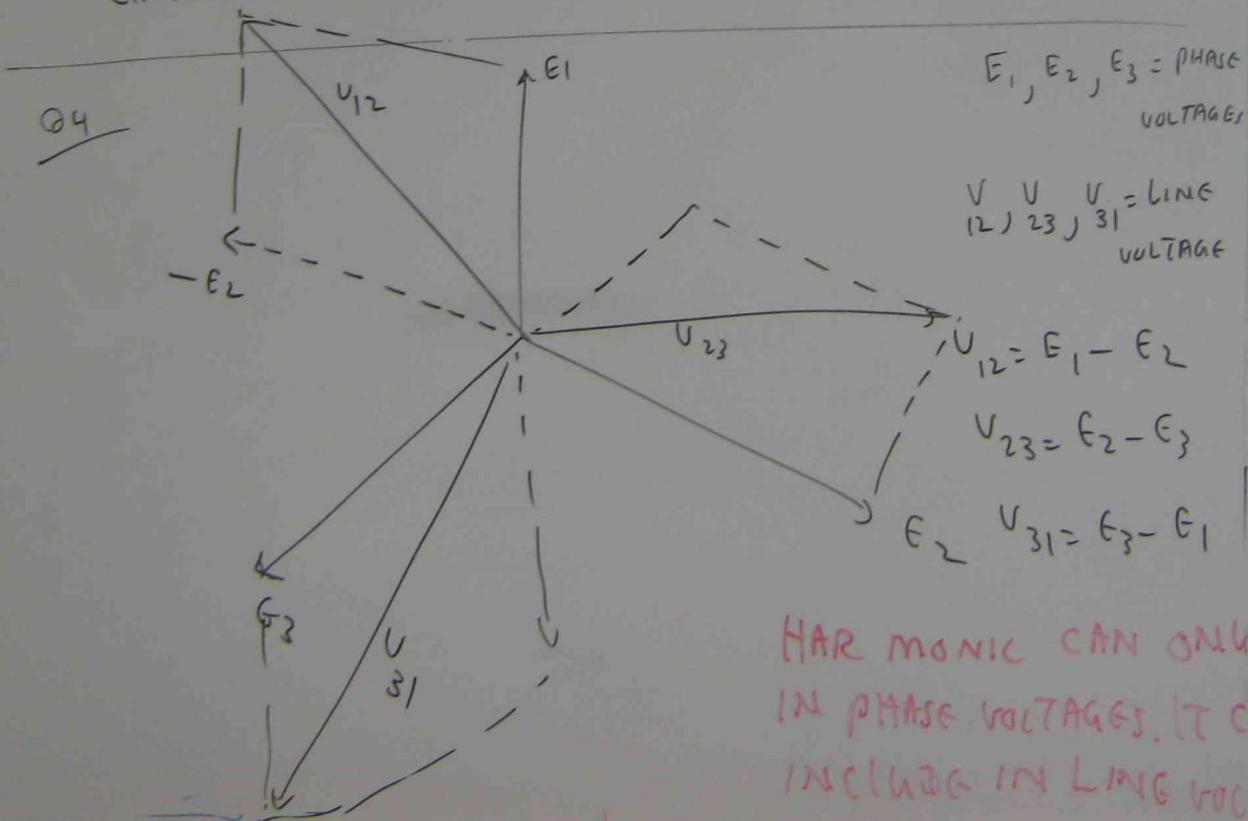Q7 EXPLAIN THE EFFECT OF CORE TYPE AND SHELL TYPE MAGNETIC CIRCUITS ON THIRD HARMONIC



COMBINED 3<sup>rd</sup> HARMONIC

$$V_1 = E_1 +$$

$$V_2 = E_2 +$$

$$V_1 = E_1 +$$

$$V_2 = E_2 +$$

$$V_{12} = V_1 - V_2 = (E_1 -$$

$$-(E_1 + E_2))$$

$$= (E_1 + E_2)$$

$$= E_1 + E_2$$

$$\rightarrow = E_1 - E_2$$

ON THREE PHASE

ON THIRD HARMONIC

2<sup>nd</sup> HARMONIC

1<sup>st</sup> TYPE MAGNETIC

$E_1, E_2, E_3$  = PHASE  
VOLTAGE

$V_{12}, V_{23}, V_{31}$  = LINE  
VOLTAGE

$$V_{12} = E_1 - E_2$$

$$V_{23} = E_2 - E_3$$

$$V_{31} = E_3 - E_1$$

HARMONIC CAN ONLY INCLUDE

THIS IN THREE, IT CAN NOT

BE IN LINE VOLTAGE

COMBINED 3<sup>rd</sup> HARMONIC

$$\text{F}_{\text{AV}} \sim$$

$$E_{3\text{rd}} = E_{3\text{max}} \sin 3\omega t \rightarrow \text{PHASE 1}$$

$$E_{3\text{rd HARMONIC}} = E_{3\text{max}} \sin 3(\omega t - 120^\circ) \rightarrow \text{PHASE 2}$$

PH 2

$$V_1 = E_1 + E_{3\text{rd HARMONIC}} (\text{PH 1})$$

$$V_2 = E_2 + E_{3\text{rd HARMONIC}} (\text{PH 2})$$

$$\sin(A - B) = \sin A \cos B - \cos A \sin B$$

$$V_1 = E_1 + E_{3\text{max}} \sin 3\omega t$$

$$V_2 = E_2 + E_{3\text{max}} \sin 3(\omega t - 120^\circ) = E_2 + E_{3\text{max}} \sin(3\omega t - 360^\circ)$$

$$V_{12} = V_1 - V_2 = (E_1 + E_{3\text{max}} \sin 3\omega t) - (E_2 + E_{3\text{max}} \sin(3\omega t - 360^\circ))$$

$$= (E_1 + E_{3\text{max}} \sin 3\omega t) - (E_2 + E_{3\text{max}} (\sin 3\omega t \cos 360^\circ - \cos 3\omega t \sin 360^\circ))$$

$$= (E_1 + E_{3\text{max}} \sin 3\omega t) - (E_2 + E_{3\text{max}} \sin 3\omega t)$$

$$= E_1 + E_{3\text{max}} \sin 3\omega t - E_2 - E_{3\text{max}} \sin 3\omega t$$

$$= E_1 - E_2$$

Q5


THREE HARMONIC VOLTAGES EXIST IN THE PHASE, BUT CAN NOT EXIST IN THE LINE VOLTAGE.  
THE THIRD HARMONIC CURRENTS FLOW IN THE PHASES AND THE LINES AND RETURN IN THE FOURTH WIRE.

Q6

THE THIRD HARMONIC VOLTAGES IN THE 3 PHASES ARE IN SERIES AROUND DELTA AND THEY CAUSE A THIRD HARMONIC CURRENT TO CIRCULATE.

IT IS NOT POSSIBLE TO MEASURE THE THIRD HARMONIC VOLTAGE WHILE THE DELTA IS CLOSED AS IT CAUSES THE THIRD HARMONIC CURRENT TO FLOW IN THE PHASES. NO THIRD HARMONIC CURRENT EXISTS IN LINES BUT IT EXISTS IN PHASES

CORE TYPE

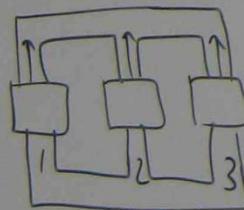


3 LIMBS

THERE IS NO HARMONIC RETURN PATH.

HARMONIC WILL INCLUDES IN LINE CURRENTS.

Q7

SHELL TYPE

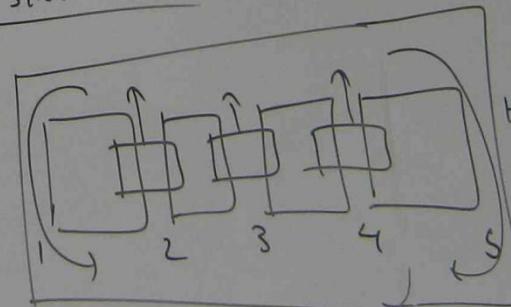

5 LIMBS

HARMONIC RETURN PATH IS PROVIDED.  
HARMONIC WILL ONLY CIRCULATE IN CORE. IT WILL NOT FLOW OUT

Q8

A 100 MVA 3 AUTO TRANSFORMER LINE VOLTAGE

A



↑  
U<sub>Supply</sub> = 23 kV  
↓

B

C

(a)

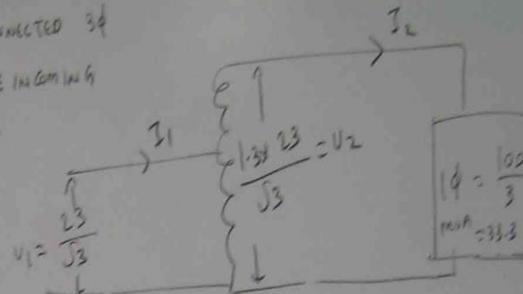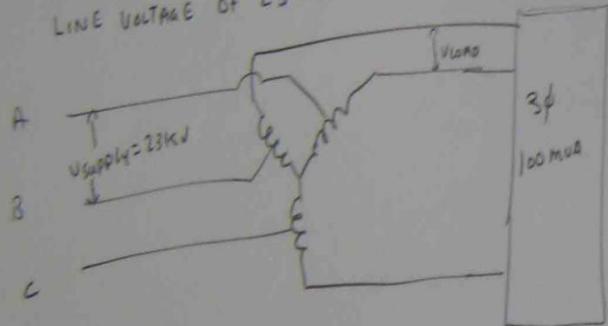Q8 A 100 MVA 3φ LOAD IS TO BE SUPPLIED BY A STAR CONNECTED 3φ AUTO TRANSFORMER WHOSE CONNECTIONS ARE SHOWN BELOW. THE INGINIUS LINE VOLTAGE OF 23 KV IS TO BE BOOSTED BY 30%.



$$I = \frac{V \cdot A}{\text{Voltage}}$$

$$I = \frac{\text{MVA} \times 10^3}{\text{kVA}/\text{pk}}$$

(a) CALCULATE THE CURRENTS IN THE AUTO TRANSFORMER WINDINGS

(b) CALCULATE APPARENT POWER RATING OF AUTO TRANSFORMER.


HARMONIC RETURN PATH IS PROVIDED.  
HARMONIC WILL ONLY CIRCULATE IN CORE. IT WILL NOT FLOW OUT.

$$I_1 = \frac{33.33 \times 10^3}{13.27} = 2486 \text{ Amp.}$$

$$\text{TOTAL POWER} = \frac{1931 \times 3.99 + 13.27 \times 4417}{1000}$$

$$= 66.3 \text{ MVA}$$
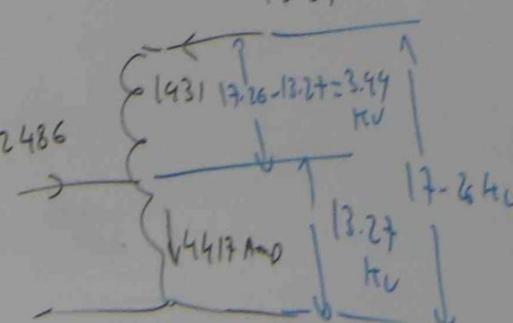
$$3\phi = 66.3 \times 3 = 198 \text{ MVA}$$



REVIEW QUESTIONS



- ① SKETCH CORE TYPE AND SHELL TYPE 34 TRANSFORMER
- ② WHAT ARE MAJOR INSULATION AND MINOR INSULATION
- ③ CALCULATE IRON CORE FLUX DENSITY AND RMS MAGNETIZING CURRENT FOR THE FOLLOWING SINGLE PHASE TRANSFORMER

$$N_p = 400, \quad E_p = 3000 \text{ V RMS}, \quad f = 60 \text{ Hz}$$

CORE C.S.A = 200 sq cm, CORE LENGTH = 230 cm

AIR GAP = 0.4 mm  $\mu_s = 1900$

① CORE TYPE SHELL TYPE

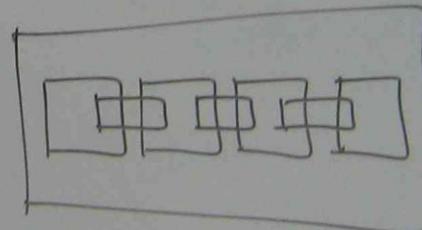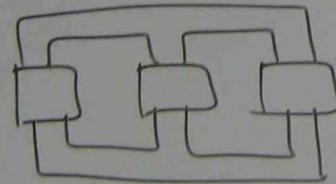

- ② MAJOR INSULATION - INSULATION BETWEEN WINDING AND CORE  
INSULATION BETWEEN H-U AND L-U WINDING

MINOR INSULATION - INSULATION BETWEEN TRANSFORMER TURNS

$$③ E_p = 4.44 \phi f N$$


$$3000 = 4.44 \times \phi \times 60 \times 400$$

$$\phi = \frac{3000}{4.44 \times 60 \times 400}$$

$$= 0.0282 \text{ wb}$$

$$\text{FLUX DENSITY } B = \frac{\phi}{A} = \frac{0.0282}{200 \times (10^2)^2} = 1.41 \text{ T}$$

$$H = \frac{B}{\mu_0 \mu_r}$$

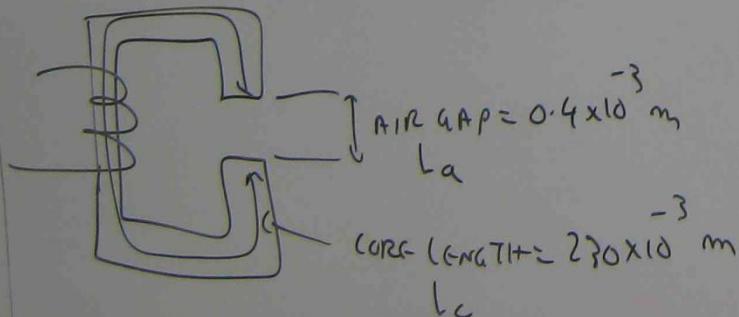

$$\boxed{\sum H L = N \times I}$$

$$H_{\text{air}} \times L_{\text{air}} + H_{\text{core}} \times L_{\text{core}} = N \times I$$

$$\frac{B}{\mu_0 \mu_r} \times L_{\text{air}} + \frac{B}{\mu_0 \mu_r} \times L_{\text{core}} = 400 \times I$$

$$\frac{1.41}{4\pi \times 10^{-7} \times 1} \times 0.4 \times 10^{-3} + \frac{1.41}{4\pi \times 10^{-7} \times 1900} \times 270 \times 10^{-3} = 400 \times I$$

$$I = I_{\text{max}} = 4.52 \text{ Amp}$$

$$I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}} = \frac{4.52}{1.4142} = 3.2 \text{ Amp.}$$

REVIEW QUES TODAY

- ① SKETCH CORE TYPE AND SHELL TYPE 34 TRANSFORMER
- ② WHAT ARE MAJOR INSULATION AND MINOR INSULATION
- ③ CALCULATE IRON CORE FLUX DENSITY AND RMS MAGNETIZING CURRENT FOR THE FOLLOWING SINGLE PHASE TRANSFORMER


$$N_p = 400, \quad E_p = 3000 \text{ V RMS}, \quad f = 60 \text{ Hz}$$

CORE C.S.A = 200 sq cm, CORE LENGTH = 230 cm


AIR GAP = 0.4 mm  $\mu_\infty = 1900$

①

CORE TYPE

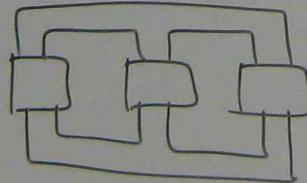

SHELL TYPE

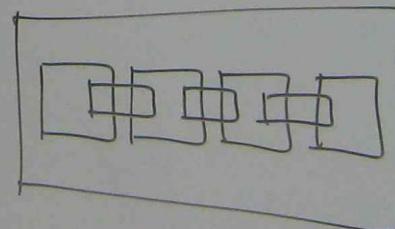

②

MAJOR INSULATION - INSULATION BETWEEN WINDING AND CORE  
INSULATION BETWEEN H.U AND L.U WINDING

MINOR INSULATION - INSULATION BETWEEN TRANSFORMER TURNS

$$③ E_p = 4.44 \phi f N$$


$$3000 = 4.44 \times \phi \times 60 \times 400$$

$$\phi = \frac{3000}{4.44 \times 60 \times 400}$$

$$= 0.0282 \text{ wb}$$

$$\text{Flux density } B = \frac{\phi}{A} = \frac{0.0282}{200 \times (10^{-2})^2} = 1.41 \text{ T}$$

$$H = \frac{\beta}{\mu_0 \mu_r}$$

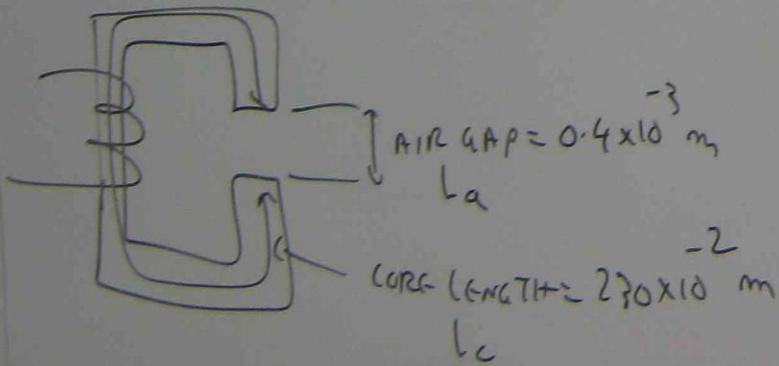

$$\boxed{\sum H L = N \times I}$$

$$H_{\text{air}} \times L_{\text{air}} + H_{\text{core}} \times L_{\text{core}} = N \times I$$

$$\frac{\beta}{\mu_0 \mu_r \text{AIR}} \times L_{\text{air}} + \frac{\beta}{\mu_0 \mu_r \text{IRON}} \times L_{\text{core}} = 400 \times I$$

$$\frac{1.41}{4\pi \times 10^{-7} \times 1} \times 0.4 \times 10^{-3} + \frac{1.41}{4\pi \times 10^{-7} \times 1900} \times 270 \times 10^{-2} = 400 \times I$$

$$I = I_{\text{MAX}} = 4.52 \text{ Amp}$$

$$I_{\text{rms}} = \frac{I_{\text{MAX}}}{\sqrt{2}} = \frac{4.52}{1.4142} = 3.2 \text{ Amp.}$$

(u) FIND ALL DAY EFFICIENCY OF THE FOLLOWING TR Ansformer

200 KVA 14 IRON LOSS = 700W, FULL LOAD COPPER LOSS = 900 W

24 HR LOAD CYCLE

TIME	POWER FACTOR	OUT PUT
8 hr	PF 0.9 LAGGING	130 WATT
5 hr	PF 0.8 LAGGING	100 KVA
4 hr	30 KVA & 20 KW	
3 hr	ENGAGED WITH NO LOAD	
THE REST OF TIME	DE ENGAGED	

TIME	LOAD RATIO	PF	LOAD	HR	KW/H	$(\text{LOAD RATIO})^2 \times \text{COPPER LOSS} \times \text{HR}$	IRON LOSS $\times$ HR	TOTAL INPUT
8	$\frac{180/\text{PF}}{200} = \frac{180/0.4}{200}$ = 1	0.9	180	8	1440 W-HR $= 1.44 \text{ kWh}$	$(1)^2 \times 900 \times 8$ $= 7200 \text{ Wh}$ $= 7.2 \text{ kWh}$	$700 \times 8 = 5600$ $= 5.6 \text{ kWh}$	14.24 kWh
5 hr	$\frac{100/\text{PF}}{200} = \frac{100/0.8}{200}$ $= 0.625$	0.8	$100 \times 0.8$ $= 80 \text{ kW}$	5	400 kWh	$(0.625)^2 \times 900 \times 5$ $= 1.757$	$700 \times 5 = 3500$ $= 3.5 \text{ kWh}$	405.25 kWh
4 hr	$\frac{30}{200} = 0.15$		20	4	80 kWh	$(0.15)^2 \times 900 \times 4$ $= 0.081$	$700 \times 4 = 2800$ $= 2.8 \text{ kWh}$	82.88 kWh
3 hr			0		0		$700 \times 3 = 2100$ $= 2.1 \text{ kWh}$	2.1 kWh
			TOTAL O/P	481.44 kWh			TOTAL Z/p	504.37 kWh

AVERAGE  
EFFICIENCY

$(\text{Loss Ratio})^2 \times \text{Copper Loss} \times \text{HR}$	$\text{Iron Loss} \times \text{HR}$	$\text{TOTAL INPUT}$	
$0 \text{ W-HR}$ $\text{kWh}$	$(1)^2 \times 900 \times 8$ $= 7200 \text{ Wh}$ $= 7.2 \text{ kWh}$	$700 \times 8 = 5600$ $= 5.6 \text{ kWh}$	$14.24 \text{ kWh}$
$\text{W-hr}$	$(0.625)^2 \times 900 \times 5$ $= 1.757$	$700 \times 5 = 3500$ $= 3.5 \text{ kWh}$	$405.25 \text{ kWh}$
$\text{W-hr}$	$(0.15)^2 \times 900 \times 4$ $= 0.081$	$700 \times 4 = 2800$ $= 2.8 \text{ kWh}$	$82.88 \text{ kWh}$
$0$	$700 \times 3 = 2100$ $= 2.1 \text{ kWh}$	$2.1 \text{ kWh}$	
$44$ $\text{h}$	$\text{TOTAL Z/p}$	$504.37 \text{ kWh}$	

AU/DAY  
EFFICIENCY =  $\frac{\text{Q/p kWh}}{\text{I/p kWh}} \times 100$

$= \frac{481.44}{504.37} \times 100$

$= 95.45\%$