
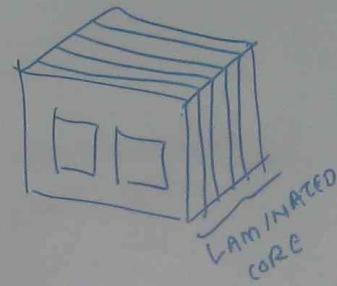
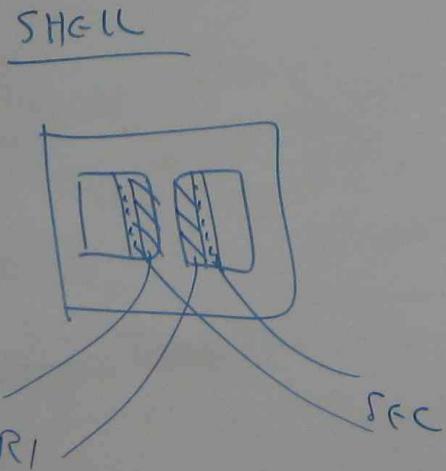


$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$E = 4.44 \text{ } 4f \text{ } N$$

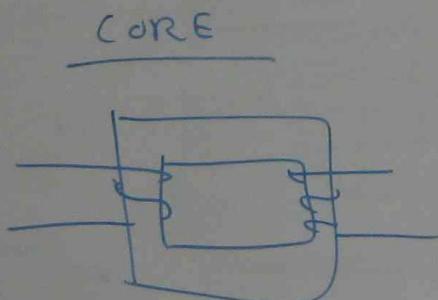

TO REDUCE EDDY CURRENT
in Hysteresis Loss

POWER TRANSFORMER

SAME PRINCIPLE

+


FORCED AIR COOLING
FORCED OIL COOLING

PARALLEL CONNECTION

SAME VOLTAGE


SAME RATING

SAME POLARITY

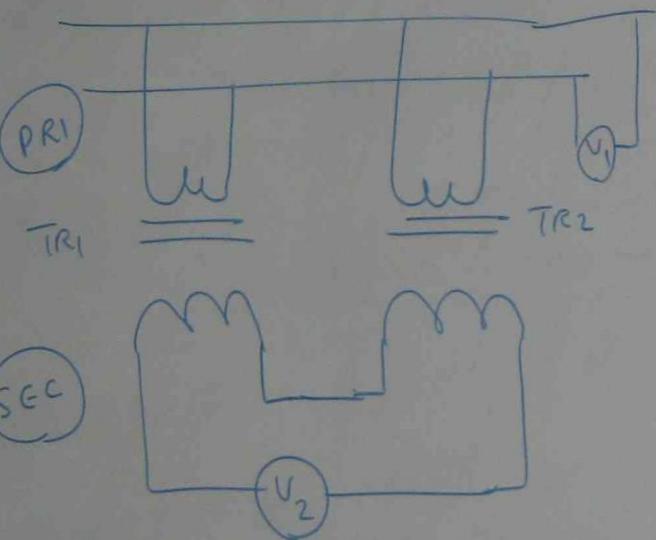


IF $U_2 \approx 0$

THEN CONNECT

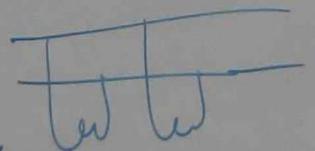



TEST
AGAIN

IF $U_2 \approx$ LINE SECONDARY
VOLTAGE

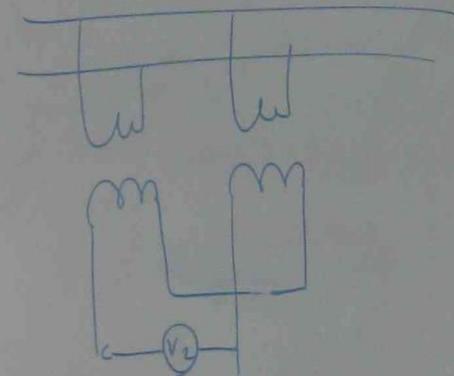

IF $U_2 \approx 0$


THEN
CONNECT

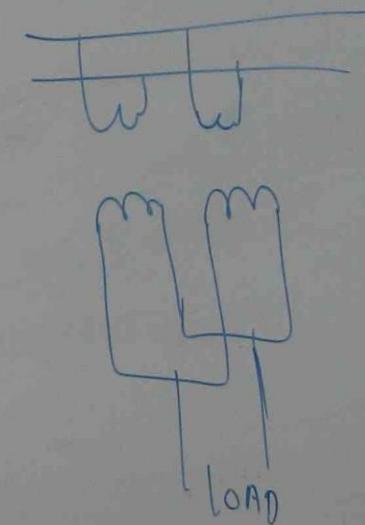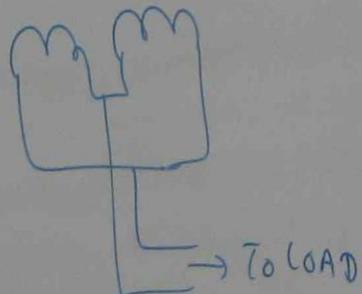

IF
 V_2 IS STILL NOT
 EQUAL TO ≈ 0

YOU CAN NOT CONNECT
 THESE TWO TRANSFORMERS
 IN PARALLEL

TRANSFORMER EQUIVALENT CIRCUIT

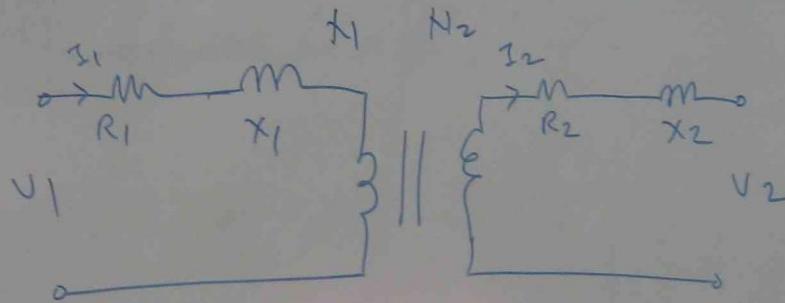

$$\frac{N_1}{N_2} =$$

$$\frac{V_1}{V_2}$$


$$X_1 = 2\pi f L_1 \quad (\text{PRIMARY INDUCTIVE REACTANCE}) \quad (\Omega)$$

$$X_2 = 2\pi f L_2 \quad (\text{SECONDARY INDUCTIVE REACTANCE}) \quad (\Omega)$$

$$R_1 = \text{PRIMARY RESISTANCE} \quad (\Omega)$$

$$R_2 = \text{SECONDARY RESISTANCE} \quad (\Omega)$$
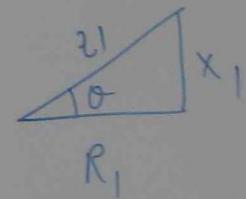
$$Z_1 = \text{PRIMARY IMPEDANCE} \quad (\Omega) = Z_1 = \sqrt{R_1^2 + X_1^2} = R_1 + jX_1$$



$$Z_2 = \text{SECONDARY IMPEDANCE} = Z_2 = \sqrt{R_2^2 + X_2^2} \quad (\Omega)$$

$$Z_2 = R_2 + jX_2$$

$$\frac{N_1}{N_2} = \text{TURN RATIO} = a$$

$$\boxed{\frac{V_1}{V_2} = \frac{N_1}{N_2} = a = \frac{I_L}{I_1}} \quad \text{BASIC}$$

$$\boxed{\frac{V_2'}{V_2} = \frac{N_1}{N_2} = a = \frac{I_2}{I_2'}} \quad \text{modified (1)}$$

V_2' = SECONDARY VOLTAGE
REFER TO PRIMARY

I_2' = SECONDARY CURRENT
REFER TO PRIMARY

$$\boxed{\frac{V_1''}{V_1} = \frac{N_1}{N_2} = a = \frac{I_1''}{I_1}}$$

V_1'' = PRIMARY VOLTAGE REFERRED
TO SECONDARY

I_1'' = PRIMARY CURRENT REFERRED TO SECONDARY

$$\boxed{\frac{R_1}{R_2} = \frac{x_1}{x_2} = \frac{z_1}{z_2} = a^2} \quad \text{BASIC}$$


$$\boxed{\frac{R_2'}{R_2} = \frac{x_2'}{x_2} = \frac{z_2'}{z_2} = a^2} \quad \text{modified}$$

$$\boxed{\frac{R_1}{R_1''} = \frac{x_1}{x_1''} = \frac{z_1}{z_1''} = a^2}$$



COMPLETE TRANSFORMER EQUIVALENT CIRCUIT

X_m = CORE INDUCTIVE REACTANCE

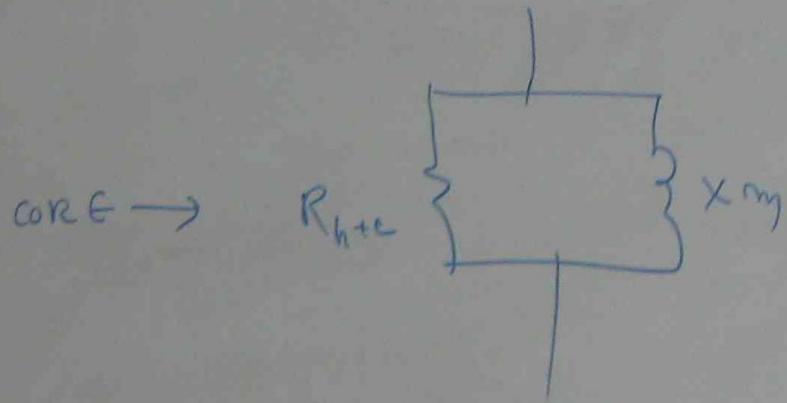R_{h+c} = EDDY CURRENT + HYSTERESIS RESISTANCE
of TRANSFORMER CORE




STANCE

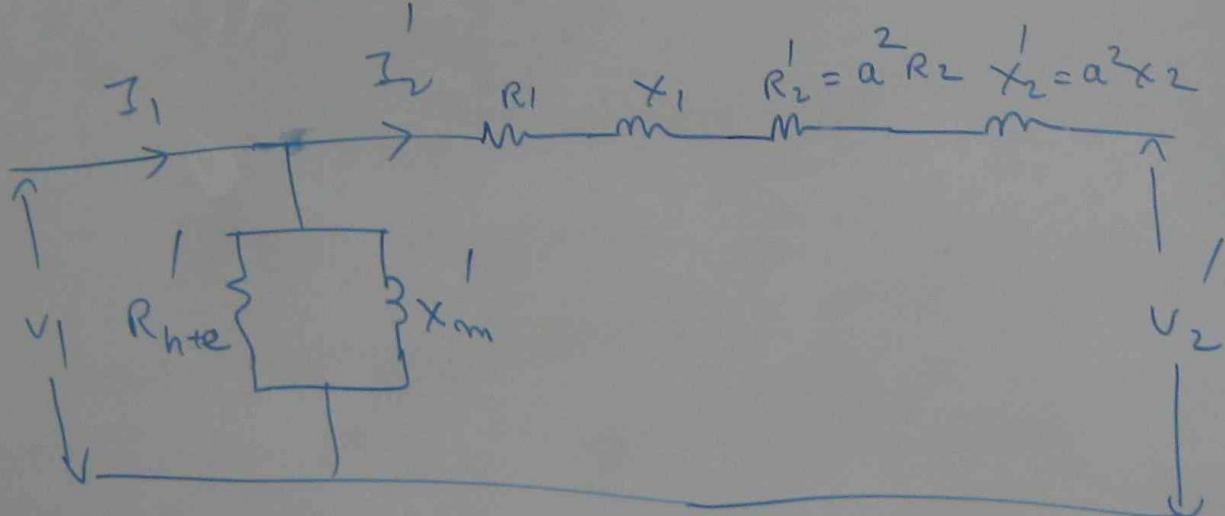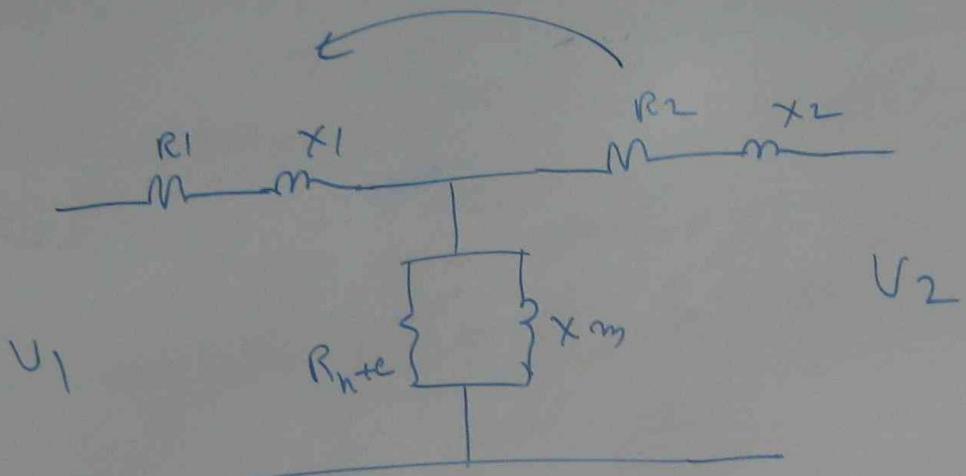

R_2' = SECONDARY RESISTANCE REFERRED TO PRIMARY
 X_2' = INDUCTING REACTANCE

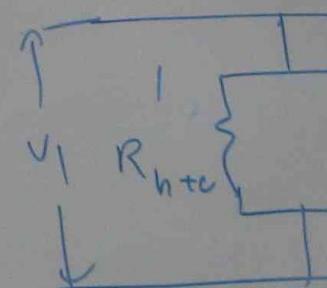
$$R_1 + R_2' = R_e' =$$
$$X_1 + X_2' = X_e' =$$
$$Z_e' = \sqrt{(R_e')^2 + (X_e')^2}$$



$$R_1 + R_2' = R_e' = \text{TOTAL EQUIVALENT RESISTANCE REFER TO PRIMARY}$$

$$X_1 + X_2' = X_e' = \text{INDUCTIVE REACTANCE}$$
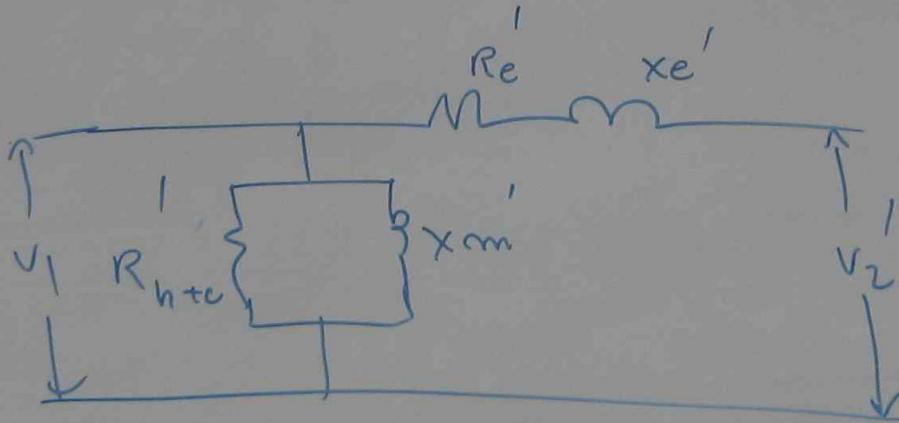
$$Z_e' = \sqrt{(R_e')^2 + (X_e')^2} = R_e' + j X_e' = \text{TOTAL EQUIVALENT IMPEDANCE REFER TO PRIMARY}$$





R REFERRED TO PRIMARY

FINAL EQUIVALENT CIRCUIT OF TRANSFORMER

TUTORIAL ③

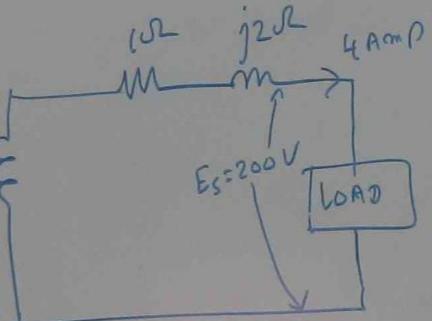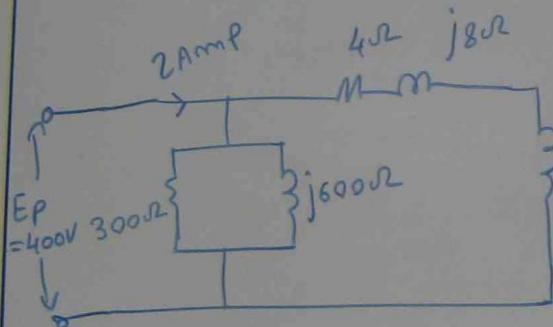Q1 REFER THE FOLLOWING SINGLE PHASE TRANSFORMER EQUIVALENT CIRCUIT AND CALCULATE THE FOLLOWINGS.



PRIMARY	SECONDARY
$R_1 = 4\Omega$	$R_2 = 1\Omega$
$X_1 = j8\Omega$	$X_2 = j2\Omega$
$I_1 = 2 \text{ Amp}$	$I_2 = 4 \text{ Amp}$
$V_1 = 400V$	$V_2 = 200V$

- (a) TURN RATIO
- (b) SECONDARY RESISTANCE REFER TO PRIMARY
- (c) SECONDARY INDUCTIVE REACTANCE REFER TO PRIMARY
- (d) SECONDARY CURRENT REFER TO PRIMARY
- (e) SECONDARY VOLTAGE REFER TO PRIMARY

$$\begin{aligned} R_{htc}^1 &= 300\Omega \\ X_m^1 &= j600\Omega \end{aligned}$$

$$(a) \text{ TURN RATIO } (a) = \frac{V_1}{V_2} = \frac{400}{200} = 2$$

$$(b) R_2^1 = a^2 R_2 = 2^2 \times 1 = 4\Omega$$

$$(c) X_2^1 = a^2 X_2 = 2^2 \times j2 = j8\Omega$$

$$(d) I_2' = ?$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = a = \frac{I_2}{I_1}$$

$$a = \frac{I_2}{I_1}$$

$$I_2' = \frac{I_2}{a} = \frac{4}{2} = 2 \text{ Amp}$$

$$(e) V_2' = ?$$

$$\boxed{\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1} = a}$$

$$\frac{V_1}{V_2} = a \rightarrow \boxed{\frac{V_2}{V_2} = a}$$


$$V_2' = a V_2 = 2 \times 200 = 400 \text{ V}$$

TUTORIAL ①


Q1 SUET CH CORE TYPE AND SHELL TYPE TRANSFORMER

Q2 WHY IS THE LAMINATED CORE USED IN TRANSFORMER?

Q1

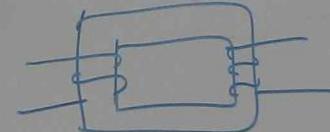

CORE TYPE

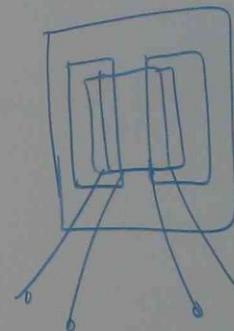


SHELL TYPE

Q2 TO REDUCE HYSTERESIS AND EDDY CURRENT


POWER LOSSES IN THE CORE, LAMINATED IRON CORE IS UTILIZED.

POWER LOSSES IN TRANSFORMER

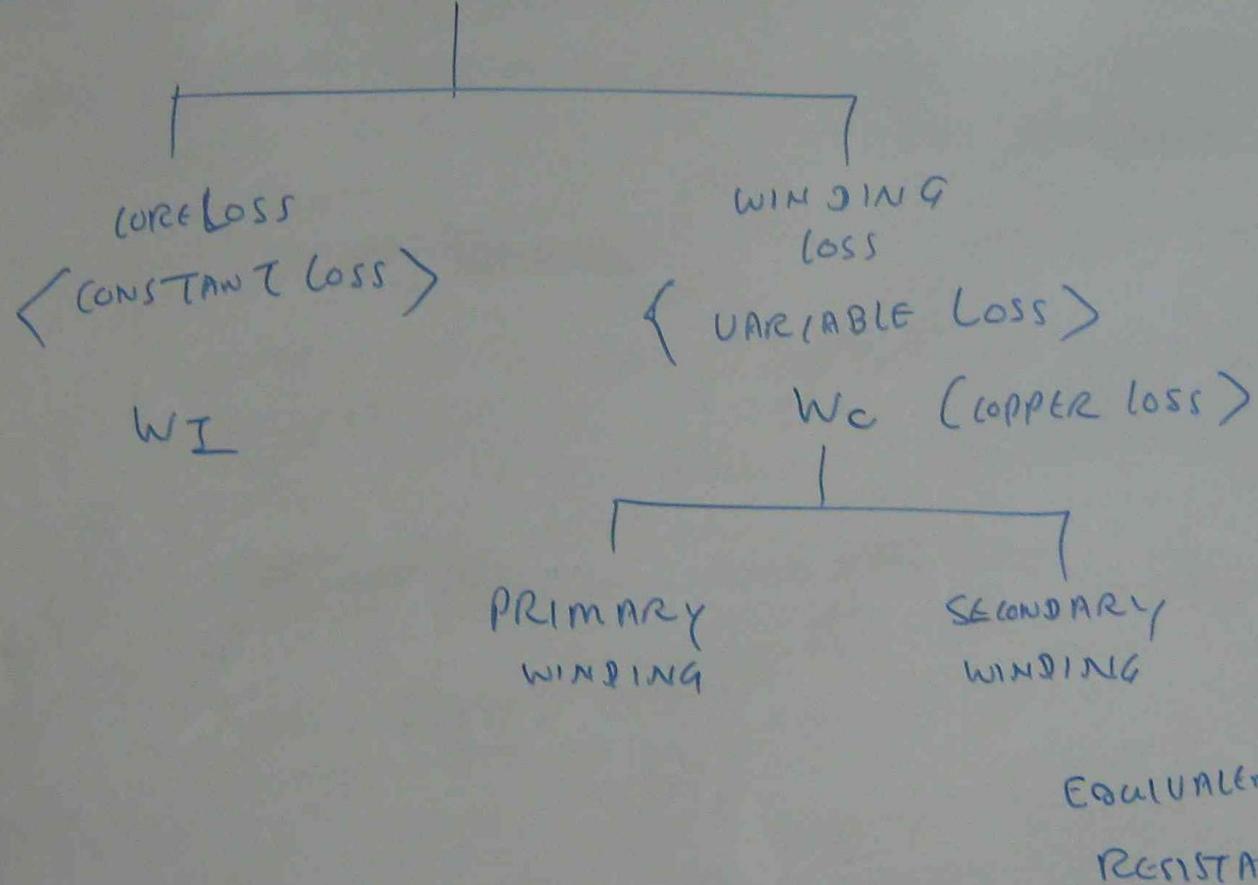

F1

TUTORIAL ③

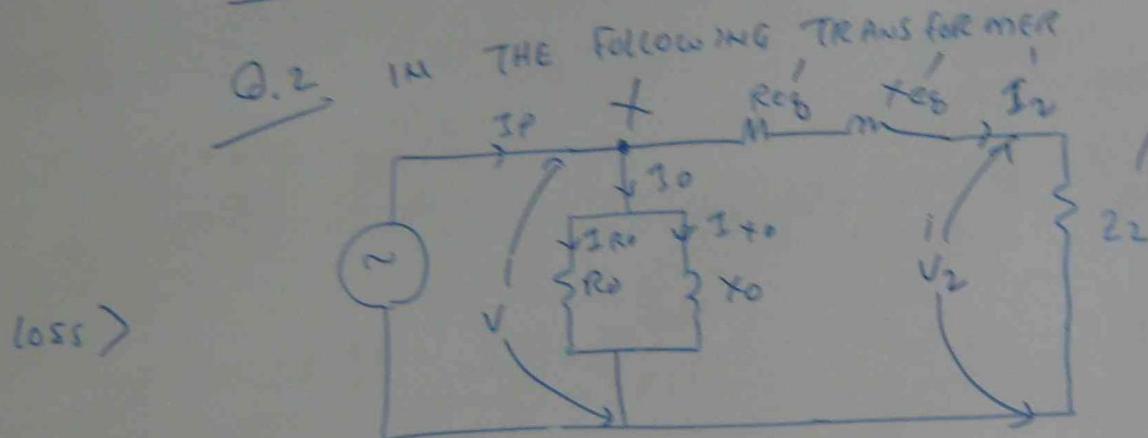

$$V = \sqrt{L} \omega$$

$$V \angle \theta$$

BY
SG

$$R'_e_g = 0.2 \Omega, \quad X'_e_g = j0.8 \Omega$$

$$R_o = 300 \Omega, \quad X_o = j400 \Omega$$

EQUIVALENT
RESISTANCE

$$V = 250 \angle 0^\circ$$

$$Z_2' = 6 + j3 \Omega$$

FIND (a) IRON LOSS (b) NO LOAD CURRENT (c) SECONDARY LOAD CURRENT

(d) TOTAL PRIMARY CURRENT (e) COPPER LOSSES (f) SECONDARY

TERMINAL VOLTAGE (g) POWER IN WATT CONSUMED BY LOAD

(h) % EFFICIENCY

$$(a) \text{ Iron loss} = \text{ core loss} = \frac{V^2}{R_0} = \frac{(250)^2}{300} = 208 \text{ WATT}$$

$$(b) \bar{I}_o = \bar{I}_{R_0} + \bar{I}_{X_0}$$

$$\bar{I}_{R_0} = \frac{V}{R_0} = \frac{250}{300} = 0.833 \text{ Amp}$$

$$\bar{I}_{X_0} = \frac{V}{X_0} = \frac{250}{\sqrt{400}} = \frac{250}{400 \angle 90^\circ} = 0.625 \angle -90^\circ = -j0.625$$

$$\bar{I}_o = \bar{I}_{R_0} + \bar{I}_{X_0} = 0.833 + (-j0.625) = 0.833 - j0.625$$

$$\bar{I}_d = \sqrt{0.833^2 + 0.625^2} \left(-\tan^{-1} \frac{0.625}{0.833} \right) = 1.04 \angle -36.86^\circ \text{ Amp}$$


SECONDARY LOAD CURRENT


LOSSES (f) SECONDARY

WATT CONSUMED BY LOAD

(c) SECONDARY LOAD CURRENT $I_2' = ?$

EFFICIENCY

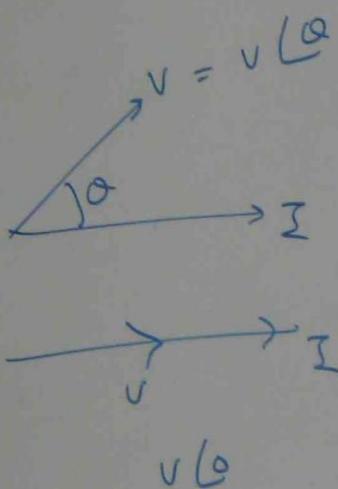

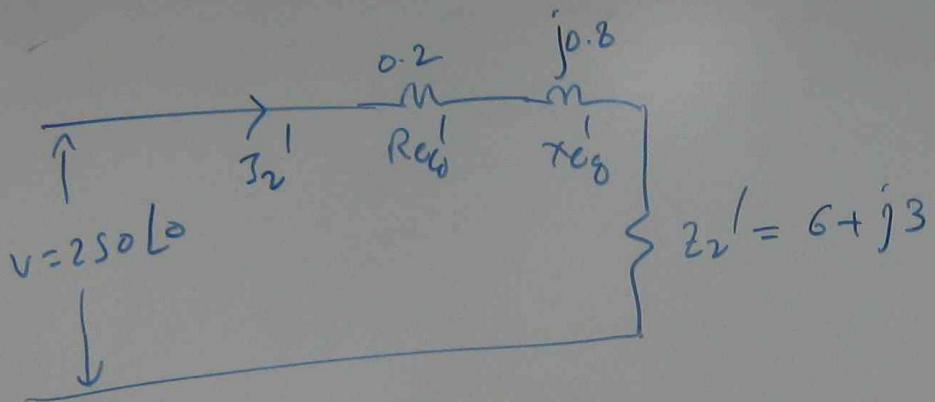

$$I_2' = \frac{250\angle 0^\circ}{R_{eq}' + jX_{eq}' + Z_2'}$$

$$= \frac{250\angle 0^\circ}{0.2 + j0.8 + 6 + j3}$$

$$= \frac{250\angle 0^\circ}{6.2 + j3.8}$$

$$= \frac{250\angle 0^\circ}{\sqrt{6.2^2 + 3.8^2} \left[\tan^{-1} \frac{3.8}{6.2} \right]} = \frac{250\angle 0^\circ}{7.27 \left[31.4^\circ \right]}$$

$$= 34.3 \angle -31.4^\circ \text{ Amp.}$$

(d) $I_p = I_2' + I_0$

$$= 34.3 \angle -31.4^\circ + 1.04$$

$$= 34.3 \cos 31.4^\circ - j 34.3 \sin 31.4^\circ$$

$$= (34.3 \times 0.853 - j 34.3 \times 0.5)$$

$$= 29.25 - j 17.8 +$$

$$= 30.08 - j 18.4$$

(e) copper loss

(f) $V_2' = V -$

$$(d) I_p = I_2' + I_0$$

$$= 34.3 \angle -31.4^\circ + 1.04 \angle -36.86^\circ$$

$$= (34.3 \cos 31.4^\circ - j 34.3 \sin 31.4^\circ) + (1.04 \cos 36.86^\circ - j 1.04 \sin 36.86^\circ)$$

$$\approx (34.3 \times 0.853 - j 34.3 \times 0.521) + (1.04 \times 0.8 - j 1.04 \times 0.6)$$

$$= 29.25 - j 17.8 + 0.832 - j 0.624$$

$$= 30.08 - j 18.4 \text{ Amp} = \sqrt{30.08^2 + 18.4^2} \angle -\tan^{-1} \frac{18.4}{30.08}$$

$$= 35.26 \angle -31.4^\circ \text{ Amp}$$

$$(e) \text{ Copper loss} = (I_2')^2 \times R_{eq}' = (34.3)^2 \times 0.2 = 235.2 \text{ WATT}$$

$$(f) V_2' = V - I_2' (R_{eq}' + j X_{eq}')$$

$$\begin{aligned}
 v_2^l &= 250 \angle 0^\circ - 34.3 \angle -31.4^\circ (0.2 + j0.8) \\
 &= 250 \angle 0^\circ - 34.3 \angle -31.4^\circ + \sqrt{0.2^2 + 0.8^2} \angle \tan^{-1} \frac{0.8}{0.2} \\
 &= 250 \angle 0^\circ - 34.3 \angle -31.4^\circ \times 0.824 \angle 75.9^\circ \\
 &= 250 \angle 0^\circ - 28.26 \angle 75.9^\circ + (-31.4) = 250 \angle 0^\circ - 22.26 \angle 44.5^\circ \\
 &= 250 - 28.26 (\cos 44.5^\circ + j \sin 44.5^\circ) \\
 &= 250 - 28.26 (0.7132 + j0.7) = 250 - 20.15 - j19.78 \\
 &= 229.85 - j19.78 = \sqrt{229.85^2 + 19.78^2} \angle -\tan^{-1} \frac{19.78}{229.85} \\
 &\quad = 230.7 \angle -4.91^\circ \text{ VOLT}
 \end{aligned}$$

77

$$(g) \text{ Power in load} = (I_2^l)^2 \times R_{\text{LOAD}} = (34.3)^2 \times 6 = 7058.94 \text{ WATT}$$

(h) INPUT power = LOAD power + core loss + winding loss



$$= 7058.94 + 208 + 235.2 = 7502.14 \text{ W}$$

$$\% \text{ Efficiency} = \frac{\text{OUTPUT}}{\text{INPUT}} \times 100 = \frac{7058.94}{7502.14} \times 100 = 94.08\%$$

TRANSFORMER OPEN CIRCUIT TEST / SHORT CIRCUIT TEST

TO FIND TRANSFORMER CORE RESISTANCE AND WINDING RESISTANCE,
OPEN CIRCUIT TEST AND SHORT CIRCUIT TEST ARE DONE.

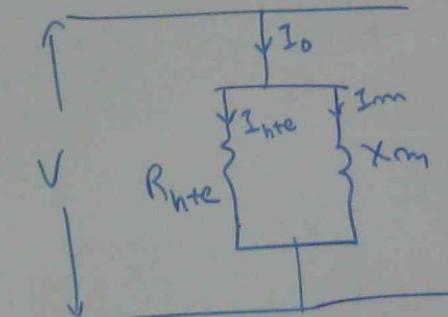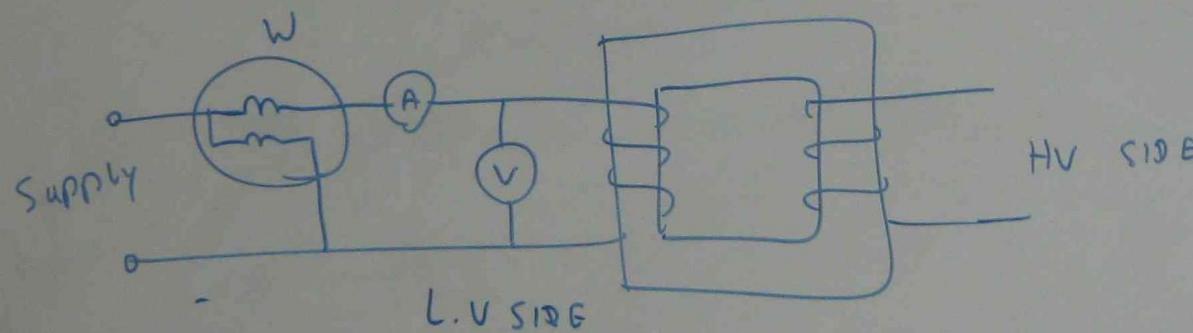OPEN CIRCUIT TEST \longrightarrow CORE RESISTANCE + INDUCTIVE
REACTANCE



$$P = \frac{V^2}{R}$$

$$R_{hfe} = \frac{(\text{VOLT METER READING})^2}{\text{WATT METER READING}}$$

$$R = \frac{V^2}{P}$$

$$X_m = \frac{\text{VOLT METER READING}}{\text{AMMETER READING}}$$


ST

AND WINDING RESISTANCE,

TEST ARE DONE.

AC + INDUCTIVE
REACTANCE

V SIDE

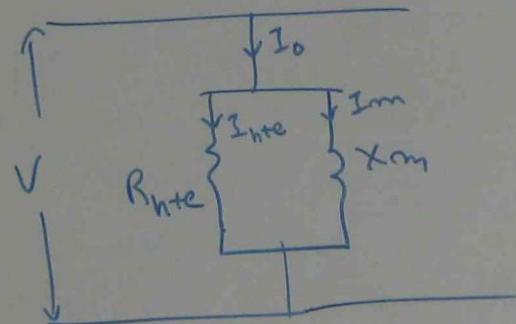

WATT METER

READING =
(W)

VOLT METER READING × AMP METER READING × $\cos\theta$
(V) (I)

$$\cos\theta = \frac{W}{V \times I}$$


$$\theta = \cos^{-1} \frac{W}{VI}$$

$$\sin\theta = \sqrt{1 - \cos^2\theta}$$

VOLT METER READING

$$X_m = \frac{\text{VOLT METER READING}}{\text{AMP METER READING} \times \sin\theta}$$

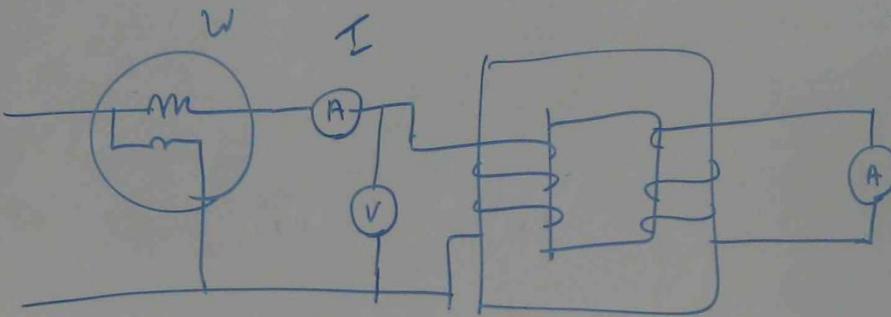SHORT CIRCUIT TEST \rightarrow WINDING RESISTANCE + INDUCTIVE REACTANCE



HV

LV

$$\frac{I^2}{2} \times R_{WINDING} = W$$

$$R_{WINDING} = \frac{W}{I^2}$$

$$X_{WINDING} = \sqrt{Z_{WINDING}^2 - R_{WINDING}^2}$$

$$I Z_{WINDING} = V$$

$$Z_{WINDING} = \frac{V}{I}$$

TUTORIAL ④

① IN OPEN CIRCUIT TEST ON 4 KVA SINGLE PHASE TRANSFORMER, THE FOLLOWING RESULTS ARE RECORDED.


$$V_o = 250 \text{ V}, \quad I_o = 1 \text{ Amp}, \quad P_o = 70 \text{ WATT}$$

IN SHORT CIRCUIT TEST, THE FOLLOWING RESULTS ARE RECORDED

$$V_{sc} = 100 \text{ V}, \quad P_{sc} = 80 \text{ W}, \quad I_{sc} = 7 \text{ Amp}$$

FIND R_{h+e} , X_m , R_{eq} (REFERRED TO PRIMARY), X_{eq} (REFERRED TO PRIMARY)

THEN DRAW THE EQUIVALENT CIRCUIT

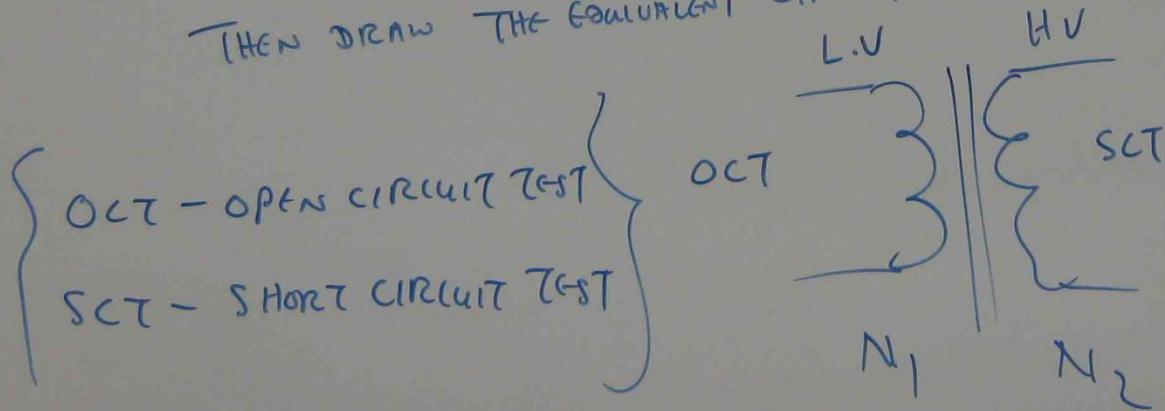

OCT

$$R'_{h+c} = -\frac{V^2}{P} = \frac{250^2}{70} = 892.8 \Omega$$

$$\omega = V I \cos \theta$$

$$\cos \theta = \frac{\omega}{VI} = \frac{70}{250 \times 1} = 0.28$$

$$\theta = \cos^{-1} 0.28 = 73.7^\circ$$

$$\sin \theta = \sin 73.7 = 0.959$$

$$X_m' = \frac{V}{I \sin \theta} = \frac{250}{1 \times 0.959} = 260.68 \Omega$$

SCT

R''

WINDING


$$R''_{\text{WINDING}} = \frac{w}{I^2} = \frac{80}{7^2} = \frac{80}{49} = 1.632 \Omega$$

WINDING

$$Z''_{\text{WINDING}} = \frac{v}{I} = \frac{100}{7} = 14.28 \Omega$$

$$X''_{\text{WINDING}} = \sqrt{\left(Z''_{\text{WINDING}}\right)^2 - \left(R''_{\text{WINDING}}\right)^2}$$
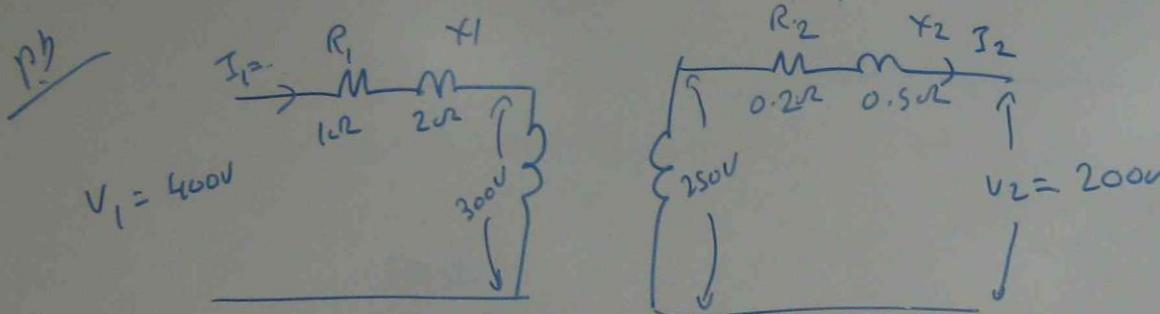
$$= \sqrt{(14.28)^2 - (1.632)^2} = 14.19 \Omega$$



IN ABOVE CIRCUIT, FIND

- (a) a
- (b) Z_1
- (c) β_1
- (d) Z_2
- (e) I_2

- (f) R_2' , X_2' , Z_2'
- (g) R_1'' , X_1'' , Z_1''
- (h) % VOLTAGE REGULATION

$$(a) \cdot a = \frac{U_1}{U_2} = \frac{400}{200} = 2$$

$$(b) Z_1 = \sqrt{R_1^2 + X_1^2} = \sqrt{1^2 + 2^2} \\ = \sqrt{5} \\ = 2.236 \Omega$$

$$(c) I_1 = \frac{400 - 300}{Z_1}$$

$$= \frac{100}{2.236}$$

$$= 44.7 \text{ Amp}$$

$$(d) Z_2 = \sqrt{R_2^2 + X_2^2}$$

$$= \sqrt{0.2^2 + 0.5^2}$$

$$= 0.538 \Omega$$

$$(e) I_2 = \frac{250 - 200}{0.538}$$

$$= 92.9 \text{ Amp}$$

$$(f) R_2' = a^2 R_2 = 2^2 \times 0.2 = 4 \times 0.2 = 0.8 \Omega$$

$$X_2' = a^2 X_2 = 2^2 \times 0.5 = 4 \times 0.5 = 2 \Omega$$

$$Z_2' = a^2 Z_2 = 2^2 \times 0.538 = 2.152 \Omega$$

$$(g) R_1'' = \frac{R_1}{a^2} = \frac{1}{2^2} = \frac{1}{4} = 0.25 \Omega$$

$$X_1'' = \frac{X_1}{a^2} = \frac{2}{4} = 0.5 \Omega$$

$$Z_1'' = \frac{Z_1}{a^2} = \frac{2.236}{4} = 0.559 \Omega$$

$$(h) \% \text{ REGULATION} = \frac{\text{NO LOAD VOLTAGE} - \text{FULL LOAD VOLTAGE}}{\text{NO LOAD VOLTAGE}} \times 100$$

$$= \frac{250 - 200}{250} \times 100 = 20\%$$