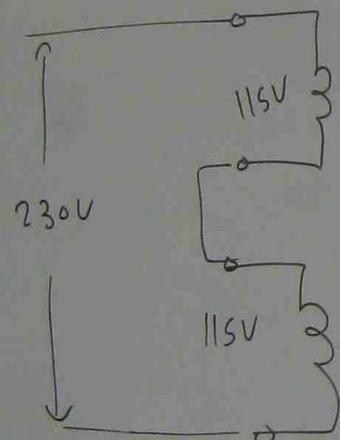




CONNECTING TRANSFORMER WINDINGS IN SERIES AND PARALLEL

TO SUPPLY HIGHER CURRENTS, WINDINGS ARE TO BE CONNECTED IN PARALLEL


TO SUPPLY HIGHER VOLTAGE, WINDINGS ARE TO BE CONNECTED IN SERIES




H.V & L.V COILS IN
SERIES

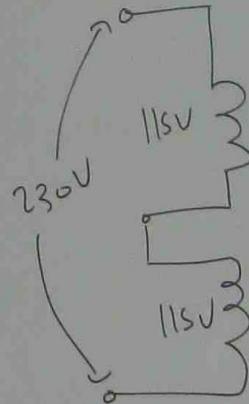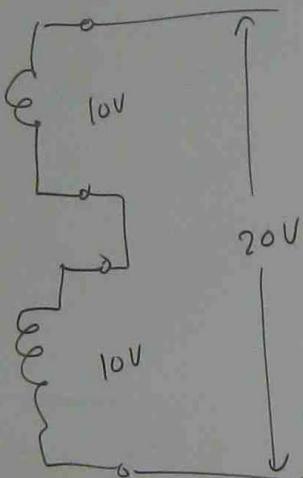


H.V COILS IN SERIES

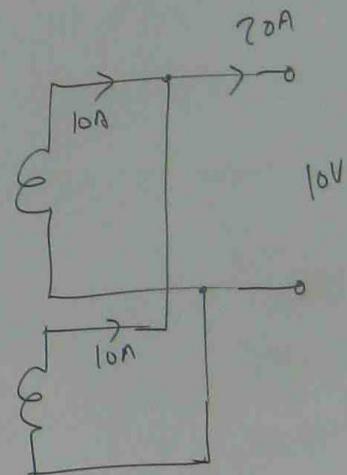


L.V COILS IN PARALLEL

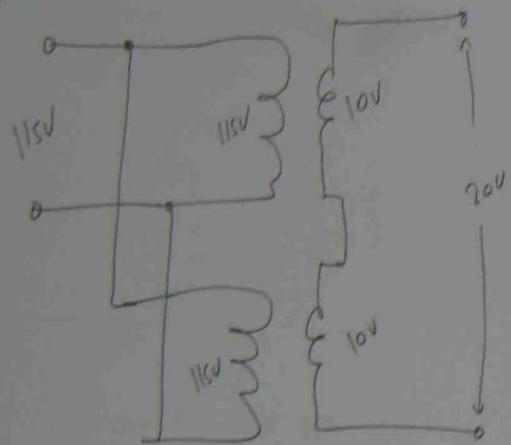

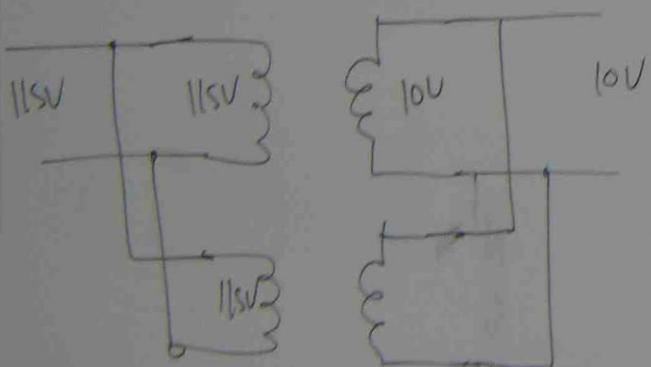H.V COILS IN PARALLEL, L.V
COILS IN SERIES



H.V & L.V COILS IN PARALLEL

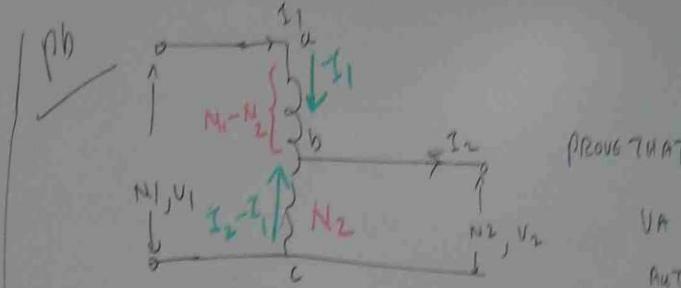

PROVE THAT

$$\text{VA RATING OF AUTO TRANSFORMER} = \left(1 - \frac{1}{k}\right) \times \text{VARATING OF 2 WINDINGS TRANSFORMER}$$

$$\text{WHERE } k = \frac{U_1}{U_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

TO OPERATE SMOOTHLY

MAGNETIZING FORCE = MAGNETIZING FORCE

$a \rightarrow b$

$b \rightarrow c$

$$I_1(N_1 - N_2) = (I_2 - I_1) N_2$$

$$I_1 N_1 - I_1 N_2 = I_2 N_2 - I_1 N_2$$

$$I_1 N_1 = I_2 N_2 \Rightarrow \frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\frac{I_1}{I_2} = k$$

$$\therefore \frac{I_1}{I_2} = \frac{N_2}{N_1} = k$$

V.A RATING OF AUTO TR AND FOR MTR

X V.A RATING OF
2 WINDINGS
TRANSFORMER


TOTAL V.A RATING OF AUTO TRANS FOR MTR =

$$V_A \xrightarrow{a \rightarrow b} + V_A \xrightarrow{b \rightarrow c}$$

$$= I_1 (V_1 - V_2) + (I_2 - I_1) V_2$$

$$= V_1 I_1 - V_2 I_1 + V_2 I_2 - V_2 I_1$$

$$= V_1 I_1 + V_2 I_2 - 2 V_2 I_1$$

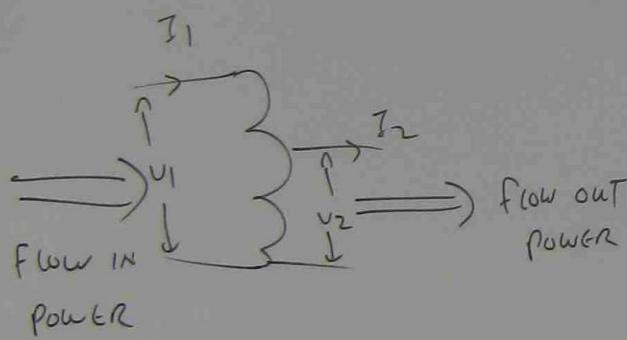

Flow in power = Flow out power

$$V_1 I_1 = V_2 I_2$$

Thus

$$V_A \xrightarrow{\text{AUTO TR}} = V_1 I_1 + V_1 I_1 - 2 V_2 I_1$$



AUTO TR

$$V_A \xrightarrow{\text{AUTO TR}} = 2 V_1 I_1 - 2 V_2 I_1 \quad (1)$$

$$V.A \text{ OF } 2 \text{ WINDING TR} = V_1 I_1 + V_2 I_2$$

$$\approx 2 V_1 I_1 - (2)$$

PHASE SHIFT TRANSFORMER

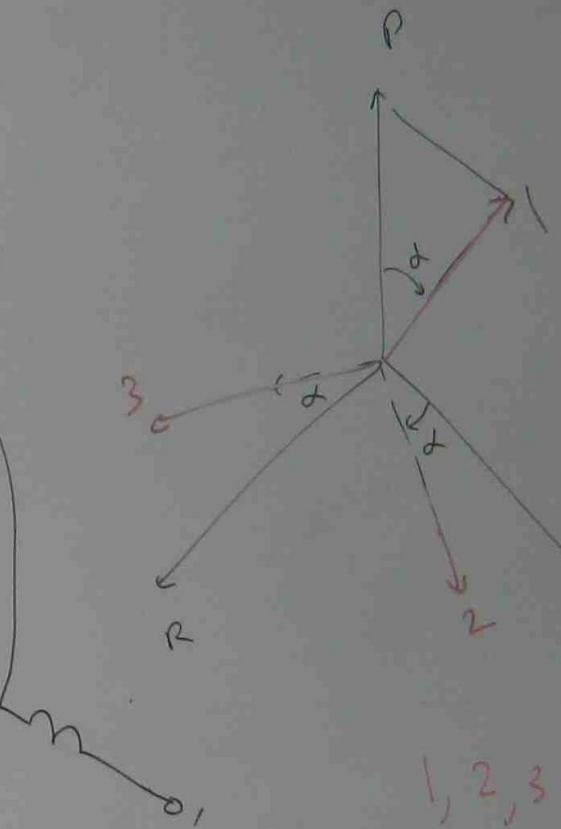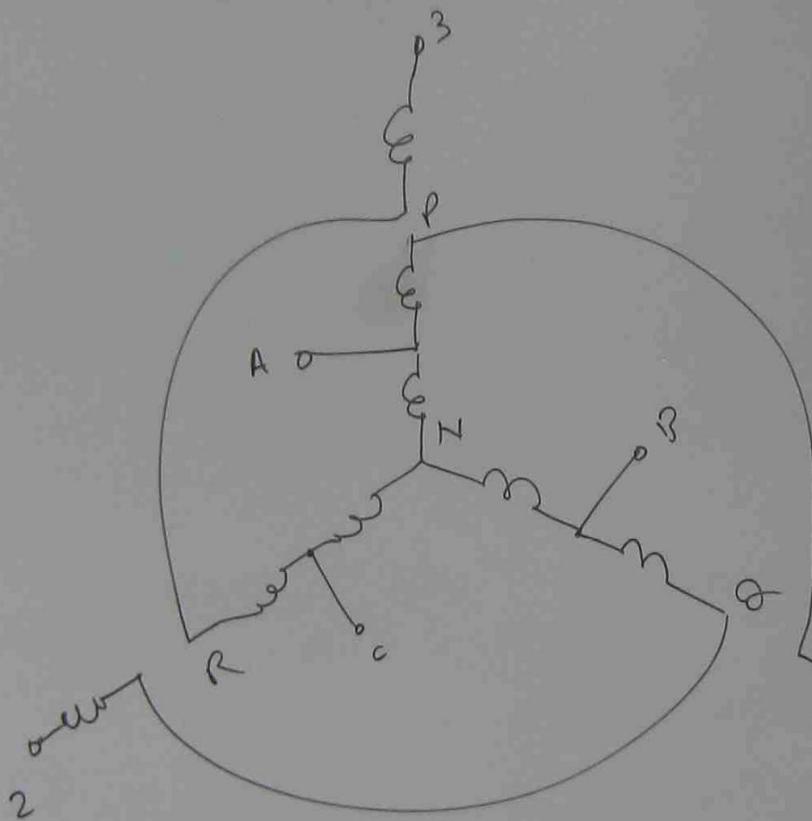

ph

A PHASE SHIFT TRANSFORMER IS DESIGNED TO CONTROL 150 MVA ON A 230 kV 3 ϕ LINE. THE PHASE ANGLE IS VARIABLE BETWEEN ZERO AND $\pm 15^\circ$.

(a) CALCULATE APPROXIMATE BASIC POWER RATING OF TRANSFORMER

(b) CALCULATE LINE CURRENTS IN IN COMING AND OUT GOING LINES.

$$S_T = 0.025 S_L \alpha_{\max}$$

S_T = BASIC POWER RATING OF TRANSFORMER

S_L = APPARENT POWER CONTROLLED BY TRANSMISSION LINE

α_{\max} = MAXIMUM PHASE SHIFT ANGLE

0.025 = COEFFICIENT

$$S_I = 0.025 \times 150 \times 15 = 56 \text{ mVA}$$

$$I = \frac{\text{mVA} \times 10^3}{\int_B E(Ku)}$$

$$= \frac{150 \times 10^3}{1.7321 \times 230}$$

$$= 377 \text{ Amp.}$$


OVER HEAD LINE AND TRANSFORMER

WHEN FULLY LOADED LINE ABSORBS REACTIVE POWER, TRANSFORMER ALWAYS ABSORBS REACTIVE POWER.

$$\text{VAR ABSORBED} = \frac{(\text{UA OF LOAD})^2}{\text{RATED UA}} \times X_T$$


BOOSTER TRANSFORMER

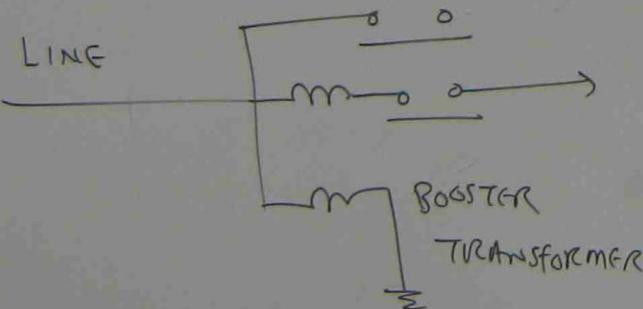BOOSTER TRANSFORMER IS UTILIZED TO BOOST THE VOLTAGE IF SUPPLY VOLTAGE FALLS BELOW NORMAL




PHASE SHIFT TRANSFORMER

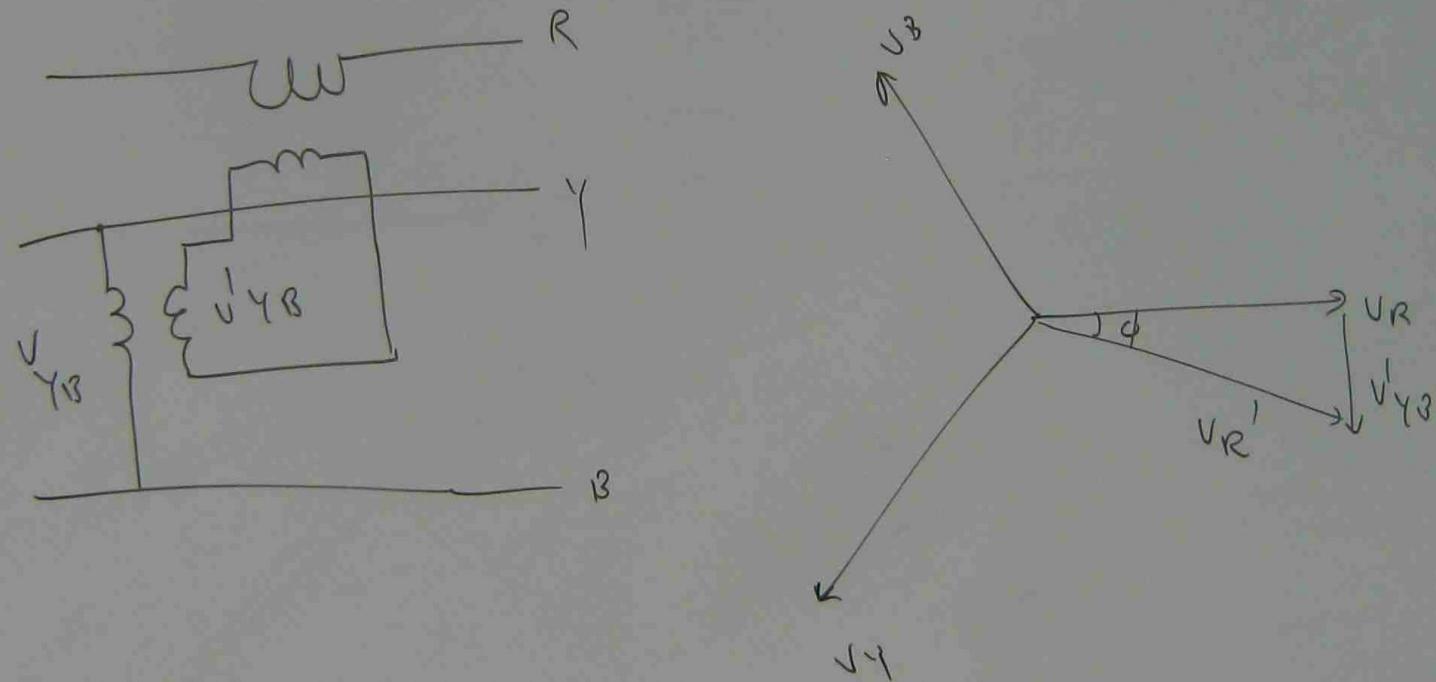
BY THE USE OF TAPPINGS ON THE ENGRAGING TRANSFORMER,
SEVERAL VALUE OF PHASE SHIFT MAY BE OBTAINED



VOLTAGE CONTROL IN DISTRIBUTION NETWORK

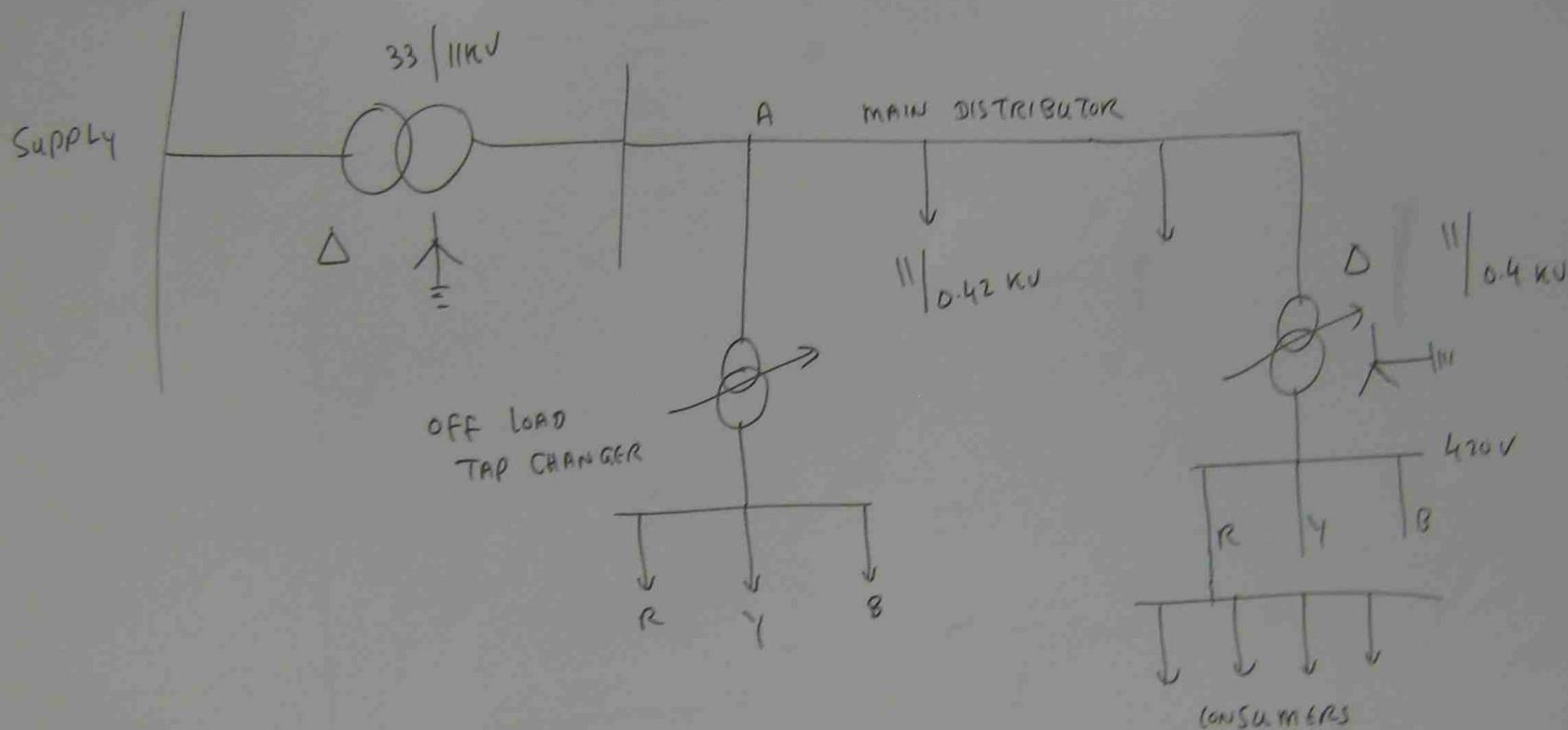

CONSTANT CURRENT TRANSFORMER

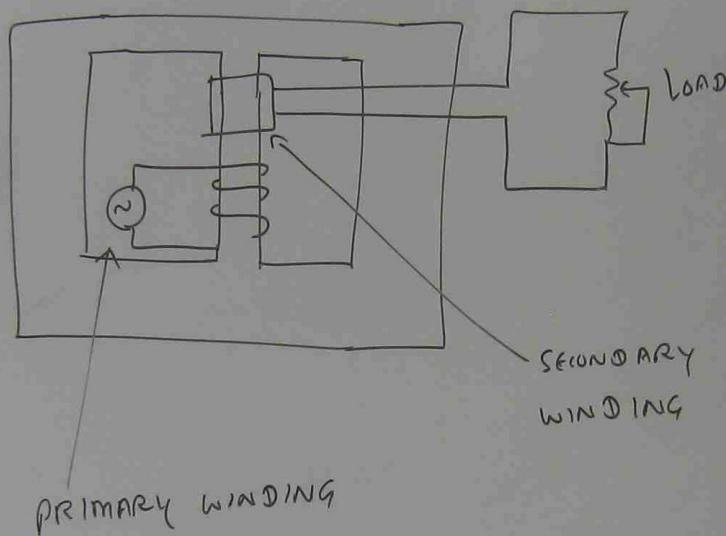

A CONSTANT CURRENT TRANSFORMER IS DESIGNED TO
SATISFY THE CONSTANT CURRENT REQUIREMENT WHILE
THE VOLTAGE DROP VARIES WITH THE LOAD.

THE SECONDARY VOLTAGE VARIES DIRECTLY WITH THE
LOAD IN A CONSTANT CURRENT TRANSFORMER

Review Questions (1)

(1) DESCRIBE ALL DAY EFFICIENCY OF TRANSFORMER.

ALL DAY EFFICIENCY IS THE RATIO OF ENERGY OUT PUT IN A GIVEN PERIOD AND ENERGY IN PUT FOR THE SAME PERIOD.

(2) A 1500 KVA 34 TRANSFORMER WITH IRON LOSS 15 KW AND FULL LOAD COPPER LOSS 16 KW HAS THE FOLLOWING LOAD CYCLE

6 HR FULL LOAD 0.8 PF

9 HR 75% LOAD 0.9 PF

3 HR 50% LOAD UNITY PF

REMAINING DAY PRIMARY IS ENERGIZED
WITH SECONDARY NO LOAD

CALCULATE ALL DAY EFFICIENCY.

OUTPUT kWh

$$6 \times 1500 \times 1 \times 0.8 = 7200 \text{ kWh}$$

$$9 \times 1500 \times 0.75 \times 0.9 = 9112 \text{ kWh}$$

$$3 \times 1500 \times 0.5 \times 1 = 2250 \text{ kWh}$$

$$18562 \text{ kWh}$$

LOSSES

$$\text{IRON LOSS} = 15 \times 24 = 360 \text{ kWh}$$

$$\text{COPPER LOSS(kWh)} = (\text{LOAD RATIO})^2 \times \text{FULL LOAD COPPER LOSS} \times \text{HR}$$

$$6 \times 16 \times (1)^2 = 96$$

$$9 \times 16 \times (0.75)^2 = 81$$

$$3 \times 16 \times (0.5)^2 = 12$$

$$\text{TOTAL LOSSES} = 549 \text{ kWh}$$

$$\begin{aligned}
 \text{ALL DAY EFFICIENCY} &= \frac{\text{ALL DAY OUT PUT}}{\text{ALL DAY OUT PUT} + \text{LOSSES}} \times 100 \\
 &= \frac{18562}{18562 + 549} \times 100 \\
 &= 97.13\%
 \end{aligned}$$

(3) TRANSFORMER A RATED 15 MVA $\%Z_a = 3+j6\%$

TRANSFORMER B RATED 30 MVA $\%Z_b = 4+j8\%$

(a) CALCULATE $\%Z$ OF BOTH TRANSFORMERS BASED ON
30 MVA.

(b) $\%LOAD$ SHARE TO SUPPLY 12 MVA AT UNITY P.F

$$\boxed{\% Z_2 = \% Z_1 \times \frac{MVA_2}{MVA_1}}$$

ner,

$$\% Z_A(2) = (3+j6) \times \frac{30}{15}$$

$$= (3+j6) \times 2$$

$$= 6 + j12$$


$$\% Z_B = 4 + j8$$

$$\begin{aligned}
 MVA_A(A) &= MVA_{\text{TOTAL}} \times \frac{\% Z_B}{\% Z_A + \% Z_B} = 12 \times \frac{4 + j8}{6 + j12 + 4 + j8} \\
 &= 12 \times \frac{4 + j8}{10 + j20} \\
 &= \frac{12 \times 4 (1 + j2)}{10 (1 + j2)} \\
 &= 4.8 \text{ MVA}
 \end{aligned}$$

$$\frac{30}{15}$$




2
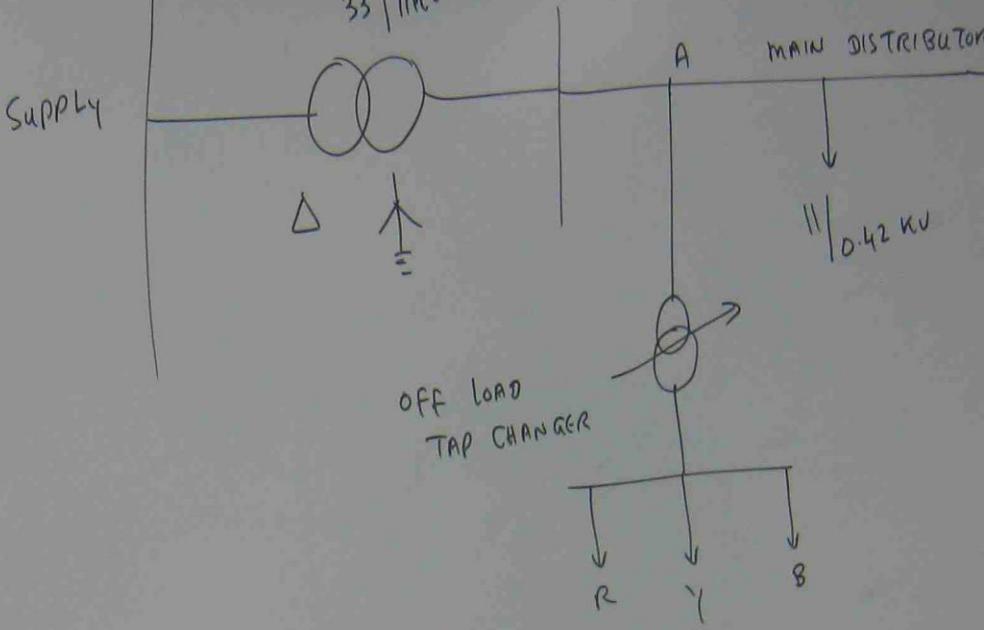
$$\begin{aligned}
 & \times \frac{\gamma_z B}{\gamma_z A + \gamma_z B} = 12 \times \frac{4 + j8}{6 + j12 + 4 + j8} \\
 & = 12 \times \frac{4 + j8}{10 + j20} \\
 & = 12 \times \frac{4 (1 + j2)}{10 (1 + j2)} \\
 & = 4.8 \text{ mVA}
 \end{aligned}$$



$$\begin{aligned}
 MVA_A(B) &= MVA_{TOTAL} \times \frac{\gamma_z A}{\gamma_z A + \gamma_z B} \\
 &= 12 \times \frac{6 + j12}{10 + j20} \\
 &= \frac{12 \times 6 (1 + j2)}{10 (1 + j2)} \\
 &= 7.2 \text{ MVA}
 \end{aligned}$$

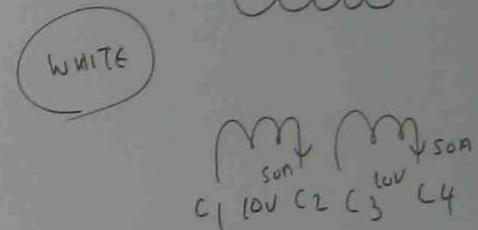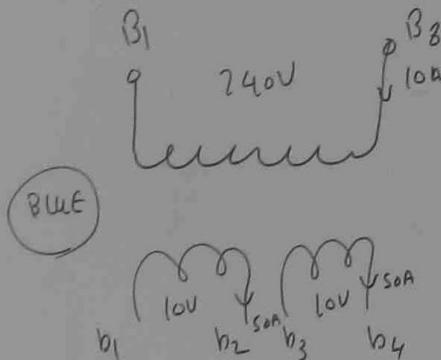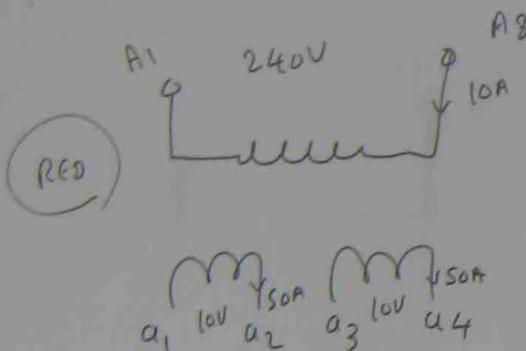PRACTICAL CONNECTING VOLTAGE WINDINGS TO SUPPLY REQUIRED VOLTAGE
AND CURRENT



CONNECT
(1) PRIMARY = 720V, 10A

SECONDARY = 10V, 300A

(2) PRIMARY = 240V, 30A

SECONDARY = 60V, 50A

(3) PRIMARY = 240V, 30A

SECONDARY = 20V, 150A