

REVIEW QUESTION 1/4

Q1 How will you check polarity of transformer for parallel operation?

Q3 DESCRIBE HOW INSULATION AND VOLTAGE LEVEL DETERMINE THE ARRANGEMENT OF WINDINGS?


Q3 WRITE THE EFFICIENCY EQUATION FOR TRANSFORMER

Q4 WRITE THE EQUATION TO CALCULATE MAXIMUM EFFICIENCY

Q5 DRAW THE APPROXIMATE EQUIVALENT CIRCUIT OF ONE PHASE OF 3 ϕ TRANSFORMER


Q6 DRAW THE BLOCK DIAGRAM FOR (i) NO LOAD TEST
(ii) SHORT CIRCUIT TEST

Q1

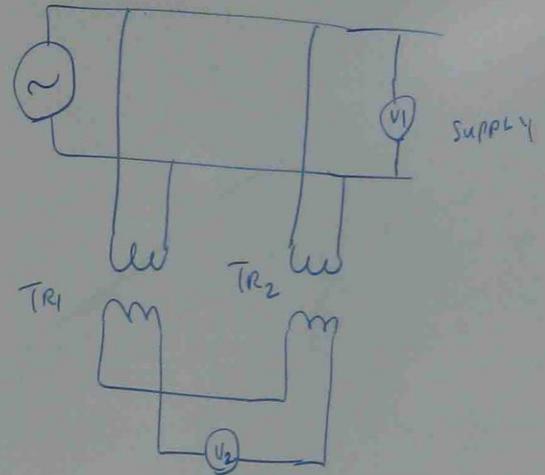



$$V_2 \approx 0$$

THEN CONNECT

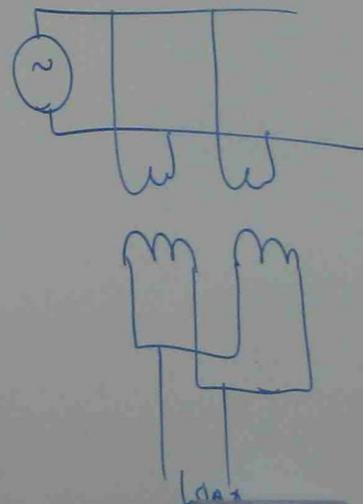


$V_2 =$ LINE VOLTAGE (V_1)

CHANGE CONNECTION & RE-TEST

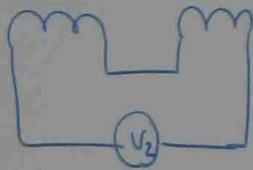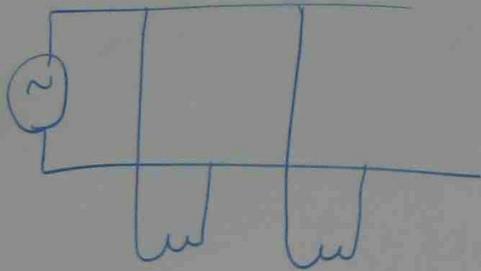

IF $V_2 \approx 0$

THEN CONNECT

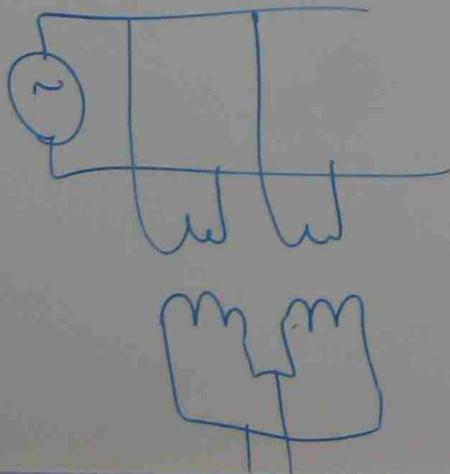

FLEXIBLE DELIVERY WEB SITE NOTES

IF YOU CAN NOT GET DOWN LOAD

— GIVE ME YOUR USB TO COPY

(OR)

SEND USB BY POST TOGETHER WITH
STAMPED & ADDRESSED ENVELOPE TO

To - U KYAW NAING
PO BOX 227
MARRICKVILLE

NSW 1475

Q 2 L.V WINDING HAS LARGER CROSS SECTIONAL AREA AND LESS INSULATION
THEY ARE MOUNTED RIGHT NEXT TO THE CORE TO ACHIEVE A BETTER
SPACING FACTOR.

THE H.V WINDING REQUIRES MORE INSULATION MATERIAL TO WITHSTAND
THE LARGER VOLTAGE. THEY ARE MOUNTED NEXT TO L.V WINDING.

Q 3

$$\% \text{ EFFICIENCY} = \frac{L \times \text{FULL LOAD V.A} \times \text{PF}}{L \times \text{FULL LOAD V.A} \times \text{PF} + P_{OC} + L^2 P_{SC}} \times 100$$

$$L = \text{LOAD RATIO} = \frac{\text{ANY LOAD}}{\text{FULL LOAD}}$$

V.A = VOLT-AMP

P_{OC} = OPEN CIRCUIT LOSS (IRON LOSS)

P_{SC} = SHORT CIRCUIT LOSS (COPPER LOSS)

Q4


AT MAXIMUM EFFICIENCY

OPEN CIRCUIT POWER LOSS = SHORT CIRCUIT POWER LOSS
(IRON LOSS) (COPPER LOSS)

$$P_{oc} = I^2 P_{sc}$$

$$\therefore I = \sqrt{\frac{P_{oc}}{P_{sc}}}$$

Q5

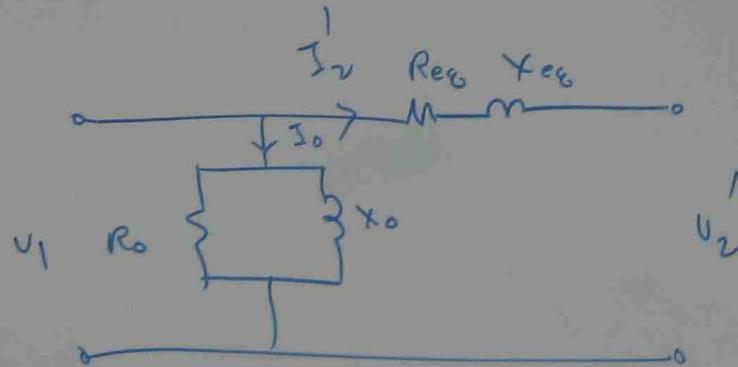


$$R_{1eq} = (R_1 + R_2') \quad , \quad R_2' = R_2 \left(\frac{N_1}{N_2}\right)^2$$

$$X_{1eq} = (X_1 + X_2') \quad , \quad X_2' = X_2 \left(\frac{N_1}{N_2}\right)^2$$


Q6

NO LOAD TEST

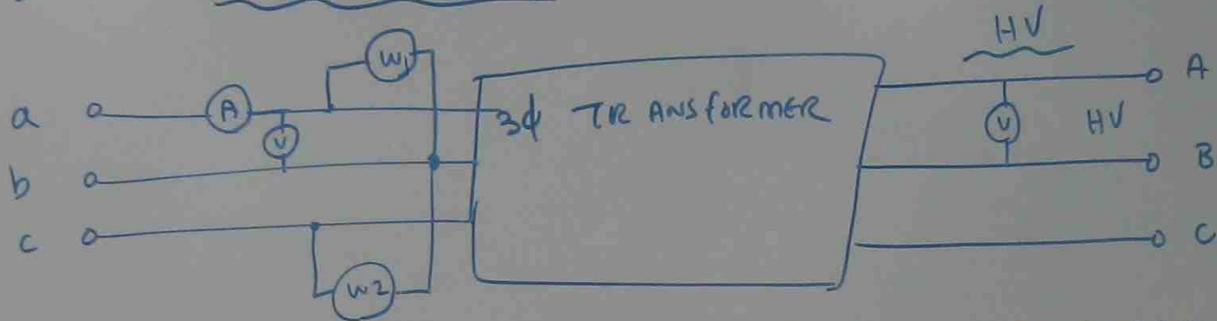

SUPPLY AT L.V

$$W_T = W_1 + W_2$$

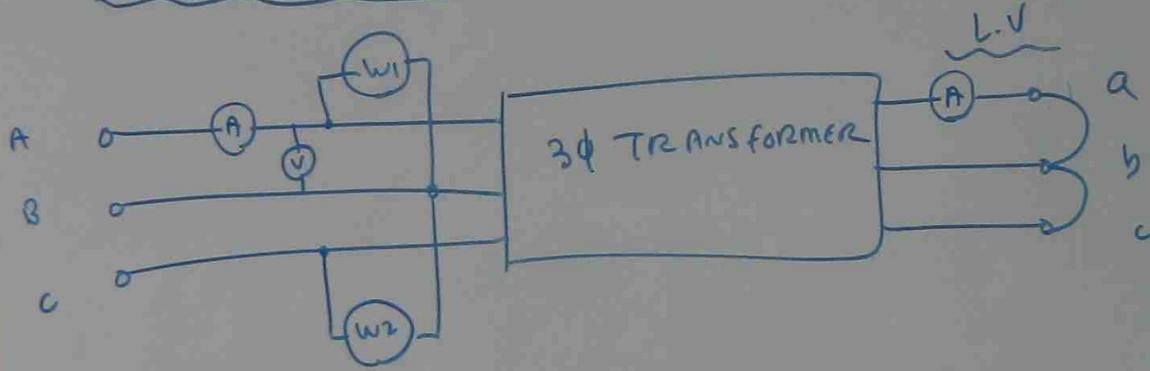

SUPPLY AT H.V

Q7

THE EXCITATION CURRENT MEASURED ON THE L.V SIDE OF 500 KVA
 Δ/Y 11 KV/415 V TRANSFORMER IS 12 AMP. IT'S EQUIVALENT

IMPEDANCE (PHASE REFERRED TO H.V SIDE IS $4.8 + j32 \Omega$.)

(a) EXPRESS THE EXCITATION CURRENT (UNIT ON BOTH HV/L.V SIDES
OF TRANSFORMER

(b) EXPRESS THE EQUIVALENT IMPEDANCE (UNIT ON HV & L.V SIDES OF
TRANSFORMER.

$$\text{HV SIDE LOAD CURRENT (I)} = \frac{500 \times 10^3}{\sqrt{3} \times 11 \times 10^3} = 26.2 \text{ Amp LINE}$$

$$\text{L.V SIDE LOAD CURRENT (I)} = \frac{500 \times 10^3}{\sqrt{3} \times 415} = 696 \text{ Amp LINE}$$

$$a = \frac{V_1(\text{Ph})}{V_2(\text{Ph})} = \frac{11000}{415/\sqrt{3}} = 45.8$$

$$Z_1 = a^2 Z_2$$
$$4.8 + j32 = (45.8)^2 Z_2$$

$$Z_2 = \frac{4.8 + j32}{(45.8)^2} =$$




Q3

SKETCH THE FOLLOWING WINDING CONNECTIONS AND THEIR ASSOCIATED




VOLTAGE PHASOR DIAGRAM FOR

(i) DELTA (ii) STAR.

(i) DELTA

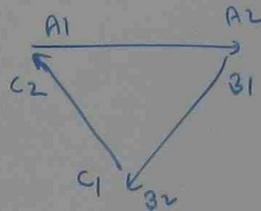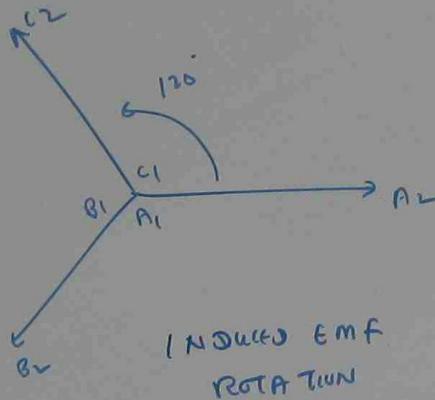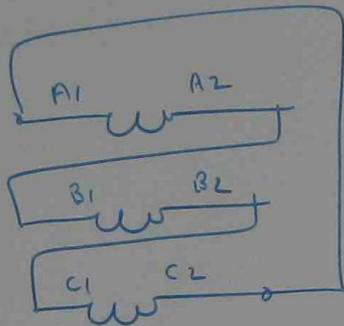

VOLTAGE PHASOR DIAGRAM

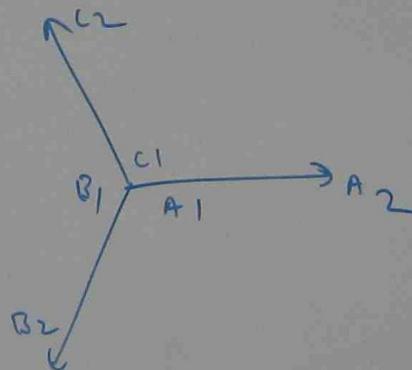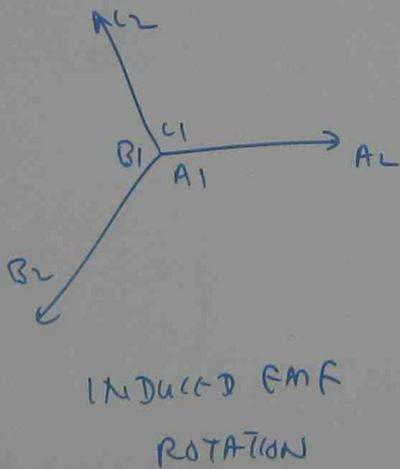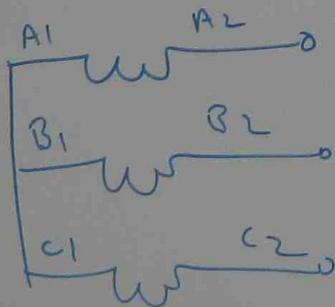

VOLTAGE PHASOR DIAGRAM


Q9 LIST THE FACTORS THAT ARE REQUIRED FOR SATISFACTORY PARALLEL OPERATION OF TRANSFORMERS.

- SAME VOLTAGE RATIO
- SAME PERCENTAGE IMPEDANCE
- SAME POLARITY
- SAME PHASE SEQUENCE
- SAME INHERENT PHASE ANGLE DIFFERENCE BETWEEN PRIMARY AND SECONDARY TERMINALS.

Q10 10 MVA, Δ Δ 33kV/11kV
 (OCT) LINE VOLTAGE = 11kV (SCT)
 LINE CURRENT = 15 AMP LINE VOLTAGE = 1650V
 POWER = 75 kW LINE CURRENT = RATED
 POWER = 90 kW

FIND CORE AND WINDING RESISTANCE & INDUCTIVE REACTANCE.

OCT - NO LOAD TEST

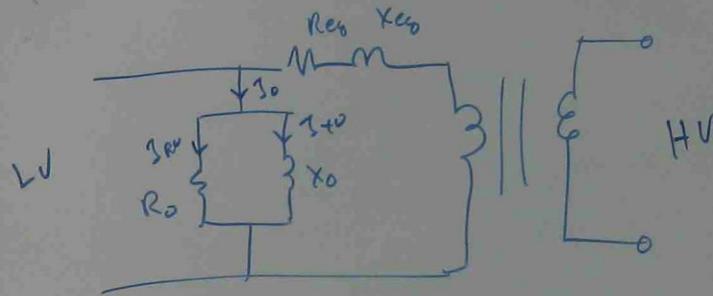

$$E = \frac{11 \text{ kV}}{\sqrt{3}} = 6350 \text{ V}$$

$$I_{Lph} = 15 \text{ AMP} = I_0$$

$$\text{Power} = 75 \text{ kW}$$

3ϕ

$$\text{Power } 1\phi = \frac{75}{3} = 25 \text{ kW}$$

$$R_0 = \frac{U_0^2}{\text{Power}} = \frac{6350^2}{25 \times 10^3} = 1613 \Omega$$

$$I_{R0}'' = \frac{V}{R_0''} = \frac{6350}{1613} = 3.94 \text{ Amp}$$

$$I_{X0}'' = \sqrt{(I_0'')^2 - (I_{R0}'')^2}$$

$$= \sqrt{15^2 - 3.94^2} = 14.47 \text{ Amp}$$


$$X_0'' = \frac{V_0}{I_{X0}''} = \frac{6350}{14.47} = 438.8 \Omega$$

$$V_{SC} = \frac{1650}{\sqrt{3}} = 952 \text{ V}$$

$$Z_e = \frac{V_{SC}}{I_{SC}'} = \frac{952}{175} = 5.42 \Omega$$

$$X_e' = \sqrt{(Z_e')^2 - (R_e')^2}$$
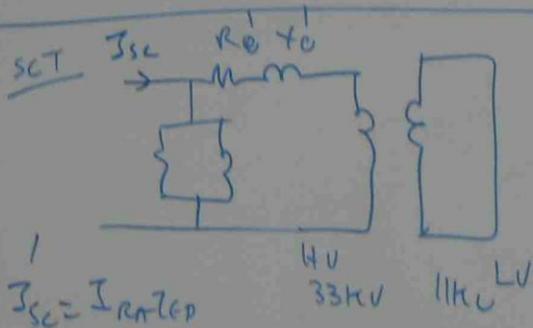
$$= \sqrt{5.42^2 - 0.98^2} = 5.3 \Omega$$



$$= \frac{10 \times 10^6}{\sqrt{3} \times 33 \times 10^3} = 175 \text{ Amp}$$


$$3(I_{sc}')^2 \times R_e' = 90 \times 10^3$$

$$3(175)^2 \times R_e' = 90 \times 10^3 \Rightarrow R_e' = 0.98 \Omega$$

$$R_0' = a^2 R_0'' = \left(\frac{33/\sqrt{3}}{11/\sqrt{3}}\right)^2 \times 1613 = 14500 \Omega$$


$$X_0' = a^2 X_0'' = \left(\frac{33/\sqrt{3}}{11/\sqrt{3}}\right)^2 \times 438.8 = 39500 \Omega$$
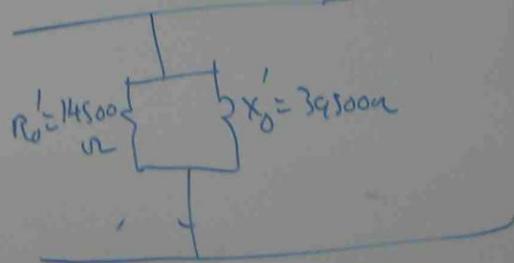
$$R_e' = 0.98 \Omega \quad X_e' = 5.3 \Omega$$




Q6

NO LOAD TEST

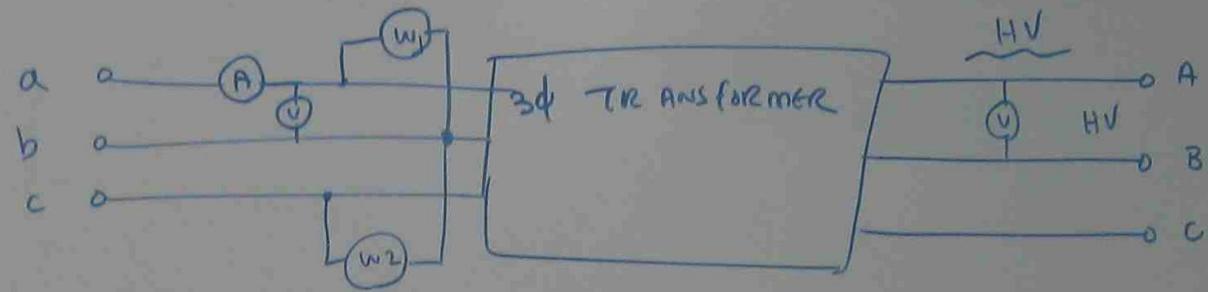

SUPPLY AT L.V

$W_T = W_1 + W_2$

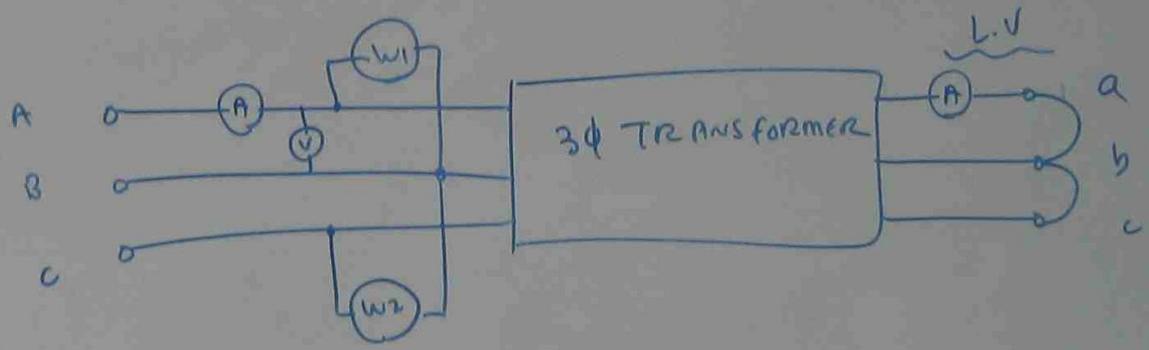

SUPPLY AT H.V

S.30

Q11 DESCRIBE THE PRINCIPLE METHODS USED TO COOL LARGE 3 ϕ TRANSFORMERS AND THE REASONS FOR THEIR USE.

Q12 DESCRIBE THE MEANINGS OF THE FOLLOWING VECTOR SYMBOLS
(i) D20 (ii) Zdg (iii) Dy1 (iv) Yz11





Q13 500 V / 250 V 1 ϕ TRANSFORMER RATED 10 KVA.
DIAGRAM FOR AUTO TRANSFORMER = 750 / 250 V
CALCULATE THE RATING OF AUTO TRANSFORMER

Q11 NATURAL AIR COOLING IS INSUFFICIENT FOR LARGE POWER TRANSFORMERS.
FORCED AIR (OR) FORCED OIL COOLING SYSTEMS ARE TO BE UTILIZED.


AS THE COPPER WINDINGS OF TRANSFORMER PRODUCED A LOT OF COPPER LOSSES HEAT,
IT CAN DOWNGRADE THE INSULATION RESISTANCE OF TRANSFORMER WINDINGS.

BY PROVIDING THE COOLING SYSTEM, TRANSFORMER LIFE CAN BE LONGER.

Q12

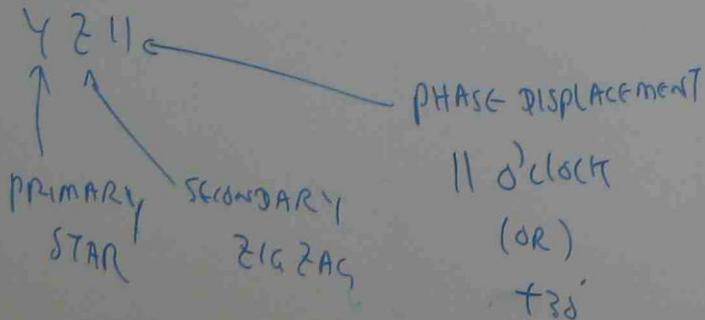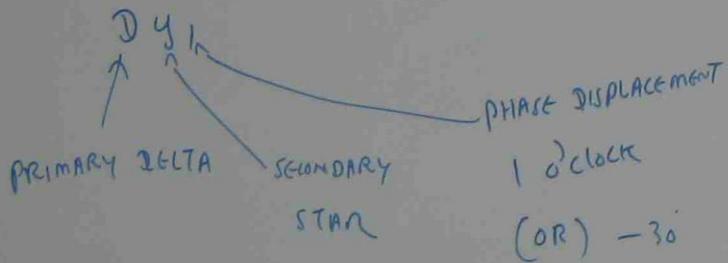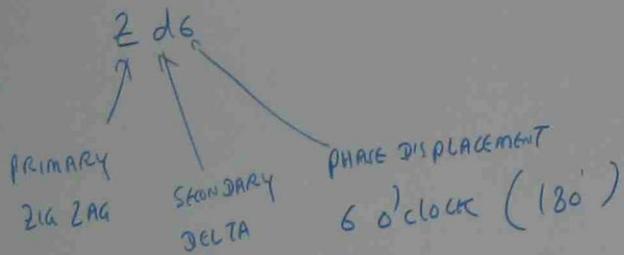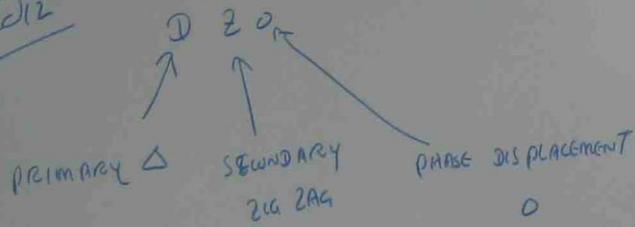

Q13

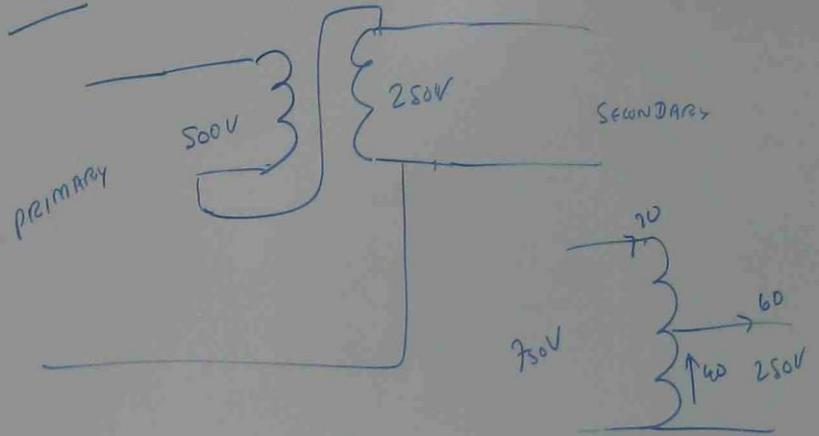

$$I_{PRI} = \frac{10 \text{ kVA}}{500 \text{ V}} = \frac{10 \times 10^3}{500} = 20 \text{ A}$$

$$I_{SEC} = \frac{10 \text{ kVA}}{250 \text{ V}} = \frac{10 \times 10^3}{250} = 40 \text{ A}$$

$$k = \frac{750}{250} = 3$$

$$\text{Auto TR power} = \left(1 - \frac{1}{k}\right) \times \text{TR power}$$

$$= \left(1 - \frac{1}{3}\right) \times 10$$

$$= 0.667 \times 10 = 6.67 \text{ kVA}$$

Q14

LIST THE REQUIREMENT OF THE OIL IN OIL IMMERSED TRANSFORMER

Q15

LIST THE IMPORTANT CHARACTERISTICS OF OIL IN OIL TESTING.

Q16

WHICH TRANSFORMER CAN CARRY HARMONICS?

Δ , Δ WITH NEUTRAL, Δ WITHOUT NEUTRAL

Q17

WHAT ARE THE DISADVANTAGE OF HARMONICS?

Q18

EXPLAIN THE EFFECT OF DELTA CONNECTION ON THIRD HARMONICS

Q19

EXPLAIN THE EFFECT OF CORE TYPE & SHELL TYPE CIRCUITS ON THIRD HARMONICS

Q20

DESCRIBE THE FACTORS WHICH GOVERN THE TRANSPORTATION OF LARGE POWER TRANSFORMERS.

Q14 Low viscosity, HIGH FLASH POINT, Low acidity
SATISFACTORY INSULATOR

Q15 ELECTRIC STRENGTH, WATER CONTENT, LOSS TANGENT,
RESISTIVITY, ACIDITY, SLUDGE, FLASH POINT


Q16 $\lambda \Delta$ - HARMONIC CURRENT CAN CIRCULATE IN Δ
 $\lambda \lambda$ WITH NEUTRAL - HARMONIC CURRENT CAN BE TAKEN AWAY
BY NEUTRAL
 $\lambda \lambda$ WITHOUT NEUTRAL - HARMONIC CURRENT CAN NOT BE TAKEN
AWAY. IT WILL COMBINE WITH LINE
VOLTAGES AND LINE VOLTAGES WILL BE
DISTORTED.

Q17 LINE VOLTAGE WAVE FORM IS DISTORTED.
POWER LOSS IS HIGHER
TRANSFORMER INSULATION DIELECTRIC STRENGTH
IS DOWNGRADED.

Q 18


NO HARMONIC CURRENT EXISTS IN LINE BUT IT EXISTS IN PHASES.

Q 19

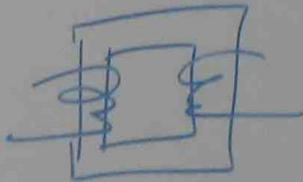

CORE TYPE

NO HARMONIC RETURN
PATH

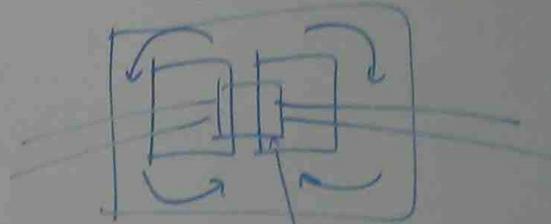

SHELL TYPE

PRIMARY + SECONDARY

HARMONIC CURRENT CAN BE TAKEN AWAY
BY OUTER LIMBS

Q 20

TRANSFORMER WEIGHT, THE STRENGTH OF ROADS, STRENGTH OF
BRIDGE, THE HEIGHT OF TUNNELS ARE TO BE CONSIDERED.

INSTEAD OF TRANSPORTING THE BIG UNIT, SMALL UNITS ARE TO BE
TRANSPORTED AND THEN PARALLEL CONNECTION IS TO BE MADE.

Q11 DESCRIBE THE PRINCIPLE METHODS USED TO COOL LARGE 3 ϕ TRANSFORMERS AND THE REASONS FOR THEIR USE.

Q12 DESCRIBE THE MEANINGS OF THE FOLLOWING VECTOR SYMBOLS
(i) D20 (ii) Zdg (iii) Dy1 (iv) Yz11

Q13 500V / 250V 1 ϕ TRANSFORMER RATED 10 KVA.

DIAGRAM FOR AUTO TRANSFORMER = 750 / 250 V





CALCULATE THE RATING OF AUTO TRANSFORMER

Q11 NATURAL AIR COOLING IS INSUFFICIENT FOR LARGE POWER TRANSFORMERS.
FORCED AIR (OR) FORCED OIL COOLING SYSTEMS ARE TO BE UTILIZED.


AS THE COPPER WINDINGS OF TRANSFORMER PRODUCED A LOT OF COPPER LOSSES HEAT,
IT CAN DOWNGRADE THE INSULATION RESISTANCE OF TRANSFORMER WINDINGS.

BY PROVIDING THE COOLING SYSTEM, TRANSFORMER LIFE CAN BE LONGER.

Q12

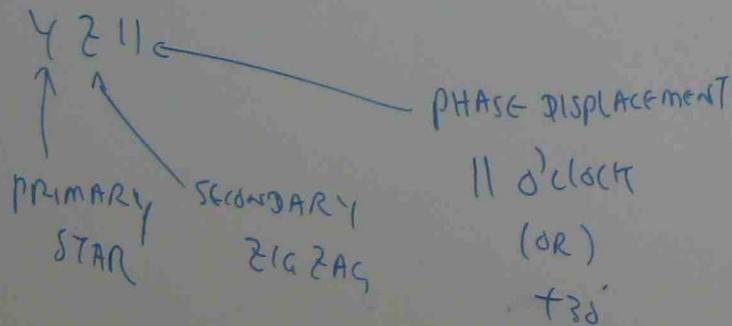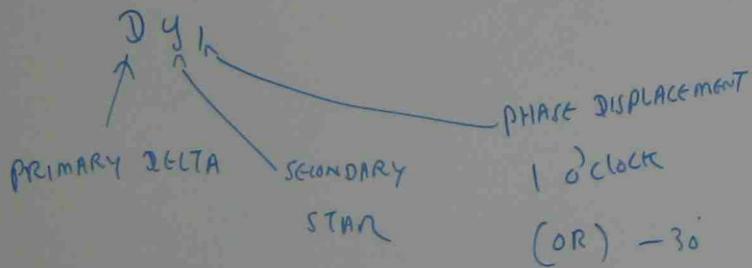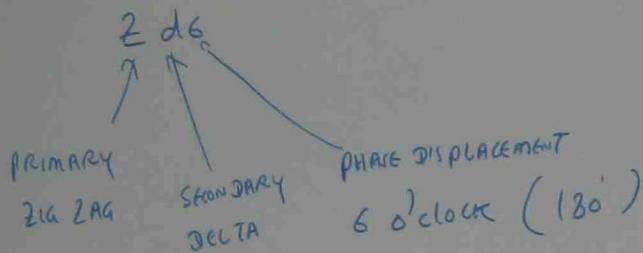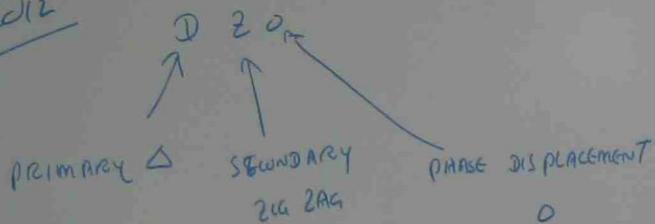

Q13

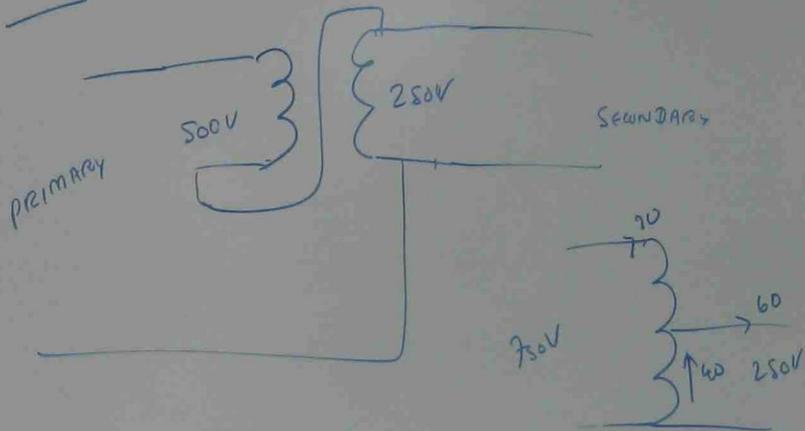

$$I_{PRI} = \frac{10 \text{ kVA}}{500 \text{ V}} = \frac{10 \times 10^3}{500} = 20 \text{ A}$$

$$I_{SEC} = \frac{10 \text{ kVA}}{250 \text{ V}} = \frac{10 \times 10^3}{250} = 40 \text{ A}$$

$$k = \frac{750}{250} = 3$$

$$\text{Auto TR POWER} = \left(1 - \frac{1}{k}\right) \times \text{TR POWER}$$

$$= \left(1 - \frac{1}{3}\right) \times 10$$

$$= 0.667 \times 10$$

$$= 6.67 \text{ kVA}$$