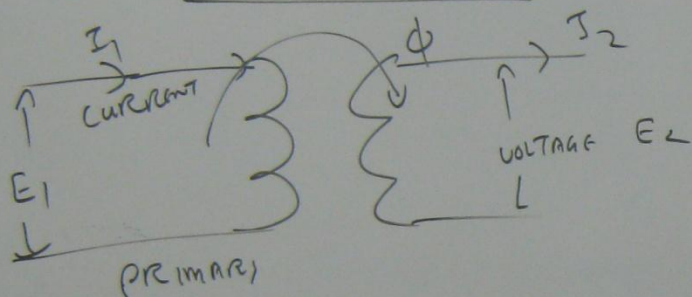


TRANSFORMER




$$\frac{E_1}{E_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2} = a$$


IRON CORE — LAMINATED CORE
TO REDUCE EDDY CURRENT LOSS.

CORE CONSTRUCTION


SHELL

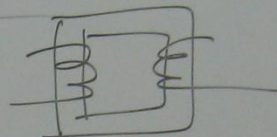

CORE

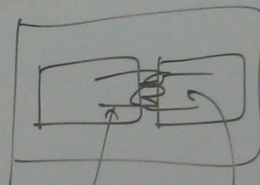


PRIMARY WINDING
SECONDARY WINDING

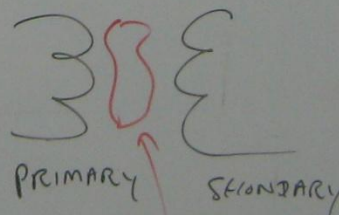

INSULATION

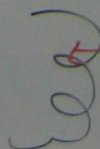MAJOR INSULATION — INSULATION BETWEEN WINDINGS.



INSULATION BETWEEN TURNS → MINOR INSULATION

TRANSFORMER VOLTAGE EQUATION

$$E = 4.44 f N \Phi$$

f = frequency (Hz)

N = No. of turns

Φ = Flux (wb)


$$\Phi = \text{flux density} \times \text{core c.s.a}$$

$$\phi = B \times A$$

pb CALCULATE IRON CORE FLUX DENSITY AND RMS
MAGNETIZING CURRENT FOR THE FOLLOWING 1 ϕ

TRANSFORMER

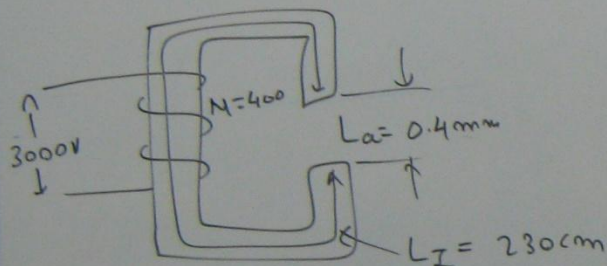$N_p = 400$ $E_p = 3000$ V (RMS), CORE CSA = 200 cm^2
CORE LENGTH = 230 cm, AIR GAP = 0.4 mm $\mu_r = 1900$



$$H \times L = N \times I$$

MAGNETIZING

$$\text{FORCE} = \frac{\text{FLUX DENSITY}}{\text{PERMEABILITY}}$$

$$= \frac{B}{\mu}$$

$$H_a \times L_a + H_I \times L_I = N \times I$$

$$\frac{B}{\mu} \times L_a + \frac{B}{\mu} L_I = N \times I$$

$$\frac{\phi / A}{\mu_0} \times \frac{0.4}{1000} + \frac{\phi / A}{\mu_r \mu_0} \times \frac{230}{100} = 400 \times I$$

$$E = 4.44 f \phi N$$

$$3000 = 4.44 \times 50 \times \phi \times 400$$

$$\phi = 0.028 \text{ wb}$$

$$\frac{0.028 / 200 \times 10^{-4}}{4\pi \times 10^{-7}} \times \frac{0.4}{100} + \frac{0.028 / 200 \times 10^{-4}}{1900 \times 4\pi \times 10^{-7}} \times \frac{230}{100} = 400 \times I$$

$$I = 4.5 \text{ A}$$

(max)

$$I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}}$$

$$= \frac{4.5}{\sqrt{2}}$$



$$= 3.17 \text{ Amp}$$

TRANSFORMER COOLING — AIR
 FREE FROM MOISTURE
 SILICA GEL

OIL
 LOW VISCOSITY
 HIGH FLASH POINT
 LOW ACIDITY
 LOW SLUDGE
 HIGH INSULATION
 PROPERTIES


AS 1767, AS 1883 → TRANSFORMER OIL

PARALLEL CONNECTION

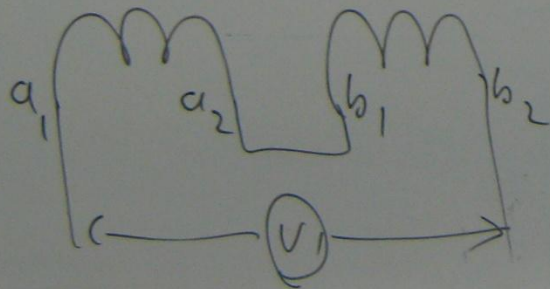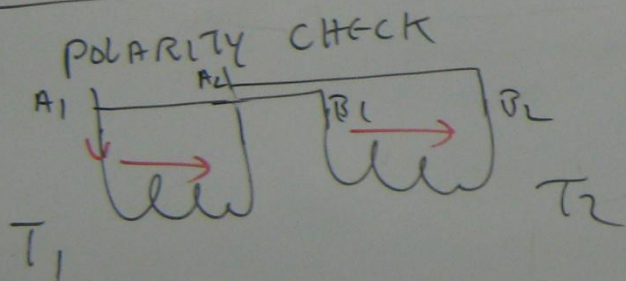

$$V_1 \approx 0$$

THEN CONNECT

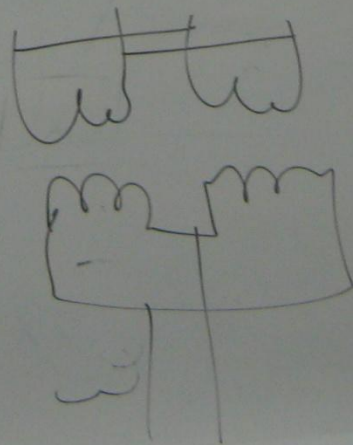


$V \approx$ LINE VOLTAGE
 CHANGE THE CONNECTION & TEST AGAIN

pb TRANSFORMER (A) RATED 15 MVA
 $\%Z_a = 3 + j6\%$

TRANSFORMER (B) RATED 30 MVA

$\%Z_b = 4 + j8\%$
 CALCULATE (a) $\%Z$ of 30 MVA TRANSFORMER
 BASED ON 15 MVA

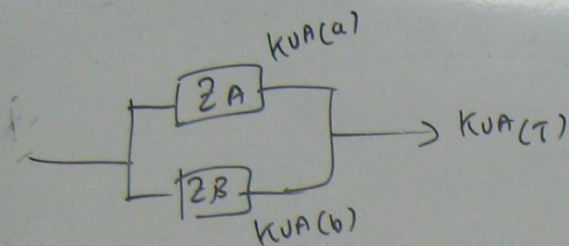(b) MVA SUPPLIED BY
 EACH TRANSFORMER WHEN
 THE COMBINATION OF
 THEM ARE SUPPLYING
 12 MVA UNITY P.F



$$KVA(a) = \frac{Z_B}{Z_A + Z_B} \times KVA(T)$$

$$KVA(b) = \frac{Z_A}{Z_A + Z_B} \times KVA(T)$$

$$\% X_2 = \frac{MVA(BASE)}{MVA_1} \times \% X_1$$

$$(a) Z_2 = \frac{MVA(BASE)}{MVA_1} \times Z_1$$

$$= \frac{15}{30} (4 + j8)$$

$$Z_B = 2 + j4 \quad \text{Base on 15 MVA}$$

$$Z_A = 3 + j6 \quad \text{Base on 15 MVA}$$

$$KVA(a) = \frac{Z_B}{Z_A + Z_B} \times KVA_T$$

$$= \frac{2 + j4}{3 + j6 + 2 + j4} \times 12$$

$$= \frac{\sqrt{2^2 + 4^2}}{\sqrt{5^2 + 10^2}} \times 12$$



$$= 4.79 \text{ MVA}$$

$$KVA(b) = \frac{Z_A}{Z_A + Z_B} \times 12$$

$$= \frac{3 + j6}{3 + j6 + 2 + j4} \times 12$$

$$= \frac{\sqrt{3^2 + 6^2}}{\sqrt{5^2 + 10^2}} \times 12 = 7.19$$

TRANSFORMER EQUIVALENT CIRCUIT

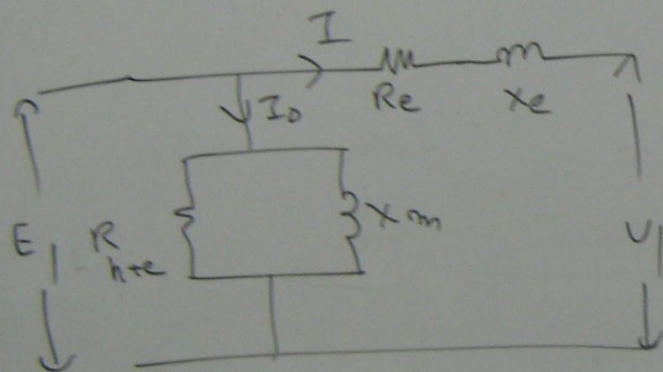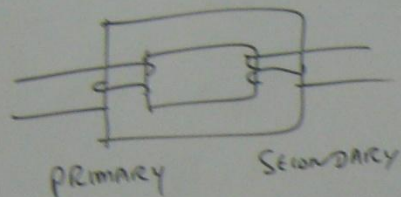

$$R_e = R_1 + a^2 R_2$$

R_1 = PRIMARY WINDING RESISTANCE

R_2 = SECONDARY WINDING RESISTANCE


$$a = \frac{N_1}{N_2} = \text{TURN RATIO}$$

$$X_e = X_1 + a^2 X_2$$

R_{htc} = CORE RESISTANCE

X_m = CORE INDUCTIVE REACTANCE

OPEN CIRCUIT TEST

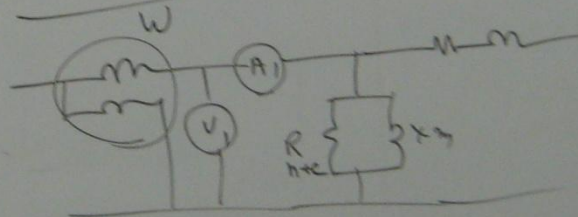


$$R_{htc} = \frac{V^2}{W}$$

$$VAR = \sqrt{(V I)^2 - (W)^2}$$

$$X_m = \frac{V^2}{VAR}$$

SHORT CIRCUIT TEST

L.V WINDING SIDE IS SHORT CIRCUITED

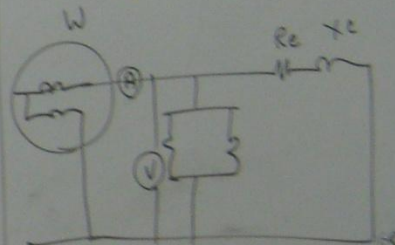


$$I^2 R_e = W$$

$$R_e = \frac{W}{I^2}$$

$$Z_e = \frac{V}{I}$$

$$X_e = \sqrt{Z_e^2 - R_e^2}$$

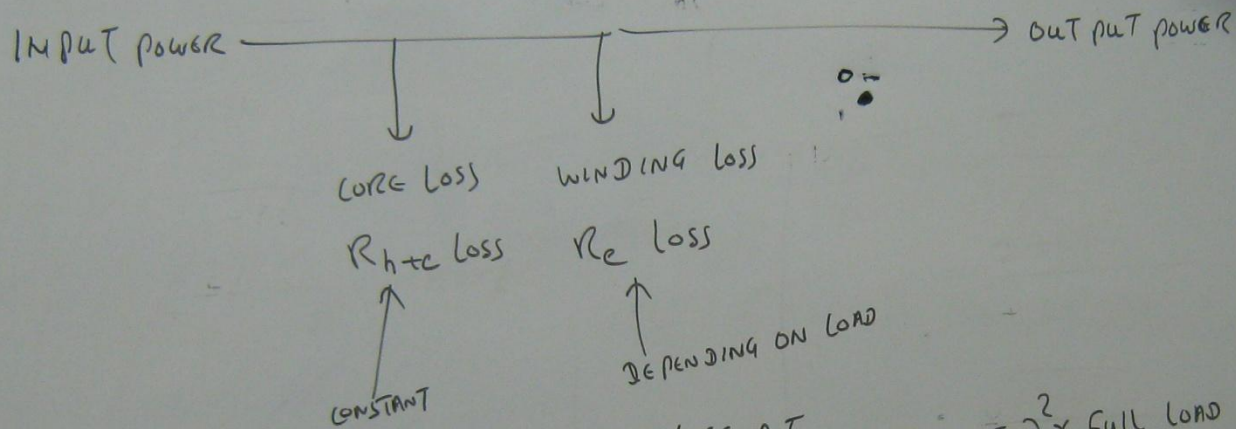

WINDING LOSS AT ANY LOAD (COPPER LOSS) $= (\text{LOAD RATIO})^2 \times \text{FULL LOAD COPPER LOSS}$

$\frac{1}{2}$ LOAD COPPER LOSS $= \left(\frac{1}{2}\right)^2 \times \text{FULL LOAD COPPER LOSS}$

TRANSFORMER MAXIMUM EFFICIENCY

CONSTANT LOSS = VARIABLE LOSS
 (CORE LOSS) (COPPER LOSS)

12-4-19

pb

THE FOLLOWINGS ARE TEST RESULTS OF 3 ϕ 66/11KV 30 MVA

Y/Y TRANSFORMER

NO LOAD TEST

L.V SIDE = 11KV, L.V SIDE CURRENT = 50 AMP
VOLTAGE
POWER = 25 KW

SHORT CIRCUIT TEST

LINE VOLTAGE = 1650V, LINE TO LINE CURRENT = RATED CURRENT
POWER = 20 KW.

$$R_{h+c} = \frac{V_{ph}^2}{1\phi \text{ NO LOAD POWER}} = \frac{(11000/\sqrt{3})^2}{\frac{25000}{3}} = 4840\Omega$$

$$I_m = \sqrt{I^2 - I_{h+c}^2} = \sqrt{50^2 - \left(\frac{V_{ph}}{R_{h+c}}\right)^2} = \sqrt{50^2 - \left(\frac{11000/\sqrt{3}}{4840}\right)^2}$$

$$= 49.98 \text{ AMP}$$

$$X_m = \frac{V_{ph}}{I_m} = \frac{11000/\sqrt{3}}{49.98} = 127.06\Omega$$

SHORT CIRCUIT TEST

$$I^2 \times R_{eq} = 1\phi \text{ SHORT CIRCUIT POWER}$$

$$\left(\frac{30 \times 10^6}{\sqrt{3} \times 66 \times 10^3}\right)^2 \times R_{eq} = \frac{20 \times 10^3}{3}$$

$$R_{eq} = 0.097\Omega$$

$$Z_{eq} = \frac{V_{ph}}{I} = \frac{1650/\sqrt{3}}{\frac{30 \times 10^6}{\sqrt{3} \times 66 \times 10^3}} = 3.63\Omega$$


$$X_{eq} = \sqrt{(Z_{eq}')^2 - (R_{eq}')^2}$$

$$= \sqrt{3.63^2 - 0.097^2}$$

$$= 3.62\Omega$$

$$R_{h+c}^1 = a^2 (R_{h+c}') = \left(\frac{66}{11}\right)^2 \times 4840$$

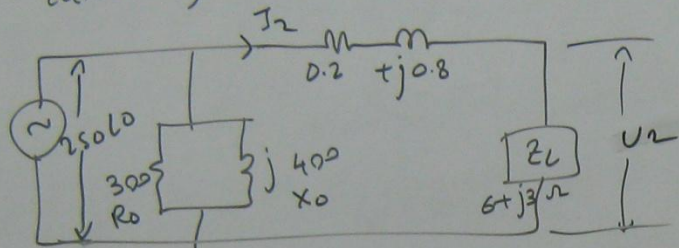1ph) IN THE FOLLOWING PROBLEM, FIND (a) IRON LOSS, (b) SECONDARY LOAD CURRENT, (c) COPPER LOSS, (d) LOAD POWER, (e) EFFICIENCY



$$(a) \text{ IRON LOSS} = \frac{V^2}{R_0} = \frac{250^2}{300} = 208.1 \text{ WATT}$$

$$\begin{aligned} (b) I_2 &= \frac{V}{Z_c + Z_L} \\ &= \frac{250}{0.2 + j0.8 + 6 + j3} \\ &= \frac{250}{6.2 + j3.8} \\ &= \frac{250}{\sqrt{6.2^2 + 3.8^2}} = 34.38 \text{ Amp} \end{aligned}$$

$$\begin{aligned} (c) \text{ COPPER LOSS} &= I_2^2 R_e \\ &= (34.38)^2 \times 0.2 \\ &= 236.39 \text{ WATT} \end{aligned}$$

$$\begin{aligned} (d) \text{ LOAD POWER} &= I_L^2 \times R_L = 34.38^2 \times 6 \\ &= 7075 \text{ WATT} \end{aligned}$$

$$\begin{aligned} \text{INPUT} &= \text{LOAD POWER} + \text{COPPER LOSS} + \text{IRON LOSS} \\ &= 7075 + 236.39 + 208.1 \\ &= 7536 \text{ WATT} \end{aligned}$$

$$\begin{aligned} \% \text{ EFFICIENCY} &= \frac{\text{OUTPUT}}{\text{INPUT}} \times 100 \\ &= \frac{7075}{7536} \times 100 = 94.1\% \end{aligned}$$

TRANSFORMER AT LOAD —
 — % REGULATION (VOLTAGE DROP)
 — EFFICIENCY (→ ALL DAY EFFICIENCY)

$$\% \text{ VOLTAGE REGULATION} = \% R \cos \theta \pm \% X \sin \theta$$

+ LAGGING
- LEADING

pb A 1500 KVA 6600/415V 3 ϕ Δ / λ TRANSFORMER

$$\% R = 1.8, \% X = 9$$

MAXIMUM EFFICIENCY OCCURS AT $\frac{1}{4}$ LOAD
 CALCULATE (a) IRON LOSS (b) MAX. EFFICIENCY AT 0.9 PF LAGGING

(c) FULL LOAD % REGULATION AT 0.8 PF LEADING.

$$I_{\text{LINE}} = \frac{KVA \times 10^3}{\sqrt{3} V} = \frac{1500 \times 10^3}{1.732 \times 6600} = 131.2 \text{ Amp}$$

$$\Delta \quad I_{\text{ph}} = \frac{I_{\text{LINE}}}{\sqrt{3}} = \frac{131.2}{1.732} = 75.76 \text{ Amp}$$

$$\% R = \frac{I R}{V_{\text{ph}}} \times 100$$

$$1.8 = \frac{75.76 \times R}{66 \times 10^3} \times 100$$

$$R = 1.57 \Omega$$

$$\% X = \frac{I X}{V_{\text{ph}}} \times 100$$

$$9 = \frac{75.76 \times X}{66 \times 10^3} \times 100$$

$$X = 4.36 \Omega$$

$$\text{Full Load Copper Loss} = 3 I_{\text{FL}}^2 \times R$$

$$= 3 \times (75.76)^2 \times 1.57$$

$\frac{1}{4}$ LOAD → MAXIMUM EFFICIENCY

IRON LOSS = $\frac{1}{4}$ LOAD COPPER LOSS

$$\text{IRON LOSS} = \left(\frac{1}{4}\right)^2 \times 3 \times (75.76)^2 \times 1.57$$

$$= 1689 \text{ W}$$

$$\text{O/P AT } 0.9 \text{ P.F LAGGING} = 1500 \text{ kVA} \times \text{P.F} \\ = 1500 \times 0.9$$

$$\text{MAX EFFICIENCY} = \frac{1}{4} \text{ LOAD} = \frac{1}{4} \times 1500 \times 0.9$$

$$\text{MAX EFFICIENCY COPPER LOSS} = \left(\frac{1}{4}\right)^2 \times 3 (75.76)^2 \times 1.57 = 1689$$

$$\text{MAX EFFICIENCY IRON LOSS} = 1689$$

$$\begin{aligned} \text{EFFICIENCY} &= \frac{\text{OUT PUT}}{\text{OUT PUT} + \text{IRON LOSS} + \text{COPPER LOSS}} \times 100 \\ &= \frac{\frac{1}{4} \times 1500 \times 10^3 \times 0.9}{\frac{1}{4} \times 1500 \times 10^3 \times 0.9 + 1689 + 1689} \times 100 \\ &= 99\% \end{aligned}$$

$$\% \text{ REGULATION} = \% R \cos \theta \pm \% X \sin \theta$$

FOR LEADING PF


$$\% \text{ REG} = \% R \cos \theta - \% X \sin \theta$$

$$\cos \theta = 0.8$$


$$\theta = \cos^{-1} 0.8 = 36.8$$

$$\sin \theta = \sin 36.8 = 0.6$$

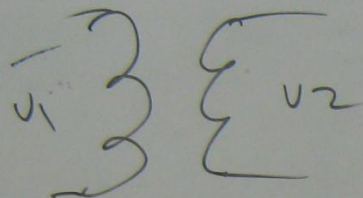
$$\begin{aligned} \% \text{ REG} &= 1.8 \times 0.8 - 5 \times 0.6 \\ &= \end{aligned}$$



2 WINDING
TRANSFORMER

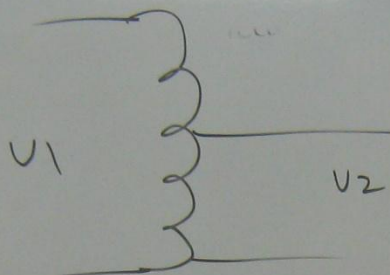


STEP DOWN AUTO TRANSFORMER

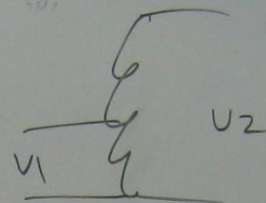


STEP UP AUTO TRANSFORMER
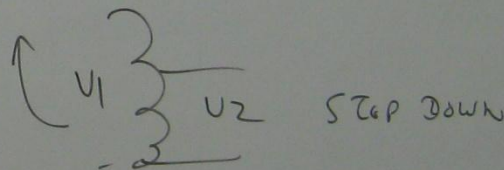
$$\text{Auto TRANSFORMER POWER RATING (U.A)} = \left(1 - \frac{1}{k}\right) \times \text{2 WINDING TRANSFORMER U.A}$$



STEP DOWN

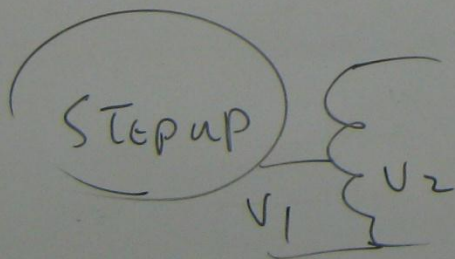

$$\text{Auto U.A} = (1 - k) \times \text{2 WINDING TR. U.A}$$

$$k = \frac{V_1}{V_2}$$

= 100 W


pb 400/200 V 2 WINDING TRANSFORMER

1 ϕ RATED 5 KVA. THE TRANSFORMER IS TO SUPPLY 600/200 V

DRAW THE CIRCUIT DIAGRAM HOW TO SUPPLY THE LOAD.

ALSO FIND IT'S RATING WHILE SUPPLYING 600/200 V.

400 } { 200
2 WINDINGS

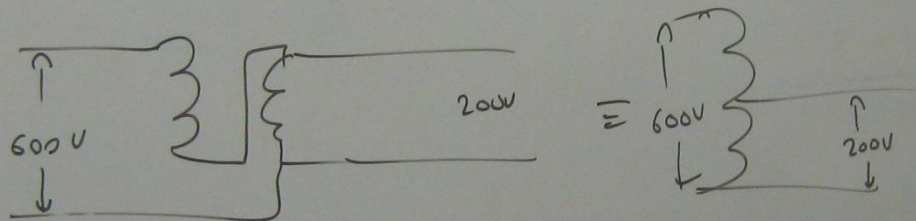

$$\text{Auto T.R } V_A = \left(1 - \frac{1}{k}\right) \times 2 \text{ WINDING T.R V.A}$$

$$k = \frac{V_1}{V_2} = \frac{600}{200} = 3$$

$$\text{Auto } V_A = \left(1 - \frac{1}{3}\right) \times 5$$

$$\rightarrow \frac{2}{3} \times 5 = 3.33 \text{ KVA}$$