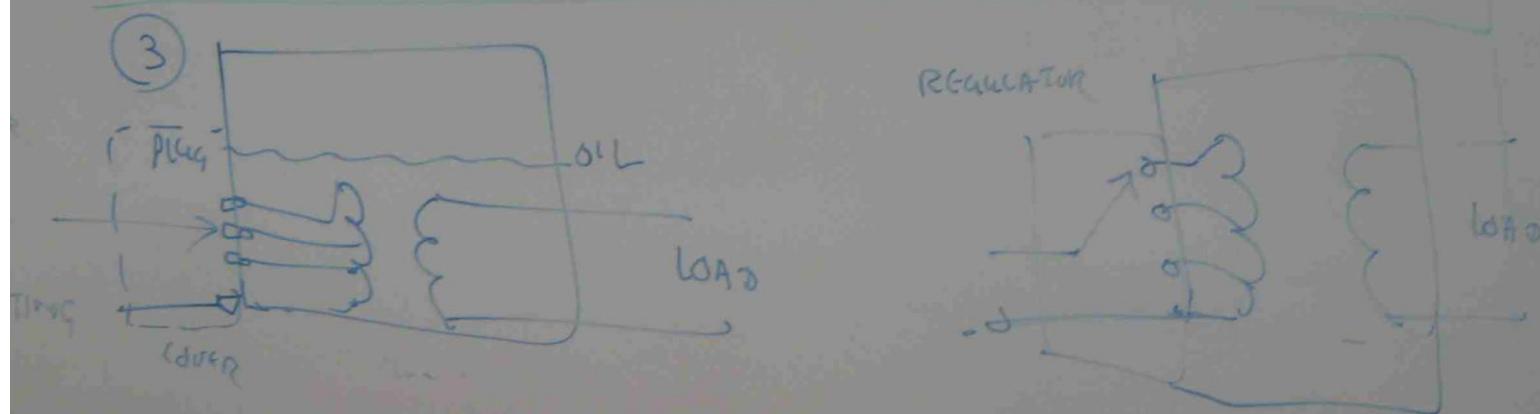


HIGH VOLTAGE SIDE HAS LOWER CURRENT. IT IS EASIER TO
HANDLE THE LOWER CURRENT. SO VOLTAGE CHANGING IS
MADE AT HIGH VOLTAGE SIDE RATHER THAN LOW VOLTAGE SIDE



ARRANGEMENT (1)

POWER TRANSFORMER TAPPINGS ARE TERMINATED JUST BELOW OIL LEVEL AND CHANGES ARE MADE MANUALLY BY MEANS OF SWINGING LINKS OR PLUGS ON TERMINAL BOARD


ARRANGEMENT (2)

THE TAPPING SELECTOR CAN BE OPERATED FROM OUTSIDE TANK BY A ROTARY
MOVEMENT OF SELECTOR HAND WHEEL

Q4 DESCRIBE BRIEFLY THE VARIOUS STAGES OF ON LOAD TAP CHANGING
USED IN POWER SYSTEM

Q5 LIST THE TWO FUNDAMENTAL FEATURES OF NO LOAD TAP
CHANGING CIRCUITS.



(4)

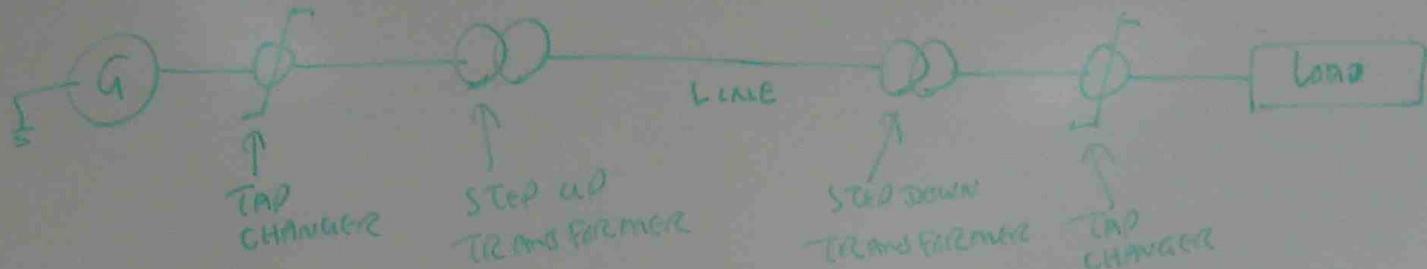

TAP CHANGERS ARE PLACED

- (i) AT POWER STATION TO THE STEP UP TRANSFORMER
- (ii) AT THE SUPPLY POINT TO CONTROL THE LOWER VOLTAGES TO SMALLER SUB STATIONS.

(5)

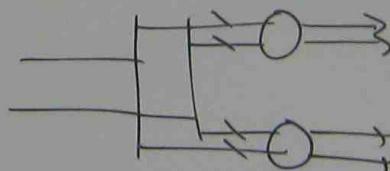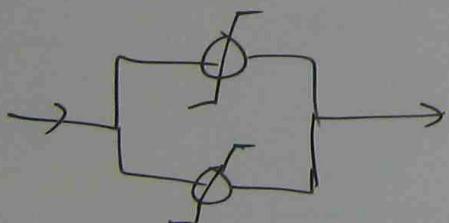

ALL TAP CHANGING CIRCUITS HAVE (i) SOME FORM OF IMPEDANCE WHICH IS INSERTED TO PREVENT THE SHORT CIRCUITING OF TAPPING SECTIONS AND (ii) A DUPLICATE CIRCUIT SO THAT THE LOAD CURRENT CAN BE CARRIED BY ONE CIRCUIT WHILE OTHER TAP CHANGER IS OUT OF ORDER.

Q6

BRIEFLY DESCRIBE THE EFFECT OF TAP CHANGING ON THE LIMITATION OF POWER SYSTEM OPERATION.

DUE TO THE DIFFERENT REACTANCE AT EACH TAP, THE ON LOAD TAP CHANGER HAS THE FOLLOWING IMPLICATIONS ON THE OPERATION OF POWER SYSTEM

(a) AT VARIOUS STEPS, THE SYSTEM IMPEDANCE CHANGES

(b) THE MINIMUM (AND) MAXIMUM TAPPINGS WILL INTRODUCE DIFFERENT FAULT IMPEDANCES.

3 ϕ TRANSFORMER VOLTAGE REGULATION, LOSSES AND EFFICIENCY

P_b 1000 kVA, 6600 / 415 V 3 ϕ Δ/λ

TRANSFORMER $\% R = 1.5$ $\% X = 4$ maximum

EFFICIENCY OCCURS AT $1/2$ LOAD

CALCULATE (a) IRON LOSS

(b) FULL LOAD EFFICIENCY AT 0.8 PF

LAGGING

(c) MAXIMUM EFFICIENCY AT 0.8
PF LAGGING

$$\% R = \frac{I_{FLph} \times R}{V_{ph}} \times 100$$

For Δ SIDE

$$V_{ph} = V_{LINE} = 6600 V$$

$$I_{FL} = \frac{(kVA \times 10^3)}{\sqrt{3} \times V_1} = \frac{(909 \times 10^3)}{1.7321 \times 6600} = 87.47 \text{ Amp}$$

(b) I. F

AT 0

$$\Delta I_{FL\ ph} = \frac{I_{FL}}{\sqrt{3}} = \frac{87.47}{1.7321} = 50.5 \text{ Amp}$$

$$I.S = \frac{50.5 \times R}{6600} \times 100$$

$$R = \frac{I.S \times 6600}{50.5 \times 100} = 1.96 \Omega$$

(c)

$$\% X = \frac{I_{FL\ ph} \times X}{V_{ph}} \times 100$$

$$X = \frac{\% X \times V_{ph}}{I_{FL\ ph} \times 100} = \frac{4 \times 6600}{50.5 \times 100} = 5.22 \Omega$$


$I_2 \rightarrow$ maximum Efficiency

$$VI = W_C_{FL}(V_2) = 3 \left[I_{FL}(I_2) \right]^2 \times R = 3 \left(\frac{50.5}{2} \right)^2 \times 1.96 = 3780 \text{ Watt}$$

$$) \% \text{ FULL LOAD EFFICIENCY} = \frac{\text{FULL LOAD OUTPUT}}{\text{FULL LOAD INPUT}} \times 100 = \frac{\text{FULL LOAD OUTPUT}}{\text{FULL LOAD OUTPUT} + WI + WCFL} \times 100 = \frac{\sqrt{3} V_L I_L \cos\phi}{\sqrt{3} V_L I_L \cos\phi + WI + 3(I_{fl})^2 R} \\ = \frac{1.7321 \times 6600 \times 87.47 \times 0.8}{1.7321 \times 6600 \times 87.47 \times 0.8 + 3750 + 3(50.5)^2 \times 1.96} \times 100 = 97.7\%$$

$$(ii) \% \text{ MAXIMUM EFFICIENCY} = \frac{\text{MAXIMUM EFFICIENCY OUT PUT}}{\text{MAXIMUM EFFICIENCY OUTPUT} + WI + WC} \times 100 \\ \text{AT } 0.8 \text{ PF LAGGING} \\ \left(\begin{array}{l} \text{LOAD = MAXIMUM} \\ \text{EFFICIENCY} \end{array} \right) \\ = \frac{\sqrt{3} V_L I_L \cos\phi}{\sqrt{3} V_L I_L \cos\phi + WI + WC} \\ = \frac{1.7321 \times 6600 \times \frac{1}{2} \times 87.47 \times 0.8}{1.7321 \times 6600 \times (\frac{1}{2} \times 87.47) \times 0.8 + 3750 + 3750} \times 100 \\ \approx 98.15\%.$$

UNBALANCED LOAD ON 3-phase TRANSFORMERS

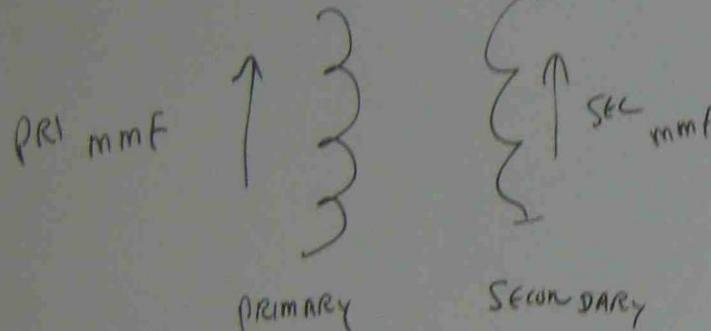


M M F - MAGNETIC MOTIVE FORCE


BALANCED LOADING

$$\text{MMF}_{\text{PRI}} = \text{MMF}_{\text{SEC}} \implies \frac{N_1}{N_2} = \frac{E_1}{E_2} = \frac{I_2}{I_1}$$

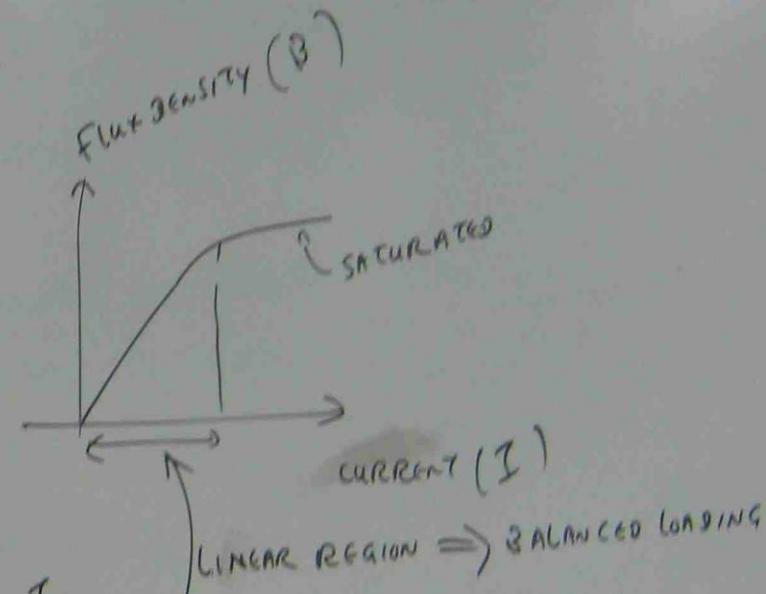
$$\text{mmf}_{\text{PRI}} \neq \text{mmf}_{\text{SEC}} \Rightarrow \frac{N_1}{N_2} \neq \frac{E_1}{E_2} \neq \frac{I_2}{I_1}$$




EXAMPLES OF UNBALANCED LOADING

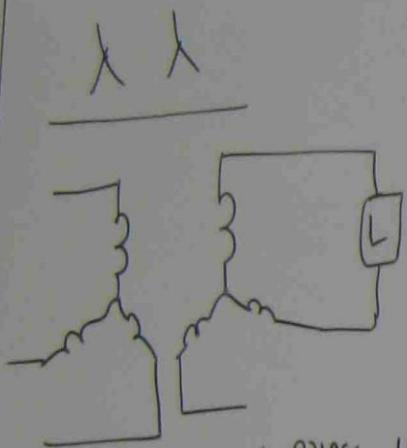


ONE PHASE IS OUT

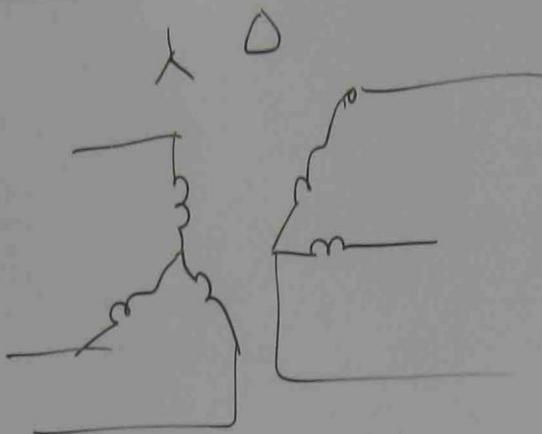

OPEN DELTA

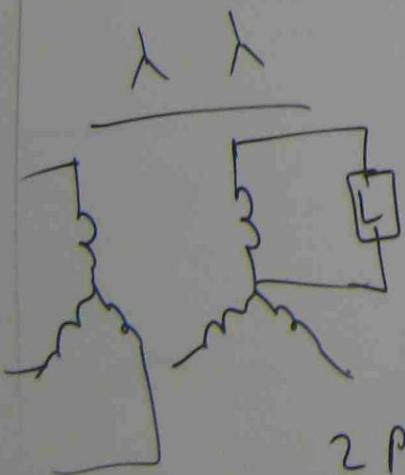

2 PHASES OUT

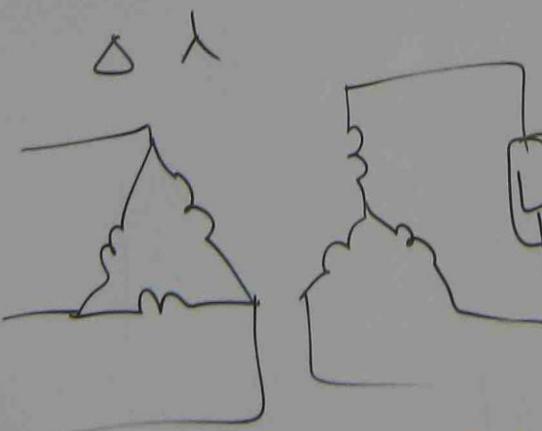

ONE PHASE OUT

(OR)

TWO PHASES OUT

IF UNBALANCED LOADING OCCURS,
TRANSFORMER CAN NO LONGER
FOLLOWS

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_L}{I_1}$$

THE SYSTEM OPERATION CAN
BE DISORDER.

FOR THIS REASON, BALANCING
/ TRANSPOSITION OF LINE
NEEDS TO BE DONE AT
EVERY INTERVAL OF
LINE SECTION

IF UNBALANCED LOADING OCCURS,
TRANSFORMER CAN NO LONGER
FOLLOWS

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

THE SYSTEM OPERATION CAN
BE DISORDER.

FOR THIS REASON, BALANCING
/ TRANSPOSITION OF LINE
NEEDS TO BE DONE AT
EVERY INTERVAL OF
LINE SECTION

$$I_{FL} = \frac{(KVA \times 10^3)}{\sqrt{3} \times V_1} = \frac{1000 \times 10^3}{\sqrt{3} \times 6600} = 87.47 \text{ Amp}$$

$$\Delta I_{FL ph} = \frac{I_{FL}}{\sqrt{3}} = \frac{87.47}{\sqrt{3}} = 50.5 \text{ Amp}$$

$$I.S = \frac{50.5 \times R}{6600} \times 100$$

$$R = \frac{I.S \times 6600}{50.5 \times 100} = 1.96 \Omega$$

$$\% X = \frac{I_{FL ph} \times X}{V_{ph}} \times 100$$

$$X = \frac{\% X \times V_{ph}}{I_{FL ph} \times 100} = \frac{4 \times 6600}{50.5 \times 100} = 5.22 \Omega$$

$\frac{1}{2} \rightarrow$ maximum efficiency

$$W_I = W_{c FL(V_2)} = 3 \left[I_{FL(V_2)} \right]^2 \times R = 3 \left(\frac{50.5}{2} \right)^2 \times 1.96 = 3750 \text{ WATT}$$

(b) ✓

AT


(c)

PARALLEL OPERATION OF 3 ϕ TRANSFORMERS

TO PARALLEL THE TRANSFORMERS, THE FOLLOWINGS MUST BE IDENTICAL

- (a) VOLTAGE RATIO
- (b) VECTOR GROUPING
- (c) %. IMPEDANCE
- (d) POLARITY

LOAD SHARING OF 3 ϕ TR

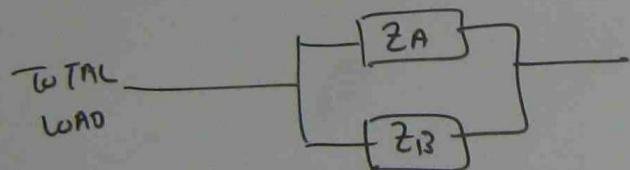

$$I_{RA} (VA) = VA_{TOTAL} \times \frac{Z_B}{Z_A + Z_B}$$

$$I_{RB} (VA) = VA_{TOTAL} \times \frac{Z_A}{Z_A + Z_B}$$

Pb TR-A $2+j5\%$ 10 MVA

TR-B $3+j7.5\%$ 20 MVA

CALCULATE (a) % IMPEDANCE OF 20 MVA TRANSFORMER TO BASE 10 MVA

(b) MVA SUPPLIED BY EACH TRANSFORMER IF LOAD IS 15 MVA AT UNITY PF

(c) WHETHER IS IT POSSIBLE TO SUPPLY 30 MVA IN COMBINATION.

(a) $\text{TRA} \rightarrow Z_A = 2+j5\% \quad (10 \text{ MVA})$

$$\text{TRB} \quad Z_{\text{NEW}} = \frac{\text{MVA NEW}}{\text{MVA OLD}} \times Z_{\text{OLD}}$$

$$= \frac{10}{20} \times (3+j7.5)$$

$$Z_B = 1.5+j3.75\%$$

$$(b) \quad \text{MVA (TR-A)} = \frac{\text{MVA (TOTAL)}}{\text{TOTAL}} \times \frac{Z_B}{Z_A + Z_B}$$

$$= \frac{15}{15+15} \times \frac{1.5+j3.75}{2+j5+1.5+j3.75}$$

$$= \frac{15 \times 1.5+j3.75}{3.5+j8.75}$$

$$= \frac{15 \times \sqrt{1.5^2+3.75^2}}{\sqrt{3.5^2+8.75^2}}$$

$$= 6.43 \text{ MVA}$$

$$\begin{aligned} \text{MVA}_{\text{TR-B}} &= \frac{\text{MVA}_{\text{TOTAL}}}{\text{TOTAL}} \times \frac{Z_A}{Z_A + Z_B} \\ &= 15 \times \frac{2 + j5}{3.5 + j8.75} \\ &= 15 \times \frac{\sqrt{2^2 + 5^2}}{\sqrt{3.5^2 + 8.75^2}} \\ &= 8.57 \text{ MVA} \end{aligned}$$

(c)

$$\begin{aligned} \text{MVA}_{\text{TR-A}} &= \frac{\text{MVA}_{\text{TOTAL}}}{\text{TOTAL}} \times \frac{Z_B}{Z_A + Z_B} \\ &= 30 \times \frac{\sqrt{1.5^2 + 3.75^2}}{\sqrt{3.5^2 + 8.75^2}} \\ &= 12.86 \text{ MVA} \end{aligned}$$

$$\begin{aligned} \text{MVA}_{\text{TR-B}} &= \frac{\text{MVA}_{\text{TOTAL}}}{\text{TOTAL}} \times \frac{Z_A}{Z_A + Z_B} \\ &= \frac{30 \times \sqrt{2^2 + 5^2}}{\sqrt{3.5^2 + 8.75^2}} \\ &= 17.04 \text{ MVA} \end{aligned}$$

TR-A HAS RATING 10 MVA BUT IT IS ACTUALLY TAKING 12.86 MVA. IT WILL BE OVER LOADED.

ALTHOUGH TOTAL NUMERICAL RATINGS OF TWO TRANSFORMER IN COMBINATION IS 30 MVA, THEY CAN NOT CARRY THE TOTAL LOAD 30 MVA BECAUSE THEIR DIFFERENT %. IMPEDANCE CAUSES DIFFERENT LOADING ON THEM.

$$\begin{aligned}
 MUA(TR-A) &= \frac{MUA_{(TOTAL)}}{Z_A + Z_B} \times \frac{Z_A}{Z_A + Z_B} \\
 &= \frac{30 \times \sqrt{2^2 + 5^2}}{\sqrt{3.5^2 + 8.75^2}} \\
 &= 17.04 \text{ MUA}
 \end{aligned}$$

TR-A HAS RATING 10MUA BUT IT IS ACTUALLY
TAKING 12.86 MUA. IT WILL BE OVER LOADED.

ALTHOUGH TOTAL NUMERICAL RATINGS OF TWO TRANSFORMER
IN COMBINATION IS 30MUA, THEY CAN NOT CARRY THE TOTAL
LOAD 30MUA BECAUSE THEIR DIFFERENT % IMPEDANCE CAUSES
DIFFERENT LOADING ON THEM.

RATING AND COOLING OF TRANSFORMERS

Q1

DESCRIBE THE PRINCIPLE METHODS USED TO COOL LARGE 3 ϕ TRANSFORMERS AND THE REASON FOR THEIR USE

Q2

BRIEFLY DESCRIBE THE FOLLOWING SYMBOLS AS SPECIFIED IN AS 2374 PART 2 - 1982 IN RELATION TO COOLING MEDIUM AND CIRCULATION TYPES

(i) SYMBOL FOR COOLING : O L G W A


(ii) SYMBOL FOR CIRCULATING TYPE: N F D

Q3

TRANSFORMER'S OUTPUT AND LIFE DEPEND VERY MUCH ON ITS COOLING CAPABILITY FOR THE FOLLOWING REASONS

(i) THE COPPER LOSSES IN TRANSFORMER VARIES WITH THE SOURCE OF LOAD CURRENT. EFFICIENT DISSIPATION OF HEAT CAN INCREASE THE LOAD CURRENT DELIVERED BY TRANSFORMER

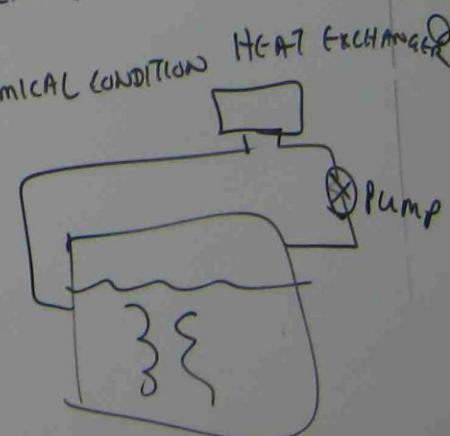(ii) THE LIFE OF TRANSFORMER IS DEPENDENT ON CHEMICAL CONDITION OF COOLING OIL AND WINDING INSULATION. THE COOLER TRANSFORMER HAS LONGER LIFE.



(i) COOLING

Q2

O - MINERAL OIL | EQUIVALENT INSULATING OIL

L - NON FLAMMABLE SYNTHETIC INSULATING
LIQUID

G - GAS

W - WATER

A - AIR


(ii) CIRCULATION

N - NATURAL

F - FORCED OIL (NOT DIRECTED)

D - FORCED OIL (DIRECTED)

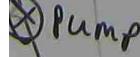EXCHANGER 3 - DESCRIBE THE ARRANGEMENT OF SYMBOLS USED IN
COOLING METHODS



1 st LETTER	2 nd LETTER	3 rd LETTER	4 th LETTER
COOLING MEDIUM WHICH IS IN CONTACT WITH TRANSFORMER WINDINGS		COOLING MEDIUM WHICH IS IN CONTACT WITH EXTERNAL COOLING SYSTEM	
KIND OF COOLING MEDIUM	KIND OF CIRCULATION	KIND OF COOLING MEDIUM	