

Goal


APPLICATION OF MAGNETISM

POWER TRANSFORMER PRINCIPLE


ELECTRICAL MACHINE
|
STATIC DYNAMIC

CHANGE VOLTAGE / CURRENT LEVEL — magnetic flux passes through coil \rightarrow induced voltage

ROTATIONAL FORCE

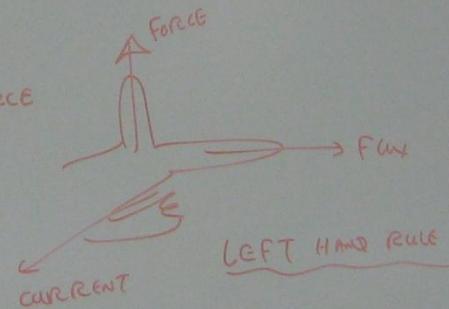

AC / DC MOTORS

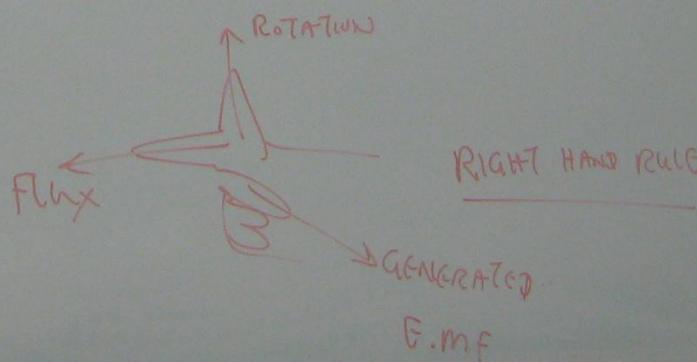

AC / DC GENERATOR

P.C. SOURCE

at coil \rightarrow INDUCED VOLTAGE

$$V = L \frac{di}{dt} = N_1 \frac{d\phi}{dt}$$


NO. OF TURNS RATE OF CHANGE OF
MAGNETIC FLUX

NO. OF TURNS DETERMINE THE VOLTAGE

TRANSFORMER

MOTORS

CONSTRUCTION OF TRANSFORMER

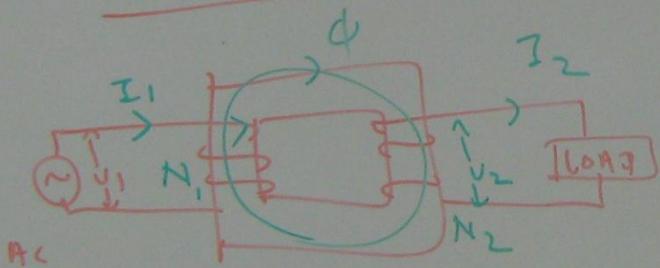

$$\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1} = a$$

TURN RATIO

WHEN PRIMARY WINDING OF TRANSFORMER IS CONNECTED TO AC SUPPLY, THE FLOW OF CURRENT PRODUCES THE MAGNETIC FLUX.

THE FLUX IS LINKED TO SECONDARY WINDING AND VOLTAGE IS INDUCED.

THE INDUCED VOLTAGE DEPENDS ON NUMBER OF

TURNS AND RATE OF CHANGE OF FLUX

$$E_1 = 4.44 f N_1 \phi_{\max} \text{ VOLT}$$

E_1 = PRIMARY VOLTAGE / ph

N_1 = PRIMARY NO. OF TURNS

f = FREQUENCY

ϕ_{\max} = FLUX (wb)

$$E_2 = 4.44 f N_2 \phi_{\max}$$

Prb ① $N_p = 350$ TURNS, $E_p = 2200$ V rms

$f = 50$ Hz, $C.S.A = 250 \text{ cm}^2$

CALCULATE MAXIMUM FLUX DENSITY
OF CORE.

$$E_p = 4.44 f N_p \phi_{\max}$$


$$2200 = 4.44 \times 50 \times 350 \times \phi_{\max}$$

$$\phi_{\max} = \frac{2200}{4.44 \times 50 \times 350} = 0.0276 \text{ wb}$$

$$B_{\max} = \frac{\phi_{\max}}{A} = \frac{0.0276}{250 \times (10^{-4})^2} = \frac{0.0276}{250 \times 10^{-4}}$$


$$= \frac{0.0276 \times 10^4}{250}$$

$$= 1.1 \text{ TESLA}$$

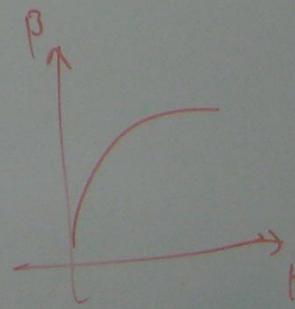

Flux
Density

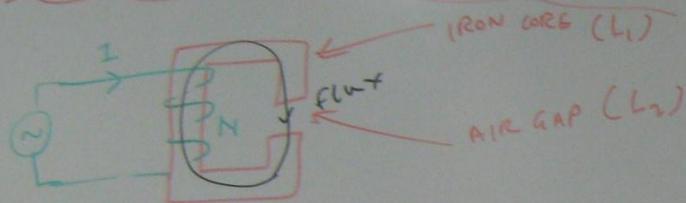CALCULATION OF MAGNETIZING FORCE IN MAGNETIC CORE



$$\begin{aligned} \text{MAGNETO force} &= \text{CURRENT} \times \text{NO. OF TURNS} \\ &= I \times N \\ &= NI \end{aligned}$$

$$NI = H \times l$$

↑ ↓
 MAGNETIZING LENGTH
 FORCE OF
 AMP-TURNS MAGNETIC
 / m PATH
 (m)

$$\beta = \mu H$$

Flux ↓
 DENSITY PERMEABILITY
 ↓ ↓
 MAGNETIZING FORCE

$$H = \frac{\beta}{\mu}$$

$$H = \frac{\beta}{\mu_0 \mu_r}$$

$$\mu = \mu_0 \times \mu_r$$


$\mu_0 = 4\pi \times 10^{-7}$ (PERMEABILITY OF AIR)

μ_r = RELATIVE PERMEABILITY

$$NI = \frac{H}{\text{IRON}} \times L_{\text{IRON}} + \frac{H}{\text{AIRCAP}} \times L_{\text{AIRCAP}}$$

$$NI = \frac{\beta}{\mu_0 \mu_r} \times L_1 + \frac{\beta}{\mu_0} \times L_2$$

Ph ②

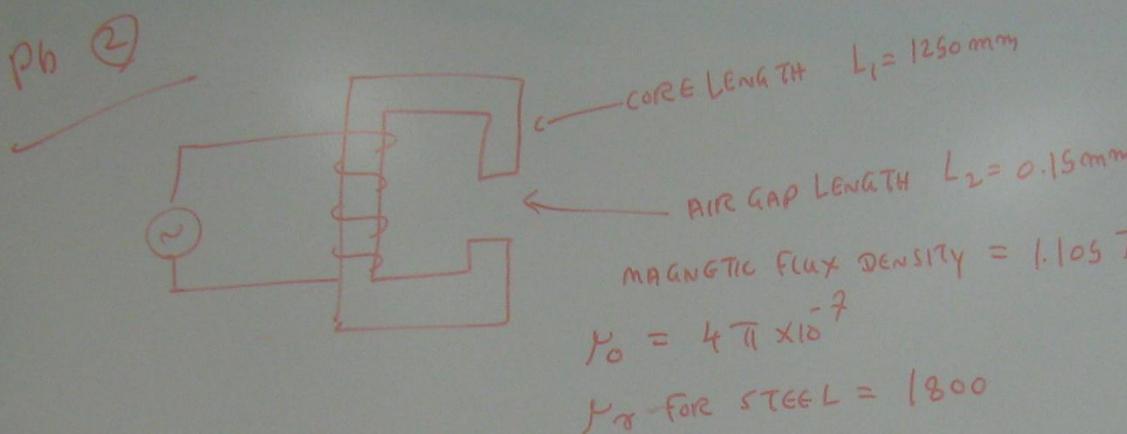

CALCULATE TOTAL MAGNETIZING FORCE.

IF NO. OF TURNS ON CORE IS 350 TURNS, CALCULATE

I_{max} AND I_{rms} FOR THE COIL.

TOTAL MAGNETIZING FORCE = IRON CORE + AIR GAP

$$= \frac{H_I}{I} \times L_I + \frac{H_A}{A} L_A$$

=

$$= \frac{\beta}{\mu_0 4\pi}$$

$$= \frac{1.105}{4\pi \times 10^{-7} \times 180}$$

$$\rightarrow 625$$

$$= 75$$

$$NI =$$

$$350 \times I_{max} =$$

$$I =$$

$$I_{rms} =$$

CORE LENGTH $L_1 = 1250 \text{ mm}$

AIR GAP LENGTH $L_2 = 0.15 \text{ mm}$

MAGNETIC FLUX DENSITY = 1.105 T
 $= 4\pi \times 10^{-7} \times 1800$

FOR STEEL = 1800

ING FORCE.

E IS 350 TURNS, CALCULATE
FOR THE COIL.

ORG + AIR GAP

$L_I + H_A L_A$

$$= \frac{\beta}{\mu_0 4\pi} \times L_1 + \frac{\beta}{\mu_0} L_2$$

$$= \frac{1.105}{4\pi \times 10^{-7} \times 1800} \times \frac{1250}{1000} + \frac{1.105}{4\pi \times 10^{-7}} \times \frac{0.15}{1000}$$

$$\rightarrow 625 + 131.9$$

$$= 756.9 \text{ Amp-turn}$$

$$N I = 756.9$$

$$350 \times I_{\text{max}} = 756.9$$

$$I_{\text{max}} = \frac{756.9}{350}$$

$$= 2.16 \text{ Amp}$$

$$I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}} = \frac{2.16}{1.4142} = 1.53 \text{ Amp}$$

VOLTAGE RATED
RMS VALUE OF
CONTINUOUS THAT
APPLIED TO WIND

$$E = 4.44 f N$$

$$f = \text{FREQ}$$

$$N = \text{NO}$$

$$E = \text{VOL}$$

RATING OF TRANSFORMER

$$\times \frac{0.15}{1000}$$

VOLTAGE RATING

RMS VALUE OF HIGHEST
CONTINUOUS THAT CAN BE
APPLIED TO WINDING

$$E = 4.44 f N \phi$$

↑
FLUX (wb)

f = FREQUENCY
(Hz)

N = NO. OF TURNS.

E = VOLTAGE

CURRENT RATING

RMS VALUE OF HIGHEST
CONTINUOUS CURRENT
THAT CAN BE APPLIED
WITHOUT CAUSING
EXCESSIVE TEMPERATURE
RISE

$$I^2 R = \text{COPPER LOSS}$$

WINDING RESISTANCE

V.A RATING (POWER RATING)

NOMINAL VOLTAGE × NOMINAL CURRENT

$$\text{LOAD RATIO} = \frac{\text{V.A AT ANY LOAD}}{\text{RATED V.A}}$$

$$\text{V.A AT ANY LOAD} = \frac{\text{LOAD RATIO} \times \text{RATED V.A}}{(L)}$$

$$\text{WATT AT ANY LOAD} = L \times \text{RATED V.A} \times \text{POWER FACTOR}$$

G of Transformer

CURRENT RATING
RMS VALUE OF HIGHEST
CONTINUOUS CURRENT
THAT CAN BE APPLIED
WITHOUT CAUSING
EXCESSIVE TEMPERATURE
RISE

$$I_R = \frac{\text{COPPER}}{\text{WINDING RESISTANCE}}$$

U.A RATING (POWER RATING)
NOMINAL VOLTAGE \times NOMINAL CURRENT

$$\text{LOAD RATIO} = \frac{\text{U.A AT ANY LOAD}}{\text{RATED U.A}}$$

$$\text{U.A AT ANY LOAD} = \frac{\text{LOAD RATIO} \times \text{RATED U.A}}{(L)}$$

$$\text{WATT AT ANY LOAD} = L \times \text{RATED U.A} \times \text{POWER FACTOR}$$

Pb3 FIND PRIMARY AND SECONDARY CURRENT OF
4 KVA 400/200 V 1Ø TRANSFORMER

$$V_p I_p = V_s I_s = \text{RATED U.A}$$

$$400 I_p = \text{RATED U.A}$$

$$400 I_p = 4000$$

$$I_p = \frac{4000}{400} = 10 \text{ Amp}$$



$$V_s I_s = 4000$$

$$200 I_s = 4000$$

$$I_s = \frac{4000}{200}$$

$$= 20 \text{ Amp}$$

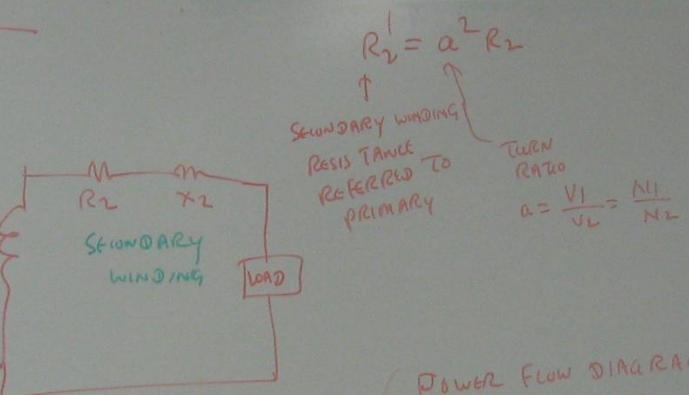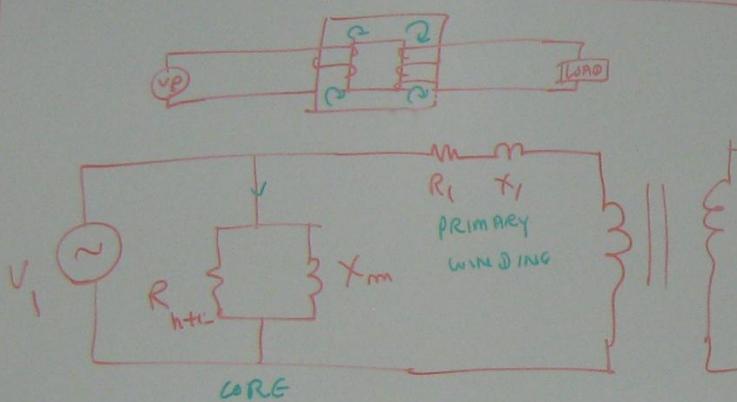LOSSES IN TRANSFORMER & EQUIVALENT CIRCUIT



$$R_e = \text{TOTAL EQUIVALENT RESISTANCE REFERRED TO PRIMARY}$$

$$X_e = \text{TOTAL EQUIVALENT REACTANCE REFERRED TO PRIMARY}$$


$$Z_e = \text{TOTAL EQUIVALENT IMPEDANCE REFERRED TO PRIMARY}$$

$$R_e' = R_1 + a^2 R_2$$


$$X_e' = X_1 + a^2 X_2$$

$$Z_e' = \sqrt{(R_e')^2 + (X_e')^2}$$

(POWER FLOW DIAGRAM OF TRANSFORMER)

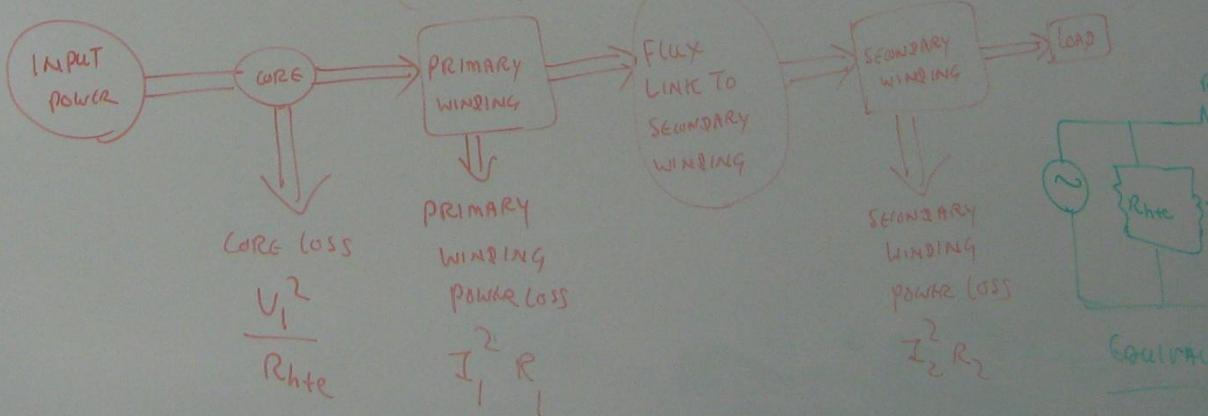

EQUIVALENT CIRCUIT

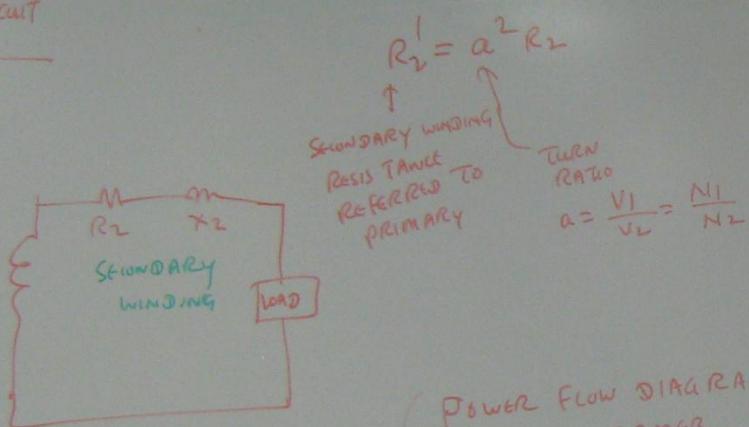

$$X_2' = a^2 X_2$$

SECONDARY WINDING
REACTANCE REFERRED TO PRIMARY

R_e' = TOTAL EQUIVALENT
RESISTANCE REFERRED TO PRIMARY

X_e' = TOTAL EQUIVALENT
REACTANCE REFERRED TO PRIMARY



Z_e' = TOTAL EQUIVALENT
IMPEDANCE REFERRED TO PRIMARY


$$R_e' = R_1 + a^2 R_2$$

$$X_e' = X_1 + a^2 X_2$$

$$Z_e' = \sqrt{(R_e')^2 + (X_e')^2}$$

(POWER FLOW DIAGRAM OF)
TRANSFORMER

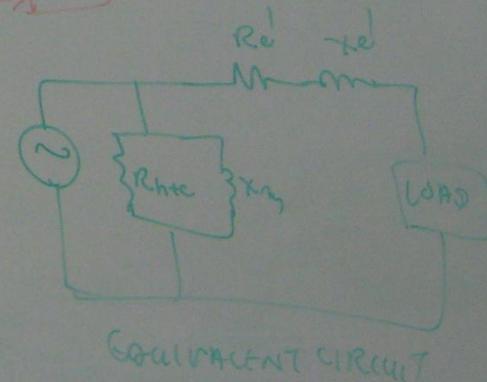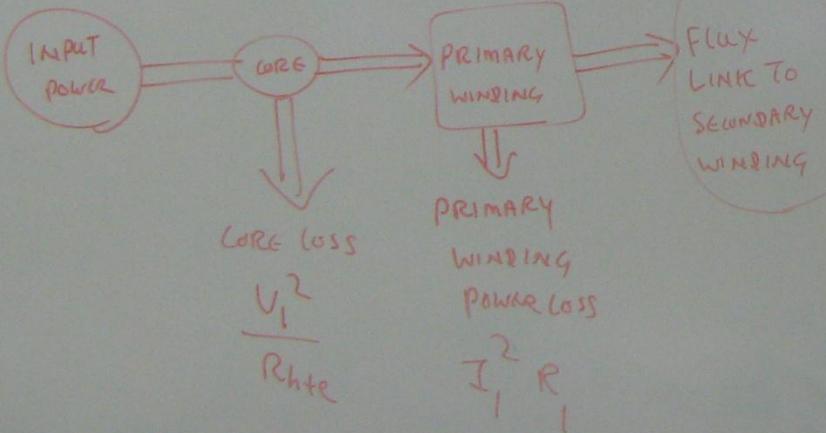

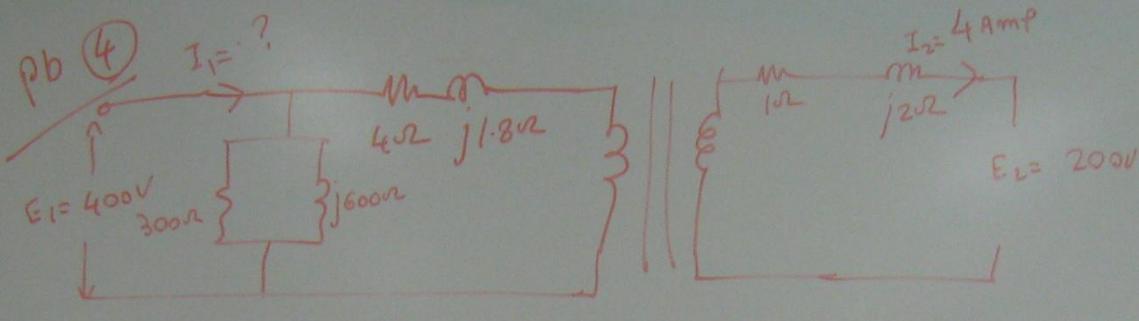

IN ABOVE CIRCUIT, CALCULATE

- (i) SECONDARY RESISTANCE REFERRED TO PRIMARY
- (ii) SECONDARY INDUCTIVE REACTANCE REFERRED TO PRIMARY
- (iii) TOTAL EQUIVALENT RESISTANCE REFERRED TO PRIMARY
- (iv) TOTAL EQUIVALENT INDUCTIVE REACTANCE REFERRED TO PRIMARY
- (v) PRIMARY CURRENT
- (vi) DRAW A SIMPLIFIED EQUIVALENT CIRCUIT DIAGRAM.

$$(i) R_2' = 1.8 \Omega$$

$$R_2' = ?$$


$$R_2' = a^2 R_2 =$$

$$(ii) X_2' = ?$$

$$(iii) R_e' = ?$$

$$(iv) X_c' = Y$$

$$(v) \frac{V_1}{V_2}$$

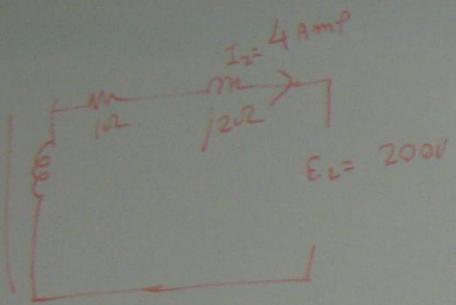

+ T.F.
 -
 REFLUX REFERRED TO PRIMARY
 LEAKAGE REFERRED TO PRIMARY
 INDUCTIVE REACTANCE REFERRED TO
 PRIMARY
 CAPACITIVE REACTANCE REFERRED TO
 PRIMARY

EQ EQUIVALENT CIRCUIT

$$(i) R_2' = 1\Omega$$

$$R_2' = ?$$

$$a = \frac{E_1}{E_2} = \frac{400}{200} = 2$$

$$R_2' = a^2 R_2 = 2^2 \times 1 = 4\Omega$$

$$(ii) X_2' = a^2 x_2 = 2^2 \times 2 = 8\Omega$$



$$(iii) R_e' = R_1 + a^2 R_2 = 4 + 4 = 8\Omega$$

$$(iv) X_C' = x_1 + a^2 x_2 = 1.8 + 2^2 \times 2 =$$



$$= 1.8 + 8 = 9.8\Omega$$

$$(v) \frac{V_1}{V_2} = a = \frac{I_2}{I_1}$$
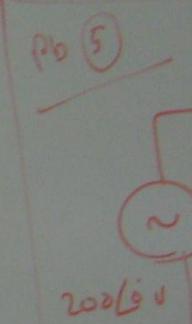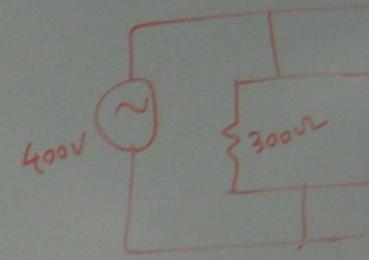
$$2 = \frac{4}{I_1} \Rightarrow I_1 = \frac{4}{2} = 2Amp$$



CALC

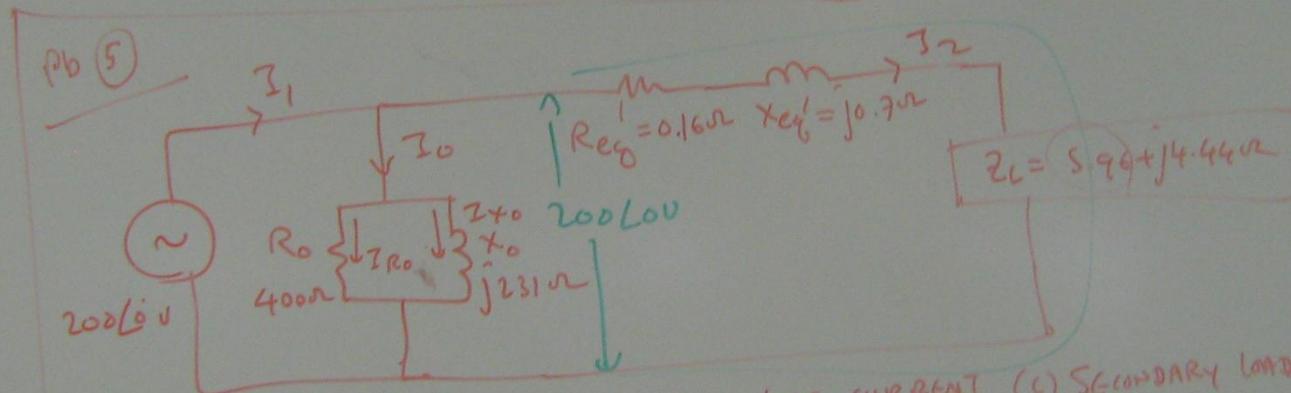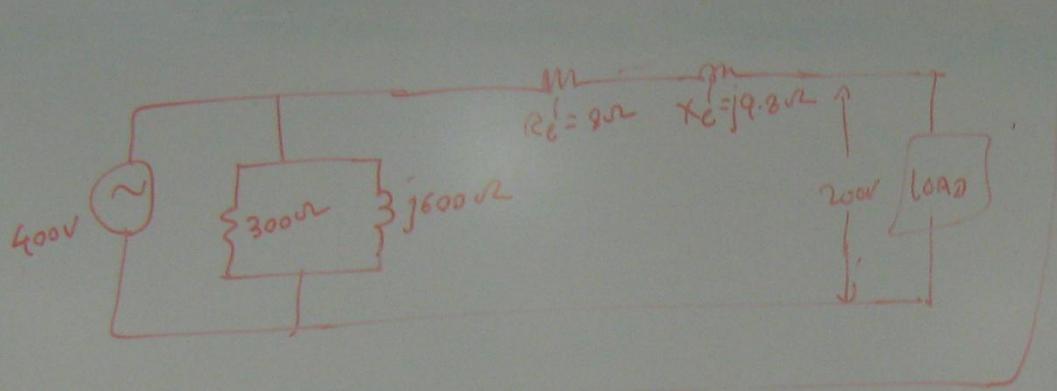

- CALCULATE
- (a) IRON LOSS
 - (b) NO LOAD CURRENT
 - (c) SECONDARY LOAD CURRENT
 - (d) TOTAL PRIMARY CURRENT
 - (e) COPPER LOSS
 - (f) POWER CONSUMED BY LOAD
 - (g) EFFICIENCY OF GUGN CIRCUIT.

$$\frac{4}{2} = 2 \text{ Amp}$$

$$(a) \text{ IRON Loss} = \frac{V_1^2}{R_O} = \frac{200^2}{400} = \frac{200 \times 200}{400} = 100 \text{ W}$$

$$\begin{aligned}(b) I_O &= I_{R_O} + I_{X_O} \\ &= \frac{200}{400} + \frac{200}{j231} \\ &= 0.5 + \frac{0.86}{j}\end{aligned}$$

$$\begin{aligned}j &= \sqrt{-1} \\ &= 0.5 + \frac{0.86}{j} \times \frac{j}{j} \\ &= 0.5 + \frac{j0.86}{(j)^2} \\ &= 0.5 + j0.86\end{aligned}$$

$$I_O = 0.5 - j0.86$$

$$\begin{aligned}I_O &= \sqrt{0.5^2 + 0.86^2} \quad \left[\tan^{-1} \frac{0.86}{0.5} \right] \\ &= 1 \quad \left[-59.8^\circ \right] \text{ Amp.}\end{aligned}$$

$$(c) I_2 = \frac{200 \angle 0^\circ}{0.12 + j0.7 + 5.96 + j4.44}$$

$$= \frac{200 \angle 0^\circ}{6.12 + j5.14}$$

$$= \frac{200 \angle 0^\circ}{\sqrt{6.12^2 + 5.14^2}} \quad \left[\tan^{-1} \frac{5.14}{6.12} \right]$$

$$= \frac{200 \angle 0^\circ}{7.9} \quad \left[39.2^\circ \right] = 25.3 \quad \boxed{-39.2 \text{ A}}$$

$$(d) I_1 = I$$

(e)

$$(d) I_1 = I_o + I_2$$

$$= 0.5 - j0.86 + 25.3 \angle -39.2^\circ$$

$$= 0.5 - j0.86 + 25.3 (\cos 39.2^\circ - j \sin 39.2^\circ)$$

$$= 0.5 - j0.86 + 19.6 - j16$$

$$= 20.1 - j16.86$$

$$= \sqrt{20.1^2 + 16.86^2} \angle -\tan^{-1} \frac{16.86}{20.1}$$

$$= 26.2 \angle -40^\circ \text{ Amp}$$

$$(e) \text{ copper loss} = I_2^2 R_{\text{reg}} =$$

$$= (25.3)^2 \times 0.16$$

$$= 102.4 \text{ WATT}$$

(f)

$$\text{power consumed by load} = I_2^2 R_L$$

$$= 25.3^2 \times 5.96$$

$$= 3815 \text{ WATT}$$

$$(g) \text{ input power} = \text{load power} + (\text{iron loss} + \text{copper loss})$$

$$= 3815 + 100 + 102.4$$

$$= 4017.4 \text{ W}$$

$$\text{Efficiency} = \frac{\text{output}}{\text{input}} \times 100 = \frac{3815}{4017.4} \times 100$$

$$= 95\%$$