

ph

500 KVA 3Ø TRANSFORMER. VOLTAGE RATIO 6600 / 440V. IRON LOSS = 2.9 kW.

FULL LOAD COPPER LOSS = 4 kW.

FIND % EFFICIENCY AT (a) FULL LOAD 0.6 PF LAGGING

(b) $\frac{1}{2}$ LOAD 0.8 PF LAGGING

(c) $\frac{1}{4}$ LOAD 0.7 PF LAGGING

$$\text{TRANSFORMER \% EFFICIENCY} = \frac{\text{LOAD RATIO} \times \text{RATED V.A} \times \text{PF (output)}}{\text{LOAD RATIO} \times \text{RATED V.A} \times \text{PF} + \text{IRON LOSS} + (\text{LOAD RATIO})^2 \times \text{FULL LOAD COPPER LOSS}}$$

IN PUT

(a) FULL LOAD 0.6 PF LAGGING

$$\text{OUTPUT} = \text{LOAD RATIO} \times \text{RATED V.A} \times \text{PF}$$

$$= 1 \times 500 \text{ KVA} \times 0.6 = 300 \text{ kW}$$

$$\text{IRON LOSS} = 2.9 \text{ kW}$$

$$\text{COPPER LOSS} = I^2 \times \text{Full Load Copper Loss} = 1^2 \times 4 \text{ kW} = 4 \text{ kW}$$

$$\begin{aligned}\% \text{ EFFICIENCY} &= \frac{300}{300 + 2.9 + 4} \times 100 \\ &= \frac{300}{306.9} \times 100 \\ &\approx 97.75\%\end{aligned}$$

$$(b) \text{ Output} = \frac{1}{2} \times 500 \text{ kW} \times 0.8 = 200 \text{ kW}$$

$$\text{IRON loss} = 2.9 \text{ kW}$$

$$\begin{aligned} \text{COPPER loss} &= L^2 \times \text{Full load copper loss} \\ &= \left(\frac{1}{2}\right)^2 \times 4 = 1 \text{ kW} \end{aligned}$$

$$\% \text{ EFFICIENCY} = \frac{87.5}{87.5 + 2.9 + 0.25} \times 100$$

$$= \frac{87.5 \times 100}{90.65} \\ = 96.5\%$$

$$\begin{aligned} \% \text{ EFFICIENCY} &= \frac{200}{200 + 2.9 + 1} \times 100 \\ &= \frac{200}{203.9} \times 100 \\ &= 98.08\% \end{aligned}$$


$$(c) \text{ Output} = \frac{1}{4} \times 500 \times 0.7 = 87.5 \text{ kW}$$

$$\text{IRON loss} = 2.9 \text{ kW}$$

$$\text{COPPER loss} = \left(\frac{1}{4}\right)^2 \times 4 = 0.25 \text{ kW}$$


TRANSFORMER % REGULATION
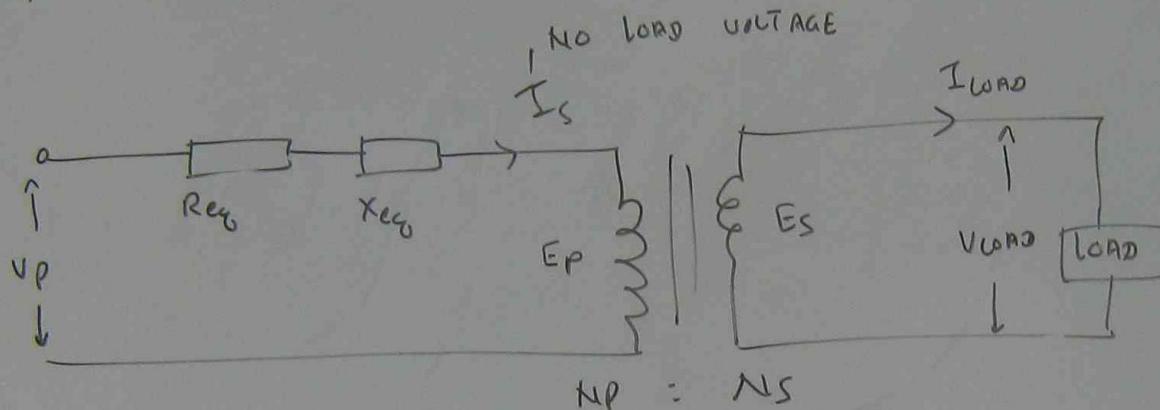
$$\% \text{ REGULATION} = \frac{\text{NO LOAD VOLTAGE} - \text{FULL LOAD VOLTAGE}}{\text{NO LOAD VOLTAGE}} \times 100$$



$$E_p = \frac{N_p}{N_s} \times V_{LOAD}$$

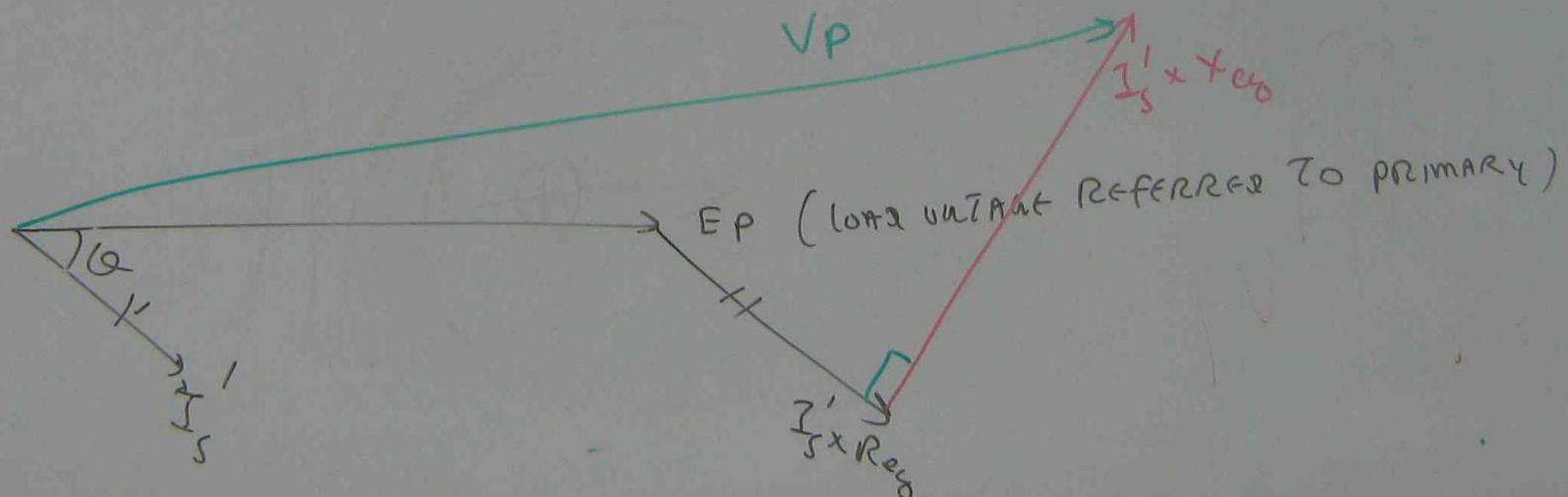N_p = PRIMARY TURNS
 N_s = SECONDARY TURNS.



LAGGING P.F


% REGULATION =

$$\frac{I_s \left(R_{eq} \cos\theta + X_{eq} \sin\theta \right)}{V_p} \times 100$$

LEADING P.F



% REGULATION =
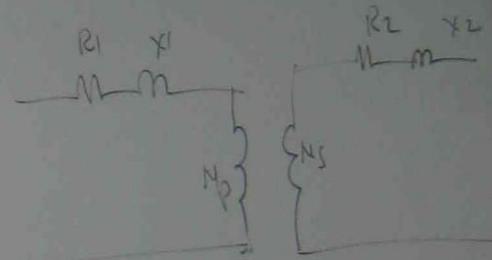
$$\frac{I_s \left(R_{eq} \cos\theta - X_{eq} \sin\theta \right)}{V_p} \times 100$$



$$R_{eq} = R_1 + \left(\frac{N_p}{N_s} \right)^2 R_2$$
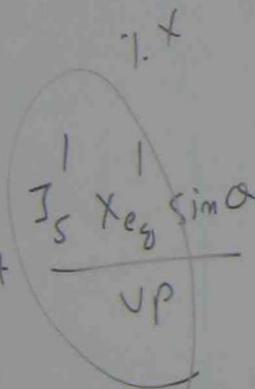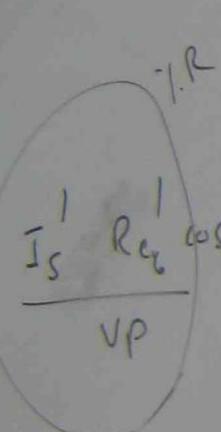
$$X_{eq} = X_1 + \left(\frac{N_p}{N_s} \right)^2 X_2$$



$$\frac{I_s \left(R_{eq} \cos\theta + X_{eq} \sin\theta \right)}{V_p} \times 100 = \% R \cos\theta + \% X \sin\theta \quad \leftarrow \text{LAGGING PF} = \% \text{ REGULATION}$$

$$\frac{I_s \left(R_{eq} \cos\theta - X_{eq} \sin\theta \right)}{V_p} \times 100 = \% R \cos\theta - \% X \sin\theta \quad \leftarrow \text{LEADING PF} = \% \text{ REGULATION}$$

ph

100 KVA, 34 TRANSFORMER. $N_p = 400$, $N_s = 80$, $R_p = 0.3 \Omega$, $R_s = 0.01 \Omega$

$X_p = 1.1 \Omega$, $X_s = 0.035 \Omega$, $V_p = 2200 \text{ V}$, $V_s = 440 \text{ V}$.

$$X_L = 2 \pi f L$$

FIND (a) $Z_{eq}^1 = ?$ (b) $V_s^1 = ?$ (c) 1. REGULATION FOR 0.8 PF LAGGING A SECONDARY TERMINAL VOLTAGE.
(d) 1. REGULATION FOR 0.8 PF LEADING A SECONDARY TERMINAL VOLTAGE.


$$\frac{N_p}{N_s} = \frac{V_1}{V_2} = a = \frac{I_2}{I_1}$$

TURN
RATIO

$$R_{eq}^1 = R_1 + \left(\frac{N_p}{N_s} \right)^2 \times R_s = 0.3 + \left(\frac{V_1}{V_2} \right)^2 \times 0.01 = 0.3 + \left(\frac{2200}{440} \right)^2 \times 0.01$$

$$= 0.3 + 25 \times 0.01 = 0.55 \Omega$$
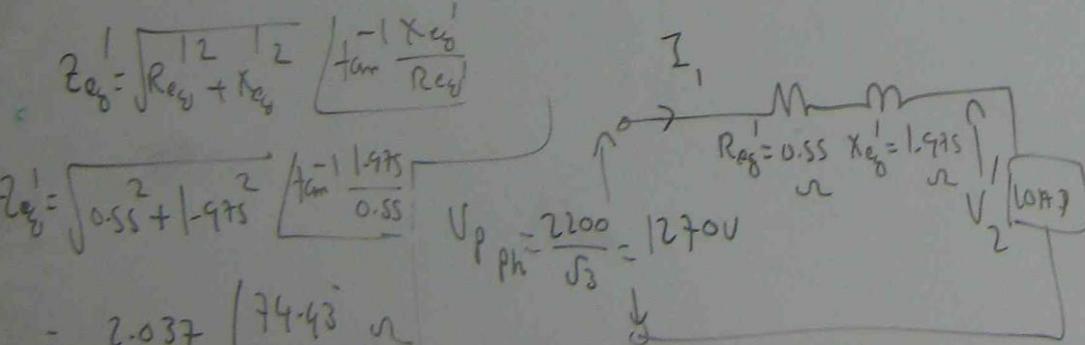
$$X_{eq}^1 = X_1 + \left(\frac{N_p}{N_s} \right)^2 \times X_s = 1.1 + \left(\frac{2200}{440} \right)^2 \times 0.035 = 1.1 + 25 \times 0.035 = 1.975 \Omega$$



$$I_1 = \frac{\text{KVA} \times 10^3}{\sqrt{3} \times V_p} = \frac{100 \times 10^3}{\sqrt{3} \times 2200}$$

$$= 26.24 \text{ Amp.}$$

0.8 PF LAGGING

$$\cos \phi = 0.8 \rightarrow \phi = \cos^{-1} 0.8 = 36.8^\circ$$

$$\text{LAGGING} \Rightarrow 26.24 \quad [-36.8^\circ]$$

10 $VA = V \times I$

34 $V = \sqrt{V^2 - I^2 R^2}$

$2\pi f L$

$$V_p = V_2^1 + I_1 Z_{eq}$$

$$1270 = V_2^1 + 26.24 \angle -36.8^\circ \times 2.037 \angle 74.43^\circ$$

$$1270 = V_2^1 + 53.4 \angle 74.43^\circ + (-36.8^\circ)$$

$$1270 = V_2^1 + 53.4 \angle 37.63^\circ$$

$$V_2^1 = 1270 - 53.4 \angle 37.63^\circ$$

$$= 1270 - (53.4 \cos 37.63^\circ + j 53.4 \sin 37.63^\circ)$$

$$= 1270 - (42.29 + j 32.6)$$

$$= 1270 - 42.29 - j 32.6$$

$$= 1227.71 - j 32.6$$

$$= \sqrt{1227.71^2 + 32.6^2} \angle -\tan^{-1} \frac{32.6}{1227.71}$$


$$= 1228.14 \angle -1.43^\circ \text{ V}$$

$$\sqrt{3} \times 1228.14 = 2127.6 \text{ V}$$

$$\% \text{ REG} = \frac{V_1 - V_2}{V_1} \times 100$$

$$= \frac{2200 - 2127.6}{2200} \times 100$$

$$= 3.29 \%$$

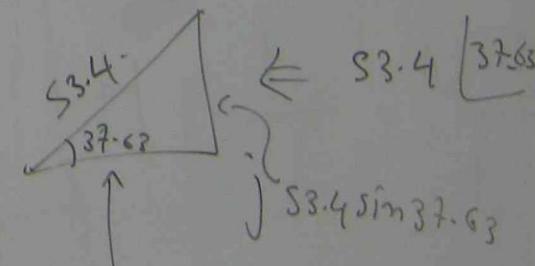

$$S3.4 \cos 37.63^\circ$$

$$8.14 = 2127.6$$

V

$\times 100$

$$127.6 \quad \times 100$$

$$53.4 \quad [37.63]$$

$$45\sin 37.63$$

(b) 0.8 pF LEADING

$$I = 26.24 \quad [36.8] \text{ Amp}$$

$$V_p = V_2 + I_C Z_{C8}$$

$$1270 = V_2 + 26.24 \quad [36.8] \times 2.037 \quad [74.43]$$

$$1270 = V_2 + 53.4 \quad [111.23]$$

$$V_2 = 1270 - 53.4 \quad [111.23]$$

$$= 1270 - 53.4 (\cos 111.23 + j \sin 111.23)$$

$$= 1270 - 53.4 (-0.362 + j0.932)$$

$$= 1270 + 19.33 - j49.76$$

$$= 1289.33 - j49.76$$

$$V_2 = \sqrt{1289}$$

= 1290

% RGA =

=

$$U_2 = \sqrt{1289.33^2 + 49.36^2} \quad \boxed{-\tan^{-1} \frac{49.36}{1289.33}}$$


$$= 1290.2 \quad \boxed{-2.2} \quad \checkmark \quad \rightarrow U_2 \text{ LINE} = \sqrt{3} \times 1290.2 =$$

$$\% \text{ REGA} = \frac{U_1 - U_2}{U_1} \times 100$$


$$= \frac{1270 - 1290.2}{1270} \times 100$$

$$= -1.59 \%$$

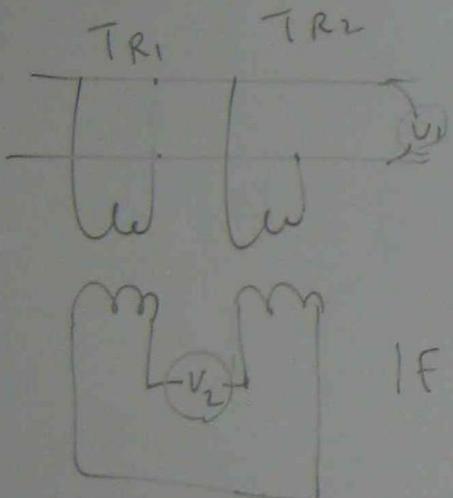TRANSFORMER PARALLEL OPERATION AND SHARING OF LOAD
BETWEEN PARALLEL CONNECTED TRANSFORMERS




IF $V_2 \approx 0$ THEN CONNECT

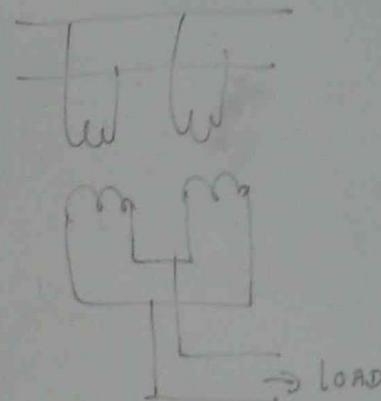


TR A LOAD =

TR B LOAD =

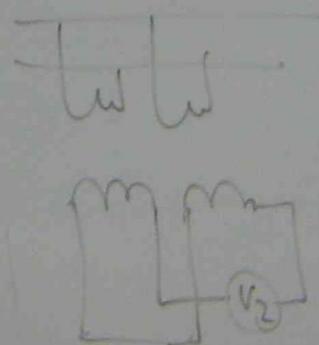
IF $V_2 = \text{LNG VOLTAGE}$ \rightarrow CHANGE CONNECTION




IF $V_2 \approx 0 \rightarrow$

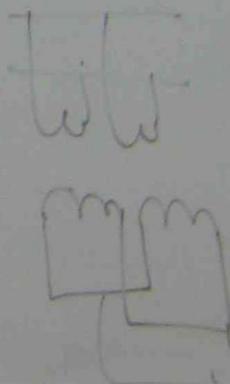

BOOTH TRANSFORMERS
HAVE SAME RATING

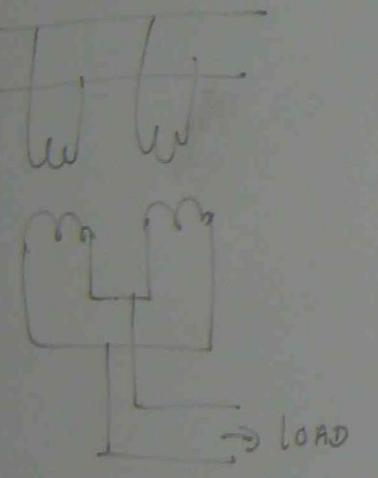

BOOTH TRANSFORMERS
HAVE SAME RATING

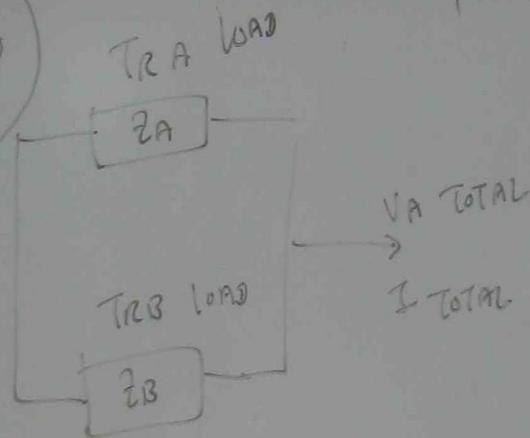

$$TR_A \text{ LOAD} = VA_{\text{TOTAL}} \times \frac{Z_B}{Z_A + Z_B}$$

$$TR_B \text{ LOAD} = VA_{\text{TOTAL}} \times \frac{Z_A}{Z_A + Z_B}$$

TRANSFORMERS HAVE DIFF

SELECT BASE V.

TR_A IMPEDANCE
REFERRED TO B
V.A


TR_B IMPEDANCE
REFERRED TO B
V.A

$$TR_A \text{ LOAD} = VA$$

$$TR_B \text{ LOAD} = VA$$

IF $V_2 \approx 0 \rightarrow$

Both Transformers
have same ratings

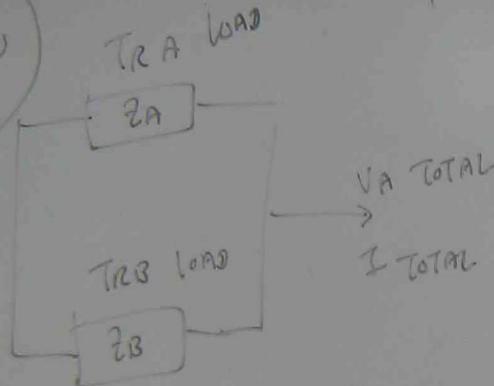

$$TRA \text{ LOAD} = VA \text{ TOTAL} \times \frac{Z_A}{Z_A + Z_B}$$

$$TRB \text{ LOAD} = VA \text{ TOTAL} \times \frac{Z_B}{Z_A + Z_B}$$

Transformers have different ratings

Select Base V.A

TRA Impedance

REFERRED TO BASE

$$Z_A' = Z_A \times \frac{\text{BASE V.A}}{\text{TRA V.A}}$$

V.A

TRB Impedance


REFERRED TO BASE

$$Z_B' = Z_B \times \frac{\text{BASE V.A}}{\text{TRB V.A}}$$

V.A

$$TRA \text{ LOAD} = VA \text{ TOTAL} \times \frac{Z_B'}{Z_A' + Z_B'}$$
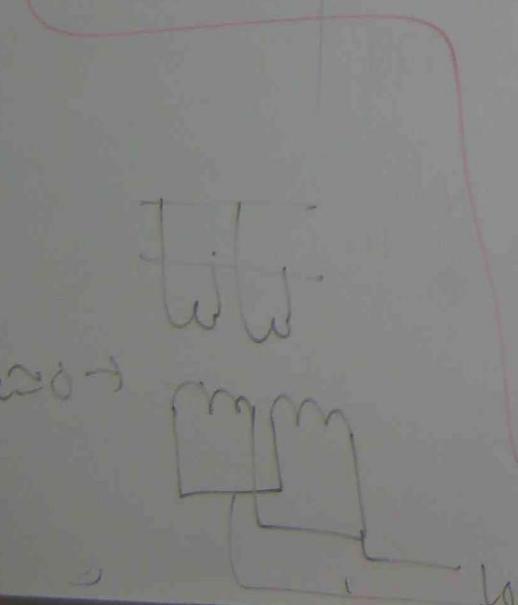
$$TRB \text{ LOAD} = VA \text{ TOTAL} \times \frac{Z_A'}{Z_A' + Z_B'}$$



PB ①

500 KW LOAD PF 0.85 LAGGING IS SUPPLIED BY
 TWO TRANSFORMERS CONNECTED IN PARALLEL.

TR A - 800 KVA

$$Z_A = 3 + j 5 \Omega$$

TR B - 800 KVA

$$Z_B = 2 + j 4 \Omega$$

FIND LOAD SHARE OF EACH TRANSFORMER

PB ②

1000 KW LOAD, PF 0.9 LAGGING IS SUPPLIED BY
 TWO TRANSFORMERS CONNECTED IN PARALLEL.

TR A - 1000 KVA

$$Z = 4 + j 6 \Omega$$

TR B - 500 KVA

$$Z = 3 + j 2 \Omega$$

FIND LOAD ON EACH TRANSFORMER

$$\text{Ph1} \quad V.A = \frac{\text{WATT}}{\text{P.F}} \quad \leftrightarrow \quad \text{WATT} = V.A \times \text{P.F}$$

$$V.A_{\text{TOTAL}} = \frac{500}{0.85} = 588.2 \text{ kVA}$$

P.F = cosθ

SAME RATING

$$\text{TRA load} = V.A_{\text{TOTAL}} \times \frac{Z_B}{Z_A + Z_B}$$

Ph2

$$= 588.2 \times \frac{2 + j4}{3 + j5 + 2 + j4}$$

$$= 588.2 \times \frac{2 + j4}{5 + j9}$$

$$= 588.2 \times \frac{\sqrt{2^2 + 4^2}}{\sqrt{5^2 + 9^2}}$$

$$= 588.2 \times \frac{4.47}{10.29} = 255.5 \text{ kVA}$$

$$\text{TR}_B \text{ load} = V.A_{\text{TOTAL}} \times \frac{Z_A}{Z_A + Z_B}$$

$$= 588.2 \times \frac{3 + j5}{10.29} = 588.2 \times \frac{\sqrt{3^2 + 5^2}}{10.29} = \frac{588.2 \times 5.83}{10.29} = 333.3 \text{ kVA}$$

TRA load

TR

VAR

$$PF = \cos \theta$$

$$VA_{TOTAL} = \frac{1000}{0.9} = 1111 \text{ kVA}$$

SELECT BASE U.A = 1000 kVA

Ph2

$$\therefore Z_A = Z_A \times \frac{\text{BASE U.A}}{\text{TRA U.A}} = (4+j6) \times \frac{1000}{1000} = 4+j6$$

$$Z_B = Z_B \times \frac{\text{BASE U.A}}{\text{TRA U.A}} = (3+j2) \times \frac{1000}{1000} = 3+j2$$

$$\text{TRA Loss} = V_{A\text{ TOTAL}} \times \frac{Z_B}{Z_A + Z_B} = 1111 \times \frac{6+j4}{4+j6+6+j4} = 1111 \times \frac{\sqrt{6^2+4^2}}{10+j10}$$

$$= 1111 \times \frac{\sqrt{6^2+4^2}}{\sqrt{10^2+10^2}} = \frac{1111 \times 7.21}{14.14} = 566.55 \text{ kVA}$$

$$\text{TR B Loss} = V_{A\text{ TOTAL}} \times \frac{Z_A}{Z_A + Z_B} = 1111 \times \frac{4+j6}{14.14} = 1111 \times \frac{\sqrt{4^2+6^2}}{14.14}$$

$$= \frac{1111 \times 7.21}{14.14} = 566.55 \text{ kVA} \quad \times$$

3kVA