
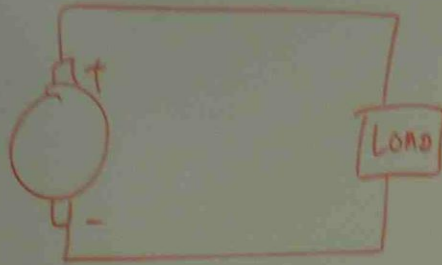



COMPARING power systems

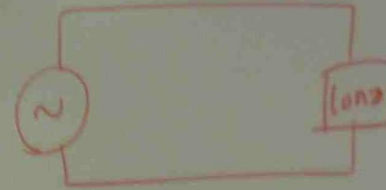


2 wires DC system



1 ϕ AC system

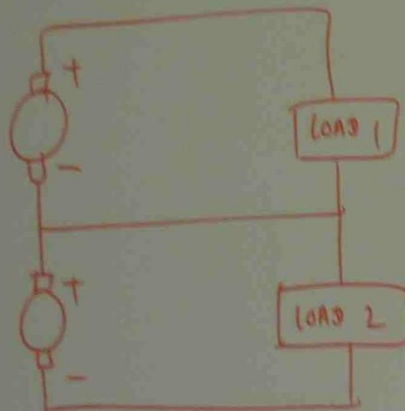


3 wires DC system

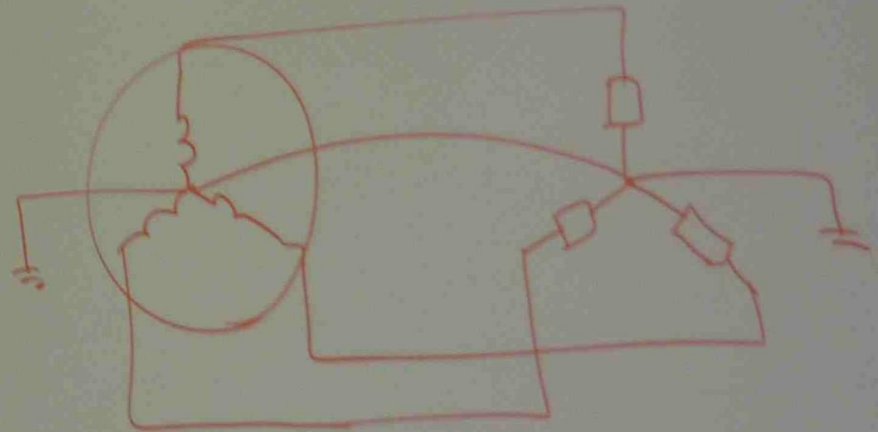

3 ϕ AC system


ph

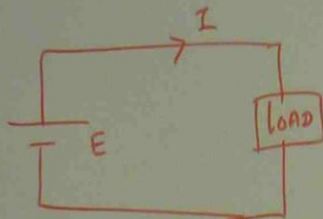COMPARE THE COPPER WEIGHT OF 3 ϕ WIRES SYSTEM AND SIMPLE DC SYSTEM.



SIMPLE DC SYSTEM

$$\text{DC POWER} = E \times I$$

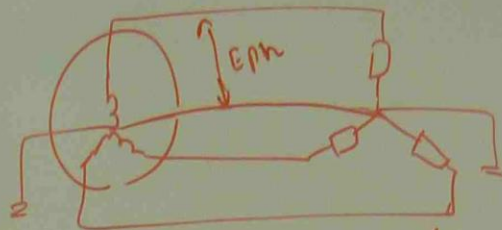


$$3\phi \text{ AC POWER} = 3 E_{ph} I \cos \phi$$

ASSUMPTION (1)

SAME POWER IS PRODUCED.

$$\text{DC POWER} = 3\phi \text{ AC POWER}$$

$$E \times I = 3 E_{ph} I \cos \phi$$

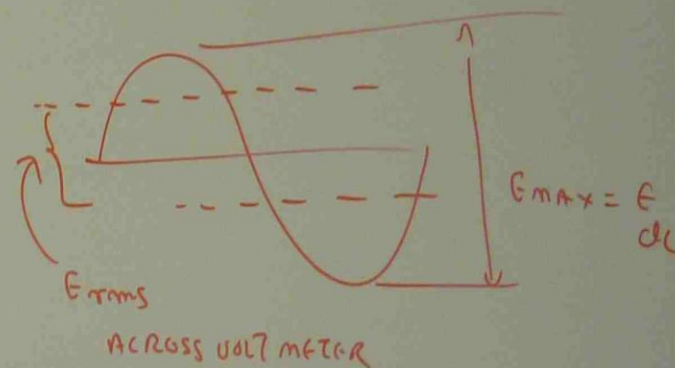

ASSUMPTION (2)

SAME VOLTAGE LEVEL

$$\therefore E = E_{max}$$

$$E_{ph} = \frac{E_{max}}{\sqrt{2}} \quad (\text{RMS})$$

$$E \times I = 3 \frac{E_{max}}{\sqrt{2}} I \cos \phi \rightarrow I = \frac{3 I \cos \phi}{\sqrt{2}} \quad \text{--- (1)}$$

Assumption (3)

Power losses are to be compared

DC power loss : 3ϕ AC power loss

$$2 I^2 R_1 : 3 (I')^2 R_2$$

$$2 \left(\frac{3 I' \cos \theta}{\sqrt{2}} \right)^2 R_1 : 3 (I')^2 R_2$$

$$2 \times \frac{9 (I')^2 \cos^2 \theta}{2} R_1 : 3 (I')^2 R_2$$

$$9 \cos^2 \theta R_1 : 3 R_2$$

$$3 \cos^2 \theta R_1 : R_2$$

$$3 \cos^2 \theta \frac{\rho L}{A_1} : \frac{\rho L}{A_2}$$

$$R = \frac{\rho L}{A}$$

ρ = RESISTIVITY

L = LENGTH

A = CROSS SECTIONAL AREA
(C.S.A)

SAME LENGTH L

SAME MATERIAL ρ

$$\frac{3 \cos^2 \theta}{DC \text{ CSA}} : \frac{1}{AC \text{ CSA}}$$

$$\frac{DC \text{ CSA}}{3 \cos^2 \theta} : AC \text{ CSA}$$


$$\frac{1}{3 \cos^2 \theta} : \frac{AC \text{ CSA}}{DC \text{ CSA}}$$

$$\frac{AC \text{ } 3\phi \text{ LINE C.S.A}}{DC \text{ LINE C.S.A}} : \frac{1}{3 (\text{POWER FACTOR})^2}$$


VOLTAGE VARIATIONS IN POWER SYSTEM

LINE RESISTANCE AND LINE INDUCTIVE REACTANCE CAUSE VOLTAGE DROP AND VARIATION OF LINE VOLTAGE.

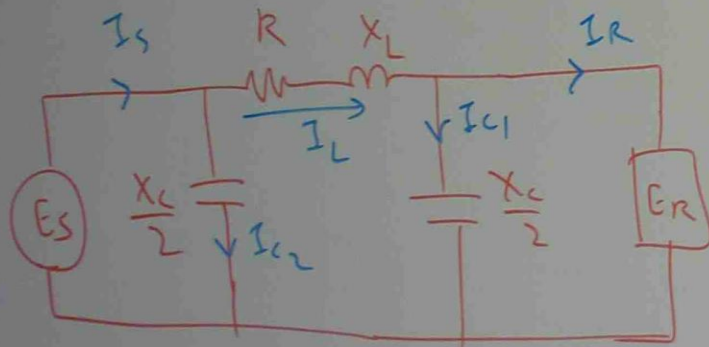- TO COMPENSATE LINE VOLTAGE DROP, (1) USE HIGH VOLTAGE TRANSMISSION SYSTEM
(2) USE TAP CHANGER (OR) VOLTAGE REGULATOR
(3) USE POWER FACTOR IMPROVEMENT SYSTEM
(FREE RUNNING SYNCHRONOUS MOTOR CONNECTED TO DISTRIBUTION STATION BUS BAR)




II EQUIVALENT CIRCUIT

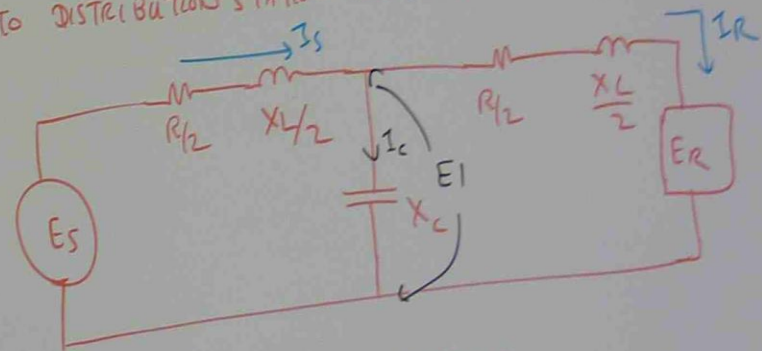


I EQUIVALENT CIRCUIT

II EQUIVALENT VECTOR DIAGRAM

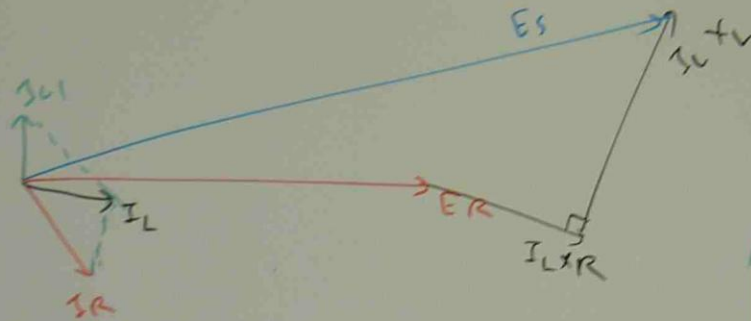


I EQUIVALENT CIRCUIT VECTOR DIAGRAM

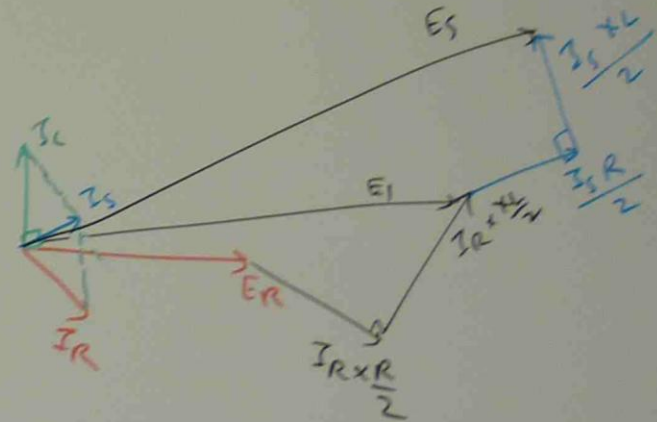



By studying the vector diagrams,
the component that effects the
line voltage variations can be identified.

TAP CHANGER — ON LOAD
 — OFF LOAD


INDUCTION MOTOR

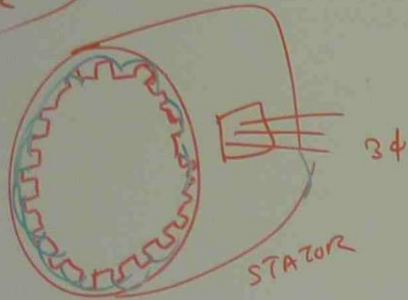


SYNCHRONOUS MOTOR

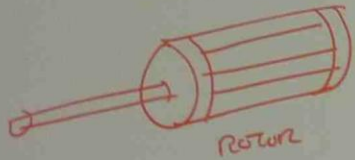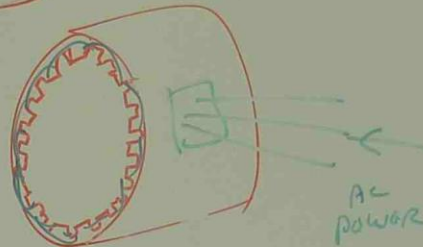


ROTOR

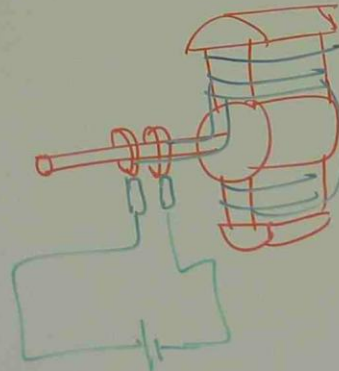


DC EXCITATION

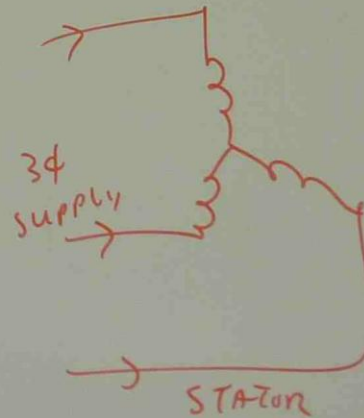

I_{dc} = FIELD EXCITATION CURRENT

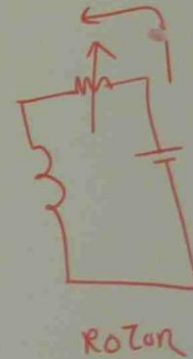

ROTOR

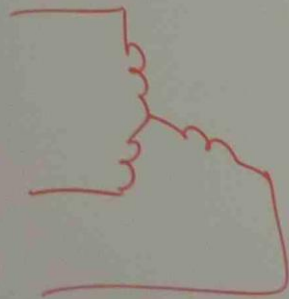

STATOR

LAGGING P.F

COMPONENTS OF CIRCUIT BREAKER

ANTI PUMPING DEVICE

A DEVICE WHICH PREVENTS THE CIRCUIT BREAKER RECLOSING AFTER OPENING

SHUNT TRIP

A TRIP RELEASE ENERGIZED BY A SOURCE OF VOLTAGE WHICH MAY NOT BE DEPENDENT ON MAIN CIRCUIT VOLTAGE

RELEASE

A DEVICE MECHANICALLY CONNECTED TO THE CIRCUIT WHICH RELEASES THE HOLDING.

