

FIND MATCHING INDUCTANCE AND CAPACITANCE FOR GIVEN TRANSMISSION LINE

By USING SMITH CHART.

$$f = 6 \times 10^7 \text{ Hz} \\ (60 \text{ MHz})$$

$$Z_s = 25 - j15$$

$$Z_0 = 50 \Omega$$

$$Z_s / Z_0 = \frac{25 - j15}{50} = 0.5 - j0.3$$

FOR MATCHING

$$Z_s^* = 0.5 + j0.3$$


$$Z_L = 100 - j25$$

$$Z_L / Z_0 = \frac{100 - j25}{50}$$

$$= 2 - j0.5$$

MATCHING

$$Z_L^* = 2 + j0.5$$

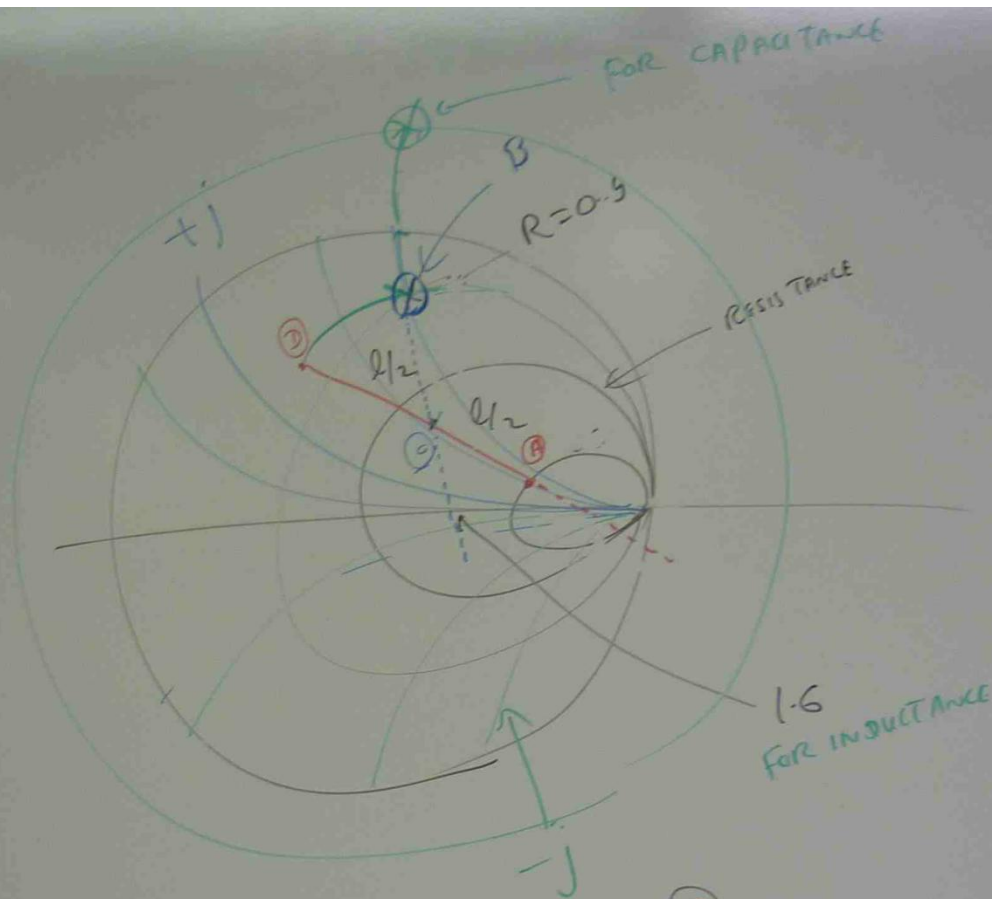

LOCATE  $0.5 + j0.3$  FOR (D)

$2 + j0.5$  FOR (A)

JOIN A & D

DRAW (D) (A) TO CROSS THE HORIZONTAL  
LINE

NOTE HORIZONTAL CUTTING POINT

$$VSWR = 1.5$$

DIVIDE THE LINE (A D)

MARK THE MIDDLE POINT

(C)

USE THE MIDDLE POINT AS CENTRE

RADIUS  $\frac{\lambda}{2}$  DRAW THE ARC UNTIL IT MEETS RESISTANCE 0.5 LINE

MARK THE MEETING POINT.

(B)

JOIN (B) & (C), DRAW THE LINE BC UNTIL IT CUTS  
THE HORIZONTAL LINE.

NOTE THE HORIZONTAL CUTTING POINT 1.6

$$L = \frac{\text{HORIZONTAL CUTTING POINT OF LINE BD} \times Z_0}{2\pi f} \quad (H)$$

$$= \frac{1.6 \times 50}{2 \times 3.1416 \times 6 \times 10^7} = 2.12 \times 10^{-7} \text{ H}$$


$$= 0.212 \text{ } \mu\text{H}$$

AT (B) POINT DRAW THE CURVES PARALLEL TO OTHER CURVES UNTIL IT MEETS THE FIRST INNER CIRCLE.

$$\text{CAPACITANCE} = \frac{\text{READING OF THE MEETING POINT ON FIRST INNER CIRCLE}}{Z_0 \times 2\pi \times f} \quad (f)$$

$$= \frac{0.5}{50 \times 2 \times 3.1416 \times 6 \times 10^7}$$

=

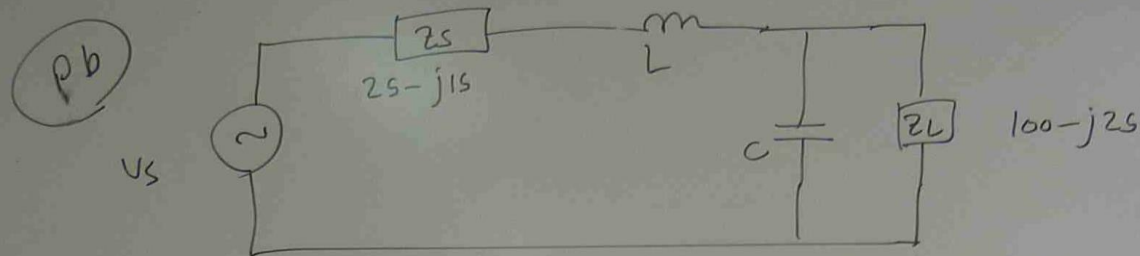

FIND MATCHING INDUCTANCE AND CAPACITANCE FOR GIVEN TRANSMISSION LINE

By USING SMITH CHART.

$$f = 6 \times 10^7 \text{ Hz}$$

(60 MHz)

$$Z_s = 25 - j15$$

$$Z_0 = 50 \Omega$$

$$Z_s / Z_0 = \frac{25 - j15}{50} = 0.5 - j0.3$$

FOR MATCHING

$$Z_s^* = 0.5 + j0.3$$

$$Z_L = 100 - j25$$

$$Z_L / Z_0 = \frac{100 - j25}{50}$$

$$= 2 - j0.5$$

MATCHING

$$Z_L^* = 2 + j0.5$$





NOTE HORIZONTAL CUTTING POINT

$$VSWR = 1.5$$

DIVIDE THE LINE (A D)

MARK THE MIDDLE POINT

(C)

USE THE MIDDLE POINT AS CENTRE

RADIUS  $\frac{l}{2}$  DRAW THE ARC UNTIL IT MEETS RESISTANCE 0.5 LINE

MARK THE MEETING POINT.

(B)

JOIN (B) & (C), DRAW THE LINE BC UNTIL IT CUTS  
THE HORIZONTAL LINE.

NOTE THE HORIZONTAL CUTTING POINT 1.6

$$L = \frac{\text{HORIZONTAL CUTTING POINT OF LINE BD} \times Z_0}{2\pi f} \quad (H)$$

$$= \frac{1.6 \times 50}{2 \times 3.1416 \times 6 \times 10^7} = 2.12 \times 10^{-7} \text{ H}$$

$$= 0.212 \mu \text{H}$$

AT (B) POINT DRAW THE CURVES PARALLEL TO OTHER CURVES UNTIL IT MEETS THE FIRST INNER CIRCLE.

$$CAPACITANCE = \frac{\text{READING OF THE MEETING POINT ON FIRST INNER CIRCLE}}{Z_0 \times 2\pi \times f} \quad (f)$$

$$= \frac{0.5}{50 \times 2 \times 3.1416 \times 6 \times 10^7}$$

$$=$$



Step (15)

26-b

$f = 6 \times 10^8 \text{ Hz}$

0.78 it is susceptance  $\rightarrow 0.78 / Z_0 = 0.0156 \text{ S}$

$Z_0 = 50$

$\therefore C =$


$$\frac{0.0156}{2\pi \times 6 \times 10^8}$$

$= 41.4 \text{ pF}$

## The Complete Smith Chart
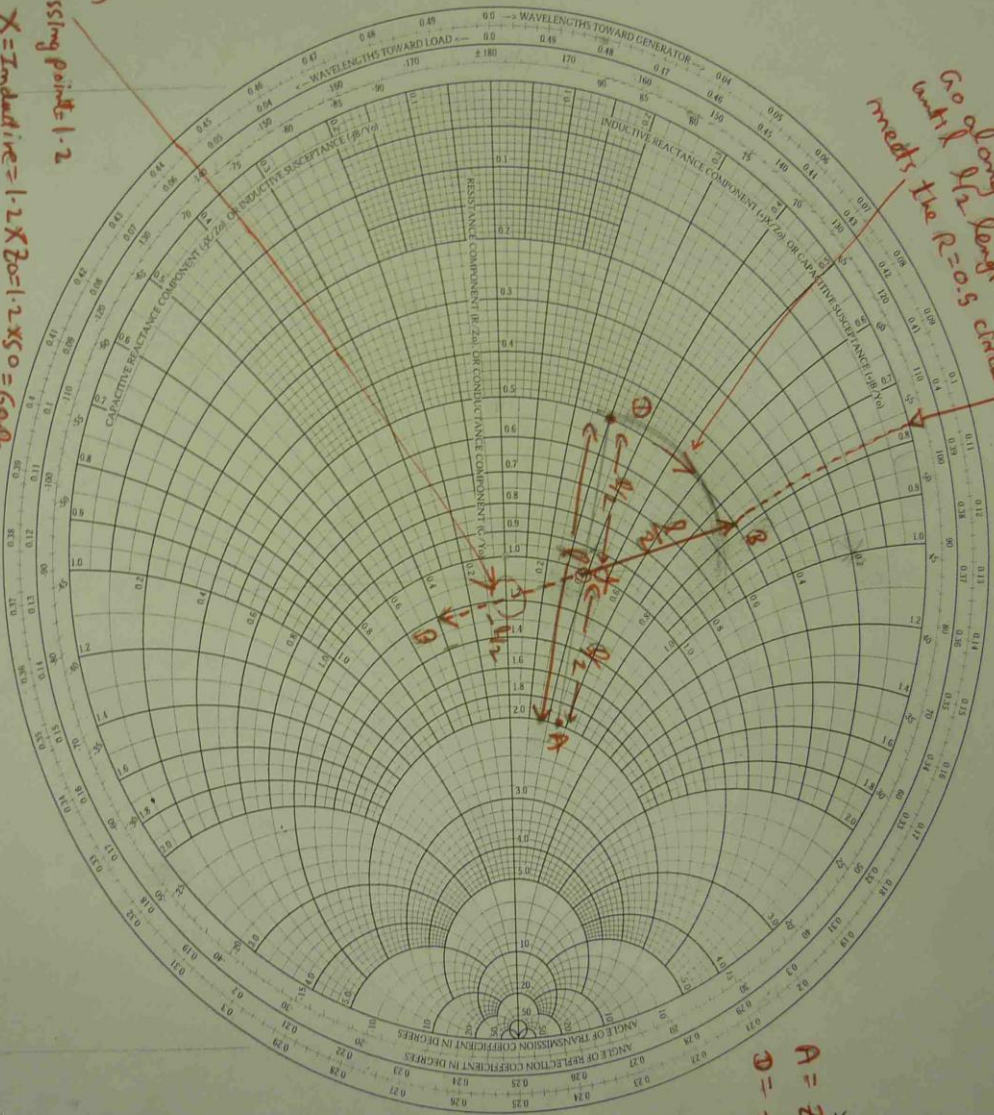
### Black Magic Design

Go along the arc until  $\lambda/2$  length meets the  $R=0.5$  circle




$A = Z_L$   
 $D = Z_S$

Step (6)  
crossing point 1.2

$$\therefore X = \text{Inductive} = 1.2 \times B_0 = 1.2 \times 50 = 60 \Omega$$
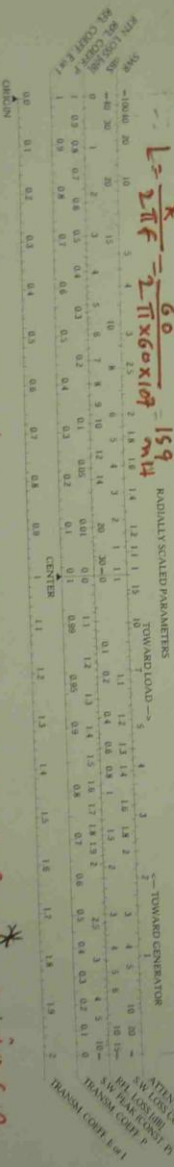
$$L = \frac{X}{2\pi f} = \frac{60}{2\pi \times 6 \times 10^8} = 15.9 \text{ nH}$$



Step (1) At meeting point, find susceptance

Then convert to C

Step (6) At d point reverse  $\lambda/2$  find horizontal crossing point

It is (X) convert to L


Step (1) Place A point for  $Z_L = 2 + j0.5 \Omega$

Step (2) Place D point for  $Z_S = 0.5 + j0.3 \Omega$

Step (3) Join A and D; length =  $\lambda$

Step (4) at  $\lambda/2$  point, take meeting centre with meeting  $\lambda/2$  more around  $R = 0.5$  circle until it meets

## WAVE GUIDES

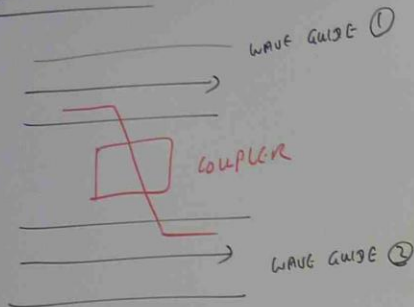


## DIPLEXER


A DIPLEXER IS A PASSIVE DEVICE THAT IMPLEMENTS FREQUENCY DOMAIN MULTIPLEXING.
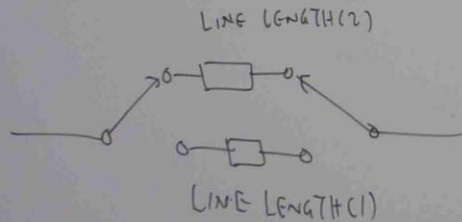
## PHASE SHIFTER

PHASE SHIFTERS ARE DEVICES USED TO ADJUST TRANSMISSION PHASE IN A SYSTEM



## PHASE SPLITTER

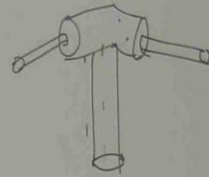


PHASE SPLITTERS ARE LOW LOSS REACTIVE SPLITTERS FOR DISTRIBUTION OF RF SIGNALS TO RADIO ANTENNAS


## CIRCULATORS

CIRCULATOR IS A PASSIVE ELECTRONIC COMPONENT WITH 3 (OR) MORE PORTS IN WHICH THE PORTS CAN BE ACCESSED IN SUCH A WAY THAT WHEN A SIGNAL IS FEED INTO ANY PORT IT IS TRANSFERRED TO NEXT PORT ONLY

ANTENNA

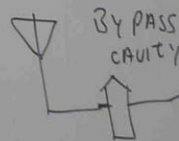

BY PASS CAVITY

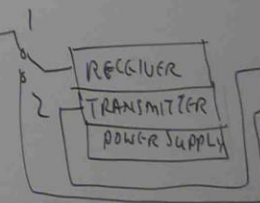


ISOLATOR


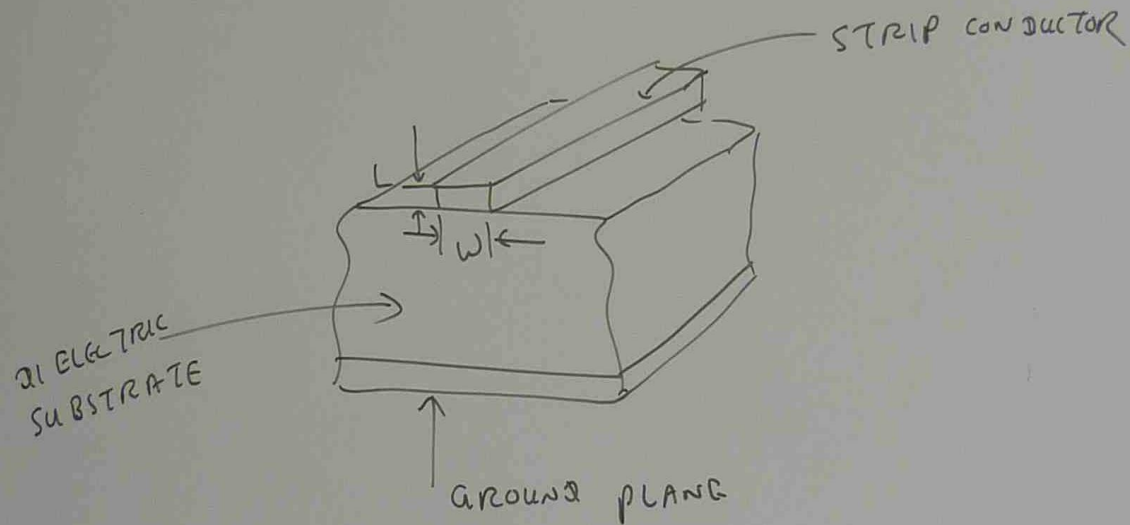
## MICRO STRIP TRANSMISSION LINE

MICRO STRIP TRANSMISSION LINE IS A KIND OF HIGH GRADED PRINTED CIRCUIT CONSTRUCTION CONSISTING OF A TRACK OF COPPER OR OTHER CONDUCTOR ON AN INSULATING SUBSTRATE.





## SUBSTRATE MATERIAL

IMPORTANT QUALITIES OF DIELECTRIC SUBSTRATE INCLUDES

- MICROWAVE DIELECTRIC CONSTANT
- THE FREQUENCY DEPENDENCY
- SURFACE FINISH AND FLATNESS
- DIELECTRIC LOSS TANGENT
- THE COST
- THERMAL EXPANSION AND CONDUCTIVITY
- DIMENSIONAL STABILITY WITH TIME
- SURFACE ADHESION PROPERTIES
- POROSITY

## COMMON SUBSTRATE MATERIALS

PLASTIC - CHEAP, GOOD SURFACE ADHESION  
POOR MICROWAVE PROPERTIES  
LOW THERMAL CONDUCTIVITY

CERAMICS - RIGID, HARD, DIFFICULT TO SHAPE  
CUT AND DRILL

### SINGLE CRYSTAL

DIELECTRIC CONSTANT 9.4 TO 11.6

SURFACE ROUGHNESS  $\frac{1}{100}$  MICRON

### SINGLE CRYSTAL GALLIAN

- DIELECTRIC CONSTANT = 13

LOSS TANGENT  $\frac{6}{10000}$

THERMAL CONDUCTIVITY 0.3 WATT/CM/DEG.

### KINDS OF MICROSTRIP LINES

SINGLE STRIP LINE

DUAL STRIP LINE



