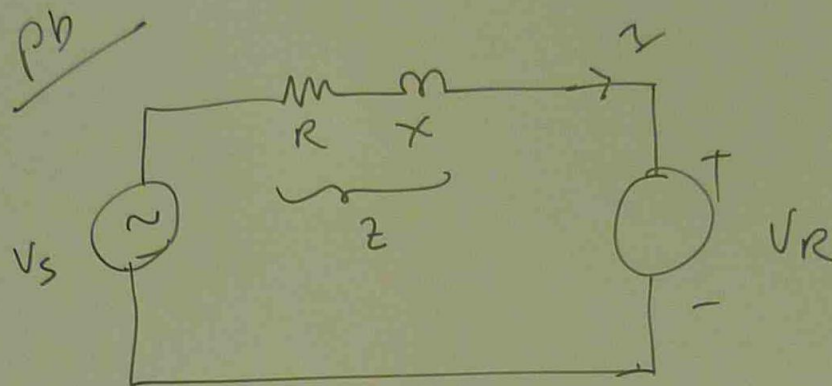


POWER TRANSMISSION LINE



IN ABOVE CIRCUIT, THE LOAD CONSUMES
1500 WATT AT POWER FACTOR OF 0.8
AND VOLTAGE OF 460V. THE TRANSMISSION
LINE IMPEDANCE $Z = 2 + j5 \Omega$
CALCULATE SENDING END VOLTAGE FOR

(a) LAGGING POWER FACTOR

(b) LEADING POWER FACTOR.

$$V_R = 460V$$

$$I = \frac{\text{power}}{V \times \cos \phi}$$

$$= \frac{1500}{460 \times 0.8} = 4.08 \angle -36.8 \text{ Amp Lagging PF}$$

$$\overline{V_S} = \overline{V_R} + I Z$$

$$= 460 \angle 0 + 4.08 \angle -36.8 (2 + j5)$$

$$= 460 + 4.08 \angle -36.8 \left(\sqrt{2^2 + 5^2} \angle \tan^{-1} \frac{5}{2} \right)$$

$$= 460 + 4.08 \angle -36.8 \times 5.39 \angle 68.2$$

$$= 460 + 22 \angle 31.4$$

$$= 460 + 22 (\cos 31.4 + j \sin 31.4)$$

$$= 479 + j11.4$$

$$= \sqrt{479^2 + 11.4^2} \angle \tan^{-1} \frac{11.4}{479} = 479 \angle 1.4^\circ V$$

LEADING PF

$$\overline{V_S} = \overline{V_R} + I Z$$

$$= 460 \angle 0 + 4.08 \angle +36.8^\circ \times (2 + j9)$$

$$= 460 + 4.08 \angle 36.8^\circ \times 5.39 \angle 68.2^\circ$$

$$= 460 + 22 \angle 105.1^\circ$$



$$= 460 + 22 (\cos 105.1^\circ + j \sin 105.1^\circ)$$

$$= 454 + j21.2$$

$$= \sqrt{454^2 + 21.2^2} \angle \tan^{-1} \frac{21.2}{454}$$

$$= 455 \angle 2.7^\circ \checkmark$$

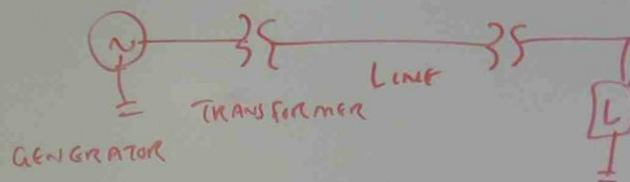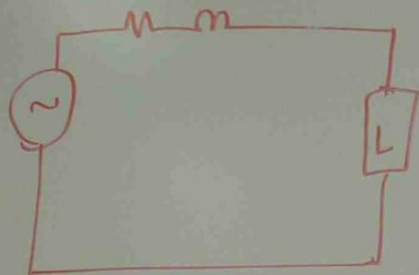PER UNIT REPRESENTATION OF POWER LINE EQUIPMENTS



LINE IMPEDANCE

$$Z_{(pu)} = \frac{Z(\Omega)}{Z(\text{BASE})} = \frac{Z(\Omega) \times VA(\text{BASE})}{(\text{BASE VOLTAGE})^2}$$

$Z_1(\Omega)$ AT VA_1, V_1


TO FIND Z_1 AT VA_2 AND V_2

$$Z_2(pu) = Z_1(pu) \times \frac{V_2^2}{V_{\text{BASE}}^2} \times \frac{VA_{\text{BASE}}}{VA_2}$$

VA = VOLT AMP (APPARENT POWER)

$VA(\text{BASE})$ = BASE VOLT AMP.

ph

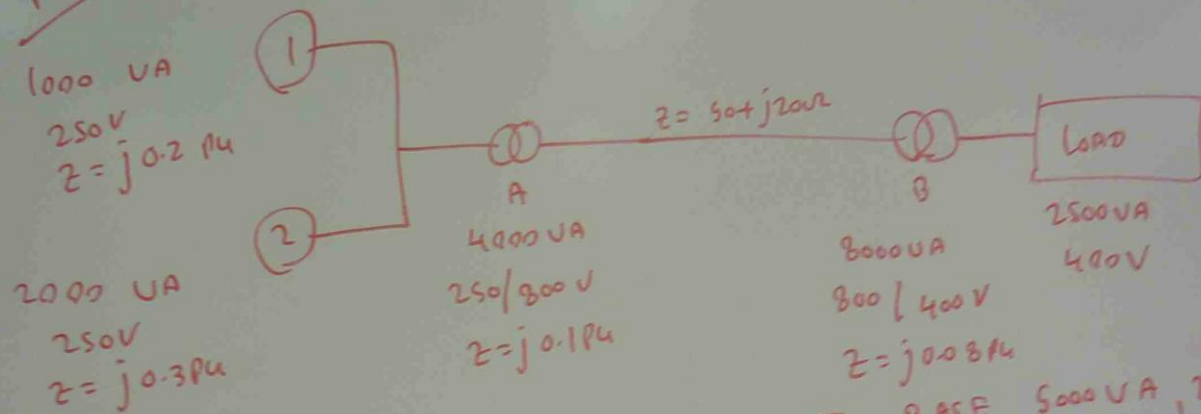

CALCULATE P.U IMPEDANCE REFERRED TO BASE 5000 VA, 250V

BASE 5000 VA

250V (BASE) (BASE VOLTAGE AT PRIMARY

RESPECTIVE BASE VOLTAGE AT SECONDARY,

IS 800V

GENERATOR (1)

$$Z_{pu}(5000) = j0.2 \times \frac{250^2}{250^2} \times \frac{5000}{1000} = j1.0 \text{ pu}$$

GENERATOR (2)

$$Z_{pu}(5000) = j0.3 \times \frac{250^2}{250^2} \times \frac{5000}{2000} = j0.75 \text{ pu}$$

Transformer (A)

$$Z_{pu}(5000) = j0.1 + \frac{250^2}{250^2} \times \frac{5000}{4000} = j0.125 pu$$


Transformer (B)

$$Z_{pu}(5000) = j0.1 \times \frac{400^2}{250^2} \times \frac{5000}{8000} = j0.128 pu$$


$$\frac{\text{Load}}{VA} = \frac{VA}{VA_{BASE}} = \frac{2500}{5000} = 0.5 pu$$

LINE
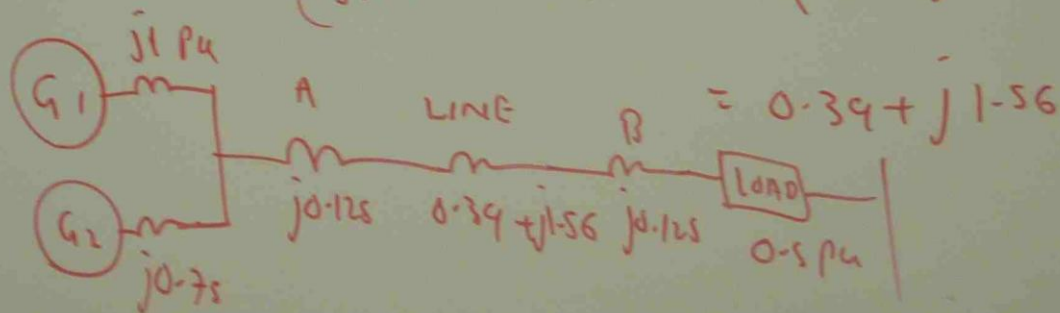
$$Z(pu) = \frac{Z(\Omega) \times VA_{BASE}}{(BASE VOLTAGE)^2} = \frac{(50 + j20) \times 5000}{(800)^2}$$



Pb

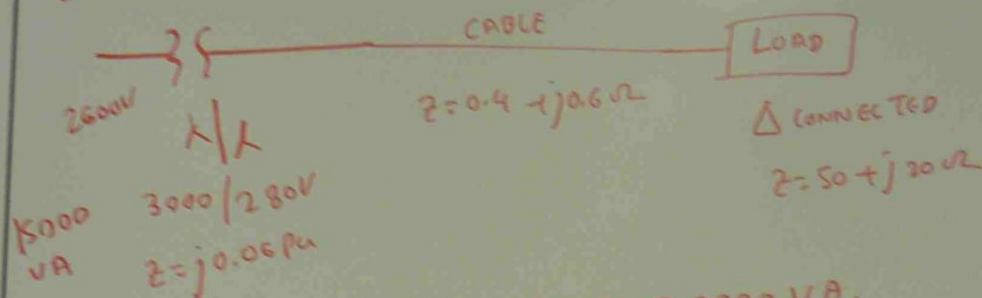

TAKE BASE VOLTAGE 2600V, 20000 VA.
 FIND EQUIVALENT DIAGRAM.

TRANSFORMER

$$Z(20000) = j0.06 \times \frac{3000^2}{2600^2} \times \frac{20,000}{15,000}$$

$$= j0.107 \text{ pu}$$

CABLE

$$Z(\text{pu}) = \frac{Z(\Omega) \times \text{VA BASE}}{(\text{BASE V})^2} = \frac{(0.4 + j0.6) \times 20,000}{(2600)^2}$$


$$= 0.136 + j0.204 \text{ pu}$$

LOAD $\Delta \rightarrow \times$ CONVERGE SLOW

$$Z_{pu} = \frac{50 + j20}{3} \times \frac{20,000}{(V_{BASE})^2}$$

$$\begin{aligned} 3000V &\longrightarrow 280V \\ 2600V &\longrightarrow ? = 280 \times \frac{2600}{3000} \\ \text{BASE} & \\ &= 242.7 \end{aligned}$$
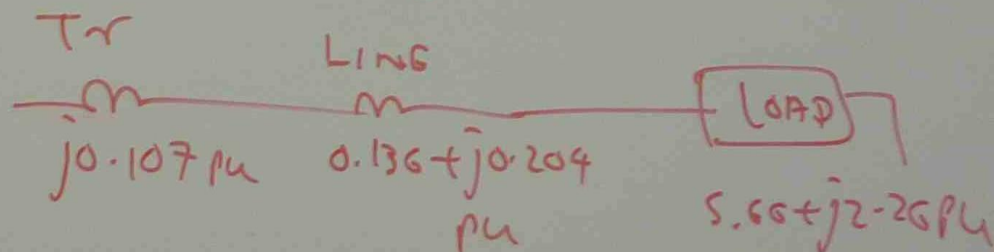
$$\begin{aligned} Z_{pu} &= \frac{50 + j20}{3} \times \frac{20,000}{(242.7)^2} \\ &= 5.66 + j2.26 \text{ pu} \end{aligned}$$



CALCULATION OF LINE INDUCTANCE AND LINE CAPACITANCE

LINE RESISTANCE $R = \frac{\rho L}{A}$

LINE INDUCTANCE

$$L = 2 \times 10^{-7} \ln \frac{GMD}{GMR} \text{ H/m}$$




GMD = GEOMETRIC MEAN DISTANCE
BETWEEN LINE CONDUCTORS

GMR = GEOMETRIC MEAN RADIUS OF
LINE CONDUCTOR



$$GMD = D$$

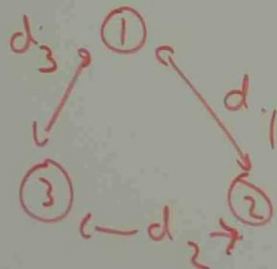

$$GMD = \sqrt[3]{D_1 \times D_2 \times D_3}$$

GMR = RADIUS "R"

LINE CAPACITANCE

$$C = \frac{2\pi \epsilon}{\ln \frac{GMD}{GMR}} \quad \text{F/m}$$

$$= \frac{2\pi \times \frac{10^{-9}}{36\pi}}{\ln \frac{GMD}{GMR}} = \frac{1 \times 10^{-9}}{18 \ln \frac{GMD}{GMR}} \quad \text{F/m}$$

LINE INDUCTIVE REACTANCE

$$X_L = 2\pi f L \quad (\Omega)$$

LINE CAPACITIVE REACTANCE

$$X_C = \frac{1}{2\pi f C} \quad (\Omega)$$

$$L = 0.741 \times 10^{-3} \log_{10} \frac{GMD}{GMR} \quad H/mile$$

$$C = \frac{0.0382}{\log_{10} \frac{GMD}{GMR}} \quad \mu F/mile$$

Pb DETERMINE THE CONSTANTS IN π MODEL SINGLE PHASE LINE HAVING THE FOLLOWING SPECIFICATIONS.

OUTSIDE DIAMETER = 0.629 in

SPACING = 12 ft

GEOMETRIC MEAN RADIUS = 0.01987 ft

RESISTANCE/mile = 0.1966 Ω

LINE LENGTH = 25 miles.

$$R = 0.1966 \times 25 = 4.92 \Omega$$

$$L = 0.741 \times 10^{-3} \log_{10} \frac{12}{0.01987}$$

$$= 2.06 \times 10^{-3} \text{ H/mile}$$


$$\textcircled{25 \text{ miles}} \quad L = 2.06 \times 10^{-3} \times 25 = 51.5 \times 10^{-3} \text{ H}$$

$$C = \frac{0.0388}{\log_{10} \frac{G_{MD}}{G_{MR}}} = \frac{0.0388}{\log_{10} \frac{12}{0.01987}}$$


$$= 0.0146 \mu\text{F/mile}$$

$\textcircled{25 \text{ miles}}$
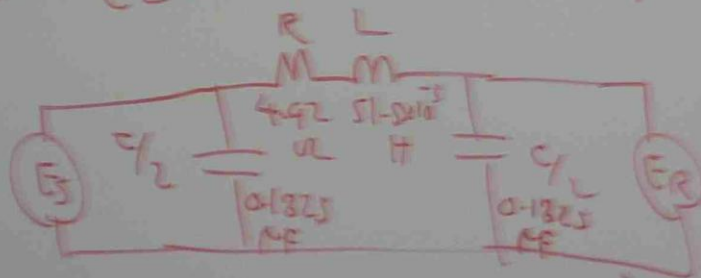
$$C = 0.0146 \times 25 = 0.365 \mu\text{F}$$



pb

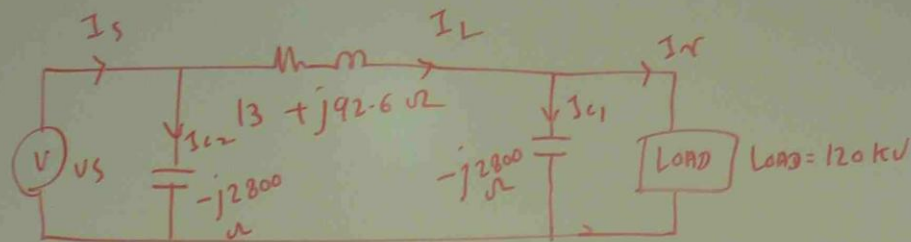

A load on given line is 12000 kW, unity P.F supplied at 120 kV. Calculate I_s , V_s , power supplied by generator.

$$V_r = 120,000 \angle 0^\circ \text{ V} \quad I_r = \frac{P}{V_r \cos \phi} = \frac{12000 \times 10^3}{120 \times 10^3} = 100 \text{ A} = 100 \angle 0^\circ \text{ A}$$

$$I_{c1} = \frac{V}{-jX_{c1}} = \frac{120,000}{-j2800} = j42.9 \text{ A}$$


$$I_L = I_r + I_{c1} = 100 + j42.9 \text{ A} = \sqrt{100^2 + 42.9^2} \angle \tan^{-1} \frac{42.9}{100} = 109 \angle 23.2^\circ \text{ Amp.}$$

$$\begin{aligned} V_s &= V_r + I_L Z = 120,000 + 109 \angle 23.2^\circ \times (13 + j92.6) \\ &= 120,000 + (100 + j42.9) \times (13 + j92.6) \\ &= 120,000 - 2670 + j9820 \\ &= 117300 + j9820 = 117700 \angle 4.7^\circ \text{ V} \end{aligned}$$

$$\bar{I}_{C2} = \frac{\bar{V}_S}{-jX_{C2}} = \frac{117300 + j9820}{-j2800} = -3.52 + j41.9 \text{ A}$$

$$\bar{I}_S = \bar{I}_{C2} + \bar{I}_L = -3.52 + j41.9 + 100 + j42.9 = 96.5 + j84.8$$

$$= 128.5 \angle 41.3^\circ \text{ A}$$

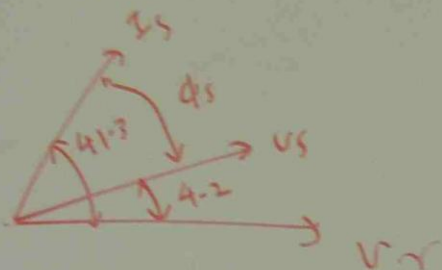

$$\phi_S = 41.3 - 4.2 = 36.5$$

$$P = V_S I_S \cos \phi_S$$

$$= 117700 \times 128.5 \times \cos 36.5$$

$$= 12160,000 \text{ W}$$

$$= 12160 \text{ kW}$$



IN ABOVE CIRCUIT, THE LOAD CONSUMES 4000 W AT PF 0.8 LAGGING. THE SENDING END VOLTAGE IS 600 V AND THE IMPEDANCE $Z = 1 + j4 \Omega$. DETERMINE LOAD VOLTAGE

TOTAL POWER PROVIDED BY GENERATOR = 4000 W

$$I = \frac{P}{V \cos \phi} = \frac{4000}{600 \times 0.8} = 8.32 \angle -36.8^\circ \text{ A}$$

$$\bar{V}_s = \bar{V}_r + I Z$$

$$600 \angle \phi = V_r + 8.32 \angle -36.8^\circ (1 + j4)$$

$$600 \cos \phi + j 600 \sin \phi = V_r + 8.32 \angle -36.8^\circ \times 4.12 \angle 76^\circ$$

$$600 \cos \phi + j 600 \sin \phi = V_r + 34.3 \angle 39.1^\circ$$

$$600 \cos \phi + j 600 \sin \phi = V_r + 34.3 (\cos 39.1^\circ + j \sin 39.1^\circ)$$

$$600 \cos \phi + j 600 \sin \phi = V_r + 26.6 + j 21.6$$

$$600 \cos \phi = V_r + 26.6$$

$$600 \sin \phi = 21.6$$

$$\phi = \sin^{-1} \frac{21.6}{600} = 2.06$$

$$600 \cos 2.06 = V_r + 26.6$$

$$V_r = 573 \text{ V}$$

$$L = 0.741 \times 10^{-3} \log_{10} \frac{GMD}{GMR} \quad H/mile$$

$$C = \frac{0.0388}{\log_{10} \frac{GMD}{GMR}} \quad \mu F/mile$$

✓ DETERMINE THE CONSTANTS IN π MODEL
SINGLE PHASE LINE HAVING THE FOLLOWING
SPECIFICATIONS.

OUTSIDE DIAMETER = 0.629 in

SPACING = 12 ft

GEOMETRIC MEAN RADIUS = 0.01987 ft

RESISTANCE / mile = 0.1966 Ω

LINE LENGTH = 25 miles.

$$R = 0.1966 \times 25 = 4.92 \Omega$$

$$L = 0.741 \times 10^{-3} \log_{10} \frac{12}{0.01987}$$

$$= 2.06 \times 10^{-3} \text{ H/mile}$$


$$\textcircled{25 \text{ miles}} \quad L = 2.06 \times 10^{-3} \times 25 = 51.5 \times 10^{-3} \text{ H}$$


$$C = \frac{0.0388}{\log_{10} \frac{GmD}{GmR}} = \frac{0.0388}{\log_{10} \frac{12}{0.01987}}$$

$$= 0.0146 \mu\text{F/mile.}$$

$\textcircled{25 \text{ miles}}$
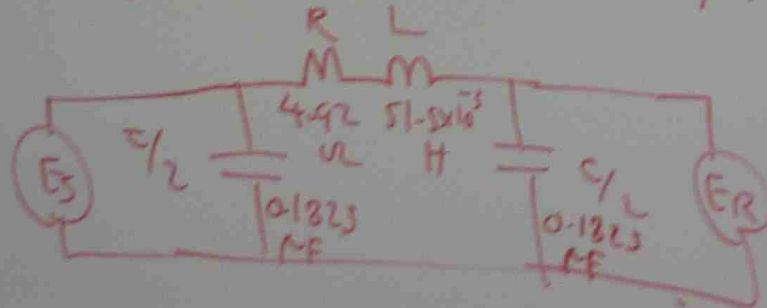
$$C = 0.0146 \times 25 = 0.365 \mu\text{F}$$



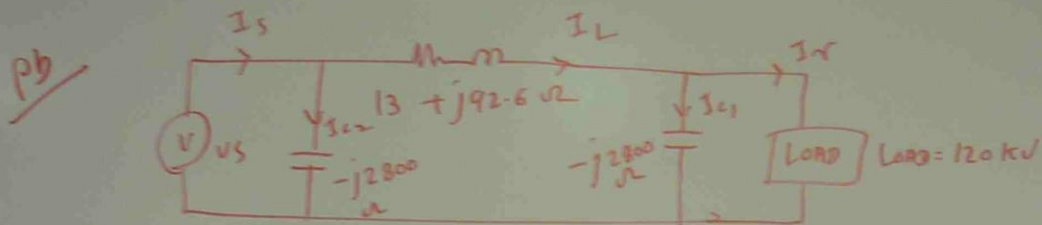

1. Load on given line is 12000 kW, unity P.F. supplied at 120 kV. Calculate I_s , V_s , power supplied by generator.

$$\bar{V}_r = 120,000 \angle 0^\circ \text{ V} \quad \bar{I}_r = \frac{P}{V_r \cos \phi} = \frac{12000 \times 10^3}{120 \times 10^3} = 100 \text{ A} = 100 \angle 0^\circ \text{ A}$$

$$\bar{I}_{C1} = \frac{V}{-jX_{C1}} = \frac{120,000}{-j2800} = j42.9 \text{ A}$$


$$\bar{I}_L = \bar{I}_r + \bar{I}_{C1} = 100 + j42.9 \text{ A} = \sqrt{100^2 + 42.9^2} \angle \tan^{-1} \frac{42.9}{100} = 109 \angle 23.2^\circ \text{ Amp.}$$

$$\begin{aligned} \bar{V}_s &= \bar{V}_r + \bar{I}_L \bar{Z} = 120,000 + 109 \angle 23.2^\circ \times (13 + j92.6) \\ &= 120,000 + (100 + j42.9) \times (13 + j92.6) \\ &= 120,000 - 2670 + j9820 \\ &= 117300 + j9820 = 117700 \angle 4.2^\circ \text{ V} \end{aligned}$$

$$\bar{I}_{C2} = \frac{\bar{V}_S}{-jX_{C2}} = \frac{117300 + j9820}{-j2800} = -3.52 + j41.9 \text{ A}$$

$$\bar{I}_S = \bar{I}_{C2} + \bar{I}_L = -3.52 + j41.9 + 100 + j42.9 = 96.5 + j84.8$$

$$= 128.5 \angle 41.3^\circ \text{ A}$$

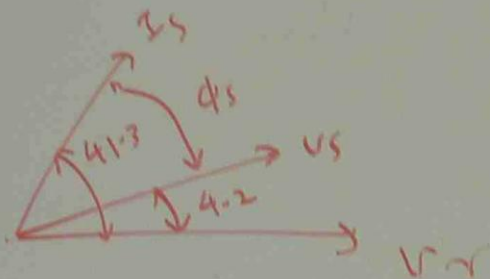


$$\phi_S = 41.3 - 4.2 = 36.5$$

$$P = V_S I_S \cos \phi_S$$

$$= 117700 \times 128.5 \times \cos 36.5$$

$$= 12160,000 \text{ W}$$

$$= 12160 \text{ kW}$$

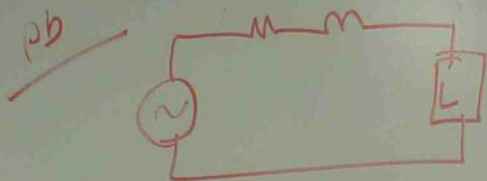

IN ABOVE CIRCUIT, THE LOAD CONSUMES 4000 W AT PF 0.8 LAGGING. THE SENDING END VOLTAGE IS 600 V AND THE IMPEDANCE $Z = 1 + j4 \Omega$. DETERMINE LOAD VOLTAGE

TOTAL POWER PROVIDED BY GENERATOR = 4000 W

$$I = \frac{P}{V \cos \phi} = \frac{4000}{600 \times 0.8} = 8.32 \angle -36.8^\circ \text{ A}$$

$$\bar{V}_s = \bar{V}_r + I Z$$

$$600 \angle \phi = V_r + 8.32 \angle -36.8^\circ (1 + j4)$$

$$600 \cos \phi + j 600 \sin \phi = V_r + 8.32 \angle -36.8^\circ \times 4.12 \angle 76^\circ$$

$$600 \cos \phi + j 600 \sin \phi = V_r + 34.3 \angle 39.1^\circ$$

$$600 \cos \phi + j 600 \sin \phi = V_r + 34.3 (\cos 39.1^\circ + j \sin 39.1^\circ)$$

$$600 \cos \phi + j 600 \sin \phi = V_r + 26.6 + j 21.6$$

$$600 \cos \phi = V_r + 26.6$$

$$600 \sin \phi = 21.6$$

$$\phi = \sin^{-1} \frac{21.6}{600} = 2.06$$

$$600 \cos 2.06 = V_r + 26.6$$

$$V_r = 573 \text{ V}$$

