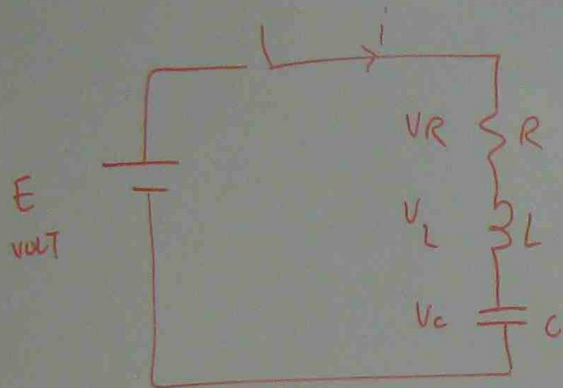


SOLVING THE SECOND ORDER DIFFERENTIAL EQUATION



$$V_R + V_L + V_C = E$$

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = E$$

$$\frac{d}{dt} iR + \frac{d}{dt} L \frac{di}{dt} + \frac{d}{dt} \frac{1}{C} \int i dt = \frac{d}{dt} E$$

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

$$\frac{R}{L} \frac{di}{dt} + \frac{d^2 i}{dt^2} + \frac{1}{LC} i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

Compare with

$$a \frac{d^2 i}{dt^2} + b \frac{di}{dt} + c i = 0$$

$$a m^2 + b m + c = 0$$

$$m = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$m = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

LET

$$\alpha = \frac{R}{2L}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\beta = \sqrt{\alpha^2 - \omega_0^2}$$

IF $\alpha > \omega_0 \Rightarrow$ OVER DAMP \longrightarrow

IF $\alpha = \omega_0 \Rightarrow$ CRITICAL DAMP \longrightarrow

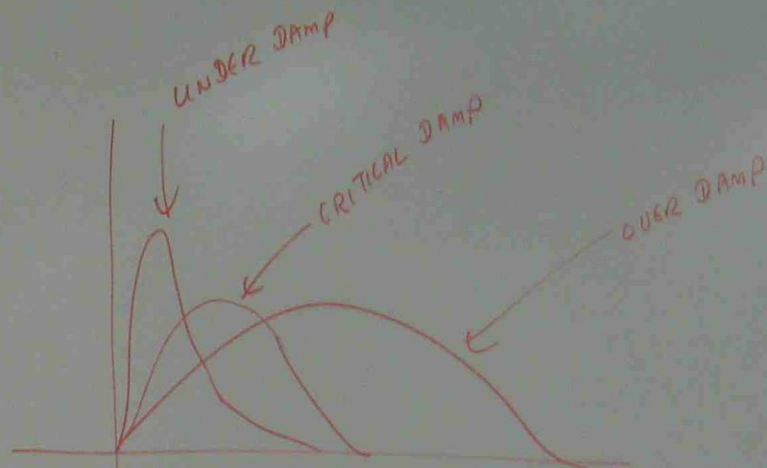IF $\alpha < \omega_0 \Rightarrow$ UNDER DAMP \longrightarrow




$$i = e^{-\alpha t} (A_1 e^{\beta t} + A_2 e^{-\beta t})$$

$$i = e^{-\alpha t} (A_1 + A_2 t)$$

$$i = e^{-\alpha t} (A_1 \sin \beta t + A_2 \cos \beta t)$$

ph) IN A GIVEN CIRCUIT, $E = 100V$, $R = 500\Omega$, $L = 0.25H$, $C = 100\mu F$.

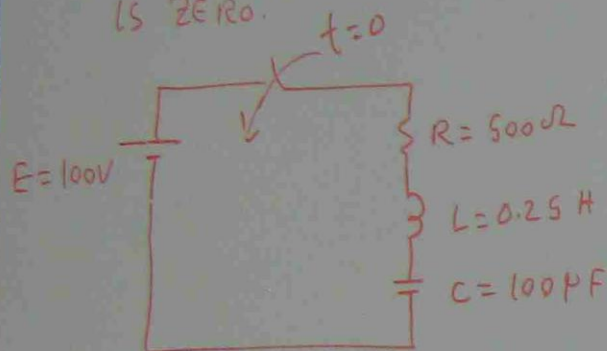DETERMINE THE EQUATION OF THE CURRENT IF THE INITIAL CHARGE ON CAPACITOR IS ZERO.



$$\alpha = \frac{R}{2L} = \frac{500}{2 \times 0.25} = 1000$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.25 \times 100 \times 10^{-6}}} = 200$$

$$\beta = \sqrt{\alpha^2 - \omega_0^2}$$

$$= \sqrt{1000^2 - 200^2}$$

$$= 979.8$$

$\alpha > \omega_0 \Rightarrow$ OVER DAMP

$$i = e^{-\alpha t} \left[A_1 e^{\beta t} + A_2 e^{-\beta t} \right]$$

$$= A_1 e^{(-\alpha + \beta)t} + A_2 e^{(-\alpha - \beta)t}$$

$$= A_1 e^{(-1000 + 979.8)t} + A_2 e^{(-1000 - 979.8)t}$$

$$i = A_1 e^{-20.2t} + A_2 e^{-1979.8t}$$

① $t=0 \rightarrow i=0$

$$0 = A_1 e^{-20.2 \times 0} + A_2 e^{-1979.8 \times 0}$$

$$A_1 + A_2 = 0 \quad \text{--- (1)} \Rightarrow A_1 = -A_2$$

$$i = A_1 e^{-20.2t} + A_2 e^{-1979.8t}$$

$$\frac{di}{dt} = A_1 \frac{d}{dt} e^{-20.2t} + A_2 \frac{d}{dt} e^{-1979.8t}$$

$$\frac{di}{dt} = -20.2 A_1 e^{-20.2t} + (-1979.8) A_2 e^{-1979.8t}$$

II

$$L \frac{di}{dt} = \text{INDUCTOR VOLTAGE}$$

$$t=0 \rightarrow L \frac{di}{dt} = E$$

$$\frac{di}{dt} = \frac{E}{L} = \frac{100}{0.25} = 400$$

$$400 = -20.2 A_1 e^{-20.2 \times 0} - 1979.8 A_2 e^{-1979.8 \times 0}$$

$$-20.2 A_1 - 1979.8 A_2 = 400$$

$$-20.2(-A_2) - 1979.8 A_2 = 400$$


$$A_2 = -0.2041$$

$$A_1 = 0.02041$$

$$i = 0.02041 e^{-20.2t} - 0.2041 e^{-1979.8t}$$

- A2

EXERCISE

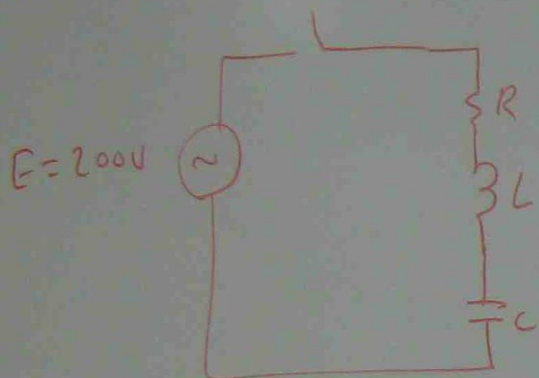

$$E = 200V, R = 100\Omega, L = 0.5 \text{ Henry}$$

$$C = 200\mu F$$

FIND THE EQUATION OF THE CURRENT

IF THE INITIAL CHARGE ON CAPACITOR IS

20 MICROCULOMBS

$$\Delta = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

COMPARE Δ & ω_0 SELECT THE EQUATION

CONDITION (1)

$$t = 0 \rightarrow i = 0$$

CONDITION (2)

$$Q = 20 \text{ mC}$$

$$V_C = \frac{Q}{C} = \frac{20 \times 10^{-3}}{200 \times 10^{-6}}$$

$$= 100V$$

$$V_C = \frac{1}{C} \int i dt$$

$$t = 0 \left| \frac{di}{dt} = \frac{E}{L} = \frac{100V}{0.5}$$

$$= 200$$

$$m = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

LET

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\beta = \sqrt{\alpha^2 - \omega_0^2}$$

IF $\alpha > \omega_0 \Rightarrow$ OVER DAMP

$$i = e^{-\alpha t} (A_1 e^{\beta t} + A_2 e^{-\beta t})$$

IF $\alpha = \omega_0 \Rightarrow$ CRITICAL DAMP

$$i = e^{-\alpha t} (A_1 + A_2 t)$$

IF $\alpha < \omega_0 \Rightarrow$ UNDER DAMP

$$i = e^{-\alpha t} (A_1 \sin \beta t + A_2 \cos \beta t)$$

