


A47

ZCT

APPLICATION OF GRADIENT IN POWER ENGINEERING

$$\text{FORCE GRADIENT} = \frac{\text{TOTAL FORCE}}{\text{UNIT AREA}}$$

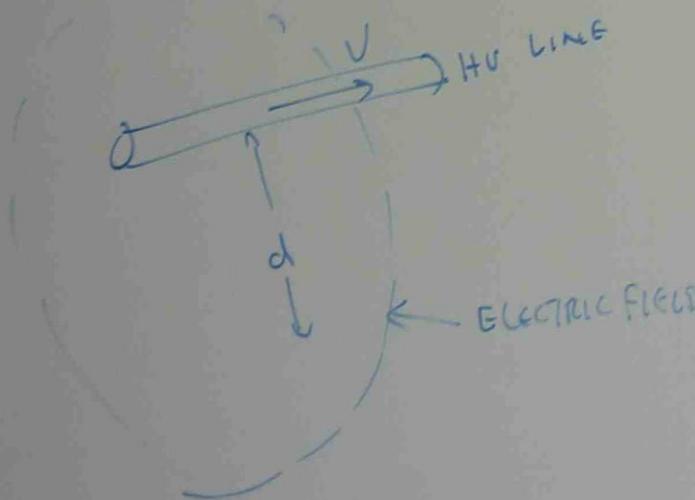
$$\text{VOLTAGE GRADIENT} = \frac{\text{VOLTAGE}}{\text{DISTANCE}}$$




ELECTRICAL
STRESS

$$\text{VOLTAGE GRADIENT} = \frac{E}{d} \quad V/cm$$

IT NEEDS TO RELIEVE ELECTRICAL STRESSES

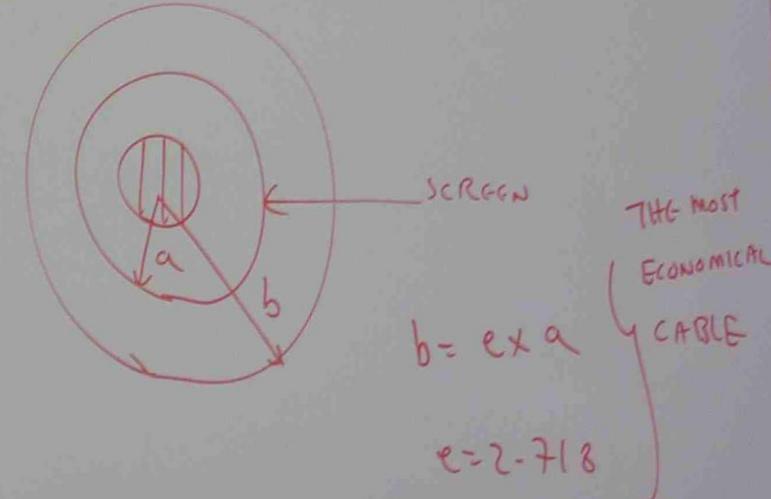

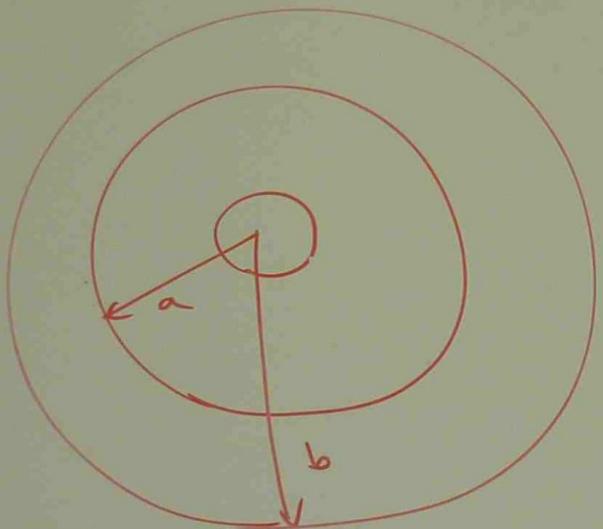Ex A SINGLE CORE CONCENTRIC CABLE IS TO BE MANUFACTURED FOR 200 KV, 50 Hz LINE. THE PAPER USED HAS MAXIMUM PERMISSIBLE SAFE STRESS OF 10^7 V/m (rms) AND A DIELECTRIC CONSTANT OF 4.5. CALCULATE THE DIMENSION FOR THE MOST ECONOMICAL CABLE AND THE CHARGING CURRENT PER Km.



$$b = e \times a \quad (\text{MOST ECONOMICAL CABLE})$$

$$e = 2.718$$

$$\text{GRADIENT} = \frac{E}{\text{DISTANCE}}$$

$$10^7 = \frac{200 \times 10^3}{a}$$

$$a = \frac{200 \times 10^3}{10^7} = 0.02 \text{ m}$$

$$b = e \times a = 2.718 \times 0.02 = 0.0544 \text{ m}$$

APPLICATION OF NATURAL LOG FUNCTION
IN POWER ENGINEERING

$$\log = \log_{10}$$

$$\text{NATURAL LOG} \rightarrow L_m = \log_{2.718}$$

CAPACITANCE OF UG CABLE

$$= \frac{2\pi \epsilon}{\ln \frac{b}{a}} \quad F/km$$

$$\epsilon = \text{DIELECTRIC CONSTANT} = \epsilon_r \times \epsilon_0$$

↑ ↓

RELATIVE
DIELECTRIC
CONSTANT OF
MATERIAL

8.85×10^{-12}

$$C = \frac{2 \times 3.1416 \times 4.5 \times 8.85 \times 10^{-12}}{\ln \frac{0.0544}{0.02}}$$

$$= 2.5 \times 10^{10} F/km$$

$$X_c = \frac{1}{2\pi f c}$$

$$= \frac{1}{2 \times 3.1416 \times 60 \times 2.5 \times 10^{10}}$$

$$= \frac{10^{10}}{2 \times 3.1416 \times 2.5 \times 60}$$


$$= 10615710 \Omega/km$$

$$\text{CHARGING CURRENT } (I_c) = \frac{V}{X_c}$$


$$= \frac{200 \times 10^3}{10615710}$$

$$= 0.0188 \text{ Amp} / \text{km}$$

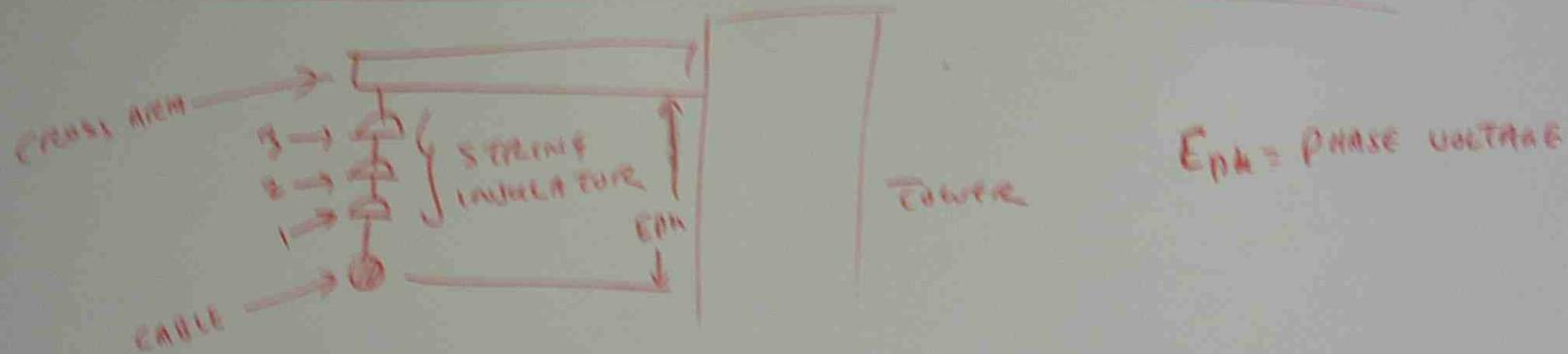DERIVATION of Formula A To compare the required QUANTITIES IN POWER ENGINEERING



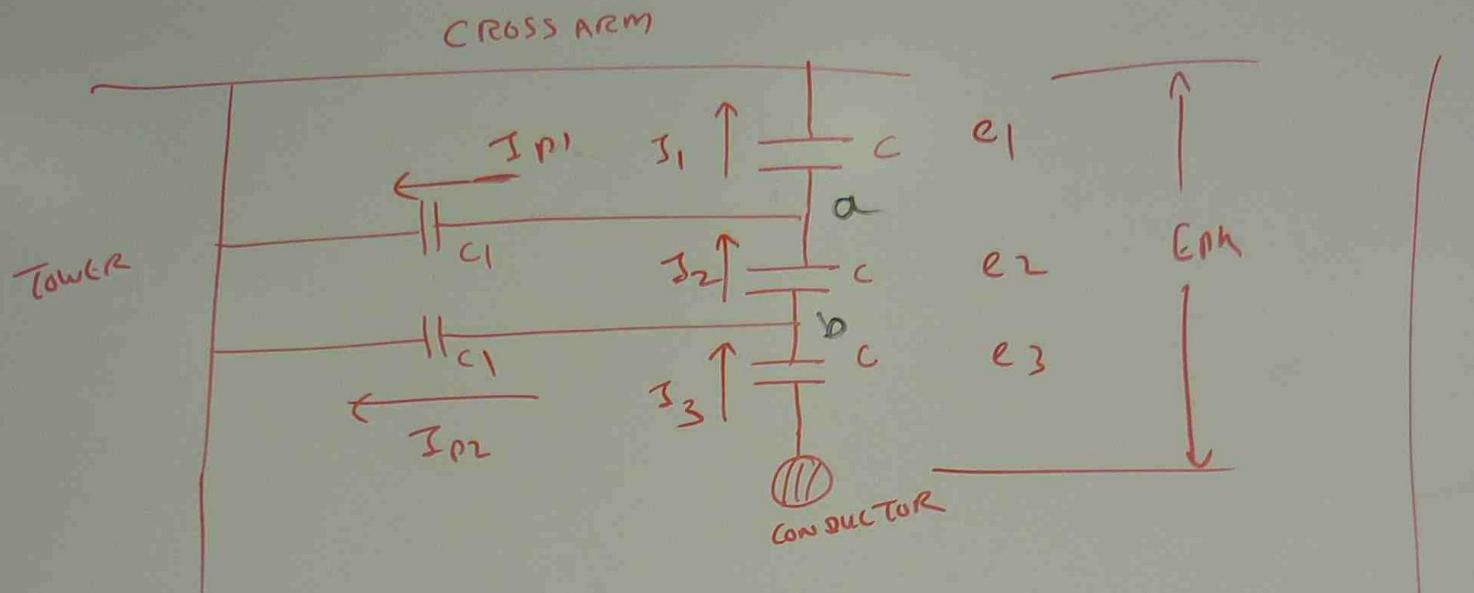Ex BRIEFLY DESCRIBE HOW THE CAPACITANCE OCCURS
FOR 3 STRING INSULATORS. DERIVE THE
EQUATION FOR POTENTIAL GRADING.



$$e_1 + e_2 + e_3 = \text{PHASE VOLTAGE}$$

AT POINT (a)

$$I_2 = I_1 + I_{P1} \quad \therefore C_1 = kC$$

$$C_1 e_2 = C_1 e_1 + C_1 e_1$$

$$C_1 e_2 = C_1 e_1 + kC e_1$$

$$e_2 = e_1 + k e_1$$

$$e_2 = (1+k) e_1 \quad \text{--- (1)}$$

$k = \frac{C_1}{C} = \text{RATIO BETWEEN AIR CAPACITANCE & INSULATOR CAPACITANCE}$

AT POINT (b)

$$I_3 = I_2 + I_{P2}$$

$$ce_3 = ce_2 + c_1 (e_1 + e_2)$$

$$ce_3 = ce_2 + \kappa c (e_1 + e_2)$$

$$e_3 = e_2 + \kappa (e_1 + e_2)$$

$$e_3 = (1+\kappa)e_1 + \kappa (e_1 + (1+\kappa)e_1)$$

$$e_3 = [1+\kappa + \kappa(1+(1+\kappa))] e_1$$

$$e_3 = [1+\kappa + \kappa + \kappa + \kappa^2] e_1$$

$$e_3 = [1+3\kappa+\kappa^2] e_1 \quad - \textcircled{2}$$

$$E_{ph} = e_1 + e_2 + e_3$$

$$E_{ph} = e_1 + (1+\kappa)e_1 + (1+3\kappa+\kappa^2)e_1$$

$$E_{ph} = e_1 [1+(1+\kappa) + 1+3\kappa+\kappa^2]$$

$$E_{ph} = e_1 \left[1 + 1 + \kappa + 1 + 3\kappa + \kappa^2 \right]$$

$$E_{ph} = e_1 \left[3 + 4\kappa + \kappa^2 \right]$$

$$e_1 = \frac{E_{ph}}{3 + 4\kappa + \kappa^2}$$

$$e_2 = (1 + \kappa) e_1$$

$$= (1 + \kappa) \times \frac{E_{ph}}{(3 + 4\kappa + \kappa^2)}$$
$$= \frac{E_{ph} (1 + \kappa)}{3 + 4\kappa + \kappa^2}$$

$$e_3 = (1 + 3\kappa + \kappa^2) e_1$$

$$= (1 + 3\kappa + \kappa^2) \times \frac{E_{ph} (1 + \kappa)}{(3 + 4\kappa + \kappa^2)}$$
$$= \frac{E_{ph} (1 + \kappa) (1 + 3\kappa + \kappa^2)}{(3 + 4\kappa + \kappa^2)}$$

