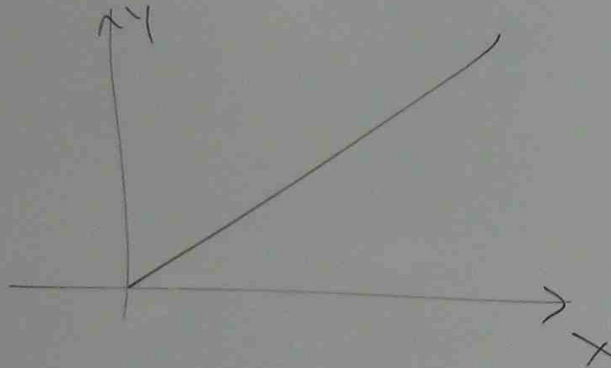


G047 — POWER ENGINEERING MATHEMATICS


LINEAR / NON LINEAR AND EXPONENTIAL FUNCTIONS

LINEAR




LINEAR
FUNCTION

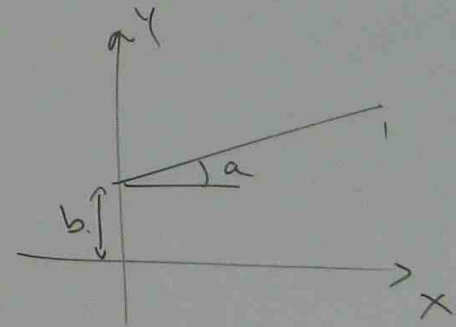VOLTAGE DROP IN TRANSMISSION
LINE IS LINEAR FUNCTION




$$y = ax + b$$

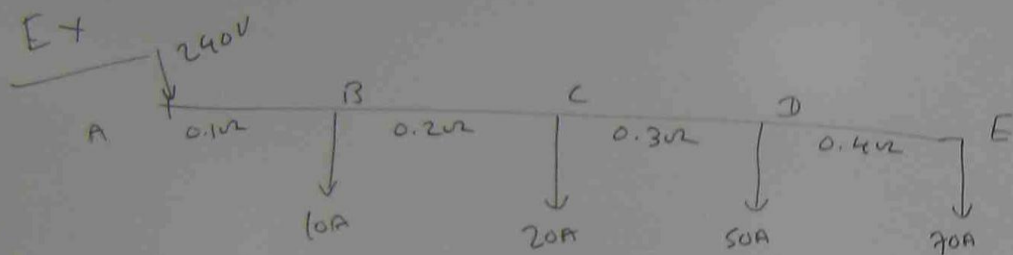MATHEMATICAL EQUATION
FOR LINEAR FUNCTION



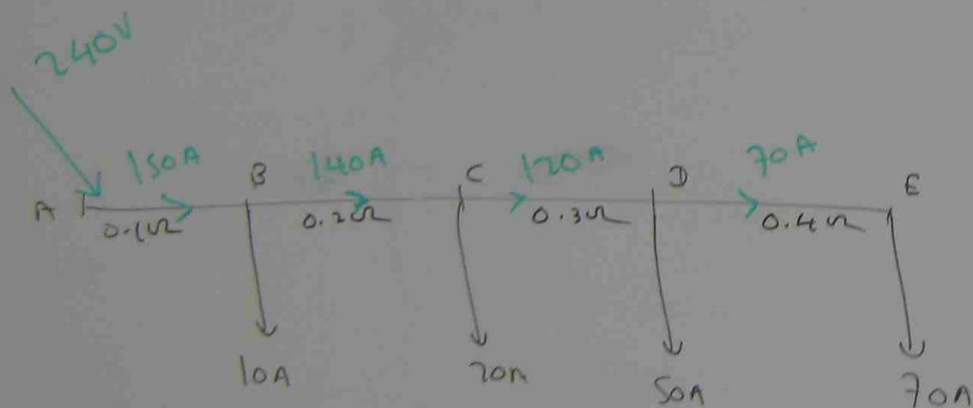FIND THE LOAD VOLTAGES AT A, B, C, D, E
FOR GIVEN POWER LINE.



$$\begin{aligned}
 V_B &= V_A - I_{AB} \times R_{AB} \\
 &= 240 - 150 \times 0.1 \\
 &= 240 - 15 = 225 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_C &= V_B - I_{BC} \times R_{BC} \\
 &= 225 - 140 \times 0.2 \\
 &= 225 - 28 \\
 &= 197 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_D &= V_C - I_{CD} \times R_{CD} \\
 &= 197 - 120 \times 0.3 \\
 &= 197 - 36 \\
 &= 161 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_E &= V_D - I_{DE} \times R_{DE} \\
 &= 161 - 70 \times 0.4 \\
 &= 161 - 28 \\
 &= 133 \text{ V}
 \end{aligned}$$

FIND LINE EFFICIENCY


LINE OUTPUT

$$\text{power} = V_B I_B + V_C I_C + V_D I_D + V_E I_E$$

$$= 225 \times 10 + 197 \times 20 + 161 \times 50 + 133 \times 70$$

$$= 23550 \text{ WATT}$$

$$\text{LINE POWER LOSS} = \sum I^2 R$$

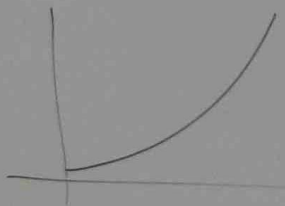


NON LINEAR
FUNCTION

$$\begin{aligned} \text{TOTAL POWER LOSS} &= I_{AB}^2 R_{AB} + I_{BC}^2 R_{BC} + I_{CD}^2 R_{CD} \\ &\quad + I_{DE}^2 R_{DE} \end{aligned}$$

$$\begin{aligned} \text{TOTAL POWER LOSS} &= (150)^2 \times 0.1 + (140)^2 \times 0.2 + (120)^2 \times 0.3 + (70)^2 \times 0.4 \\ &= 12450 \text{ WATT} \end{aligned}$$

$$\begin{aligned} \text{TOTAL INPUT POWER} &= \text{TOTAL POWER LOSS} + \text{LINE OUTPUT POWER} \\ &= 12450 + 23550 \\ &= 36000 \text{ WATT} \end{aligned}$$




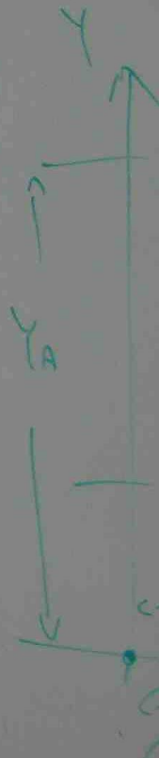
$$\begin{aligned} \text{LINE EFFICIENCY} &= \frac{\text{LINE OUTPUT POWER}}{\text{LINE INPUT POWER}} \times 100 \\ &= \frac{23550}{36000} \times 100 \\ &= 65.4\% \end{aligned}$$



2 x 0.4





APPLICATION OF LINEAR FUNCTION IN POWER SYSTEM DESIGN

< LOAD CENTRE >

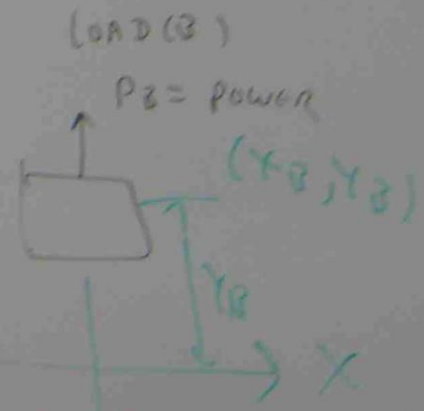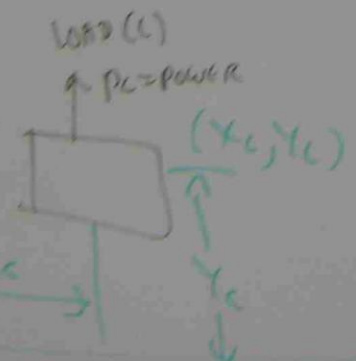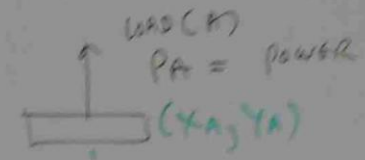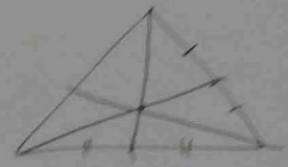

LINEAR FUNCTION IN DESIGN

CENTRE >

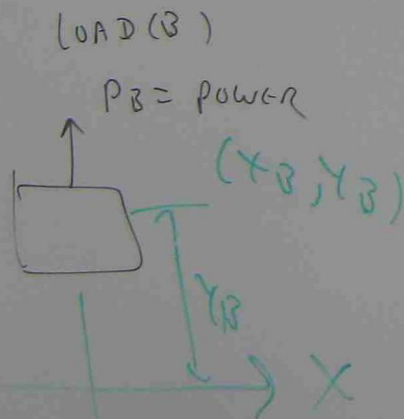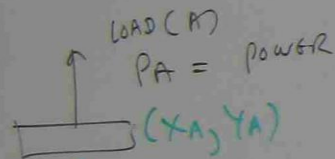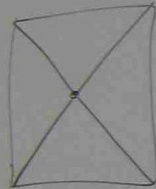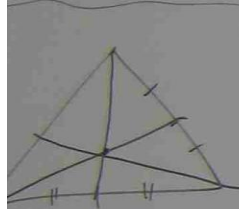

LOCATION of POWER STATION

$$\bar{X} = \frac{P_A x_A + P_B x_B + P_C x_C}{P_A + P_B + P_C}$$


$$\bar{Y} = \frac{P_A y_A + P_B y_B + P_C y_C}{P_A + P_B + P_C}$$

Ex 3 TOWNS (A, B, C) ARE LOCATED AS FOLLOWS.
 DETERMINE THE MOST SUITABLE PLACE TO LOCATE THE
 ELECTRICAL POWER STATION TO SUPPLY THOSE TOWNS.

A - 1000 MW (3, 5) km,

B - 300 MW (7, 10) km,

C - 400 MW (4, 17) km

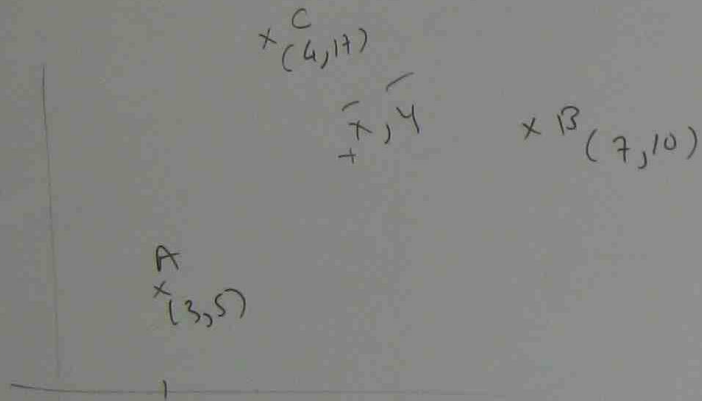

$$\bar{Y} = \frac{P_A Y_A + P_B Y_B + P_C Y_C}{P_A + P_B + P_C}$$

$$= \frac{1000 \times 5 + 300 \times 10 + 400 \times 17}{1000 + 300 + 400}$$




$$= 8.7 \text{ km}$$

$$\bar{X} = \frac{P_A X_A + P_B X_B + P_C X_C}{P_A + P_B + P_C}$$


$$= \frac{1000 \times 3 + 300 \times 7 + 400 \times 4}{1000 + 300 + 400} = 3.94 \text{ km}$$

EXPONENTIAL FUNCTION

$$y = e^x \quad e = 2.718$$

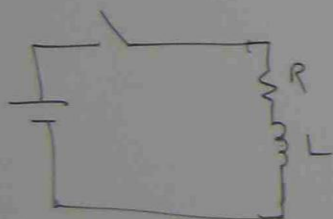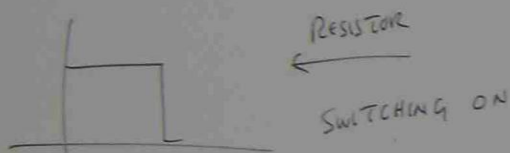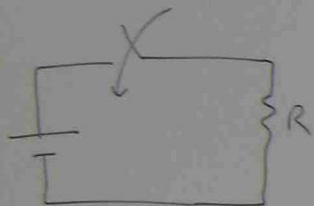

R = RESISTANCE
L = INDUCTANCE
t = TIME

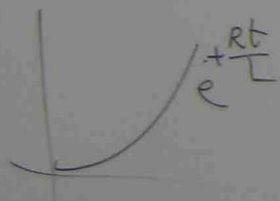


SWITCH ON



SWITCH OFF

TRANSIENT CIRCUITS

SHORT CIRCUIT CURRENT

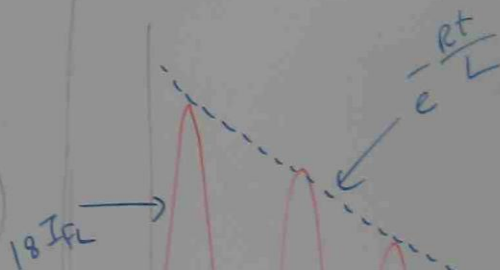

4 → 5 I_{FL}


NORMAL
FULL WAVE
CURRENT

SHORT
CIRCUIT
CURRENT

TRANSIENT SHORT
CIRCUIT CURRENT



STEADY
STATE
SHORT
CIRCUIT
CURRENT

γ = PROPAGATION
CONSTANT

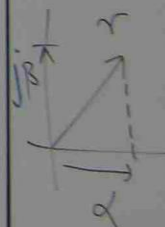

HORIZONTAL
COMPONENT OF
PROPAGATION CONSTANT

$$\frac{V_1}{V_2} =$$

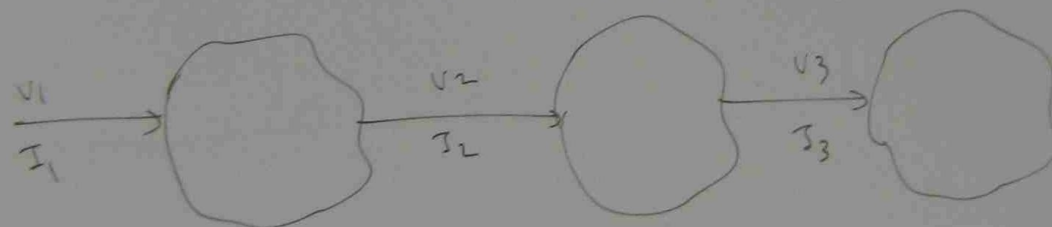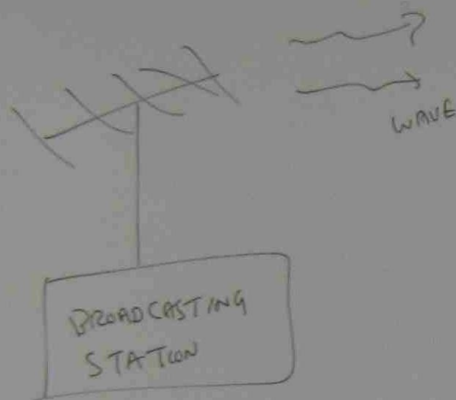

WAVE PROPAGATION

γ = PROPAGATION CONSTANT



HORIZONTAL COMPONENT OF PROPAGATION CONSTANT

$$\frac{V_1}{V_2} = e^{\gamma_1} \quad \frac{V_2}{V_3} = e^{\gamma_2} \quad \frac{V_3}{V_4} = e^{\gamma_3}$$

$j\beta$ = VERTICAL COMPONENT OF PROPAGATION CONSTANT

$$\gamma = \alpha + j\beta$$

$$\gamma_1 = \alpha_1 + j\beta_1$$

4-5 Hz

NORMAL FULL WAVE CURRENT

STEADY STATE SHORT CIRCUIT CURRENT

$$(a) \ 5 \angle 36.8 = 5 \cos 36.8 + j 5 \sin 36.8 = 5 \times 0.8 + j 5 \times 0.6 = 4 + j3$$

$$(b) \ 5 \angle -36.8 = 5 \cos(-36.8) + j 5 \sin(-36.8) = 5 \times 0.8 - j 5 \times 0.6 = 4 - j3$$

$$(c) \ 5 \angle -120 = 5 \cos(-120) + j 5 \sin(-120) = 5(-0.5) + j 5(-0.866) \\ = -2.5 - j 4.33$$

$$(d) \ 5 \angle 250 = 5 \cos(250) + j 5 \sin(250) = 5(-0.342) + j 5(-0.939) \\ = -1.71 - j 4.695$$