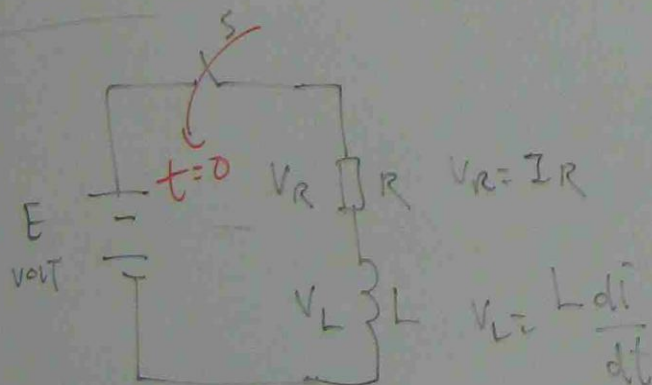


# DIFFERENTIAL EQUATION & APPLICATION OF DIFFERENTIAL EQUATION IN ELECTRICAL CIRCUIT CALCULATION

$$\frac{dy}{dt} + 3y = 4 \quad (\text{FIRST ORDER})$$

$$\frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 4 = 0 \quad (\text{SECOND ORDER})$$

RL CIRCUIT



$$E = V_R + V_L$$

$$E = IR + L \frac{di}{dt}$$

$$i = I \left( 1 - e^{-\frac{R}{L}t} \right)$$

VALUE OF CURRENT  
AT  $t=0$

SWITCHING  
ON  $t=0$

$$i = I \left( 1 - e^{-\frac{R}{L}t} \right)$$




$$i = I \left( 1 - e^{-\frac{R}{L}t} \right)$$

$$= I - I e^{-\frac{R}{L}t}$$

VARIABLE  
CONSTANT WITH  $e$  FUNCTION

SWITCHING OFF

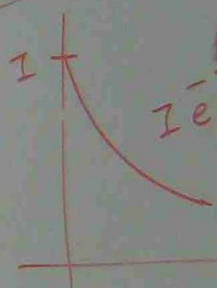

GENERALIZE


FOR ANY

THE EQU

$L$

$i(t)$

SWITCHING OFF

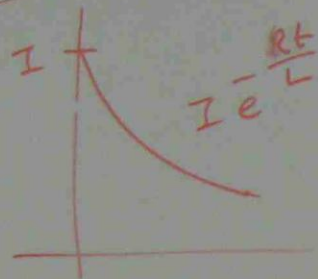

GENERALIZED FORMAT  
FOR ANSWER OF  
THE EQUATION

$$L \frac{di}{dt} + IR = E$$

$$i(t) = I_p + A e^{-\frac{t}{\tau}}$$


$$\tau = \frac{L}{R}$$

$$-e^{-\frac{Rt}{L}}$$

$$-I e^{-\frac{Rt}{L}}$$

VARIABLE  
WITH  $e$  FUNCTION

ph

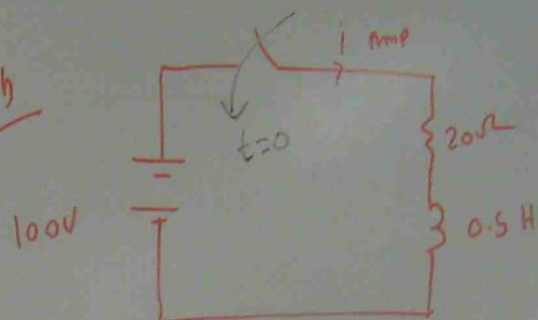

FOR THE CIRCUIT SHOWN ABOVE, DETERMINE THE FOLLOWING VALUES  
AFTER THE SWITCH HAS BEEN CLOSED.

- THE FINAL VALUE OF CURRENT
- THE INITIAL VALUE OF CURRENT
- TIME CONSTANT OF THE CIRCUIT
- THE EQUATION OF THE CURRENT
- THE INITIAL RATE OF CHANGE OF CURRENT.

(a) SWITCH CLOSED, INDUCTOR IS SHORT CIRCUITED

$$I_{\text{FINAL}} = \frac{V}{R} = \frac{100}{20} = 5 \text{ A}$$

$$(b) I_{\text{INITIAL}} = 0$$



(c) TIME CONSTANT  $(\tau) = \frac{L}{R} = \frac{0.5}{20} = 0.025 \text{ sec} = 25 \text{ ms}$

(d)  $E = IR + L \frac{dI}{dt}$

$100 = 20I + 0.5 \frac{dI}{dt}$  CIRCUIT EQUATION

$i(t) = \underset{\substack{\uparrow \\ \text{FINAL CURRENT}}}{I} (1 - e^{-t/\tau})$

$= 5 (1 - e^{-\frac{t}{0.025}})$

$i(t) = 5 (1 - e^{-40t})$

(e)  $\frac{di(t)}{dt} = \frac{d}{dt} 5 (1 - e^{-40t})$

$= \frac{d}{dt} 5 - \frac{d}{dt} 5 e^{-40t}$


$= 0 - 5 \times (-40) e^{-40t}$

RATE OF CHANGE OF CURRENT  $= 200 e^{-40t} \text{ A/s}$

ph  
+  
200V  
DE TO  
CURR  
SWIT  
ASSU  
HAD  
INITI  
(OR)

WHEN SWITCH

(2)

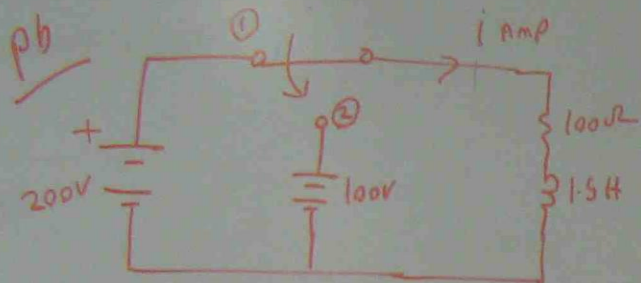

$$E = IR + L \frac{dI}{dt}$$

$$i(t) = I_p + A e^{-t/\tau}$$

↑ FINAL

$$\tau = \frac{L}{R} = \frac{1.5}{100} = 0.015$$

$$I_p = 1 \text{ Amp} \leftarrow \text{FINAL}$$

$$i(t) = 1 + A e^{-\frac{t}{0.015}}$$

DETERMINE THE EQUATION OF THE CURRENT IN ABOVE FIGURE AFTER SWITCHING TO POSITION ②.

ASSUME THAT STEADY STATE CURRENT HAD BEEN ATTAINED IN POSITION ①

INITIAL CURRENT  $I(0) = \frac{200V}{100\Omega} = 2 \text{ Amp.}$

(OR)  $i(t) \Big|_{t=0} = 2 \text{ Amp}$  (NOT STEADY STATE)

WHEN TIME ( $t=0$ ), THE INITIAL CURRENT IS 2 Amp.

$$i(t) \Big|_{t=0} = 2$$

$$e^{-\frac{0}{0.015}}$$

$$2 = 1 + A e^0$$

$$2 = 1 + A$$


$$2 = 1 + A$$

$$\therefore A = 2 - 1 = 1$$

$$\therefore i(t) = 1 + 1 e^{-\frac{t}{0.015}} = 1 + e^{-\frac{t}{0.015}}$$

SWITCH AT

②

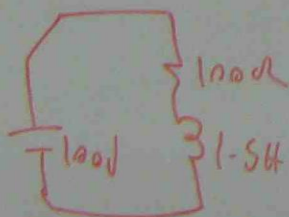

FINAL CURRENT  $= \frac{100}{100} = 1 \text{ Amp.}$


↑  
STEADY STATE  
CONSTANT  
VALUE

## RESPONSE OF RL AND RC CIRCUITS TO AC VOLTAGE

$$e = E_m \sin(\omega t + \phi)$$

$$V_R = iR$$

$$V_L = L \frac{di}{dt}$$

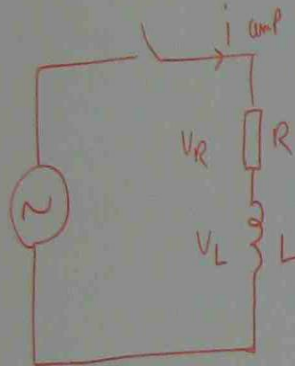

$$V_R + V_L = e$$

$$iR + L \frac{di}{dt} = E_m \sin(\omega t + \phi)$$

$$i = i_c + i_p$$

↑  
COMPLEMENTARY  
COMPONENT


↑  
PARTICULAR  
COMPONENT

GENERAL SOLUTION

$$i = A e^{-\frac{t}{\tau}} + I_p \sin(\omega t + \phi - \phi)$$

pb

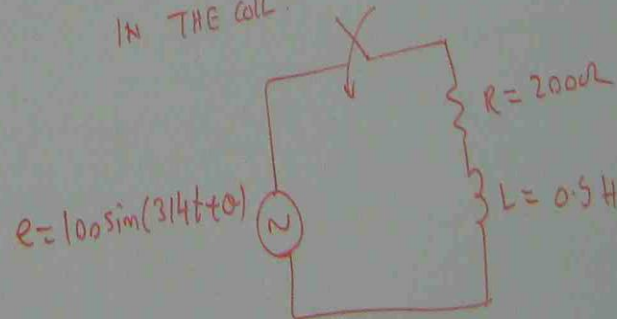AN E.M.F  $e = 100 \sin(314t + \phi)$  VOLT IS APPLIED TO A COIL OF RESISTANCE  $200\Omega$  AND INDUCTANCE  $0.5$  HENRY WHEN  $\phi$  IS  $30^\circ$ . DETERMINE THE EQUATION OF THE RESULTING CURRENT IN THE COIL.



$$\begin{aligned} X_L &= \omega L \\ &= 314 \times 0.5 \\ &= 157 \end{aligned}$$

$$Z = R + jX_L = 200 + j157$$


$$\phi = \tan^{-1} \frac{157}{200} = 38^\circ$$



GENERAL SOLUTION

$$i = A e^{-\frac{t}{\tau}} + I_p \sin(\omega t + \alpha - \phi)$$

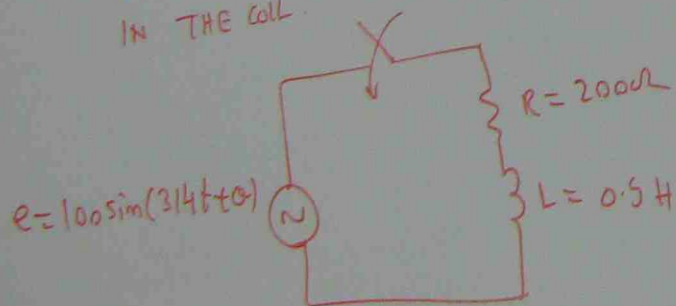pb) An E.M.F  $e = 100 \sin(314t + \alpha)$  VOLT IS APPLIED TO A COIL OF RESISTANCE  $200 \Omega$  AND INDUCTANCE  $0.5$  HENRY WHEN  $\alpha$  IS  $30^\circ$ . DETERMINE THE EQUATION OF THE RESULTING CURRENT IN THE COIL.



$$\begin{aligned} X_L &= \omega L \\ &= 314 \times 0.5 \\ &= 157 \end{aligned}$$

$$Z = R + jX_L = 200 + j157$$

$$\phi = \tan^{-1} \frac{157}{200} = 38.13^\circ$$

$$i = A e^{-\frac{t}{\tau}} + I_p \sin(\omega t + \alpha - \phi)$$

$$\tau = \frac{L}{R} = \frac{0.5}{200} = 0.0025 = 2.5 \text{ ms}$$

$$\theta - \phi = 30 - 38.13 = -8.13$$

$$i = A e^{-\frac{t}{2.5 \times 10^{-3}}} + I_p \sin(314t - 8.13)$$

$$I_p = \frac{E}{Z} = \frac{100}{\sqrt{R^2 + X_L^2}} = \frac{100}{\sqrt{200^2 + 157^2}} = 0.392$$

$$i = A e^{-400t} + 0.392 \sin(314t - 8.13)$$

$$t=0 \rightarrow i=0$$

$$0 = A e^{-400 \times 0} + 0.392 \sin(314 \times 0 - 8.13)$$

$$0 = A e^0 + 0.392 \sin(-8.13)$$


$$0 = A - 0.392 \sin 8.13$$

$$A = 0.0556$$

$$i = 0.0556 e^{-400t} + 0.392 \sin(314t - 8.13)$$

0.3932

RC circuit

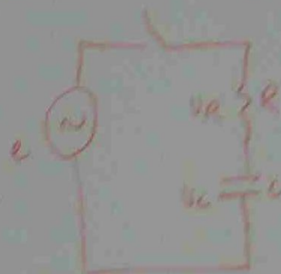

$$e = E_m \sin(\omega t + \phi)$$

$$V_R = iR$$

$$V_C = \frac{1}{C} \int i dt$$

$$V_R + V_C = e$$

$$iR + \frac{1}{C} \int i dt = e = E_m \sin(\omega t + \phi)$$

$$\frac{d}{dt}(iR) + \frac{d}{dt} \left[ \frac{1}{C} \int i dt \right] = \frac{d}{dt} [E_m \sin(\omega t + \phi)]$$


$$R \frac{di}{dt} + \frac{1}{C} \int i dt = E_m \omega \cos(\omega t + \phi)$$

$$R \frac{di}{dt} + \frac{1}{C} i = E_m \omega \cos(\omega t + \phi)$$
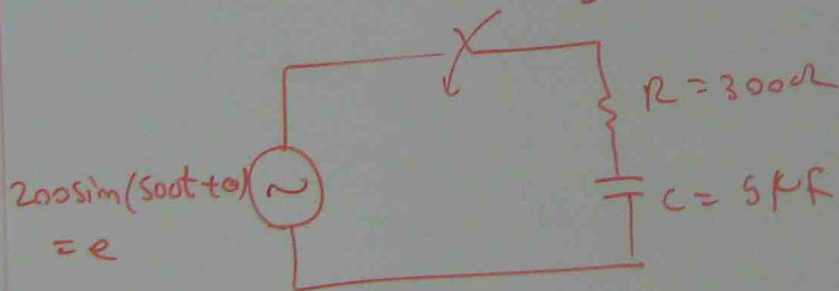
### THE GENERAL SOLUTION

$$\hat{i} = A e^{-t/\tau} + I_p \sin(\omega t + \theta - \phi)$$

pb AN E.M.F OF  $e = 200 \sin(500t + \theta)$  VOLT IS APPLIED TO AN RC CIRCUIT WHERE  $R = 300 \Omega$  AND  $C = 5 \mu F$  WHEN  $\theta$  IS  $60^\circ$ . DETERMINE THE EQUATION OF THE CIRCUIT IF THE INITIAL CHARGE ON THE CAPACITOR IS 250 MICRO COLUMBS.



$$\hat{i} = A e^{-t/\tau} + I_p \sin(\omega t + \theta - \phi)$$

$$\tau = R \cdot C = 300 \times 5 \times 10^{-6} = 1.5 \times 10^{-3}$$

$$\theta = 60^\circ$$



$$\begin{aligned}
 Z &= R - jX_C = 300 - j \frac{1}{2\pi fC} \\
 &= 300 - j \frac{1}{500 \times 5 \times 10^{-6}} \\
 &= 300 - j400 \, \Omega \\
 &= \sqrt{300^2 + 400^2} \angle -\tan^{-1} \frac{400}{300}
 \end{aligned}$$

$$Z = 500 \angle -53.1^\circ \, \Omega$$

$$\phi = -53.1^\circ$$

$$I_p = \frac{E}{Z} = \frac{200}{500} = 0.4$$

$$i = A e^{-\frac{t}{1.5 \times 10^{-3}}} + 0.4 \sin(500t + 60 - (-53.1))$$

$$i = A e^{-666.7t} + 0.4 \sin(500t + 113.1) \text{ Amp}$$

$$t=0 \rightarrow i(0) = A e^{-666.7 \times 0} + 0.4 \sin(500 \times 0 + 113.1)$$

$$i(0) = A + 0.4 \sin 113.1 \quad \text{--- (1)}$$

$$q = \int i dt = 250 \, \mu C$$

INITIAL

$$iR + \frac{1}{C} \int i dt = e$$

$$iR + \frac{1}{C} \times q = e$$

$$i \times 300 + \frac{250 \times 10^{-6}}{5 \times 10^{-6}} = 200 \sin 60$$

$$i \times 300 + 50 = 200 \sin 60$$

$$i(0) = \frac{200 \sin 60 - 50}{300} = 0.4107$$

①

$$0.4107 = A + 0.4 \sin 113.1$$

$$A = 0.0433$$

$$i(t) = 0.0433 e^{-666.7t} + 0.4 \sin(500t + 113.1)$$